

Switching Circuits and Logic Design
Prof. Indranil Sengupta
Department of Computer Science and Engineering
Indian institute of Technology, Kharagpur

Lecture – 17
Minimization Using Karnaugh Maps (Part- II)

So, in the last lecture if we recall we are talked about the concept of Karnaugh map method of minimizing a function and through examples we showed how we can handle or minimize 3 variable functions.

(Refer Slide Time: 00:35)

Introduction

- We now show how the K-map can be extended to four variables.
 - It will be a 4 x 4 cell array.
- The basic concept of labeling the variables remains the same:
 - Adjacent cells differ in the value of a single variable.
 - Top-bottom and left-right cells are also considered adjacent.
 - The four corner cells are considered adjacent to each other.

$2^4 = 16$

IIT KHARAGPUR | NPTEL ONLINE CERTIFICATION COURSES | Switching Circuits & Logic Design

(Refer Slide Time: 00:36)

4-variable Karnaugh Map

AB \ CD	00	01	11	10
00				
01				
11				
10				

Handwritten annotations:

- Horizontal arrow from 01 to 00 in the 01 row.
- Vertical arrow from 11 to 01 in the 01 column.
- Binary strings: 0101 and 0111 with a horizontal line underneath.
- Binary strings: 0110 and 1110 with a horizontal line underneath.
- Function: $f(A, B, C, D)$

So, in this lecture we shall extend our discussion to handle 4 variable functions so, we shall be extending our discussion to 4 variables. Now, recall we mentioned that it is not so easy to extend Karnaugh map concept to larger number of variables. Of course, in books we will see that the authors have said that you can do it up to 6, but up to 4 is easy, 5 becomes difficult, 6 becomes quite difficult beyond 6 is impossible. So, whatever examples I showed here will be only up to 4.

So, if you have 4 variables then how many minterms are possible 2 to power 4 equal to 16 . So, first thing is that you need to have 16 cells and they will be organized in a 4 by 4 cell array. So, there will be 4 rows and 4 columns, 4 rows and 4 columns. The basic concept of labeling remains the same, you will see that the way you label the rows and columns it will always be ensured the neighboring cells will always be differing in a single variable.

This will and also there will be a neighborhood relationship between the right and left and also top and bottom. Top-bottom and left-right adjacency will also be provided or ensured. Not only that, you will see that the four corner cells will be considered adjacent to each other. Why? We shall see just a little later.


Let us consider a 4 variable Karnaugh map like this; this is just an extension of a 3 variable map where we consider a function with 4 variables let us say A, B, C, D where in this diagram I am showing AB along the rows and CD along the columns. And just like a

3 variable function the way we label the columns in the gray code order 0 0 0 1 1 1 1 0 here we are doing the same thing for both rows and columns 0 0 0 1 1 1 1 0. Why?

You consider any two cells let us say these two cells the first cell corresponds to 0 1 0 1 0 1 0 1, the second cell to corresponds to 0 1 1 1 0 1 1 1. We check they defer in a single variable this last position sorry second last position 1 0 1 it defers in the second last position right.

Now, you take any pair of cells vertically take this and this the upper cell corresponds to 0 1 1 0, lower cells corresponds to 1 1 1 0. You see this are all adjacent only the first variables is different, the other 3 are the same right.

(Refer Slide Time: 03:54)

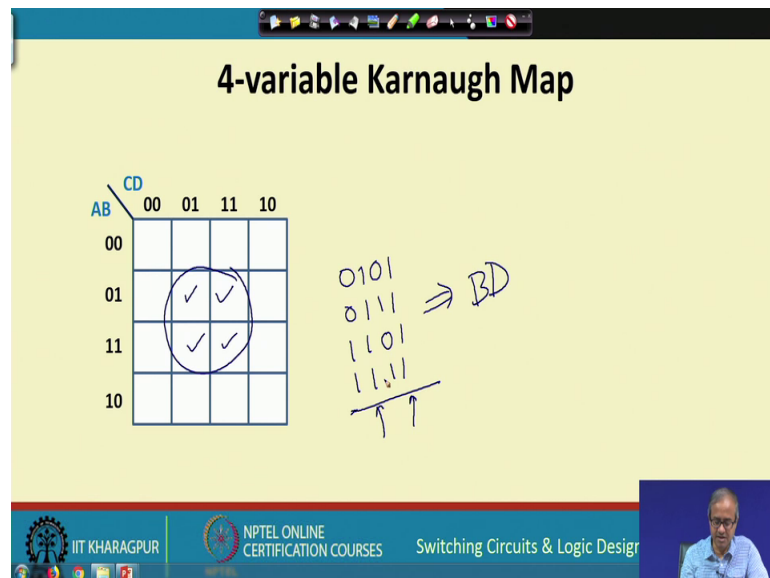

The same thing you can extend to a cube of size 4, let us consider these 4 this 4 corresponds to I am just writing on the binary 0 1 0 1 then 0 1 1 1 then 1 1 0 1 and 1 1 1 1.

So, you see here the second and fourth variables are the same 1 this is also 1, but the first and the third variables which is A or C they are changing. So, if you form a cube out of this 4 this will be corresponding to B and D minimized form will be only BD, A and C will they will be cancelled out.


(Refer Slide Time: 04:47)

4-variable Karnaugh Map


CD	00	01	11	10
AB	00			1
01				1
11				1
10				1

0010
0110
1110
1010

CD'



IIT KHARAGPUR NPTEL ONLINE CERTIFICATION COURSES Switching Circuits & Logic Design



Similar, is the case if you take a cube vertically like this they will correspond to 0 0 1 0 0 1 1 0 1 1 0 1 0 1 0. So, again this 1 0 is common the first two are changing they will be cancelled out. So, C and D will remain it will be CD' right.


(Refer Slide Time: 05:16)

4-variable Karnaugh Map


CD	00	01	11	10
AB	00			✓
01				
11				
10	✓			✓

0000
0010
1000
1010

⇒ $B'D'$



IIT KHARAGPUR NPTEL ONLINE CERTIFICATION COURSES Switching Circuits & Logic Design




Now, I talked about the 4 corner cells right suppose, there are 2 minterms in the 4 corner cells they are also considered neighbors. So, I can make a big cube of size 4 using the 4 corner cells which is showed like this, how let us write down and see.

This cells corresponds 0 0 0 0, this cell corresponds to 0 0 1 0. The left one corresponds to 1 0 0 0 and this one is 1 0 1 0, you see last variable is always 0, second variable is also 0, the first and third are changing.


So, same way first and third will cancel out and this will be equivalent to B bar D bar right. So, the same concept you can make cubes as you wish.

(Refer Slide Time: 06:08)

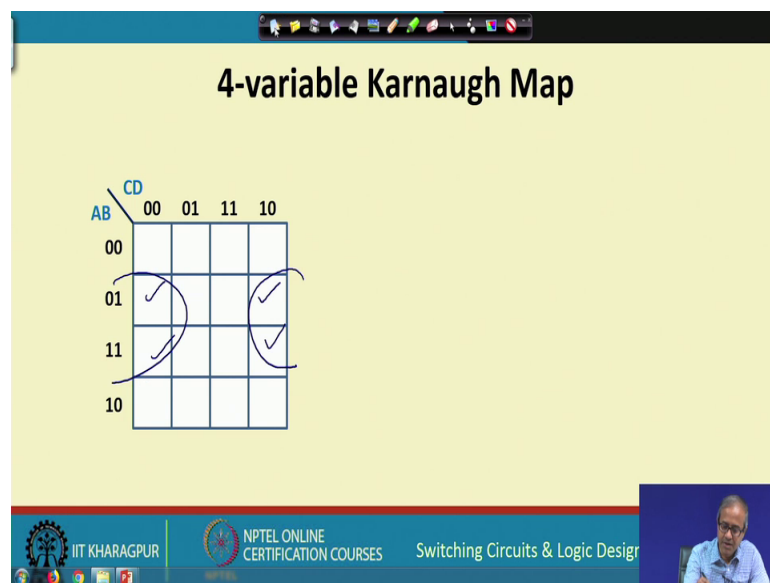

If you have this, this and this, this you can makes cube like this right.

(Refer Slide Time: 06:15)

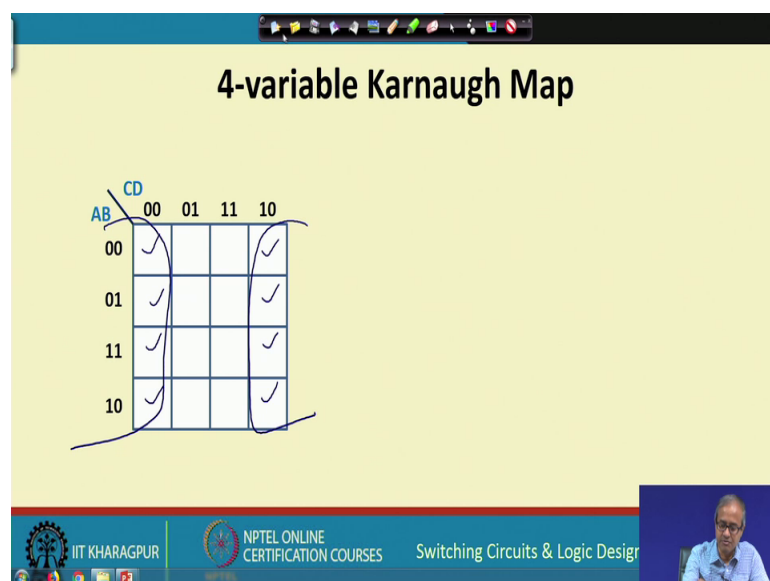

If you have this 4 and also this 4, then you can make a cube of size 8 like this; same concept you can use right.

(Refer Slide Time: 06:28)

The slide is titled "4-variable Karnaugh Map". It contains two 4x4 grids. The left grid is empty, with the top row labeled 'CD' (00, 01, 11, 10) and the left column labeled 'AB' (00, 01, 11, 10). The right grid is filled with decimal values from 0 to 15, arranged in a 4x4 grid. The top row is labeled 'CD' (00, 01, 11, 10) and the left column is labeled 'AB' (00, 01, 11, 10). The values are: Row 00: 0, 1, 3, 2; Row 01: 4, 5, 7, 6; Row 11: 12, 13, 15, 14; Row 10: 8, 9, 11, 10. At the bottom of the slide, there are logos for IIT KHARAGPUR, NPTEL ONLINE CERTIFICATION COURSES, and the text "Switching Circuits & Logic Design". A small video inset of a person is visible in the bottom right corner.

So, this is the same Karnaugh map where I am showing the cells labeled by the decimal equivalent of AB CD values. So, numbers are made like this 0 1 2 3 4 5 6 7 and you skip to the last one 8 9 10 11 then 12 13 14 15. This is because this 11 is coming first before 10 right similarly in the columns these are reverse because 11 is coming first then 10 all right.

Now, let us take some examples.

(Refer Slide Time: 07:01)

Example 1

	CD			
	00	01	11	10
AB				
00			1	
01	1	1		1
11				1
10				1

$A'B'C' + B'CD + B'CD$

Let us take function like this where you can see that there are 6 true minterms. Now, if I follow a rule let us try to get the cubes constructed, this can be 1 cube I cannot make it any larger. This is 1 cube, these two 1's they are adjacent this is 1 cube. Now, one thing you see this is also a cube I am showing it dotted, this and this you can also make a cube out of this.

But this is not required because I have already covered all the true minterms with this 3 cubes so, I do not require these this cube any more ok. This will be my best solution, minimum number of cubes which is covering all of them. But if I consider this dotted cube also it will not make it any minimum, it will be even one more. But here what is the solution, this 2 cubes 0 1 which is A bar B and 00 01 D cancels out, C is 0 C bar then let us consider is one vertically

So, 01 and 11 A cancels out B is 1 it is B and it is 10. So, C D bar and the last one this top and bottom 00 and 10 A cancels out B is 0 B bar and 11 CD. This is the minimized form of this function right, let us take another example.

(Refer Slide Time: 09:05)

Example 2

	CD				
		00	01	11	10
AB		00	01	11	10
		1	1	1	1
		1	1	1	1
		1	1	1	1
		1	1	1	1
		1	1	1	1

$CD' + A'D' + BC'D$

Let us take an example like this well some of the largest cubes immediately see is one is this cube of size 4 that is another size 4 you can see which will be these two plus these two.

You see you can take these two separately, but this will not be the biggest one because you can also take these two, this will be the bigger one and these two 1's are still remaining. You can of course, take a cube like this, but again this will be left out, but instead you take a cube like this and this will cover everything I do not need any further cube.

So, what will be the expression this column this A and B are cancelling out, AB will not be there 1 0. So, just CD' plus these two these two 4 00 01 which is A' and 00 and 10 C cancels out D' and lastly you have this two 01 11 means B and 01 $C'D$, this is your minimized form.

So, once you do it like this you cannot minimize it any further just you think that a I mentioned tell me tell it once more.

(Refer Slide Time: 10:41)

Example 2

AB \ CD	00	01	11	10
00	1			1
01	1	1		1
11		1		1
10				1

IIT KHARAGPUR | NPTEL ONLINE CERTIFICATION COURSES | Switching Circuits & Logic Design

Suppose we had constructed a cube like this, we had constructed this cube also like this biggest possible, but suppose I also have constructed a cube like this then this cube will also this 1 is also remaining left out.

So, I I will also have to include it so you see I need one extra cube here and this cube this cube these two this is redundant because this cells that this cube is covering, these cells are already covered by some other cubes. So, a particular cell a true minterm need to be covered by at least one of the cubes.

So, if I have 1 cube whose cells are already covered by some other cubes I do not need to include that cube at all you can leave it out; that is why I can remove this cube from my map and only 1 2 and 3 this cubes will do ok. This is what we are done.


Take another example.

(Refer Slide Time: 11:58)

Example 3

	CD				
		00	01	11	10
AB					
00		1			1
01			1	1	
11			1	1	
10		1			1

$BD + B'D'$

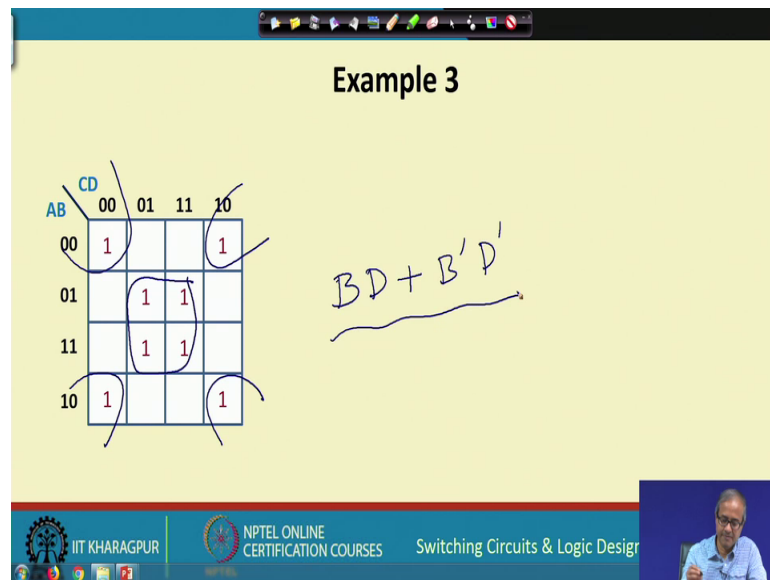

IIT KHARAGPUR | NPTEL ONLINE CERTIFICATION COURSES | Switching Circuits & Logic Design

This is the very nice example regular example which shows four 1's in the corners. This is very easy, the middle four will be 1 cube and the four corners will be (Refer Time: 12:14), this will be the another cube.


So, what will be the expression? The four middle one will be 0 1 1 1 it will B 0 1 1 1 again D or the four corner 1's 0 0 1 0 B bar 0 0 1 0 D bar. This will be function BD or B bar D bar right.

(Refer Slide Time: 12:48)

Example 4

	CD				
		00	01	11	10
AB					
00			1	1	
01		1	1		
11		1	1		
10			1	1	

$c'D + BC' + B'D$

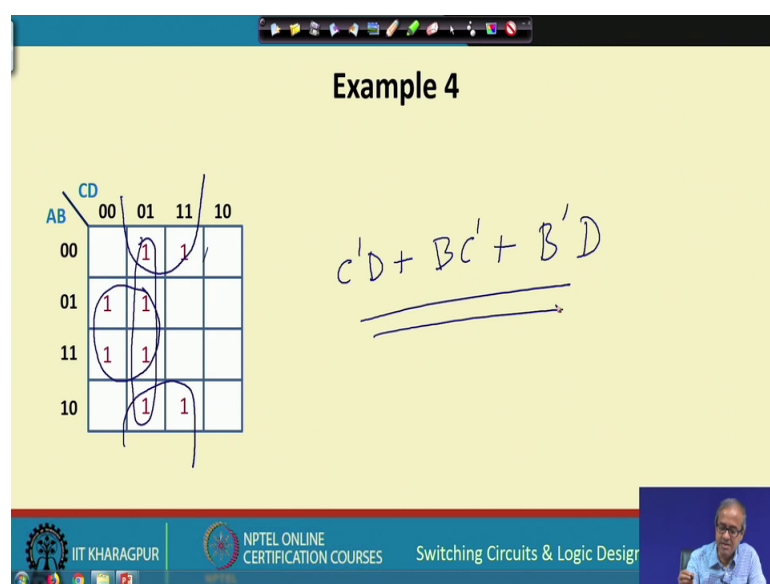

IIT KHARAGPUR | NPTEL ONLINE CERTIFICATION COURSES | Switching Circuits & Logic Design

Let us look at some more examples. Take an example like this.

So, here again let us try to make the cube as large as possible like one I can see this four I can make, this four I can make, these four I can make. Now, you see these two 1's are have been left out.

(Refer Slide Time: 13:02)

Example 5

	CD	00	01	11	10
AB	00			1	
01	1	1	1		
11		1	1	1	
10		1			

$$A'Bc' + A'CD + AC'D + ABC$$

$$+ \underline{\underline{BD}}$$

X

So, I can make these two together or I can make the cube of four these two plus these two right, this is the biggest.

So, this will be my best cover. So, if we do it this way this long one A B are cancelled it will C bar D plus this q 1 D left; it will be B and C bar. And these two 00 and 10 it will be B bar and 0 1 1 1 C cancels out D this will be the minimized form right.

(Refer Slide Time: 14:05)

Example 4

AB \ CD	00	01	11	10
00		1		1
01	1	1		
11	1	1		
10		1		1

IIT KHARAGPUR | NPTEL ONLINE CERTIFICATION COURSES | Switching Circuits & Logic Design

So, when we choose these cells it should be judicious, you should not select something like this I select this, I select this then I select this, this is not minimum because you are then we get bigger I can these two and these two make it cube of size 4 right.

So, I will try here I shall try to make it as large as possible the cubes ok. This is another cyclic kind of a structure like you see I can find these 4 cubes, but the other four 1's are isolatives. So, I can have 1 cube with these two, 1 cube with these two, 1 cube with these two, 1 cube with these two. So, what does this mean see let me again go back.

So, our first premise or assumption was that we try to make the cube as large as possible ok. The second thing I mentioned that if I find that a cube is covering some cells which are already covered by some other cubes then drop or delete this cube, I do not need this ok. You see in this example the first I am saying is that this is the largest cube, but the other four well I cannot leave them out because each of them having at least 1 or 1 which is not covered by any one; these are not covered by any other cube.


So, when we include this four you see that the bigger cube is no longer required because the four 1's in the bigger cube they are already covered by this 4 smaller cubes. So, even though this is the bigger one I do not need this. So, my cover here is look like this because this middle one will be redundant is not required.

So, what will the expression the left one will be $A \bar{B}$ and $00 \ 01 \ C \bar{D}$. This top one $00 \ 01$ will be $A \bar{B} \ C \bar{D}$ plus these two will be $11 \ 10$ will be $A \text{ and } 01$ is $C \bar{D}$ plus this two 11 is AB and $11 \ 10$ is C ok.

This will be my minimized form, but if you also include this middle one then you also include another term which is redundant not required; it will be actually be B and D BD , BD is not required at all. So, you unnecessary you are using five terms.

These four are sufficient, this will covering BD automatically right, this something you should remember.

(Refer Slide Time: 17:19)

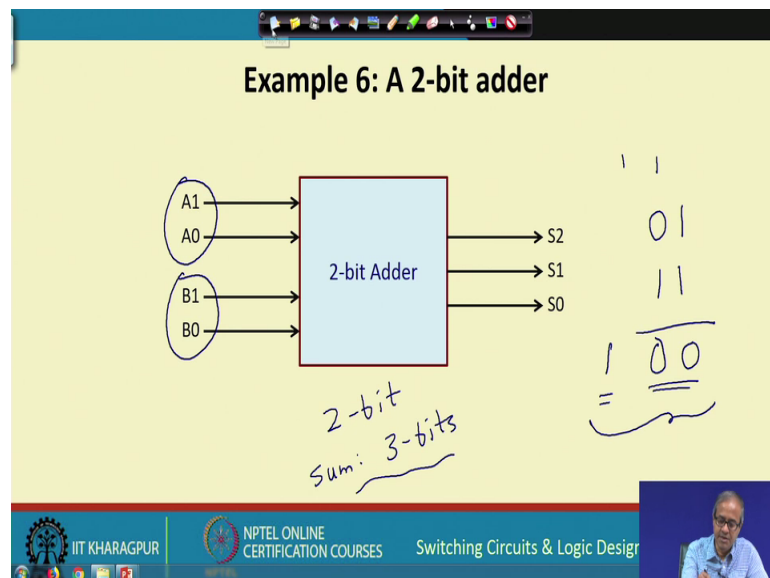

Ok here let us take a slightly bigger and a more realistic example suppose we are trying to design a 2-bit adder. So, how is this 2-bit adder it takes 2 numbers this numbers are 2 bits each and adds them up. Let us say one of the number is $0 \ 1$ and the other number is $1 \ 1$.

So, if I add them up $1 \ 1$ is 0 with the carry of $1 \ 1 \ 0 \ 1$ is 0 with the carry of 1 . So, the final carry out will be 1 . So, my sum will be actually 3-bits 2-bits and the possible carry out. So, the sum will be 3-bits

So, whenever we add two 2 bit numbers your sum will become 2 bits one more right because there is a chance of 1 carry bit coming out right. Let us look into these examples and see how you can use the Karnaugh map for minimization.

(Refer Slide Time: 18:39)

Example: 2-bit adder – S2

A1	A0	B1	B0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Karnaugh Map for S2:

A1A0 \ B1B0	00	01	11	10
00				
01			1	
11		1	1	1
10			1	1

Block Diagram: A 2-bit adder with inputs A1, A0, B1, B0 and outputs S2, S1, S0.

$2^4 = 16$

ONLINE EDUCATION COURSES Switching Circuits & Logic Design

Well here, first let us look at the truth table this is the truth table of the adder.

So, just recall in the adder I have said that there will be 4 inputs; the first number A 1 A 0 then B 1 and B 0. And there will be 3 outputs S 2 S 1 and S0. Let us see in the truth table I am showing this 4 A 1 A 0 B 1 B 0 are the inputs and there are 3 outputs S 2 S 1 S 0.

So, for 4 input there will be 2 to the power 4 or 16 minterms, which I am showing in 4 rows 0 0 0 0 0 0 1 up to 1 1 1 1 there are 16. So, if we just add you think in terms of equivalent decimal it will be easier 0 0 plus 0 0 means 0 plus 0 is 0. So, sum is 0 0 0 0 plus 1 sum is 1 is 0 0 1 0 plus 2 1 0 is 2 sum is 2 2 is 0 1 0 0 plus 3 sum is 3.

So, 0 1 1 is 3 0 1 is 1 1 plus 0 is 1 0 0 1 1 plus 1 is 2 0 1 0 is 2 1 plus 2 is 3 0 1 1 1 plus 3 is 4 1 0 0 2 plus 0 is 2 0 1 0 2 plus 1 is 3 2 plus 4 is 4 1 0 0 2 plus 3 is 5 1 0 1 3 plus 0 is 3 3 plus 1 is 4 3 plus 2 is 5 and 3 plus 3 is 6 1 1 0.

(Refer Slide Time: 21:01)

A1	A0	B1	B0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	1
1	1	1	1	1	1	0

Example: 2-bit adder – S2

		B1B0			
A1A0		00	01	11	10
00					
01				1	
11		1	1	1	1
10			1	1	

Now, in this Karnaugh map we are showing the Karnaugh map corresponding to the output is 2; that means, this column of the total. So, how many 1's are there 1 2 3 4 5 and 6?

So, you see there are 6 1's correspond to you see first one correspond to 0 1 1 1. So, 0 1 1 1 this one, second one is 1 0 1 0 1 0 this one, third one is 1 0 1 1 1 0 1 1 this one, fourth one is 1 1 0 1 1 0 1 1 1 0 and finally, 1 1 1 1 right. So, these are there.

(Refer Slide Time: 21:59)

A1	A0	B1	B0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Example: 2-bit adder – S2

		B1B0			
A1A0		00	01	11	10
00					
01				1	
11		1	1	1	1
10			1	1	

$S2 = A1 \cdot B1 + A1A0B0 + A0B1B0$

Now, if you try to form the cubes in this case you see that you will be getting large cube here, you will be getting smaller cube here and another smaller cube here that is all; you cannot minimize any further.

So, what will be the expression for S2? Your S2 will be this bigger one A0 cancels out only A1A1 and 11 on 10 on B1A1 and B1 or let us take this one first 11 which is A1A0 and 0111; that means, it will B0; B0 or this one 0111 is A0A011B1B0. This is the function minimized form, this is the expression for S2 right ok.

(Refer Slide Time: 23:10)

A1	A0	B1	B0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	✓1	0
0	0	1	1	0	✓1	1
0	1	0	0	0	0	1
0	1	0	1	0	✓1	0
0	1	1	0	0	✓1	1
0	1	1	1	1	0	0
1	0	0	0	0	✓1	0
1	0	0	1	0	✓1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	✓1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	✓1	0

Example: 2-bit adder - S1

		B1B0			
		00	01	11	10
A1A0	00			1	1
	01	1			1
	11	1		1	
	10	1	1		

$$S1 = A_1'A_0B_1 + A_1'B_1B_0 + A_1B_1B_0' + A_1A_0'B_1' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0$$

Let us now, see what will be S1? Similar is the case for S1, if we look at S1 there are 12345678 1's and if you check the 8 1's are distributed like this.

So, you see here the cubes will be like this you cannot minimize it too much. These two, then these two and here these two, these two and these two are isolated 1's you cannot group them together; they will be isolated. So, there will be 12345 and 6, 6 cubes.

So, the expression for S1 will be slightly bigger; look at this one it will be A1A0A1A0 and 1110B1 sorry not A1A0A1 dash A0 dash A1 dash A0 dash B1 ok, plus let us look at this one 00 and 01 A1 dash. This will be A1 dash 10 B1 B0 plus let us look at this one 11 10 is A1A100 B1 dash B0 dash.

And this one 10 A1A0 dash and 00 01 is B1 dash B1 dash and the two isolated 1's this one will be 01 01; which means A1 dash A0 B1 dash B0 and the last one will be 1 1 1

1 which is $A_1 A_0 B_1 B_0$. So, I see this expression is little more complex, but it is the minimum form you cannot minimize it any further all right.

(Refer Slide Time: 25:42)

A1	A0	B1	B0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Example: 2-bit adder - S0

	B1B0			
A1A0	00	01	11	10
00		1	1	
01	1			1
11	1			1
10		1	1	

$S_0 = A_0 B_0' + A_0' B_0$

Now, finally, the expression for S0 the last one here you see for S0 there are 1 2 3 4 5 6 7 8 1's which are disturbed like this. Now, these are pretty nicely distributed because you can very nicely form the cubes like this 1 cube will be this, this four 1's another cube will be this these four 1's.

So, S0 you can write this two will be A_0 and 00 and 10 and B_0 bar plus this two 00 and 10 A_0 bar 01 11 B_0 . This is the minimum form right. So, in this way you can minimize the expressions this the minimum form.

So, we have seen that in case of this 2-bit adder so, how we can create or represent the 3 output functions S2 S1 S0 in the Karnaugh map and then use the cubes to minimize the sum of products expression. So, we have seen I mean how to minimize this functions earlier for 3 variables and now for 4 variables.

So, Karnaugh map is very easy to use, very simple graphically if you wants you can find the cubes from there directly you can write down the minimized form that is the big advantage.

So, with this we come to the end of this lecture. In the next lecture we shall be looking at a few other issues and the concepts regarding the Karnaugh map methods of

minimization; before we move on to some other technique, which is more systematic which can be used for larger functions for minimizing switching expressions.

Thank you.