

Power Electronics
Prof. B.G. Fernandes
Department of Electrical Engineering
Indian Institute of Technology, Bombay
Lecture - 15

In our last lecture we discussed the principle of operation of fully controlled bridge in which all the 4 switching elements are thyristors. We derived the expression for an average value of output voltage and it is given by $2 V_m \sin \alpha$. This expression is valid if the current is continuous. I will repeat; this expression is valid only if the load current is continuous.

Let, we found that for α in between 0 to $\pi/2$, average value of the output voltage is positive, current is unidirectional. So, power supplied by the source to the load is positive. So, we call it as conversion, AC to DC converter and for α greater than $\pi/2$, we found that average value of the output voltage becomes negative, current is again unidirectional which is positive. So, power supplied by this source, by the source is negative.


In other words, source is absorbing power. Load is supplying power back to the source. So, we call this as inverter or inversion, power inversion. Average value of the output voltage can be negative for α greater than $\pi/2$, only if the load is of RLE type. It is possible only for RLE type of load.

Motor will act like a generator only if torque developed by it is negative. In other words, torque is given by $K \omega$, either I_A has to reverse or e has to reverse, polarities of e should reverse. Only by changing or only by increasing α greater than $\pi/2$, machine will not act like a generator. So, for the machine to act like a generator I have to either interchange armature terminals or I have to interchange the field terminals.

Let me tell you 1 thing, convertor fed a DC machine reversing the armature terminals or field terminals using the mechanical contactors does not make a sense, because both are inductive circuits. Field circuit is highly inductive, even armature has a finite inductance. Using mechanical contactors I have to or to interchange the 2 terminals I have to use the mechanical contactors. So, momentarily we are breaking an inductive circuit.

So, what happens if I break an inductive circuit? Arching will take place. That is what I said, using mechanical contactors in a convertor fed machine, to for the machine to act like a generator, does not make much sense. So, is there a solution? Is there a way out? There is, we will see.


(Refer Slide Time: 4:50)

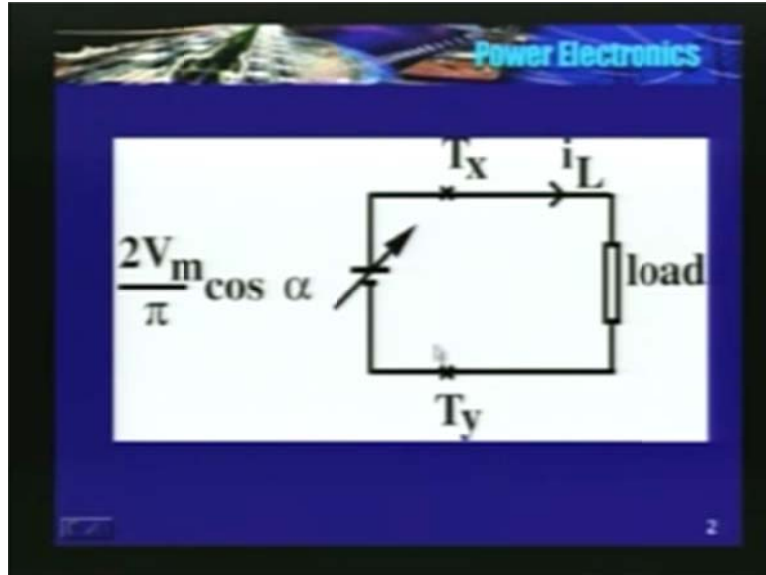

Say, this is the equivalent circuit of the fully controlled bridge, $\frac{2V_m}{\pi} \cos \alpha$. So, magnitude of this voltage varies as a function of alpha. There are at any given time, 2 thyristors are conducting T_x and T_y , so either T_1, T_2 or T_3, T_4 and here is a load. So, applied voltage to the load is equal to the output voltage of the bridge minus 2 device drops, remember, 2 device drops.

So, if you assume that in the device, assume that the device are ideal that is average value of the output voltage applied to the load is $\frac{2V_m}{\pi} \cos \alpha$ itself. Otherwise, it is this value minus twice or 2 device drops is the voltage applied to the load.


(Refer Slide Time: 5:54)

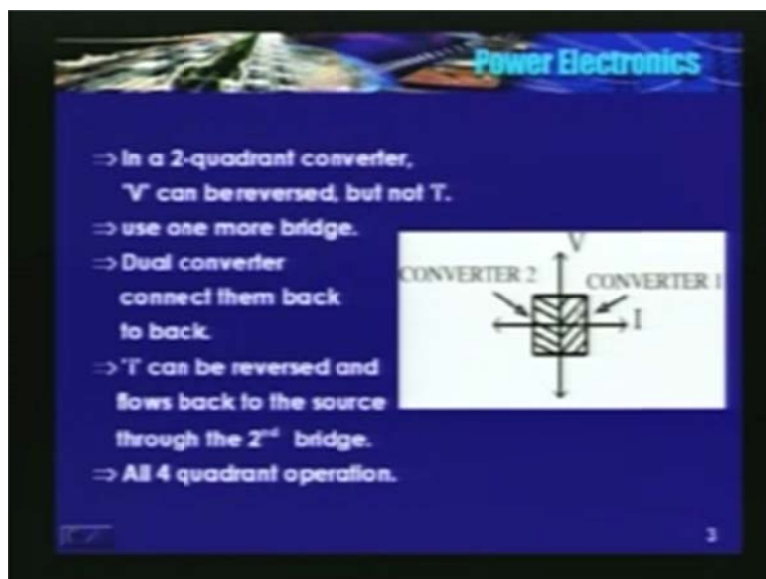

So, we use only 1 convertor, wherein, voltage is reversing but the current cannot reverse. So, we will use 1 more convertor connected back to back. In the sense, current can flow back to the source **with the** through the second convertor. So, there are 2 convertors, hence, the name dual convertor. So, if you see a convertor 1, voltage can be positive or negative, current is always positive. So, operation is in quadrant 1 or quadrant 4.

Now, I have connected another bridge in a reverse fashion, wherein, current can flow back to the source. Now, negative current **corresponds to** with respect to the bridge 1, the direction of current flowing in convertor 2 is in the opposite direction. So, voltage again can be positive or negative. So, operation is either in the quadrant 2 or in quadrant 3. So, in other words, using a dual convertor I can have all 4 quadrant operations, all 4 quadrant operation is possible.


(Refer Slide Time: 7:38)

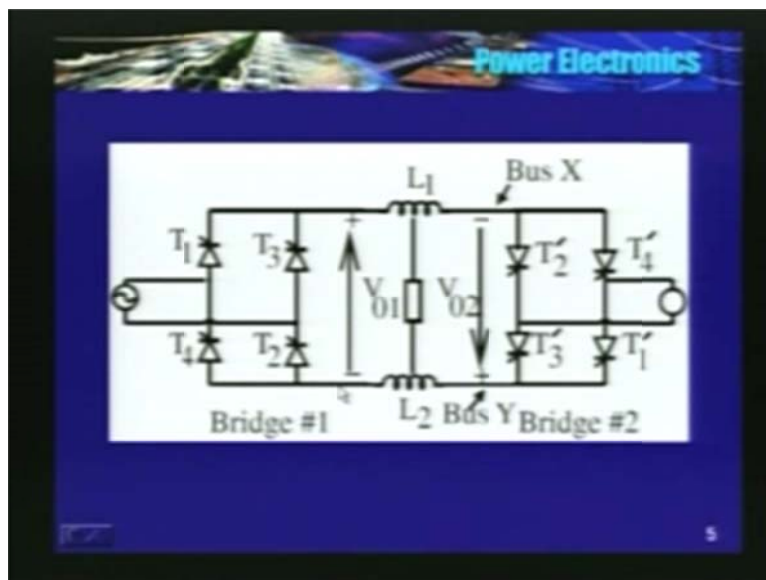

So, here is a circuit, power circuit; single phase bridge, T₁ to T₄. I have another bridge here, T₁ dash to T₄ dash, connected in the reverse fashion. 2 bridges are interconnected by 2 inductors and in the center I am connecting a load. The purpose of this inductor, I will tell you sometime later.

What is the principle of operation of this bridge? Assume that both the convertors are working and let alpha be the trigger angle or alpha₁ be the trigger angle for the bridge 1. Now, what is the relationship between alpha₁ and the trigger angle of the bridge 2? So, let it be alpha₂.

(Refer Slide Time: 8:41)

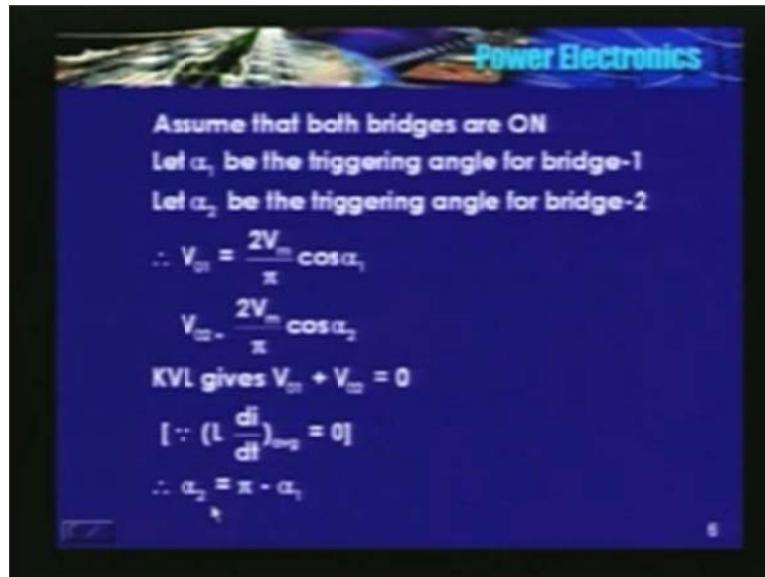


We know if the current is continuous, average value of the output voltage of the bridge 1 is given by $2 V_m$ by π into $\cos \alpha_1$. Similarly, for the second bridge it is $2 V_m$ by π into $\cos \alpha_2$. Remember, both the bridges are being supplied by the same source. What does the KVL gives? Though there is an inductor, average value across this, average value of the voltage across inductor is 0.

So, I have taken V_{01} with respect to bus y, with respect to this V_{01} , potential of this bus is V_{01} and see here, I have connected this region in a opposite direction, back to back. So, T_1 dash is here, T_1 is here, T_4 dash, T_3 dash and T_2 dash and output voltage of this bridge is V_{02} with respect to this bus X, so V_{02} .

So, the KVL gives V_{01} plus V_{02} should be 0 because voltage across this plus this is 0. So, it gives the relationship between α_2 and α_1 is this. The trigger angle for the bridge 2 is π minus α_1 .

(Refer Slide Time: 10:28)

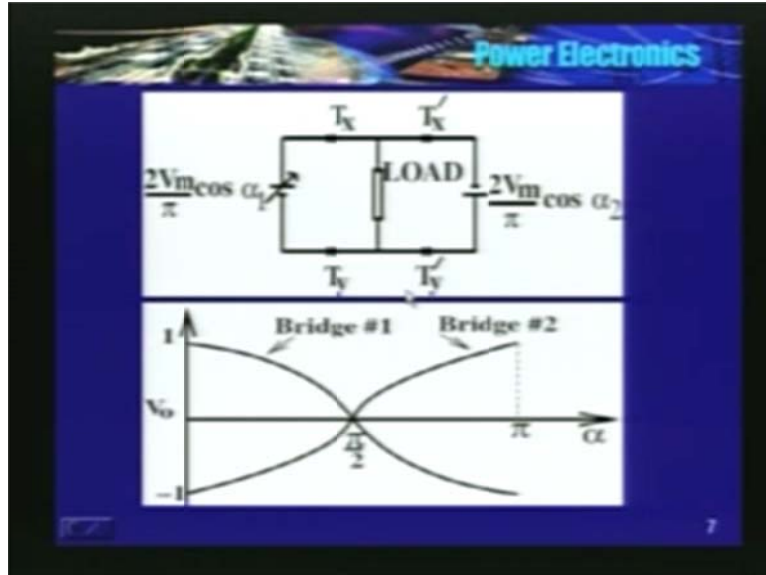

So, here is the equivalent circuit; $\frac{2V_m}{\pi} \cos \alpha_1$, output voltage of the bridge 1, 2 devices are conducting at a time. $\frac{2V_m}{\pi} \cos \alpha_2$ is the output voltage of the bridge 2, again 2 devices are conducting here. I have not shown the inductor, the load is connected in between. Now, if I plot the output voltage, average value of the output voltage with α_1 and α_2 , how do they look like?


For the bridge 1 it is given by this equation, 0 at π by 2 . This waveform you drew, you have already drawn for single phase fully controlled bridge. So, α_1 is 0 , α_2 is π . So, magnitude is the same, it is minus 1 . So, I am calling $\frac{V_m}{\pi}$ by π is equal to 1 or 1 per unit. So similarly, therefore, $\frac{V_m}{\pi}$ by π minus $\frac{V_m}{\pi}$ by π is minus 1 per unit. At π by 2 , both are 0 s and this is the variation. How does the ...

(Refer Slide Time: 11:59)

Power Electronics

V_{o1} is the voltage w.r.t Bus Y and
 V_{o2} is the voltage w.r.t Bus X.
 Assume that ' L_1 ' is combined
 with ' L_2 '.
 $V_L = V_{o1} + V_{o2}$
 If both are w.r.t Bus Y, then
 $V_L = V_{o1} - V_{o2}$
 \Rightarrow Average voltage across $L = 0$,
 but not instantaneous voltage.
 \Rightarrow If both bridges are ON, there
 will be a circulating current.

(Refer Slide Time: 12:13)

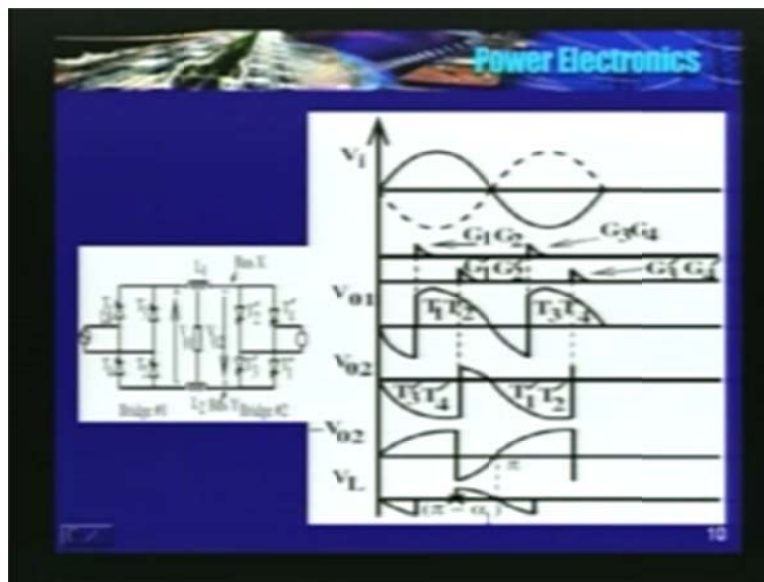

Let us draw the waveforms, output waveforms. How do they look like? At α_1 which is less than $\pi/2$, G_1 and G_2 or T_1 and T_2 are triggered. G_1 and G_2 are the gates of T_1 and T_2 and at $\pi + \alpha_1$, T_3 and T_4 are triggered for the bridge 1. At ωt is equal to α , **alpha is a trigger**, α_1 is a trigger angle for bridge 1 and α_2 is the trigger angle for bridge 2. So, G_1 and G_2 are triggered in the positive half at α and $\pi + \alpha_1$, G_3 and G_4 or T_3 and T_4 are triggered.

So, **how does the** how does V_{o1} look like? So, till T_1 and T_2 are triggered, T_3 and T_4 were conducting, remember. Recall whatever, all these things we have studied. So, prior to T_1 and T_2 ,

T_3 and T_4 were conducting. So, output voltage is negative because from 0 to π , V_{BA} is negative, this is V_{BA} and this is V_{AB} . V_{BA} is negative, so V_{O1} is negative.

At α_1 , T_1 and T_2 are triggered. Now, the output voltage is V_{AB} . So instantaneously, there is a jump. Now, Output voltage is V_{AB} , it will continue till π plus α_1 . At that instant, T_3 and T_4 are triggered. This waveform we have already studied. How does V_{O2} look like? Now, just reverse this bridge, in the sense, take this minus and plus, α_2 is the trigger angle for the bridge 2 and the relationship between α_1 and α_2 is α_2 is equal to π minus α_1 .

So, somewhere at this instant, G_1 dash and G_2 dash, the gates corresponds to T_1 dash and T_2 dash are triggered. Remember, in the positive half, T_1 and T_2 are triggered. Similarly, here I am triggering, similarly here, T_1 dash and T_2 dash are triggered in the positive half, somewhere here. So, till T_1 dash and T_2 dash are triggered, T_3 dash and T_4 dash were carrying current or they were conducting. So, output voltage is negative, T_3 T_4 .

So, the moment T_1 dash and T_2 dash are triggered, output voltage which is again V_{AB} , it is positive. So, average value, the magnitude of average value that is V_0 , magnitude of V_{O1} is equal to magnitude of V_{O2} , if you find. Average value of V_{O1} may be equal to average value of V_{O2} and let us see what is the voltage waveform appearing across L_1 or what is the voltage waveform that comes across L_1 .

Now, V_{O1} is this. Now, I will reverse the polarities of V_{O2} . Say this is V_{O2} , now minus V_{O2} looks like this. Same waveform, I am inverting it. Same waveform has to be inverted. So now, with respect to the bus y or this bus, this is V_{O1} and with respect to this bus, potential of this is minus V_{O2} . What do you observe from these 2 waveforms? I said, mod of V_{O1} may be equal to mod of V_{O2} . But then instantaneous value of V_{O1} is not equal to instantaneous value of V_{O2} , remember. Mod of V_{O1} maybe equal to mod of V_{O2} but then instantaneous value of V_{O1} is not equal to the instantaneous value of V_{O2} .

So therefore, there is a potential difference between the voltage across the ... So, there will be a current flowing from bridge 1 to bridge 2 or in other words, there is a circulating current, hence the name the circulating current type convertor. So, in a dual convertor, if both the convertors are carrying current simultaneously, they are known as circulating current type. If only 1 bridge is carrying current it is known as non circulating type because only 1 bridge is carrying current, only 1 bridge is supplying current to the load. Second bridge is completely off. So, no current can flow through the second bridge. Hence, the name non circulating type.

So, V_L is nothing but V_{O1} minus of V_{O2} , so here is this. You will find that average value of this waveform is 0. Now, let us see how a dual convertor can be used to control a DC motor? Now, this load will connect a DC machine here. Let us assume that machine is running stably at some constant speed, ω and corresponding E_B , back EMF is of the order of 90 volts, let us assume. If back EMF is 90 volts, applied voltage, output voltage of the bridge should be higher than 90 volts only then the current will flow. In other words, output voltage of the bridge should be equal to $I_a r_a$ plus E_B .

So, let us assume that V_{01} , the magnitude of V_{01} is equal to the magnitude of V_{02} is around 100 volts. The output voltage of the bridge is 100 volts, the magnitudes and E_B is of the order of 90 volts. So, let us assume that corresponding trigger angle for the bridge 1 is around 45 degrees. So therefore, α_2 is π minus 45 is equal to 135.

So I will repeat; α_1 is 45, α_2 is 135, corresponding V_0 , magnitude of V_{01} is 100, magnitude of V_{02} is again 100 and E_B is 90, it is possible. Now, I want to feed the, you want to use the regenerative braking and reverse the speed of operation. Initially, motor was running, as a machine was operating as a motor and was rotating in the clock wise direction. Torque is positive, speed is also positive.

(Refer Slide Time: 21:18)

Power Electronics

- $E_b > V_0$
- i_a reverses and flows through bridge 2.
- $\Rightarrow E_b$ is still +ve, i_a is -ve. $\therefore T$ is -ve.
- \Rightarrow Regenerative braking
- \Rightarrow M/c is still running in clockwise.
- \Rightarrow II quadrant operation.
- $\Rightarrow \omega \downarrow$.
- \Rightarrow continue $\uparrow \alpha_1$ towards 90° ($\alpha_2 \downarrow$ towards 90°).
- At $\alpha_1 = 90^\circ$, $V_{01} = 0$ (ω approaches 0)
- $\uparrow \alpha_1$ beyond 90° ($\alpha_2 \downarrow$ below 90°).
- Bridge 1 \rightarrow Inverter and
- Bridge 2 \rightarrow Converter.
- Bridge 2 supplies power, m/c starts rotating in -ve direction.
- E_b reverses, \therefore III quadrant (reverse motoring)

12

Quadrant 1 operation, torque is positive, positive torque and direction of rotation, omega is again clock wise.

(Refer Slide Time: 21:33)

Power Electronics

Assume that the motor is rotating at ' ω ' in the clockwise direction and corresponding $E_b = 90V$ & $V_m = -V_m = 95V$.
 Let $\alpha_1 = 45^\circ$ ($\alpha_2 = 135^\circ$)
 V_m is supplying power to the m/c.
 I_a is positive which means T is also +ve.
 Now, $\uparrow \alpha_1$ to 60° or ($\downarrow \alpha_2$ to 120°) $\rightarrow V_m \downarrow$
 E_b cannot change instantaneously
 $\therefore \omega$ cannot change instantaneously.

11

Now, what I will do is, increase α_1 towards 90 slowly.

(Refer Slide Time: 21:40)

Power Electronics


The diagram shows a bridge rectifier circuit with thyristors T_1, T_2, T_3, T_4 and diodes D_1, D_2, D_3, D_4 . The waveforms for V_i , V_{o1} , V_{o2} , and V_L are plotted. V_i is a sine wave. V_{o1} and V_{o2} are half-wave rectified sine waves. V_L is the load voltage. The firing angle α_1 is indicated.

10

So, V_{o1} becomes less than E_B . When I am increasing α_1 towards 90, simultaneously I have to do or I have to decrease **alpha of** α_2 of the bridge 2. So, I am increasing α_1 towards 90. Similarly, α_2 is decreased towards 90 of bridge 2. Now, you will find that V_{o1} is less than E_B . So, if the terminal voltage is less than the back emf, now, **current can** the direction of current can reverse.

So now, initially, if the current was entering terminal A of armature, now it will leave the terminal A. How does it will flow? Now, it will flow through the bridge 2.

(Refer Slide Time: 22:57)

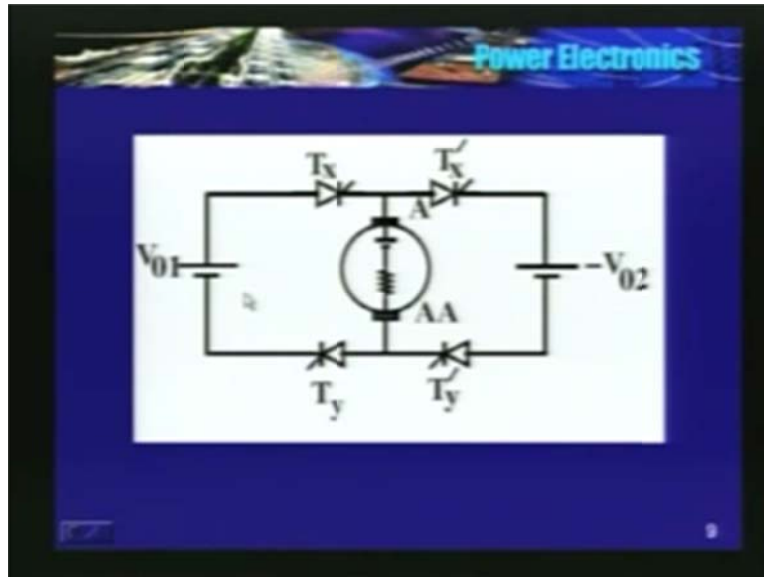

See, in this direction. Initially, the current was flowing in this fashion. Current was flowing in this direction, this was 100 volts, 90, E_B was 90. Magnitude of V_{02} is also 100. See, I have made it, now I will reverse the terminals here. Now, I have reduced V_{01} by increasing α_1 towards 90.

So, V_{01} has reduced or V_{01} is less than E_B . Now, current can leave this terminal. So, it can flow through T_x back to source. So, this is the path. If this operation is known as the motoring, this is the regenerating action or motor is acting like a generator, feeding energy back to the source. Machine is feeding power back to the source, there is no mechanical input, speed falls.

As the speed falls, I am also reducing V_{01} or in other words, α_1 is approaching towards 90 degrees, α_2 is also approaching towards 90 degrees. Speed is falling, assume that speed is approaching 0, at that time V_{01} has also approached 0 and V_{02} has also approached 0, corresponding α_1 is and α_2 , both are approximately 90 degrees.

Now, continue to increase α_1 above 90, what will happen? This will, V_{01} will change polarities. Now, this will become minus, V_{02} will become plus. Now, initially quadrant 1 then we went to quadrant 2 operation because speed was, though it was falling, speed was still in the same direction. Direction of rotation is the same, still in the clockwise direction. Torque has reverse because initially current enter the polarity A sorry current will enter terminal A. Now, current is leaving terminal A, torque is negative. So, we are in the quadrant 2 operation.

Power is been feed back to the source through the second bridge. Current is flowing back to the source through the second bridge, regenerative braking. So, ω falls, continuity increase

towards 90 degrees. At α_1 is equal to 90, V_1 is also 0. ω approaches 0, increase α_1 beyond 90 degrees, α_2 below 90 degrees.

Now, bridge 1 is acting like an inverter and bridge 2 is acting like a convertor. Now, bridge 2 supplies power to the machine. Now, machine starts rotating in the negative direction. So, quadrant 1, it is known as forward motoring, quadrant 3 is known as the reverse motoring. Direction of rotation is opposite.

Now, increase **alpha** α_1 towards 180 degrees, therefore, α_2 decreases towards 0. So, average value of the output voltage increases. Both the magnitudes are increasing. So, the speed is also increasing. At steady state, machine is running in the reverse direction at some ω . Now, if you want to do again regenerative braking, follow the same steps. The operation goes to quadrant 4.

So, this is the principal of the operation of dual convertor fed DC motor. Enough of theory, now let see, let us solve 1 or 2 problem in convertor fed DC motor.

(Refer Slide Time: 28:17)

Problem 1.1
 Armature current $I_a = 30 \text{ A}$
 EMF constant = 0.17 V/rpm
 Assume large L
 I_a is constant in arm. ckt.
 In rectifier operation
 Determine speed & supply P.F.

Sol: Av $V_o = \frac{2V_m}{\pi} \cos \alpha$
 $= \frac{2 \cdot 230 \cdot \sqrt{2}}{\pi} \cos 30$
 $= 179 \text{ V}$
 $\therefore E_b = 179 - 30 \cdot 0.3 = 170 \text{ V}$

A very simple problem; a fully controlled bridge supplying power to a DC machine, R_A is of the order of 0.3 ohms, EMF constant is of the order of 0.17 volts per rpm. Problem says that assume a large inductor is connected in armature circuit. So, the moment you see this sentence, you need to assume that the armature current is continuous. Determine speed and supply power factor. **Alpha is** alpha to the bridge 1 is or trigger angle is maintained at 30 degrees.

What is the average value of the output voltage? Since, the current is continuous, it is $2 V_m$ by π into $\cos \alpha$. I am saying that current is continuous because a large inductor is connected in the armature circuit. So, you can safely assume that current is continuous. So therefore, an average value for alpha is equal to 30 degrees is found to be is 179 volts. So, V minus $I_a r_a$ is equal to E_b .

So, E_B is of the order of 170 volts. Armature current is 30 amperes, it is given. It is constant and you can assume that I_A is constant and ripple free.

(Refer Slide Time: 29:50)

Power Electronics

$$E_b = K\phi\omega$$

∴ EMF constant is in V/rpm

$$\therefore E_b = (K\phi)N$$

$$\therefore N = \frac{170}{0.17} = 1000\text{rpm}$$

motor current is constant
and ripple free $I_m = 30\text{A}$

$$I/p \text{ VA} = 230 * 30 = 6900 \text{VA}$$

$$o/p \text{ Power} = V_o I_m = 179 * 30 \text{W}$$

(Neglecting inverter losses)

$$P.F = \frac{179 * 30}{230 * 30} = 0.77 \text{ lag}$$

14

Now, how do I determine the speed? EMF constant is given. EMF constant is volts per rpm. The magnitude of E_B is known. So, I can calculate speed because volts per rpm into rpm is volts. So, E_B divided by EMF constant will give you the speed. It is found to be 1000 rpm. How do I determine the supply power factor?

There are 2 ways. 1 way is we have assumed that armature current is constant and ripple free. So, I average is 30 amperes. What is the power supplied to the load? V average into I average is power supplied to the bridge or input power to the bridge is V average into I average. So, V_o into I average is the power input. What is the input V_A ? It is V_{rms} into I_{rms} . V_{rms} is same as 230 volts because we are assuming that input is ideal sinusoid, current is constant and ripple free and magnitude is 30 amperes. So, rms value of this current wave form is 30 amperes.

We have found that if the current is constant and ripple free, each device is conducting for pi radians. If each device conducts for pi radians, rms value is same as the average value. So, I_{rms} is also 30 ampere here. So, input V_A is 230 into 30 that is 6900 V_A . That V average into I average is 179 into 30 watts.

So therefore, power factor is power divided by volts ampere, **is of the** so it is found to be 0.77 and it is lagging. Remember, the moment you introduce alpha, power factor lags. Even at alpha is equal to 0, power factor is not unity. Displacement angle may be unity, remember displacement angle is not equal to power factor angle. So, they are different. **Displacement angle may be unity sorry displacement angle is equal to 0**. In other words, displacement factor may be unity but that does not mean that power factor is unity. So, power factor is 0.77 lakh.

What is the second method? Second method I have already discussed. Source current is a square wave for π radians. The fundamental component of the square wave is $\frac{4}{\pi}$ into the magnitude of the current is the peak value. So, rms is divided by $\sqrt{2}$. So, the rms value of the fundamental component of source current is $\frac{2\sqrt{2}}{\pi}$ into the current. **It is of** for this case, it is around 27 amperes.

For a fully controlled bridge, we found that displacement angle is same as trigger angle. In another words, ϕ_1 is a same as α . So, displacement factor **is same** is equal to \cos of the trigger angle. Source current may be a square wave, so therefore, it has fundamental component and it has a higher frequency components. I told you that only the fundamental component of the input voltage and current are responsible for power transfer. The higher frequency component gives rise to $I^2 R$ heating or additional heating in the machine. The other effect will see some time later.

So, power transferred is V_1 into I_1 into $\cos \phi_1$. The fundamental component of the input voltage, the fundamental component of the source current into the \cos of the angle between these 2 wave forms divided by V_{rms} into I_{rms} . Since input voltage is sinusoid, fundamental component is same as the rms component. So, V_1 cancels with V_{rms} .

We found that the fundamental component for the square wave is $\frac{2\sqrt{2}}{\pi}$ into 30 where 30 is magnitude of the current that is flowing in the load which is assumed to be constant and repel free. So, it is of 27 amperes, α is 30.

(Refer Slide Time: 35:47)

Or
RMS value of fundamental component
of source current = $\frac{2\sqrt{2}}{\pi} 30 = 27 \text{ A}$
 $\cos \phi = \cos \alpha$
 $\therefore \text{P.F} = \frac{V_1 \cos \phi}{V_{rms} I_{rms}} = \frac{27 * \cos 30}{30} = 0.779$

So, **cos power factor sorry power factor** is given by **point**, in this case it is found to be 0.779. Both the cases, they have to tally and both the cases, they have to give the same answer. It is up to you to choice which ever method is convenient for you. You do not need to follow the method 2 or method 1, it is up to you.

Part 2 of the problem is regenerating braking is used. But in this case, problem says, polarity of back EMF is reversed. See, I have not discussed this. I all the time I have discussed, reversing the armature terminals or reversing the armature current. Here the problem says, back EMF, polarities of back EMF is reversed. It is possible by reversing the flux. How flux is reversed, let us not discuss, either they would have used a dual convertor or they would have used a contactor, may can break, interchange the field terminals.

So problem says, calculate alpha and power feedback to the source. Armature current is maintained at the previous value, the same current of 30 ampere is flowing.

(Refer Slide Time: 37:15)

1.2. Regeneration: Polarity of back emf is reversed by reversing the 'f'
 Calculate 'α' and power fed back.
 Armature current is maintained at previous value.

Sol: At the instant of polarity reversal
 $E_b = -170 \text{ V}$
 $\therefore V_a = -170 + I_a R_a$
 $= -161 \text{ V} = \frac{2V_m}{\pi} \cos \alpha$
 $\Rightarrow \alpha = 141^\circ$

Power o/p from generator = $170 \times 30 = 5100 \text{ W}$
 Armature copper loss = $0.3 \times 30^2 = 270 \text{ W}$
 \therefore Power fed back = $5100 - 270 = 4800 \text{ W}$
 $= 161 \times 30 = 4800 \text{ W}$

The circuit diagram shows a DC voltage source V_{in} on the left, a resistor R_a at the top, and an armature circuit on the right. The armature circuit consists of an ammeter A and an ammeter AA in series with a back EMF source E_b . The current I_a is indicated flowing clockwise through the circuit.

So, here is the equivalent circuit, mind you, he has interchanged, the operator has interchanged the polarities of back EMF. Simultaneously, he has increased alpha greater than 90. I did tell you in my beginning of lecture, increasing alpha alone above 90 degrees in the single convertor will not ensure where the machine or motor will act like a generator.

Similarly, here interchange the terminals alone, not ensure the motor to act like a generator. I have to interchange or I have to interchange the polarities and simultaneously increase alpha above 90 degrees. So, this is the equivalent circuit. Current is still flowing in this direction. Prior to the polarity reversal, E_B was 170 degrees. For alpha is equal to 30 we found that V_{O} or the V_{in} is 179. 30 amperes is the current that it is flowing, R_A is 0.3 volts, so 170 is a voltage here.

Now, E_B is minus 170, current is still flowing in this direction of 30 amperes. What is α , what is the value or what is the magnitude of V_{in} ? It should be 161 volts. I_{r_a} drops, the difference between this should be I_{r_a} drops. Current is still flowing in this direction. If this is 170, this is 161.


So, current is continuous. Listen, current is still continuous, so therefore, alpha is 141. What is the amount or what is the power feed back to the source? It is nothing but V_{in} into I average or

output power of the generator minus I_A square into R_A . What is the power output of the generator? E_B into I_A , 170 into 30 is the output power of the generator minus I square R losses 270 watts. Therefore, power fed back is power output minus I square r losses. This should also be equal to V_1 into I_1 into \cos of the angle between V_1 and I_1 **we are**, because we are assuming that converter is loss less. In other words, efficiency of the converter is 100%. Generally, efficiency is very high. In all the problems solving, we have neglected device drops. Actually, the voltage applied to the load is slightly less than $2 V_m \pi$ into $\cos \alpha$ because 2 devices are conducting at a time.

If you recall 1 of the assumptions that we made in the very first lecture of converters is that source inductance is 0. But now, let us consider the effect of source inductance because source inductance is always finite because power is fed back, power is being fed through transmission lines or underground cables, there is a transformer at 1 end, it has its own leakage inductance. So, source inductance is finite.


Now, let us see effect of source inductance. If the source inductance is 0, the moment T_3 is triggered, T_1 turns off because current can instantaneously change.

(Refer Slide Time: 42:00)

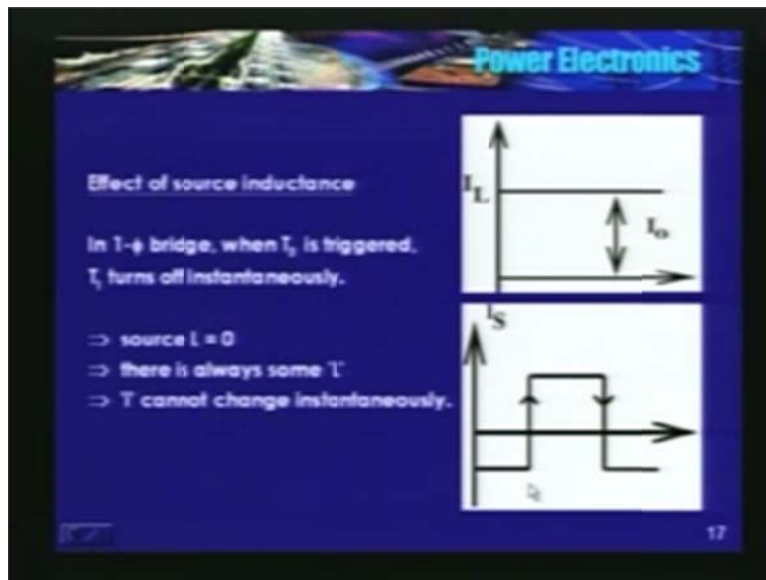

See, here is the wave form. I_L is the constant and ripple free. Somewhere at α , T_3 might have triggered. So, the moment you trigger T_3 , T_1 turns off. T_1 turns off and current reverses. At this instance, T_1 is triggered, T_3 turns off and positive current and here T_3 is triggered, T_1 turns off, negative current. So, current changes instantaneously. This is possible only if the source inductance is 0. If there is a finite source inductance, what will happen now? What will happen to the output voltage? We will see.


(Refer Slide Time: 42:48)

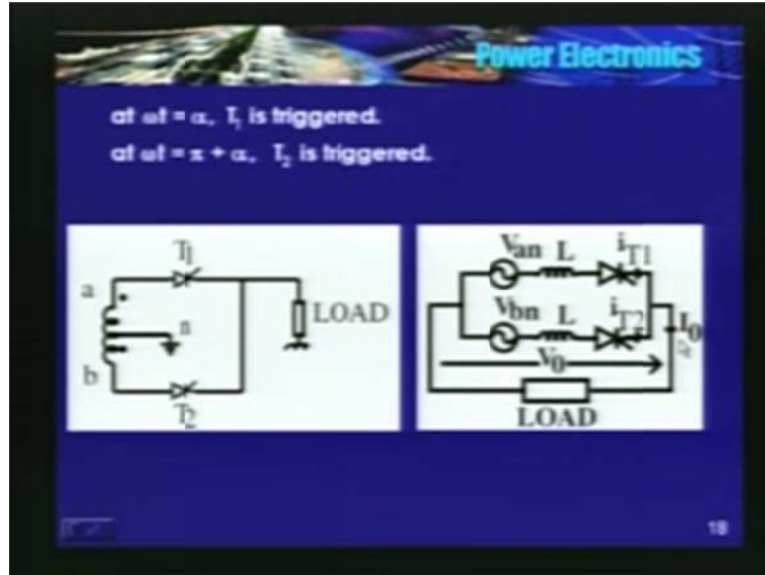

Let us consider a simple case. Now, I am using a center tap transformer, T_1 and T_2 . Let me tell you 1 thing, you can do this analysis for a fully controlled bridge also, similar steps. So, V_{an} is the voltage induced in the upper half of the transformer and V_{bn} in the lower half. L is the leakage inductance or inductance of this path. Similarly, L is the leakage inductance of transformer, i_{T1} and i_{T2} are thyristors of the load. At α , T_1 is triggered, at $\pi + \alpha$, T_2 is triggered.

Now, source inductance is finite. Now, how does output voltage look like? Initially, the entire I_0 was flowing through i_{T1} , through T_1 , entire load current was flowing through T_1 . T_2 is triggered, now, current through T_1 starts decreasing. It cannot come down to 0 instantaneously because of this L . At the same time, current through T_2 starts increasing. Since, we assume as load current is constant and ripple free, I_0 is constant. So, i_{T1} is equal to or $i_{T1} + i_{T2}$ should be equal to I_0 . So, i_{T1} decreases, i_{T2} increases, so the sum remains I_0 .

(Refer Slide Time: 44:49)

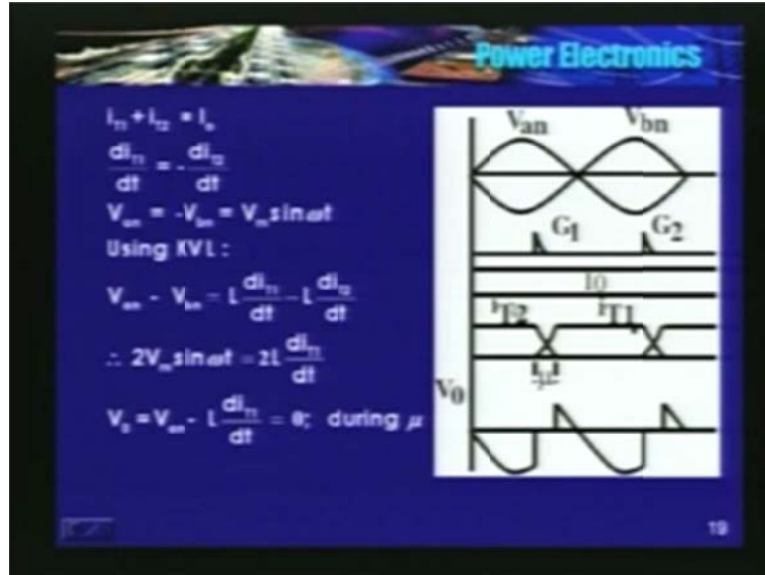

Now, what does the KVL gives? KVL is V_{an} is equal to minus V_{bn} is $V_m \sin \omega t$. For KVL, if I use KVL, V_{an} minus V_{bn} is equal to $L \frac{di_{T1}}{dt}$ by dt minus $L \frac{di_{T2}}{dt}$ by dt . See in this circuit, if I use KVL, V_{an} minus V_{bn} is equal to voltage drop across this inductor and voltage drop across this inductor, KVL. Here current is decreasing, this current is increasing. So, $\frac{di_{T1}}{dt}$ by dt is equal to minus of $\frac{di_{T2}}{dt}$ by dt . Current slowly decreasing, current slowly increasing.


Similarly here, i_{T2} T, current through this thyristor 2 is decreasing and is increasing in the thyristor T_1 and both the thyristors are conducting for a finite time what is known as μ . Now, substitute this condition in this equation. We will find that $V_m \sin \omega t$ is equal to $L \frac{di_{T1}}{dt}$ by dt .

What is V_o ? This voltage is nothing but V_{an} minus $L \frac{di_{T1}}{dt}$ by dt . We found that V_{an} is equal to $L \frac{di_{T1}}{dt}$ by dt during this, during μ . So, output voltage is 0 during μ . In other words, when both the thyristors are conducting, output voltage becomes 0 in a single phase. So in this period, output voltage is 0. So, prior to T_1 , T_2 was conducting, voltage is negative, same wave form. During μ , output voltage is 0. Then T_2 , current through T_2 becomes 0. In other words, entire current, T_1 is carrying now. Now, V_o is nothing but V_{an} itself, that is $V_m \sin \omega t$. Now, this is the wave form.

So, you will find that there is a net reduction in the output voltage. If source inductance is 0, you would have got instantaneous rise here and would have followed this way. Output voltage would have been instantaneous change and would have followed this way. But then here, due to source inductance for a finite time, this output voltage is 0.

So, from observing this wave form, we can conclude that because of the source inductance there is a reduction in the output voltage. What is the magnitude of the reduction in the output voltage? We will find out. We will derive an expression.

(Refer Slide Time: 48:21)

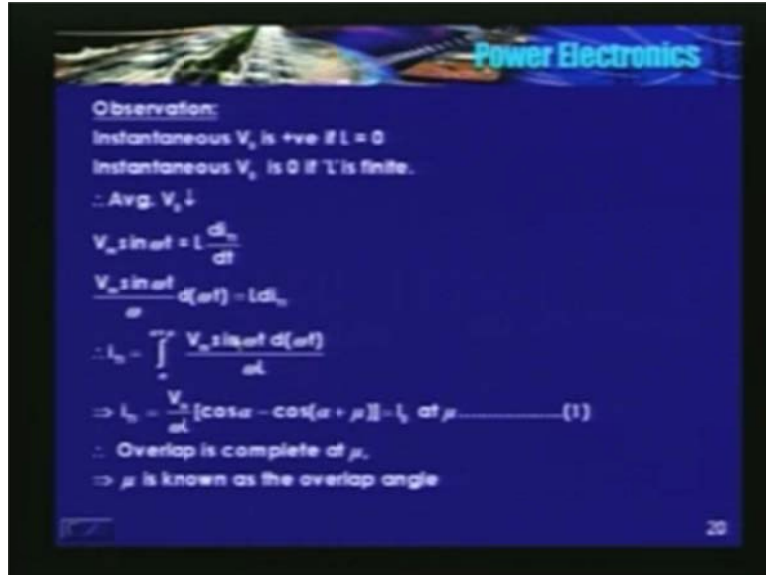

So, here is a, where are the various equations? They are very simple and straight forward. At alpha, $2\alpha + \mu$, i_{T1} is given by this equation because $V_m \sin \omega t$ is equal to $d i_{T1}$ by dt . So, I can derive this equation from this. Integrate this and at alpha, at ωt is equal to $\alpha + \mu$, i_{T1} is nothing but I_0 .

I will repeat; when ωt is equal to $\alpha + \mu$, this quantity is I_0 itself because entire current, i_{T1} is carrying. So, since both the thyristors were conducting during μ , this period is known as overlap period or overlap angle. μ is also known as the overlap angle. What is the expression for the average output voltage? because, now there is a 0 voltage period during μ . From alpha to $\alpha + \mu$, the average, alpha to $\alpha + \mu$, the instantaneous value of the output voltage is 0. So, expression for average, V_0 is $2 \int_{\alpha}^{\alpha + \mu} \sin \omega t d(\omega t) + \int_{\alpha + \mu}^{2\pi + \alpha} 0 d(\omega t)$.

(Refer Slide Time: 49:59)

Power Electronics

$\therefore \text{Avg } V_o = \frac{2}{\pi} \int_{\alpha}^{\alpha+\pi} V_m \sin(\omega t) dt$
 $= \frac{2V_m}{\pi} [\cos(\alpha) + \cos(\alpha+\pi)]$
 Using Eq. 1
 $\frac{V_o}{\pi} \cos(\alpha + \mu) = \frac{V_o}{\pi} \cos \alpha - \frac{I_0 \omega L}{\pi}$
 Substituting in the above equation
 $V_o = \frac{2V_m}{\pi} - \frac{2V_o}{\pi} \cos \alpha$
 \therefore Equivalent circuit
 $V_o = 0$ for $\mu = \pi$ or $\alpha = 2\pi$
 $\mu = \pi$ \rightarrow one overlap mode
 \rightarrow no powering mode I
 \rightarrow Load is a current source
 \rightarrow Magnitude V_o is independent of terminal V
 $\mu = \alpha - 2a$
 \rightarrow Load is pure L
 \rightarrow Possible

So, here is the expression. From alpha plus mu 2 pi plus alpha, it is $V_m \sin \omega t$. It is not that alpha to pi plus alpha it is $V_m \sin \omega t$, it is alpha to mu sorry alpha plus mu to pi plus alpha, it is $V_m \sin \omega t$. So, you will find that average V_0 is given by this equation.

In our previous expression that was here, $\cos \alpha + \mu$, so we will substitute for this factor and solve it. You will get this expression. So, V_m by pi into $\cos \alpha + \mu$ is equal to V_m by pi into $\cos \alpha - I_0 \omega L$. This is from a previous equation, equation number 1. Now, if I substitute this in this, I will get this equation. Now, can I draw an equivalent circuit of this equation? Here is it, $2 V_m$ by pi into $\cos \alpha$ which is again varying.

There are 2 thyristors here, at any given time. In this case, there may be 1 but then if I use this bridge, 2 devices are conducting at a time into ωL by pi into I_0 is the voltage drop due to source inductance, mind you. R represented by resistor here, ωL by pi. So, I_0 is the current that is flowing through the load. So, remaining is the voltage across the load, V_0 . What is our another observation?

You find this from this expression that average V_0 is 0 for 2 values of mu. One is mu is equal to pi or mu is equal to pi minus 2 alpha. So, both these values, average value of V_0 is 0. Or let us take first condition, mu is equal to pi. First of all, can I have that sort of a condition? In the sense, for entire pi duration, there is a short circuit. In other words, output voltage is 0 for pi radians, both the thyristors starts are conducting, the entire positive half cycle is an overlap period for thyristor 1 and the remaining pi radians in the negative half is the overlap period for another thyristor.

In other words, source does not supply any power to the load. But then we have assumed that load current is constant and repel free and there is no period or in other words, there is source does not supply power to the load at all. How is this possible? This is possible only if the load is an ideal current source. Remember, is an ideal current source. Voltage, terminal voltage is

independent of or the current that is flowing is independent of the terminal voltage. Voltage applied during μ to a load is 0 but then constant current is flowing, this is possible only if the load is an ideal current source.

The second condition is μ is equal to $\pi - 2\alpha$. So, let us draw the wave form. How does it look like? At α T_1 is triggered, overlap period is $\pi - 2\alpha$. So, this is μ , this should be α , so this is $\pi - 2\alpha$. Again at α , in the next half, at α one more thyristor is triggered that is T_2 is triggered. This is the competition overlap period and at this point **overlap** commutation overlap, commutation is complete. Entire current, thyristor starts carrying.

So, if you see here, average value of the output voltage is 0, positive half is equal to negative half. So, what sort of a load? It is an ideal inductor. So second case, ideally, it may be possible but for that matter, even the first case if I connect **a constant** an ideal constant current source, a single phase bridge is feeding. So, μ is π , it is possible. The second case if I have an ideal inductor, I can have a situation wherein, overlap period is equal to $\pi - 2\alpha$.