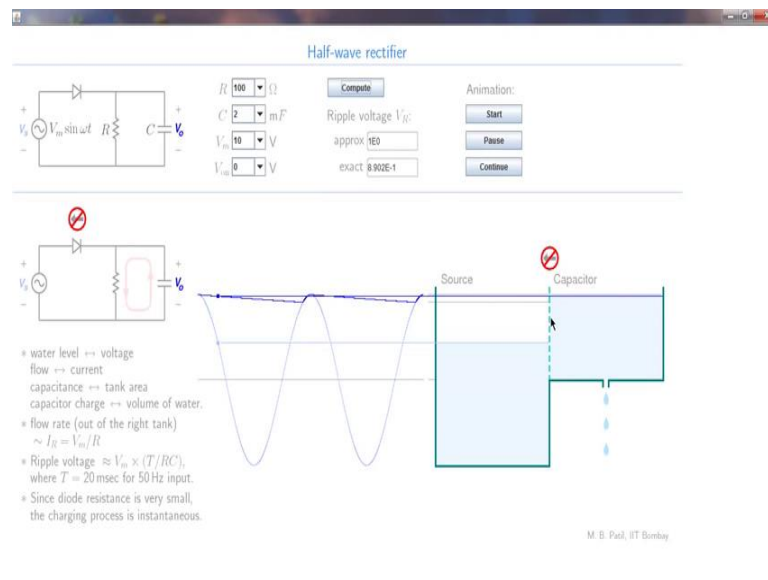


Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture - 20
Diode rectifiers (continued)

Welcome to Basic Electronics. In the last class, we discussed a half-wave rectifier circuit, and looked at the various waveforms namely the input and output voltages, diode current and capacitor current. To help in visualizing the circuit operation, we will now look at an animation which mimics charging and discharging of the filter capacitor. The animation will help us to understand clearly the reason behind the ripple voltage at the output. We will also get to know which factors are responsible for the ripple voltage and therefore, how to make it smaller. We will then take up a numerical example, work out expressions for the various quantities of interest and calculate those quantities for the given circuit. Let us get started.

(Refer Slide Time: 01:13)



Here is an animation and the component values can be set here, for example, R can be 100 or 150 or 200 ohms; C can be 1, 1.5 or 2 millifarads; V m the peak of the input voltage can be 10 or 12 or 5; and V on for the diode can be either 0 or 0.7 volts. So, let us compute and when we compute many things happen here we will look at it soon. The

ripple voltage V_r is approximately 2, and we will look at this approximate way of calculating V_r . And if you do it more exactly it turns out to be 1.66 volts.

Before we start the animation, let us note a few things. So, there are two tanks here, one corresponding to the source and the other tank corresponding to the capacitor. And there is going to be water in these tanks and that water level corresponds to the voltage either the source voltage or the capacitor voltage, which is the same as the output voltage. Water flow is going to correspond to current. So, there is going to be water flow out of this tank, there is going to be water flow into this tank, and that corresponds to current.

Capacitance corresponds to the area of the tank, for example, if this tank was wider then that means, the capacitor is larger. And the capacitors charge is equivalent to the volume of the water inside. So, if this tank has a certain volume of water that corresponds to the charge on the capacitor.

The flow rate out of the right tank that is the flow rate over there is equivalent to the load current, current through the resistor, which is approximately V_m by R , because we have seen that the voltage across the resistor which is V_o is nearly equal to V_m . Also it is good to note this formula ripple voltage V_r is given by V_m times T - the period of the input waveform divided by Rc . We are actually going to derive this formula soon. For our 50 hertz input, the time period is 20 milliseconds. Also since the diode resistance is very small the charging process is instantaneous as we have already remarked earlier.

So, with these in mind let us now look at the animation. So, what we will do is we will just let the animation run for some time and then comment on what is happening. So, just observe for two cycles. So, let us now relate what is happening in this picture to our actual circuit. So, there is this source, it is like an artificial tank, there is no such tank in nature. And its water level goes up and down, it just keeps going up and down forever, just like the source here. This source tank is separated from the capacitor tank with a membrane or a wall. Now this wall is rectifying. So, it allows water to flow from there to there, but not the other way, and that is the meaning of this arrow here; the same as this arrow because the diode does not allow current in that direction.

Let us now comment on the size of the currents involved, in particular the load current and the diode current; where is the load current in this picture? The load current is right here. So, the load current basically is responsible for discharging the capacitor here, and


this water flow is responsible for emptying the tank - the capacitor tank and that is a relatively slow process because we do not want the level to drop drastically, we want the level to be in fact a constant. Now, what happens is this source level goes up and when it goes above the capacitor level, then there is a sudden water flow from the source to the capacitor.

And let us just watch it once again. So, as we see this process is going on continuously and whatever water is lost from the capacitor tank has to be replenished from the source in a very short time, because it is only a short time that the water level in the source is higher than the capacitor level. So, the water flow that happens in that short time must be larger much larger than this water flow. And that means that the peak diode current must be much larger than the average load current.

Let us now try to understand the relationship between the ripple voltages; that is this difference here. And the capacitance values, the resistance value and V_m - the input amplitude. Let us consider the capacitance first. Where is the capacitance in this picture? The capacitance is the volume of this tank; it represents the capacity. Now, suppose we increase the capacitance from 1 to 2 millifarad, what would happen, the capacitance would then increase the tank would increase in size.

Now, we have not really change the resistance value, so the flow rate which corresponds to the average load current which is V_m by R that is not changing. And therefore, in a given time that is in one period the water the volume of the water that is lost from this tank would still be the same, but now the area of this tank has increased. So, what it means is the height or the ripple that this situation corresponds to will now be lower. So, let us check that out.


(Refer Slide Time: 10:08)

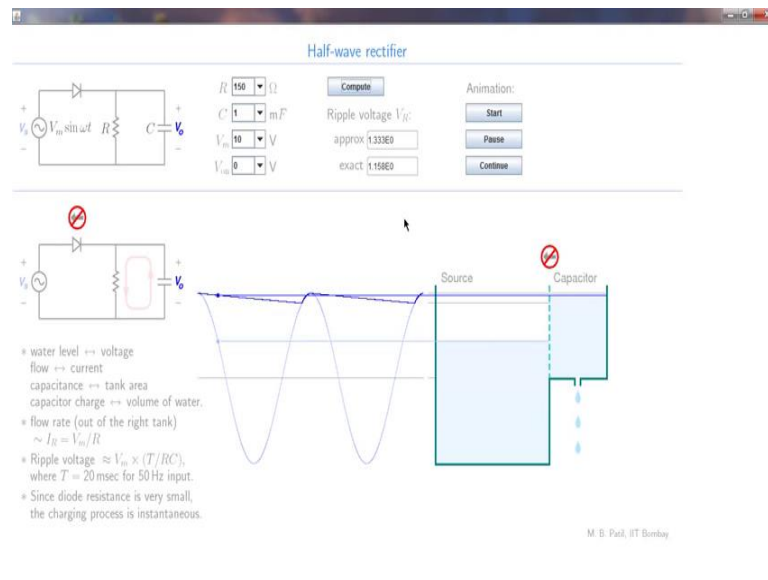

So, remember the earlier ripple is two. And now let us compute again. Now, the new ripple voltage is 1; and as we expected the size of this tank has increased. What if we increase the resistance value, let us say from 100 to 150. What would happen then? Now as you have seen the resistance controls this flow out of the capacitor tank and it is given by approximately V_m/R . So, if I increase the resistance, this flow is going to decrease. And in the same amount of time that is one period the volume of the water that is lost from this capacitor tank will then reduce.

And we have to then replenish only a smaller volume and that corresponds to a decrease in the ripple voltage. And let us check that out or from 100 to 150, the ripple voltage with 100 is 2 volts and with 150. Let us compute, it is 1.33 volts and that is what we expect.

(Refer Slide Time: 11:10)

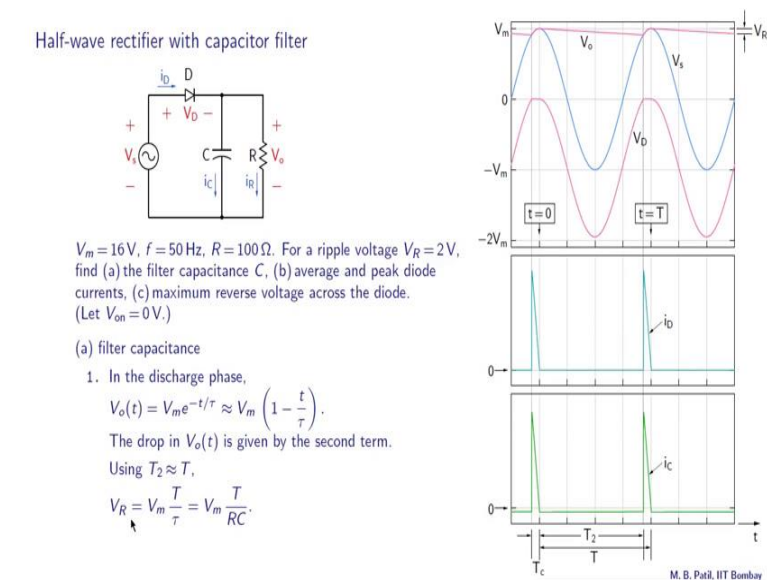

So, let us look at this example half-wave rectifier with capacitor filter. We are given V_m to be 16 volts frequency, 50 hertz of course, about this we do not have too much choice because as same as the mains frequency, R -the load resistor is 100 ohms and for a ripple voltage of 2 volts, we want to find the filter capacitance. So, we will do that first, and with that capacitance value then we will look at what is the average and peak diode current, and what is the maximum reverse voltage that appears across the diode. And in all of these calculations, we will assume that V_{on} is 0 volts; and in reality different V_{on} like 0.7 volts does not really make too much difference and we already seen that in the plots that we saw earlier.


So, let us begin with the a-part calculation of the filter capacitance. Let us recall that the diode conducts in a relatively small interval, then it is off, then again it conducts in the next cycle and so on. This part corresponds to the charging that is increase of voltage and the maximum is V_m . And these part this interval which is marked as T_2 here from there to there. This corresponds to discharging of the capacitor through the resistor. So, the diode is off, and because the capacitor is discharging through the resistor, we have this drop in the output voltage. At this point, once again the diode starts conducting and the capacitor voltage the output voltage increases.

So, now that discharging process corresponding to this $R-C$ circuit with the diode off is described by this equation V_o of t is $V_m e^{-t/\tau}$. Now, τ normally

is selected for a small ripple and that happens if the time constant Rc is much larger than one period. And if that is the situation t by τ is much less than 1 and then $V_m e^{-t/\tau}$ can be approximated as $V_m (1 - t/\tau)$. Now, at $t = 0$, our capacitor voltage is V_m at $t = T/2$ this is 0, this is $T/2$; at $t = T$, our capacitor voltage has dropped by V_r that is our ripple voltage.

In other words if we substitute $t = T/2$ here then $V_m (1 - T/2\tau)$ should be equal to $V_m - V_r$. Now, the problem is that $T/2$ is not known and this is where we make an approximation; that approximation is that $T/2$ is nearly equal to T . So, what we are saying is this $T/2$ is nearly equal to the entire time period. Now, this is not an unreasonable approximation because the time during which the diode conducts is indeed small compared to the time period, and therefore this is a reasonable approximation. So, with that approximation, we now get V_r is $V_m T/2\tau$; now $T/2$ is approximately T . So, therefore, V_r is $V_m T/\tau$ which is $V_m T/Rc$.

(Refer Slide Time: 15:28)

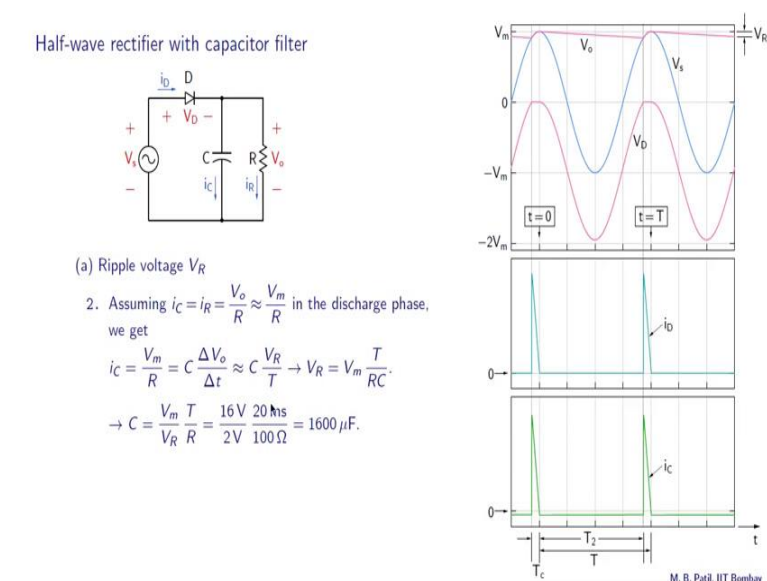


Here is another way of computing the ripple voltage; we start with i_C equal to i_R in the discharge phase, the diode is not conducting and i_C and i_R are therefore, equal in magnitude. i_R is V_o/R and V_o is approximately constant which is equal to V_m and that holds if the ripple voltage is small. So, we have i_C equal to V_m/R ; and i_C is also equal to $C \frac{dV_o}{dt}$ which is V_o appears across the capacitor as well. And if we look at V_o in the discharge phase, it falls linearly and we have seen the condition for that to

happen that is the time constant $R C$ is much larger than the period T of the input waveform.

So, if V_o is falling linearly then the derivative is constant. And we can calculate the derivative by using ΔV_o divided by Δt and that is written here ΔV_o is the same as V_r and Δt in the discharge phase is actually $T/2$ if we come down that is $T/2$. And once again we will make this approximation that $T/2$ is nearly equal to T and therefore, we get i_C equal to V_m by R equal to $C V_r$ by T and that gives us a value for V_r . So, V_r is $V_m T$ by $R C$.

From this expression for V_r we can now obtain $C V_m$ by R times T by R . And we have been given these values and we want to find C . So, V_m is 16 volts, V_r we require it to be 2 volts, the time period corresponds to the input frequency of 50 hertz which is 20 milliseconds and R the load resistance is 100 ohms. When we calculate this number, it turns out to be 1600 microfarads or 1.6 millifarads.

(Refer Slide Time: 18:05)

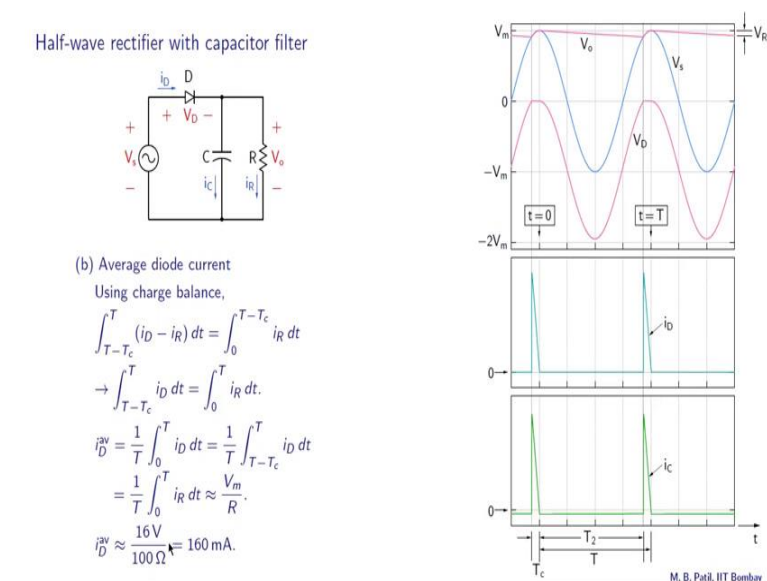

Let us now look at the average diode current, and we can use charge conservation to obtain this. Charge conservation requires that the change in Q for the capacitor in one period must be 0. And since $i_C = dQ/dt$ we require the integral of i_C over one period to be 0. So, let us look at the capacitor current which is shown here. Now, in this interval marked T_c here, the capacitor current is positive, the diode conducts the capacitor gets charged like that. And in this second interval, the diode is not conducting i_D is 0 and we

have only this R and C in parallel. Now, the capacitor is supplying current to the register. So, i_C is negative.

So, we see that here this is a negative current. And now charge conservation requires that the integral under this curve should be exactly equal and opposite to the integral of this curve or the area under i_C in that interval, so that is our starting point. And let us see what that implies. In the charging phase, i_D is equal to i_C plus i_R . So, therefore, we can write i_C as i_D minus i_R ; and in the discharging phase this i_D is 0 and therefore, i_C is equal to minus i_R .

So, let us now put it all together and obtain an equation which results from charge conservation that is what we get. So, this i_D minus i_R is nothing but i_C in the charging phase, and therefore the limits here are $T - T_c$ to T , what is $T - T_c$, this is our 0, this is our T , this point $T - T_c$ is this point right here. So, $T - T_c$ to T is basically this interval marked here. What about 0 to $T - T_c$, this is our 0 and 0 to $T - T_c$. So, we are talking about the discharge phase now. So, these two integrals must be equal. And we can simplify things, we can club this integral $i_R dt$ with the one on the right hand side. And then we get integral $i_D dt$ $T - T_c$ to T is integral $i_D dt$ from 0 to T .

And now we want the average value of the diode current. What is the average value? It is simply the integral from 0 to T $i_D dt$ and 0 to t essentially means $t - t_c$ to t because the diode does not conduct in this other interval, and that we need to divide by the period t , so that is what we get. And since this and that are equal, we get i_D average equal to 1 over T integral $i_R dt$ over one period. Now, i_R is nearly constant as we have seen before. So, it is just V_m by R and the average value of i_D turns out to be equal to the average value of i_R that is V_m by R . And for this example it turns out to be 16 volts by 100 ohms that is R and that is 160 milli amperes.

To summarize, we have used an animation based on the analogy between the half-wave rectifier and hydraulic system. This analogy helped us to identify the factors responsible for a nonzero ripple voltage at the output. After that we worked out an approximate formula for the ripple voltage; and used it in a numerical example. In the next class, we will complete the half-wave rectifier problem and then take up the full-wave rectifier circuit, until then goodbye.