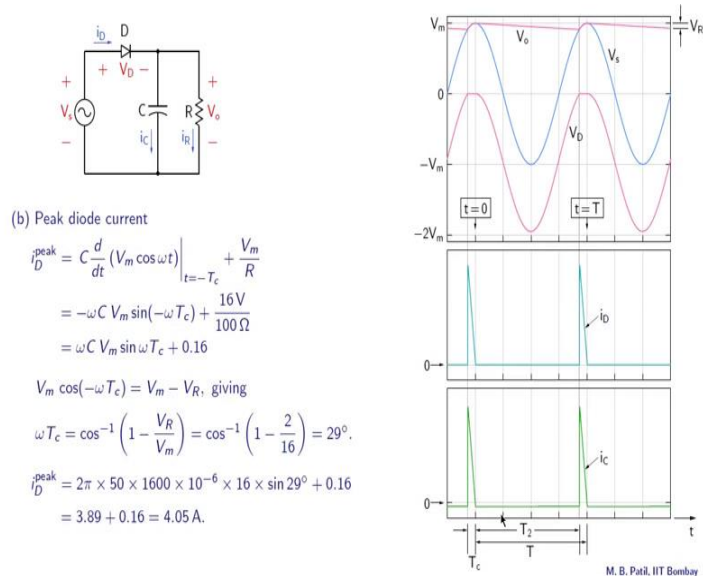


Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture - 21
Diode Rectification (continued)

Welcome back to Basic Electronics. In this lecture, we will continue with the half-wave rectifier example from the previous class. We will estimate the maximum current that flows through the diode and also obtain an analytic expression for that current. We will then repeat the calculations; that are ripple voltage, average and peak diode currents for a full-wave rectifier circuit. Finally, we will compare the half-wave and full-wave rectifier circuits with respect to different criteria. So, let us get started.

(Refer Slide Time: 00:54)



Let us now talk about the peak diode current. And to begin with let us remind ourselves of what i_D looks like as a function of time, this plot here i_D is nonzero only in this short interval marked as T_c here, and otherwise it is 0. Now what is i_D given by i_D is given by i_C plus i_R ; i_R is more or less a constant because V_o is constant approximately equal to V_m . So, therefore, i_R is V_m by R and that is already known. What we need to now worry about is this capacitor current. And in particular, we need to worry about i_C in the charging interval this interval here, because that is when this diode is conducting. Now, when the diode is conducting this voltage is 0, and therefore V_c is the same as V_s . So,

therefore, the capacitor current i_C which is $c \frac{dV_c}{dt}$ is the same as $c \frac{dV_s}{dt}$. And the diode current is maximum when i_C is maximum, because this current here is a constant.


So, we need to now answer two questions: one when is this derivative $\frac{dV_s}{dt}$ maximum because c times that derivative is going to give us the maximum capacitor current and therefore the maximum diode current. And second what is the value of that derivative. And to answer those questions, let us once again look at the interval in which the capacitor is getting charged that is when the diode is conducting that is this interval here. And we are interested in finding the maximum value of $\frac{dV_s}{dt}$ in this interval. So, this is how V_s varies and clearly the maximum slope happens at this point right here and that is $T = -\tau_c$ this is over $T = 0$. So, this is $T = -\tau_c$. So, what we need to do now is to find the slope $\frac{dV_s}{dt}$ at this $T = -\tau_c$, so that is the equation for the peak diode current $c \frac{dV_s}{dt}$ evaluated at $T = -\tau_c$ plus the register current i_R , which is approximately constant V_m by R .

V_s is $V_m \cos \omega t$ and that is because we have taken our time equal to 0 at this point here. So, when we differentiate, we get this result this 0.16 is coming from $i_R V_m$ by R . And the first term the capacitor current is $\omega C V_m \sin \omega T_c$. Now, in this expression we know everything $\omega C V_m$ except T_c . So, T_c is something that we need to figure out. And let us see how that can be done approximately and that is from this equation. So, what can you say about the value of V_o at this point $T = -\tau_c$ that is nothing but $V_m - V_R$ because the difference between these two is V_R and therefore at $T = -\tau_c$ V_o is $V_m - V_R$. So, we can use that condition to get $V_m \cos$ of $-\omega T_c$ equal to $V_m - V_R$ and that gives us an idea of what T_c should be. So, ωT_c then a is \cos^{-1} of $1 - \frac{V_R}{V_m}$; V_R is 2 volts V_m is 16 volts, and ωT_c then turns out to be 29 degrees.

When you use your calculator to compute this ωT_c , you need to be a little careful because your calculator may give this value in radians, and then you need to convert that into degrees or you can you keep it in radians, but then be aware that it is in radians. Now, we have got ωT_c now it is a simple matter of substituting ωT_c here and this current then can be evaluated, like that. So, this is the peak diode current the first part here is 2π times f or ω f is 50 hertz, C is 1600 microfarads, we have already computed that earlier, V_m is 16 volts then followed by \sin of 29 degrees, that 29 degrees is coming from ωT_c .

So, all of this turns out to be 3.89 to that we have to add the register current 0.16 ampere. So, it is 3.89 plus 0.16 about 4 amperes. One important thing to note here is that the maximum capacitor current is much larger than the average register current and that we can also see from this figure here that is the maximum capacitor current and this value here the one which is going negative is the average register current.

(Refer Slide Time: 07:32)

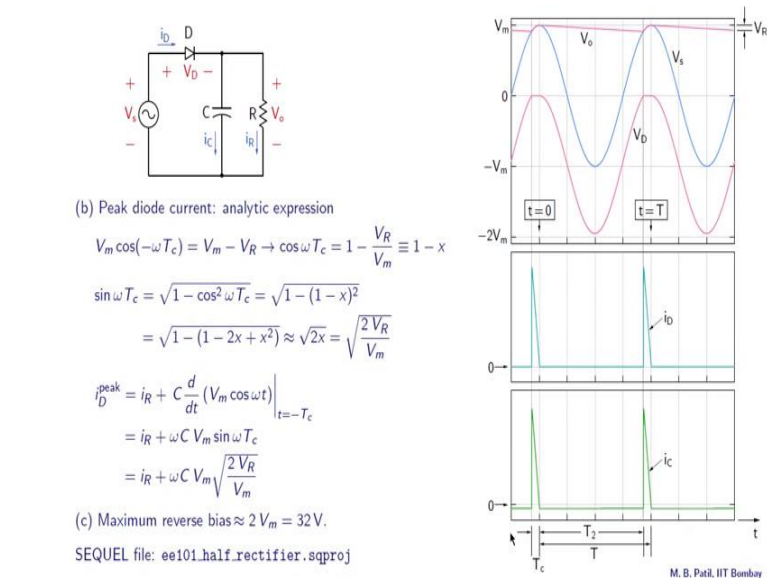

Let us now obtain an analytic expression for the peak diode current. We begin with this condition the source voltage at minus T_c is equal to V_m minus V_R at that point we have seen that in the last slide and that gave us an expression for $\cos \omega T_c$ as 1 minus V_R by V_m . And earlier we calculated ωT_c using a calculator got a numerical value for ωT_c and then proceeded. Now, we want to do the same thing analytically.


So, let us write V_R by V_m as x , what is x in this case, V_R is 2 volts V_m is 16 volts. So, x is 2 by 16 or 1 by 8. So, x is small compared to 1; and we will use that. From $\cos \omega T_c$, we can write $\sin \omega T_c$ as $\sqrt{1 - \cos^2 \omega T_c}$ square root of that, so that is $\sqrt{1 - (1 - x)^2}$ is $\sqrt{1 - 1 + 2x - x^2}$ so that is $\sqrt{2x - x^2}$. And now let us expand this we get $\sqrt{2x - x^2} \approx \sqrt{2x}$ because x^2 is much smaller than $2x$. So, $\sqrt{2x}$ is $\sqrt{2} \times \sqrt{x}$. So, \sqrt{x} is $\sqrt{1/8}$ which is $1/\sqrt{8}$. So, $\sqrt{2x}$ is $\sqrt{2} \times 1/\sqrt{8} = 1/2$. So, $\sin \omega T_c \approx 1/2$. So, $i_D^{\text{peak}} = i_R + \omega C V_m \times 1/2$. So, $i_D^{\text{peak}} = 0.16 + \omega C V_m \times 1/2$. So, $i_D^{\text{peak}} = 0.16 + 3.89 = 4.05$ amperes.

And now you can use this result to get the peak diode current is i_R plus $C \frac{dV_s}{dt}$ evaluated at t equal to minus T_c and as we have seen in the last slide this is the same as $\omega C V_m \sin \omega T_c$. And the $\sin \omega T_c$ can now come from this result and that is what we get finally. What about the maximum reverse bias, we have already seen earlier that it is going to be two times V_m , where V_m is the peak value of the input voltage. Let us quickly go through that argument once again V_D is equal to V_s minus V_o . Now, V_o is nearly constant that is equal to V_m and therefore, V_D is equal to V_s shifted down by V_m because V_D is V_s minus V_o and that essentially is this waveform here. And the lowest value is minus $2 V_m$ so that means the maximum reverse bias is $2 V_m$ in this case it is 32 volts.

And we should keep in mind that all these calculations that we are doing are not simply academic curiosity, these numbers that is the average diode current the peak diode current, the maximum reverse bias are very important in practice, because that will decide what diode we are going to pick over here; and consequently the cost of the circuit that we are going to build.

Here is the sequel circuit file. So, you can run the simulation, and check whether you get all of these results given here. You can also change some of these component values for example, you can make this capacitance double of what it is now, predict what the new ripple voltage is going to be, what is the new peak diode current and so on. And then check with the simulation results whether your predictions are correct. In general, it is always good to at least have some idea of what to expect from your simulation, and not just run the simulation blindly and see what you get. Sometimes, your predictions may not be correct and that is even better because then you will figure out what mistake you made and chances are that you will not make the same mistake again.

(Refer Slide Time: 12:24)

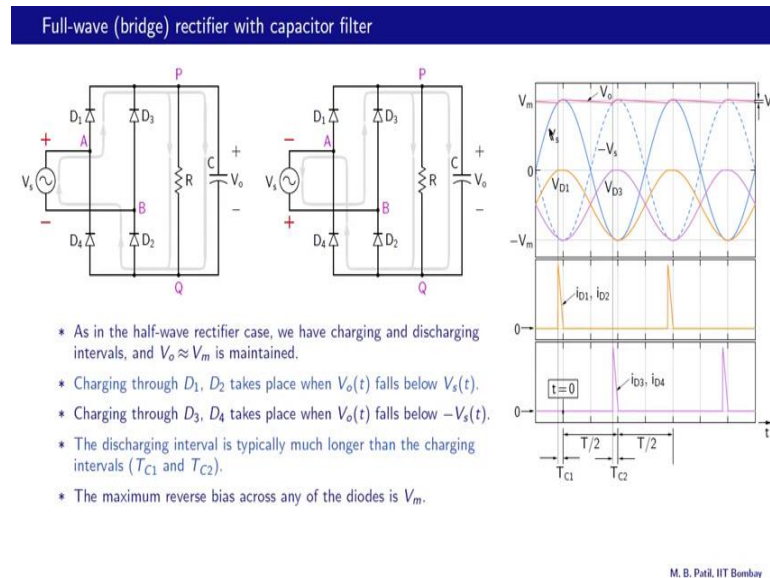

We now look at the full-wave or bridge rectifier with capacitor filter. And at this point, it may be a good idea to go back a few slides and revise the case of full-wave rectifier without a filter. What we will do now is make a few observations and then take up a numerical example. First as in the half-wave rectifier case, we have charging and discharging intervals and V_o is approximately maintained at V_m . So, let us look at the waveforms this is the input voltage V_s that dashed curve is the negative of input voltage; V_s curve goes from plus V_m to minus V_m and that is the output voltage, the one shown in the pink graph. And the output voltage is nearly constant, but there is a small ripple the difference between the maximum and minimum output voltage levels that is called V_r .


When the input voltage V_s goes beyond the output voltage D_1 and D_2 conduct and when minus V_s goes beyond the output voltage D_3 and D_4 conduct. And once again the diode currents will turn out to be large compared to the load current. So, those points are listed here. The discharging interval is typically much longer than the charging intervals T_{c1} and T_{c2} ; this is T_{c1} here. And in the T_{c1} interval, D_1 and D_2 conduct and D_3 and D_4 are not conducting at that time; in the T_{c2} interval, D_3 and D_4 conduct and D_1 and D_2 remain off. The maximum reverse bias across any of the diode is V_m here is the diode voltage V_{D1} and it is actually the same as V_{D2} . And we notice that it goes from 0 to minus V_m . So, the maximum reverse bias across D

1 or D 2 is V_m ; this one is V_D 3 the same as V_D 4. And once again the maximum reverse bias across D 3 or D 4 is V_m .

Now, this also that V_D 1 or V_D 2 is 0 when D 1 and D 2 conduct. Similarly, V_D 3 and V_D 4 are 0; and D 3 and D 4 conduct. So, we observe that there are many similarities between the half-wave rectifier, and full-wave rectifier with filter. The main difference is in the charging of the capacitor. In the half-wave rectifier, there was only one charging interval; in the full-wave rectifier, there are two charging intervals within one period. For example, if we go from t equal to 0 to t equal to T , this point here then there is one interval in which charging takes place through i_D 3 and i_D 4 and another interval in which charging takes place through i_D 1 and i_D 2.

Apart from that things are very similar there is a charging interval in which the output voltage that is the capacitor voltage follows the input voltage, and the charge on the capacitor gets replenished. And when the input voltage goes down, the charging stops and now the capacitor discharges through the load register like that.

(Refer Slide Time: 17:18)

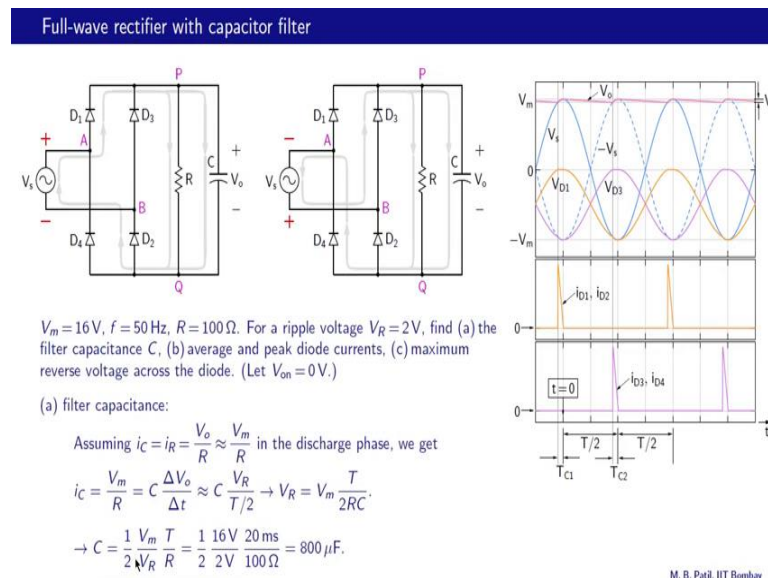


Here is a numerical example, and we have kept the numbers the same as the half-wave rectifier circuit. The maximum voltage input voltage is V_m equal to 16 volts, frequency is 50 hertz again, the load resistance is 100 ohms and for the same ripple voltage of 2 volts, we want to find the filter capacitance, the average and peak diode currents and the

maximum reverse voltage appearing across each diode. Once again, we will assume the voltage drop across the diodes to be 0 volts and when they conduct.

Let us look at the filter capacitance first. When the diodes are not conducting we have R and C, the capacitor discharging through the load resistor, and we are talking about this interval or this interval in these intervals the capacitance current is the same as the resistor current in magnitude. So, i_C is equal to i_R , and since V_o is nearly constant we have i_C equal to V_m by R the capacitor current is given by $C \frac{dV}{dt}$. And since this variation is once again linear, we can replace $\frac{dV}{dt}$ by $\frac{\Delta V_o}{\Delta t}$. ΔV_o is the same as ripple voltage here; and Δt is the duration of the discharge interval. So, let us take this interval for example.

So, that is from t equal to 0 to this point here which is nearly equal to T by 2. So, we substitute for Δt T by 2 and then we get V_R equal to $V_m T$ by 2 $R C$. And capacitance is now V_m by $V_R T$ by T divided by 2, this half is new here, it was not there in the half-wave rectifier. And when we substitute all the numbers, we get 800 microfarads.


(Refer Slide Time: 19:49)

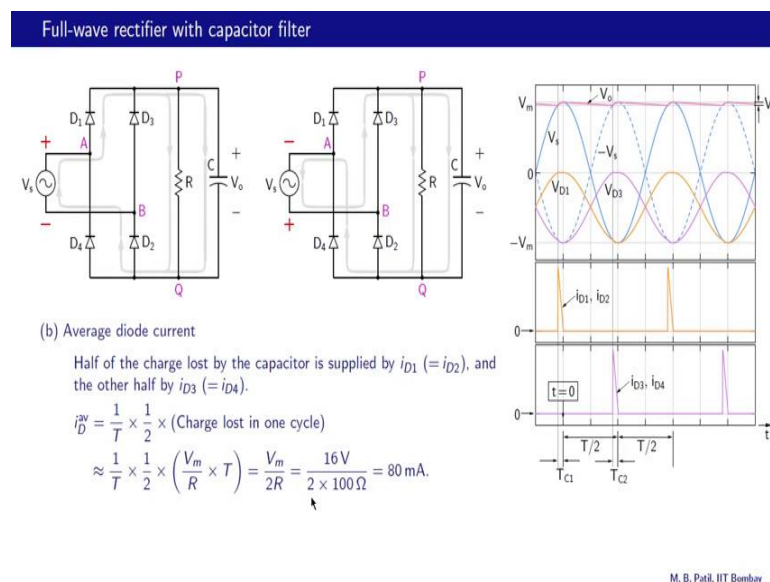

What about the average diode current. Now, as we observed earlier half of the charge lost by the capacitor is supplied by i_{D1} or i_{D2} , because $D1$ and $D2$ conduct at the same time; and the other half is supplied by $D3$ and $D4$ that is this situation here. And therefore, we can write the average diode current let us say through $D1$ is 1 over T times

half of the charge lost in one cycle; and the charge lost in one cycle is easy to calculate, it is simply the register current the average current times the time period T. So, this T cancels and we end up with V m by 2 R, so that 16 volts by 2 times 100 ohms which is 80 milliamps.


(Refer Slide Time: 21:04)

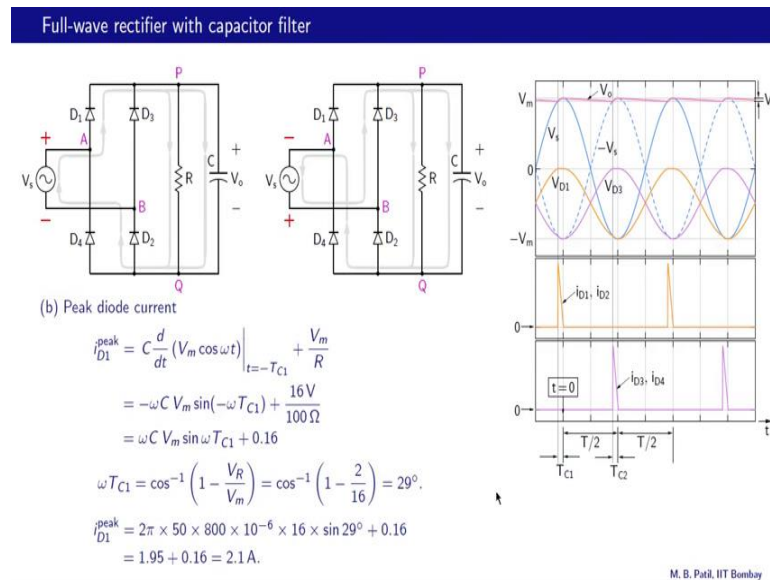

Let us look at the peak diode current and let us say we are talking about i_{D1} . So, i_{D1} is maximum here. And as before this is the sum of i_C and i_R , because the current it is applying both the resistor and the capacitor. And the resistor current of course, we already know its approximately V_m by R , and the capacitance current like in the half-wave case is the slope of this is given by the slope of this input voltage, and it is maximum at t equal to minus T_{C1} , so that is what we get.

And the next step now is to find T_{C1} . And we do that following the same procedure that we used for the half-wave rectifier that is we know that at this time, which is minus T_{C1} . The output voltage is V_m minus V_R and therefore, we can get ωT_{C1} as \cos inverse of 1 minus V_R by V_m , which turns out to be 29 degrees. So, now, we substitute this in the expression for i_{D1}^{peak} that is ωC times 50×800 microfarads V_m - 16 and sine of 29 degrees that is ωT_{C1} , so all that is the capacitor current at minus T_{C1} to that we add the resistor current 0.16 amp and we get a total of 2.1 ampere. So, that is the peak diode current for $D1$ and by symmetry it would be the same for all the diodes.

(Refer Slide Time: 23:13)

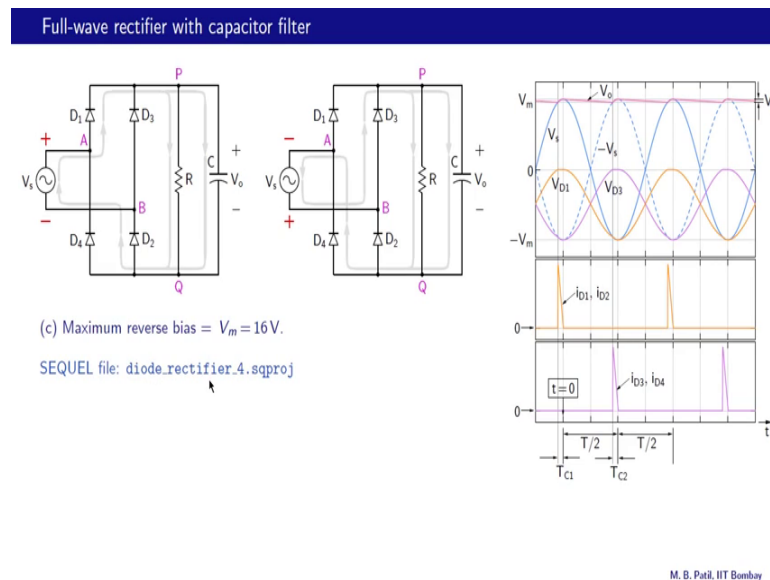

Let us look at the maximum reverse bias that each diode comes across. Let us take D 1 as an example. Here is V_{D1} when D 1 and D 2 conduct of course, V_{D1} is 0, and it goes through its maximum negative point when D 3 and D 4 conduct in this interval here. So, let us look at the circuit when D 3 and D 4 conduct this circuit D 3 is conducting. So, no voltage drop there, D 4 is conducting so no voltage drop here. So, the negative end of D 1 is at node P in the positive end is at the same as is at the same potential as node Q.

So, the difference between P and Q which is V_m appears across D 1 and that of course, is the reverse bias because V_P is higher than V_Q , so that is how we get the maximum reverse bias across d one it happens to be V_m that is 16 volts. And that is true also for the other diodes. The sequel file for this circuit is available and you can run the simulation.

(Refer Slide Time: 24:43)

Comparison of half-wave and full-wave (bridge) rectifiers with capacitive filter

For the same source voltage ($V_m \sin \omega t$), load (R), and ripple voltage (V_R), compare the half-wave and full-wave rectifiers.

Parameter	Half-wave	Full-wave
Number of diodes	1	4
Filter capacitance	C	$C/2$
Average diode current	i_D^{av}	$i_D^{\text{av}}/2$
Peak diode current	i_D^{peak}	$i_D^{\text{peak}}/2$
Maximum reverse voltage	$2V_m$	V_m

M. B. Patil, IIT Bombay

Let us now compare the half-wave and full-wave rectifier with the capacitor filter. For the same source voltage that is same V_m , same load resistance R , and the same ripple voltage. And if you recall in the numerical examples that we looked at we did follow these conditions that is we kept V_m , R and V_R the same for the half-wave example and full-wave example. So, this table shows the comparison, number of diodes one in the half-wave case, 4 in the full-wave case.

Filter capacitance if this is C then this is C by 2; average diode current if this is i_D^{av} average then this is i_D^{av} by 2. Peak diode current if this is i_D^{peak} then this is i_D^{peak} divided by 2. Maximum reverse voltage in this case it was 2 times V_m in the full wave case it was V_m . So, although the full wave rectifier requires four diodes as opposed to one here, it requires a smaller capacitor and also the diode specs are less stringent in the full-wave case and that is an advantage.

To summarize, we have carried out calculation of ripple voltage, average diode current and peak diode current for the full-wave rectifier. We then compared the half-wave and full-wave rectifier circuits with respect to different criteria; and found that the full-wave rectifier requires less stringent specifications for the components namely the filter capacitor and the diodes that is all for now.

See you next time.

