

Basic Electronics
Prof. Mahesh Pati
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture – 27
BJT amplifier (continued)

Welcome back to Basic Electronics. In the last lecture we showed that correct biasing of the BJT is crucial in amplification. We also looked at the simple biasing scheme which was found to be very sensitive to the beta of the transistor. We will now look at an improved biasing scheme and show that it is much more robust with respect to variations in the transistor beta. We will then turn our attention to the second major issue in BJT amplifiers that is adding the signal voltage to the bias voltage. We will illustrate how a coupling capacitor can be used for that purpose. So, let us get started.

(Refer Slide Time: 00:59)

BJT amplifier: improved biasing scheme

$$V_{Th} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{2.2k}{10k + 2.2k} \times 10V = 1.8V, \quad R_{Th} = R_1 \parallel R_2 = 1.8k$$

Assuming the BJT to be in the active mode.

$$\text{KVL: } V_{Th} = R_{Th} I_B + V_{BE} + R_E I_E = R_{Th} I_B + V_{BE} + (\beta + 1) I_B R_E$$

$$\rightarrow I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (\beta + 1) R_E}, \quad I_C = \beta I_B = \frac{\beta (V_{Th} - V_{BE})}{R_{Th} + (\beta + 1) R_E}$$

For $\beta = 100$, $I_C = 1.07 \text{ mA}$
 For $\beta = 200$, $I_C = 1.085 \text{ mA}$

Here is an improved circuit. And we will see that dependence of I_C or V_{CE} on the transistor beta and the circuit is much bigger than the previous circuit. To analyze the circuit let us redraw. So, what we have done here is instead of showing V_{CC} like that we have drawn that explicitly, and let us check that the circuit is still the same as before. From the base we have R_1 going to V_{CC} here from the base we have R_1 going to V_{CC} . This node is the common node or ground shown here. From the collector we have R_C going to V_{CC} same thing here collector R_C and then V_{CC} .

So, these 2 circuits are actually the same. Now what we will do is to look at this part and find the Thevenin equivalent circuit. What is the Thevenin resistance? Let us deactivate this independent voltage source and then we see R_1 and R_2 in parallel. So, that is R_{Th} . What about V_{Th} ? The open circuit voltage here; so imagine that nothing is connected here and then this voltage is R_2 divided by R_1 plus R_2 times V_{CC} . So, that is our V_{Th} . So, after making that transformation we get this circuit.

Let us calculate V_{Th} and R_{Th} . V_{Th} is R_2 by R_1 plus R_2 times V_{CC} . R_2 is 2.2 k R_1 is 10 k. So, V_{Th} is 2.2 by 10 plus 2.2 times 10 volts. And that turns out to be 1.8 volts. What about $R_{Thevenin}$? $R_{Thevenin}$ is R_1 parallel R_2 ; so 10 k parallel 2.2 k and that turns to 1.8 k. And now we know everything about circuit here. And let us now write KVL equation for this loop assuming that the BJT in active mode. So, what does KVL say, KVL says that this voltage drop V_{Th} is the sum of 3 voltage drops R_{Th} times I_B the first term here V_{BE} about 0.7 volts the second term here and R_E times I_E the third term here. Now I_E is bet plus 1 times I_B and therefore, we can write KVL as V_{Th} equal to R_{Th} times I_B plus V_{BE} plus beta plus 1 I_B times R_E .

We can now solve this equation for I_B . And we get I_B equal to V_{Th} minus V_{BE} divided by R_{Th} plus beta plus 1 times R_E . Now I see the collector current in the active mode it is simply I_B times beta. And therefore, we get this expression for I_C ; all we need to do is simply multiply this expression here by beta. Now let us calculate the collector current for beta equal to 100 first and that turns out to be 1.07 mill amperes. If we increase beta to another value let us say 200 then I_C turns out to be 1.085 mill amperes. And we notice that there is hardly any difference between these 2 numbers for all practical purposes they are the same. And this of course, is a big improvement over the previous circuit in which I_C was very sensitive to the value of beta.

Here we have changed beta by a factor of 2 and see hardly any difference in the collector current value. So, this is a big advantage of this configuration and it is therefore, commonly used for amplification.

(Refer Slide Time: 05:26)

BJT amplifier: improved biasing scheme (continued)

With $I_C = 1.1 \text{ mA}$, the various DC ("bias") voltages are

$$V_E = I_E R_E \approx 1.1 \text{ mA} \times 1 \text{ k} = 1.1 \text{ V},$$

$$V_B = V_E + V_{BE} = 1.1 \text{ V} + 0.7 \text{ V} = 1.8 \text{ V},$$

$$V_C = V_{CC} - I_C R_C = 10 \text{ V} - 1.1 \text{ mA} \times 3.6 \text{ k} \approx 6 \text{ V},$$

$$V_{CE} = V_C - V_E = 6 - 1.1 = 4.9 \text{ V}.$$

Having obtained I_C equal to 1.1 milliamps let us now proceed and get the other quantities of interest. What about V_E ? V_E is I_E times R_E and I_E is nearly equal to I_C because our beta is large enough, about 100 and if beta is 100 then alpha is beta divided by beta plus 1 or 100 divided by 101 that is very close to 1 and therefore, we can say that I_C and I_E are nearly the same. So, we will use for I_E 1.1 mill ampere. So, that times one k is 1.1 volts. And that is what is indicated over here. What about V_B ? V_B is V_E plus these voltages drop which is 0.7; so 1.1 plus 0.718 volts.

What about V_C ? V_C is V_{CC} minus $I_C R_C$. V_{CC} is 10 I_C is 1.1 million R_C is with 3.6 k. So, that turns out to be 6.6 volts. And now we see immediately that the BJT is actually at operating in the active mode. NPN, P is at 1.8 volts. N is at 6 volts. So, N is higher than P. So, therefore, the base collector junction is under reverse biased. So, that tells us that the BJT is operating under operating in active mode or linear region. What about this voltage difference V_{CE} ? 6 volts minus 1.1 So, that turns out to be 4.9 volts.

(Refer Slide Time: 07:18)

BJT amplifier: improved biasing scheme (continued)

A quick estimate of the bias values can be obtained by ignoring I_B (which is fair if β is large). In that case,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{22k}{10k + 22k} \times 10V = 1.8V$$

$$V_E = V_B - V_{BE} = 1.8V - 0.7V = 1.1V$$

$$I_E = \frac{V_E}{R_5} = \frac{1.1V}{1k} = 1.1mA$$

$$I_C \approx I_E = I_B = 1.1mA$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 10V - (1.1mA \times 1k) - (1.1mA \times 1k) = 5V$$

M. S. Park @ Nanyang

There is a way to quickly estimate the bias values. If we assume that beta is very large same finite, and what is the implication of large beta? The base current I_B is I_C over beta and if beta is large then the base current is small. So, what we are going to do is ignore the base current which is fair if beta is large. And in that case this current is 0 negligibly small and therefore, these 10 volts gets divided between R_1 and R_2 . This is like an open circuit. So, there is no current there and then we can obtain V_B simply by voltage division R_2 by R_1 plus R_2 R_2 by R_1 plus R_2 times V_{CC} .

So, that turns out to be 1.8 volts. Once we get V_B we know that the base emitter junction is under forward bias. So, there is a voltage drop of 0.7 volts there. So, 1.8 minus 0.7 that is 1.1 volts I_E once we get V_E , I_E is simply V_E divided by R_E , R_1 point one milliamp. And if beta is large then alpha is equal to 1 and I_C and I_E R then equal. So, I_C is alpha times I_E nearly equal to I_E that is 1.1 milliamp. And then we can quickly find V_{CE} . V_{CC} minus $I_C R_C$ time minus $I_E R_E$. V_{CC} minus this voltage drop minus this voltage drop that is V_{CE} .

So, that is 10 minus 3.6 k times 1.1 milliamp that is $I_C R_C$ minus 1 k times 1.1 milliamp that is $I_E R_E$. And that turns out to be 5 volts. So, there is a slight difference here. The earlier V_{CE} was 4.9 when we actually consider the value of beta about 100. And if you consider beta to be very large then it is 5 volts. So, 4.9 there and 5 here not a big difference and very often this quick estimate of the bias values is very helpful.

(Refer Slide Time: 09:53)

Adding signal to bias

- As we have seen earlier, the input signal $v_s(t) = \hat{V} \sin \omega t$ (for example) needs to be mixed with the desired bias value V_B so that the net voltage at the base is $v_B(t) = V_B + \hat{V} \sin \omega t$.
- This can be achieved by using a coupling capacitor C_B .
- Let us consider a simple circuit to illustrate how a coupling capacitor works.

M. S. Ravi Kumar

We have now found a reasonably good biasing scheme which is insensitive to the transistor beta value. And now the next challenge is to add the signal to the bias. So, here in this circuit there is no signal anywhere. There are only DC quantities or bias quantities not to that we want to add the signal. If we cannot add the signal of course, the whole amplifier is useless because then it will not be amplified. So, the input signals V_s of t which is typically taken as a sinusoidal. For example needs to be mixed with the desired bias value V_B , so that the net voltage at the base this voltage is the DC component which we have already computed in the last slide and in that example it was 1.8 volts plus the signal.

Now, the signal we have taken as a sinusoidal, but in general it need not be a sinusoidal for example, we have any audio application then it is not one signal frequency, but whole bunch of frequencies, with it is different Fourier components and so on, So, if you lo at the audio signal in time domain it will lo very different from a pure sinusoidal, but for simplicity of analysis we often take $V \text{ cap } \sin \omega t$ as the input signal. So, let us proceed with that.

So now, the challenge is to mix these 2. And this can be done by using the coupling capacitor C_B ; the coupling capacitor here. So, we have the signal here $V \text{ cap } \sin \omega t$ for example, and we have the rest of the amplifier. And we connect the signal to the rest of the amplifier with this coupling capacitor. It is called coupling capacitor because it

couples the signal to the amplifier. And how does it work. So, let us explain that by considering a simple circuit that will illustrate this idea of a coupling capacitor.

(Refer Slide Time: 12:18)

RC circuit with DC + AC sources

We are interested in the solution (currents and voltages) in the "sinusoidal steady state" when the exponential transients have vanished and each quantity $x(t)$ is of the form X_0 (constant) + $X_m \sin(\omega t + \alpha)$.

There are two ways to obtain the solution:

(1) Solve the circuit equations directly:

$$\frac{v(t)}{R_1} + \frac{v(t) - V_0}{R_2} = C \frac{d}{dt} (v(t) - v_0(t))$$

(2) Use the DC circuit + AC circuit approach.

M. S. Elshorbagy

Let us start with this simple R C circuit. Let us leave the BJT aside for the moment because it makes life more complicated and for this R C circuit we have 2 sources one is DC source V_0 and one is sinusoidal source $V_m \sin \omega t$. And we are interested in the solution. What do we mean by the solution currents and the voltages in the circuit in the sinusoidal steady state? And we have come across this term earlier what is sinusoidal steady state that is when the exponential transients are vanished. And the exponential transients arise because we have a time constant in this circuit.

So, there will things like $e^{-t/\tau}$ raise to things like $\sin t$ by τ . And if t is sufficiently large then those terms would go to 0 and that is what we mean by the exponential transients have vanished. So, after that has happened each quantity X of t could be able to, it could be this voltage it could be this current is of the form the constant X_0 plus a sinusoid. And the sinusoid has amplitude of X_m and a phase of α .

Our job now is to find X_0 and X_m and α ; that means the complete solution for X of t in the sinusoidal steady state. There are 2 ways of going about it. One solves the circuit equations directly let us see how to do that, let us say that this node voltage is v sub a , and this is total voltage that is it has constant part as well as a sinusoidal part. Now this


Similarly, we have current given by a constant plus sinusoidal varying part. And we are considering the sinusoidal steady state in a circuit and this resistor is part of that circuit. And we know that for resistor the total instantaneous voltage is simply R times the total instantaneous current, and when we substitute for PR and IR, we get this relationship. And we can split this into 2 equations one capital V capital R times IR this part, and small v and small i is R times small i small R. These are the DC quantities VR and IR and these sinusoidal varying quantities.

In other words, we can think of a resistor, in this situation where there is DC and sinusoidal part, to be described by 2 circuits a DC circuit and an AC circuit in the DC circuit we have the DC quantities capital V capital R and capital I capital R they are related by this equation which is the resistor equation. Then we have the AC circuit in which we have small v small R the sinusoidal varying part small i small R again the sinusoidal varying current and they are also related by the same behavioral equations. So, small v small R is R times small i small R.

So, in the DC circuit as well as in the AC circuit the resistor essentially looks the same. It behaves like a resistor and the relationship is V equal to R times i where V and i could be either DC quantities or they could be the sinusoidal varying quantities.

(Refer Slide Time: 18:56)

Capacitor in sinusoidal steady state




Let $v_C(t) = V_C + v_c(t)$ where $V_C = \text{constant}$, $v_c(t) = \hat{V}_C \sin(\omega t + \alpha)$.
 $i_C(t) = I_C + i_c(t)$ where $I_C = \text{constant}$, $i_c(t) = \hat{I}_C \sin(\omega t + \beta)$

Since $i_C(t) = C \frac{dv_C}{dt}$, we get $[I_C + i_c(t)] = C \frac{d}{dt} (V_C + v_c(t))$

This relationship can be split into two:

$I_C = C \frac{dV_C}{dt} = 0$, and $i_c(t) = C \frac{dv_c}{dt}$

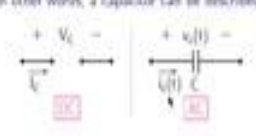In other words, a capacitor can be described by



M. S. Park @ IIT Bombay


Let us repeat it for the capacitor now. So, we have again total instantaneous voltage a DC part, and a sinusoidal part total instantaneous current a DC part and a sinusoidal part. So,

these are constants and these varies sinusoidal and because the capacitor involves derivative we have made this alpha and beta different, and at this stage we do not know what the relationship between alpha and beta is, but we will find out.

Now, since total instantaneous current i_C is the derivative of the total instantaneous voltage. We substitute for i_C like that and for v_C like that, and now we can once again split this equation into 2, the first one relating the DC quantities I_C is equal to $C \frac{d}{dt} V_C$ and that is 0 because C is a constant. The second equation this small i_C is $C \frac{d}{dt}$ of small v_C , that is the second equation. And this equation looks pretty much like capacitor equation. And what does this correspond to, this is saying that the DC current is 0 so; that means, in the DC situation the capacitor is an open circuit, not surprising and in the AC situation or the sinusoidal situation, we have the same equation as we would have for the total instantaneous quantities.

So, the capacitor in this situation in the AC situation looks like a capacitor. And can we now figure out what is the relationship between alpha and beta, we can turn this into a phasor, and then go through the phasor analysis and then we will see that the current leads the voltage and therefore, they are related by beta equal to alpha plus pi by 2.

(Refer Slide Time: 21:25)

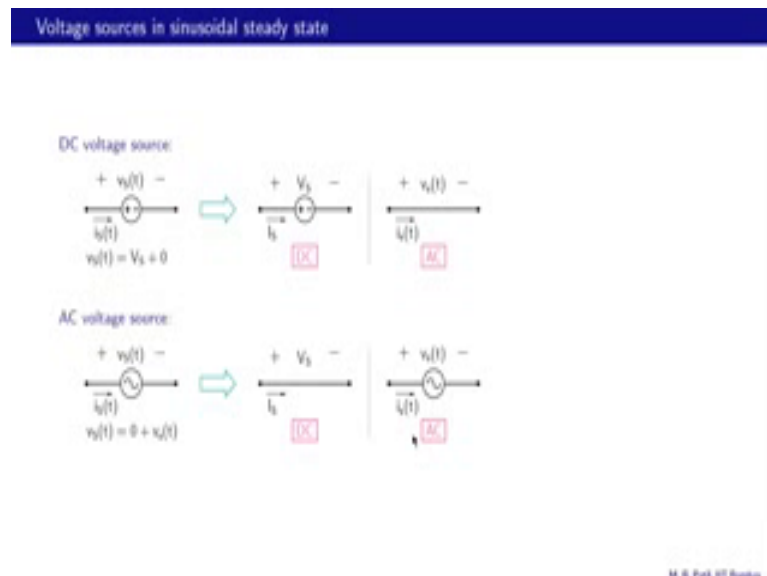

What about a DC voltage source? The equation is the total instantaneous voltage is a constant and because it is a constant there is no sinusoidal varying part that is 0 and So, in the DC circuit we have that constant voltage source and in the AC circuit we have

voltage equal to 0, that is a short circuit. And the DC current capital I capital S is shown in the DC circuit and the sinusoidal current of the AC current is shown in the AC circuit that is small I sub small s.

Let us look at an AC voltage source. The equation is the total instantaneous voltage is 0 DC plus the sinusoidal part, the time varying sinusoidal. Now since the DC part is 0 the DC circuit simply has V_A is equal to 0 which is a short circuit and sinusoidal is then incorporated in the AC part. So, the AC circuit is simply voltage source an I C source and the I C circuit is a short circuit. Once again the DC current is shown in the DC circuit, capital I capital S and the AC or the sinusoidal current is shown in the AC circuit small I sub small s.

(Refer Slide Time: 23:10)

RC circuit with DC + AC sources

DC circuit: $\frac{V_A}{R_1} + \frac{V_A - V_S}{R_2} = 0$ (1)

AC circuit: $\frac{v_a}{R_1} + \frac{v_a - v_s}{R_2} = C \frac{d}{dt} (v_a - v_s)$ (2)

Adding (1) and (2), we get $\frac{V_A + v_a}{R_1} + \frac{V_A + v_a - V_S - v_s}{R_2} = C \frac{d}{dt} (v_a - v_s)$ (3)

Compare with the equation obtained directly from the original circuit

$$\frac{V_A + \frac{v_a - V_S}{R_2}}{R_1} = C \frac{d}{dt} (v_a - v_s)$$
 (4)

Eqs. (3) and (4) are identical since $v_a = V_A + v_s$

→ Instead of computing $v_a(t)$ directly, we can compute V_A and $v_s(t)$ separately and then use $v_a(t) = V_A + v_s(t)$.

M. S. Fall 07, Boston

We can now use the findings in our original R C circuit. So, we replace R 2 with it is DC equivalent which is also registered and the AC equivalent that is also a resistor. Similarly, for R 1 what about the capacitor; the capacitor as we have seen in the DC circuit it is an open circuit and in the AC circuit it looks like a capacitor the DC source in the DC circuit is a DC source and in the AC circuit is a short circuit 0 volts. Similarly, the AC source is a short circuit in the DC circuit and in the AC circuit it is the sinusoidal source. So, we have split the original circuit into DC circuit and an AC circuit and we know how to get these from the original circuit by systematically replacing each of the components.

Now, let us write equations for these 2 circuits the DC and AC circuits for the DC circuit. We have V_A over R_1 this V_A over R_1 that current plus V_A minus V_0 by R_2 V_A minus V_0 by R_2 that current, and they should add up to 0, because this is an open circuit remember capital B so capital A is a constant voltage. For the AC circuit we have small V sub small divided by R_1 that current plus this current which small V small a divided by R_2 . So, that is the sum of those 2 currents, that current and that current. And let us remember that this quantity is sinusoidal varying quantity and it has no constant in it.

Now these 2 currents the addition of these 2 must be equal to the capacitor and that is given by $C \frac{d}{dt} V_s$ minus V_A . So, that is the equation we get for the AC circuit. If we add equations one and 2, we end up with equation 3 here, and what is it saying it is saying that the DC b a plus a $C \frac{d}{dt} V_s$ divided by R_1 that is the total instantaneous current plus the DC b a plus a $C \frac{d}{dt} V_s$ minus V_0 divided by R_2 , that is the total instantaneous current through R_2 should be equal to $C \frac{d}{dt} V_s$ minus V_A , and both of these are sinusoidal quantities.

Let us compare this equation with what we had obtained earlier directly from the original circuit. And that equation is here this is the total instantaneous quantity. This is also the total instantaneous quantity. This is instantaneous V_A minus V_0 . This is also the instantaneous V_A minus V_0 . And what about this capacitor current $C \frac{d}{dt} V_s$ minus the instantaneous V_A , now this instantaneous V_A has 2 parts one is a constant part and one is the sinusoidal part. And the derivative of the constant part of course, is 0 and therefore, we get the same terms as this one here.

So, in other words equation 3 and 4 are actually the same. And this a very powerful statement because now instead computing V_A directly from equation 4 we can compute the constant part using equation 1 the sinusoidal part using equation 2 and then use the instantaneous V_A as the sum of DC V_A and the AC V_A . We can do this computation separately and that is big advantage and then just simply add them to get the total quantity. So, this is very useful approach splitting the original circuit into a DC part and then AC part. Working on the DC circuit and the AC circuit separately it turns out to be much simpler than the than working on the original circuit and then simply adding the 2 solutions to get the total instantaneous quantities.

To summarize we looked at the robust BJT biasing scheme and showed that it is relatively insensitive to the beta of the transistor. We then discussed the use of a coupling capacitor to couple the signal voltage to the amplifier. We have considered an R C circuit to explain how a coupling capacitor works. In the next class we will consider a BJT amplifier with the coupling capacitor. So, see you next time.