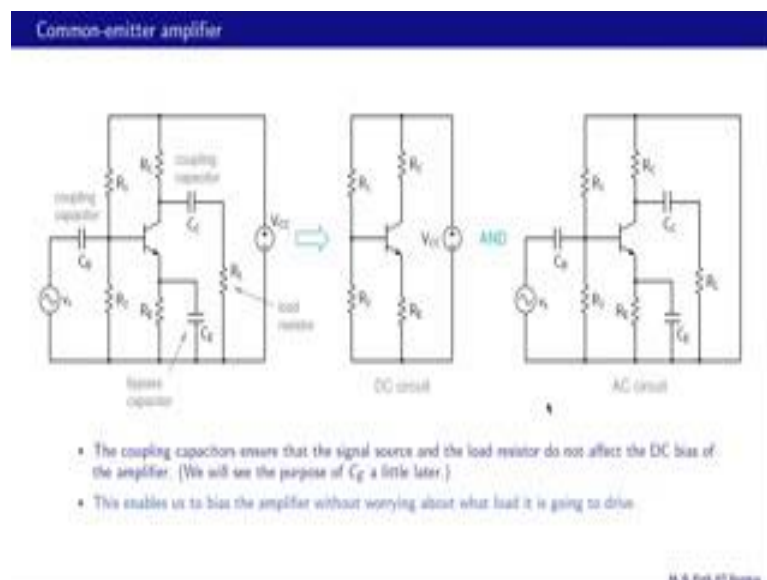


Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture – 28
BJT amplifier (continued)

Welcome back to Basic Electronics. In this lecture our main focus is the small signal equivalent circuit of a BJT. First we will explain the meaning of the term small signal condition. We will then derive the most basic form of the BJT small signal model. And explain how it is related to the bias quantities, in particular the bias value of the collector current. So, let us begin.

(Refer Slide Time: 00:44)



We are now in a position to look at the complete common emitter amplifier circuit shown here. And remember that we have actually considered this part earlier already when we look at biasing of the amplifier, and now all of these things are added on top of it. So, there is a coupling capacitor here going to the source voltage then there is another coupling capacitor and that is how the load is connected the load resistor. And there is a third capacitor which we call the bypass capacitor and that is going from the emitter to the ground. We will treat this as the common reference node or the ground. And now let us see what the DC circuit for this amplifier is and the AC circuit for the amplifies.

Thus the DC circuit and how do we get this. We recall that the capacitor is an open circuit in the DC situation. So, this capacitor is an open circuit and so is this and this. So, therefore, this R_L is not essentially, not in the circuit V_s is not in the circuit and this is an open circuit and that boils down to this circuit here. Then that is the DC circuit what about the AC circuit, AC circuit is here the resistors remain as resistors as we have seen earlier, capacitors also remain as capacitors. The AC source remains as AC source, and the DC source it is replaced with the short circuit. So, that is what we have got for the AC circuit.

What about the transistor. That is still big a question mark and we have to of course, tackle that question V_s 1 otherwise we really cannot proceed further, but what we see already is that this DC circuit is identical to the one that we considered when we talked about biasing. So, the coupling capacitors ensure that the signal source and load resistor do not affect the DC bias of the amplifier and that is a very big advantage because we do not need to worry about what we are going to have as a load resistance or what source voltage is going to drive this amplifier, when we design the biasing components. And as we said let us look at the purpose of CE a little later that is not a coupling capacitor that is a bypass capacitor, and just repeating it once again this fact that the DC circuit is not affected by either V_s or R_L enables us to bias the amplifier without worrying about what load it is going to try.

So, that is a big benefit and the next step now is to look at what this AC circuit how that can be simplified.

(Refer Slide Time: 04:18)

Common-emitter amplifier: AC circuit

- The coupling and bypass capacitors are "large" (typically, a few μF), and at frequencies of interest, their impedance is small.
For example, for $C = 10\ \mu\text{F}$, $f = 1\ \text{kHz}$,
$$Z_C = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-6}} = 16\ \Omega$$
which is much smaller than typical values of R_1 , R_2 , R_C , R_E (a few $\text{k}\Omega$).
 $\Rightarrow C_B$, C_C , C_E can be replaced by short circuits at the frequencies of interest.
- The circuit can be re-drawn in a more friendly format.
- We now need to figure out the AC description of a BJT.

M. S. Park @ Samsung

Here is the AC circuit once again. Now it turns out that the coupling and bypass capacitors are large typical a few micro farads R_1 tens of micro farads. And at the frequencies of interest their impedance turns out to be small. Let us take an example say C is 10 micro farads and f is 1 kilo hertz at this frequency the impedance of the capacitor is one over omega C in magnitude. Omega is 2 pi times one kilo hertz and C is 10 times 10 raise to minus 6. So, that turns out to be only 16 ohms. And this impedance is much smaller than typical values of the resistances in the circuit like R_1 , R_2 , R_C , R_E which are in the range of a few kilo ohms. And therefore, what we can do is we can replace these capacitors C_B , C_C and C_E with short circuits because their impedance is so, small. And let us see what we get in that case.


So, this is what the circuit reduces to. What have we done we have replaced C_B with the short circuit C_C also with the short circuit and C_E also with the short circuit. And because of that what has happened is this emitter has got effectively connected to the ground directly bypassing this R_E resistor like that. And now it is clear why this capacitors C_E is called the bypass capacitor.

Now, this circuit can be redrawn in a more friendly format and let us do that like that. And let us first check that these 2 circuits are actually the same. Let us start with the transistor. Here is a transistor from the base we have V_s going to ground R_1 going to ground and R_2 going to ground. What about this case? Here is the base here R_2 going

to ground V_s going to ground and R_1 also going to ground, because we have a short circuit here. What about the collector? From the collector we have R_C and R_L connected in parallel and going to ground. Here from the collector we have R_L going to ground and also R_C going to ground. And the emitter is connected directly to ground in both cases all right. So, these 2 circuits are indeed identical and we can proceed further.

The next question now is, what is the AC description of the BJT? So, let us look at that in the next slide.

(Refer Slide Time: 07:33)

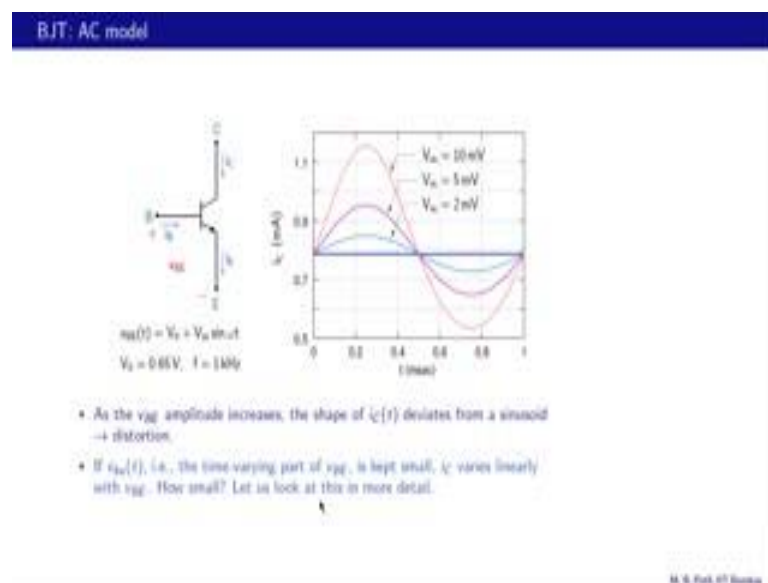

So, the question we want to answer now is what is the transistor behavior when a sinusoidal input voltage is applied and super imposed on DC bias value. In particular, we will look at the base emitter voltage of this form, where V_0 is a constant, let us say 0.65 volts corresponding to a forward bias. And on top of that there is this sinusoidal id with the frequency of let us say f equal to one kilo hertz. And in this graph we have plotting I_C the collector current, the total collector current as a function of time. And we are only showing one cycle of the input waveform which corresponds to one millisecond. Let us look at these curves one by one.


So, this is blue curve corresponds to V_{BE} equal to V_0 , and with now sinusoidal part there. So, it is just V_0 constant. And that is why the collector current is also a constant. If you apply V_B equal to the same constant plus $V_m \sin \omega t$ with V_m equal 2 millivolts, this is what. We get if we increase that amplitude V_m to 5 millivolts this is

what we get. And if we increase it further to 10 millivolts this is what we get. And as we are looking at these closely you will surely notice some difference in the shape of these 3 curves. As V_{BE} varies with time we expect I_C of t also to vary with time, and when V_{BE} increases above the base value V_0 then I_C will go above this base value that is the DC collector current corresponding to base emitter voltage of V_0 . And when the base emitter voltage goes below V_0 , then we expect the collector current to go below that I_C , DC value here and that is what is happening.

Now, in this case when V emits 2 millivolts, we can see that these positive and negative excursions are equal and that is what the sinusoid should like. But if we increase V_m to 10 millivolts we see that this positive excursion is larger this difference here than the negative excursion. And clearly therefore, there is some distortion in the collector wave form for V_m equal to 10 millivolts. So, that is the first point we make. As the V_B amplitude increases the shape of I_C t deviates from a sinusoidal and that causes distortion.

Now, suppose we want to write an equation for this I_C of t only the time varying part of this I_C of t . What would that look like? It would be sinusoidal and its amplitude would be that height over there. So, it would be some $I_C \text{ cap sin } \omega t$. And that is exactly the same form as the time varying part of the base emitter voltage. So, in other words the time varying parts or the sinusoidal part of the collector current and the base emitter voltage are proportional to each other. And that is the second point we want to make. If V_{BE} of t that is the time varying part of V_{BE} is kept small when I_C varies linearly with V_{BE} . And the next question that arises is how small. Let us look at that in more detail in the next slide.

(Refer Slide Time: 12:34)

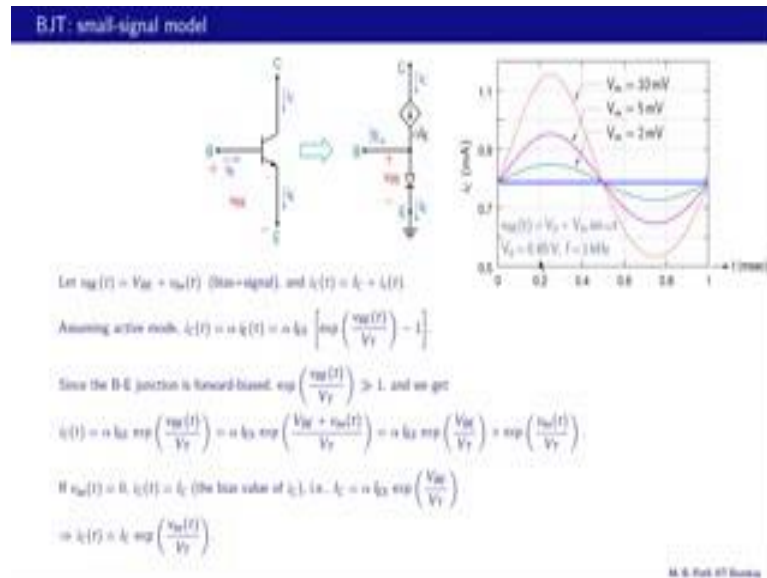

Here is the graph again of the collector current versus time. And the base emitter voltage is constant which is 0.65 plus $V_m \sin \omega t$ and the frequency is one kilohertz. And the base collector junction for these calculations was assumed to be under reverse biased, the exact value of the reverse bias is of course, is not important. Now in these conditions that is in the active mode or in the linear region the device model as we have seen before is given here; the base emitter diode and then the controlled current source. If this is IE that is α times IE . So, we are of course, very familiar with this model manner.

Let us start with V_{BE} in the instantaneous base emitter voltage equal to the constant part and the time varying part. In this case $V_m \sin \omega t$ and the constant part of course, we call as the bias and the time varying part is the signal. And similarly the collector current also would be a constant part plus a time varying part. And assuming active mode the collector current is α times IE of t . And what is IE ? It is $I_S e^{\frac{V_{BE}}{V_T}}$ minus one this is the total instantaneous base emitter voltage that is the total instantaneous emitter current and this is of course, simply special case of the Ebers moll model as we have seen earlier.


Now, since the base emitter junction is forward biased, this term will be much larger than this one here, and we can simply ignore that one and get I_C of t is equal to α times $I_S e^{\frac{V_{BE}}{V_T}}$. This is same as that one except we are not written that one there equal to α times I_S . Now this V_{BE} the instantaneous voltage

we are going to substitute with V_{BE} plus the busy part plus the time varying part like that. And now this is like e^{a+b} which is $e^a \times e^b$ and that brings us to this equation I_C of t is αe^s times $e^{V_{BE}}$ by V_T this is the constant V_{BE} or the biased value of V_{BE} times $e^{V_{BE}}$ of t divided by V_T this is the time varying V_{BE} this part here.

now if V_{BE} the small case of small b e^b is 0 if this time varying part is 0 then what do we have for base emitter voltage it is simply this constant value in our example 0.65 and then if we substitute that here I_C of t this becomes one and we are left with α times I_{ES} times exponential V_{BE} by V_T . So, 0.65 divided by V_T and that is the bias value of I_C with no signal and that is shown here in the dark blue curve just constant straight line. So, if V_{BE} is 0 if the signal is 0 then the total instantaneous current collector current is the bias value of the collector current that is I_C capital I of capital C the DC part of I_C here is α times I_{ES} times $e^{V_{BE}}$ by V_T .

And now this part is also appearing here and therefore, we can say that I_C of t is instead of writing this expression, we just write I_C and that multiplied by $e^{V_{BE}}$ by V_T , where V_{BE} is the signal V_{BE} . So, from all of this algebra we get I_C of t that instantaneous collector current is the DC or bias collector current multiplied by $e^{V_{BE}}$ of t divided by V_T . So, in this term there is only the time varying component of V_{BE} , in this term there is only the constant component of V_{BE} . Let us remember that and let us go further with this.

(Refer Slide Time: 18:18)

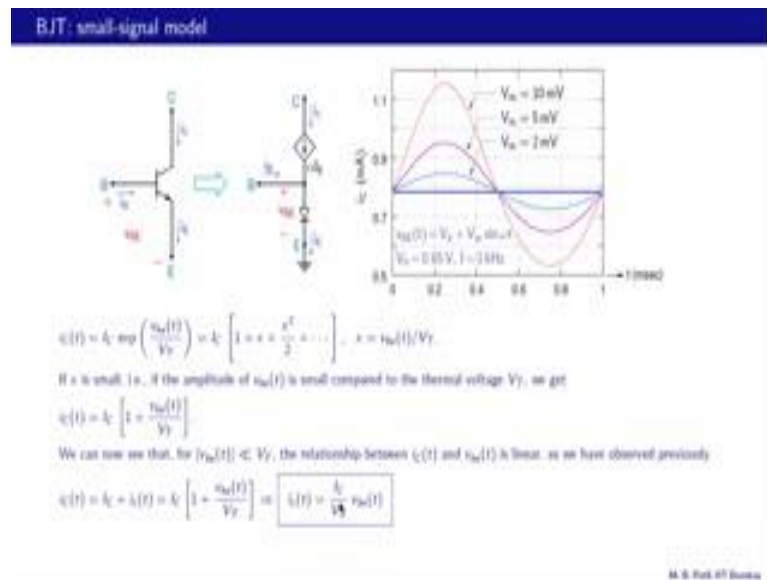

Here is the relationship between I_C and V_{BE} . Once again this quantity is the total instantaneous collector current it includes the both DC and the signal collector current. This capital I_C is the DC or biased value of the collector current, this V_{BE} is the signal base emitter voltage, it does not include the bias or DC base emitter voltage all right. Let us now take a specific example say, this one, where V_{BE} is given by $V_m \sin \omega t$ with V_m equal 2 millivolts. Let us define a variable x as V_{BE} by V_T where V_T is the thermal voltage 26 millivolts and V_{BE} of t in this particular case it is going to be limited to 2 millivolts in magnitude. So, this magnitude of x is always going to be smaller than 2 millivolts divided by 26 millivolts. Say one by 12 all right. Now what we will do is expand this e^x using the Taylor's series and this is what we get. Since our x is small in magnitude compared to one we can ignore terms like x^2 by $2x$ cube by 6 and so on as compared to x , and therefore we get I_C of t as approximately equal to I_C times $1 + x$.


So, in summary if x is small that is if the amplitude of V_{BE} the signal part of the base emitter voltage is small, compared to the thermal voltage V_T . Then we get I_C of t the total instantaneous collector current equal to I_C which is the DC or bias current times $1 + x$ and x is V_{BE} divided by V_T . Let us now write the total instantaneous collector current as the sum of DC collector current and the signal collector current. So, this is our left hand side here. This is the right hand side.

The DC collector current cancels out and we get I_C of the signal collector equal to I_C by V_T where this I_C is the DC or bias collector current times the signal base emitter voltage as a function of time. What does this equation say? This equation says that the signal collector current is directly proportional to the signal base to emitter voltage because these quantities are constants. Note that the collector current does depend on the base to emitter voltage, but only on the constant part of the base to emitter voltage, namely 0.65 volts in this case. So, this relationship looks like I_C of t equal to k times V_{BE} of t where k is simply a constant which does not depend on time.

What are the implications of this equation? It says that if x is small, that is if the amplitude of the signal base to emitter voltage is small compared to V_T then the signal collector current is directly proportional to the signal base to emitter voltage. If V_{BE} of t is sinusoidal as in this case and if the amplitude of V_{BE} is small, then we expect the collector current also to be sinusoidal. And that is indeed what we observed in this case which corresponds to an amplitude V_m of 2 millivolts for the base to emitter voltage which is small compared to the thermal voltage about 25 millivolts.

Now, let us take this case where the amplitude of the base to emitter voltage is larger 10 millivolts. The maximum value of x now is 10 millivolts by 25 millivolts. That is 0.4 and that is not small any more with respect to one. So, what; that means, is we cannot ignore these higher order terms with respect to x . And that shows up as distortion over here. Now this condition in which the variation of base to emitter voltage is small compared to the thermal voltage V_T is called the small signal condition. And it is very important to keep in mind that this equation which we have derived is only valid if the small signal condition is satisfied. So, it is under this condition that we will now derive the BJT small signal model.

(Refer Slide Time: 23:57)

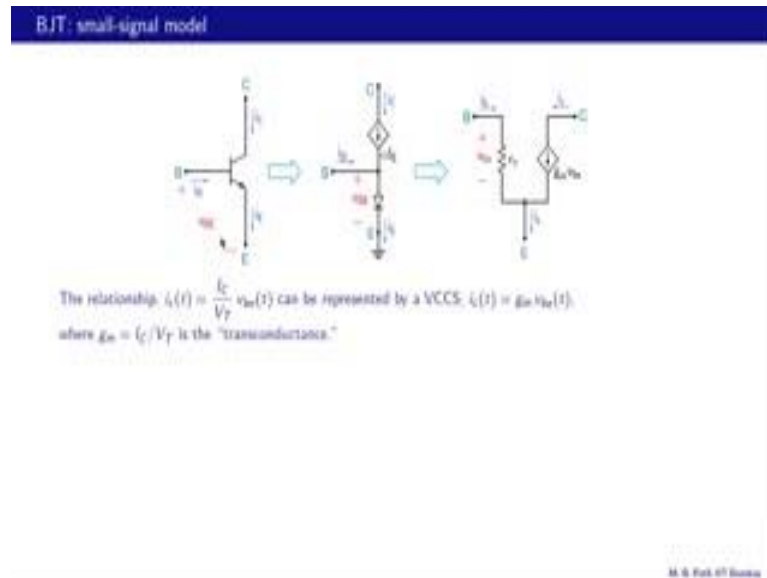

And that brings us to the small signal model of the BJT, and it is now clear why it is called small signal. Because the base emitter signals voltage must be small as compared to the thermal voltage V_T . And then we have this relationship that we saw in the last slide.

Now, this equation can be rewritten as I_C of t the signal part equal to V_{BE} of t times g_m where g_m is I_C by V_T . Now g_m is a constant because I_C is a constant for a given bias condition that is for a given bias value of the base emitter voltage and V_T is a constant. So, this g_m which is the I_C by V_T is called the trans conductance parameter of the transistor. And it is very important to remember that it is not an absolute constant because it depends on the bias condition in particular it depends on the bias value of the base emitter voltage.

To summarize we have addressed a very important issue in this lecture namely the small signal condition in the context of a BJT and its applications. We have derived the hybrid pi model of the BJT under the small signal condition. In the next class we will put all these findings together and look at the complete small signal circuit for the common emitter amplifier, until then goodbye.