

Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture – 37
Instrumentation amplifier

Welcome to Basic Electronics. In the last class we are seen how difference amplifier works, we have also seen that its input resistance is relatively small and why that is not desirable. In this class we will continue with the difference amplifier and consider the effect of resistance mismatch on this common mode rejection performance. We will first consider a simple case in which only one resistance value deviates from its nominal value, after that we will consider a more general case where all resistances are allowed to vary to the extent given by the tolerance specified by the manufacturer. Let us start.

(Refer Slide Time: 01:05)

Difference amplifier

Consider the difference amplifier with $R_3 = R_1$, $R_4 = R_2 \rightarrow v_o = \frac{R_2}{R_1}(v_2 - v_1)$

The output voltage depends only on the differential mode signal ($v_2 - v_1$).
 i.e. A_c (common mode gain) = 0

In practice, R_3 and R_1 may not be exactly equal. Let $R_3 = R_1 + \Delta R$.

$$v_o = \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1 = \frac{R_2}{R_1 + \Delta R + R_2} \left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1$$

$$\approx \frac{R_2}{R_1} (v_2 - v_1), \text{ with } x = \frac{\Delta R}{R_1 + R_2} \quad (\text{show this})$$

$|A_c| = \frac{\Delta R}{R_1 + R_2} \frac{R_2}{R_1} \ll |A_d| = \frac{R_2}{R_1}$ However, since v_1 can be large compared to v_2 , the effect of A_c cannot be ignored.

M. S. Patil IIT Bombay

Let us consider this difference amplifier with R_3 equal to R_1 , and R_4 equal to R_2 . As we have seen before V_o is R_2 by R_1 times V_{i2} minus V_{i1} . So, in this formula the output voltage depends only on the differential mode input signal; that is V_{i2} minus V_{i1} . And in other words the common mode gain is exactly 0, there is no contribution of the common mode input signal here. That is the ideal world, in reality what happens is these resistance values are not exact; for example if you want R_1 equal to 1 k it would not be

exactly 1 k. If you use 1 percent resistances then R_1 would be anything between 0.99 k to 1.01 k.

So, in real life these resistance values are not exactly what we intend them to be, and therefore R_3 and R_1 may not be exactly equal. So, let us take this simple case where R_4 is exactly equal to R_2 , but R_3 is not exactly equal to R_1 ; and let R_3 be R_1 plus some small ΔR . In this case our v_o also will get modified, and let us see what that is. If you recall our final expression came from this expression here and now for R_4 we can use R_2 and for R_3 we can use R_1 plus ΔR and then we get this expression here. And now we do some algebra which of course you need to do and arrive at this final result.

What we do in short is take R_1 plus R_2 common here from the denominator and then we end up with $1 + x$ in the denominator; where x is ΔR over $R_1 + R_2$. Then we use the approximation that one over $1 + x$ is approximately $1 - x$. And finally, we use these definitions. After all that algebra we end up with this expression here for v_o ; R_2 by R_1 v_d is the differential input mode signal minus x times v_c , v_c is the common mode input signal.

Now, this part is the same as before R_2 by R_1 times v_d , R_2 by R_1 times v_d but now we have added this common mode part and therefore the common mode gain is not 0 anymore. From this result how do we get the differential mode gain and the common mode gain? That is easy. For differential mode gain we put the common mode input equal to 0 and then the output voltage divided by v_d gives us the differential mode gain that is $A_{sub d}$ and that in this case is clearly R_2 over R_1 .

Similarly, to get the common mode gain what we do is we put the input differential mode voltage to be 0 that is v_d equal to 0 and then take the ratio of v_o and v_c , and then we will get R_2 by R_1 times minus x . So, that is our common mode gain. Now the minus sign is not so important, so we will not only talk about magnitudes. So, the magnitude of A_c the common mode gain is R_2 by R_1 times x ; x is ΔR divided by $R_1 + R_2$. This of course is a small number because ΔR is small compared to R_1 or R_2 and A_d the differential mode gain is R_2 by R_1 and that of course is the same as before.

So, clearly A_c is much smaller than A_d because we have this small pre multiplier here and that is good news of course, but the problem is the common mode voltage can be

much larger than the differential mode input voltage. And we have already seen an example of that in our bridge circuit. If you recall v_c was 7.5 volts there and v_d was 37.5 millivolts. In that case clearly v_c was much larger compared to v_d , and therefore the effect of A_c may not be small over all, because A_c gets multiplied by v_c and v_c is large.

(Refer Slide Time: 06:28)

Difference amplifier

$$v_0 = v_c + (v_d/2)$$

$$v_0 = v_c + (v_d/2)$$

$$[A_d] = \frac{R_2}{R_1} \quad [A_c] = \frac{R_2}{R_1 + R_2} \quad \text{where } x = \frac{\Delta R}{R_1 + R_2}$$

In our earlier example, $v_c = 7.5 \text{ V}$, $v_d = 0.0375 \text{ V}$.

With $R_1 = 1 \text{ k}$, $R_2 = 10 \text{ k}$, $x = \frac{0.01 \text{ k}}{11 \text{ k}} = 0.00091 \rightarrow [A_d] = 0.00091 \frac{10 \text{ k}}{1 \text{ k}} = 0.0091$, $[A_c] = \frac{10 \text{ k}}{11 \text{ k}} = 0.91$

$$[v_0^d] = [A_d v_d] = 0.0091 \times 7.5 = 0.068 \text{ V}$$

$$[v_0^c] = [A_c v_c] = 0.91 \times 0.0375 = 0.341 \text{ V}$$

The (spurious) common-mode contribution is substantial.

If we measure v_0 , we will conclude that $v_0 = \frac{v_d}{A_d}$, but in reality, it would be different.

\rightarrow need a circuit which will drastically reduce the common-mode component of the output.

Here is the summary: the common mode gain is x times R_2 by R_1 where x is ΔR divided by R_1 plus R_2 . And remember this ΔR came from R_3 which was assumed to be R_1 plus ΔR . The differential mode gain is R_2 by R_1 as we already seen. And now let us take a numerical example: we will take the same common mode input voltage and differential mode voltage as the bridge circuit example. So, our common mode voltage is 7.5 volts and the differential mode voltage is 0.0375 volts or 37.5 millivolts.

So, these serve as the input to our circuit V_{i1} and V_{i2} , and they are coming from a circuit like the bridge circuit we have seen earlier. Let us take R_1 as 1 k and R_2 as 10 k. So, the gain of our difference amplifier is R_2 by R_1 , so it would be 10 k by 1 k that is 10. What is x ? x is ΔR divided by R_1 plus R_2 . ΔR is let us say 1 percent of R_1 which is 0.01 k and R_1 plus R_2 is 1 k plus 10 k or 11 k. So, this x turns out to be 0.00091.

So, the common mode gain A_c is x times R_2 by R_1 there, so that multiplied by 10 k by 1 k or 0.0091. And the differential mode gain is R_2 by R_1 or 10. Clearly this A_c is very


small compared to A_d . Now let us look at the actual output voltage the common mode part of the output voltage and the differential mode part of the output voltage. Here is the common mode part which is A_c times v_c and that is 0.0091 times 7.5 or 0.068 volts; 68 millivolts.

Let us look at v_{od} now the differential mode part of the output voltage; that is A_d times v_d so that is 10 times 0.0375 that is our v_d or 0.357 volts. So, we see that this spurious common mode contribution is substantial. So, this is like 0.07 something like one-fifth of the differential mode output voltage, so it can give raise to errors. And if we measure v_o let us say we get v_o as 100 millivolts, what do we conclude? We will conclude that you are our v_d is actually v_o by A_d or 100 millivolts by 10 or 10 millivolts.

In reality that would not be quite correct because the output also as this contribution from the common mode voltage. And therefore, clearly there will be an error which we definitely do not want. So, in conclusion we need A circuit which will drastically reduce the common mode component at the output.

(Refer Slide Time: 10:32)

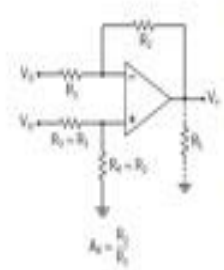Difference amplifier: resistance mismatch



$$V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{i2} - \frac{R_2}{R_1} V_{i1}$$

Let $V_{i1} = V_{i2} = V_c \rightarrow A_c = \frac{V_o}{V_c}$

$$A_c = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) - \frac{R_2}{R_1}$$

$$= \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right)$$

Assume ideal op-amp with $R_1 = R_3^0(1 + \epsilon_1)$, etc. 1% resistor $\rightarrow \epsilon = 0.01$.

$$\rightarrow A_c \approx \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2^0}{R_1^0} \frac{R_3^0}{R_4^0} (1 + \epsilon_1)\right) \times \frac{R_4^0}{R_3^0(1 + \epsilon_2)}$$

Using $(1 + \epsilon_1)(1 + \epsilon_2) \approx 1 + \epsilon_1 + \epsilon_2$ if $|\epsilon_1| \ll 1, |\epsilon_2| \ll 1$.

and $\frac{1}{1 + \epsilon} \approx 1 - \epsilon$ if $|\epsilon| \ll 1$.

$$A_c \approx \frac{R_4}{R_1 + R_4} (\epsilon_1 - \epsilon_2 - \epsilon_3 + \epsilon_4)$$

Let us now consider the general case in which all of these resistance values are allowed to be inaccurate. We will continue to take R_3 to be nominally equal to R_1 and R_4 to be nominally equal to R_2 .

So, let us begin again with our expression for v_o and see what happens if we allow all of these resistance values to be inaccurate. In particular our interest is to get the common mode gain. So, let V_{i1} be equal to V_{i2} equal to v_c the common mode voltage. In other words we are removing the effect of the differential mode input voltage on v_o . With this condition if we find v_o then our common mode gain will simply be that v_o divided by v_c . And if we substitute V_{i1} equal to V_{i2} equal to v_c here then v_o by v_c which is equal to a_{oc} the common mode gain turns out to be simply $1 + \frac{R_2}{R_1} \times \frac{R_4}{R_3 + R_4 - R_2}$.

Let us rewrite this expression as $\frac{R_4}{R_3 + R_4} \times$ this bracket, and of course you should verify that these two are actually the same. So far we have not really returned these resistances in terms of the inaccuracies or the tolerance values and we will do that now. Also we will assume that the op-amp itself is perfect in the sense it has got same R_r of infinite. So therefore, the op-amp does not have any effect on the common mode gain.

So, how do we incorporate the effect of the tolerance values in the resistances? Using this equation, for example R_1 we can write as the nominal value of R_1 which we will denote by $R_{10} \times (1 + x_1)$. And this x_1 represents the effect of the tolerance value. For example, if we are using 1 percent resistors then this x_1 can be anywhere between minus 0.01 to plus 0.01. And we do not explicitly write this plus minus sign here because that is understood.


So, with this substitution now our original expression for A_c looks like this and note that we have not really changed this pre factor it is the same as before, and we will commit on that later. But in the bracket we have replaced R_2 with $R_{20} \times (1 + x_2)$, R_3 with $R_{30} \times (1 + x_3)$ and so on. And our job now is to simplify this expression and arrive at A_c in terms of x_1, x_2, x_3, x_4 and in doing that we will find some approximation very useful.

For example if u_1 and u_2 are small compared to 1, then we can write $1 + u_1 \times 1 + u_2$ as $1 + u_1 + u_2$. And we can do that because this term $u_1 \times u_2$ is much smaller compared to any of these terms. Similarly $\frac{1}{1 + u}$ is approximately $1 - u$ if u is small compared to 1, and this is something we have already used earlier if we recall.

So, when we go through all of this algebra we end up with the following relationship A_c equal to R_4 by R_3 plus R_4 , this factor which is the same as this factor here times x_1 minus x_2 minus x_3 plus x_4 . So, this entire bracket reduces to x_1 minus x_2 minus x_3 plus x_4 and it is easy to see why we do not have $R_2 = 0$ and $R_1 = 0$ etcetera here, because $R_2 = 0$ by $R_1 = 0$ is exactly the same as $R_4 = 0$ by $R_3 = 0$. So, all these it is cancels out.

(Refer Slide Time: 15:29)

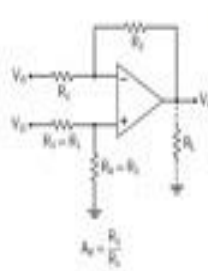Difference amplifier: resistance mismatch



$$A_c = \frac{R_4}{R_1 + R_2} (x_1 - x_2 - x_3 + x_4)$$

$$\frac{R_1}{R_1 + R_2} = \frac{R_1^2}{R_1^2 + R_2^2}$$

(1) $R_1^2 = R_2^2$ (i.e., $R_1^2 = R_2^2$)

$$A_c = \frac{1}{2} (x_1 - x_2 - x_3 + x_4)$$

$$= \frac{1}{2} 4x = 2x \text{ (worst case)}$$

(2) $R_1^2 < R_2^2$ (i.e., $R_1^2 < R_2^2$)

$$A_c = \frac{(R_2^2 / R_1^2)}{1 + (R_2^2 / R_1^2)} (x_1 - x_2 - x_3 + x_4) = 4x \text{ (worst case)}$$

M. G. Park of Boston

It turns out that if we are interested in first order terms in x_1 , x_2 , x_3 , x_4 then we do not need to take into account the exact value of R_4 by R_3 plus R_4 , we can substitute $R_4 = 0$ by $R_3 = 0$ plus $R_4 = 0$ here without changing the first order expression for A_c . So, we will do that. And what we do now is take two special cases just to get an idea of the approximate range of A_c .

Case 1: $R_1 = 0$ and $R_2 = 0$ are equal, so these two resistance values are equal; these two resistance values are also equal. So, all four resistors are the same the nominal values are the same. What do we get in this case? In this case we get A_c equal to this is R_4 by R_4 plus R_4 because all resistance is are equal, so that is half and then we get x_1 minus x_2 minus x_3 plus x_4 . Now in these circuits we are always interested in the worst case value of A_c ; that means, the largest possible magnitude for A_c .

And when will the largest possible magnitude of A_c happen? It will happen for example, if x_2 is negative, x_3 is negative, x_1 is positive and x_4 is also positive and all of them have their maximum values in magnitude. So, when we consider that we get half times


four x because all of these will then add up and that is $2x$. So for example, if we use 1 percent resistances then this will be 2 times x or 0.2 .

Case 2: now in which R_{10} is much smaller than R_{20} . That means, this ratio R_2 by R_1 is much larger than 1. And this of course, is a more realistic situation because our difference amplifier has a gain of R_2 by R_1 and we are likely to make that R_2 by R_1 large. We continue to use R_3 equal to R_1 and R_4 equal to R_2 . And therefore, if R_{10} is much less than R_{20} what it means is R_{30} is also much less than R_{40} . And now let us see what happens to our common mode gain.

The common mode gain the pre factor is R_{40} by R_{30} plus R_{40} we can rewrite that as R_{40} by R_{30} divided by 1 plus R_{40} by R_{30} . Now this number is much larger than 1 because of this condition and therefore this is nearly equal to 1. And once again this bracket as a maximum value of 4 times x that is the worst case, so therefore in this case the common mode gain would be 4 times x in the worst situation.

So, again if you have 1 percent resistances the common mode gain would be 4 times 0.01 or 0.04 . So, we say that the common mode gain is not exactly negligible in these circuits and therefore we need to worry about it.

(Refer Slide Time: 19:12)

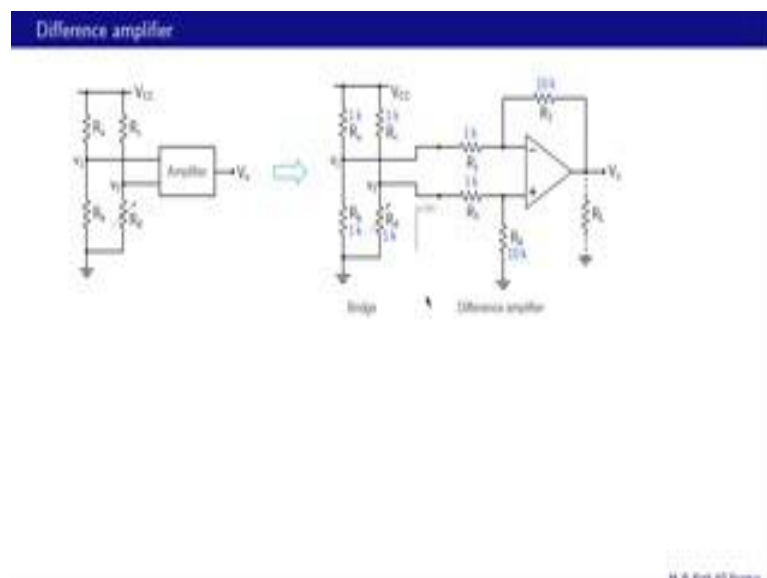

Before we go further let us do a quick summary. The difference amplifier does give us the desired functionality namely v_o equal to k times v_2 minus v_1 ; that is it amplifies

only the difference between the input voltages and that is exactly what we want for situation like this.

But there are two difficulties: one its input resistance is not too large and therefore when we connect the amplifier and the bridge circuit together it is going to disturb these values the input values themselves and that of course is not desirable. Second, its common mode gain is not exactly negligible. What we would like now is to look at a circuit which will address both of these issues namely; the input resistance and CMRR.

(Refer Slide Time: 20:28)

Improved difference amplifier

$$V_1 = V_2 \rightarrow V_A = V_B; V_A = V_B \rightarrow i = \frac{1}{R_1} (V_1 - V_2)$$
 Large input resistance of A1 and A2 so the current through the two resistors marked R_1 is also equal to i .

$$V_A - V_B = i(R_2 + 2R_3) = \frac{1}{R_1} (V_1 - V_2)(R_2 + 2R_3) = (V_1 - V_2) \left(1 + \frac{2R_3}{R_1} \right)$$
 Finally $V_o = \frac{R_4}{R_3} (V_A - V_B) = \frac{R_4}{R_3} \left(1 + \frac{2R_3}{R_1} \right) (V_1 - V_2)$
 This circuit is known as the "instrumentation amplifier".

Here is an improved difference amplifier. What we will do is to understand its functionality first, we will check that it is indeed difference amplifier that is it is amplifying only the difference between V_{i2} and V_{i1} . And then we will look at in what way it is an improvement our previous difference amplifier circuit.

So, let us look at the functionality part first, and let us start with this block and we realise that it is already familiar to us it is impact the difference amplifier circuit that we have been discussing. What is the difference? We had R_2 here and R_1 here now we have R_4 here and R_3 here. So, this R_4 and this R_4 is the same, this R_3 and this R_3 is the same. And if you recall the condition for the circuit to work as A difference amplifier was R_2 by R_1 equal to R_4 by R_3 .

So, in this case what it requires is R_4 by R_3 is equal to R_4 by R_3 which is of course true. So therefore, this part is simply A difference amplifier and this v_o is then given by R_4 by R_3 times v_{o2} minus v_{o1} . And now let us see what this rest of the circuit is doing. Since the op-amps are working in the linear region we can say that v_{plus} and v_{minus} are nearly the same for each of the op-amps and let us see what that implies.

It implies that this voltage v_a is the same as V_{i1} and also this voltage v_b is the same as V_{i2} . And once we know these v_a and v_b we can now get i_1 which is v_a minus v_b divided by R_1 , and that is therefore the same as V_{i1} minus V_{i2} divided by R_1 .

Next let us use the fact that these op-amps A_1 and A_2 this have large input resistances and therefore, these currents are 0. And therefore this i_1 must be the same as the current through this R_2 and also this second R_2 here. So, that is the current path that we expect. And once we know this current path we can now find v_{o1} minus v_{o2} . This voltage drop which is i_1 times R_2 plus this voltage drop which is i_1 times R_1 plus this voltage drop which is i_1 times R_2 . And we already have i_1 here and we put it all together to get this expression v_{o1} minus v_{o2} is V_{i1} minus V_{i2} times this vector here.

Once we know v_{o1} minus v_{o2} it is easy to get the final output voltage v_o , because we have already looked at this and we know the gain of this stage is R_4 by R_3 . So, then v_o is R_4 by R_3 times v_{o2} minus v_{o1} and now we substitute for v_{o2} minus v_{o1} from here and get R_4 by R_3 times 1 plus $2 R_2$ by R_1 times V_{i2} minus V_{i1} . So, this circuit is indeed difference amplifier it is amplifying only the difference between V_{i2} and V_{i1} , and it turns out to be a famous and very commonly used circuit it is called the Instrumentation Amplifier.

To conclude we have seen that the difference amplifier needs to be improved both in terms of input resistance and common mode rejection capability. We have started looking at another circuit the instrumentation amplifier. We will continue with this circuit in the next class and see how it provides better performance as compared to the difference amplifier. See you next time.