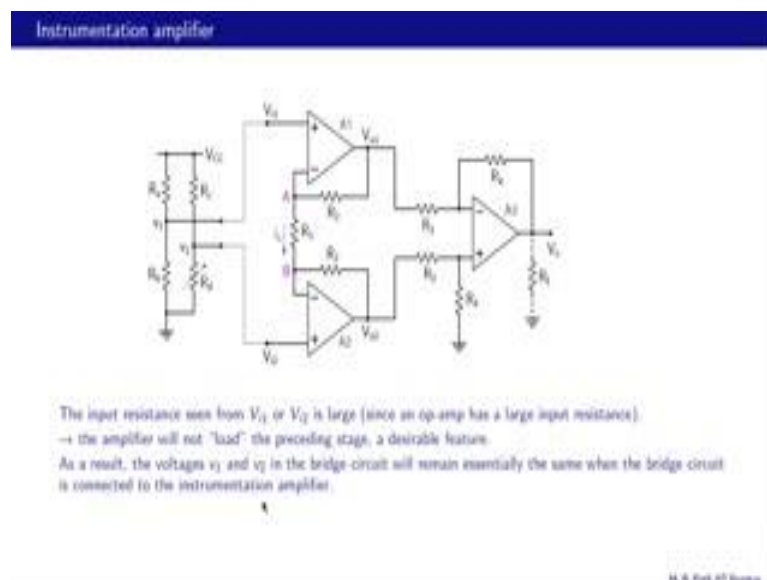


Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture – 38
Instrumentation amplifier (continued)

Welcome back to Basic Electronics. In the last lecture we have started looking at the Instrumentation Amplifier. We will continue with that discussion we will see how the instrumentation amplifier is better both in terms of input resistance and common mode rejection. We will look at two additional op-amp circuits, in this lecture the current to voltage convertor and the integrator. So, let us start.

(Refer Slide Time: 00:47)




The input resistance as seen from V_1 or V_2 is obviously large, because we are looking into the op-amp directly and the op-amp has a large input resistance. And therefore, this instrumentation amplifier will not load the preceding stage and that of course is a very desirable feature.

In other words it will not draw any current when we connect it to for example, the bridge circuit that we have seen earlier, like that. So, now, when we connect the amplifier to the bridge circuit this current is almost 0, and therefore v_1 will not get disturbed this current is also 0 so therefore v_2 also will not get disturbed. And now when we make the measurement we can expect our v_0 to be what it really should be.

So, the voltages v_1 and v_2 in the bridge circuit will remain essentially the same when the bridge circuit is connected to the instrumentation amplifier.

(Refer Slide Time: 02:06)

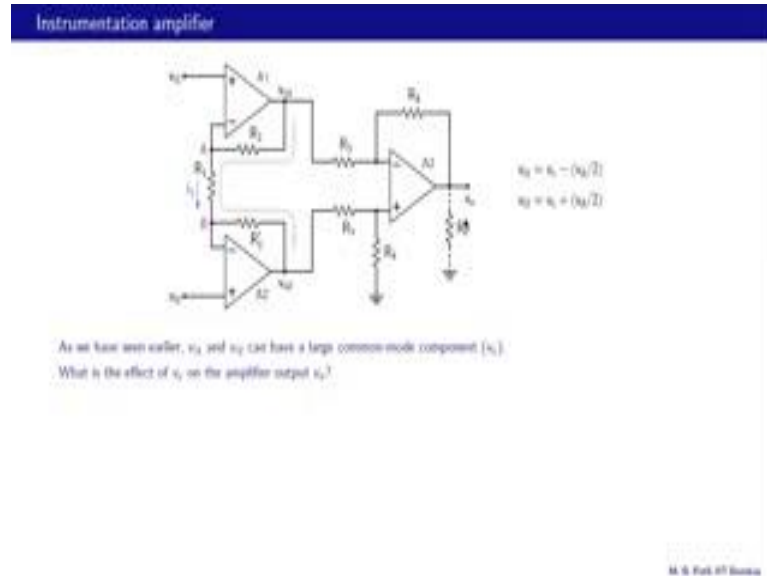

So, the instrumentation amplifier is definitely superior to the difference amplifier, because it offers so much larger input resistance. And therefore, when we connect this to the bridge circuit for example these voltages V_{i1} and V_{i2} will not get disturbed, and therefore our measure output would be a two reflection of what we are trying to quantify.

Now, let us look at the other important issue that is the performance of the instrumentation amplifier with respect to common mode input voltages. As we have seen before V_{i1} and V_{i2} can have a large common mode component. V_{i1} is given by v_c minus v_d by 2 V_{i2} is given by v_c plus v_d by 2. And we have seen earlier in the bridge circuit is ampere that we see can be quite larger for example 7.5 volts there and v_d was only 37.5 millivolts in that example.

And now we want to know; what is the effect of this common mode input voltages on the amplifier output v_o there.

(Refer Slide Time: 03:24)

Instrumentation amplifier: common-mode rejection

Note that v_{01} serves as v_{i1} for the difference amplifier, and v_{02} as v_{i2} . Let us find the differential-mode and common-mode components associated with v_{i1} and v_{i2} .

$v_{i1} = v_{01} = v_{02}$, $v_{i2} = \frac{1}{2}(v_{01} + v_{02})$

$v_{i1} = (R_1 + R_2 + R_3) \frac{1}{R_1} \left[\left(v_1 - \frac{v_2}{2} \right) - \left(v_2 - \frac{v_1}{2} \right) \right] = \left(1 + \frac{R_2 + R_3}{R_1} \right) v_1$

$v_{i2} = \frac{1}{2} \left[\left(v_1 - \frac{v_2}{2} \right) + \left(v_2 + \frac{v_1}{2} \right) - v_2 \right] = v_2$

$\rightarrow v_2$ has gain amplified but not $v_1 \rightarrow$ overall improvement in CMRR

(Note that resistor mismatch in the second stage needs to be considered, but it will have a limited effect.)

$v_0 = v_1 - (v_2/2)$
 $v_0 = v_2 + (v_1/2)$

M. S. Park @ Samsung

When we look at the common mode rejection performance of the instrumentation amplifier we will assume that the op-amps themselves are perfect; that means they have very high CMRR infinity. So, the finite CMRR of the instrumentation amplifier as a role will arise only because of resistance mismatch. So, this R 2 and R 2 prime are supposed to be same, but they would not exactly the same because of tolerance values. Similarly, this R 3 and R 3 prime would be slightly different. And R 4 and R 4 prime would be slightly different. So, as a result of that the instrumentation amplifier will have a finite CMRR and that is what we want to find.

Let us note that V o 1 this voltage serves as the input V i 1 of this difference amplifier and similarly V o 2 serves as the input V i 2 of the difference amplifier. And now we will find the differential mode and common mode components of this input voltage. What is the differential mode input voltage? We will denote that by V i d prime so that is equal to V o 2 minus V o 1, V o 2 minus V o 1, and the common mode component V i c prime is half V o 1 plus V o 2.

What is V i d prime is V o 2 minus V o 1, so it is this voltage plus that plus that. So, its R 2 prime plus R 1 plus R 2 times i 1 with a negative sign because we are looking at V o 2 minus V o 1. What is i 1? it is v a minus v b divided by R 1 and v a itself is V i 1 which is the same as v c minus v d by 2. V b is the same as V i 2 which is v c by v d by 2. So,

when we put all that together we get this expression here. And v_c cancels out and we are left with $1 + R_2 + R_2'$ divided by R_1 times v_d .

So, that is our differential mode input voltage as seen by the difference amplifier. Let us now look at the common mode voltage seen by the difference amplifier and that is $\frac{V_{o1} + V_{o2}}{2}$. So, that is half this is V_{o1} , what is V_{o1} ? It is v_a plus this voltage drop that is i_1 times R_2 and v_a is V_{i1} which is $\frac{v_c - v_d}{2}$. So, $\frac{v_c - v_d}{2}$ plus this voltage drop $i_1 R_2$.

What about V_{o2} ? It is v_b which is the same as V_{i2} which is $\frac{v_c + v_d}{2} - i_1 R_2'$, so that is V_{o2} . And now we see that this $\frac{v_d}{2}$ of course get cancelled $v_c + v_c$ is $2 v_c$. And this i_1 times $R_2 - R_2'$ is a very small quantity, because R_2 and R_2' are actually are actually supposed to be matched and their difference would be negligible compare to v_c . So therefore, overall we have the i_c prime nearly equal to v_c ; the common mode voltage at the input of the instrumentation amplifier.

So, something very significant as happened let us see what that is. At this stage our common mode voltage was v_c and the differential mode voltage was v_d and that is why V_{i1} was given by $\frac{v_c - v_d}{2}$ V_{i2} by $\frac{v_c + v_d}{2}$. When we come here our differential mode input voltage has got amplified $1 + R_2 + R_2'$ divided by R_1 . And this gain could be substantial could be 20 could be 50, whereas our common mode input voltage as remained equal to v_c . And of course is a very big advantage. In short v_d as got amplified but not v_c , and therefore that leads to an overall improvement in the CMRR.

So, we have come up to this point and now we want to see what the output voltage of the instrumentation amplifier is. Let us take the simple case first in which there is no resistor mismatch, so R_4 and R_4' are equal R_3 and R_3' are equal. In that case this is a perfect difference amplifier and its gain is $\frac{R_4}{R_3}$, so therefore the output voltage would be $\frac{R_4}{R_3}$ times $V_{o2} - V_{o1}$. And the common mode component of V_{o1} and V_{o2} which is v_c will get cancelled out and we will get an amplified version of this quantity at the output.

So, at the output we will have no common mode voltage at all, and therefore the CMRR of the entire instrumentation amplifier would be infinite. In real life of course the resistor

mismatch in the second stage needs to be considered, but it will surely have a limited effect, and let us see why. Let us compare two: cases 1 in which this difference amplifier gets V_{i1} and V_{i2} as inputs directly without this stage, and in that case what is the common mode voltage it sees it is v_c ; what is the differential mode input voltage it sees, it is v_d : that is case 1.

Case 2: the instrumentation amplifier. Now what is the common mode voltage it sees? It is v_c , and what is the differential mode input voltage it sees? It is an amplified form of v_d and that is a difference. So therefore, the overall gain that the common mode voltage goes through is much much smaller relative to the gain that the differential mode voltage goes through and gives us much better performance than the plain difference amplifier that we have seen before.

(Refer Slide Time: 10:42)

Current-to-voltage conversion

Some circuits produce an output in the form of a current. It is convenient to convert this current into a voltage for further processing.
 Current-to-voltage conversion can be achieved by simply passing the current through a resistor, $V_{out} = I_s R$.

However, this simple approach will not work if the next stage in the circuit (such as an amplifier) has a finite R_i , since it will modify V_{s1} to $V_{s2} = I_s (R_i \parallel R)$, which is not desirable.

M. S. Elshorbagy

Let us now look at current to voltage conversion and that is relevant because some circuits produce an output in the form of a current, and it is then convenient to convert this current into a voltage for further processing. For example, we might want to display that voltage or we might want to amplified further and so on. Now what is the simplest way of converting a current to a voltage? Just pass it through a resistor. So, this is our signal current I_s we pass it through a resistance R and that produces an output voltage I_s times R . And that is exactly what we want; we have got a voltage which is proportional to our signal current.

Fair enough, but there is a problem with that approach. Let us say we want to now amplify or measure this V_o by connecting an amplifier between this node and down, like that. This is our amplifier with the voltage gain of A_v . So, we would expect this V_o to be A_v times V_o which is A_v times I_s times R . Now that is not what happens because this amplifier has an input resistance R_i which comes in parallel with R and therefore this V_o would now change to I_s times R parallel R_i , like that. And that of course, is not desirable and why did not this happen because this amplifier as loaded our source circuit.

(Refer Slide Time: 12:43)

Current-to-voltage conversion

$V_- \approx V_+$, and $i_- \approx 0$ so $V_o = V_- - I_s R = -I_s R$.
 The output voltage is proportional to the source current, irrespective of the value of R_L , i.e., irrespective of the next stage.
 Example: a photocurrent detector.
 $V_o = I_s R$. (Note: The diode is under a reverse bias, with $V_- = 0V$ and $V_o = V_{bias}$)

M. S. Park of Samsung

So, let us now look at an op-amp circuit which avoids this problem. Here is an op-amp circuits which can be used to convert a current to a voltage. How does it work it is very easy to understand. This current is 0 because that is an input current for the op-amp and therefore our signal current I_s would go through this resistance R , and v_o would then be v_{-} minus minus this voltage drop. And since v_{-} and v_{+} are nearly equal assuming the op-amp to be operating in the linear region. This node is at virtual ground, so therefore v_o would be 0 minus I_s times R , like that. And note particularly that the load resistance simply does not enter this equation. So, this relationship is independent of what we connect as the load, and that of course is what we wanted.


Let us take a look at an example; that is a photocurrent detector. What is a photocurrent? Photocurrent is a current that we generate by shining light on a semiconductor device;

typically a diode. These diodes of course are specially made, but they are basically the same as a p-n junction.

So, let us look at the circuit; here is the circuit. This v bias is negative let us say minus 5 volts, this node is at virtual ground. So, the n terminal of the diode is at 0 volts and the p is at minus 5 volts for example. So therefore, the diode is under reverse bias. In this situation if we shine light on this diode this reverse current can change significantly and that is our signal current. So, what is the output voltage in this case? This i prime would also go through this R like that and therefore v o is 0 volts plus this voltage drop that is i prime times R.

(Refer Slide Time: 15:19)

Op-amp circuits (linear region)

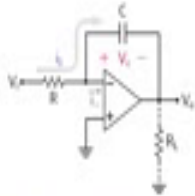

$V_+ \approx V_- = 0V \rightarrow i_1 = V_1/R$
 Since $i_- \approx 0$, the current through the capacitor is i_1 .
 $\Rightarrow C \frac{dV_c}{dt} = i_1 = \frac{V_1}{R}$
 $V_c = V_- - V_o = 0 - V_o = -V_o \rightarrow C \left(-\frac{dV_o}{dt} \right) = \frac{V_1}{R}$
 $V_o = -\frac{1}{RC} \int V_1 dt$
 The circuit works as an integrator.


M. S. Park @ Samsung

So, that is a common application of this current voltage converter. Here is another useful op-amp circuit; let us see what it is doing. We will assume that the op-amp is operating in the linear region. So, v minus and v plus are nearly equal therefore this is at virtual ground that gives us $i_1 = v_1 / R$ or v_1 / R . Since i_- is 0 that is in input current for the op-amp the current through the capacitor it is also i_1 like that. And what is the current through capacitor it is $C \frac{dV_c}{dt}$. So, therefore, we have $C \frac{dV_c}{dt}$ equal to i_1 equal to v_1 / R .

Now, we want to relate v_c and v_o ; what is v_c ? Its $v_- - v_o$ and we know that v_- is 0 volts, so therefore v_c is $0 - v_o$ that is simply $-v_o$. So, instead of v_c here we can put $-v_o$ so that gives us this equation $C \frac{d(-v_o)}{dt} = \frac{v_1}{R}$

to v_i by R . In other words v_o is minus 1 over Rc integral $V_i dt$, and v_c that this circuit is working as an integrator. So, it integrates the applied input voltage.

(Refer Slide Time: 17:01)

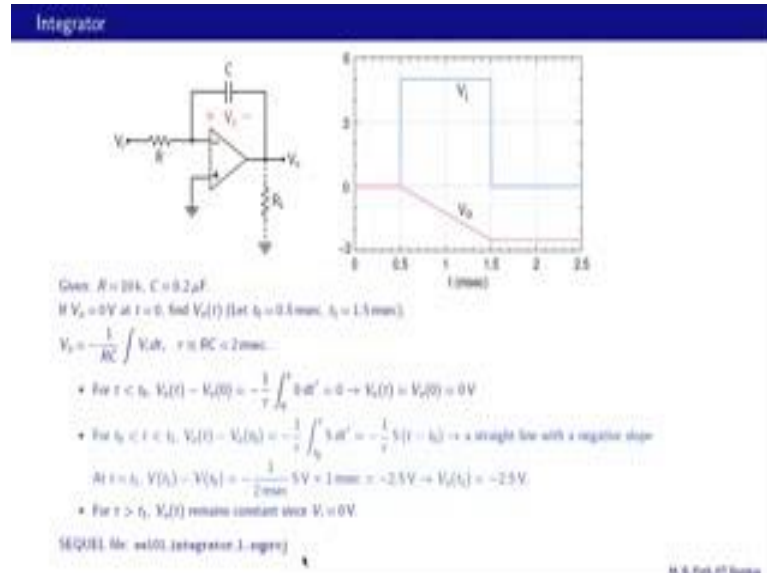

Let us look at an example of the integrator circuit given R is equal to $10k$, c equal to 0.2 micro farads. And the input voltage waveform is given it is 0 up to this point up to point 5 millisecond, then it raises appropriately to 5 volts then it remains at 5 volts up to 1.5 milliseconds and then it comes down to 0 states at 0 thereafter. That is our input voltage, we have also given that the output voltage this is 0 at t equal to 0 . And given these conditions given these component values we want to find v_o as a function of time.

Let us use t_0 to denote this time at which v_i is going from low to high, so t_0 is 0.5 milliseconds and let us use t_1 to denote this time at which v_i is going from high to low so t_1 is 1.5 milliseconds. Now what do we know about the integrator; we know that v_o is given by minus 1 over Rc integral $V_i dt$ this Rc we will denote by τ . And what is the value of τ ? R is $10k$ c is 0.2 micro farads, so 10 times 0.2 is 2 kilo times micro is milli; so τ is 2 milliseconds.

What we will do now is to consider three different intervals this one that is 0 to t_0 this one from t_0 to t_1 and this one that is t greater than t_1 . And in each of these intervals we will find v_o of t and then finally we will put it all together. So, let us start with this first interval that is t less than t_0 . So, what we can do now is to evaluate this integral from 0 to t where t is somewhere in this intervals. On the left hand side we will get v_o of t


minus v_0 at 0 and on the right hand side we will get minus 1 over tau integral 0 to t v_i dt and v_i is 0 here. So therefore, this whole right hand side becomes simply 0 and therefore v_o of t becomes equal to v_o of 0 that is 0 volts; as shown here by the red line.

Next let us consider the interval from t_0 to t_1 that is 0.5 milliseconds to 1.5 milliseconds. Throughout this interval v_i is constant 5 volts, so let us find the output voltage now. Again we integrate v_i from t_0 to t and on the left hand side we will get v_0 at t minus v_0 at t_0 and on the right hand side we will get minus 1 over tau t_0 to t integral V_i dt and v_i is 5 volts. So therefore, this turns to be minus 1 over tau 5 times t minus t_0 . And this is simply a straight line, this is our y, this is a constant and this is our x. So, it is the form y equal to m x plus c . So, that is a straight line, and as we can see it as a negative slope minus 5 divided by tau.

So, we expect v_o to go down at this point a straight line with negative slope, so something like this and now let us calculate what v_o should be at t_1 that is 1.5 milliseconds. At t equal to t_1 all we need to do now is substitute t equal to t_1 in this expression. So, v_o at t_1 minus v_o at t_0 is equal to minus 1 over tau, tau is 2 milliseconds times 5 volts times t minus t_0 ; that is t_1 minus t_0 , t_1 is here t_0 is here. So, t_1 minus t_0 is 1 millisecond so that is 1 millisecond. So, this turns out to be 5 divided by 2 or 2.5 volts, these milliseconds will cancel with these milliseconds and we are left with minus 2.5 volts. So, that gives us the output voltage at t_1 , and that is what v_o of t looks like up to t equal to t_1 .

After this point the input voltage is 0 and therefore this integral will be 0, and therefore v_o will not change. So, for t greater than t_1 v_o remains constant since v_i is equal to 0 volts, like that. So, that is our overall v_o of t. There is a circuits file available for this example and you can check out the simulation you can try to increase this capacitance. For example from 0.2 micro farads to 0.5 micro farads work out what you expect for v_o and then simulate and check whether your prediction is correct. You can also try to change this v_i from 5 volts to let say 3 volts again work out v_o of t and check if it is according to your prediction.

(Refer Slide Time: 23:35)

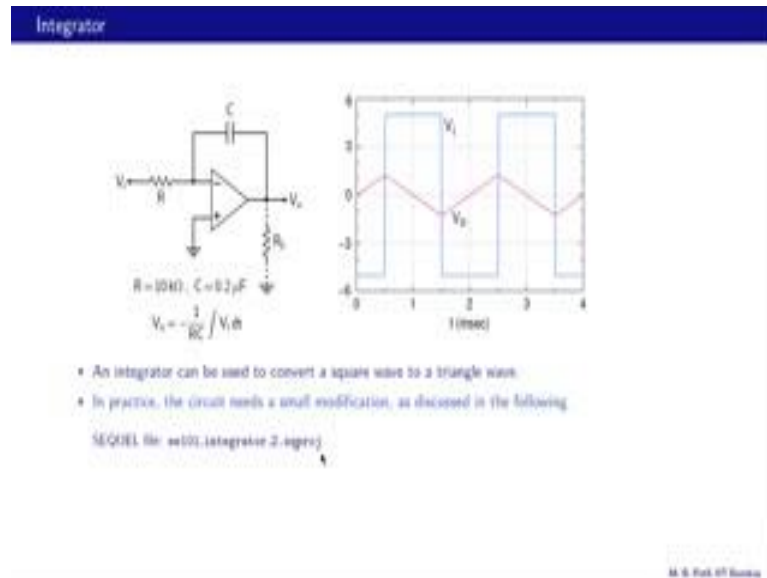

What we saw previously was a simple example just to get used to the numbers and the action of the integrator, but an integrator can actually be used for doing something very useful and that is to convert a square wave to a triangle wave. So, here is our input square wave going from minus 5 volts to plus 5 volts with a period of 2 milliseconds and that is our output triangle wave. And with these numbers you should really work out what v_o of t is going to be and check that this plot is indeed correct.

Now, in practice this circuit will not work in its present form and we will see what the reason is, it will require a small modification and we will also discuss that modification. But the basic idea is brought out very clearly in this graph, square wave input and triangle output. Again the sequel circuit file is available for the circuits and you can check out the results.

To conclude we have seen that the instrumentation amplifier offers a high input resistance and a high CMRR and that makes it well suited for sensed applications. We have looked at two additional op-amp circuits; the current to voltage converter and the integrator. In the next lecture we will look at some non idealities associated with an op-amp and how they can affect the circuits we have considered earlier. So see you next time.