

**Basic Electronics**  
**Prof. Mahesh Patil**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Bombay**

**Lecture - 05**  
**Phasors**

Welcome back to Basic Electronics. So far we have looked at circuits with dc sources, there are many situations in which there is a sinusoidal voltage source in the circuit and in particular we are interested in the solution in the so called sinusoidal steady state. In this lecture we will first look at the meaning of the term sinusoidal steady state; we will then look at a convenient way to represent voltages and currents in that situation using a new concept called Phasor. We will also look at how phasors can be used to represent R L and C in the sinusoidal steady state.

(Refer Slide Time: 01:02)

Sinusoidal steady state

$$R(C \dot{V}_c) + V_c = V_m \cos \omega t, \quad t > 0 \quad (1)$$

The solution  $V_c(t)$  is made up of two components,  $V_c(t) = V_c^{(H)}(t) + V_c^{(P)}(t)$ .  
 $V_c^{(H)}(t)$  satisfies the homogeneous differential equation,

$$R(C \dot{V}_c) + V_c = 0, \quad (2)$$

from which,  $V_c^{(H)}(t) = A \exp(-t/\tau)$ , with  $\tau = RC$ .  
 $V_c^{(P)}(t)$  is a particular solution of (1). Since the forcing function is  $V_m \cos \omega t$ , we try

$$V_c^{(P)}(t) = C_1 \cos \omega t + C_2 \sin \omega t.$$

Substituting in (1), we get,

$$\omega RC (-C_1 \sin \omega t + C_2 \cos \omega t) + C_1 \cos \omega t + C_2 \sin \omega t = V_m \cos \omega t.$$

$C_1$  and  $C_2$  can be found by equating the coefficients of  $\sin \omega t$  and  $\cos \omega t$  on the left and right sides.


M. S. Patil of IIT Bombay

So let us begin; let us try to understand the meaning of this term sinusoidal steady state with help of this example, it is an R C circuit with a sinusoidal input voltage, there is a switch here which closes at t equal to 0 and initially the capacitor is uncharged; that means, V c is 0. Let us begin with the circuit equation this equation 1 here, what does it say? It says that this voltage drop plus this voltage drop must be the same as the source voltage, this voltage drop is R times the current and the current is c b b c d t. So, that is

what this says here  $R$  times  $C$   $V_c$  prime, plus  $V_c$  must be equal to  $V_m \cos \omega t$ , for  $t$  greater than 0 that is when the switch is closed.

The solution  $V_c$  of  $t$  is made up of 2 components, a homogeneous component indicated with this superscript  $h$  here and a particular component indicated with this superscript  $p$ . The homogeneous component  $V_c^h t$  satisfies the homogeneous differential equation,  $R C V_c^h \text{ prime} + V_c^h = 0$ . So, we drop the source term and that is all we get this equation and this equation has this solution  $A e^{-t/\tau}$ , with  $\tau$  equal to  $R$  times  $C$ . Let us now look at the second part the particular solution, since the forcing function is  $V_m \cos \omega t$ , we can try  $V_c^p$  of  $t$  equal to  $C_1 \cos \omega t$ , plus  $C_2 \sin \omega t$  as a candidate solution and when we substitute this in equation 1, we get this equation here and the constants  $C_1$  and  $C_2$  can be found by equating the coefficients of  $\sin \omega t$ , and  $\cos \omega t$  on the left and right sides.

(Refer Slide Time: 03:18)

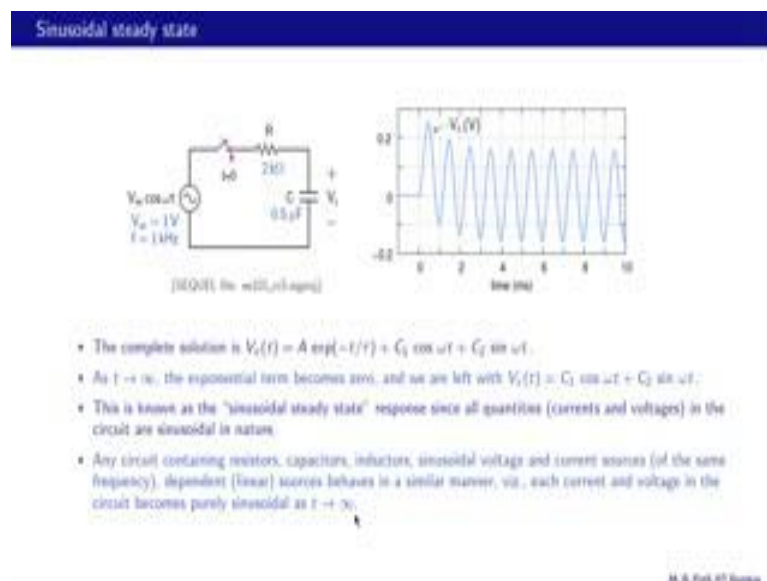


Here is a specific example with  $V_m$  equal to 1 volts,  $f$  is equal to 1 kilo hertz 2 k here; 0.5 micro here for the capacitance and then we get this  $V_c$  shown in this figure. The complete solution is  $A e^{-t/\tau}$  from the previous slide, that is the homogeneous part plus  $C_1 \cos \omega t$ , plus  $C_2 \sin \omega t$  this is the particular part of the solution. Now as  $t$  tends to infinity, the exponential term becomes 0 this goes to 0 and we are left with  $V_c$  of  $t$  equal to  $C_1 \cos \omega t$  plus  $C_2 \sin \omega t$  this part here.

And we can observe that in this plot as well, this is our  $t$  equal to 0 that is the time when the switch closes, and in the beginning there is some exponential transient and then finally, the transient vanishes and we have the sinusoidal steady state. So, this is known as the sinusoidal steady state response, since all quantities currents and voltages in the circuit are sinusoidal in nature and this turns out to be generally true for any circuit, containing resistors capacitors inductors, sinusoidal voltage and current sources dependent sources such as CCCS, C CVS etcetera. So, any circuit containing these components behaves in a similar manner that is each current and voltage in the circuit becomes purely sinusoidal as  $t$  tends to infinity. So, each quantity each current and each voltage, in the circuit would have this form in the sinusoidal steady state ok.

(Refer Slide Time: 05:07)

Sinusoidal steady state: phasors

- In the sinusoidal steady state, "phasors" can be used to represent currents and voltages.
- A phasor is a complex number.  
 $\mathbf{X} = X_m \angle \theta = X_m \exp(j\theta)$   
 with the following interpretation in the time domain.  
 $x(t) = \text{Re} \{ \mathbf{X} e^{j\omega t} \}$   
 $= \text{Re} \{ X_m e^{j\theta} e^{j\omega t} \}$   
 $= \text{Re} \{ X_m e^{j(\omega t + \theta)} \}$   
 $= X_m \cos(\omega t + \theta)$
- Use of phasors substantially simplifies analysis of circuits in the sinusoidal steady state.
- Note that a phasor can be written in the polar form or rectangular form.  
 $\mathbf{X} = X_m \angle \theta = X_m \exp(j\theta) = X_m \cos \theta + j X_m \sin \theta$   
 The term  $\omega t$  is always implicit.



M. S. Fall 07 Lecture

Let us continue and now we want to introduce Phasors. In the sinusoidal steady state phasors can be used to represent currents and voltages. So, let us see what a phasor is a phasor is. A complex number that is why it is written in boldface here, it has got a magnitude of  $X_m$  and an angle of  $\theta$ . So, that is the phasor  $\mathbf{X}$  and we can rewrite this as  $X_m \angle \theta$  here is to  $j\theta$ , and it has the following interpretation in the time domain. Corresponding to the phasor  $\mathbf{X}$  we have a time domain quantity denoted by  $x(t)$  and the interpretation is like this  $x(t) = \text{Re} \{ \mathbf{X} e^{j\omega t} \}$  that is phasor  $\mathbf{X}$  multiplied by  $e^{j\omega t}$ .

So let us see what that turns out to be; our phasor is nothing but  $X_m$  times  $e$  raised to  $j\theta$  that gets multiplied by  $e$  raised to  $j\omega t$ . Now we can combine these 2 terms to get  $e$  raised to  $j\omega t + \theta$ , what is  $e$  raised to  $j\omega t + \theta$ ? It is  $\cos$  of  $\omega t + \theta$ , plus  $j \sin$  of  $\omega t + \theta$  and we are only taking the real part of that expression, so therefore, we get  $X_m \cos \omega t + \theta$ . So, that is what a phasor  $X$  corresponds to in the time domain.

Let us make some more comments, use of phasors substantially simplifies analysis of circuits in the sinusoidal steady state and we will look at some examples of that. Note that a phasor can be written in the polar form or rectangular form, this is the polar form  $X_m \angle \theta$  also called the magnitude angle form, that is the same as  $X_m e^{j\theta}$  and that can be written as  $X_m \cos \theta + j X_m \sin \theta$  this is called the rectangular form. This figure shows how the polar and rectangular forms of  $X$  can be represented, this axis is the real part of  $X$  which is the complex number, this axis is the imaginary part of  $X$ , this is our phasor it has got a magnitude of  $X_m$  and angle of  $\theta$ .

Alternatively we can also write this component which is the real component of  $X$  and this component which is the imaginary component of  $X$ , and that gives us the rectangular form. Now one final remark very important the term  $\omega t$  is always implicit. So, when we write a phasor for example  $X$  here, we do not write  $\omega t$  over there, but it is understood that  $\omega t$  is always implicit and that is how it comes in this time domain expression here.

(Refer Slide Time: 08:32)

Time domain	Frequency domain
$v_1(t) = 3.2 \cos(\omega t + 30^\circ) \text{ V}$	$V_1 = 3.2 \angle 30^\circ = 3.2 \exp(j\pi/6) \text{ V}$
$i(t) = -1.5 \cos(\omega t + 60^\circ) \text{ A}$ $= 1.5 \cos(\omega t + \pi/3 - \pi) \text{ A}$ $= 1.5 \cos(\omega t - 2\pi/3) \text{ A}$	$I = 1.5 \angle (-2\pi/3) \text{ A}$
$v_2(t) = -0.1 \sin(\omega t) \text{ V}$ $= 0.1 \cos(\omega t + \pi) \text{ V}$	$V_2 = 0.1 \angle \pi \text{ V}$
$i_2(t) = 0.18 \sin(\omega t) \text{ A}$ $= 0.18 \cos(\omega t - \pi/2) \text{ A}$	$I_2 = 0.18 \angle (-\pi/2) \text{ A}$
$i_3(t) = \sqrt{2} \cos(\omega t + 45^\circ) \text{ A}$	$I_3 = 1 + j1 \text{ A}$ $= \sqrt{2} \angle 45^\circ \text{ A}$

Let us now take a few examples to see how something can be represented in the time domain and in the frequency domain. Here is a voltage  $V_1$  of  $t$   $3.2 \cos \omega t$  plus  $30$  degrees volts, we can write this in the phasor form; the magnitude is  $3.2$  and the angle is  $30$  degrees. So, that is what the phasor looks like  $3.2$  angle  $30$  degrees.

We can also write that as  $3.2 e^{j\pi/6}$ , because  $30$  degrees is the same as  $\pi/6$  radians. Another example  $I$  of  $t$  is  $-1.5 \cos \omega t$  plus  $60$  degrees. Now it is not quite in the form that we would like, because we have this minus sin over here. So, let us rewrite this expression as  $1.5 \cos \omega t$  plus  $\pi/3$  that is  $60$  degrees minus  $\pi$ ; this minus  $\pi$  accounts for this minus sin here and that follows from trigonometric identities. Now we can combine these, these 2 terms and get  $\omega t$  minus  $2\pi/3$  and now we can write the corresponding phasor like that. Now we took  $1.5$  and angle minus  $2\pi/3$ .

Next example  $V_2$  of  $t$  equal to  $-0.1 \cos \omega t$ ; once again we do not want this minus sin here so we rewrite this expression as  $0.1 \cos \omega t$  plus  $\pi$ , this plus  $\pi$  accounts for this minus sin over here and note that we can either write plus  $\pi$  here or we can write minus  $\pi$  like we did in the last example here. Now the corresponding phasor is magnitude  $0.1$  and angle equal to  $\pi$ ; next we have  $I_2$  of  $t$  equal to  $0.18 \sin \omega t$ . Now we require cos over here not sin so therefore, let us rewrite this expression as  $0.18 \cos \omega t$  minus  $\pi/2$  and now we can write the corresponding phasor like that,  $I_2$  equal to  $0.18$  that is the magnitude  $0.18$  angle minus  $\pi/2$ , so that is the angle. Let us take an

example of the reverse transformation now, the frequency domain description is given phasor  $I_3$  that is  $1 + j1$  in amperes.

Now we want to convert that into the time domain form, now this is in the rectangular form we first convert that into the polar form like that. So, they are square root 2 angle 45 degrees, and this we can write in the time domain directly like that.

(Refer Slide Time: 11:54)

**Addition of phasors**

Consider addition of two sinusoidal quantities:

$$v(t) = v_1(t) + v_2(t)$$

$$= V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2)$$

Now consider addition of the phasors corresponding to  $v_1(t)$  and  $v_2(t)$ .

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2$$

$$= V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2}$$

In the time domain,  $\mathbf{V}$  corresponds to  $\tilde{v}(t)$ , with

$$\tilde{v}(t) = \text{Re}[\mathbf{V}e^{j\omega t}]$$

$$= \text{Re}[(V_{m1} e^{j\theta_1} + V_{m2} e^{j\theta_2}) e^{j\omega t}]$$

$$= \text{Re}[V_{m1} e^{j(\omega t + \theta_1)} + V_{m2} e^{j(\omega t + \theta_2)}]$$

$$= V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2)$$

which is the same as  $v(t)$ .

M. G. Park of Bunko

So  $I_3$  of  $t$  is square root 2 cos omega t plus 45 degrees, and remember always that this omega t is implicit. So, we do not write that in the phasor, but we understand that it is always there. Let us now talk about addition of Phasors, first let us consider adding 2 sinusoidal time domain quantities like this  $V$  of  $t$  equal to  $V_1$  of  $t$ , plus  $V_2$  of  $t$ .  $V_1$  of  $t$  is given by  $V_{m1} \cos \omega t$  plus theta 1, and  $V_2$  of  $t$  is given by  $V_{m2} \cos \omega t$  plus theta 2. Now consider the addition of the corresponding Phasors; this phasor corresponds to  $V_1$  of  $t$ , this phasor corresponds to  $V_2$  of  $t$ . So,  $V_1$  therefore, is  $V_{m1} e^{j\theta_1}$  and it would  $V_{m1}$  and angle theta 1.  $V_2$  similarly is  $V_{m2} e^{j\theta_2}$ . In the time domain this phasor  $\mathbf{V}$  which is  $V_1$  plus  $V_2$  corresponds to  $\tilde{v}(t)$ , with  $\tilde{v}(t)$  equal to real part of phasor  $\mathbf{V}$  times  $e^{j\omega t}$ .

As we have seen earlier this is how a phasor can be written in the time domain. So, now, we substitute for  $\mathbf{V}$  that is  $V_{m1} e^{j\theta_1}$ , plus  $V_{m2} e^{j\theta_2}$  like that; and now we can combine this  $e^{j\theta_1}$  and  $e^{j\omega t}$  to obtain  $e^{j(\omega t + \theta_1)}$  and similarly  $e^{j(\omega t + \theta_2)}$  here. Now

we need to take the real part of this entire expression, and that turns out to be  $V_m \cos(\omega t + \theta_1)$ , plus  $V_m \cos(\omega t + \theta_2)$ . This in fact, is the same as  $V$  of  $t$  right there. Now what is the conclusion? The conclusion is that if we have 2 sinusoidal varying quantities such as  $V_1$  of  $t$  and  $V_2$  of  $t$  here, we can obtain their sum by either directly adding them or we can add the corresponding phasors like here and then from the resulting phasor  $V$  here, we can obtain the time domain quantity like that.

(Refer Slide Time: 14:22)

**Addition of phasors**

- Addition of sinusoidal quantities in the time domain can be replaced by addition of the corresponding phasors in the sinusoidal steady state.
- The KCL and KVL equations,  $\sum i_k(t) = 0$  at a node, and  $\sum v_k(t) = 0$  in a loop, amount to addition of sinusoidal quantities and can therefore be replaced by the corresponding phasor equations,  $\sum I_k = 0$  at a node, and  $\sum V_k = 0$  in a loop.

M. S. Ravi Kumar

So from the last slide we can say that addition of sinusoidal quantities in the time domain can be replaced by addition of the corresponding phasors in the sinusoidal steady state. Now this is very important for us because of the following point; the KCL and KVL equations, that is  $\sum I_k$  of  $t$  equal to 0 at a node that is all currents at a given node add up to 0 and  $\sum v_k$  of  $t$  equal to 0 in a loop, that is all voltages as we go along a loop add up to 0.

These equations amount to addition of sinusoidal quantities and can therefore, be replaced by the corresponding phasor equations, what are the phasor equations?  $\sum$  of the phasor currents equal to 0 at a node and  $\sum$  of the phasor branch voltages is equal to 0 in a loop.

(Refer Slide Time: 15:26)

**Impedance of a resistor**

Let  $i(t) = I_m \cos(\omega t + \theta)$   
 $v(t) = R i(t)$   
 $= R I_m \cos(\omega t + \theta)$   
 $= V_m \cos(\omega t + \theta)$

The phasors corresponding to  $i(t)$  and  $v(t)$  are, respectively:  
 $I = I_m \angle \theta$ ,  $V = R \times I_m \angle \theta$

We have therefore the following relationship between  $V$  and  $I$ ,  $V = R \times I$ .  
 Thus, the impedance of a resistor, defined as,  $Z = V/I$ , is

$Z = R + j0$

M. S. Park © 2010

Let us now introduce the concept of impedance starting with impedance of a resistor first; here is a resistor in the time domain that is the resistor current  $I$  of  $t$ , and  $V$  of  $t$  is the voltage across the resistor.

Now in the frequency domain we replace this current with phasor  $I$  and the voltage with phasor  $V$ ; and now we can write phasor  $V$  equal to phasor  $I$  times something called  $Z$ , where  $Z$  is called the impedance and let us actually show that we can do that. Let  $I$  of  $t$   $V$   $I_m \cos \omega t + \theta$ , then we have  $V$  of  $t$  equal to  $R$  times  $I$  of  $t$  that is valid at all times and that is equal to  $R$  times  $I_m \cos \omega t + \theta$  after substituting for  $I$  of  $t$  from there, and we might define that as  $V_m \cos \omega t + \theta$  where  $V_m$  is  $R$  times  $I_m$ . Now the phasors corresponding to  $i$  of  $t$  and  $v$  of  $t$  are respectively for  $I$  we have  $I_m \angle \theta$ ,  $I_m$  is the magnitude and  $\theta$  is the angle; for  $V$  we have  $R I_m \angle \theta$ ,  $R I_m$  is the magnitude and  $\theta$  is the angle.

We have therefore, the following relationship between phasor  $V$  and phasor  $I$ , that is  $V$  is equal to  $R$  times  $I$  as simple as that and we can see that from here  $V$  is  $R I_m \angle \theta$   $I$  is  $I_m \angle \theta$ . So, therefore,  $V$  is simply  $R$  times  $I$  and therefore, the impedance of a resistor which is defined as  $Z$  equal to  $V$  by  $I$  is,  $Z$  equal to  $R + j0$  from here  $Z$  is equal to  $R$  and  $R$  is a real number. So, we write that real number as  $R + j0$ . So, the impedance of a resistor is the resistance itself.



(Refer Slide Time: 17:55)

**Impedance of a capacitor**

Let  $v(t) = V_m \cos(\omega t + \theta)$

$$i(t) = C \frac{dv}{dt} = -C \omega V_m \sin(\omega t + \theta)$$

Using the identity,  $\cos(\phi + \pi/2) = -\sin \phi$ , we get

$$i(t) = C \omega V_m \cos(\omega t + \theta + \pi/2)$$

In terms of phasors,  $\mathbf{V} = V_m \angle \theta$ ,  $\mathbf{I} = \omega C V_m \angle (\theta + \pi/2)$

$\mathbf{I}$  can be rewritten as,

$$\mathbf{I} = \omega C V_m e^{j(\theta + \pi/2)} = \omega C V_m e^{j\theta} e^{j\pi/2} = j\omega C (V_m e^{j\theta}) = j\omega C \mathbf{V}$$

Thus, the impedance of a capacitor,  $\mathbf{Z} = \mathbf{V}/\mathbf{I}$ , is  $\mathbf{Z} = 1/(j\omega C)$ .

and the admittance of a capacitor,  $\mathbf{Y} = 1/\mathbf{Z}$ , is  $\mathbf{Y} = j\omega C$ .

Let us follow the same process now for a capacitor, and find its impedance marked as  $Z$  over here again.

So let this voltage across the capacitor  $v$  of  $t$  be equal to  $V_m \cos \omega t + \theta$ , what is the current? Current in that direction is  $C \frac{dv}{dt}$  and when we differentiate this quantity we get  $-\omega C V_m \sin \omega t + \theta$ . And now we can use the identity  $\cos \phi + \pi/2 = -\sin \phi$  and we get  $\mathbf{I}$  of  $t$  equal to  $C \omega V_m \cos \omega t + \theta + \pi/2$  like that. In terms of phasors phasor  $\mathbf{V}$  is  $V_m \angle \theta$ ,  $V_m$  is the magnitude and  $\theta$  is the angle and phasor  $\mathbf{I}$  is  $\omega C V_m \angle \theta + \pi/2$ .  $\omega C V_m$  is the magnitude and  $\theta + \pi/2$  is the angle.

Now we can rewrite  $\mathbf{I}$  as  $\mathbf{I} = \omega C V_m e^{j(\theta + \pi/2)}$  that is  $\omega C V_m e^{j\theta} e^{j\pi/2}$  and this quantity  $e^{j\pi/2}$  is nothing but  $j$ . So, we get then  $j \omega C V_m e^{j\theta}$ . Now this quantity is nothing but the phasor  $\mathbf{V}$  and therefore, we can write  $\mathbf{I}$  as  $j \omega C \mathbf{V}$ . In short phasor  $\mathbf{I}$  is equal to  $j \omega C$  times phasor  $\mathbf{V}$ , and therefore the impedance of a capacitor  $\mathbf{Z}$  is equal to  $\mathbf{V}/\mathbf{I}$  is  $\mathbf{Z} = 1/(j \omega C)$  and the admittance which is defined as  $\mathbf{Y} = \mathbf{I}/\mathbf{V}$  is  $\mathbf{Y} = j \omega C$  notice that we have  $\omega$  here now; that means, at low frequencies the impedance of a capacitor is large and at high frequencies the impedance is small.

(Refer Slide Time: 20:37)

**Impedance of an inductor**

Let  $i(t) = I_m \cos(\omega t + \theta)$

$$v(t) = L \frac{di}{dt} = -L \omega I_m \sin(\omega t + \theta)$$

Using the identity,  $\cos(\phi + \pi/2) = -\sin \phi$ , we get

$$v(t) = L \omega I_m \cos(\omega t + \theta + \pi/2)$$

In terms of phasors,  $I = I_m \angle \theta$ ,  $V = \omega L I_m \angle (\theta + \pi/2)$

$V$  can be rewritten as,

$$V = \omega L I_m e^{j(\theta + \pi/2)} = \omega L I_m e^{j\theta} e^{j\pi/2} = j\omega L (I_m e^{j\theta}) = j\omega L I$$

Thus, the impedance of an inductor,  $Z = V/I$ , is  $Z = j\omega L$ .

and the admittance of an inductor,  $Y = 1/Z$ , is  $Y = 1/(j\omega L)$ .

M. S. Rathi © 2014


Let us now repeat the process for an inductor let  $i$  of  $t$  be  $I_m \cos \omega t + \theta$ , then we get  $v$  of  $t$  as  $L \frac{di}{dt}$ , we can differentiate  $I$  of  $t$  and get  $v$  of  $t$  equal to  $-\omega L I_m \sin \omega t + \theta$ .

Now, we can use the identity  $\cos \phi + \pi/2$  is equal to  $-\sin \phi$  and get  $v$  of  $t$  has  $L \omega I_m \cos, \omega t + \theta + \pi/2$ . So, we have replaced this  $-\sin \omega t + \theta$  by  $\cos \omega t + \theta + \pi/2$ . Now in terms of phasors we have  $I$  equal to  $I_m \angle \theta$ ,  $I_m$  is the magnitude and  $\theta$  is the angle and  $V$  equal to  $\omega L I_m \angle \theta + \pi/2$  that is the angle and  $V$  can be rewritten as  $V$  equal to  $\omega L I_m e^{j\theta + \pi/2}$ , that is  $\omega L I_m e^{j\theta} e^{j\pi/2}$ , this is nothing but  $j$ ; so that becomes  $j \omega L I_m e^{j\theta}$  and this quantity is nothing but our phasor  $I$ .

So finally, we get phasor  $V$  equal to  $j \omega L$  times phasor  $I$  and from there the impedance of an inductor  $Z$  equal to  $V$  by  $I$  is  $Z$  equal to  $j \omega L$ , and the admittance of an inductor  $Y$  equal to  $I$  by  $V$  is  $Y$  equal to  $1$  over  $j \omega L$ . Notice that the inductor impedance also depends on the frequency, but it is directly proportional to the frequency; so at low frequencies the impedance is small and at high frequencies the impedance is large.

(Refer Slide Time: 22:47)

Sources

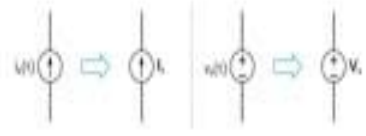

- An independent sinusoidal current source,  $i(t) = I_m \cos(\omega t + \theta)$ , can be represented by the phasor  $I_m \angle \theta$  (i.e., a constant complex number).
- An independent sinusoidal voltage source,  $v(t) = V_m \cos(\omega t + \theta)$ , can be represented by the phasor  $V_m \angle \theta$  (i.e., a constant complex number).
- Dependent (linear) sources can be treated in the sinusoidal steady state in the same manner as a resistor, i.e., by the corresponding phasor relationship. For example, for a CCVS, we have:  
 $v(t) = r i_c(t)$  in the time domain,  
 $V = r I_c$  in the frequency domain.

M. S. El-Helwan

Let us now look at sources sinusoidal current source and sinusoidal voltage source and independent sinusoidal current source  $I_s$  of  $t$  equal to  $I_m \cos \omega t + \theta$  can be represented by the phasor,  $I_m \angle \theta$  magnitude  $I_m \angle \theta$  that is simply a constant complex number. So, we have this source in the time domain and the corresponding phasor in the frequency domain, and that  $I_s$  is a constant. Similarly an independent sinusoidal voltage source  $v_s$  of  $t$  is equal to  $V_n \cos \omega t + \theta$  can be represented by the phasor  $V_m \angle \theta$ , that is the constant complex number like that. What about dependent sources? Dependent sources can be treated in the sinusoidal steady state, in the same manner as we treated a register that is by the corresponding phasor relationship.

For example, let us consider a CCVS that is current controlled voltage source; in the time domain we have  $v$  of  $t$  that is the voltage across the CCVS equal to  $r$ , a constant times  $i_c$  of  $t$  where  $I_c$  of  $t$  is the controlling current. Now in the frequency domain this relationship becomes  $V$  phasor equal to  $R$  times  $I_c$  phasor as simple as that; and similarly we can write relationships for the other dependent sources such as CCCS or VCVS etcetera.

In summary we have seen what phases are and how they can be used to represent currents and voltages in the sinusoidal steady state. We have also seen how R I and C can

be represented in the sinusoidal steady state using Phasors. In the next lecture we will extend these ideas to circuits, until then goodbye.