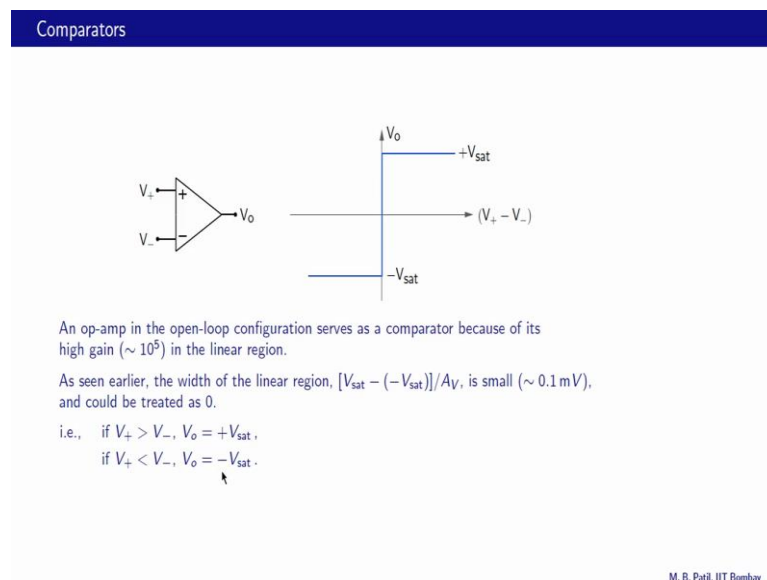


Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture - 51
Schmitt triggers (continued)

Welcome back to Basic Electronics. In the last class we have seen how a Schmitt trigger works we will now look at some applications of the Schmitt trigger we will see the advantage of using a Schmitt trigger as a comparator we will also look at the use of a Schmitt trigger in wave form generation. So, let us begin.

(Refer Slide Time: 00:41)




We will now look at some applications of Schmitt triggers, but before that let us talk about comparators, what is a comparator? It has 2 inputs plus and minus and 1 output, if V_+ is higher than V_- then the output is high and if V_- is higher than V_+ then the output is low and this figure here shows the relationship between V_o and $V_+ - V_-$.

Now this relationship looks familiar to us because we have seen that in the context of op-amp. An op-amp in the open loop configuration can serve as a comparator because of its very high gain something like hundred thousand in the linear region. This is our linear region and as we have seen the gain in the linear region is very high. As seen earlier the width of the linear region this width here is $V_{sat} - (-V_{sat})$ divided by A_V and

that is very small something like 0.1 millivolts and we can treat that as 0. So, in short if V_{plus} is greater than V_{minus} we can say that V_o is plus V_{sat} and otherwise V_o is equal to minus V_{sat} .


(Refer Slide Time: 02:12)

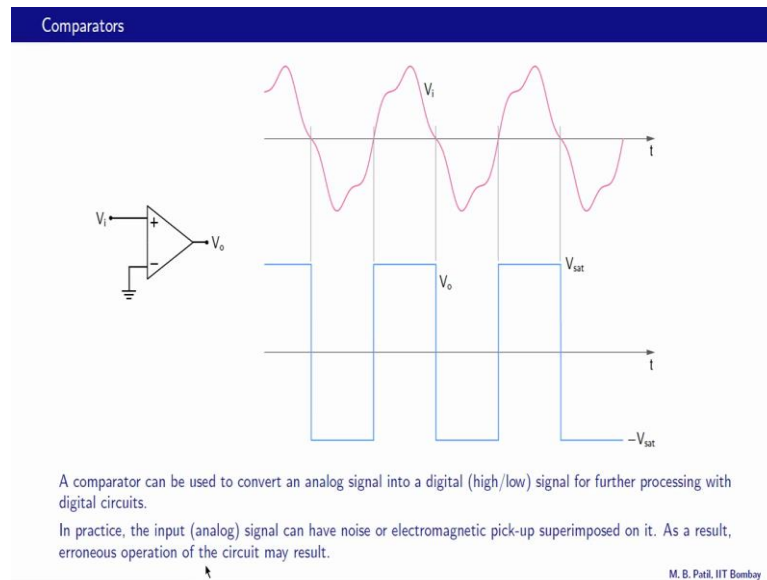

Here is an example of how a comparator works. This is a signal V_i which is applied here V_{minus} is at 0 grounded and if V_{plus} which is the same as the V_i is positive then V_o is high otherwise it is low. So, in this region V_o is high in this region V_o is low and so on and these levels actually need not be plus V_{sat} and minus V_{sat} there are comparators which can give levels of 0 and some positive voltage, but that is not important for our discussion. So, a comparator can be used to convert an analog signal for example this one into a digital that is high low kind of signal this 1 for further processing with digital circuits and we are going to look at digital circuits later.

In practice the input analog signal can have noise or electromagnetic pick up superimposed on it and because of that erroneous operation of the circuit may result and let us see an example of that situation in the next slide.


(Refer Slide Time: 03:50)

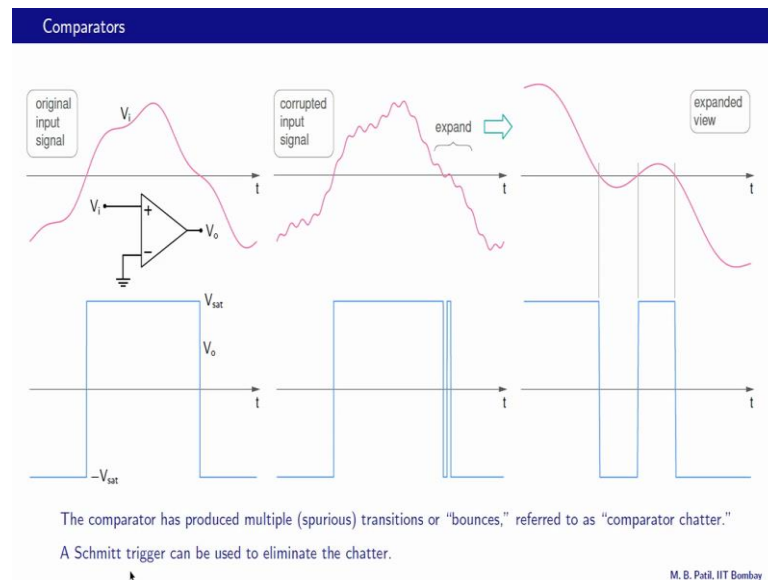

So, this is the situation we consider this is our input voltage and once again we have connected the minus input to ground and the plus input to V_i . So, the expected output is given here when V_i is positive we expect the output to be plus V_{sat} and when V_i is negative we expect the output to be minus V_{sat} , here as well as here. What happens with practice is that the input signal is not always clean there could be some noise or electromagnetic pick up riding on it and therefore, the original signal might get corrupted and might look like this for example.

And because of that instead of one transition that we expect from plus V_{sat} to minus V_{sat} we might have multiple transitions as shown here and let us expand this part to get a clearer picture of this situation. So, let us expand that part over here. So, this is our input signal and instead of crossing 0 only once as in this case it is crossing it here and then here and then here again and because of that the output transition is not just 1, but 1 2 and 3 and this is definitely not desirable. So, what has happened is the comparator has produced multiple spurious transitions or bounces which are referred to as comparator chatter. It turns out that we can use a Schmitt trigger to eliminate this chatter and let us see how we can do that in the next slide.

(Refer Slide Time: 06:07)

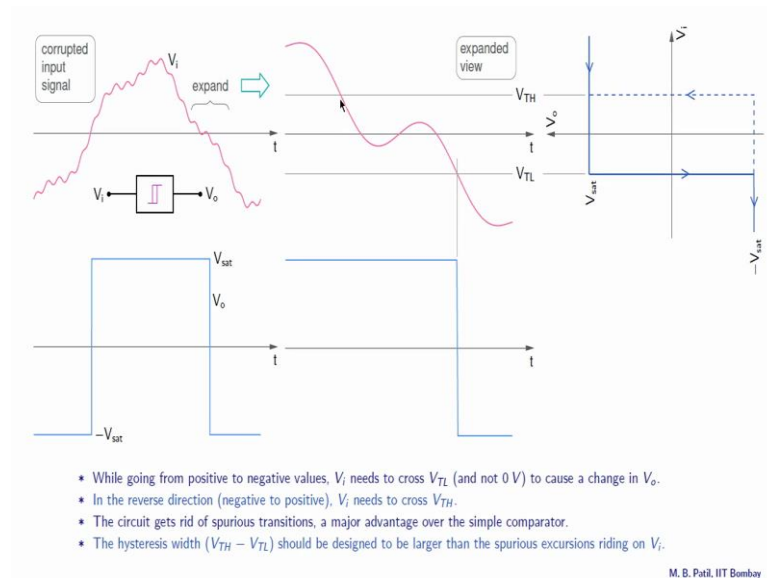

Let us now see how replacing the comparator with the Schmitt trigger helps in the situation. So, here is our corrupted input signal same as in the last slide and now this Schmitt trigger gives us only one transition and let us try to understand how that is possible. So once again let us expand this part to get this V_i versus time curve here and it has crossed zero, three times 1 2 and 3, but that has resulted in only one transition in the output that 1 and let us now try to understand why that happened.


So, here is our V_o versus V_i relationship for the Schmitt trigger and it looks a little different because our V_i axis is now drawn vertically, but it is the same as we have seen earlier this is V_{TH} , this is V_{TL} , this is the high V_o level V_{sat} and this is the low V_o minus V_{sat} . When the input voltage is here we are here on this V_o versus V_i relationship and now what is happening as time proceeds this input voltage is coming down so we are going in that direction and when is the output going to change the output is going to change not at V_{TH} , but at V_{TL} ; that means, the output will only change when the input voltage reaches this point and that is exactly where this transition is occurring.

Now what happens in between is not really important even if you had several transitions in this region it does not really matter because the input voltage has to cross this V_{TL} level to produce the transition at the output. So, that is how these spurious transitions are taken care of.

Let us summarize while going from positive to negative values V_i needs to cross V_{TL} and not 0 volts to cause a change in V_o . So, we are going from positive to negative it has to cross this point which is V_{TL} and only then the change in output will happen. In the reverse direction negative to positive V_i need to cross V_{TH} negative to positive. So, we are going like that and now we have to cross this level V_{TH} for the output to change.

The circuit gets rid of spurious transitions which is a major advantage over the simple comparator. The hysteresis width V_{TH} minus V_{TL} should be designed to be larger than the spurious excursions riding on V_i this is our hysteresis width and we should design it such that it is larger than these excursions which are adding on the input voltage then we will not have this problem of multiple transitions.

(Refer Slide Time: 10:04)

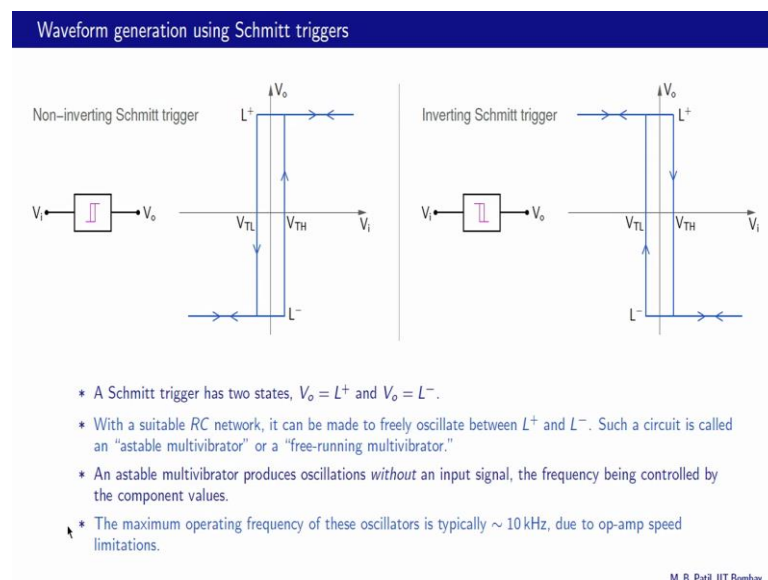


We will now look at another application of Schmitt triggers and that is to generate wave forms. In particular square wave output voltages here is a summary of the V_o versus V_i relationship for a non-inverting Schmitt trigger and an inverting Schmitt trigger and here are the symbols.

Let us make few important points a Schmitt trigger has 2 states V_o equal to L^+ and V_o equal to L^- , L^+ to L^- , L^- to L^+ . With a suitable RC network connected to this Schmitt trigger it can be made to freely oscillate between these 2 levels L^+ and L^- and such a circuit is called astable multivibrator or free-running multivibrator. An astable multivibrator produces oscillations without an input signal the

frequency being controlled by the component values such as resistance or capacitors and we should remember that the maximum operating frequency of these kinds of oscillators is typically about 10 kilohertz and that is because of op-amp speed limitations. As we have seen earlier op-amp has a Fahrenheit slew rate and therefore, this maximum operating frequency is limited.

(Refer Slide Time: 11:41)

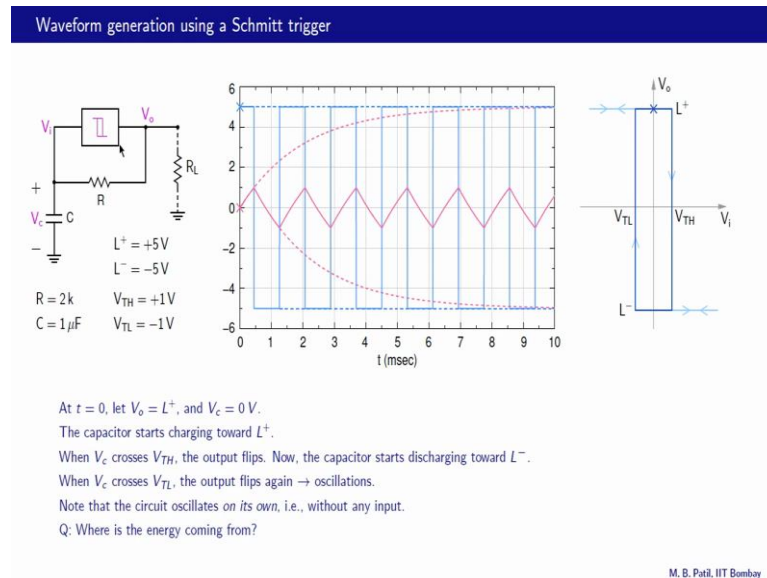

Let us take a look at this circuit, what do we have here? We have an inverting Schmitt trigger and that is its V_o versus V_i relationship and its reproduced here, this is the high tripping point V_{TH} , low tripping point V_{TL} - L^+ is the high level of V_o and L^- is the low level of V_o , this axis is V_o this axis is V_i , V_o is here and V_i is here. So, V_i is the same as the capacitor voltage.

Let us take some numbers R equal to $2k$, C equal to 1 micro Fahrenheit L^+ plus plus 5 volts L^- minus minus 5 volts V_{TH} plus 1 volt V_{TL} minus 1 volt. So, this is plus 1 volt here minus 1 volt, plus 5 minus 5 and as we will discover this circuit oscillates between high and low and let us see how that happens.

Let us start at t equal to 0 with V_o equal to L^+ and V_c equal to 0 ; that means, the capacitor is uncharged and V_c and V_i are the same. So, our V_c equal to V_i equal to 0 and our V_o is L^+ . So, we are right here that is the data point that we have right now at t equal to 0 , what happens now? This input current is 0 , this V_o is plus 5 volts capacitor voltage is 0 . So, the capacitor is going to start charging towards V_o that is plus

5 volts and the time constant of course, is R times C is only one R here and that are 2 k times 1 micro or 2 milliseconds.


Note the scale here this entire period is 10 milliseconds. So, let us show this charging process that is how the capacitor will charge. Since the time constant is 2 milliseconds in about 5 time constants that is 10 milliseconds it would charge towards 5 volts and the charging process would be almost completed. Now it does not quite reach there and let us see why. Let us look at what is happening with respect to this V_o vs V_i relationship we started of here at t equal to 0. So, our V_c or V_i was 0 our V_o was plus 5 and now this capacitor has started charging, what does it mean? That means, V_i has started increasing V_i and V_c are the same, so therefore, we are moving like that.

And what happens when V_i crosses V_{TH} the output flips like that and now what happens is this V_o has become minus 5 volts and the capacitor will now start discharging and will eventually reach minus 5 volts, but again that does not happen why? Because as the capacitor discharges we are moving like that V_o is minus 5 and V_i is decreasing so we are moving in that direction and when we cross V_{TL} again the output is going to change and this process is going to result in oscillations like that.

So, at this point the output changed to plus 5 again, the capacitor now starts charging again towards 5 volts like that and so on. So, this process just keeps repeating and we have oscillations. So, our V_o is a square wave where plus 5 to minus 5 and we get this kind of wave form for V_c or V_i .

Note that the circuit oscillates on its own that is without any input there is no input anywhere for this circuit. Question, where is the energy coming from, what is the answer to that? Remember there is an op-amp sitting inside. So, that is where the energy is coming from specifically the power supply of the op-amp.

(Refer Slide Time: 17:13)

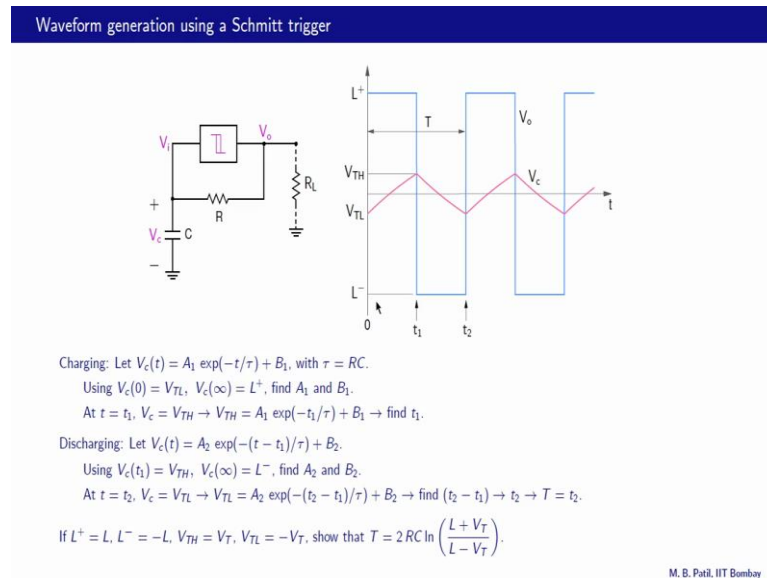

Let us now find the period of oscillation here are the wave forms V_o going from L^+ plus to L^- minus and V_i or V_c going from V_{TL} to V_{TH} . If you recall in the last example we had V_{TL} is equal to minus 1 volt V_{TH} is equal to plus 1 volt L^- minus was minus 5 volts and L^+ plus was plus 5 volts, all right. So, where do we begin let us consider this portion, this is the charging process and the capacitor is going to charge towards L^+ plus and that process can be described by this expression $V_c(t) = A_1 e^{-t/\tau} + B_1$ where τ is simply R times C . What is V_c at 0? This is our t equal to 0 to V_c is V_{TL} . What is V_c at infinity? At infinity this capacitor voltage would reach L^+ plus. So, that is our V_c at infinity.


Now, using these 2 conditions we can find A_1 and B_1 , you are suppose to do it as homework and now let us use the condition that at t equal to t_1 this point V_c is equal to V_{TH} . So, we substitute V_c is equal to V_{TH} in this expression $A_1 e^{-t_1/\tau} + B_1$ by V_{TH} , A_1 and B_1 are already known from these conditions and that gives us t_1 .

Let us now look at the discharging transient this part at t equal to t_1 the capacitor voltage is equal to V_{TH} and then it starts decreasing and it would have gone all the way to L^- minus as t tends to infinity. However, that does not happen because at t equal to t_2 the output voltage flips and let us now describe this part of the transient in this equation here $V_c(t) = A_2 e^{-(t - t_1)/\tau} + B_2$ and this amounts to taking this t_1 as the reference or the origin and that turns out to be convenient plus B_2 .

Now, to find A_2 and B_2 we need 2 conditions on V_c of t what are those 2 conditions? One at t equal to t_1 V_c is V_{TH} . What about the second condition? As t tends to infinity V_c would have reached L minus, so that is the second condition. So, using these 2 conditions we can find A_2 and B_2 and now we can use the condition that at t equal to t_2 V_c is equal to V_{TL} . So, we substitute V_{TL} over here and t_2 over here and then we get V_{TL} equal to $A_2 e^{-t_2 - t_1 / \tau} + B_2$ and A_2 and A_2 of course, are already known from here, all right. So, with this equation we can now obtain $t_2 - t_1$, t_1 is already known and therefore we can get t_2 and t_2 is the same as the time period T .

So, let us now take a special case let us say that L plus and L minus are equal in magnitude for example, this maybe 10 volts this may be minus 10 volts and V_{TH} and V_{TL} are also equal in magnitude for example, this may be 2 volts and this maybe minus 2 volts. In that case we can show that this time period that is a period of oscillation is given by $2 RC \times \log \frac{L + V_t}{L - V_t}$, where L is this L plus and V_t is the same as V_{TH} . Now you are encouraged of course, to go through all of this algebra and arrive at this result.


(Refer Slide Time: 21:56)

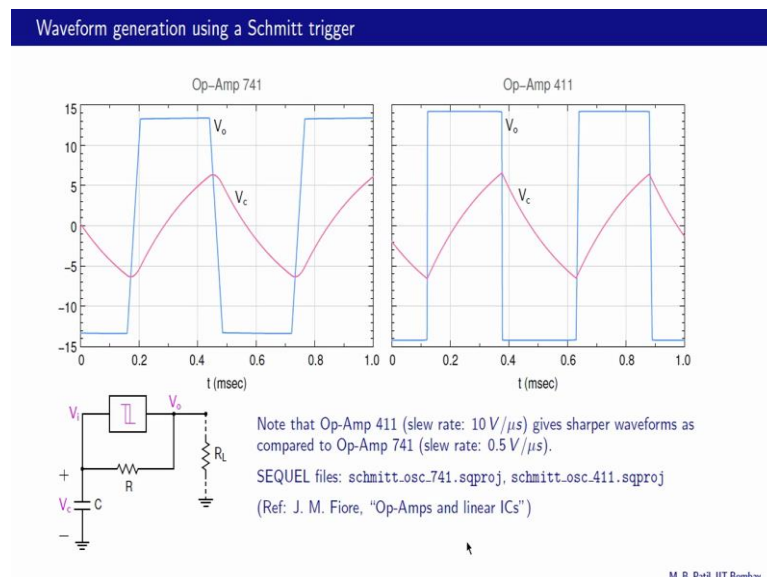

If you hookup this circuit in the lab you will realize that it cannot be pushed to arbitrarily high frequencies and that is because op-amps have a finite slew rate for example, op-amps 741 has a slew rate of 0.5 volts per micro second. This is the wave form obtained

with op-amp 741 and as we can see it is not as sharp as we would expect theoretically, we have these slopes here. Whereas, if we use another op-amp with a higher slew rate like op-amp 411 which has much higher slew rate 10 volts per micro second then we can get sharper wave forms. So, that is an important point and we should remember that if we want to implement that in the lab or for some application.

(Refer Slide Time: 22:57)

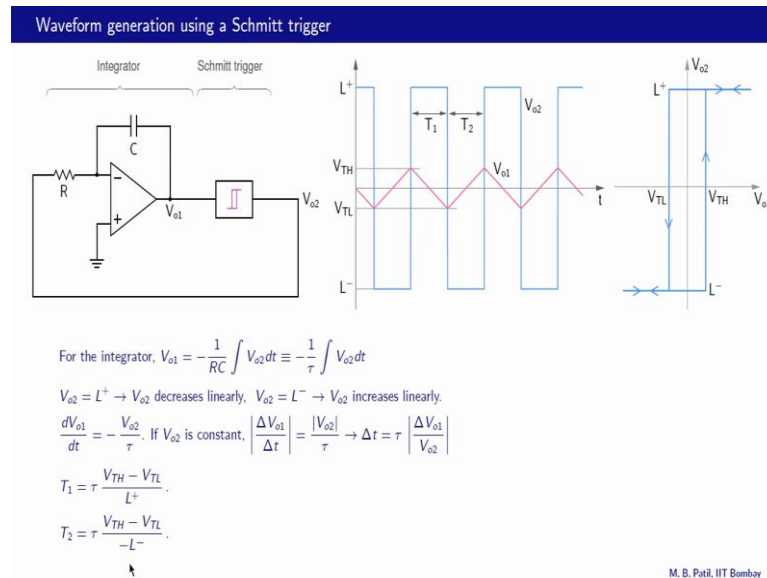

Here is another oscillator circuit that uses Schmitt trigger. It has an interrogator and a Schmitt trigger connected in a circular fashion that is the output of the interrogator goes as the input of the Schmitt trigger and the output of the Schmitt trigger is the input of the integrator. The V_o versus V_i relationship for the Schmitt trigger is shown here, it is a non-inverting Schmitt trigger, V_{TH} and V_{TL} are the tripping points and the L^+ and L^- are the high and low output voltage levels. This axis is the output of the Schmitt trigger and in this case it is V_{o2} and this axis is the input of the Schmitt trigger and in this case it is V_{o1} .

So, note that V_{o2} servers as input for the integrator. These are the wave forms that are V_{o2} the blue 1 and that is V_{o1} and V_{o1} is a triangular wave form in this case as opposed to the capacitor voltage wave form that we saw in the last circuit. Let us look at how this circuit works let us start with the integrator. For the integrator we have V_{o1} which is the output equal to minus 1 over RC integral $V_{o2} dt$, V_{o2} is the input for the integrator and we rewrite that as minus 1 over τ integral $V_{o2} dt$ if V_{o2} is positive V_{o1} will


decrease and V_o . If V_o2 is negative then V_o1 will increase and that is because of this negative sign.

So, let us consider the case where V_o2 is positive let us say this interval marked t_1 here. So, here V_o1 is decreasing because V_o1 is positive and what is happening in terms of this V_o versus V_i relationship for the Schmitt trigger? V_o2 is 5 so we are here and V_o1 is decreasing so we are going in that direction. When we cross V_{TL} output is going to flip from high to low and that is what happens here.

When V_o2 changes its sign as it goes from L_+ to L_- there is a change of sign here and therefore, V_o1 now starts increasing that is what we are seeing over here and in terms of this plot what is happening is V_o2 is negative L_- so that is here and V_o1 is increasing so we are going in that direction. And now when we cross V_{TH} V_o2 will change once again from negative to positive. So, that is what happens at this point, V_o2 changes from L_- to L_+ and this process keeps repeating and that is how we get oscillations.

Let us now compute the period of oscillation what is the period of oscillation? T that is equal to T_1 plus T_2 , we can compute T_1 and T_2 individually and then add the two. And an easy way to do that is to just differentiate this equation when we do that we get $dV_o1/dt = -V_o2/\tau$ and if V_o2 is constant then we can write $\Delta V_o1/\Delta t = -V_o2/\tau$ just taking only magnitudes here. That gives us $\Delta t = \tau \times \Delta V_o1/V_o2$ and now we can apply that to each of these intervals T_1 as well as T_2 and that gives us $T_1 = \tau \times (V_{TH} - V_{TL})/V_o2$ that is our ΔV_o1 divided by V_o2 , V_o2 is L_+ at that time. What about T_2 ? Similar ΔV_o1 is once again the same this difference and V_o2 is now L_- and of course, we have to take the magnitude of that so therefore, we have put a minus L_- here, so that is T_1 and T_2 . So, the period is T_1 plus T_2 and that gives us the frequency equal to $1/T$.

(Refer Slide Time: 28:21)

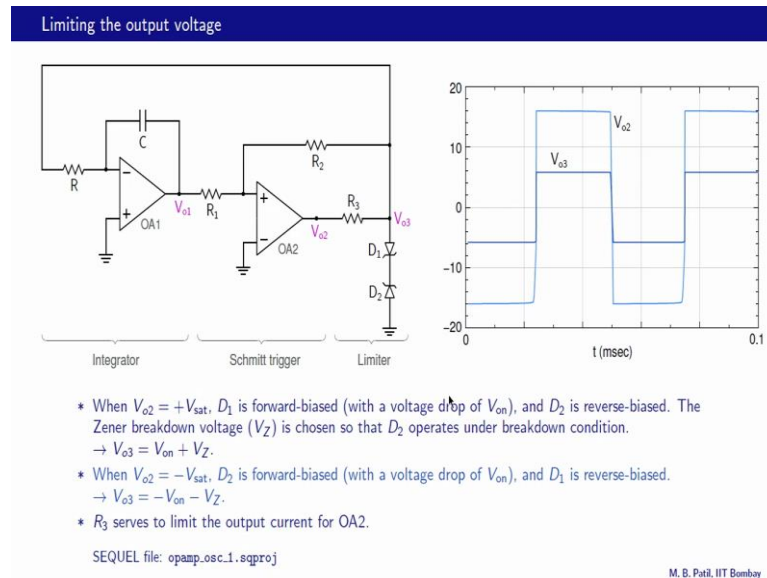

Sometimes we are interested in limiting the output voltage that is produced by this Schmitt trigger which we call V_{o2} in our previous slide and that can be done using this diode pair and we have looked at this diode pair and seen how it works as a voltage limiter when we were talking about diodes. When V_{o2} is high let say this is our V_{o2} level the high level then D_1 conducts in the forward direction, D_2 conducts in the reverse breakdown mode and then V_{o3} this output voltage is V_{on} plus V_Z , V_{on} appearing here and V_Z appearing here. When V_{o2} is minus V_{sat} this level then what happens is D_2 conducts in the forward direction D_1 conducts in the reverse built on mode. So, V_{on} appears here V_Z appears here and the output voltage V_{o3} is minus V_{on} minus V_Z , that level.

Now, let us look at the purpose of R_3 and that is to limit this current that we draw from this second op-amp. What is the voltage that is appearing across R_3 ? It is the difference between V_{o2} and V_{o3} either that or that and you can calculate R_3 . So, that the current that we draw from OA2 the second op-amp is within its current limits. Here is the circuit file you can simulate this circuit and take a look at the results.

To conclude we have seen the advantage of Schmitt trigger as a comparator, we have also looked at wave form generation using a Schmitt trigger. In the next class we will continue our discussion of the Schmitt triggers, until then goodbye.