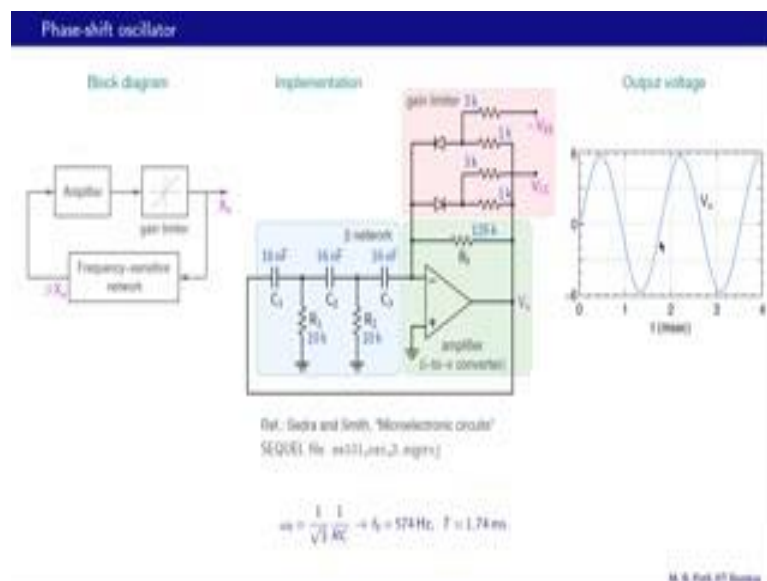


Basic Electronics
Prof. Mahesh Patil
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Lecture – 54
Sinusoidal oscillators (continued)

Welcome back to Basic Electronics. In this lecture, we will continue with sinusoidal oscillators; and look at how the output amplitude can be controlled using a gain limiting network. After that, we will consider an important limitation of amplifier circuits, which we have not addressed so far, and that is frequency response. We will first look at the frequency response of an inverting amplifier for different gain values; we will then explain this frequency response with a realistic model of the op-amp. Let us get started.

(Refer Slide Time: 00:57)



So, here is our complete implementation. And let us first relate the implementation with our block diagram. What is X_o in the implementation that is of course V_o , what about X_f which is beta times X_o . X_f in this case is this current here not shown, but as we discussed in the last slide X_f in this case is not a voltage, but it is a current. What is our A , our A is not a voltage to voltage gain, but it is a voltage it is a current to voltage gain and that to be found to be equal to minus R_f . Now, for this beta network we found that ω_0 would be $1/\sqrt{3}RC$ and that gave us f_0 equal to 574 hertz and we have already done that calculation previously just repeating it here. And our R_f ,


we found in the last slide should be equal to 12 times R, R here is 10 k. So, twelve times 10 k is 120 k, and we make it slightly larger than 120 k, so that is how we get this 125 k and that is done as we mentioned earlier to make sure that the circuit does oscillate on power up.

This is the gain limiter block. And we have seen this circuit earlier, if you recall. Let us see how it works. We have seen that the gain of this amplifier is minus R f. Now, when this voltage is small these diodes are off, and the only resistance then is R f, so the gain is large. When this voltage increases either in the positive direction or in the negative direction one of these diodes turns on and then this net resistance decreases and that is how the gain decreases as the voltage increases, so that is how gain limiting is achieved.

Here is the output voltage obtained by simulation. And the circuit file is specified here, you can try out the simulation as well. And let us check whether it shows the correct frequency. The frequency of oscillation that we expect is f_0 equal to 574 hertz and that gives us a period T equal to $1/f_0$ equal to 1.74 milliseconds. And we see that in 1.74 milliseconds somewhere here, we do have 1 cycle, and therefore the result seems to be correct.

Now, the question that arises is can we do something about this amplitude, the answer in this case is yes, we can play with these parameters here, and use those to change the amplitude of the output voltage. And let us see how that can be done.

(Refer Slide Time: 04:21)

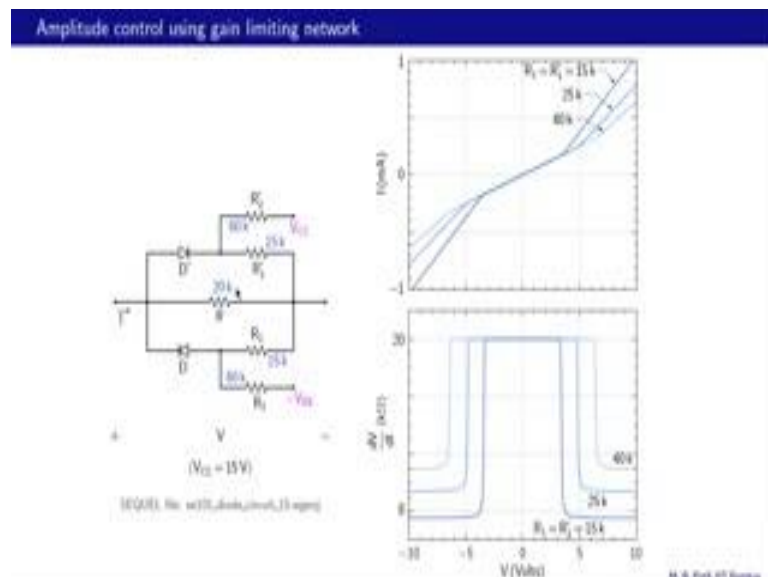


Here is the gain limiting network that we used in the phase shift oscillator. The values are a little different but not very important. And if you recall we have seen this circuit earlier with these values 60 k, 16 k and 20 k and in that situation we had obtained I versus V given by this dark curve here and dV/dI where V is this voltage and I is this current was given by this curve here. So, in this region of the voltage, the resistance is constant and then on either side it starts dropping because one of these diodes starts conducting; or our gain limiting happens when this resistance falls here.

Let us now connect this picture with the amplifier that we saw in the phase shift oscillator in the last slide. And if you recall the gain was proportional to minus Rf . So, when the resistance is high the gain is high; and when the resistance drops the gain becomes low. In other words, the gain is constant in this region; and outside it drops and that is what causes amplitude limiting. Now, if we increase the width of this region then we will also increase the amplitude, so that is the basic idea behind amplitude control here.

How can we change the width of this region, there are different ways of doing it. We can change R_1 and R_1 prime together or we can change R_2 and R_2 prime together or we can change this power supplier. Of course, the last option is not very practical because we do not want to change the power supply values. What we have done here in this plot is we have changed R_1 and also R_1 prime. This is the plot for 15 k the dark one as we have seen already. The next plot is for 25 k; that means, this resistance is 25 k, this one is also 25 k and the one after that is for 40 k.

As we change the resistance value, we notice that the breakpoint also shifts. Here is the break point for 15 k; for 25 k it is here, and for 40 k it is here. It can be more clearly seen in this bottom picture that is the break point for 15 k; for 25 k it is here and for 40 k it is here. So, if we change the resistance from 15 k to 40 k, what it means is that the amplitude will change from about this much to about that much. And let us check that out now with the help of simulation in the next slide.


(Refer Slide Time: 07:44)

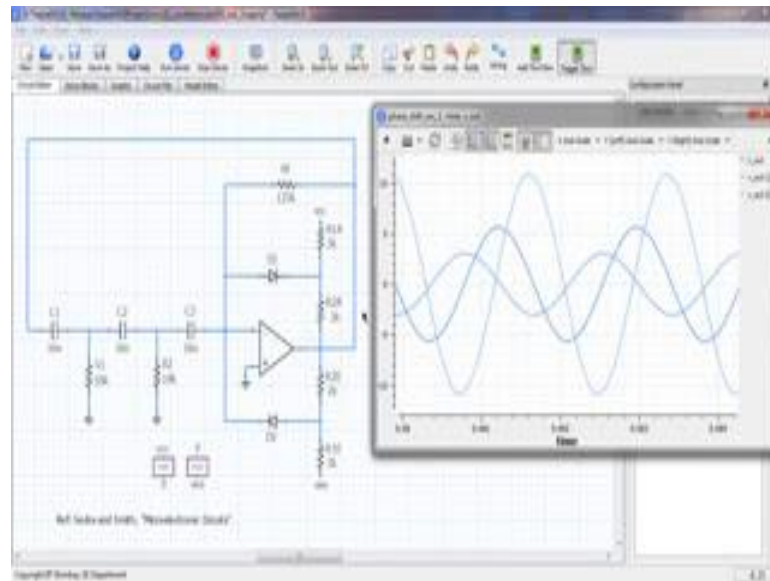

Let us now look at the simulation results for the phase shift oscillator. The component values here R and C and R_f are the same as what we had in the last slide. So, the frequency of oscillation is expected to be the same namely 574 hertz and that corresponds to a time period of 1.74 milliseconds if you recall. What we have done here is change this resistance and that means that we also change this resistance and the output voltage is plotted for three different values of the resistance. This waveform corresponds to a resistance of 0.5 k, this one 21 k, and this one 22 k, and the amplitude control can be clearly observed.

The frequency of oscillation of course, does not change and we can check that out we can identify the peaks, for example, this one and this one, see the difference between these two peaks and that should turn out to be 1.74 milliseconds and that will be also true about the other waveforms. So, we can take the difference between this and that or that and that and all of these will turn out to be 1.74 milliseconds. Now, one comment about the phase of these waveforms, the phase is different for each of them, but the phase is not particularly relevant here and we can just ignore it.

(Refer Slide Time: 09:26)

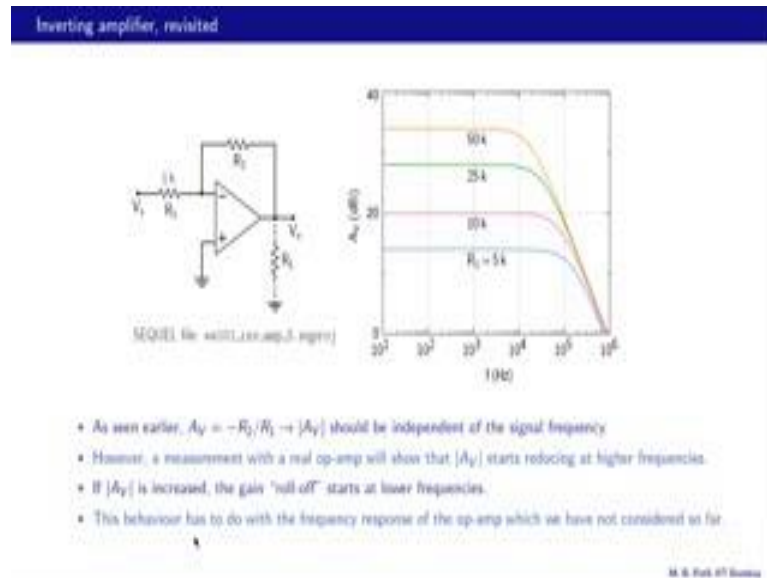


Let us now revisit the inverting amplifier, which we have seen earlier; and discuss a very important topic, which we have not touched upon so far. So, here is an inverting amplifier circuit with R_1 equal to 1 k. And we are going to change R_2 , consider different values of R_2 and that is why we have not specified the value here. As we have seen earlier, the voltage gain for this amplifier is minus R_2 by R_1 . And we expect the gain to be independent of the signal frequency, but that does not happen in real life. The measurement with a real op-amp shows that the gains starts reducing at higher frequencies and let us see how. Here is a plot of the gain in dB versus frequency in hertz where the frequency is plotted on a log scale. And we consider various values of R_2 - 5 k, 10 k, 25 k, and 50 k. Let us look at the R_2 equal to 5 k curve, what is the gain for this R_2 it is R_2 by R_1 . So, 5 k by 1 k or 5 we have to convert that to dB of course, and that gives us this value here.

Now, the important point to observe is that the gain is constant for much of this frequency range all the way up to say 10 kilo hertz or little higher than that, but at some point it starts falling and this fall is called the roll-off the gain with frequency. What happens if we change R_2 from 5 k to 10 k, the gain doubles and we have a higher gain here, but also the roll-off of the gain with frequency starts happening at a lower frequency. Now, for 5 k it happened here; for 10 k it is happening here; and for 50 k its happening at an even lower frequency, so that is a very important point to observe and it has of course, important practical implications as well. So, if the gain is increased the

gain roll-off starts at lower frequencies. And this behavior has to do with the frequency response of the op-amp which we have not considered so far. So, let us look at it now.

(Refer Slide Time: 12:09)

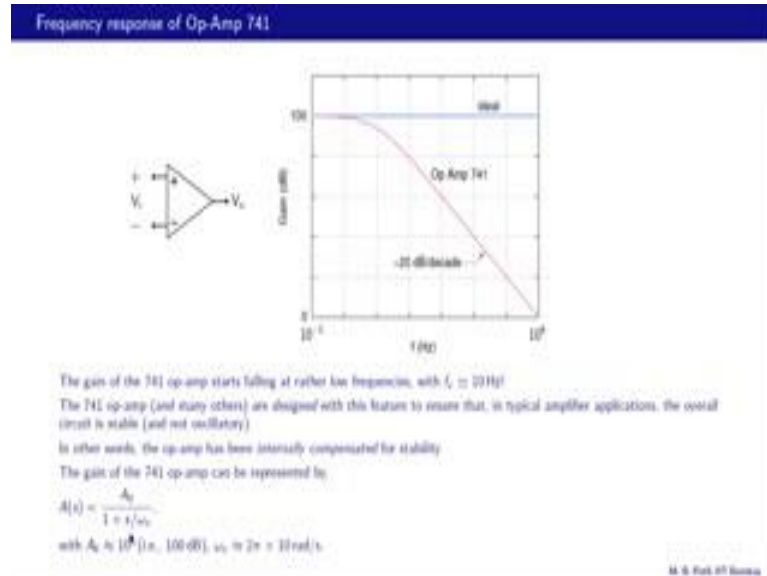


Let us start with the frequency response of the op-amp; in particular op-amp 741 here is the gain in dB versus frequency in hertz and we are plotting the frequency on log scale going from 0.1 hertz all the way up to 1 mega hertz here. So, it is 0.1 hertz, 1 hertz, 10 hertz 100 hertz and so on. Now the ideal response of the op-amp 741 would be flat that is it would be independent of the frequency, but this is what the real response looks like it starts dropping off at some frequency here and then it reduces at the rate of minus 20 dB per decade. And if we join this asymptote with this one, they intersect at about 10 hertz. So, what it means is that the gain of the 741 op-amp starts falling at rather low frequencies with a cutoff frequency or 3 dB frequency of only 10 hertz.

And this may come as a surprise, but this fall off at 10 hertz is not accidental the 741 op-amp and many others in fact, are designed with this feature that is a fall off at a relatively low frequency like 10 hertz. And that is done to ensure that in typical amplifier applications, the overall circuit is stable and not oscillatory. In other words, the op-amp has been internally compensated for stability. And you will learn more about stability of amplifiers in an advanced analog circuits course. For now, it suffices to know what the op-amp 741 frequency response is like; and with that in mind we will now try to

understand the frequency response of the inverting amplifier which we saw in the last slide.

The frequency response of the 741 op-amp can be represented by this equation here A of s or $j\omega$ equal to A_0 divided by $1 + s$ by ω_c . And it is easy to figure out where this is coming from. This is our frequency response. We have only one corner frequency somewhere here two asymptotes that one and that one; and this asymptote has a slope of minus 20 dB per decade. So, what it indicates is that there is only one single pole in this entire system. And therefore, A of s is equal to A_0 by $1 + s$ by ω_c . A_0 is the low frequency gain which is 100 dB, 100 dB corresponds to 10^5 . So, A_0 is just a constant equal to 10^5 ; and ω_c is the cutoff or corner frequency that is somewhere here; and in hertz, it is about 10 hertz in radians per second, it is 2π times 10 radians per second.


(Refer Slide Time: 15:32)

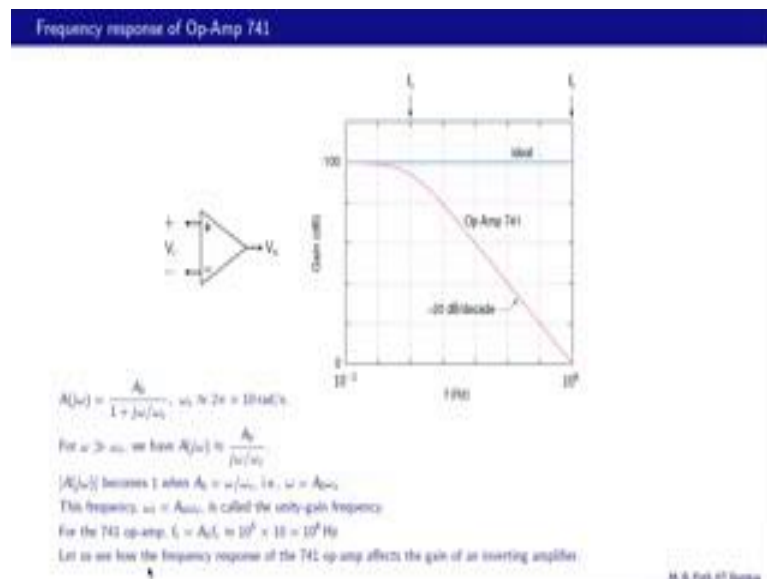

So, here is our A of $j\omega$ again, A_0 which is a constant divided by $1 + j\omega$ by ω_c , where ω_c is about 2π times 10 radians per second. Now, let us consider the case where ω is much larger than ω_c so that means, we are away from this cutoff frequency say somewhere here. And in that case, this one is small and we get A of $j\omega$ equal to A_0 divided by $j\omega$ by ω_c . And note that this quantity becomes 1, the magnitude of A of $j\omega$ becomes 1, when A_0 is equal to ω by ω_c that is when ω becomes equal to A_0 times ω_c . And this frequency

omega equal to A naught times omega c is called the unity gain frequency; and it is denoted by omega with a subscript t. And for the 741 op-amp, the corresponding frequency in hertz which is denoted by f with a subscript t is A 0 times f c, where f c is this corner frequency or the 3 dB frequency that is 10 raise to 5 times 10, A 0 is 10 raise to 5 and f c is 10 hertz. So, that f t for the 741 op-amp turns out to be 10 raise to 6 hertz. So, that is our unity gain frequency for the 741 op-amp. So, f c is marked over here in the plot and f t is 10 raise to 6 hertz. Now, let us see how the frequency response of the 741 op-amp affects the gain of an inverting amplifier.

(Refer Slide Time: 17:34)

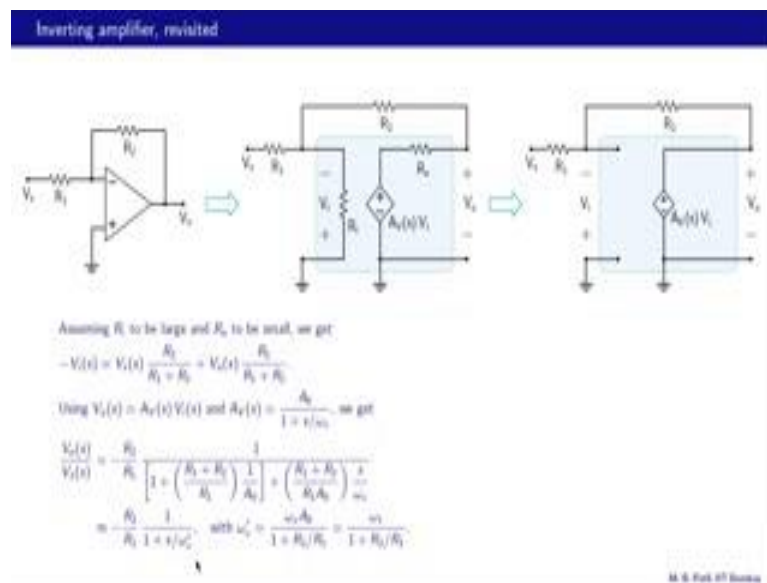

Here is our inverting amplifier and we want to understand its frequency response now which we have seen earlier. First, what we will do is replace the op-amp with its equivalent circuit model consisting of the input resistance R_i , the output resistance R_o and this gain element. We will assume that the input resistance is very large. So, that becomes an open circuit the output resistance is very small, so that is a short circuit, and that gives us this equivalent circuit over here. Open circuit here and a short circuit here. And now what we want to do is to get V_o by V_s as a function of frequency and that frequency dependent of course, will come from the frequency dependence of A_V of the op-amp which is shown over here as A_V of s .


So, let us start with the voltage at this node with respect to ground and we can obtain that by superposition. We have V_s here and we have V_o here with respect to ground. And

using these two voltage sources, we can calculate the voltage at this node by superposition. And what is that node voltage that is minus V_i with respect to ground. So, that gives us one equation like that. So, minus V_i is equal to V_s times R_2 by R_1 plus R_2 plus V_o times R_1 by R_1 plus R_2 ; and this part we have got using superposition.

Now, let us use the fact and that V_o is a V times V_i , this voltage is a V times V_i . And we also know the frequency dependence for the op-amp gain that is A_V of s equal to A_0 divided by $1 + s$ by ω_c . So, using these two and putting these back here we get the following relationship between V_o and V_s minus R_2 by R_1 , 1 divided by all of this and you are definitely encouraged to derive this equation yourself. Now, this term is small because A_0 is a large number 10^5 .

And therefore, we can ignore this term with respect to this 1 here. And now we can rewrite the gain of the inverting amplifier V_o by V_s this one as minus R_2 by R_1 times 1 divided by $1 + s$ over ω_c . Now, this expression here is the same as this term; and ω_c is ω_c times A_0 divided by $1 + R_2$ by R_1 . Now, ω_c times A_0 we have seen before and that is denoted by ω_t that is the unity gain frequency of the op-amp. And for op-amp 741 as we have seen earlier, it is 2×10^6 radians per second. So, now, we know the gain of the inverting amplifier as a function of frequency, this expression here; and we can now proceed and plot the gain versus frequency for different values of R_2 .

(Refer Slide Time: 21:14)

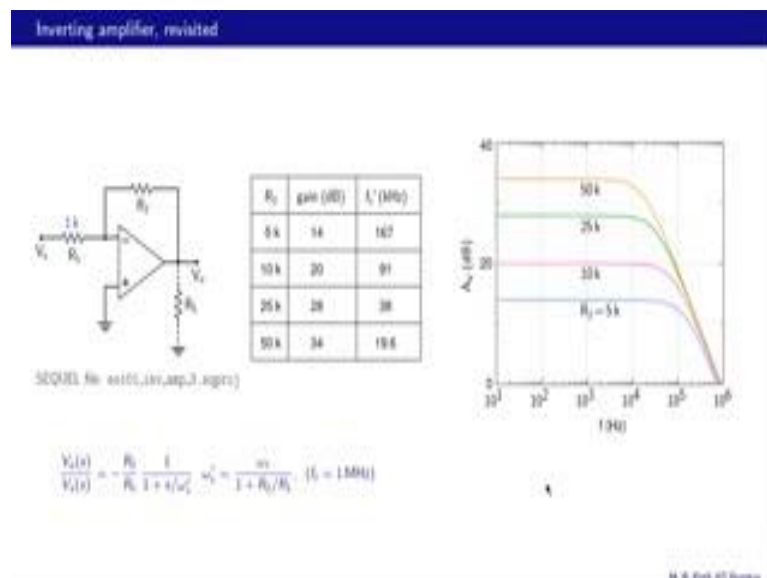

So, here is the gain expression again V_o by V_s minus R_2 by R_1 times 1 by $1 + s$ by ω_c prime. So, just a single pole, where ω_c prime is ω_t divided by $1 + R_2$ by R_1 ; and ω_t is 2π times f_t , where f_t is one megahertz for the 741 op-amp. So, now what we will do is prepare this table, and also plot the gain as a function of frequency for various values of R_2 . For each R_2 , we will note down the gain the low frequency gain which is given by R_2 by R_1 , and also the corner frequency or the 3 dB frequencies which is f_c prime the same as ω_c prime by 2π .

With R_2 equal to 5 k, the gain is 5 k by 1 k or 5, and that is 4 dB; and the corner frequency f_c prime is f_t divided by $1 + R_2$ by R_1 , so that is 1 mega hertz divided by 6 that turns out to be 167 kilo hertz. And we can see that in this plot here this is 14 dB and the intersection of these two asymptotes this one and this one should be the corner frequency. So, let us see this is 1-kilo hertz, 10-kilo hertz, 100-kilo hertz, that is 200-kilo hertz. So, these asymptotes will intersect somewhere between these two and we see that that is indeed happening.

When R_2 is increased to 10 k, the gain goes up, but f_c prime - the corner frequency goes down. And now we are in a position to understand why this happens we have this R_2 here in the denominator, and therefore as R_2 goes up f_c prime goes down. And that of course, reflects in this graph here. The gain has gone up and the 3 dB point or the corner frequency has moved from there to there and so on; as we keep increasing R_2 the gain goes on increasing, but f_c prime the corner frequency goes on decreasing, so that explains our earlier observation. And the important message to take home from here is that there is a tradeoff between gain and bandwidth; we cannot have high gain as well as high corner frequency at the same time.

To summarize, we have looked at amplitude control in sinusoidal oscillators using a gain limiting network; we then looked at the frequency response of an inverting amplifier and explain why the gain drops at high frequencies. In the next class, we will start our discussion of digital circuits, until then goodbye.