

Microwave Theory and Techniques
Prof. Girish Kumar
Department of Electrical Engineering
Indian Institute of Technology, Bombay

Module - 03
Lecture – 14
ABCD – Parameters


Hello, in the last few lectures we have been talking about transmission line. We saw different types of transmission line like coaxial line, microstrip line, strip line and waveguides. After that we looked into transmission line loaded with a load impedance Z_L , then we took different cases of Z_L for example, Z_L equal to 0, Z_L equal to infinity, Z_L equal to Z_0 , and then we took 2 special cases of length equal to $\lambda/4$ and $\lambda/2$. And we saw that when the length is $\lambda/4$ it acts as a quarter wave transformer.

After that we discuss about smith chart, and we actually saw how easily we can plot complex impedance values and also how impedance matching can be done using smith chart. So, we looked into two different techniques one was lumped element technique and the second one was single step matching. Today we are going to talk about ABCD and S parameters.

So, now we are not going to learn what you studied in your very low class which is ABCD, but we are actually going to look at the ABCD parameters which are defined in terms of voltages and currents. And then we will talk about S parameters which are defined in terms of wave parameters because at microwave we actually are more interested in the waves than just in voltages and currents. Then you might wonder then why we are discussing about ABCD parameters which are mainly concerned with voltages and currents. So, I am going to show you how ABCD parameters are very convenient to solve a complex network, and then we will talk about how ABCD parameters can be converted to S parameters.

(Refer Slide Time: 02:15)

ABCD Parameters

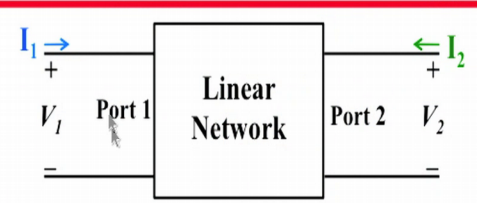

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$


$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \text{ ohm}$

$V_1 = AV_2 - BI_2$

$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \text{ mho}$

$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$

$I_1 = CV_2 - DI_2$


Microwave Theory and Techniques | Prof. Girish Kumar, IIT Bombay
2

So, let us first look at what is the definition of the ABCD parameter. So, here we have a two port network, so port 1, port 2 and this is a linear network and let us see that the input voltage here at port 1 is V 1 and at port 2 voltage is V 2.

Current is coming into the port 1, and current is also coming into the port 2. In fact, this has been a general definition you might have studied Z parameters or Y parameters. In case of Z parameters just to refresh your memory. What we have generally for Z parameters? V 1 and V 2 are on one side, I 1 and I 2 are on the other side and in between there is a Z matrix Z 11, Z 12, Z 21, Z 22. In terms of Y matrix or Y parameters we have I 1, I 2 on the left side and V 1, V 2 or on the right side and then there is a Y matrix.

In fact, there are hybrid parameters are also there which actually consist of voltages and currents and you might have studied those hybrid parameters for transistors. Here we are going to look at ABCD parameters and the way ABCD parameters are defined which actually becomes easier later on as we will see to solve a complex network. So, let us see what ABCD parameters are related to.

So, voltage at port 1 and current at port 1, relate to voltage at port 2 and current at port 2. Now, you might see there is a minus sign over here this minus sign is coming because we have taken this current as in coming at port 2. If we take this current I 2 as outgoing then this will become plus. In fact, many a times you can just think about it that if this is I 2 which is coming in just think about this is current let us say I 2 dash and which is leaving

here, then I_2 dash will be nothing but minus I_2 and that will be here then plus I_2 dash, ok. So, it just says matter of notation.


So, how do we define ABCD parameter? Let us open the matrix first. So, V_1 is nothing but A multiplied by V_2 then minus B times I_2 . And what is I_1 ? I_1 is nothing but C multiplied by V_2 minus D times I_2 . So, these are the ABCD parameters. Now, by using these 2 equations we can find out the ABCD parameter. So, let us see what is A ? We can say from here A will be equal to V_1 by V_2 provided I_2 is equal to 0. So, if we put a boundary condition is I_2 equal to 0 which is what has been put over here, then what will be A ? V_1 divided by V_2 . So, you can actually think about A is nothing but voltage ratio provided I_2 is equal to 0. And in what condition I_2 will be equal to 0? If this particular port is open circuit then I_2 will be equal to 0.

Now, let us see how we define B . B is nothing but V_1 divided by minus I_2 provided V_2 is equal to 0. So, if we put V_2 equal to 0, so we can see here if V_2 is put 0 here then V_1 divided by minus I_2 will be equal to B . Now, as you can see this is voltage divided by current. So, the unit of this will be ohm or you can say this will represent the impedance value.

Now, let us see what is C . So, to define C you can see from this particular expression, if we put I_2 equal to 0. So, what I_2 equal to 0 would mean? This term will become 0. So, we can say from here C is nothing but I_1 divided by V_2 provided I_2 equal to 0. So, I_2 be equal to 0 means open circuit, and this unit will be now I divided by V . So, that will be equal to mho. So, the unit of the C is mho. What is D ? So, again from here we can find the value of D . If we make V_2 equal to 0, if V_2 is 0 then this term will become 0. So, then I_1 divided minus I_2 will be equal to D . So, you can see that this is the expression provided V_2 is equal to 0 and what V_2 equal to 0 would mean that you actually short circuit the port 2. So, this is how we can actually define ABCD parameters.

(Refer Slide Time: 06:54)

ABCD Parameters for Series Impedance

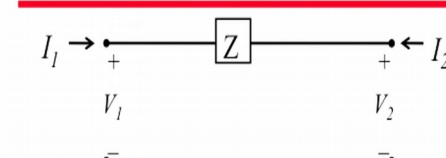


$V_1 = V_2 - Z I_2$ and $I_1 = -I_2$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

For Symmetrical Network:
 $A = D$

For Reciprocal Network:
 $AD - BC = 1$

NPTTEL  Microwave Theory and Techniques | Prof. Girish Kumar, IIT Bombay 3

Now, let us just take some example and see how we can find out ABCD parameter. To start with will take a very simple problem and then we will built up on these small small little little things to analyze a more complicated configuration. So, ABCD parameters for series impedance, so you can see here those are basically port 1 you can say this is port 2 and there is a only single element which is a series impedance.

So, now for this particular case we can write the voltage equation and current equation and you have to remember basically that we have to write V_1 and I_1 on one side and V_2 and I_2 on the other side. So, with that objective in mind let us say what is V_1 . So, V_1 is nothing but we can say this voltage plus voltage drop over here. So, V_1 will be equal to V_2 plus you can say $I_1 Z$ or $I_1 Z$ is equal to minus $I_2 Z$. So, we can say that V_1 is nothing but V_2 minus Z times I_2 . So, that will be this voltage equal to this voltage drop plus this voltage over here. And what is I_1 ? Again why we are writing in this particular form because, we have to write in this particular fashion.


So, what is I_1 equal to? I_1 is nothing but equal to minus I_2 . So, from here you compare this particular thing with this particular equation over here. So, we can say that V_1 is $A V_2$. So, what is coefficient of V_2 ? 1. So, that is 1 here. What is now V_1 is equal to B times minus I_2 and what will be B here then? Z . So, now, let us see I_1 , I_1 is nothing but C times V_2 well there is a nothing corresponding to V_2 that means C is equal to 0.

And then from here we can say I_1 is equal to then D times minus I_2 the term. So, from here we can say compare this. So, D will be equal to nothing but 1. So, we can say that ABCD matrix for this particular case is nothing but $\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$. Please try to remember this because we are going to use this later on, few properties of ABCD parameter. So, one of the property is that if the network is symmetrical, then A will be equal to D . As you can see if you look on this side or you look from this side the network is nothing but a symmetrical network. So, A should be equal to D , you can see that A and D are 1 and 1. So, they are equal.

Now, for reciprocal network it is AD minus BC is equal to 1. Actually this term really corresponds to the determinant of matrix ABCD. So, what will be the determinant? AD minus BC . So, the determinant of the matrix if that is equal to one this is a reciprocal network. What reciprocal network means? That if I give a input on this side whatever the output I get if I get this same input on this side then I should get the same output here. So in fact, all these networks will be reciprocal which have let us say resistor, inductor, capacitor, transmission line other thing. So, of course, if it consists of active network then it will not be reciprocal.

(Refer Slide Time: 10:24)

ABCD Parameters for Shunt Admittance

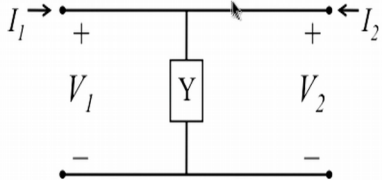


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$V_1 = V_2$ and $I_1 = YV_2 - I_2$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

\Rightarrow Symmetrical Network
and Reciprocal Network



Microwave Theory and Techniques | Prof. Girish Kumar, IIT Bombay

4

So, now let us take another example. So, this time will take an example of ABCD parameters for Shunt Admittance. So, we have here again as before port 1 here, port 2

here, now instead of having a series impedance in the previous case, now we have a shunt admittance.

So, now we want to write ABCD parameters of this I have just written it again. This is how we have define ABCD parameter. So, again we want V_1 I_1 on the left side. So, what is V_1 ? This voltage is same as this voltage which is equal to V_2 . So, V_1 is equal to V_2 . And, what about the current I_1 ? So, we can say that just general you think about, this current and this current these 2 currents are going into this. So, we can say that I_1 plus I_2 will be nothing but this particular current and that current will be nothing but V_2 times Y and then we can write I_1 plus I_2 was written there I_2 goes to the other side.

So, now this is similar to the form which we wanted, V_1 I_1 on the left side, V_2 I_2 on the right hand side. So, again now comparison let us say now ABCD. So, you look from here. So, V_1 is nothing but $A V_2$. So, the coefficient of V_2 will be 1, so it is write here. Now, V_1 is B times I_2 when there is a no term of I_2 that means, B is equal to 0. For now C let us say what is I_1 is C times V_2 , so C will be Y and then I_1 is this expression here from here then I_1 is $C V_2$ minus $D I_2$. So, we can say from here D is equal to 1. So, this is ABCD matrix for shunt admittance which is nothing but $1 \ 0 \ Y \ 1$. So, again you can say that this is symmetrical network why because A is equal to D ; it is also reciprocal network because AD minus BC will be equal to 1. So, 1 into 1 is 1 minus 0 . So, AD minus BC is equal to 1.

(Refer Slide Time: 12:39)

ABCD Parameters for Transmission Line

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos(\beta l) & jZ_0 \sin(\beta l) \\ jY_0 \sin(\beta l) & \cos(\beta l) \end{bmatrix}$$

For $l = \frac{\lambda}{4}$, $\beta l = \frac{2\pi}{\lambda} l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} = \frac{\pi}{2}$

$$\Rightarrow \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & jZ_0 \\ jY_0 & 0 \end{bmatrix}$$

Microwave Theory and Techniques | Prof. Gresh Kumar, IIT Bombay
5

Let us just take now another case of a transmission line. You might have studied about transmission line and you know that let us say if we want to define a voltage V_1 then voltage V_1 is nothing but equal to $V_2 \cos \text{hyperbolic } \gamma l$ plus $Z_0 \sin \text{hyperbolic } \gamma l$, similarly one can write expression for I_1 . Now, in this particular case here we are assuming that this line is loss less or we can say most of the time line losses will be very very small. So, that $\cos \text{hyperbolic } \gamma l$, what is γ ? γ is $\alpha + j\beta$. So, α will be negligible or α is equal to 0 for ideal transmission line. So, $\cos \text{hyperbolic } \gamma l$ will become now $\cos \beta l$, and $\sin \text{hyperbolic } \gamma l$ will become $j \sin \beta l$. So, this is what is the ABCD matrix for a transmission line.


We will take one of the special case as we will see later on when we take on more circuit examples that this will be a 1 of the special cases which will come several time. So, let us look at that right now, when length is equal to $\lambda/4$. And if we substitute l equal to $\lambda/4$ what will happen to βl ? So, β is $2\pi/\lambda$ so that is $2\pi/\lambda$ by $\lambda/4$ we substitute that. So, βl becomes $\pi/2$.

So, $\cos \pi/2$ is equal to 0, $\sin \pi/2$ is equal to 1, $\sin \pi/2$ will be 1, so we will be left with $j Y_0$ and $\cos \pi/2$ will be equal to 0. So, this will be the ABCD matrix for transmission line of length l equal to $\lambda/4$. I just want to mention of you additional thing here many books instead of writing β they write k . So, β is equal to k which is equal to $2\pi/\lambda$.

Again one more thing I want to mention here. So, this λ will be equal to λ_0 in free space, but otherwise say for coaxial line λ will be equal to λ_0 , by square root ϵ_r for microstrip line it will be λ equal to λ_0 divided by square root ϵ_e . And we have given you the formulas how to calculate ϵ_e for microstrip line. So, please use that when you are designing something for microstrip line.

(Refer Slide Time: 15:25)


ABCD Parameters for Cascaded Network

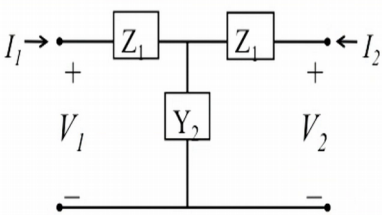

ABCD parameters of cascaded circuits are obtained by multiplying individual ABCD parameters.

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y_2 & 1 \end{bmatrix} \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 + Z_1 Y_2 & 2Z_1 + Z_1^2 Y_2 \\ Y_2 & 1 + Z_1 Y_2 \end{bmatrix} \Rightarrow \text{Symmetrical and Reciprocal Network}$$


Microwave Theory and Techniques | Prof. Girish Kumar, IIT Bombay
6

Now, let us just take a another case now here it is ABCD parameters for cascaded network. So, what we have here? We have two series impedances Z_1 and Z_1 here and we have a shunt admittance which is Y_2 . Now, this particular problem can be solved if we want to write voltage equation and current equation you can solve that. So, you can actually write here let us say here node equation here so which will be let us say some node 3. So, we can say that $V_3 \times Y_2 + V_3 - V_1$ divided by Z_1 plus $V_3 - V_2$ divided by Z_1 , and then you can solve the equation or you can write a loop equation here loop equation here.

However, we are not going to use that technique that can be done there is no problem at all, but since we have already studied ABCD parameters for series elements we have also studied ABCD parameters for shunt element. So, now, we are going to use the concept of ABCD parameters of cascaded circuit which can be obtained by multiplying individual ABCD parameters. What it really implies?

First let us just see, we have 3 different circuit element. So, what we do? If you recall Britishers used to say divide and rule. Well, I have modified that particular statement I say divide and solve. So, you divide this particular network into 3 different networks. So, this will be from here to here, one network which consist of only series impedance, then from here to here it will be the shunt admittance network and then from here to here we will have a series impedance network.

So, what is this cascaded business? So, let just see from here just recall now we had taken I_1 as here and just imagine that the current was entering here. Now, the current which was entering here which was minus, but that minus current can be thing about positive current over here. And then the current which is leaving here which was actually minus which will act as a entering here. So, if you look at just this particular network. So, V_1, I_1 for this let us say I did mention a V_3 node here. So, that will be V_3 node over here.

So, we can actually say that ABCD parameter of this, whatever is the current going out from here will become input current and input voltages over here so that means, this ABCD matrix can be multiplied with this. And then again whatever is the current coming in the same current is going just the directions are different. So, you have to take care of that part which is inherent of ABCD matrix. So, what we can do actually? That to find out the overall ABCD matrix what we simply need to do it is multiply ABCD matrices of these 3 separate elements.

So, let us see for the series impedance, what we had seen? ABCD parameters are $1, Z_1, 0, 1$; for shunt we had $1, 0, Y_2, 1$; for series this $1, Z_1, 0, 1$. So, now, all you have to do it is multiply these 3 matrices of course, you do one by one. So, first you multiply this matrix with this matrix here and then after that this resultant matrix is to be multiplied by this matrix here. So, just one step in between, you simplify this is the expression you will get. And just you see whether you have done any mistake or not you can make a quick check whether the network is symmetrical or and reciprocal or not. You can see from here if you look from this side or we look from this side, network is symmetrical from both the sides.

So, hence A should be equal to D. Let us see whether we have got that or not. So, this is $1 + Z_1 Y_2$, this is $1 + Z_1 Y_2$. So, we can say A is equal to D. Now, this network is reciprocal because all these are nothing but RLC component. So, that is reciprocal network. So, let us see AD minus BC is equal to 1 or not. So, now, you multiply this with this here what we will get? $1 + 2 \text{ times } Z_1 Y_2 + Z_1^2 Y_2^2$. Now, minus this term here $2 Z_1 Y_2$.

So, you can say that $2 Z_1 Y_2$ will get cancel by these two terms combined together and this is now $Z_1^2 Y_2^2$. So, we had also got $Z_1^2 Y_2^2$. So,

subtraction from here to here will lead to a value which is equal to 1 so that means, this is a reciprocal network and that really means that so far we have done the current calculations.

Now, we are going to take many many more examples later on about ABCD parameters, especially just to mention that I did take an example of transmission line. So, we will see many cases later on where this particular component may be a transmission line or this component may be a transmission line or there may be some lump element. So, you have to wait for few more lectures, and then we are going to take several examples where we are going to use these properties of ABCD parameters and specially we will use the concept of divide and solve the problem.

(Refer Slide Time: 21:16)

The slide features a blue header with the title "S-Parameters for Two Port Network" in yellow. Below the header is a diagram of a "Two Port Network" represented by a central box. On the left side, labeled "Port 1", there is an incoming wave a_1 (blue arrow pointing right) and a reflected wave b_1 (blue arrow pointing left). On the right side, labeled "Port 2", there is a transmitted wave b_2 (green arrow pointing right) and a reflected wave a_2 (green arrow pointing left). Below the diagram, the S-parameter equations are presented in red and green text:

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$$

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} \quad S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} \quad S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

Below the equations, the wave relationships are given in green:

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

The slide also includes a small logo in the bottom left corner and a footer at the bottom center that reads "Microwave Theory and Techniques | Prof. Gresh Kumar, IIT Bombay". A small number "7" is visible in the bottom right corner of the slide area.

Now, we are going to the next particular topic which is S parameters. Here we have defined S parameters for 2 port network, but by the way S parameters are valid for n port network also. Just to tell you that ABCD parameters are defined only for 2 ports, but S parameters are defined for n port, but for simplicity let us just take 2 port and then we will extend this concept to n ports.

So, let us see what we have here. So, here a_1 is the incoming wave. So, it is not same as current it is a incoming wave and b_1 is reflected wave. So, we are talking about now microwave frequency, where we do not talk about voltages and currents whereas, there we call let us say an antenna which will receive the signal and through the antenna we

can transmit the signal. So, there are incoming waves or outgoing waves. Similarly for an amplifier there will be an incoming wave there will be outgoing wave. So, generally speaking when we deal with S parameters they are dealing with waves.

So, a_1 is incoming wave similarly a_2 is incoming, so a parameters are incoming. So, over here b_1 is outgoing sometimes just say or leaving wave. So, this is the outgoing wave or leaving wave, ok. Sometimes in some books they also talk this as a transmitted wave also or over here they use the term reflected wave. So, in this case if this is incident this is you can say reflected and if this is incident this can be transmitted wave, ok. So, it all depends how you look at it, but basically we just say that a_1 or all a's are incident wave all b's are reflected wave.

Now, we will define the S parameter. So, we can actually define b_1 , b_2 on this side that means, there are the reflected wave these are the incident wave and this is how we define S parameters, ok. We can open the matrix let us look at here. So, b_1 is equal to $S_{11} a_1$ plus $S_{12} a_2$, we can write b_2 as $S_{21} a_1$ plus $S_{22} a_2$. So, now, from here just as we did in terms of ABCD parameter will just exactly the similar thing. So, let us say from here how we can find the value of S_{11} ? So, we can find S_{11} by making let us say a_2 equal to 0. So, if a_2 is equal to 0 then S_{11} will be given by b_1 divided by a_1 . So, we can see that S_{11} is nothing but b_1 divided by a_1 provided a_2 is equal to 0.

Now, here unlike the previous case where voltage equal to 0 implied short circuit current equal to 0 implied open circuit here a_2 equal to 0 implies match load termination. If you recall when we had mentioned about it that if something is going from here and over here, so nothing should reflect path and if nothing will reflect, but only when it is terminated into a match load, ok. And here we are defining everything in terms of characteristic impedance Z_0 . So, if this particular port is terminated with a characteristic impedance of Z_0 that means, load is equal to Z_0 in that case nothing will reflect. So, a_2 will be equal to 0.

So, please remember when we define S parameter we are not dealing with short circuit or open circuit we are more dealing with the match load termination. So, now, let us see from here how we define S_{12} . So, S_{12} will be equal to b_1 divided by a_2 provided a_1 is equal to 0. So, we can see that S_{12} is nothing but b_1 divided by a_2 when a_1 is equal to 0. So, what a_1 equal to 0 really means that means, now port 1 is terminated into

match load and what it really means here. So, this means that when we are giving input at port 2 what is the output at port 1 or what is the wave going out here.

Now, let us see what is S_{21} , S_{21} is nothing but b_2 divided by a_1 provided a_2 is equal to 0. And similarly we can find out S_{22} . What is S_{22} ? S_{22} is nothing but b_2 divided by a_2 provided a_1 is equal to 0. So, please remember these things. So, S_{11} actually can also be termed in a slightly different way that is look at the port 1 here this is S_{11} . What is b_1 ? Reflected wave. What is a_1 ? Incident wave.

So, what we are basically saying S_{11} is nothing but reflected wave at port 1 divided by incident wave at port 1. Let us see what is S_{22} . S_{22} we have to look at the port 2 here what it shows here this is a incident wave, this is the reflected wave provided this is terminated with the match load to get a_1 equal to 0 so that means, S_{22} is nothing but a reflected wave which is b_2 divided by a_2 . So, this is same thing as reflection coefficient at port 2. This is the same thing as reflection coefficient at port 1.

Now, let us see what is S_{21} . S_{21} is defined as b_2 by a_1 . What is b_2 ? Wave going over here. What is a_1 ? Incident wave over here; provided a_2 is equal to 0 so that means, if we terminate this thing into a match load, then what is the transmitted wave to this particular value divided by the incident. So, hence this you can say will actually give the gain of the amplifier or loss of any given circuit. So, that is why many a times b_2 is mentioned as transmitted wave when a_1 is the input here ok. But if you look at S_{12} , what is S_{12} ? That is b_1 divided by a_2 provided a_1 is equal to 0. So that means, if input is given at port 2 which is a_2 then what is the wave going towards this. So, in this particular case if the input is at port 2, then b_1 becomes transmitted wave. So, b_1 divided by a_2 , ok.

So, in the next lecture we are going to talk in more detail about S parameters, how these reflection coefficients and transmission coefficients are define. So, just you summarize today's lecture. So, we actually started with the very simple ABCD parameters which are define in terms of input voltages and current and output voltages and current. And the benefit of that is that for one network if this input voltage and current is defined in terms of output voltage and current then that output voltage current becomes input voltage and current for the next port, and then we can find the next to next port output voltages and currents. So, you can keep cascading these things and simply by multiplying ABCD of

first to second to third or fourth or nth different components can be there and you can find ABCD parameters of the entire network simply by doing the matrix multiplication.

And then we did look at a few simple examples, one was series impedance, then another one was shunt impedance, then we looked at the transmission line, and then we also looked at one case with consisted of series shunt series, ok. And after ABCD parameters we looked at S parameters. Now, ABCD parameters are defined in terms of voltages and currents, S parameters are defined in terms of incoming wave and outgoing wave. And in the next lecture we will see that how ABCD parameters are related with S parameters. How we can convert from ABCD parameters to S parameters and also we will look at what are the different properties of S parameters, and what happens when you go from 2 port to n ports. So, what are the different things we will look into that and we will also see how to calculate S parameter for a given network.

So, with that thank you very much. See you next time. Bye.