


Fundamentals of Power Electronics
Prof. L. Umanand
Department of Electronic Systems Engineering
Indian Institute of Science, Bengaluru

Lecture – 33

Example on shunt regulator

(Refer Slide Time: 00:27)

EXAMPLE

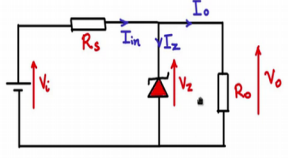

$V_i \Rightarrow 9\text{v to } 13\text{v}$
 $Z_{\text{ener}} \Rightarrow 5\text{v, } 400\text{mW}$
 What is range of R_o ?


$125\Omega \leq R_o < \infty$

$$I_{Z\text{max}} = \frac{P_Z}{V_Z} = \frac{400\text{mW}}{5\text{V}} = 80\text{mA}$$

$$R_s = \frac{V_{i\text{max}} - V_Z}{I_{Z\text{max}}} = \frac{13 - 5}{80\text{mA}} = 100\Omega$$

$$P_{R_s} = \frac{(V_{i\text{max}} - V_Z)^2}{R_s} = \frac{(13 - 5)^2}{100} = 0.64\text{W}$$

$$I_{o\text{max}} = \frac{V_{i\text{min}} - V_Z}{R_s} = \frac{9 - 5}{100} = 40\text{mA}$$
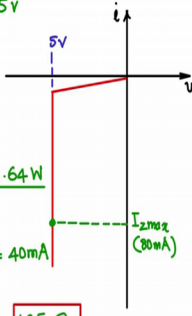
$$R_{o\text{min}} = \frac{V_Z}{I_{o\text{max}}} = \frac{5}{40\text{mA}} = 125\Omega$$


Let us now look at an example of this shunt regulator circuit and try to gain more insight into this by putting in some numbers. So, let us say that V_i is the unregulated voltage V_i varies from 9 volts to 13 volts, this is the spec. So, this is a unregulated V_i varies from 9 to 13 volts. Then this Zener, let us say the Zener is the 5 volt Zener, because we want 5 volt at the output so we need to take a 5 volt Zener and let us say the Zener has a spec of 400 milliwatts. What is the range of output R_o naught? So, let us try to work it out and find out.

So, let us say I_z , I_z is the current. What is I_z max? I_z max should be such that the max power dissipation of the Zener 400 milliwatts is not exceeded. So, P_z if I take P_z 400 milliwatts divided by V_z , V_z into I_z is P_z , which is 400 milliwatts by 5 volts this will give you 80 milliamps. So, I_z max or I_z the current through this branch should not exceed 80 milliamps, if it exceeds 80 milliamps then the power dissipation limit of this Zener is crossed and it will blow.

So, this is one limiting value that you would get and if you actually plot it on the Zener reverse characteristic, as this is a Zener reverse characteristic this is 5 volts here and let us say this is the $I_{z \max}$ operating point this is $I_{z \max}$ and that is 80 milliamps as calculated like this here.


So, now, R_s let us try to find what is this R_s . $V_{i \max}$ take $V_{i \max}$ which is 13 volts minus this node potential which is V_z divided by I_{in} . Now, I_{in} will take it as $I_{z \max}$ assuming that I_{naught} is 0. This is one of the extreme conditions that we saw earlier. So, that would be 13 minus 5 divided by 80 milliamps and which is 100 ohms.

So, what it means is that under worst case condition when there is no load and R_{naught} is infinity all the current I_{in} flows into I_z , and that would be $I_{z \max}$. Now, that current I_{in} is maximum and V_i is max, so $V_{i \max} - V_z$ by $I_{z \max}$ will give you the value of R_s and what should be the power rating of R_s . So, the power rating of R_s is given by $V_{i \max} - V_z$ that is voltage potential difference across R_s square by the value of R_s which is 13 minus 5 square by R_s which is 100 and this turns out to be 0.64 Watts. So, we have selected R_s .

Next let us look at R_{naught} . So, first what is the maximum value of R_{naught} I_{naught} that can be allowed through R_{naught} ? So, $I_{naught \max}$ is even under minimum input voltage condition $V_{i \min} - V_z$ divided by R_s will be the I_{in} that flows here under minimum input condition. And at that condition what is the minimum R_{naught} that you can apply. 9 minus 5 divided by 100 and that is 40 milliamps, that is the maximum I_{naught} that you can allow through the output and therefore, $R_{naught \min}$ if it is max I_{naught} you write down the $R_{naught \min}$ which is $V_z - V_{naught}$ potential is V_z divided by $I_{naught \max}$ which is 5 volts divided by 40 milliamps this one and comes to 125 ohms.

So, therefore the range of R_{naught} is 125 ohms on one side, on the other side it is open circuit or infinite. So, this implies that R_{naught} can take a minimum value of 125 ohms and a maximum value of open circuit. So, this is the range of R_{naught} for this particular circuit for this kind of specification.

(Refer Slide Time: 06:47)

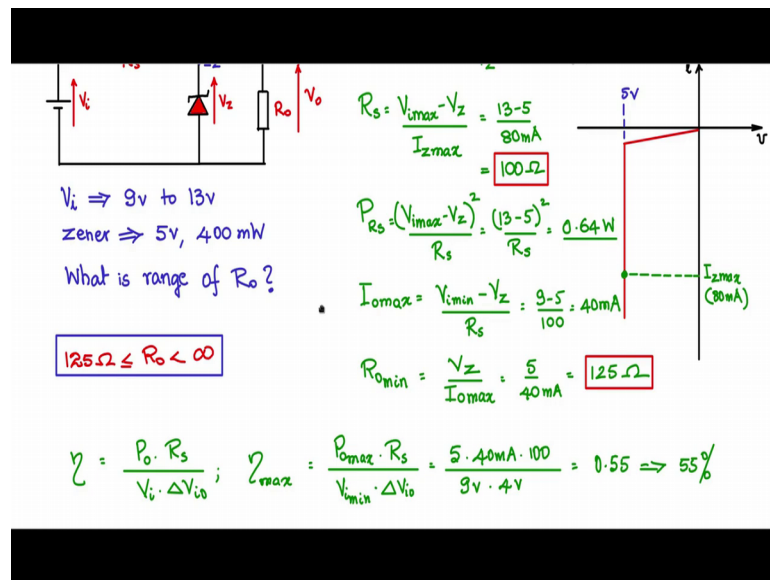

What is efficiency? You can calculate the efficiency of this to complete the understanding. So, efficiency is we have found out that V_o into R_s by V_i into ΔV_{io} or the delta input output differential.

Now, let us say efficiency max. What is the max efficiency? P_o is max. So, we will make P_o max, R_s is a fixed value calculated for this particular circuit, V_{imin} take V_{imin} and ΔV_{io} . When you take V_{imin} ΔV_{io} will naturally be smaller minimum of and therefore the efficiency would be the max possible that you would get.

So, if you calculate V_o max which is V_o 5 volts into I_o max 40 milliamp into R_s which is 100 ohms divided by V_{imin} which is 9 volts. ΔV_{io} , when it is 9 volts and the output is 5 volts V_{io} will be 9 minus 5, 4 volts and this turns out to be 0.55 or 55 percent. So, the efficiency of this circuit for these specifications is 55 percent at max load condition.