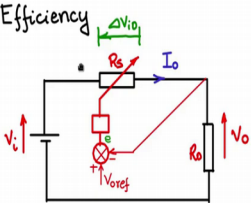


Fundamentals of Power Electronics
Prof. L. Umanand
Department of Electronics Systems Engineering
Indian Institute of Science, Bengaluru

Lecture – 37
Efficiency of series

(Refer Slide Time: 00:28)



Efficiency $\leftarrow \Delta V_{io}$

$$\eta = \frac{P_o}{P_i} = \frac{V_o I_o}{V_i I_o} = \frac{V_o}{V_i}$$

$$= \frac{V_o}{(V_o + \Delta V_{io})}$$

Eg. $V_o = 5V$ & $V_i = 15V$ $\eta = \frac{5}{15} = \frac{1}{3}$
 $V_o = 5V$ & $V_i = 10V$ $\eta = \frac{5}{10} = \frac{1}{2}$

What is the efficiency of the series regulator? So, you see the circuit you have in the power loop just three components, you have the input source V_i , you have R_s and you have R_{load} . So, efficiency is given by P_{naught} by P_i . If, I_{naught} is flowing in this power loop, you have P_{naught} is V_{naught} into I_{naught} , and it is a same current I_{naught} which is flowing through the input source also. So, we have V_i into I_{naught} , and efficiency simply v_{naught} by V_i .

So, if the input output differential is very large, then you will see that the efficiency is low. If the output is very close to the input comparable to the value of V_i , then you will see that the efficiency is high. Let me rewrite the efficiency as V_{naught} divided by V_i can be replaced with V_{naught} plus ΔV_{io} that is a input output differential. Now, as you see that as the input output differential is very large if it starts becoming larger, then the efficiency goes down.

So, an example say V_{naught} is 5 volts, and V_i is 15 volts input output differentially is 10. So, you have 5 by 15, which is efficiency one-third 33 percent. For the same 5 volts,

if V_i is 10 volts, then efficiency is 50 percent $1/2$. So, if you see that the difference between V_{naught} and V_i if it starts becoming smaller and smaller efficiency is better and in fact that is the reason the low dropout regulators, where the input output differential is small how much higher efficiency.