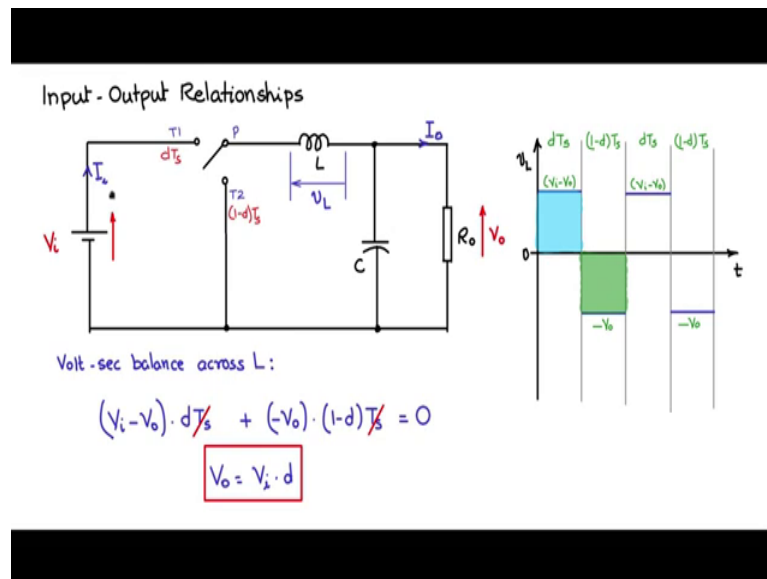


Fundamentals of Power Electronics
Prof. L. Umanand
Department of Electronics Systems Engineering
Indian Institute of Science Bengaluru

Lecture – 47
Input-output relationship

(Refer Slide Time: 00:27)



Now, I will demonstrate to you for the circuit that we had discussed till now, how to get the Input output relationship by application of the volt second balance. So, let us take this buck converter circuit which we have discussed and let me mark this current I naught; I naught is the output current that flows through the output load register R naught, the voltage across the output is V naught V i is the voltage of the unregulated input. Now the inductor, so when you want to apply the volt second balance you have to look for the inductor or the coil in the circuit and take the voltage across that coil.

So, you go to the inductor take the voltage across that and mark that vL look at the way I have put the arrow what it basically means is that when you are making a measurement using a physical device or virtually you are to mentally keep the common of the probe here and the measurement probe on the side that is what the arrow mark indicates. So, I could as well now use the arrow mark on this fashion which means that, if the arrow is pointing on to the right then you keep the common of the probe on the left and make

them use the measurement probe on the right. But here what I am doing is I am keeping the common probe here and the measurement probe here.

So, let us also mark the time periods for which P T1 is on and time period for which P T2 is on or P T1 is off which is $1 - dT_s$. Let us also put a graph here indicating that will indicate the wave shape of the voltage waveform the inductance and let us divide the time scale in this fashion I will call this period as dT_s time period during which P T1 is ON $1 - dT_s$ time period during which P T2 is ON dT_s again the second cycle starts and $1 - dT_s$, so these are the time periods. Now let us look at the voltage waveform across the inductor. So, during the dT_s period the pole is connected to T1 and V_P is equal to V_i on this side of the inductor in the steady state this is V_{naught} .

So, in the steady state the capacitor would have charged up we are talking of steady state conditions only because we want to have the steady state input output relationship and during that time we know the volt second balance occurs across the inductor voltage. So, this is V_{naught} here and this is V_i here during the dT_s period, so therefore I will say it is constant $V_i - V_{naught}$ during that time the voltage across the inductor.

Then during the time $1 - dT_s$ P is connected to T2, so this is grounded the inductor is freewheeling so let us say the voltage here is 0 V_P is 0 . But V_{naught} is there V_{naught} does not discharge so quickly we are talking of the switching cycle, so minus V_{naught} appears across the inductance. So, it has to be minus voltage here because then only volt second balance will occur, so you will see minus V_{naught} appearing across that then again during the next cycle dT_s P is connected to T1 you have $V_i - V_{naught}$ and during $1 - dT_s$ time when P is connected to T2 you have minus V_{naught} appearing across the inductor.

So, this is the inductor current wave shape and during this time what is the volt second this is a rectangular voltage no need to do integral you can find out the area just by the height into the time width, so we have $V_i - V_{naught}$ into dT_s . So, let us calculate the volt second balance across the inductor, so during this time V_i into V_{naught} into dT_s is the area of this rectangle. Now the other rectangle is this which is minus V_{naught} into $1 - dT_s$.

So, that is minus V_{naught} into $1 - dT_s$ now that should be equal to 0 these 2 should add up to 0 or basically what it means is these 2 should cancel each other. So, here I can

remove this $T_s T_s$ so the remaining portions if I simplify you see V_{naught} into d and you have a minus $V_{naught} (1-d)$ if you take it to the other side they become V_{naught} into d plus $(1-d)$. So, basically it becomes 1 and in the side you are having V_i into d , so if you do the algebra in simplification you will get V_{naught} is equal to V_i into d and that is the input output relationship.

Now, to get the input output current relationship you can use the amp second balance average current flowing through C is equal to 0, but for that you have to understand the waveforms the currents that go through which we have not yet come to that point. However, you can do the amp second balance. Later on I will show you how the amp second balance also work, but I have an easier method for you right now.

(Refer Slide Time: 06:32)

Volt-sec balance across L:

$$(V_i - V_o) \cdot d T_s + (-V_o) \cdot (1-d) T_s = 0$$

$$V_o = V_i \cdot d$$

INPUT OUTPUT CURRENT RELATIONSHIP

$$P_i = V_i \cdot I_i \quad ; \quad P_o = V_o \cdot I_o \quad \eta = 100\%$$

$$P_o = P_i$$

$$V_o I_o = V_i I_i$$

$$d \cdot I_o = I_i \Rightarrow I_i = I_o \cdot d$$

So, let us say I will define this as I_i and let us find the input output current relationship. So, to find the output input current relationship I will make use of the fact that the efficiency of the circuit is 100 percent meaning there is no lossy component within. So, P_i is V_i into I_i and P_{naught} is V_{naught} into I_{naught} and I must being efficiency is 100 percent no loss within. So, in such a case P_{naught} is equal to P_i or $V_{naught} I_{naught}$ is equal to $V_i I_i$.

Now, I know the input output voltage relationship here, so let me apply it here V_{naught} I will replace it by V_i into d . So, you have V_i into d into I_{naught} equals V_i into I_i , so remove V_i they cancel of and you have I_{input} current is equal to I_{naught} into d . So,

this is the input output current relationship you can get it through the capacitances amp second balance also, but that is sometime later after we know how the waveform current waveform is through the capacitor.

But for now you can use the power relationship or the power balance relationship knowing that there are no dissipative components switch is either OFF or ON no dissipation here the ideal sense inductance is a energy storage device, no dissipation capacitance is a storage device potential storage device no dissipation again.

So, all these components or dissipation less devices in the ideal sense, therefore if I take 100 percent efficiency I will get this input output current relationship knowing the input output voltage relationship. So, this is the formal way of using the volt second balance across the inductor to get the input output voltage relationship you can use it for any circuit however complex it is.