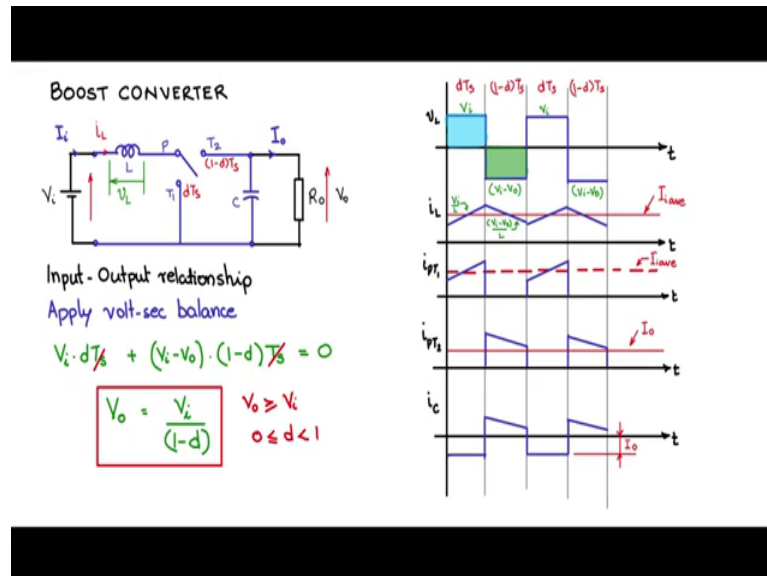


Fundamentals of Power Electronics
Prof. L. Umanand
Department of Electronics Systems Engineering
Indian Institute of Science, Bengaluru

Lecture – 51
Boost converter

(Refer Slide Time: 00:28)



Consider the boost converter circuit. We have this inductor, single pole double throw switch and the capacitor. Let us see how it operates and the various waveforms. Let me mark this I naught current flowing through the output load resistor, I in current flowing through the input source V i. Let me mark the voltage across inductor is the voltage across the inductor V_L with the common point the probe placed here and the measuring point the probe placed here.

Now, let us discuss its operation and wave forms visually and get some insight into this converter topology. Now I am going to display the wave forms here and I have split the time axis into four parts has before. Now let us say that $P T 1$ is going be on during $d T s$ period and $P T 2$ is going to be connected during $1 \text{ minus } d T s$ period. So, let me mark this time periods here on the graph $d T s$ and $1 \text{ minus } d T s$; $d T s$ and $1 \text{ minus } d T s$ together form a switching period $T s$.

So, let us plot first the voltage V_L across the inductor and during dT_s , the pole P is connected to T1 pole P is at 0 voltage and the other side of the inductor is at V_i voltage. So, a voltage V_i measured positive like this.

Now, during the period $1 - dT_s$ pole P is connected to T2. So, the potential here is V_{naught} or the pole potential is V_{naught} and this side the inductor is still V_i . So, voltage across the inductor is $V_i - V_{naught}$. Now is $V_i - V_{naught}$ positive or negative? We know that the inductor cannot support an average voltage. Therefore, the average voltage has to be 0. In steady state which means in steady state during the $1 - dT_s$ portion, there should be a negative voltage so that there is volt second balance.

So, that can happen because the voltage across the inductor during that period is $V_i - V_{naught}$ that can happen only if V_{naught} is not greater than V_i . So, it is automatic that V_{naught} will be greater than V_i in order to have the volt second balance happening. So, this will become negative like this and so on to the next cycle. V_i and $V_{naught} - V_i$ minus V_{naught} . So, this is the voltage waveform across the inductance.

So, now, let us now see the current waveform through the inductance. I am drawing this average current here; this average current flowing through the input flowing through the same inductor and the inductor has two parts the average part and the ripple part.

So, let me call this I in average and let me draw the ripple. I have drawing the ripple as a straight line and it has a slope V_i is equal to $L \frac{di}{dt}$. So, $\frac{di}{dt}$ slope have placed it as a straight line linear fixed slope. The voltage across the inductor is V_i during that time constant L is a constant; V_i by L is the slope which is the constant. And during this time $V_i - V_{naught}$ is negative. So, it is a following slope $V_i - V_{naught}$ by L is the slope. So, it repeats for the next cycle and so on. So, this is the inductor current waveform.

Next let us see the waveform of the switch P T1. So, let me draw this I average level position I average and i_{PT1} current flowing from the inductor into this and when this open the inductor current cannot be discontinuous its start flowing into P T2. So, the inductor current inductor current flows through P T1 during the time dT_s when P T1 is on. And only during dT_s time you will see the inductor current flowing through P T1, otherwise P T1 is 0.

Next let us see what is the current through $P T 2$. So, during $P T 1$ the inductor current flows through like that and during $P T 2$ during $1 - d T s$ the current flows through $P T 2$ and that is same as the inductor current portion during that time. So, this is the current through this $P T 2$.

Now, what is the average of the $P T 2$? Average of the current through $P T 2$ flows through capacitance and through the output load resistance. We know that the average the current through the capacitor has to be 0. Therefore, the average has to be I_{naught} . So, average is I_{naught} . What is the current through the capacitance? The current through the capacitance is this waveform $P T 2$ waveform shifted down by the average because the average cannot be any finite value here, it has to be 0. So, we have a 0 average current flowing here in this fashion where this amount, but the amount by which it has shifted down is I_{naught} .

So, these are the various waveforms that we see for the boost converter and using this waveforms, let us find the input output relationship and the values of the inductor capacitance and what goes on to form the single pole double throw switch. Let us now try to find the input output voltage relationship for the boost converter. So, for that we have to use the volt second balance equation. So, let us apply this volt second balance to what voltage you will be applying a to the inductor voltage. So, look for the inductor; look for the voltage across the inductor which is this waveform and later apply the volt second balance.

Now, during $d T s$ this is the volt second area, we can use, we can use a simple relationship of a rectangular area because this is a constant voltage would. So, let us apply that. So, this is V_i into $d T s$ V_i is the amplitude $d T i$ $d T i$ is the width and this is the area the rectangle during the $d T s$ period. Now during the $1 - d T s$ period the voltage across the inductance is $V_i - V_{naught}$. So, this area we will calculate $V_i - V_{naught}$ into $1 - d$ into $T s$.

Now this area positive area negative area should balance out. So, therefore, that should be equal to 0. I will remove these 2 variables or the picture. Now the remaining variables if you simplify you have a V_i into d and you have V_i and $V_i - V_{naught}$ into d . So, this V_i into d and this V_i into d will cancel out, you have a V_{naught} into $1 - d$ push it to the other side. So, you will end up with $V_{naught} = V_i / (1 - d)$. Now this is

the input output voltage relationship for the boost converter, observe $1 - d$ comes to the denominator here; d takes on values from 0 to 1. If d is 0, V_{naught} will be V_i if d is one V_{naught} will tend to infinity, but it will not actually tend to infinity d cannot take value 1 because then this will be permanently on and there would not be switching.

So, it should be less than d should be less than 1. So, V_{naught} greater than or equal to V_i and d takes on values between 0 and 1 on this fashion. So, this would be the input output relationship the boost converter and because V_{naught} is always greater than V_i we call this as the boost converter. Let us also obtain the current relationship.

(Refer Slide Time: 10:13)

Input-Output relationship
Apply volt-sec balance

$$V_i \cdot d \cdot T_s + (V_i - V_o) \cdot (1-d) \cdot T_s = 0$$

$$V_o = \frac{V_i}{(1-d)} \quad V_o \geq V_i \quad 0 \leq d < 1$$

Current Relationship

$$P_i = P_o \quad \therefore V_i I_i = V_o I_o$$


$$I_i = \frac{I_o}{(1-d)}$$

We could use the amp second balance across the capacitance or like we did last time we could use the power balance P_i is equal to P_{naught} and therefore, $V_i I_i$ is equal to $V_{\text{naught}} I_{\text{naught}}$. Now this $V_{\text{naught}} I_{\text{naught}}$ I know from the volt second balance relationship is this much. Let me substitute that $V_i I_i$ is equal to V_i by I minus d into I_{naught} . I will remove these two variables and therefore, you have $I_{\text{naught}} I_i$ is equal to I_{naught} by $1 - d$ and this is the input output current relationship. You could also get the same relationship if you take the amp second balance or the charge balance find out the area of i_c here and find out the area of i_c here, equate them and get the relationship.

But it is not a straight forward because a trapezium and find the trapezium area, we need to know this heights finding this area is easy because we this is a rectangle with height I_{naught} , but may be difficult to find this in a straight forward manner. So, we use this

current relationship we obtain a current relationship using the power balance which is much easier.

(Refer Slide Time: 11:54)

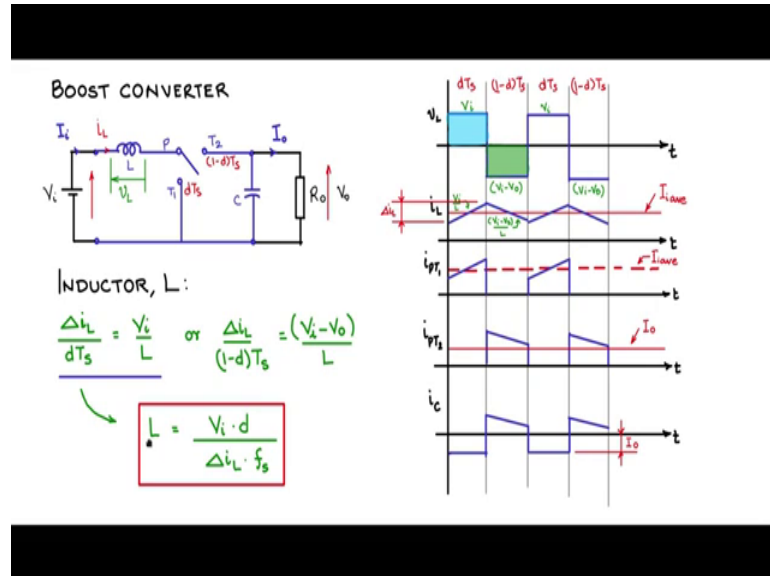

Now, let us find the values of the components L C and then identify the switch elements this of this single pole double throw switch. So, first the L consider the inductor L, what is its value? Take the inductor current wave form and we know that the height of this current ripple; let us set it as delta i L. Now this is the change in the inductor current. So, we will use a Faraday's equation V is equal to L d i by d T and we know the slope of this V i by L we have written here V i minus V naught by L for this part of the slope.

So, consider that during this d T s period; during this d T s period, there is a change of delta i L. So, d i by d T will be delta i L by d T s. So, delta i L by d T s is equal to what slope rate which is V a by V by V i by L here in this period. So, we will write that down V i by L or I could take 1 minus d into T s period. So, during that the current is falling. So, there is still a change of the same delta i L though negative slope 1 minus d T s equals V i minus V naught by L V i minus V naught by L. So, this is a negative slope; the change in delta L is negative in the sense that it is a falling value.


So, you can take absolute values for finding the value of L because the L has to be positive, you can take instead of V i minus V naught V naught minus V i. Anyway if you substitute for V naught all will boiled down to the same equation here. Let us take that equation and find out L. So L, I will push it there delta i L, I will push it down here. So,

V_i and I_i will push it up there $\Delta i_L T_s$. If I push it up and say T_s is equal to $1/f_s$, then I can put f_s in the bottom here denominator. So, this is the relationship for finding the value of L for the boost converter.

Here you know V_i ; V_i is a input spec of the un regulated dc source; d how do you find d ? We know we know V_o ; V_o is again output spec. So, knowing V_o/V_i , we can use input output relationship and find d , f_s is the designer parameter at what switching frequency are you switching these switches could be 20 kilohertz, 50 kilo hertz or 100 kilo hertz.

So, whatever the designer fixes specifies. So, that will be the switching frequency here and Δi_L . Now here i_L unlike in the case of the buck converter, the average value the inductor current was I_o in the case of the boost converter the average value the inductor current is the input current average. So, 10 percent of this input current average will be Δi_L . How do you know the input current we know V_i we know P_o and P_i are same and therefore, P_o/V_i will give you I_i ; so, you 10 percent of that will give you Δi_L . So, all these parameters are determinable from the specs and you can find out the value of L .

(Refer Slide Time: 16:00)

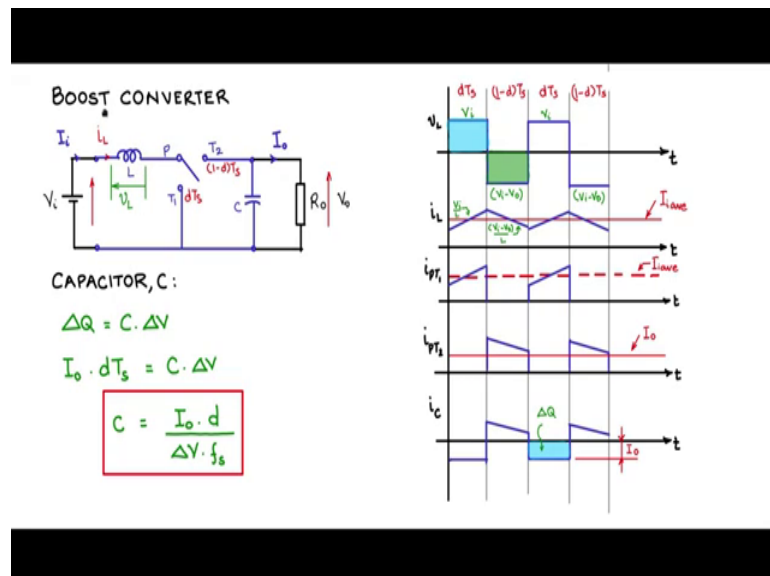


Next let us find out the value of the capacitor C , for that we have to look at the capacitor current waveform and we know from amp second balance that this area the top portion of it above the 0 line and the bottom portion of the area below the 0 line, they should match.

Now the area under this i_C curve will be the charge Q . So, in every cycle this amount of area will be ΔQ . So, let us use like in the buck converter case, we will try to find what is ΔW and ΔQ we know from physics is $C \Delta V$. So, what is ΔQ ? It is the area covered under the i_C curve i_C envelope. In this case between one minus d in T_s period and $d T_s$ period, it is much easier to find the ΔQ of this because this is a rectangle of height I_{naught} and width time with $d T_s$.

So, therefore, ΔQ will replace it by I_{naught} , I_{naught} is a height of this rectangle and the width of that the time in the time scale is $d T_s$. So, that is equal to $C \Delta V$. Now C we can write it down as $I_{\text{naught}} d T_s$. I will take it to the denominator as f_s ; f_s is $1/T_s$ and ΔV will come down into f_s . So, this is the relationship for the capacitor value. Do you know I_{naught} ? I_{naught} is obtained from the output spec. Whenever a power supply is designed P_{naught} is given P_{naught} and V_{naught} are given the voltage of the output and the power that needs to be delivered to the output, d can be found in the input output voltage relationship, f_s is a designer parameter, ΔV is again an output spec what should be the output voltage ripple and using that find out the value of C . So, this is the basis for the design the basis for the design of the C for the boost converter.

(Refer Slide Time: 18:30)

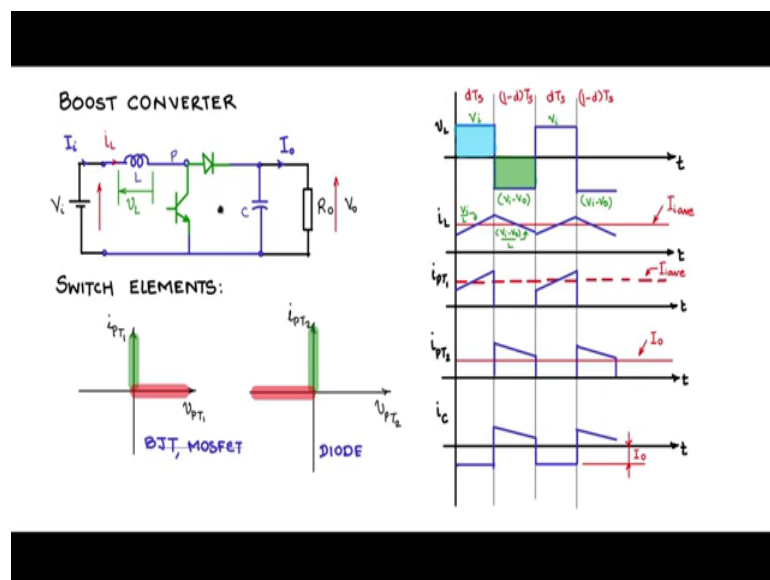

Now, let us select the switches for the single pole double throw switch and find out the ratings. So, the switch elements like we did for the buck convertor, we will use the static

characteristic for the switches, the $i-v$ characteristic. So, consider first $P-T_1$; let us consider this switch $P-T_1$ and then after words $P-T_2$. So, let us say we draw the $i-v$ characteristic of v_{P-T_1} and i_{P-T_1} . And then let us match the requirement with a practical switch characteristic and then select the component.

So, now, if you take i_{P-T_1} current flowing from P to T_1 is i_{P-T_1} positive and if you if you look at the operation of the circuit when P and T_1 are closed, the current i_L flows in this direction from P to T_1 . You can also observe i_{P-T_1} wave shape here; all are positive there is no negative component of i_{P-T_1} which means there is no current flow from through T_1 to P all current flows are P to through T_1 . So, only the positive current access or potential operating points. So, let us mark that.

So, these are potential operating points meaning that $P-T_1$ should allow positive direction of current flow from P to T_1 . Now for the voltage, when the switch is off when the switch is off what should it support what is the voltage of P pole P ? So, when T_1 is off, P and T_2 are connected. So, T and P and T_2 are connected the output voltage will come at this pole point. So, the pole voltage will become V_{naught} ; V_{naught} is positive T_1 is at ground potential.

So, $P-T_1$ is a positive voltage and the switch $P-T_1$ during off condition should support or withstand a positive voltage which means all the positive voltage points on this axis become possible operating potential operating points. So, we expect a switch to have this kind of a characteristic and we saw while we were discussing the buck converter that it is similar to a BJT or MOSFET characteristic or even an IGBT. So, I can use a BJT or a MOSFET here in place of $P-T_1$. And for $P-T_2$, let us draw the $i-v$ characteristic v_{P-T_2} and i_{P-T_2} .


So, looking at the inductor current we know that the current flows current used to flow from P to T_1 and then when you switch off $P-T_1$ and connect to $P-T_2$, the current has to flow from P to T_2 in this direction. And you can also look at $P-T_2$ current wave form all are positive there is no negative, meaning there is no current flow from through T_2 to P . So, therefore, we can say that all the positive current access can be potential operating points.

Now, when the switch $P-T_2$ is off meaning when P is connected to T_1 during that time $P-T_2$ is off, what is the voltage it will with stand? T_2 is at V_{naught} potential, P is at

ground potential when P is connected to T 1. So, P T 2 is negative and therefore, you will see that it has to withstand all negative possible negative potential. So, this character is provided by a diode. So, therefore, P T 2 should be a diode. Now let us replace the single pole double throw switch with the selected types of the switches; let us say BJT or MOSFET and the diode at the respective places.

So, let us erase some portion of this P T 1 and then introduce a BJT wherever I have introduced BJT, you can as well introduce a MOSFET or also an IGBT all are valid switches in those places; they are controlled switches. So, I have put this BJT in here to match for this characteristic requirement, then this P T 2 we said matches a diode. So, we will make some space there and introduce this diode here.

(Refer Slide Time: 23:44)

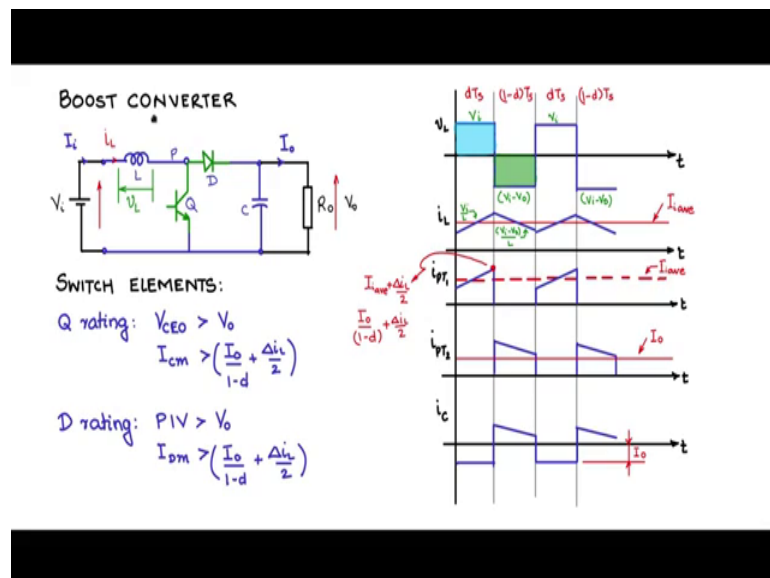

So, let us clear up this is called Q and this is D. So, this becomes the complete topology of a boost converter with the semiconductor switches in place. What are the ratings of Q and D?

So, let us say Q the ratings of that so, first the voltage rating V CEO rating. So, during the off condition, what is the voltage that Q has to with stand? During the off condition, the inductor current is passing through the diode to the output. So, the diode is conducting. So, V naught comes as the pole voltage here. So, Q should with stand at least the V naught amount of voltage. So, V CEO should be greater than V naught definitely, then what should be the max current rating I c m rating collector current max rating

should be greater than. Here you see in i_{PT1} this point here is the max current that occurs and that is $i_{in\ average} + \frac{\Delta i_L}{2}$.

So, this is $I_{in\ average} + \frac{\Delta i_L}{2}$ and $I_{in\ average}$ can be related to the I_{naught} current we know, we develop the input output current relationship where I_i is equal $I_{naught} \cdot \frac{1}{1-d}$. So, therefore, I will say $I_{naught} \cdot \frac{1}{1-d}$ is this $I_{in\ average} + \frac{\Delta i_L}{2}$. So, in terms of known items d is known I_{naught} from specs $\frac{\Delta i_L}{2}$ is known you can say what should be the current max spec for Q, $I_{naught} \cdot \frac{1}{1-d} + \frac{\Delta i_L}{2}$.

So, for the diode rating, you have the peak inverse voltage. Peak inverse voltage should be greater than what? So, when Q is conducting the diode D is off and it is seeing the peak the inverse voltage. So, during the time when Q is on, the pole point is connected to the ground. So, pole voltage is 0 and the diode cathode is connected to V_{naught} . So, therefore, at least V_{naught} amount of reverse voltage the diode has to withstand. So, it should be greater than V_{naught} and I_d maximum is like here you have i_{PT2} the max point is same $I_{naught} \cdot \frac{1}{1-d} + \frac{\Delta i_L}{2}$.

So, all other currents like average and rms currents can be calculated from the wave shapes. So, this would be the way you choose the ratings for the semiconductors switches of the boost converter.