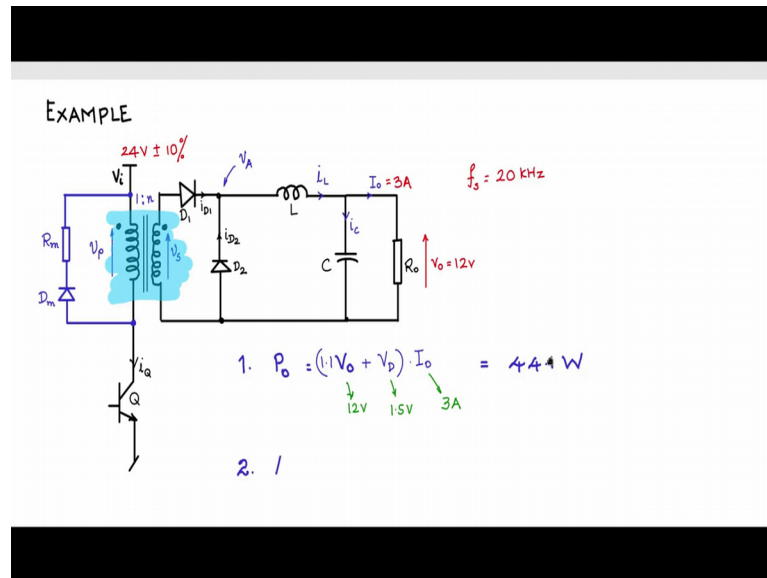


Fundamentals of Power Electronics
Prof. L. Umanand
Department of Electronics Systems Engineering
Indian Institute of Science, Bengaluru

Lecture - 69
Transformer example

(Refer Slide Time: 00:27)



Let us now take an example and design a transformer for a DC-DC converter. I have taken here an example of a forward converter where we have discussed this operation and we know how it works. So, let us say we have an output the spec output voltage spec of 12 Volts, output load current as 3 amps, switching frequency of 20 kilo hertz, input V_i as 24 Volts plus or minus 10 percent and then we need to design this transformer.

So, let us see how we go about doing that. So, step 1, we need to find what is the output power. Output power is $V_o I_o$, but we need to find what is the power of the secondary here. So, if you see the secondary because P_o here refers to when you are talking of design of the transformer, all the power right at the point of the secondary terminals.

So, you see this is the power here $V_o I_o$ and in principle the components are not ideal, there will be a diode drop especially at higher powers the diode drop here will be around 1.2 to 1.5 Volts into I_o that will come in here and then there will be resistance winding resistance and there will be some drop in the winding resistance. So,

put all that together you can increase V_{naught} by 10 percent and add the V_D drop.

So, what we can do is we can say $1.1 V_{naught}$ plus V_D will be the voltage that will be needed here to take care of a output V_{naught} of 12 Volts. So, this will give us and slightly higher voltage at the secondary so that all these drops are taken care of into I_{naught} will be the power at these terminals of the secondary. So, apply V_{naught} 12 Volts, V_D of 1.5 volts and 3 amps you will get around 44.1 Watts.

So, for this secondary output power we need to design the transformer.

(Refer Slide Time: 02:45)

2. $A_p = \frac{2.25 \cdot P_o}{\sqrt{2} \cdot K_w \cdot B_m \cdot J \cdot f_s} = 1.46172 \times 10^{-8} \text{ m}^4 = 14617.2 \text{ mm}^4$

3. $N_p = \frac{V_{imax}}{2 \cdot A_c \cdot B_m \cdot f_s} = 16.4$ Set $N_p = 17$

SELECT P36/22
 $A_c = 201 \text{ mm}^2$
 $A_w = 101 \text{ mm}^2$
 $A_p = 20100 \text{ mm}^4$
 $l_m = 53.2 \text{ mm}$

Next step is find the area product. So, the area product for a forward converter we have derived $2.25 P_{naught}$ by $\sqrt{2} K_w B_m J f_s$. P_{naught} is what we have calculated here 44.1 Watts, K_w we will take it as 0.4 a conservative value, actually an the 0.4 is actually a value where the winder is quite experienced and skilful. B_m for transformers we reduce the B_m for inductors we used to take 0.25 Tesla, but for transformers. Do not swing beyond 0.2 Tesla because we want to limit the magnetising current and also to keep the swing within the well within the linear region of the BH curve.

Then J same as before as you used for inductors 3 into 10 to the power of 6 amp per meter square or 3 amp per mm square. Frequency switching frequency 20 kilo hertz as given as a spec. Now, if you apply all these and calculate you get 1.46172 into 10 power minus 8 meter to the power 4 multiply this by 10 to the power of 12 you will get it in mm

to the power of 4, 14617.2 mm to the power of 4.

Go to the wire table as before and then search for a core which has a higher A P than this. In our case here we cancel again select P 36 bar 22 pot core which has an area product of around 20000 mm to the power of 4; A c upto 201 mm square, A w of 101 mm square, A p area product of 20100 meter to the mm to the power of 4, mean magnetic path length 53.2 mm. So, these are the characters of the core that we have selected pot core P 36 bar 22.

Next, we go to the turns primary number of turns N p is given by V i max divided by 2 A c B m f s V i max is 24 plus 10 percent which is 26.4 Volts; A c we have found out 201 into 10 power minus 6 meter square, B m 0.2 Tesla and 20 kilohertz on calculation you will land up with 16.4 set N p as 17 turns.

(Refer Slide Time: 05:38)

The image shows a handwritten derivation on a whiteboard. At the top right, there are two red annotations: $A_p = 20100 \text{ mm}^4$ and $l_m = 53.2 \text{ mm}$. The main calculation starts with the formula for the number of primary turns:
$$3. N_p = \frac{V_{i\max}}{2 \cdot A_c \cdot B_m \cdot f_s} = 16.4$$
 Green arrows point from the values 24 + 2.4 = 26.4 V to $V_{i\max}$, from 201×10^{-6} to A_c , from 0.2 T to B_m , and from 20 kHz to f_s . Below this, it says "Set $N_p = 17$ turns". Then, it sets $d_{\max} = 0.45$. The next step is the voltage balance equation:
$$V_{i\max} \cdot d_{\min} = V_{i\min} \cdot d_{\max} = (1.1 V_o + V_D)$$
 Finally, it solves for d_{\min} :
$$d_{\min} = \frac{V_{i\min} \cdot d_{\max}}{V_{i\max}} = 0.41$$

Next let us try to find out what is the turns ratio. Set d max has 0.45. Remember that this is a forward converter you cannot have a duty cycle more than 0.5. Therefore, set d max has 0.45 to be on the safer side and V i max d min should be equal to V i min, d max should be equal to whatever the output voltage; here the upgraded output voltage 1.1 V naught plus V D.

Now, using these two you can find d min because d max is set. So, d min is equal to V i min d max by V i max; you know V i min 24 minus 2.4 d max 0.45, V i max is 26.4 you

can find out d_{\min} which is 0.41 duty cycle.

Now, this 1.1 V naught plus V_D should be equal to our forward converter input output relationship n into $V_{i\max}$ into d_{\min} and here n is the only unknown 1.1 V naught V_D divided by $V_{i\max}$ and d_{\min} root apply the values at 1.35.

(Refer Slide Time: 07:06)

$$\begin{aligned}V_{i\max} \cdot d_{\min} &= V_{i\min} \cdot d_{\max} = (1.1 V_0 + V_D) \\d_{\min} &= \frac{V_{i\min} \cdot d_{\max}}{V_{i\max}} = 0.41 \\(1.1 V_0 + V_D) &= n V_{i\max} \cdot d_{\min} \\n &= \frac{(1.1 V_0 + V_D)}{V_{i\max} \cdot d_{\min}} = 1.35 \\N_s &= n \cdot N_p = 1.35 \cdot 17 = 23\end{aligned}$$

And, N_s is equal to n into N_p which will turn out to be 1.35 into 17 which is 23 turns. So, N_s is 23 turn. If you are using a demagnetising winding; remember, demagnetising winding will be very thin wire because it is only the magnetising current that will flow through it probably will be SWG 45, but you need to use the same number of turns as N_p which is 17.

(Refer Slide Time: 07:38)

4. Wire gauge

$$I_{s\text{rms}} = I_o \sqrt{d_{\text{max}}} = 2 \text{ A}$$
$$I_{p\text{rms}} = n I_{s\text{rms}} = 2.7 \text{ A}$$
$$a_{wp} = \frac{I_{p\text{rms}}}{J} = 0.9 \text{ mm}^2 \Rightarrow \text{SWG 18}, a_{wp} = 1.167 \text{ mm}^2$$
$$a_{ws} = \frac{I_{s\text{rms}}}{J} = 0.67 \text{ mm}^2 \Rightarrow \text{SWG 19}, a_{ws} = 0.8107 \text{ mm}^2$$

5. Window area check: $K_w A_w = 40.4 \text{ mm}^2$
 $N_p a_{wp} + N_s a_{ws} = 39.1 \text{ mm}^2$

Next step is to find the wire gauge. So, I s secondary rms is see do I naught into root d is the current rms current that is flowing through the secondary. So, I naught root d max you can calculate around 2 amps, 3 amps into root of 0.45. I p rms is nothing, but n times I secondary rms which is 2.7 amps. And, calculate the a wire cross section of the primary I p rms by J; J you take it as 3 amp per mm square. You will land up with 0.9 mm square. Area of the cross section of the secondary winding wire I s rms by J you have 0.67 mm square. For the primary go to the wire table and you will see that SWG 18 will fit it as a wire cross section of 1.167 mm square and SWG 19 will fit for the secondary a ws will be 0.8107 mm square.

Finally, come and do the crosscheck window area crosscheck to ensure that the windings will fit into the core. K w A w can calculate 40.4 meter mm square and N p a wp plus N s a ws will be equal to 39.1 mm square. So, you see that the window area check is satisfied and the design of the forward converter transformer is complete.