 


Analog Electronic Circuits
Professor S. C. Dutta Roy
Department of Electrical Engineering
Indian Institute of Technology Delhi
Lecture 27
Class A Power Amplifier: Efficiency Considerations

Today we are going to look at class A power amplifier and calculation of efficiency both in class A and also in class B and class AB under some idealized assumptions. If you recall the class A power amplifier circuit, a very simple circuit that was drawn yesterday with integrated circuits in mind. That is we used the minimum number of resistors and as many transistors as required.

We have a V_i plus minus, the main transistor Q_1 which is operating in the emitter follower mode. That is the collector is connected directly to plus V_{CC} and this emitter goes directly to the load R_L . The voltage here is V_o of t . We have gone back to the time domain and the current through this is i_o of t .


(Refer Slide Time: 01:56)



In order to bias the transistor we use another transistor in the current mirror mode. That is we use a Q_3 whose emitter goes to minus V_{CC} and the current I_Q of Q_3 is decided by the main transistor which is the current deciding transistor which we have called Q_2 .

Its collector is connected to the base and this is connected to a resistance R_1 . The current through this is I_{REF} , the reference current and this naturally has to go to plus V_{CC} , okay. This is the transistor and the emitter is connected to this.


(Refer Slide Time: 02:57)

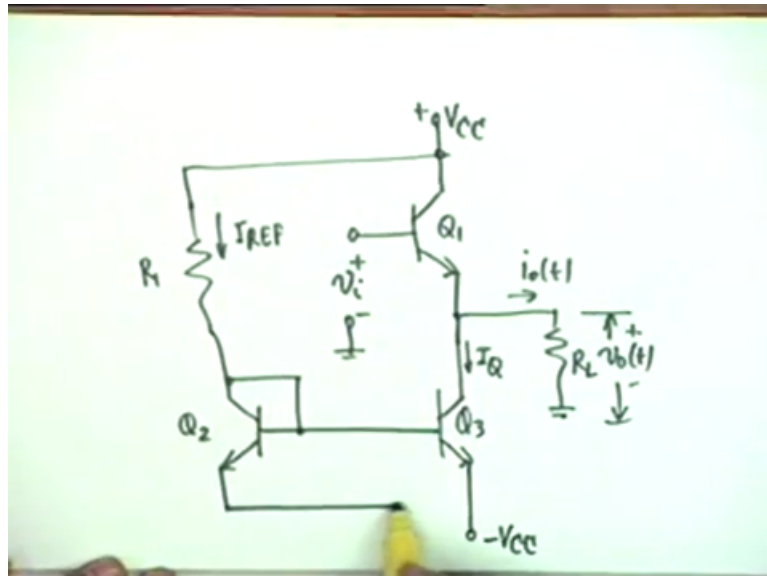

I have shown a simple current source but it could be a wiggler source depending on what value of I_Q you want. If you want a very low as compared to I_{REF} then you use a wiggler source, another resistance here, okay. Obviously I_Q is approximately equal to I_{REF} , okay. And this I_{REF} is equal to twice V_{CC} , yes, minus V_{BE} on which we will use as point 7 divided by R_1 , okay. This is the value of I_Q .

Now in order to determine the transfer characteristic of the class A amplifier that is transfer characteristic is plot of V_0 versus V_i . In order to determine that we take the total currents in total voltages. Let us called this current as $I_{sub\ total\ current\ capital\ C\ 1}$. Small i subscript capital C 1 if you recall our terminology, $I_{sub\ C\ 1}$. And then this voltage this will change with the applied signal. So this voltage will no longer called capital V_{BE} but we call small $v_{BE\ 1}$, the total voltage, alright.

(Refer Slide Time: 04:34)

 

Then obviously the relationship is that V_i is equal to v_{BE1} plus V_0 , agreed. Let us write this relationship that is worth 1000 words. This relationship as we will see $V_{sub i}$ is equal to $v_{sub BE1}$ plus V_0 . If you recall the current versus base emitter voltage characteristics v_{BE1} can be written in terms of $I_{sub C1}$ and the relationship is that this is $V_T \log$ of the current $I_{sub C1}$.

Please be careful about the notation. It is the total current divided by I_{S1} , alright. Plus V_0 , okay, V_0 and you also notice from this circuit that $I_{sub C1}$ if we ignore the base current that is if we consider β to be very large compared to unity which we assumed throughout then $I_{sub C1}$ is obviously the sum of I_Q and i_o , is not it right?

And i_o is obviously V_0 divided by R_L and therefore from these observations I can write this as V_i equal to $V_T \log$ of I_{S1} and this can be written as I_Q plus V_0 divided by R_L plus V_0 . If you see it carefully unfortunately this is my relationship between V_i and V_0 and obviously it is a transcendental equation and it can be solved only by iteration, alright?

(Refer Slide Time: 06:26)

$$\begin{aligned}
 v_i &= v_{BE1} + v_o \\
 &= V_T \ln \frac{i_{C1}}{I_{S1}} + v_o
 \end{aligned}$$

$$v_i = V_T \ln \frac{I_Q + \frac{v_o}{R_L}}{I_{S1}} + v_o$$

That is for a particular V_i you assume a value of V_o , see if the right hand side is equal to the left hand side. If not, change it and go ahead doing it till you get a reasonably good approximation between the left hand side and the right hand side. Maybe the difference is of the order of 10^{-4} . The error criteria you have to decide yourself, okay. However for very large R_L such that V_o by R_L can be ignored compared I_Q , we can find an approximate relationship, okay.

So we consider a case, case 1 in which R_L is large. If R_L is large then obviously the relationship is V_i approximately equal to $V_T \log$ of I_Q divided by I_{S1} which is a constant now. We approximate this term which varies with V_o by a constant plus V_o and this obviously is V_{BE1} , the DC voltage across the first transistor between the base and the emitter plus V_o which means that V_o is equal to V_i minus point 7 volt, our usual relationship that we got in class B also. It is the same relationship, okay.


(Refer Slide Time: 07:53)

$$\begin{aligned}
 \text{Case I } R_L \text{ large} \\
 v_i &\cong V_T \ln \frac{I_Q}{I_{S1}} + v_o \\
 &= V_{BE1} + v_o \\
 v_o &= v_i - 0.7
 \end{aligned}$$

And therefore for large load where V_0 by R_L can be ignored compared to the quotient point current I_Q , I_Q was established not by load line but by a current mirror, okay. Now this relationship obviously is very easy to plot. We shall have when V_i equal to point 7, the output voltage is 0. V_i , V_0 . V_0 is 0 when V_i equal to point 7 which means that the characteristic would be something like this. It will have an offset here. This voltage would be point 7. What would be this voltage? When V_i is 0 it should be minus point 7, okay.

So you know these two lines and then the relationship is V_0 equal to V_i minus point 7. So the slope would be unity however it does not go indefinitely because the maximum output voltage and the minimum output voltage they are both limited. What is the maximum that is permitted? V_{CC} minus $V_{CE1 \text{ sat}}$. There is a reason why I am saying V_{CE1} .


(Refer Slide Time: 09:22)

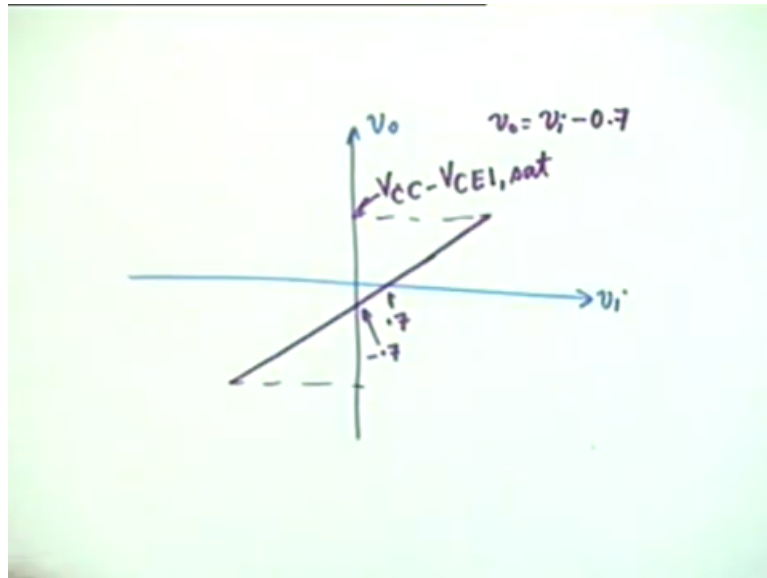

Let us look at the circuit. This voltage the maximum that can happen is in the positive side is plus V_{CC} minus the voltage up here. On the other hand on the negative side the minimum value when V_0 is negative the minimum value that can occur is minus V_{CC} plus $V_{CE3 sat}$. Is the point clear? Okay. So we have found out what the minimum is. Minus V_{CC} plus $V_{CE3 sat}$. It is therefore important.

You see even with these symmetries, even with these lower limit and upper limit the swing is not symmetrical because it does not pass through the origin. Do you not see that? But it is class A operation. Class A why do we refer to class A? In order to reduce the distortion as much as possible therefore we shall never go to saturation. But theoretical limits of the maximum positive swing is V_{CC} minus $V_{CE1 sat}$, your input voltage. What is the input here? Input voltage is this plus point 7. Similarly this voltage would be this plus point 7, okay.

(Refer Slide Time: 10:52)

 

So you know the input voltages. The input voltage must not exceed these two values either on the positive side or on the negative side. You must be well within these limits. This figure only shows the limits, okay. You should not operate the transistor so that the peak swing goes here because then you are asking for distortion. You can as well go to class AB or class B amplifier, okay.

Class A amplifier is for low power level and very little distortion, okay. However if we go back to the relationship, what was the relationship? V_i was equal to $V_T \ln$ of I_Q plus V_0 divided by R_L that divided by I_{S1} plus V_0 . This is our exact relationship, the transcendental.

(Refer Slide Time: 11:58)

Hand-drawn equations on a whiteboard showing the relationship between input voltage v_i and output voltage v_o . The equations are $v_i = V_T \ln$ and $v_i = V_T \ln \frac{I_Q + \frac{v_o}{R_L}}{I_{S1}} + v_o$.

Now a problem arises when R_L is small. When R_L is small in the previous case we considered R_L large so that the first term could be approximated by a constant, then the task was easy. When R_L is small and these two terms are comparable to each other then the problem arises because when V_i is negative, V_o will also be negative. It is an emitter follower after all.

V_o will also be negative and there is a possibility that this term may go to 0 or negative. Is that clear? So when V_i is less than 0, V_o less than 0 and if V_o is less than or equal to minus $I_Q R_L$ what will happen? This term cannot be found out.

(Refer Slide Time: 13:05)

$$v_i = V_T \ln \frac{I_Q + \frac{v_o}{R_L}}{I_{S1}} + v_o$$

R_L small

$$v_i < 0 \Rightarrow v_o < 0$$

or $v_o \leq -I_Q R_L$

Physically what will happen? Physically suppose V_o , let us consider this point. V_o equal to minus $I_Q R_L$. Under this condition this will be 0, log of 0 would be minus infinity and therefore V_i would be minus infinity and infinite negative voltage is required. Obviously this does not make sense. There must occur something physical. If we look at the circuit what will happen? Pardon me. Say it loud even if you are saying it wrongly. How does it matter?


Student: Q 1 will cut off.

Q 1 will cut off. Why? That is a good answer. Why? Yes, what was the question?

Student: I could not understand that if V_i is negative how can V_o be negative?


Because it is an emitter follower basically, is not it right? The collector is connected to plus V C C and therefore whatever voltage appears should appear here except for this drop, agreed, okay.

(Refer Slide Time: 14:13)

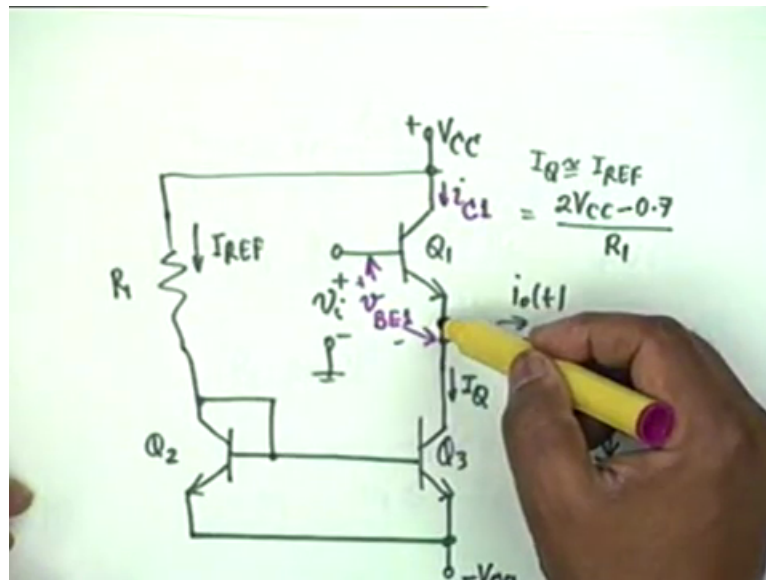

Now if V_0 is equal to minus $I_Q R_L$, what does it mean? V_0 is $i_0 R_L$ which means that i_0 is actually in this direction and the actual current would be I_Q here, right? When V_0 equal to minus $I_Q R_L$ this must be the direction of the current, agreed? So I_Q comes like this and flows like this. In other words nothing flows through Q_1 . So Q_1 goes into cut off, not saturation. Q_1 goes into cut off. Saturation it flows a current. But if it does not give a current, if it does not contribute to a current at this junction means it is cut off.


(Refer Slide Time: 15:02)

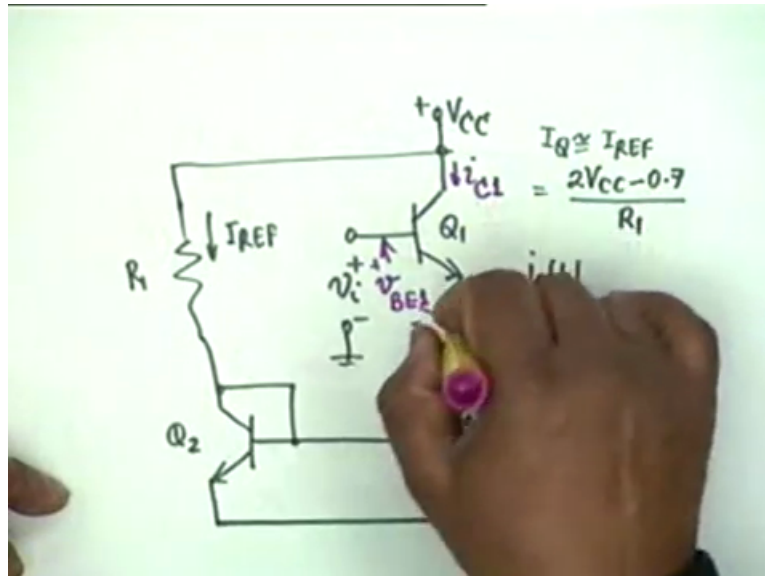

So physically much before this inequality starts affecting the circuit Q 1 shall be cut off which means that if we plot V_0 versus V_i well we will have a plot like this. I am showing it a straight line. It will not be a straight line because there is a logarithm involved. It is a transcendental equation but it is very nearly a straight line . It is not exactly a straight line.

While the upper limit is still set by $V_{CC} - V_{CE1, sat}$. The upper limit the maximum positive voltage, maximum positive value V_0 is still set by this. The maximum negative voltage will be set much before that at the level minus I_{QRL} . The absolute minimum that is possible is minus V_{CC} then plus $V_{CE3, sat}$. That we have already seen but what happens is before that I_{QRL} puts Q 1 off and if Q 1 is off then no amplification, alright, okay.

(Refer Slide Time: 16:34)

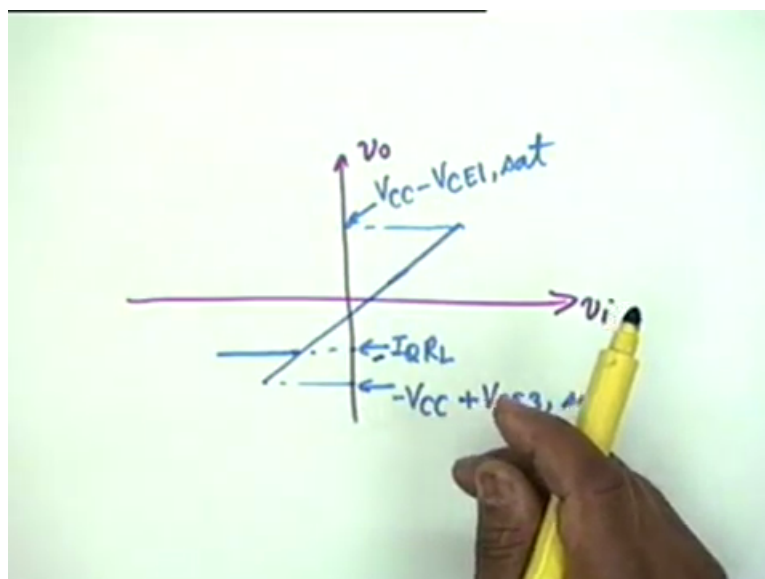


So in the case that R_L is small, one has to be careful. The swing in the negative direction would be limited unless, now this also shows you a design criteria. What should be your design criteria? Design criteria if you want as large a swing as possible, since $I_Q R_L$ is limiting your swing and R_L is given, R_L is not your choice, R_L is known and therefore you have to design your current mirror such that I_Q is approximately equal to $V_{CC} - V_{CE3, sat}$ divided by R_L . Do you understand this? You have followed this?

This picture clearly shows a design criteria that if you want as large a swing as possible, you have to take care of the negative swing. Positive swing will occur automatically because I_Q plus V_0 by R_L when V_0 is positive is positive. There is no problem but when V_0 exceeds minus $I_Q R_L$ then obviously Q_1 goes into cut off and therefore your I_Q should be approximately equal to $V_{CC} - V_{CE3, sat}$ divided by R_L .

Then we shall get an approximately equal possible swing in the positive as well as negative direction without distortion. It is not that you cannot apply a large input voltage but its negative swings will be clipped. Your wave form if it is this situation and if you have driven the transistor to insanity which means saturation on the positive side and beyond this saturation, beyond cut off in the negative side what you will get is your output waveform would be like this, agreed? Highly distorted because cut off at minus $I_Q R_L$.

(Refer Slide Time: 18:41)

 

If you want to restore this obviously you will have to go back and redesign your current mirror such that I_Q approximates this. Point clear? We will have problems on this later to be

worked out, okay. With all these now let us look at the efficiency that a class A power amplifier can give. Efficiency as I already told you is defined as the P_L average load power. The load power will be a function of time $V_L V_0 t$ multiplied by $i_0 t$. You have to take the average value over one cycle.

You are basically asking for undistorted amplification so one cycle of sin wave is good enough. Divided by the DC power that is supplied by the battery. And as I had told you earlier this DC power is mostly dissipated in the output transistors and therefore if you calculate the dissipation in the output transistors that is good enough. Or the other way is take the supply and connect an emitter there, DC emitter. The supply multiplied by the DC emitter that will be P D C.

If you want to emphasize that the power is being dissipated only at the collector then one sometimes uses the symbol η_C and calls it collector efficiency which means that the actual efficiency of the amplifier, power efficiency would be less than the collector efficiency because in collector efficiency you are not taking care. You are only taking care of collector dissipation you are not taking care of the other transistor, the current mirror transistor for example, okay.

In any case we shall ignore all other transistors. We shall also ignore in our calculation very conveniently $V_{CE sat}$. We will assume that $V_{CE sat}$ is much less than V_{CC} . It is true in practice, 15 and point 2 and therefore it can be ignored. That will keep our calculations simple.

(Refer Slide Time: 21:07)

Class A Efficiency

$$\eta_c \triangleq \frac{P_L}{P_{DC}}$$

$V_{CE, sat} \ll V_{CC}$

Now suppose in the class A amplifier $I_{Q,R,L}$ has been so selected that $V_{0,t}$ is equal to $V_{0,m}$, the maximum value multiplied by $\sin \omega t$. And $V_{0,m}$ that is the transistor has been driven to its maximum possible swing then $V_{0,m}$ would be approximately equal to what? V_{CC} because we are ignoring $V_{CE, sat}$, okay.

And therefore if you have a sinusoidal voltage $V_{CC} \sin \omega t$ across a load R_L then what is P_L ? P_L is V_{CC} peak value is V_{CC} so root mean squared value V_{CC} by root 2, square of that divided by R_L . So it would be V_{CC}^2 by $2R_L$, agreed?

(Refer Slide Time: 22:16)

Class A Efficiency

$$\eta_c \triangleq \frac{P_L}{P_{DC}}$$

$V_{CE, sat} \ll V_{CC}$

$$v_o(t) = V_{om} \sin \omega t$$

$$V_{om} \cong V_{CC}$$

$$P_L = \frac{V_{CC}^2}{2R_L}$$

If you are not convinced you calculate it out like this. $V_{CC} \sin \omega t$ whole squared divided by R_L is the instantaneous value integrates from 0 to capital T. Capital T is 2π by

omega and divide by capital T. This is P L and you can verify that this is equal to V C C squared divided by 2 R L.

Now what is the DC power supplied by this source? The effective source is twice V C C and the quotient current is I Q. We are ignoring all base currents, okay. The average current, the DC flowing through Q 1 Q 3 combination is I Q. So P D C must be twice V C C I Q, very simply, okay.

(Refer Slide Time: 23:13)

The image shows a handwritten derivation on a light green background. The first equation is the average load power P_L calculated as the average of the instantaneous power over one period T . The instantaneous power is $\frac{(V_{CC} \sin \omega t)^2}{R_L}$. The period T is given as $\frac{2\pi}{\omega}$. The integral is from 0 to T . The second equation shows the result: $P_L = \frac{V_{CC}^2}{2R_L}$. The third equation shows the DC power $P_{DC} = 2V_{CC} I_Q$.

$$P_L = \frac{1}{T} \int_0^{T = \frac{2\pi}{\omega}} \frac{(V_{CC} \sin \omega t)^2}{R_L} dt$$

$$= \frac{V_{CC}^2}{2R_L}$$

$$P_{DC} = 2V_{CC} I_Q$$

And therefore the efficiency eta which is the ratio of the two is simply 1 quarter V C C by I Q R L. You know let us multiply this by 100 so on a percent. You know that you have to adjust I Q, you have to design I Q such that I Q R L is approximately equal to V C C. V C C minus V C C E 3 but we are ignoring that and therefore eta max is only equal to 25 percent, maximum efficiency. Therefore every watt you have to be prepared to supply 3 watts, 4 watts.


Every watt of load power you have to be prepared to supply 4 watts and 3 watts are wasted. Where? Obviously in the transistors and you must allow for dissipation of these 3 watts that is wherever these output transistors are either you have to supply a cooling fins or you have to physically force cool air into them, okay. So that is the story. Class A therefore is very inefficient and I had told you that class B and class AB is resorted to when you want a higher efficiency.

And the reason for higher efficiency in class B or class AB should be clear that there is no quotient current or the quotient current is very small. You see V B E is kept at point 7 or

minus point 7 in the PNP. Then the transistors are on the onset of conduction. So the Q point in the absence of the signal, the DC that flows through Q 1 and Q 2 in the class AB amplifier is very small and therefore the quotient power dissipation is approximately 0. Power dissipation however occurs when there is a signal.

Why? Because each transistor conducts only for half the cycle. Each transistors acts as a half way rectifier and half way rectifier waveform has a DC and therefore that is a dissipation and we will show now that this efficiency in class B can be increased to 78 point 5 percent. You see the increase it is approximately pie by 4 percent.

(Refer Slide Time: 25:41)

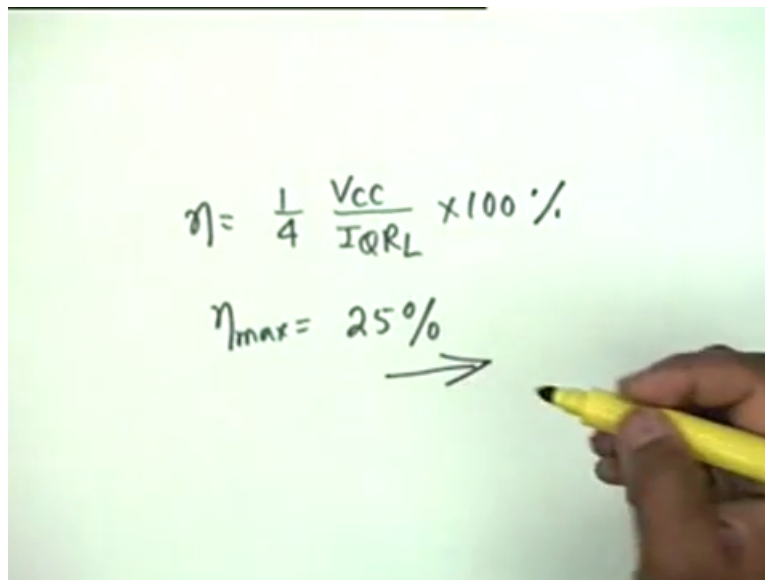

The image shows a hand holding a yellow marker writing on a whiteboard. The equations written are:

$$\eta = \frac{1}{4} \frac{V_{CC}}{I_{QRL}} \times 100\%$$


$$\eta_{max} = 25\%$$

An arrow points from the 25% result towards the right.

We will see how this comes about. But before that let us look at the power distribution in class A amplifier, okay. It is instructed to draw these diagrams. Let us say my V i t is of this form. I am drawing only one cycle. Draw these vertical lines. Suppose this is V i t then V C E 1 t would be V C C minus V 0 t, okay.

V C E 1 t, collector emitter drop if you recall the circuit, would be V C C minus V 0 of t. But V 0 is approximately equal to V i if you ignore that V B E 1 so it would be of the form V C C minus let us say V i m sin omega t which means that if this is the level V C C then to start with V C C minus V i m sin omega so to start with it will go negative, agreed? And then it will go positive like this.

(Refer Slide Time: 27:33)

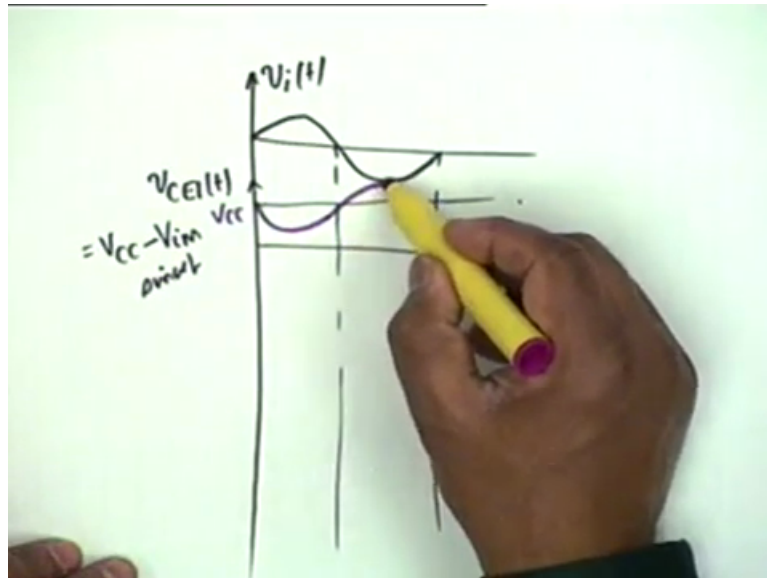


The maximum value here would be V_{CC} plus V_{im} and the minimum value would be V_{CC} minus V_{im} , is the point clear? Okay. If superimposed on V_{CC} we are not assuming that V_{im} is equal to V_{CC} that means we are assuming that because it is a class amplifier it is not driven to the maximum. We will see what happens when it is driven to the maximum.

So the minimum that it can come to is 0 and the maximum it can go to twice V_{CC} , agreed? That is the absolute maximum possible for V_{CE} , okay. As far as the current is concerned I_{C1} that will also be sinusoidal about what value? What is the average value of I_{C1} ? What is the average value?

Student: I_Q .


I_Q and therefore now current waveform would it follow? Would it be like this? In phase with V_i or out of phase? That is very simple. When the input increases, the current increases. When the base drive increases, the current decreases. So it is like this. Sorry, it is sinusoidal. The maximum is I_Q plus i_m and what is i_m ? What is this maximum value? I_Q plus V_{im} divided by R_L , agreed? V_{0m} is approximately equal to V_{im} and the minimum value is I_Q minus V_{im} by R_L , alright?

(Refer Slide Time: 29:27)

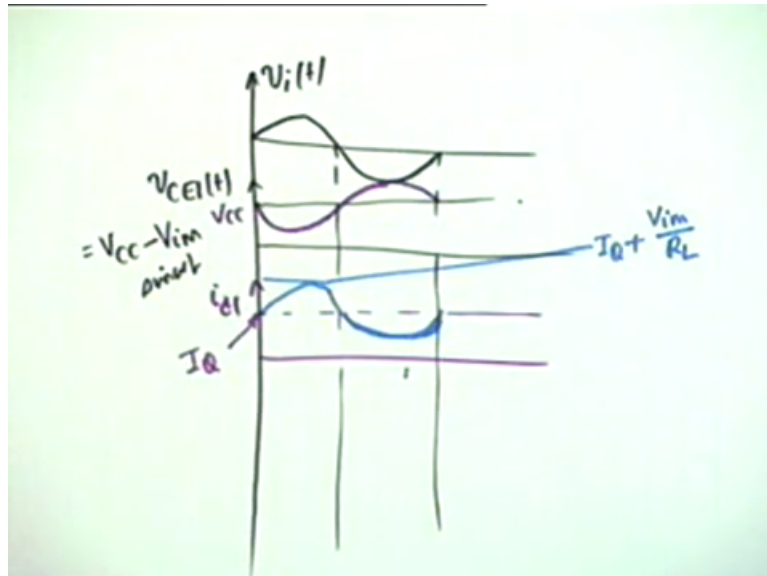

My drawings are not very good but you should take this with a pinch of salt, okay. Then the power $P_{L,t}$, the load power obviously shall be the multiplication of the black waveform and the blue waveform or you could simply square this and divide by R_L , alright? In any case it would be something like this. It is $V_{CC} I_Q$, this is the maximum value say it starts from here V_{CC} and I_Q then it goes down like this, goes down like this and comes like this.


(Refer Slide Time: 30:23)

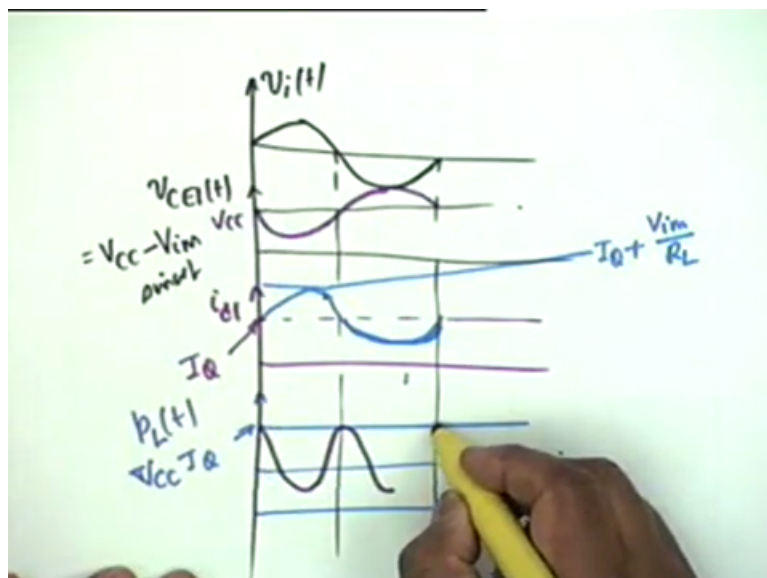

This is the power which is simply the square of this curve, alright, divided by R_L , agreed? Now the power curve $P_{L,t}$ can reach a minimum value of 0. That is I might be able to come, let me use some other colour, I might be able to come up to this under what condition? Pardon me, V_{im} is equal to V_{CC} , alright.

And under this condition that is when the class A amplifier is driven to its limits you can show very simply that. I made a mistake. This is not P_L . This is P_C . This is the power dissipated in the collector. $V_{CE} I_C$, okay, so I made a mistake here.

(Refer Slide Time: 31:36)

 

You can show that when the transistor is driven to (saturation) its limits then V_{CE} is simply $V_{CC} - V_{im} \sin \omega t$, agreed? V_{im} becomes equal to V_{CC} multiplied by I_Q then $1 + \sin \omega t$. The maximum value would be equal to I_Q , agreed? When the transistor is driven to its limits, let me look at this, this minimum will come to 0 and that can happen when i_{Cm} the maximum is equal to I_Q , okay. So this is $V_{CC} I_Q$ multiplied by $1 - \sin^2 \omega t$ which is $\cos^2 \omega t$.

And if you take the average value of this P_C which is P_C average, if you integrate this with respect to t and divide by 2π what do you expect what would be the value? $V_{CC} I_Q$ divided by 2, alright? Whereas what we have found out is that the total power supplied P_{DC} is equal to twice $V_{CC} I_Q$. So where are the other components? We have found out the dissipation in Q_1 , average dissipation in Q_1 is this $V_{CC} I_Q$ by 2.

(Refer Slide Time: 33:25)

$$P_{DC} = 2V_{CC} I_Q$$


$$P_{C1}(t) = V_{CC} (1 - \sin \omega t) \times I_Q (1 + \sin \omega t)$$

$$= V_{CC} I_Q \cos^2 \omega t$$

$$\underline{P_{C1} = \overline{P_{C1}(t)} = \frac{V_{CC} I_Q}{2}}$$

I require another $3 V_{CC} I_Q$ by 2 to be able to get this figure. Where are the others? What does Q_3 dissipate? P_{C3} , what does Q_3 dissipate? The current is a constant I_Q and the voltage across it is average voltage V_{CC} , is not it right? If you look at the circuit, let us go back. I have lost it. Here you see the voltage across Q_3 the average voltage is V_{CC} , is not it right? Because this voltage is a fluctuating sinusoidal voltage. The average value of this voltage is V_{CC} . The average current is I_Q and therefore the dissipation in Q_3 is equal to V_{CC} times I_Q .

(Refer Slide Time: 34:27)

 


So P_{C3} is $V_{CC} I_Q$. Now I have been able to get $3 V_{CC} I_Q$ by 2. What about the other one? Load power that is correct. What I missing is $V_{CC} I_Q$ by 2 which I can write as V_{CC} divided by root 2 multiplied by I_Q divided by root 2. This is the RMS value of the load

voltage and this is the RMS value of the load current and therefore this is equal to the load voltage.

And indeed P D C is equal to P L the load power plus the power dissipated in the transistor Q 1 plus the power dissipated in the transistor Q 3. And that checks. This is only to give you a physical picture of how the power is being distributed, distribution of power.

(Refer Slide Time: 35:25)

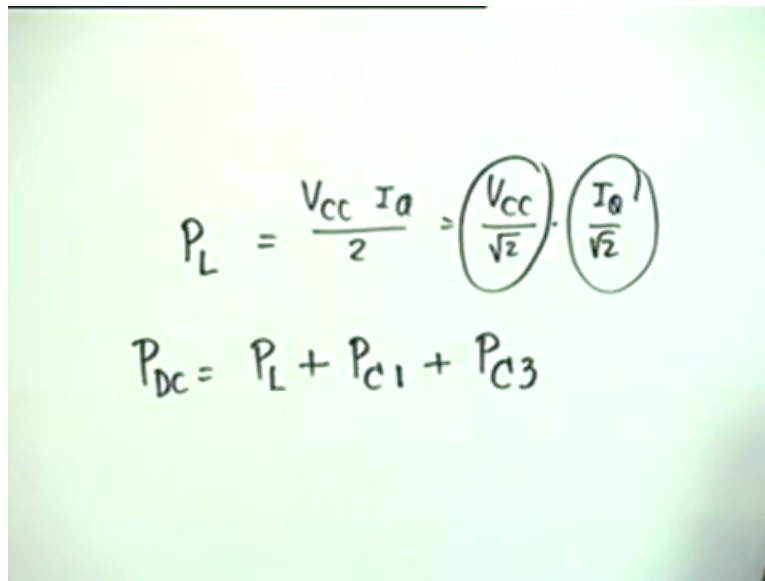
$$P_L = \frac{V_{CC} I_a}{2} = \left(\frac{V_{CC}}{\sqrt{2}}\right) \cdot \left(\frac{I_a}{\sqrt{2}}\right)$$
$$P_{DC} = P_L + P_{C1} + P_{C3}$$

Now let us look briefly at the class B amplifier. If you recall we will ignore crossover distortion, alright? We will ignore crossover distortion and we will also ignore V C E sat, is it convenient? Yes.

Student: Sir, we find out that the maximum power dissipation 50 percent is in the transformer Q 3 in this case, transistor.

Transistor Q 3. That is correct.

Student: Sir is there any major implication of this?

Any major implication? Well it has to be designed to.

Student: Sir, can I reduce this to anything?


Yes there are modifications but then what you do is you distribute it somewhere else. You see the point that is making is that Q 3 dissipation V C C I Q it is double the power dissipation of transistor Q 1. But you see in the worst case Q 1 also has to be prepared to dissipate V C C I Q. But during the operation when there is a signal transistor Q 3 dissipates twice the power

that transistor Q 1 dissipates. And transistor Q 3 has to be more robust. There is the implication.

Now what we can do is transistor Q 3 can be replaced by 2 in parallel. Then the power is split or the circuit can be modified so that this power dissipation is shifted somewhere else, is distributed, okay. Nothing else can be done because class A is class A and the maximum is 25 percent. For every watt load power you have to be prepared to dissipate 3 watts. It is unfortunate that the main transistor or it can even be fortunate because the current mirror may be added externally if it goes off. But the main transistor still remains.


Well it is a matter of opinion. But let us look at class B. As I said we ignored crossover distortion, we also ignore the $V_{CE\ sat}$. This is for convenience in calculation. This is the transistor Q 1, then we have a transistor Q 2 which is a PNP transistor and this voltage is minus V_{CC} . The power goes from here to R_L . This is $i_o(t)$ and this is $v_o(t)$, very simple circuit. The two bases are connected together and this voltage is $v_i(t)$, okay.

(Refer Slide Time: 38:14)

 

Now to have a picture of what goes on, okay, let us call this as i_{C1} and this current as i_{C2} . Then you know that i_{C1} will take care of the positive half of the load current and i_{C2} , the negative half of the load current. So if I plot i_{C1} it would look like this, okay. This is i_{C1} whereas i_{C2} , I have taken care of the direction, i_{C2} would be in between ones, is that okay?

(Refer Slide Time: 39:08)

 

I C 2 are the negative half but the directions i_{c2} comes like this so the load current is in the opposite direction. They help the load current to remain sinusoidal, okay. And I think that is all the picture that we need. Let us go into the calculation. Suppose the $V_o(t)$ is suppose $V_m \sin \omega t$, alright? Then $i_o(t)$ would be equal to $V_m / R_L \sin \omega t$. It is a resistive load, agreed?

So $p_L(t)$ would be simply $V_m^2 \sin^2 \omega t / R_L$ and the load power which is the average value of $p_L(t)$ would be simply average value of $\sin^2 \omega t$ is half, so it would be $V_m^2 / 2R_L$. We could write this term without going to the average value because if this is the voltage across the resistance R_L , the power dissipated is $V_m^2 / 2R_L$, okay.

(Refer Slide Time: 40:36)

$$\begin{aligned}
 v_o(t) &= V_m \sin \omega t \\
 i_o(t) &= \frac{V_m}{R_L} \sin \omega t \\
 p_L(t) &= \frac{V_m^2 \sin^2 \omega t}{R_L} \\
 P_L &= \overline{p_L(t)} = \frac{V_m^2}{2R_L}
 \end{aligned}$$

Now what about the DC power supply P D C. P D C which is equal to small p D C average, okay. Let us see what is small p D C t? When Q 1 conducts what is small p D C? V C C multiplied by the load current which is V m by R L sin omega t, is this point clear? When Q 1 conducts Q 2 does not. The drop is V C C and this is the load current and this is for 0 less than t less than capital T by 2.

And when Q 1 does not conduct, Q 2 conduct, the instantaneous power expression is the same, okay. So this would be T by 2 less than t less than capital T. In other words the P D C which is the average value of small p D C would be twice the average value of this expression, okay, over half the period, 0 to t by 2.

(Refer Slide Time: 42:17)

$$P_{DC} = \overline{P_{DC}(t)} = 2x$$

$$P_{DC}(t) = \frac{V_{CC} V_m}{R_L} \sin \omega t \quad 0 < t < \frac{T}{2}$$

$$= \quad " \quad \frac{T}{2} < t < T$$

What is the average of sin omega t over half the period? So it would be 2 V C C V m divided by pie R L, is that clear? The average value of sin omega t over half the period is 1 by pie and I multiply it by 2. Why? Because there are two half periods. To make one complete period there are two half periods and therefore I can now find out my efficiency.

My efficiency would be P L is V m squared divided by 2 R L and P D C is twice V C C V m divided by pie R L and this works out to pie by 4 V m divided by V C C multiplied by 100 percent, okay. And you also know that the maximum swing that is possible at the load is V C C. V m, absolute maximum is V C C therefore eta max is pie by 4 which is 78 point 6 percent.

(Refer Slide Time: 43:38)

$$\eta = \frac{V_m^2 / (2R_L)}{2V_{CC} V_m / \pi R_L}$$

$$= \frac{\pi}{4} \frac{V_m}{V_{CC}} \times 100\%$$

$$\underline{\eta_{max} = 78.6\%}$$

That is the major advantage of a class B amplifier. That is for every watt of power to be dissipated in the load you have to be prepared to supply how much? 1 point?

Student: 1 point 3.

Approximately, no it is less than 1 point 3. 1 minus point 786, okay. 1 point 214, okay, so many watts. This is the major advantage of a class B amplifier. Now in the subject of power amplifiers the quality of a power amplifier whether it is class A, class B or class AB are determined by two parameters, okay. Just like a voltage amplifier you require A_v , R_i and R_o .

In a power amplifier the impedances are not of consideration because in most of the power amplifiers it is a (amp) common collector for an emitter follower circuit. Emitter follower circuit is characterized by high input impedance and low output impedance. So it is eminently suitable for power amplification because who is feeding a power amplifier? The voltage amplifier and who is taking power? A small load maybe a loudspeaker, okay.

So input and output impedances are of no consideration. What is of consideration is efficiency. How good a power amplifier is depends on how much power you waste. How much power you can deliver to the load and how much power is delivered by the supply. The other parameter is the so called THD. All stereo amplifiers have this specification, total harmonic distortion. And this is defined as follows.

It is defined as the square root of power in harmonics divided by total power. It means what we want across the load is let us say a voltage or a current of the form $A \sin \omega t$. If

ω_0 is your input frequency this is what we want across the load. Unfortunately due to large excursions there comes nonlinearities and we get let us say $A_2 \sin 2\omega_0 t$ plus etc. We get the higher harmonics.

Harmonics means frequencies are integral multiples of the fundamental frequency and therefore if this current flow through a load then it would be square of this multiplied by the load R_L . And you know that if you have a sum of currents of different frequencies flowing through a load R_L then the power would be simply the average power dissipated due to each component. It is super position.

In other words the load power, if this is the current then it would be A_1^2 multiplied by R_L and the power due to this would be A_2^2 multiplied by R_L and the total power would be a sum of these two, okay.

(Refer Slide Time: 47:28)

Handwritten equations on a green background:

$$THD \triangleq \sqrt{\frac{\text{Power in harmonics}}{\text{Total power.}}}$$

$$A_1 \sin \omega_0 t + A_2 \sin 2\omega_0 t + \dots$$


$$\frac{A_1^2}{2} R_L + \frac{A_2^2}{2} R_L + \dots$$

This could be very easily shown. Can you? Take two terms and show that this is so. So the total power in harmonics what would it be proportional to? A_2^2 plus A_3^2 plus etc. Whereas the total power in the load would be A_1^2 plus A_2^2 plus etc. So THD total harmonic distortion would be square root of A_2^2 plus A_3^2 plus etc divided by A_1^2 plus A_2^2 plus A_3^2 and so on.

Usually what is our aim? Our aim is to make A_2, A_3, A_4 as small as possible compared to A_1 . So A_1 is usually much greater than A_i, i greater than equal to 2 which means that THD total harmonic distortion can be expressed as square root of power in the harmonics divided

by A_1 . That is the amplitude of the fundamental. Amplitude or root mean square value whatever you want. This is an approximate measure and this is what is used.

(Refer Slide Time: 48:54)

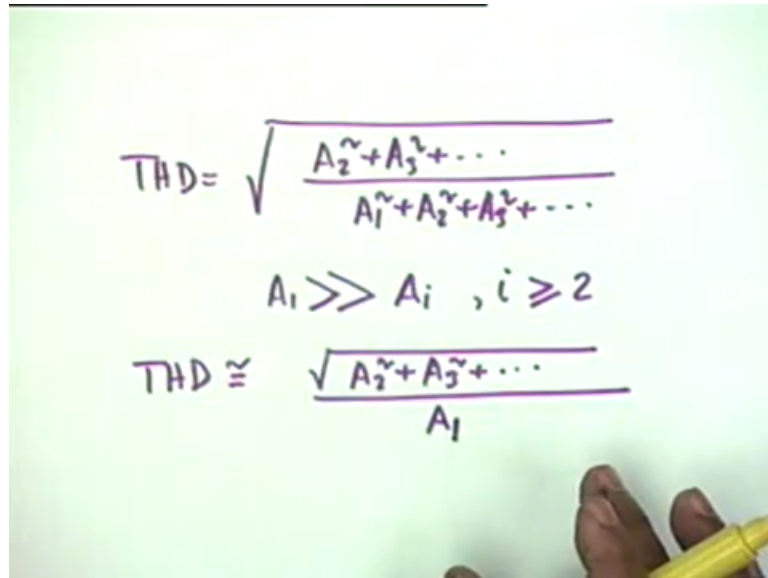
$$\text{THD} = \sqrt{\frac{A_2^2 + A_3^2 + \dots}{A_1^2 + A_2^2 + A_3^2 + \dots}}$$
$$A_1 \gg A_i, i \geq 2$$
$$\text{THD} \cong \frac{\sqrt{A_2^2 + A_3^2 + \dots}}{A_1}$$

People sometimes use a percentage measure which means that you multiply this by 100 and use a percentage, okay. We will stop here. We will in the Monday class work out problems.