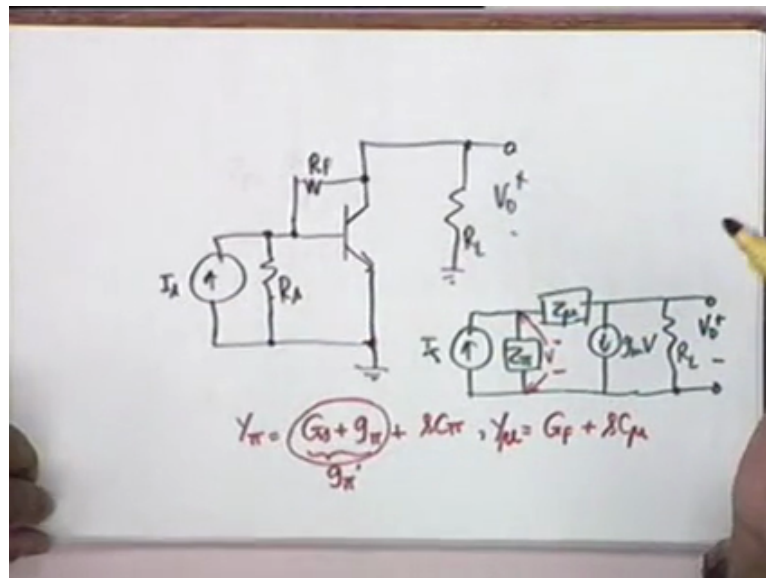


Analog Electronic Circuits.
Professor S.C. Dutta Roy.
Department of Electrical Engineering.
Indian Institute of Technology, Delhi.
Lecture-44.
Widebanding by Local Feedback.

(Refer Slide Time: 1:44)



44th lecture and we had already started last time broadband in by local feedback. We continue this discussion today. The circuit that we had considered was simply a single transistor amplifier with a feedback from the collector to the base through this resistance r_s . Obviously this is a shunt-shunt feedback but we did not use any property of feedback, we wanted to analyse it directly. This we had drawn last time and the equivalent circuit of this was drawn like this with several components combined together. Z_{π} for example takes care of r_s , the parallel combination of r_{π} and c_{π} , that is why y_{π} is equal to this.

(Refer Slide Time: 2:46)

$$\begin{aligned}
 Z_T = \frac{V_o}{I_s} &= \frac{1}{C_\pi} \frac{s+z}{s^2+b_1s+b_0} \\
 &= \frac{z}{C_\pi b_0} \frac{1+s/z}{1+\frac{b_1}{b_0}s+\frac{s^2}{b_0}} \\
 z &= \frac{G_F - g_m}{C_\mu}, \quad b_1 = \frac{g_\pi' + g_m + G_L}{C_\pi} + \frac{G_F + G_L}{C_\mu} \\
 b_0 &= \frac{G_L(G_F + g_\pi') + G_F(g_\pi' + g_m)}{C_\pi C_\mu}
 \end{aligned}$$

And in addition this quantity g_s plus g_π represented by g_π' and y_μ is the inevitable C_μ between the base and the collector and a parallel connected r_f , therefore y_μ is g_f plus sC_μ . And then we had tried to calculate the transfer function, the transfer function here is v_o over i_s , recall that the dimension obviously is that of impedance and therefore we call it Z subscribed capital T , capital T for transfer, that is the transfer impedance Z_T equals v_o by i_s and we derive this to be of the form 1 over $C_\pi s$ plus Z divided by s^2 plus $b_1 s$ plus b_0 .

Obviously this can be written in following form, Z over $C_\pi b_0$, this is the midpoint again, might be gain and then $1 + s/z$, $1 + b_1/b_0 s$ plus s^2/b_0 . Obviously few good s equal to 0 , this is the mid-band gain, Z by $C_\pi b_0$, Z is 0 , $C_\pi b_0$. The values of these constants were given earlier, Z is simply equal to g_f minus g_m divided by the C_μ , b_1 is equal to g_π' plus g_m plus G_L divided by C_π plus g_f plus G_L divided by C_μ .

And b_0 is a longish expression, $G_L(g_f + g_\pi') + G_F(g_\pi' + g_m)$ divided by $C_\pi C_\mu$. Let us not get lost in the complication of these expressions, these are, these come by algebra but nevertheless you keep this because inaudible calculate, in order to do a numerical design or analysis you shall require these formulas.

(Refer Slide Time: 4:49)

$$R_T = \frac{z}{C_{\pi} b_0} \checkmark \approx -R_F$$

$$g_m \gg G_F, \beta \gg 1, g_{\pi}' \approx g_{\pi}$$

$$\frac{V_o}{V_s} = -\frac{R_F}{R_A}$$

$$Z_{out} = \frac{Z_{\pi} + Z_{\mu}}{1 + g_m Z_{\pi}}$$

$$R_{out} = \frac{Y_{\pi}' + R_F}{1 + g_m Y_{\pi}'} \approx \frac{R_F}{\beta} + \frac{1}{g_m}$$

low

Now we had found out also the output and input impedances of this configuration and it came out, well 1st was the mid-band gain, the mid-band gain which is z_{π} by $c_{\pi} b_0$, mid-band gain, okay, z_{π} by $c_{\pi} b_0$, this was exact equation you can find out but we had shown this is approximately equal to minus r_f , approximately equal to minus r_f under the following conditions. That g_m is much greater than g_f , β is much greater than 1 and I think that is all. β much greater than 1, which means g_{π}' is approximately equal to, oh, g_{π}' was approximately equal to g_{π} , which means that r_s is much larger compared to r_{π} , agreed.

These are the assumptions under which r_t is equal to this and we had also interestingly found out that if we calculate v_0 , , no v_0 by v_s , okay, v_0 by v_s , then this is equal to minus r_f divided by r_s , okay, which was comparable to an op-amp commented in the inverting

configuration. Okay. Last time we also derived an expression for the output impedance z_{out} , z_{out} is to be obtained by open circuit and $i_{sub s}$ connecting a voltage generator at the output without r_l , z_{out} is the impedance seen by r_l and calculating the current and this was found out to be z_{π} plus z_{μ} divided by $1 + g_m z_{\pi}$ and the mid-band value r_{out} which is equal to z_{π} would be simply r_{π} prime, z_{π} is the parallel combination of r_{π} and c_{π} , plus mid-band value is r_s , $1 + g_m r_{\pi}$ prime and this is approximately equal to r_f divided by β .

(Refer Slide Time: 7:49)

$$Z_{in} = Z_{\pi} \parallel \frac{Z_p + R_L}{1 + g_m R_L}$$

$$R_{in} = Y_{\pi} \parallel \frac{R_F + R_L}{1 + g_m R_L}$$

$$\approx \frac{Y_{\pi} (R_F + R_L)}{\beta R_L}$$

low $\beta \gg 1, \beta R_L \gg Y_{\pi} + R_F$

R_{π} prime is approximately equal to r_{π} , $g_m r_{\pi}$ is β and β is much greater than 1 over g_m , okay. And this is a low value, output impedance is low because the feedback is shunt. At the output the connection is shunt, it is a voltage sampling, okay. Similarly we had found out that the input impedance z_{in} which is obtained by connecting a voltage generator at the input and finding out the current, z_{in} was equal to z_{π} parallel z_{μ} plus r_l divided by $1 + g_m r_l$ and the mid-band value was equal to r_{π} parallel r_f plus r_l , z_{μ} mid-band value is r_f , divided by $1 + g_m r_l$.

And if you carry out the algebraic ensure that this is approximately equal to $r_{\pi} r_f$ plus r_l divided by $\beta + 1$. Underwater condition, β much greater than 1 so that $\beta + 1$ is equal to β and gather this $\beta + 1$ must be much greater than r_{π} plus r_f , okay. And this is also low because of a shunt connection at the input. Okay, this is also a low value because of the shunt connection at the input. Typical values we had taken, recall this example because we shall carry this example through.

(Refer Slide Time: 9:05)

$$R_F = 10K, g_m = 0.04 \text{ S}, \beta = 50$$

$$R_L = 1K$$

$$R_{out} \approx 225 \Omega$$

$$R_{in} \approx 235 \Omega$$

$$f_H \uparrow$$

$$Z_T = R_T \frac{1 + s/z}{1 + \frac{b_1}{b_0} s + \frac{1}{b_0} s^2}$$

$$\frac{1 + \omega_H^2/z^2}{\left(1 - \frac{\omega_H^2}{b_0}\right)^2 + \left(\frac{b_1}{b_0} \omega_H\right)^2} = \frac{1}{2}$$

Quadratic in ω_H^2

Rf was 10k, gm was 0.04 mhos, beta was 50 and rl was 1k, under these conditions our r out was simply equal to 225 ohms approximately and r in approximately was 235 ohms, these are comparable values, they are lower values, okay, they are lower values. This low value of the, of the input and output impedance it is very important as we shall see when you use overall feedback or you use more than one stage of feedback. Then the matching between the preceding stage and the succeeding stage will require that you use a series-series, that you use a series-series succeeding shunt-shunt. You understand?

If the output is a shunt connection, then the matching, formatting we require a series connection at the input, so that the input impedance is much larger, okay. Now as i said last time we are left with a million-dollar question of calculating fh, the high-frequency with 3 db point. Okay, this is the motivation, we wanted to broadband the amplifier that will increase fh


as much as possible. Now if you recall the transfer function, it is not very complicated, it is some mid-band value, let say ω_{mid} multiplied by $1 + s$ by z upon $1 + b_1 s + b_0 s^2$.

And therefore ω_h shall satisfy the equation, I do not have to write anything else putting s equal to $j\omega_h$, taking the real part, imaginary part, I can do it by inspection. You see what will happen is $1 + \omega_h^2$ by letter that square, am taking the magnitude square, divided by $1 - \omega_h^2$ divided by b_0^2 , real part squared plus b_1 by $b_0 \omega_h$ whole square. This should be equal to, now, this should be equal to half, that is right, because the mid-band gain has been taken away. And the magnitude should be $1/\sqrt{2}$, magnitude square should be half.

So what you have to do is to solve for this equation, obviously this is a quartic equation of information ω_h , quartic, quartic means degree 4. ω_h^2 square but it is a quadratic in ω_h^2 , therefore it is quadratic in ω_h^2 and therefore if you are very fussy, solve quadratic, it is not very difficult, solve quadratic. Okay. Quadratic in ω_h^2 and therefore it can be solved. But if you are lazy and, and or there is a c_0 also, then obviously, obviously the degree of the equations we solved would be.

If there is another capacitor then the degree will increase by 1, therefore it will be cubic equation in ω_h^2 , then the cubic equation has to be solved to numerically. The analytical solution is not convenient, you cannot write a formula, you go through several algorithmic steps. So it is, it would be good to consider the method, the alternative methods that are available. One of them of causes the application of the miller technique.

(Refer Slide Time: 13:13)

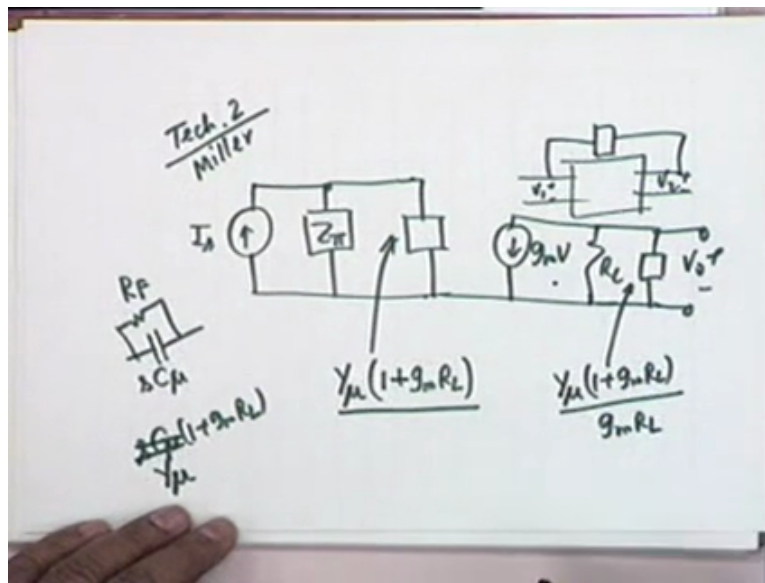

Now if you recall the equivalent circuit was is, technique 1, technique 1 is solution of the equation, exact equation. Technique 2, that is due to miller, okay, technique to, what we do is z_{π} , then since z_{μ} is the culprit, we reflect it to be important also to the output. Now if we reflect it to the input, what would this impedance, it is better to find the admittance, the admittance would be y_{μ} multiplied by 1 minus gain, 1 minus gain and gain is minus $g_m r_l$, so 1 plus $g_m r_l$. Is the point clear?

No.

Okay, if it was c_{μ} , how do you reflect this? It becomes $c_{\mu} (1 + g_m r_l)$ and therefore this admittance $s c_{\mu}$ reflects as $s c_{\mu}$ times this. Instead of $s c_{\mu}$ i have a parallel connection of $s c_{\mu}$ and r_f and therefore the admittance is g_s plus $s c_{\mu}$. Therefore this shall be replaced by y_{μ} , is a point clear now? Instead of appear capacitance, that is a capacitance in parallel with the resistance, so you take the total admittance and reflect this as $y_{\mu} (1 + g_m r_l)$. Yeah?

(())(14:46) approximation, what we do is gain...

It is the mid-band game. This is the approximation.

So here is the mid-band gain.

If you had found out take that gain and put it here, then it would not have been miller approximation, the word approximation had to be crossed out. But if you put the exact gain,

your life will be miserable because this will become less quantity, okay, life would be miserable. Anyway...

(())(15:19) impedances and voltage source in parallel...

That would not matter between this point at this point whatever the gain is. You know the miller effect is, you have an intermediate part of the circuit in which you know the gain between port 1 and port 2, then any impedance that is connected here can be reflected to the input through v_2 by v_1 and to the output through again v_2 by v_1 . So this current source and voltage output has no place, there is a bridging impedance which you do not want to take into analysis and then it is reflected to the input and reflected to the output, that is it.


But putting the r_f even will change when the mid-band again.

Putting in r_f would even change the mid-band gain, this is quite correct (())(16:14), keep your eyes closed. Okay. Now, then we have, at the output circuit what do we have? We have $g_m v$, then r_l , what is it reflected as, this is v_0 , what would be this impedance? It would not be $y \mu$, it would be $y \mu \frac{1 + g_m r_l}{g_m r_l}$, that is correct. And it is equal to $y \mu$ only under that condition...

Minus $g_m r_l$.

No, $1 - \text{gain}$, no $1 - \text{gain}$, divided by gain bandwidth product, gain bandwidth, yet. Now it would be equal to, approximately equal to $y \mu$ if g_m is much greater than 1, which we assumed. Alright, i am illustrating this, although this is not needed because the quadratic equation can be solved. But i am illustrating this to get, to get an idea of the general miller effect, not just the capacitor, let us say any impedance, then how do they reflect?

(Refer Slide Time: 17:38)

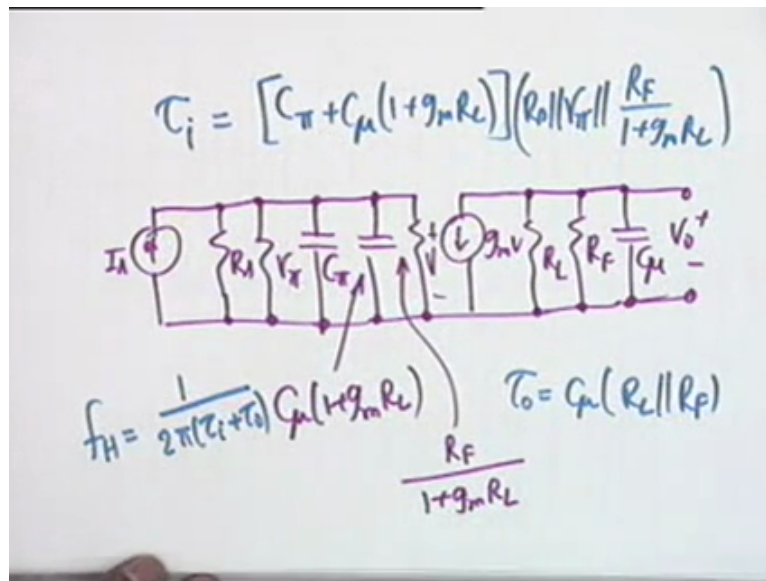

Now if you, if you expand this Miller equivalent, you shall have is, let us go to z pi, what was z pi, rs, r pi, you will understand why i am expanding this because i want to calculate the time constants, rs, r pi and then we had c pi, then miller, y mu 1+ gm rl gives me a capacitance which is c mu 1+ gm rl and a resistance, what would be its value? Rf upon 1+ gm rl, you see it will be reflected as it low impedance now and it might become comparable to rs and r pi and therefore it has to be taken into account, clear.

Okay, then we have gm v, this is v, gm v, then rl and since the reflected impedance on the right-hand side is simply y mu, it shall have rf and c mu. I am assuming that gm rl is much greater than unity, v0, i must emphasise that this is an exact, not an exact circuit, it has imperfections in many ways. Nevertheless, it gives, will show, it gives reasonably good values, okay. This is my equivalent circuit, now in order to analyse this...

Sir.

Yes?

If we take (19:22).

Would it be better... perhaps, perhaps.


It would be better or worse?

I cannot as this question now because what you have to do is to take the mid-band equivalent circuit and actually calculate the mid-band gain. It would not be gm rl obviously because rf is

going to affect it, you see there is a potential division between r_f and r_l but unfortunately r_l is not a pure resistance, it is parallel by g_m , you have to make an analysis. Now, therefore now it is not a problem, we have 2 capacitors and we can apply the method of open circuit time constants or we can analyse this exactly, the 2 frequencies, 2 critical frequencies which the 2 poles which will affect the overall effects, obviously it is the parallel combination of c_{π} and this, c_{μ} and this capacitance.

So we shall have one time constant as c_{π} plus $c_{\mu} \parallel g_m r_l$ multiplied by, multiplied by r_s parallel r_{π} parallel r_f divided by $1 + g_m r_l$. Let us call this time constant as τ_o , what shall i call, τ_o , input time constant. This will obviously give rise to a factor of the form $1 + s \tau_o$. Okay. $1 + s \tau_o$ divided by ω where ω is $1/\tau_o$. And the output time constant τ_o is simply equal to c_{μ} times r_l parallel r_f . And your f_h , the high-frequency value, high-frequency 3 db point will be simply $1/\tau_o$, do not forget the factor 2π , $2\pi \tau_o$ plus τ_o , all right.

(Refer Slide Time: 22:06)

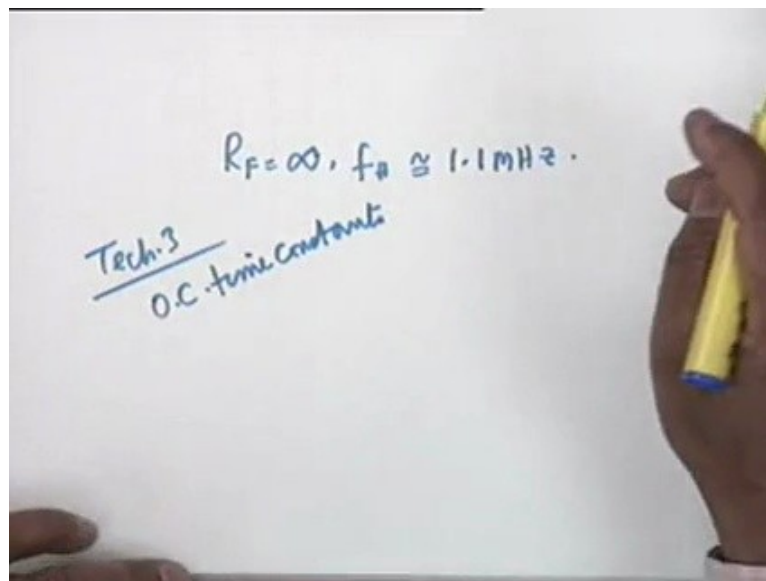

That is it, as simple as that, of course it is, it is an approximate figure. Let us take a specific example. The example that we had been considering, the example that we had considered, we require some extra values. Let us take c_{μ} equal to 2 picofarads, c_{π} equal to 25 picofarads, r_s was not given earlier, it was not required, r_s is 2.5 k, r_f was given as 10k earlier, r_l was also can read earlier, 1k, in calculating wooden output resistance is, the g_m for the transistor was 0.04 mhos and beta equal to 50. Then if we substitute the values, you get τ_o as equal to 20.2 nanoseconds, nano means 10^{-9} .

And τ_0 calculates out as 1.8 nanoseconds which is less than one 10^{th} of τ_i . Therefore the input circuit dominates f_h . Therefore f_h is approximately equal to, you can ignore this or if you do not want to ignore you add it up, okay. $1 / (2\pi\tau_i)$ and this calculates out as, I do know which I calculated, the approximate value of τ_i plus τ_0 but my result here is 7.88 megahertz, 7.88 megahertz. On the other hand, now if it is to be a broadband, obviously r_f was not there, what does it mean, r_f is infinity, if r_f is infinity and you recalculate the whole thing.

If r_f is infinity and you recalculate the whole thing, then you get f_h as equal to, approximately equal to 1.1 megahertz, so that broadbanding is by a factor of 7, almost a decade, almost a decade, factor of 7. But of course the sacrifice is, you have to sacrifice in gain.

(0)(24:22).



Approximation in miller...

(0)(24:27).

Output time constant is okay, miller only comes into effect, we have to take that help of miller because you have to find the 3 db point, the poles of the transfer function. Now as far as the output is concerned, it does not see only r_l , r_f and C_{μ} , no. It does see, we did not, we did not take into account miller in the reverse direction. If we had whatever saying would have been correct. Miller for example can be used for input impedance, that is not a problem but not in the case, you see we consider the transition to be unilateral and therefore we considered the gain v_2 by v_1 , if we consider v_1 by v_2 and reflected will be the same, yes, you will get what you wanted.

But we do not do that because usually the output impedance calculation is much simpler than f_h calculations. f_h calculation requires a set of node equations, loop equations, matrix inversions and things like that. Okay, so we want to do it by inspection, miller said okay available you. But of course you have to give a leverage, I mean you have to, you have to relax on the accuracy requirement. Technique 3, technique 3 is the method of open circuit time constant, that is without taking miller, open circuit time constants. Now this requires a bit of calculations because you will have to calculate the prevalent resistance seen by each capacitor by open circuit thing the other capacitors, okay.

(Refer Slide Time: 26:20)

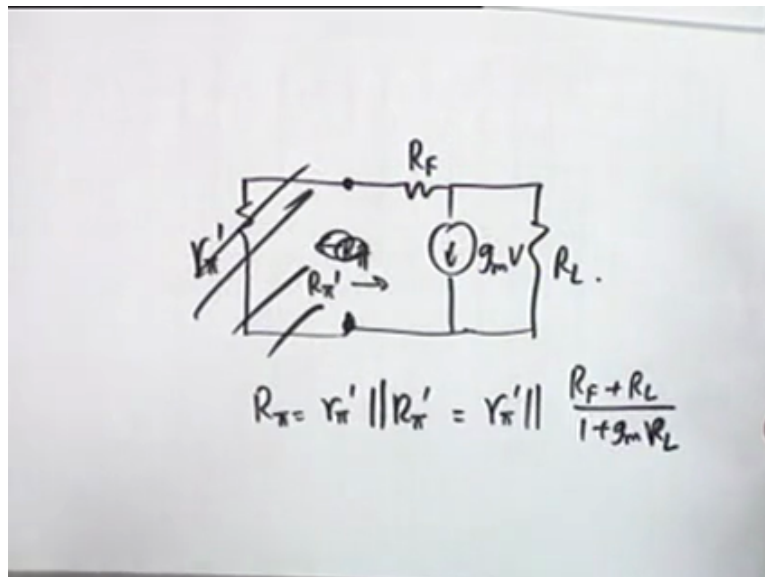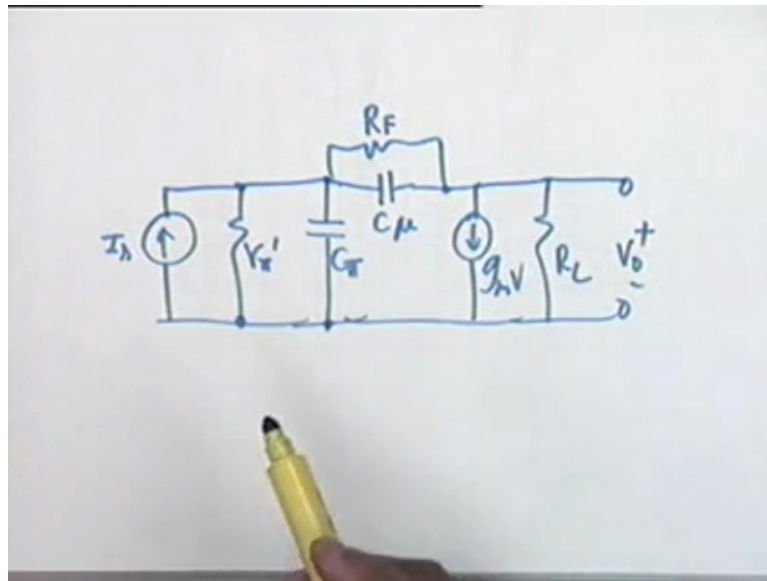


Recall the equivalent circuit, the equivalent circuit was is, then r_{π} prime, then, there are some tricks which I am going to, I have already done this but I am going to receive because you will get such calculations very often and then you should be able to do it very quickly, very quickly without even writing the loop equations and node equations and things like that, I will show you how. Not I will show you, I will indicate to you because they are not universal, you have to identify the circuit and then little bit of ingenuity of course.

The, let us draw the exact equivalent circuit and terms of its expansion because we want to isolate the capacitors r_{μ} , then this is $g_m v_{rl}$ and v_o . Now in this circuit if you want to calculate let's a resistance seen by C_{π} , then you have to open circuit C_{μ} and you have to open circuit is also. If you do that then the equivalent circuit for calculation of r_{π} , that is the

resistance seen by c_{pi} , I am drawing it from the equivalent circuit, we shall have r_{pi}' , okay, then an r_f , $g_m v$, and r_l . Alright, it is a resistance seen between these 2 points, one of the tricks is that if you can identify a series resistance or a parallel resistance isolate that.

Obviously r_{pi} would be equal to r_{pi}' parallel, what is seen by this circuit, okay. Do not include this, then you have to write extra term, okay, if you recognise this, then you open this, r_{pi}' parallel, let us call this as r_{pi}' , then you calculate r_{pi}' , which is obviously very simple task. And therefore the result is r_{pi}' parallel r_f , this we have done again and again, r_f plus r_l divided by $1 + g_m r_l$. If you do not remember the results, well it is not too bad, what you do is this is v , this is v , convert this mentally into a thevenin equivalence.

(Refer Slide Time: 29:28)

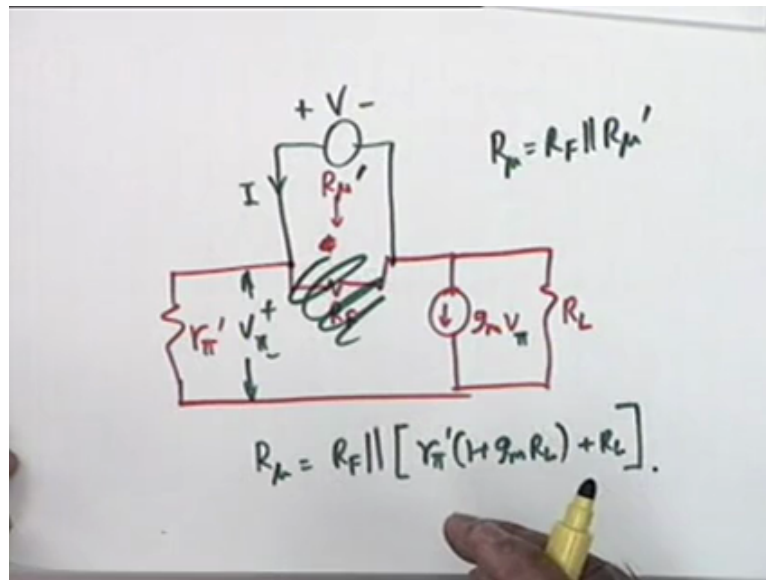

So you get $g_m r_l v$, right and therefore the equivalence source is v plus $g_m r_l v$ and the equivalent resistance is r_f plus r_l . All this can be done mentally, all right. It is not, it is not too complicated. Let us look at c_{mu} r_{mu} , the resistance seen by c_{mu} . Okay, the equivalent circuit is the following. Between these 2 points there is a resistance r_f , c_{mu} in parallel with r_f , then you have from here you have r_{pi}' and from here you get $g_m v$ and r_l . What you have to do is to connect a source here v , let us say this is the polarity and calculate the current i .

Another simplification you that the source v here in parallel with r_f , so you could as well r_{mu} would be r_f parallel r_{mu}' and you take off r_f , the circuit becomes normal simpler. Then

you can replace this by the thevenin equivalent, then it becomes a single loop and you can calculate the whole thing mentally.

Can you just repeat it again?

Can i repeat... i notice that r_{μ} is the parallel combination of r_f and the rest of the circuit. So i get rid of r_f , i write r_{μ} is equal to r_f parallel r_{μ}' where r_{μ}' is obtained by omitting this, then you have a source, a resistance and then parallel combination of current generator and r_l . And therefore you can replace this by thevenin equivalent. So v_{π} , okay and where is v_{π} ? That you must not... do not do anything to destroy this. Okay, if you make a transformation to destroy this, then of course your circuit calculations will go haywire.

So you must not destroy this, this is v_{π} . Then it becomes a simple single loop circuit and you can calculate. The result is r_{μ} is r_f parallel, now, yes? $R_{\pi}' + g_m r_l$, then it becomes multiplied, plus r_l , this is what the result is. So you know r_{π} capital r_{π} and you know capital r_{μ} and therefore you can calculate the 2 time constants.

(Refer Slide Time: 32:18)

$$f_H = \frac{1}{2\pi [\tau_{\pi} + \tau_{\mu}]}$$

$$= \frac{1}{2\pi [C_{\pi} R_{\pi} + G_{\mu} R_{\mu}]}$$

$257F$ 203Ω $2pF$ $7.79K$


And f_H will be equal to 1 over 2 pi, tau pi plus tau mu, that is 1 over 2 pi, $c_{\pi} r_{\pi}$ plus $c_{\mu} r_{\mu}$. And if we insert the values that we had already calculated, where already assumed for the transistor, please do check, my calculation says that r_{π} is 203 ohms and r_{μ} is 7.79k. Once again who dominates? Who dominates?

R_{μ} .

But c_{μ} is a small quantity, c_{π} is a large quantity. What is c_{μ} ? It was 2 picofarads and c_{π} was 25 picofarads, even then you see, even then this dominates. Is not that right? Okay but nevertheless the result comes as 7.71 megahertz, previously worked 7.88 miller approximation, so they are pretty close to each other. They are pretty close to each other. I did not calculate, did not a quadratic equation, you can also solve the quadratic equation and see how good these values are, you cannot make a generalisation however. Suppose the quadratic equation solution, the exact solution is close to this, you cannot say that method of open circuit time constant is better than miller, you cannot say, because both are approximation.

And in some cases this may be better, in some cases the other may be better. But anyway, any of these techniques is used only to estimate f_h , it cannot be calculated exactly, except when you solve the quadratic equations, okay. Now the complete local feedback, we will consider the other kind of local feedback which is used, namely an unbypassed emitter resistance, which is a series-series. The previous one was shunt-shunt, now it is a series-series and the circuit is like this.

(Refer Slide Time: 34:38)

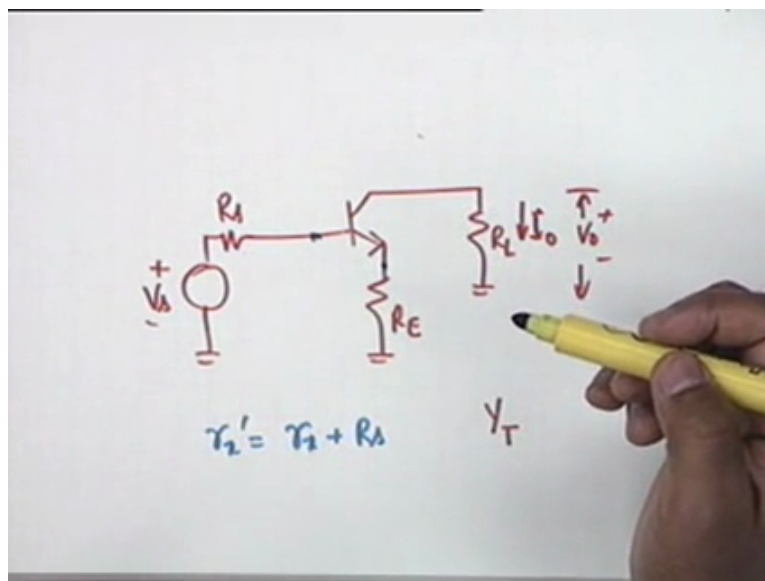


Very simple, now what should be the 1st now some voltage source or current source? Voltage source, okay. So we say r_s , we ignore everything else and we have v_s , then the feedback is through r_e and of course we have, what should be the output now? It is a series-series, so the output should be a current, let us say i_o and this is v_o , the output voltage is v_o . But our modelling should be in terms of a voltage to current, in other words the transfer function

should have the dimension of impedance or admittance? Admittance. So the transfer function should be y_t , transfer admittance, capital t subscript for transfer.

Even if you draw the equivalent circuit, you see now, since it is possible to take account of r_x , let us do that. r_x would be in series and there is one more reason why you consider r_s , because if this is an ideal voltage source, nearly ideal, the source resistance will be comparable to r_s . And therefore and since it is easy to take account of this, we do that. So what we do is let say we call r_x prime as r_x plus r_s , all right. Then you can mentally see the equivalent circuit which will have an r_x prime, then between this point and this point we will have z_{π} , parallel combination of r_{π} and c_{π} , then r_e and we shall have $g_m v_{\pi}$ and the inevitable c_{μ} , okay.

(Refer Slide Time: 36:44)

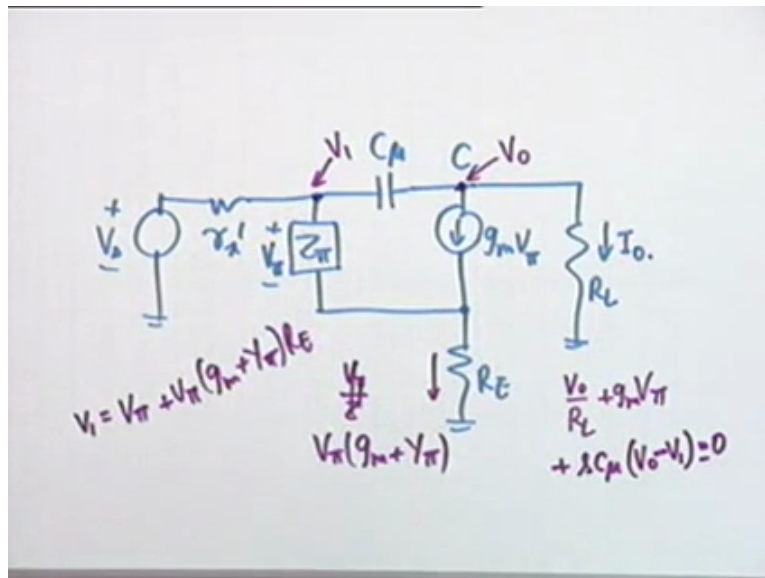

So the equivalent circuit but it is not as easy to analyse the previous circuit because r_e carries current from the base as well as from the emitter, okay, from the collector. Alright, so what we have is vs equivalent circuit, r_x prime, z_{π} , y_{π} is small g_{π} plus c_{π} , then we have c_{μ} , this is the collector, the collector sent a current to $g_m v_{\pi}$, this is v_{π} , v_{π} , v_{π} and this resistance is r_e , this goes to r_l and this is our current i_0 , this is the equivalent circuit. The 1st thing we do before doing anything else is that we identify this current, this current is obviously v_{π} over, okay, we can write this as $v_{\pi} g_m$ plus y_{π} , okay, this current.

And therefore, i have to find a relation between i_0 and v_s , i will not carry out the analysis but let us see how to look at it, how 2 located very critically and find out the shortest path. Obviously, if i know v_0 , then i know i_0 . So there are 2 notes for which the voltages are

unknown, let us call this voltage as v_0 , this voltage is v_0 and suppose this voltage is v_1 . All right, then i write in node equation here and a node equation here, all right. 2 node equations, will that solve the problem, no, there is a, there is an unknown quantity v_{pi} here also but you notice that v_1 is equal to v_{pi} , this voltage plus, plus $v_{pi} g_m$ plus y_{pi} multiplied by r_e .

Therefore i know v_{pi} in terms of v_1 , agreed and all that i have to do now is to write 2 node equations, one at v_1 and the other at v_0 . Obviously, the node equation at this node is v_0 by r_l plus $g_m v_{pi}$ plus $s c_{mu} v_0$ minus v_1 equal to 0. I cannot unfortunately apply thevenin or norton, that is my most favourite, because i do not have to write node equation. Unfortunately i cannot apply here, i not simplify, there is a control, control voltage, i cannot simplify this. I cannot, i cannot convert this into a thevenin's source because it has, it has a lot of complications around it. So leave it, leave it peacefully for the moment and if you have to write a node equation, let slightly node equation.

For this node equation will be, equation will be v_1 minus v_s divided by r_s prime, it is the current going away plus v_{pi} by z_{pi} , that is a current going through this. Plus v_1 minus v_0 as c_{mu} should be equal to 0. So eliminate v_1 and find out v_0 in terms of v_s and then find i_0 . i_0 is v_0 by r_l . If you do that, the expression, the equation that you get looks horrible but it can be put in this form.

(Refer Slide Time: 40:22)

$$Y_T = \frac{I_o}{V_s} = \frac{K(s^2 + as + b)}{s^2 + cs + d}$$


WH

i_0 by v_s as some constant k , the numerator becomes quadratic, look at the complication, as i said it is not as easy as the previous one, numerator becomes quadratic, s square plus cs plus d and the denominator is also quadratic. That the denominator would be a quadratic is

expected or not expected. There are 2 capacitors which has to be second-order transfer function, there is no question. In the previous case there was 1 zero as plus z, there are 2 zeros now. Can there be 3, can there be 3 zeros? Can the numerator be of degree 3? Yes it can, yes it can.

Okay transfer impedance after all, it is not a driving point impedance, okay. Now this looks rather complicated, we do not want to find out k, a, b, c and d and solve the equation exactly. If you solve it exactly, what would be the order of the equation to be solved for omega h? It would be, it would still be quadratic in omega h square, so it is not too bad. Although it looks a bit complicated, it is not too bad. Only thing is your a, b, k, c and d, they have to be found out, okay. So we will go in the shortcut we, we will see what the method of open circuit time constant gives us.

(Refer Slide Time: 42:12)

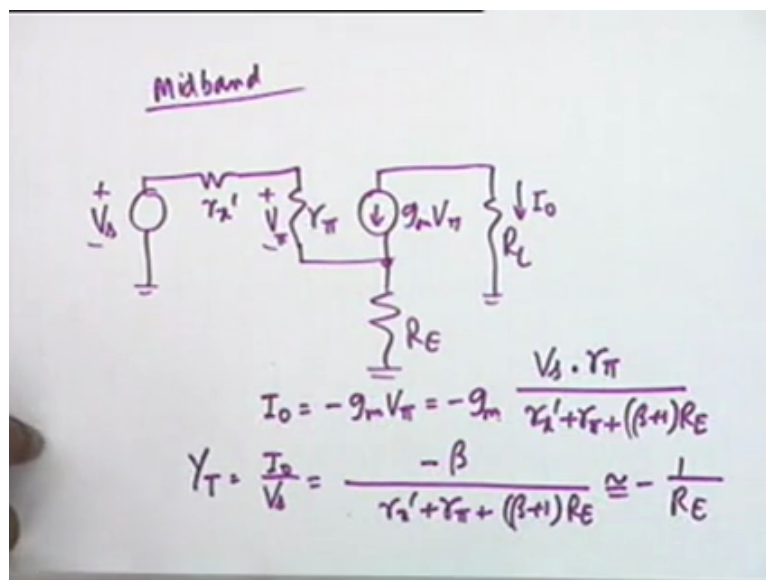


But before that, before that let us look at the mid-band quantity. It is good to have an idea of the mid-band gain, mid-band input impedance and so on. The mid-band equivalent circuit would be vs at mid-band, after all later on work we will do is simply add the pole, add the 2 poles and at the 2 zeros as or simply find out fh, we do not have to calculate the total circuit transfer function at all. Let us look at the midband, this is a shorter path. You see i did this analysis, wrote down the node equations and so on because i wanted to show you that there are 2 zeros than 2 poles.

We do not have to do this in practice, in the case of analysis and design, all that is required is to find out the fit ban gain and find out the fh, that is it. Okay and of course the input and

outputs resistances at mid-band, that suffices, let us see. This is r_x prime, then you have r_{π} , this voltage is v_{π} , $g_m v_{\pi}$ and r_l , this current is i_0 , this resistance is r_e . It should be obvious what the transfer function is, we do not have to write any node equations or any. You see, we simply write i_0 is equal to minus $g_m v_{\pi}$ and what is v_{π} ? V_{π} is v_s divided by the current, the current is r_x prime plus r_{π} plus, wonderful, $\beta + 1 r_e$ but you have to multiply this by r_{π} .


And therefore y_t is equal to i_0 by v_s , by inspection, that is why I said in the, in the actual circuit you do not have to make that frequency domain analysis. Midband is sufficient, this is equal to minus $\beta g_m r_{\pi}$ divided by r_x prime plus r_{π} plus $\beta + 1 r_e$. Do not you see that this is approximately equal to minus 1 by r_e ? Agreed, minus 1 by r_e . If that is so then what is v_0 by v_s ? What is v_0 by v_s ?

(Refer Slide Time: 44:42)

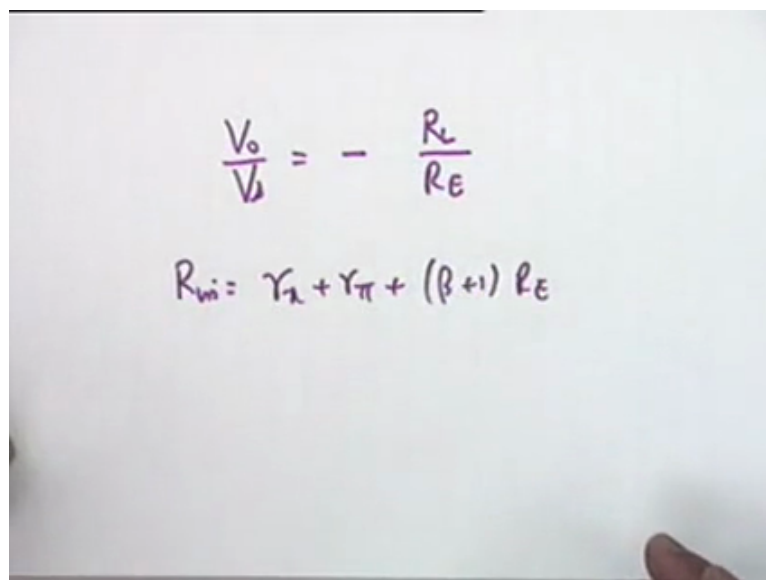

$$\frac{V_o}{V_s} = - \frac{R_c}{R_E}$$
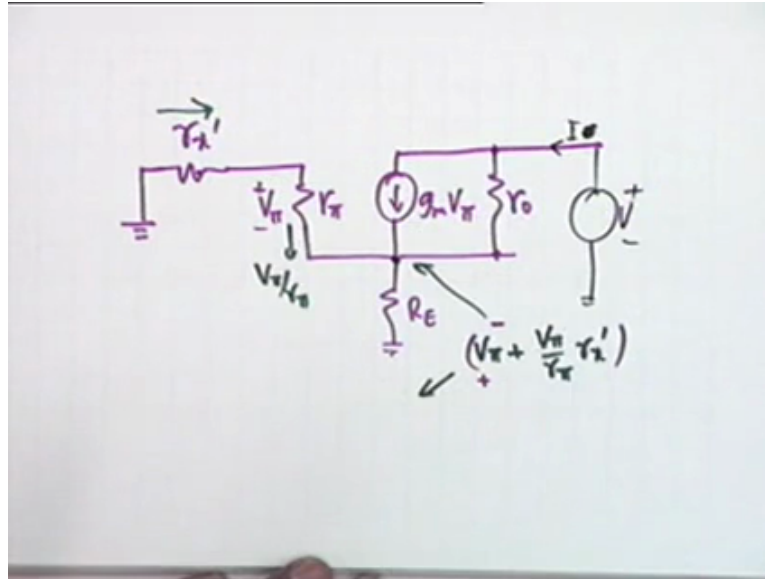
$$R_{in} = r_x + r_{\pi} + (\beta + 1) R_E$$



Minus r_l over r_e , did not we do this earlier? That with emitter unbypassed and beta large, the gain is approximately the ratio of the load resistance to the emitter resistance, in other words the gain is controlled by 2 external resistances, it becomes insensitive to the parameters of the transistors. That is a, that is a huge benefit. Now I can also see where the input impedance is. Do I? Input impedance is as seen by v_s , it is r_x prime plus r_{π} plus $\beta + 1 r_e$. So the midband input impedance r_{in} is also known, well if you are fussy you say what the source v_s r_s is, then it would be simply r_x plus r_{π} plus $\beta + 1 r_e$.

Now the question of output impedance. It is very, it is very tempting to say that the output impedance should be infinity because there is a current generator, no. This is not, if it was an independent current generator, here, what you are saying would have been tried. One has to actually calculate. Let us see what the equivalence circuit is. I will give you once again some tricks that one can apply to simplify the whole thing. To calculate the output impedance you have to put r_x prime to ground, input source is grounded, then you have r_{π} and this is v_{π} , you have $g_m v_{\pi}$, this is r_e .

In addition now, in addition now the output impedance, what you expect the output impedance to be, high or low? High and therefore it may be comparable to r_0 and therefore r_0 now further complicates matters. r_0 has to be considered, okay, do you understand why? Because it is a series-series and then what you have to do is to, if you connect a voltage generator here, v and find out this current i , find out the current i , okay, this is the circuit. Now

Sir what happens if we do not consider r_0 ?

Can you tell me what happens if we do not consider r_0 ? Pardon me? It would be infinity. That is right. And then the current generator will have 0 current, and it is a current generator anywhere and therefore you shall have infinity. It is instructed to calculate this by inspection without doing anything. You see what I do is I find out this current, let me use a different colour. This current is v_{pi} by r_{pi} and if I know this current, then do not I know this voltage, what is this voltage?


V_{pi} plus v_{pi} by r_{pi} times $r_{x'}$, this is the current. No, I beg your pardon, this is the voltage across this. Oh, this current is also v_{pi} by r_{pi} and therefore the drop across this is v_{pi} by r_{pi} $r_{x'}$. But there is a big question that I have, what about the polarity? Low as part will be positive and this part will be negative. Okay, I am going from here to here or here to here, so minus v_{pi} , minus v_{pi} by r_{pi} , this is the current multiplied by $r_{x'}$, that is what I have done. I have written the total voltage and this is the polarity.

And so if I know this voltage, then this I shall be simply $g_m v_{pi}$, wait a second, have to write a node equation here. This I shall be equal to $g_m v_{pi}$ plus the voltage across this which is v minus this quantity diverted by r_0 , one node equation, what else we have to write?

Current through r_e (49:35).

That is right, you see the current through this plus this should also be equal to i , is not that right? So these 2 equations and then almost by inspection you can write down the expression for the output impedance. I will simply give you the exact expression. And make them comments because the expression is interesting.

(Refer Slide Time: 50:06)

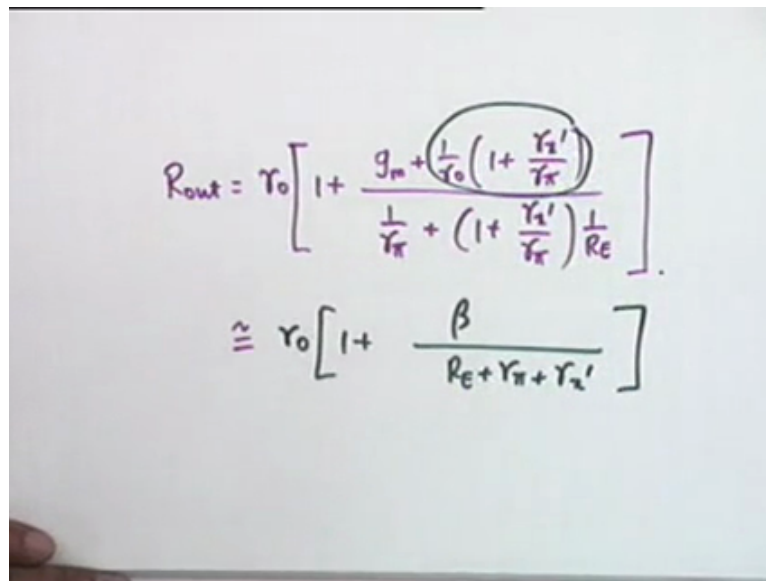
$$R_{out} = r_0 \left[1 + \frac{g_m + \frac{1}{r_0} \left(1 + \frac{r_2'}{r_x} \right)}{\frac{1}{r_\pi} + \left(1 + \frac{r_2'}{r_x} \right) \frac{1}{R_E}} \right]$$
$$\cong r_0 \left[1 + \frac{\beta}{R_E + r_\pi + r_2'} \right]$$

The r_{out} is equal to, exact expression is this, $r_0, 1 +$, now you can see that this is, is r_0 was not there, it would be infinity. $R_0, 1 + g_m + 1$ over $r_0, 1 + r_x$ prime divided by $r_\pi, 1$ over $r_\pi + 1 + r_x$ prime divided by r_π times 1 over r_E , this is take that expression. And if this quantity g_m plus, yes if this quantity can be ignored compared to g_m , is there a logic? R_0 is very high, that is right, this is, this is the reason. This is normally very small compared to g_m and therefore this is approximately $r_0, 1 + \beta$, now multiplied by $r_\pi, 1 + \beta$ divided by r_E plus r_π plus r_x prime.

Unfortunately this cannot be simplified further because these 3 resistors usually are comparable, okay. And you see that the output impedance is greater than r_0 , which was expected because it is a series-series connection, all right.

Sir i hope (51:40).

You hope, you cannot do this, you cannot write it by inspection, okay. Now a student who has not gone through ee204 cannot write down by inspection the equation, the gain of that unbypassed emitter resistance amplifier either, it would not make sense to him. But if you do some 10 examples of such similar circuits, you can almost write down by inspection. You, your equations will also be mentally decent and you will see the solutions, you will see the solutions. This is the, the sign of wisdom, okay. We close here and next time we will go for calculation of f_h .