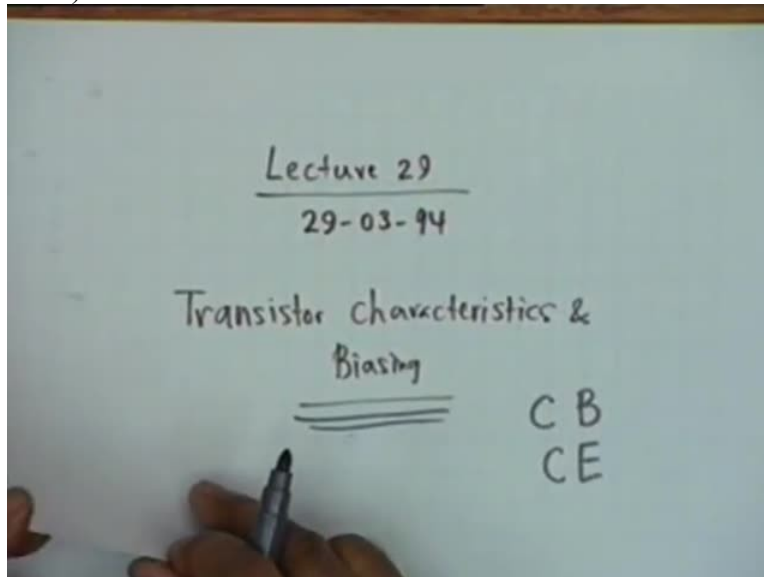


Introduction To Electronic Circuits
Professor S.C. Dutta Roy
Department of Electrical Engineering
Indian Institute of Technology Delhi
Module No 01

Lecture 29: Transistor Characteristics and Biasing


This is the 29th lecture and the topic for today is transistor characteristics and biasing. We have already seen the transistor characteristics under the common base connection.

(Refer Slide Time: 1:33)



We had also briefly discussed the common emitter connection which we would like to expand on today.

(Refer Slide Time: 1:40)

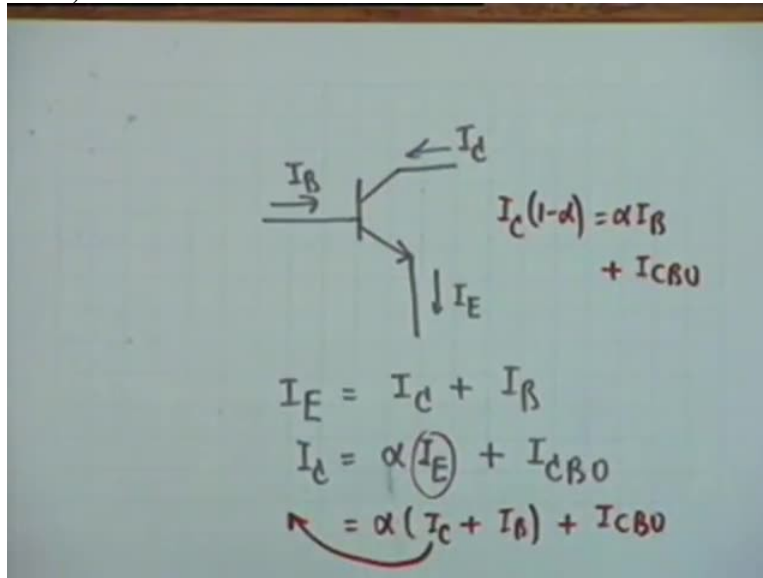

In the common emitter connection, it is the emitter terminal which is common between the input and the output. Obviously we are considering an npn transistor npn transistor and the currents are $I_{sub E}$, $I_{sub C}$ and $I_{sub B}$. Settled down quickly and quietly. These are the actual directions of currents, the base, collector and the emitter all right? The base emitter junction is forward biased and the collector base junction is reverse biased. And therefore the basic relation, one of the basic relations is that emitter current is the sum of the collector current and the base current.

And we also know that the collector current is a small is a fraction of the emitter current alpha I_E where alpha is less than 1 and in addition, because the collector junction is reverse biased, there is a reverse saturation current I_{CBO} flowing in the circuit. Now if I combine these 2 relations, these relations hold good under any connection of the transistor. What we are interested in is in showing how $I_{sub C}$, the output current varies as a function of the input current $I_{sub B}$ because this is a common emitter connection.

So what we do is we substitute for $I_{sub E}$ here from the 1st equation and therefore I get alpha $I_{sub C} + I_{sub B} + I_{CBO}$ and then take this term to the left-hand side, this term, the term containing $I_{sub C}$. And then I get $I_{sub C} 1 - \alpha$ and the left-hand side should be equal to alpha $I_{sub C} + I_{CBO}$ all right? I am interested in finding $I_{sub C}$ as a function of $I_{sub B}$.

(Refer Slide Time: 4:28)

The image shows a whiteboard with handwritten mathematical derivations. At the top left, the equation $I_C = \alpha I_E + I_{CBO}$ is written. To its right, a more detailed equation is shown: $I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$. The fractions $\frac{\alpha}{1-\alpha}$ and $\frac{1}{1-\alpha}$ are circled in red. Below the first fraction, an upward arrow points to the Greek letter β . Below the second fraction, an upward arrow points to $\beta + 1$. Below these, the equation is simplified to $I_C = \beta I_B + (\beta + 1) I_{CBO}$. At the bottom, it is noted that $\alpha = .99 \Rightarrow \beta = 99$. A blue pen is visible at the bottom right, pointing to the term I_{CBO} in the simplified equation.


And if I divide both sides by $1 - \alpha$, then the relationship that I get is I_C equals to α by $1 - \alpha$ I_B + 1 by $1 - \alpha$ I_{CBO} , the reverse saturation current. Now Jack Jack we defined last time this quantity α by $1 - \alpha$ as β , then 1 by $1 - \alpha$ can be easily shown to be equal to $\beta + 1$ and therefore I_C is equal to $\beta I_B + \beta + 1 I_{CBO}$ all right? If you ignore this term, if you ignore the I_{CBO} term, that is the reverse saturation current term, then you see that the collector current is exactly proportional to the base current and the proportionality constant is β .

This is why β is called the current amplification factor under the common emitter connection. β can be much larger than unity. For example, if α is equal to 0.99 then β is how much? 99 . β is 99 . β can be much larger than unity. The other thing is that in the reverse saturation condition, in the common base connection in the common base connection, the relationship was simply I_C equal to $\alpha I_E + I_{CBO}$. In the common base connection, the relation between input and output was simply I_C equal to $\alpha I_E + I_{CBO}$ and I_{CBO} formed a small fraction of the total current. Here you see, I_{CBO} is multiplied by a large quantity, $\beta + 1$.

And if β is 99 , then this is 100 times I_{CBO} . And therefore, the reverse saturation current contributes to a much larger fraction of the total collector current under the common emitter connection. And this current is sometimes denoted by I_{CEO} , that is it is the equivalent reverse

saturation current under the common emitter connection all right? Under the common emitter connection.

(Refer Slide Time: 7:11)

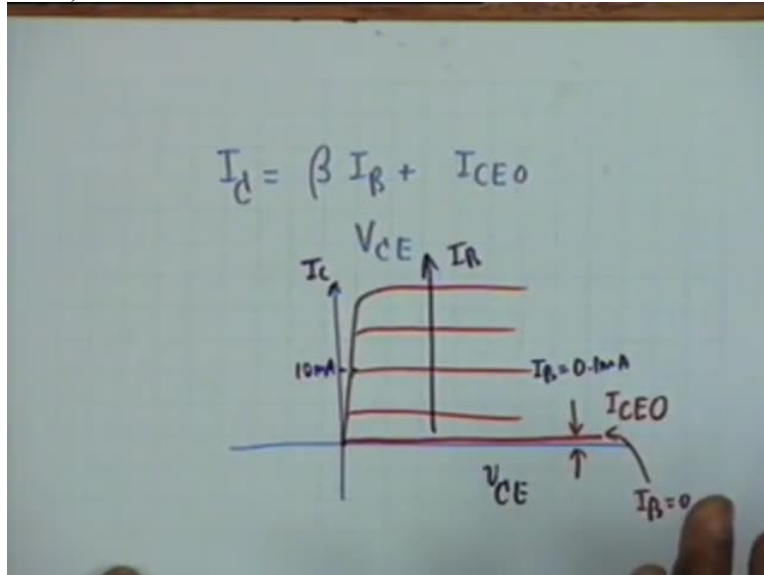


And therefore my characteristics now become I_C , the output current is $\beta I_B + I_{CEO}$ which is about which is $\beta + 1$ times I_{CEO} . Now let us look at this relationship. You notice that the input current is 0, that is base is open. Base does not contribute anything. Then I_C will consist of a small component, I_{CEO} and this is independent of V_{CE} , that is the collector to emitter voltage. It does not contain anything concerned with V_{CE} and therefore it is independent of V_{CE} . In other words, if I plot the characteristics and then β equal to 0 will give rise to a characteristic like this where this current is I_{CEO} , that is this corresponds to I_B equal to 0.

Now when I_B increases to a nonzero value, naturally the collector current increases by the amount βI_B . So equal increments of I_B shall cause equal increments of I_C . Is that clear? Equal in because I_{CEO} is a constant all right? And therefore, as we go ahead, we shall have curves like this. Each of them representing a certain value of I_B and I_B is increasing in this direction. Suppose I_B is equal to let us say 0.1 milliamperes, for a particular curve, there is a certain value of I_B all right?

And suppose this curve when extended on the left, meets this at let us say 10 milliamperere, suppose. Can you say approximately what beta is? Approximately? If you ignore I_{CEO} , then obviously the collector current, this is I_C and this is V_{CE} . It would be 10 milliamperere divided by 0.1 milliamperere. So it would be approximately 100. Now let us see some actual characteristics.

(Refer Slide Time: 9:43)

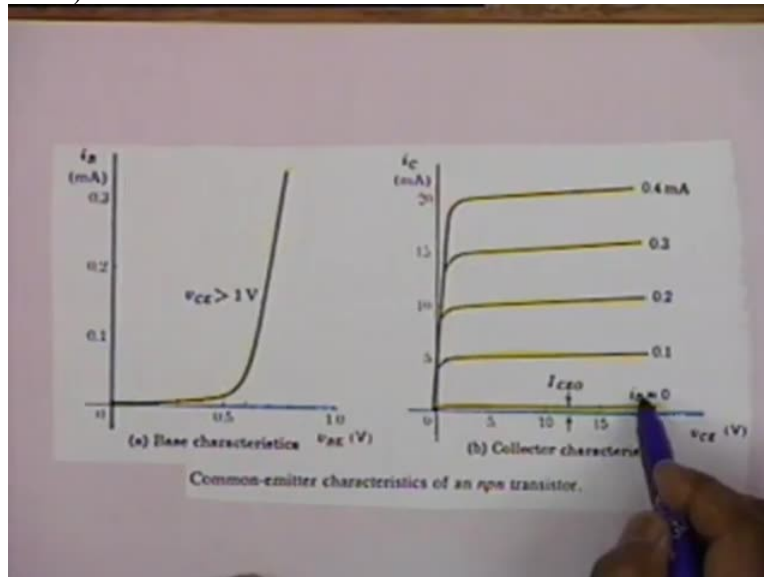


Do not try to read the read what is written here because I am going to spell it out. These are the common emitter characteristics of an npn transistor and this curve shows the input characteristics, that is I_B as a function of V_{BE} . As you know, in the common emitter connection, the base to emitter junction is forward biased. It is a diode and therefore no wonder, this characteristic is that of a diode characteristic, the base emitter junction and you can see that it is approximately a straight line which when extended to the x-axis, to the V_{BE} axis, it will cut at at a (V_0) voltage of about 0.7. This is 0.5, 0.6, 0.7 and this is why we take the input junction, the base emitter junction as equivalent to an ideal diode in series with 0.7 volt if it is silicon all right?

Now the output characteristic, that is the collector current I_C vs V_{CE} as I said when I_B is 0, no base current, all you have is I_{CEO} all right? When I_B increases to let us say 0.1 milliamperere, well the curve goes like this and you see, it cuts, if you extend this it cuts at about 5 milliamperere and therefore this is a transistor with a beta of 50, 5 by 0.1. Similarly when the when the base current goes to 0.2 milliamperere, well it cuts the axis at about 10 which which corroborates the

fact that beta is approximately equal to 50. An equal increments of base current should cause equal increments of collector current and this is approximately true in practice also. This is what the collector characteristics look like and this is the input characteristic.


(Refer Slide Time: 11:49)

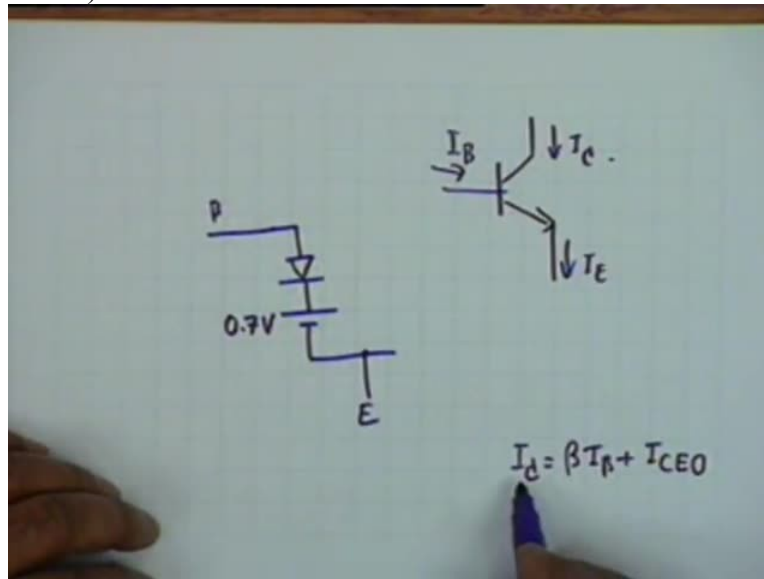

And as I said as I said, we approximate the DC operation of the common emitter transistor. DC operation in which there is a current I_B , there is a current I_E and there is a current $I_{sub C}$. Well, the input junction, base emitter junction is a forward biased diode and if this is silicon, then we approximate this by means of an ideal diode in series with 0.7 volt DC voltage and this leads us to the emitter. If you are fussy, if you wish to incorporate the slope of this line, then you should add a small resistance.


You should add a small resistance here which for the present, we ignore and as far as the output is concerned, well the output is simply $\beta I_B + I_{CEO}$ which is $\beta + 1 I_{BO}$ and this is independent of V_{CE} .

(Refer Slide Time: 12:58)

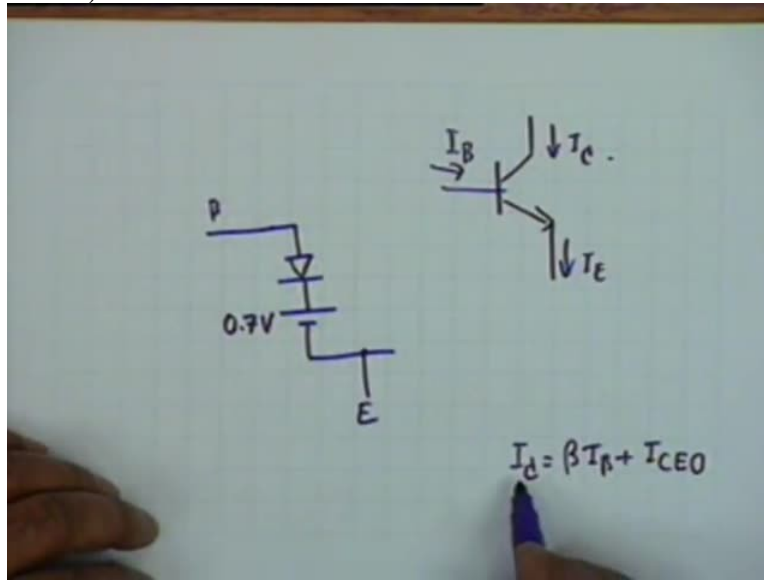


As you can see here also. It is independent of each, it is almost parallel to the VCE axis except for this region except for this region where VCE is so small that the collector base junction can no longer be reverse biased. It becomes forward biased and this region where the current increases with VCE is a very small region very small region and is called the saturation region. We shall come back to this later. As far as amplification is concerned, we are concerned with the part of the characteristic where equal increments of I_B lead to equal increments of I_C . This is the region which we are interested in for amplification.

(Refer Slide Time: 13:51)

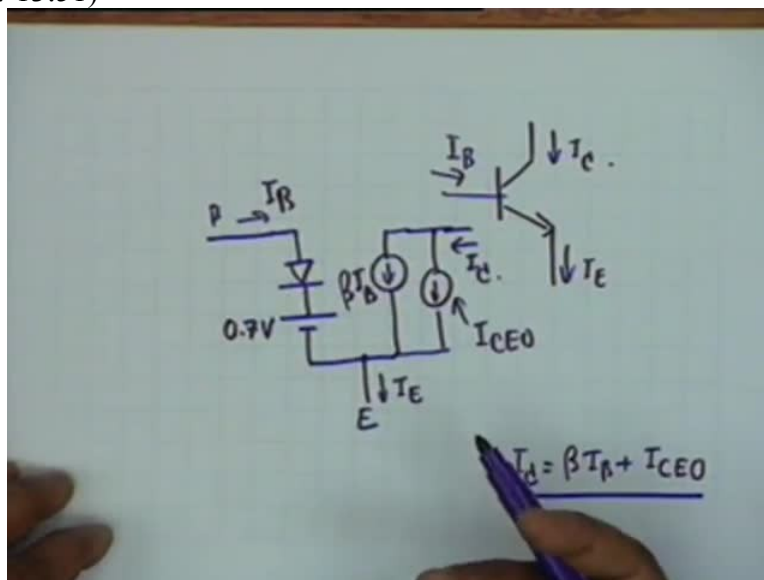

Now this characteristic $I_{sub C}$ equal to $\beta I_B + I_{CEO}$ can be represented by simply 2 current generators. One of them, well this current is I_B , the input current is I_B and this current is $I_{sub E}$ and the 2 current generators, one would be βI_B and the other would be I_{CEO} . This is the simple DC model of the (tra) common emitter transistor. And in any circuit analysis, well you can utilise this equivalent model. Then life becomes very simple. Utilising this model, one can now analyse to see why a transistor behaves like it does. Why does it amplify?

(Refer Slide Time: 14:50)

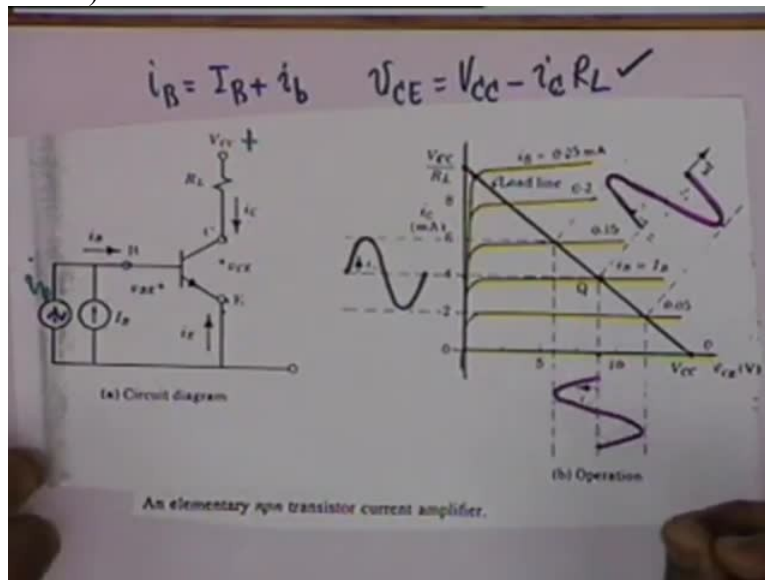

Well, you see here is a transistor, a common emitter transistor which is connected to a positive supply here, V_{CC} . It has to be connected to a positive supply because the collector base junction has to be reverse biased. This is an npn transistor, this is n, this is p and this is n. So n must be connected to positive supply to make it reverse biased. Then, it is connected to the collector through a resistance which is called the load resistance R_L . This is the transistor. For simplicity, E is shown connected directly to the output to the common terminal Jack and to the base are connected sources, 2 current sources.

One is a DC current source, I_B capital I sub capital B, a DC current source and this is an AC current source or a signal source small i_b and therefore the total current, total current $I_{sub C}$ total current shall be the sum of the 2. That is $I_{sub C} = I_B + i_b$. small i_b , this is a varying current, this is the signal current whereas this is a steady current, I_B established by some battery and some resistances as we will see later. Now if

you look at the characteristics, we have plotted the same characteristics against. In addition, this red line here simply specifies the fact that V_{CE} , the collector to emitter voltage must be the supply - the drop in R_L .

That means V_{CE} is equal to $V_{CC} - I_C \times R_L$ which is the equation to a straight line. All right? These characteristics are non-linear characteristics and therefore what we do this, we have to satisfy V_{CE} and I_C should satisfy this relation and also the characteristic curves. And therefore, we draw this straight line on the characteristic curve. How do you draw it? You put I_C equal to 0, then V_{CE} is equal to V_{CC} . That means the straight line starts from this point where this point is V_{CC} and then we put V_{CE} equal to 0.

Under that condition, I_C should be V_{CC} / R_L . So it must pass through this point which is V_{CC} / R_L and you know a straight line can be specified by 2 points. So you join them and that becomes your load line. It is a straight line dictated by the load. It is a straight line dictated by the load. Also of course, the supply voltage V_{CC} all right? Now to find out where the transistor operates, that is what would be the value of V_{CC} and I_C . It must satisfy two equations, one is a non-linear equation specified by the characteristic curve, the other is a linear equation specified by this line and therefore the intersection of these 2 shall determine, the operating point of the transistor or the so-called Q point of the transistor.

And if I specify if I figure out from here, from the characteristic curve, which one is the curve for the specified value of I_B ? Now ignore small i_B . Small i_B is a small variation or perturbation over the steady value of I_B . I identified that this is the curve on which which corresponds to the given value of I_B . Then I find out where does it intersect. This is the point and this is my Q point or left to itself, if there is no signal current, the transistor will set at this point. Set at this point means its V_{CE} will be equal to this and the collector current would be equal to this.

This is about oh I do not know, 7.5. This is about 8 and this is about 4 milliamperes. So 8 volt and 4 milliampere. That is where it the transistor will set. Now suppose on this base current, on this steady base current is superimposed a small AC base current, small i_b which for simplicity, let us assume that it is sinusoidal with a peak value of 0.05 milliampere, that is this point Q corresponds to point 0.1 milliampere and when the base current is maximum, it

becomes 0.15 milliamperes. So the Q point shifts to this point because this curve is for 0.15 milliamperes and this curve is for 0.05 milliamperes.

Equal changes in I_B leads to equal changes in I_C . This is the part that we are interested in. So when the base current fluctuates like this, when it goes to one complete cycle, what happens the collector current? At the peak of the base current, the collector current reaches the value 6 milliamperes. At the trough or the or the minimum of the base current which corresponds to 0.05, the collector current is 2 milliamperes and therefore therefore as the base current varies varies from 0.1 to 0.15, comes back to 0.1, goes back to 0.05 and then again comes back to 0.1, 1 cycle of the base current is completed, the collector current goes through a very similar variation.

When the base current increases, collector current increases. And if these lines are equi-spaced, that is equal base current increments lead to equal collector current increments, then obviously this curve shall also be sinusoidal all right? So a small base current here is able to control a large collector current here. If the peak to peak current here this 0.05 milliamperes, and the peak. I am sorry, not peak to peak. Peak to peak is how much? 0.1. And peak to peak here is from 2 to 6, 4 okay.

So when the when the base current goes through a peak to peak variation of 0.1 milliamperes, the collector current goes through a peak to peak variation of 4 milliamperes and therefore the collector current amplification factor is 40 all right? A small current at the base can produce large current variation in the collector. So there is current amplification by the transistor. In addition if you look at the phases, when the base current increases, the collector current also increases. So they are in phase. All right?


On the other hand, if you look at this voltage from collector to emitter, VCE, when the collector current increases, VCE decreases. And therefore, the VCE variation shall be out of phase with the input current variation. Is that clear? It is also shown here that when the base current increases, the collector to emitter voltage decreases. All right? When the base current decreases, the collector to emitter voltage increases. So there is a variation, corresponding variation in VCE but in opposite phase. And you see, the voltage now goes from 5 to 15, that is there is a 10 volt peak to peak variation. All right?

And this 10 volt peak to peak variation is a large amplitude variation caused by a very small current variation at the base. And therefore, there shall be a voltage amplification also. We would be able to say how much voltage variation if we knew the equivalent resistance between base and emitter. Well, we shall calculate this later but qualitatively, is the picture clear to you that the common emitter transistor can amplify current as well as voltage?

This amplification, the faithfulness of this amplification depends on where your Q point is. That is in absence of the signal, where does the transistor reside? For example, if your Q point is here if your Q point is here, that is the quiescent collector current is 0, then the transistor will conduct only when $I_{B\text{ small}}$ is positive. Is not it right? In other words, the transistor will now behave like a rectifier. That is, it will only produce the positive halves. All right? The transistor is sometimes operated under this condition and this condition is known as class B operation, class B all right?

If the transistor is biased here, let the if the Q point is here then obviously, the positive halves there shall be problems in amplification. The negative halves shall have less problem in amplification. In other words, the output waveform that you shall get shall no longer remain sinusoidal. It shall be distorted all right? And therefore, for faithful amplification where the base current variation shall lead to an exact replica but an amplified or magnified replica in the collector current, you require that part of the characteristics where the lines are equi-spaced, that is equal increments of base current lead to equal increments of collector current. Jack. This is the basic idea of amplification, how a transistor can be used as an amplifier.

(Refer Slide Time: 25:41)

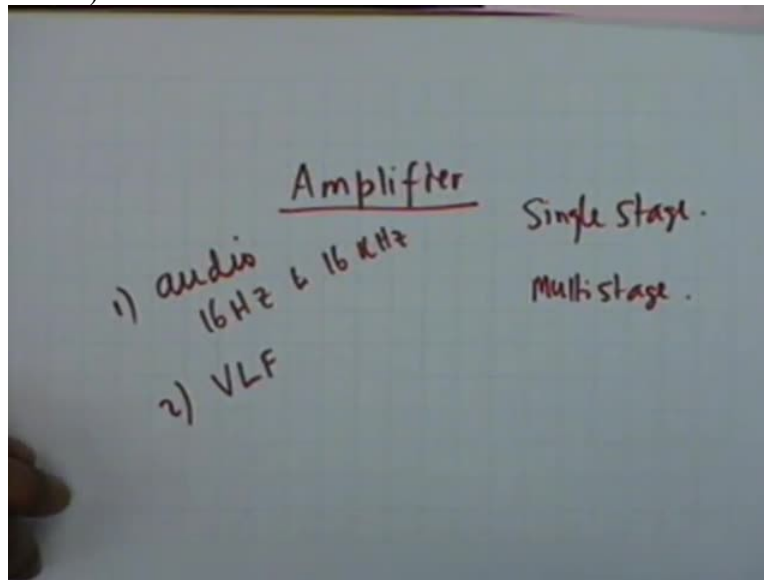

Before we take up this topic again in an actual circuit and see how the Q point is determined, let us clarify a couple of concepts, couple of terminologies that are used in connection with an amplifier. Amplifiers can be single stage or multistage. That is, if we use one transistor and around it, you introduce resistors, power supply to get some amplification, one stage, that is one device, is called a single stage amplifier. Now single stage amplifier obviously shall have limitation on the gain. How much amplification? How much amplification?


So if you want more amplification or more gain, you might use 2 such stages. Such amplifiers are called multistage amplifiers and it should be clear in the context, whether an amplifier, a given amplifier is a single stage or a multistage. For example, a stereo amplifier is usually a 3 stage amplifier, is a multistage amplifier. The 1st stage is a voltage amplifier matching microphone to the amplifier system, 2nd stage is another voltage amplifier and the last stage is a power amplifier because you have to feed power to a loud speaker.

Amplifiers can be single stage or multistage. Depending on the frequency range of operation, amplifiers can be classified as audio amplifiers, that is amplifiers which are useful in the audio range of frequencies which is 16 hertz to 16 kilo hertz. 16 hertz to 16 kilo hertz you can have for example, VLF amplifiers, very low frequency amplifiers like those used in biomedical applications where frequencies encountered are of the order of a fraction of a hertz or in

process control, a sulphuric acid plant where the variations are very slow, very low frequency amplifiers.


Or you can have let us say video amplifiers where the frequency range may vary from 30 hertz to about 4 megahertz or higher okay? Video amplifier and so on. You can so you can classify amplifiers on the basis of number of stages, on the basis of their frequency range, then on the basis of the bandwidth.

(Refer Slide Time: 28:22)

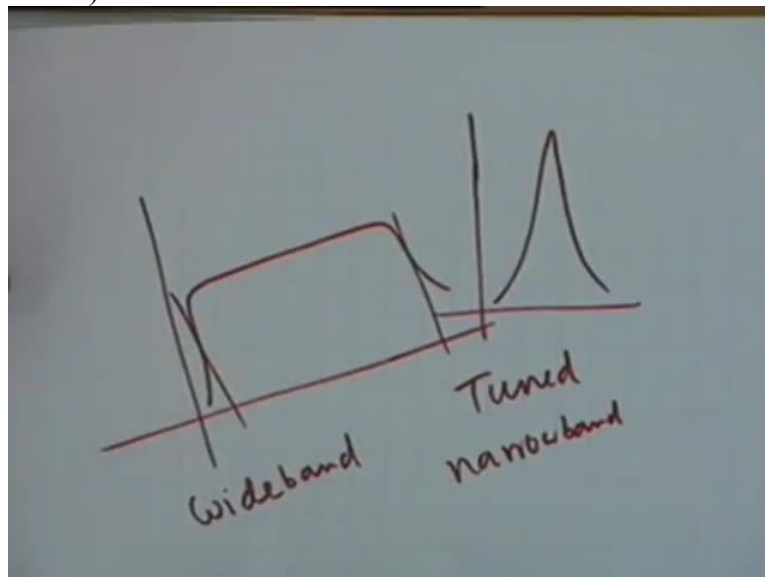

You might require an amplifier Jack as you do in the case of a radio receiver or a TV receiver so that only a narrow band of frequencies are required around a centre frequency. Well, then it is called, such an amplifier is called a tuned amplifier. On the other hand, you can have, tuned amplifier has a narrow band okay, tuned or narrowband. On the other hand if you want an audio amplifier, well obviously what you need is something like this where the 3 dB frequencies are 16 hertz and 16 kilo hertz and therefore, this is a wideband amplifier okay. These are some of the terminologies that we shall be using in future. Single stage, multistage, audio, video, VLF and narrowband or wideband amplifiers. How do you characterise amplifiers?


(Refer Slide Time: 29:26)

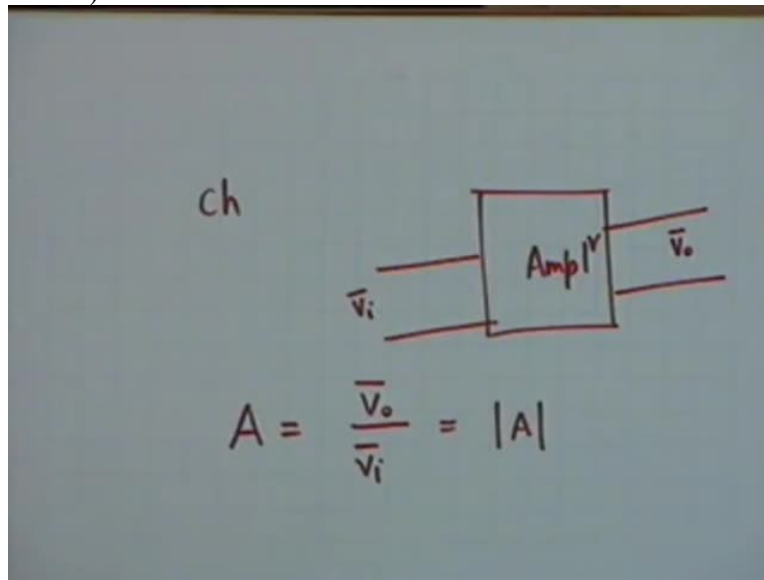

Now we consider an amplifier as a black box. There are input terminals, there are output terminals and mostly amplifiers are characterised by sinusoidal inputs and therefore one can work in terms of phasors. Let us say that the input phasor is \bar{V}_i and the output phasor is \bar{V}_o all right? Then the gain or amplification of the amplifier is denoted by A the ratio of the output phasor to the input phasor. Obviously, this would be a complex quantity. This would be a complex quantity, there would be a magnitude which is the ratio of the 2 magnitudes of the voltages and there would be a phase, $e^{j\theta}$ all right?

If the gain if the (amplitude) if the amplification is dependent on the size of the signal all right, then obviously then obviously equal increments of the input current may not lead to equal increments of the output current. If that happens, then you have good amplification.

(Refer Slide Time: 31:04)

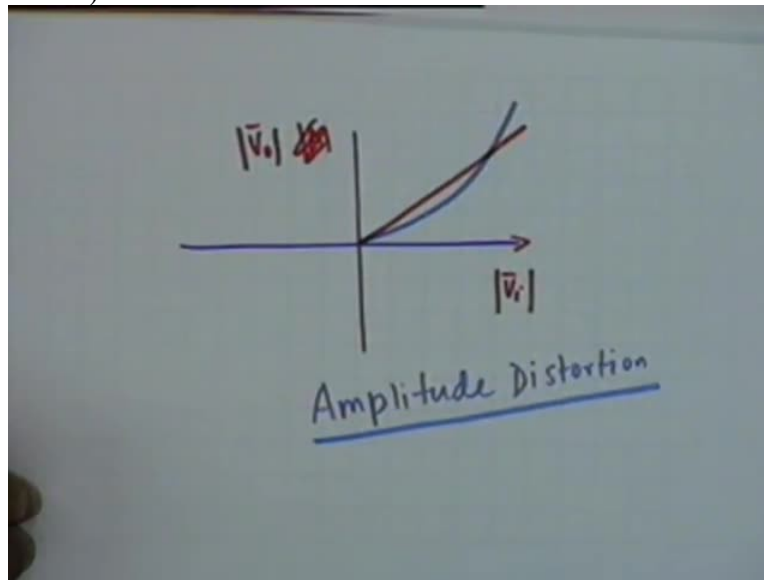


But suppose you have an amplifier suppose you have an amplifier whose characteristic, ideal characteristic would be like this okay. The gain vs signal strength, let us say V_o vs V_i , it should be a straight line all right with a slope of magnitude of A all right. Now suppose the characteristic is like this. Instead of a straight line, suppose the characteristic is like this. Then obviously obviously a sinusoidal signal shall not give you a sinusoidal output. Is that clear? The output shall be distorted. Agreed? Such distortion is called amplitude distortion amplitude distortion.

Is that clear? The characteristic that I want is that the output voltage should be linearly proportional to the input voltage. If this is not so, then a sinusoidal signal shall not give rise to a sinusoidal. It should give rise to a distorted sinusoid and under this condition, we say the (ampli) amplifier produces amplitude distortion which is very commonly the case with public address system, particularly those used for large rallies and so on. The voice is not detectable. In fact, if we put music on such a public address system, it is massacre.

For musical reproduction, we require a very very good linearity of amplification. On the other hand, the speech, most of it is not paid attention to, so somebody speaks, that is about it. And there is a large crowd okay. We will make TV news, the actual content of the speech is not important and therefore lot of amplitude distortion is tolerated in a public address system. It cannot be tolerated in music.

(Refer Slide Time: 33:20)

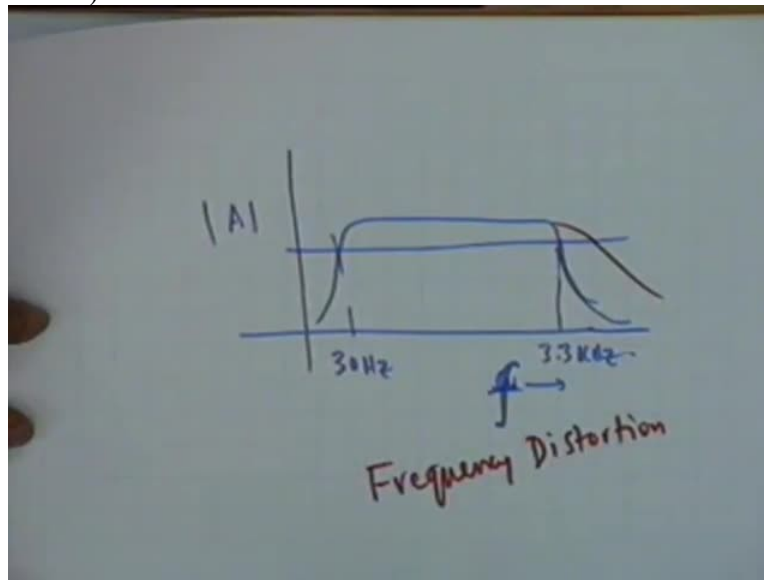


On the other hand, if you have an amplifier whose gain is sensitive to frequency, as I have said, for an audio stage, it is like this okay. Now suppose suppose the 3 dB points are 30 hertz to let us say 3.3 kilo hertz as is used in reproduction of speech signals then obviously if it is the full band audio, then such an amplifier cannot take, this is frequency in hertz. Such an amplifier cannot reproduce the full audio, that is beyond 3.3 up to about 16 kilo hertz, the gain has come down. Obviously this is also going to produce distortion all right.

This is like this is like decreasing the treble. In a stereo set, you have two controls, one is the bass control, the other is a treble control. Bass control means you either increase or decrease the low-frequency 3 dB point. If you increase the bass, the drums will come better, the tabla sound for example. On the other hand, if you increase the treble if you increase the treble, this means that you are increasing the high-frequency 3 dB point. That means, you are admitting more high-frequency and therefore a violin sound sweeter if the treble control is increased all right.

The point that I am making is that if the signal consists of certain band of frequencies and the amplifier cannot accommodate total band, it accommodates only a part of it, obviously there shall be distortion all right. For example, if you cut off the high frequency, Lata mangeshkar will not sound like Lata mangeshkar. She will sound like, I do not know. Give her (35:16) baser voice (35:17), would that be all right? Okay, so this distortion is called frequency distortion.

We have discussed 2 kinds of distortion. One is amplitude distortion and the other is frequency distortion.

(Refer Slide Time: 35:40)

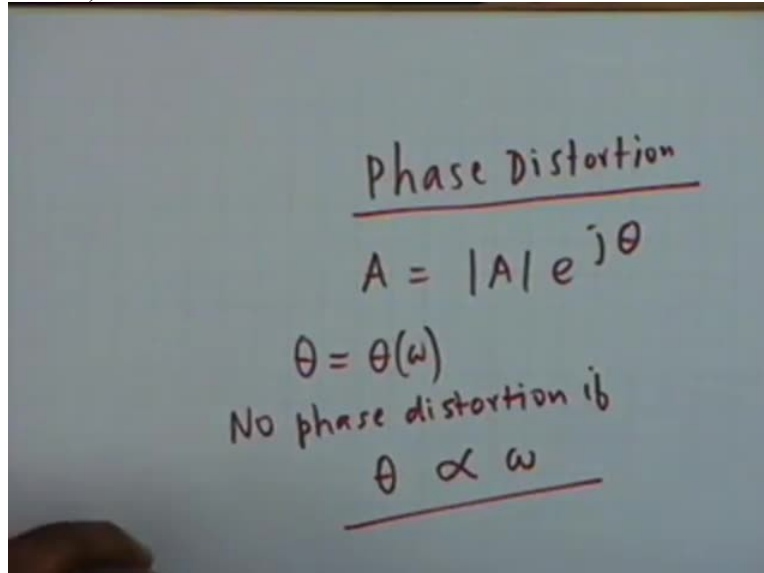


There is still a 3rd kind of distortion that one has to bother about and this is the so-called phase distortion. I shall simply state this without proof that phase distortion has to do with the angle theta. Theta usually is a function of omega. If theta is a function of omega then no phase distortion shall occur. No phase distortion shall occur if theta is a linear function of omega, if theta is proportional to omega. All right. If theta is proportional to omega, no phase distortion shall occur.

Now let me mention to you a particular situation where the situations where phase distortion is important. Phase distortion, fortunately or unfortunately cannot be detected by the ear. That is, our hearing capability is insensitive to phase distortion. Even if the phase is non-linear, it does not matter but phase distortion, our vision is very sensitive to phase distortion. So in a TV for example, the picture cannot have the phase distortion. If it does a phase distortion, you will see all kinds of distortion, will not see the correct picture.

On the other hand if it is the audio, the sound, we do not care what the phase distortion is all right. Beside this general rule, you need not know much more about phase distortion at this point of time.


(Refer Slide Time: 37:26)

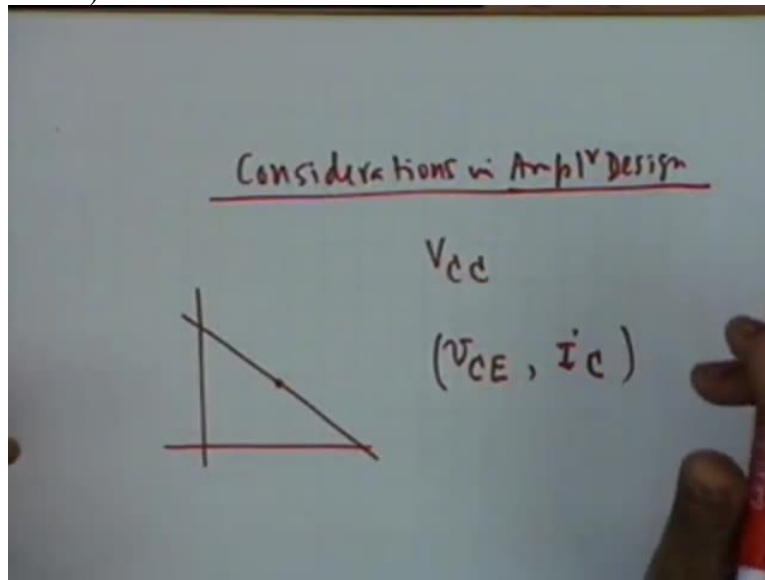

Then what are the considerations in amplifier design? Considerations in amplifier design Jack. As I have shown you with the help of the common emitter characteristics, obviously the Q point of the transistor is important. If the Q point is at a round point then you might get a lot of distortion in the amplification. And therefore, the transistor must be biased properly. That is, your choice of VCC and the resistors used to bias the transistor to a particular VCE and a particular I_{c} , these are the 2 points that determine the Q point of the transistor.

You remember, there was a load line and the Q point was somewhere in the middle. To establish this Q point at an appropriate point in the characteristic is an extremely important task. So the 1st consideration in amplifier design is its biasing. Then there are other considerations like if you want to if you want a multistage amplifier, if you want to couple one stage to the a to the other, well then coupling is important, how do you couple?


(Refer Slide Time: 38:46)

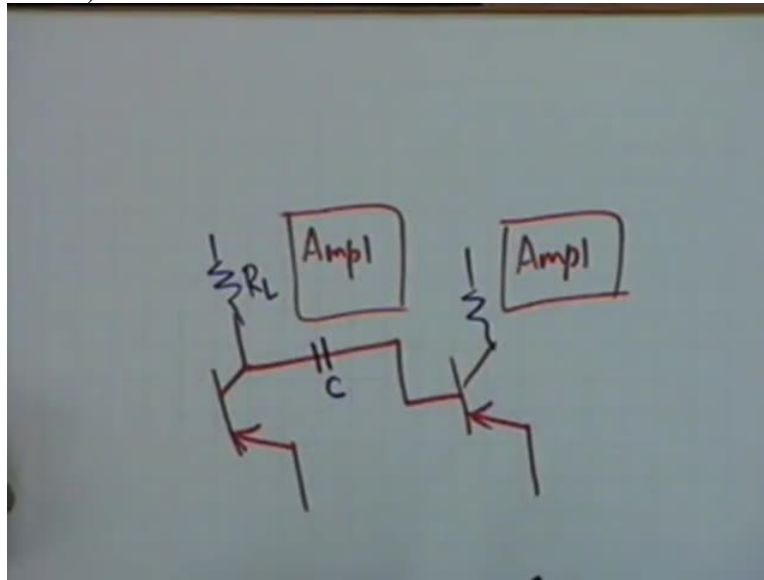

For example, you have one amplifier stage and another amplifier stage here. How do you couple? Suppose you take, you connect the collector of one stage directly to the base of the next stage. Can you connect it directly? Well, the problem is that this would be at a high voltage VCE. If you connect this to the base, then the base, base does not require that high voltage and therefore DC coupling may introduce distortion. And what you have to do is to introduce a C here, a capacitor so that DC is blocked but AC is passed.

And there is a load here, R_L . There is a load here. For every transistor, there is a load and therefore this coupling is called RC coupling, resistance capacitance coupling all right. On the other hand there can be other kinds of coupling. For example, if the capacitor is not there, then we call it direct coupling. It is not that direct coupling is not used. It is also used in some places. So direct coupling can be used, RC coupling can be used. One can also use transformer coupling as is done for example at the last stage of a stereo amplifier.


(Refer Slide Time: 40:14)

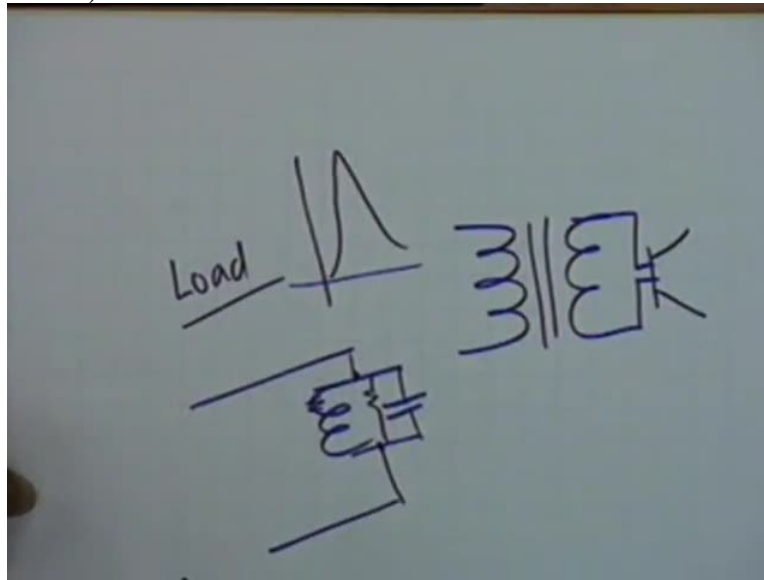

At the last stage of stereo amplifier, the transistor feeds a transformer primary, the secondary of which is connected to the loudspeaker. Okay. This is called transformer coupling. So coupling is an important consideration in amplifier design. Then the load, nature of the load, obviously the load. load can be resistive, can be inductive, can be capacitive, all kinds of loads. For example, a loudspeaker is usually considered a resistive load. On the other hand, a radio-frequency stage may have a load like this.

You may have a load like a parallel tuned circuit, parallel resonant circuit. What is the impedance at resonance? Infinity. What is the impedance at resonance of this circuit? Infinity. And therefore, just you will see later that the gain of such an amplifier is proportional to the load. And therefore, you expect infinite gain from this. Actually, you do not get infinite gain because the inductance has resistance, the capacitor has a resistance in parallel and therefore, you can get a large gain all right? And that is how you get a characteristic like this. A tuned characteristic. So the nature of the load whether it is resistive, inductive, capacitive or tuned, it is important.


(Refer Slide Time: 41:50)

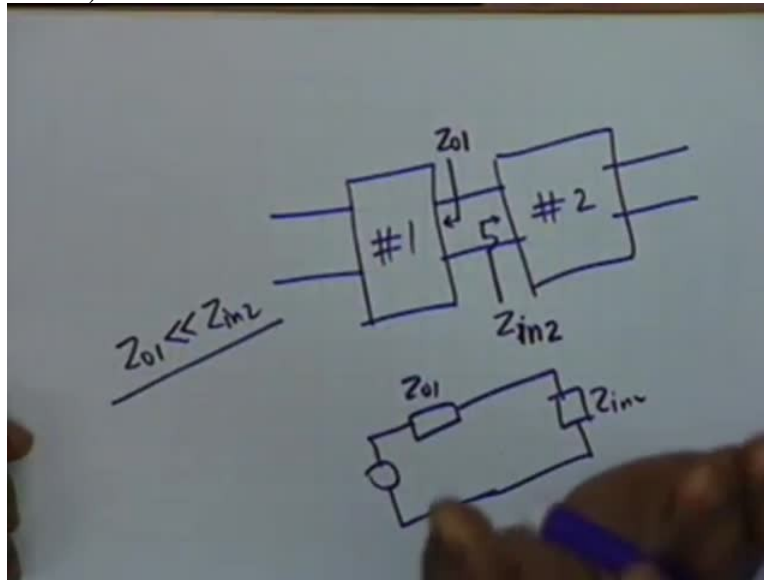

It is also important to consider, when you are connecting one amplifier stage to another, suppose this is stage 1 and this is stage 2, it is important to consider what is the input impedance of this stage Z_{in} and what is the output impedance of this stage Z_{01} and Z_{in2} . It is important to consider the relative proportion of these 2 all right. Suppose Z_{01} is very large and Z_{in2} is very small all right. Then then only a small fraction of the 1st stage output shall be coupled to the 2nd. Is not it right? Because the Thevenin equivalence says that you have Z_{01} , a voltage source, then you are connecting to Z_{in2} .

If Z_{in2} is very small compared to Z_{01} then obviously very little voltage shall go to the 2nd stage. So what is the consideration then? Z_{01} must be very small compared to the input impedance of the stage that it couples to, Z_{in2} all right. This consideration is extremely important. On the other hand, there are situations where you when you are not interested in transferring voltage. You are interested in transferring power. Well, what do you do there? You make impedance matching. That is, if you are interested in transferring maximum power from this stage to this, then Z_{01} and Z_{in2} should be complex conjugates of each other and therefore it is important what your application is.

(Refer Slide Time: 43:51)

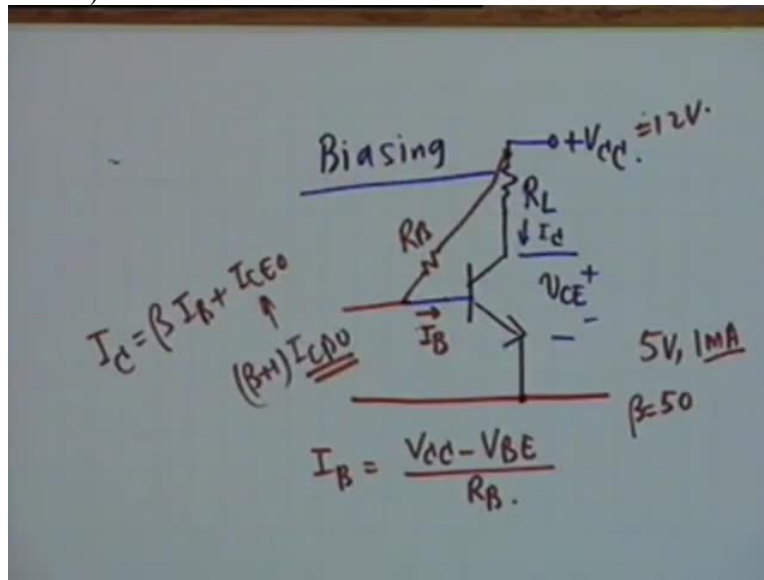

You have a a transistor, you have a load all right and you have a + VCC. You have a load R_L , you wish to establish a particular V_{CE} and a particular I_C . So the condition the condition will be satisfied if you can find out the appropriate base current and establish the corresponding base current. And one of the ways that this can be done with a single battery is that the same battery is connected to the base through a resistance let us say R_B all right. Then this will be the base current, the DC base current, I_B . Okay.

This is the circuit. This is one of the simplest circuits for establishing for biasing the transistor. Obviously, I_B the base current here shall be equal to the drop in R_B . What is the drop in R_B ? This is V_{CC} - the drop between base and emitter. And if you recall the DC equivalent circuit, this is 0.7 and therefore this will be $V_{CC} - V_{BE}$ which is 0.7 divided by R_B all right? And the job seems to be seems to have been done. This will be I_B . Beta times $I_B + I_{CE0}$ shall be I_C . I_C will be beta times $I_B + I_{CE0}$ which normally which normally is negligible.


And therefore if you know the beta of the transformer, you know what is I_C all right and if you know I_C , then you can determine R_L to find out a specific value of V_{CE} . For example, if V_{CE} is equal to be 5 volt and I_C is equal to be 1 milliampere with a beta of 50 beta of 50 then you know what your I_B required is. I_B will be 50 I am sorry 1 milliampere divided by 50, 0.02 milliampere and if V_{CE} is 12 volt, then $12 - 0.7$ divided by the resistance, that will

determine I_B . So you know R_B all right and then since you know collector current, 1 milliampere, you want 5 volts here, so 7 volts should be dropped here.

They are very simple calculations and therefore you know R_L . The disadvantage of this is that if this transistor goes bad and you replace it by another transistor of the same type, then the Q point will go haywire. The reason is the following that in mass production of transistors even though they are produced by the same process, about 1000 is perhaps the minimum number that is that is produced or fabricated in one go, these transistors vary very widely. In other words, beta can vary by a ratio of approximately 6 is to 1. You can have a lot of transistors 2N110, one thousand of them and you go on measuring beta, the lower is better maybe as low as 30, the highest maybe as low as 180, 6 is to 1 variation.

And therefore as soon as you replace the transistor, the Q point changes. Similarly, this as you see I_{CEO} is $\beta + 1 I_{CBO}$. And as soon as temperature changes, I_{CBO} as you know doubles for every 10 degrees centigrade rise in temperature. The law of variation of I_{CBO} approximately is that it doubles for every 10 degrees centigrade rise of temperature and therefore if temperature changes, then I_{CBO} rises, this quantity changes and therefore once again the Q point goes bad. Not only that, the most drastic disadvantage of this circuit is funeral to have to follow me carefully.

(Refer Slide Time: 48:27)

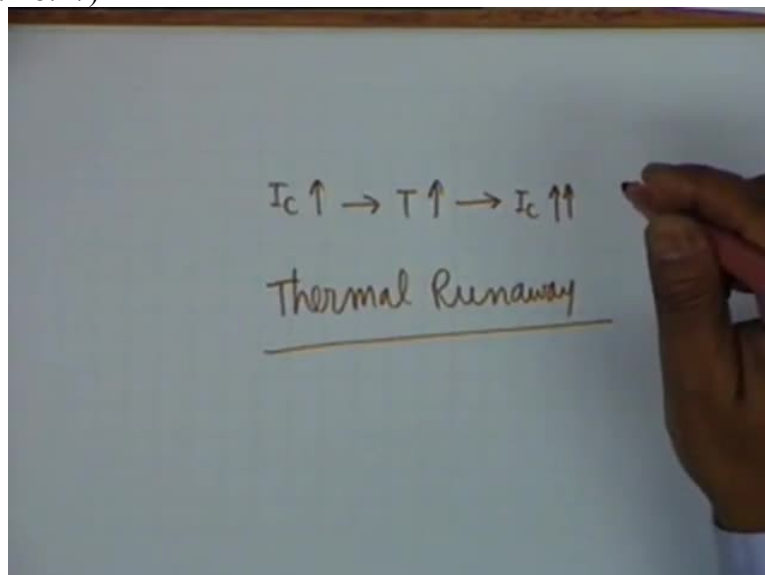


Suppose due to a small change of temperature, in this circuit, I_{C} increases. Suppose due to a small change of temperature, I_{C} increases, this collector current increases. Now what happens? If collector current increases, naturally the the heat dissipation in the transistor also increases. That is V_{CE} times I_{C} increases all right. Now this heat is generated here and is to be dissipated in the transistor and therefore it causes a further rise of temperature all right. If I_{C} increases, temperature increases.

If temperature increases, I_{C} further increases all right. And this can now be a merry-go-round situation and ultimately the transistor will be burnt. This process is called a thermal runaway. This process of burning a transistor should never be resorted to but it does happen in practice and the process is known as thermal runaway. It should be avoided. And this is one of the main disadvantages of this particular circuit. A circuit in which this does not happen has to be designed on the basis of a different kind of philosophy. The philosophy in this circuit was to establish a particular I_{B} , to establish a particular base current.

The base current is a constant. The collector current is not a constant. All right? Because it varies with beta, it varies with I_{CEO} . If I change the philosophy of maintaining a constant I_{C} , base current let it adjust to get a particular value of I_{C} , then this process of thermal runaway shall be arrested.

(Refer Slide Time: 50:38)

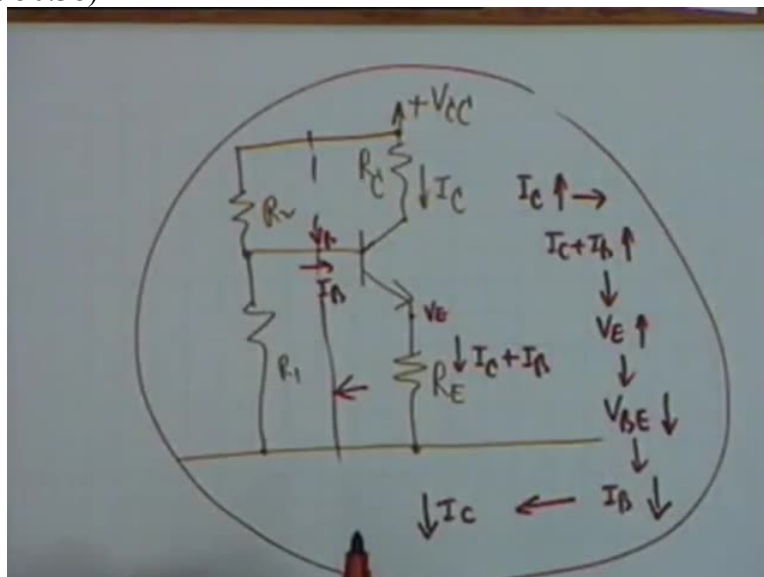

And this is done by a circuit which is known as a self biased circuit. It is a very simple circuit. You have 2 resistors here. This is + VCC, this is I_{CQ} , call this R_C and call this R_E . In the emitter also, there is a resistance and the base is biased not through one resistance but through 2 resistances, that is R_1 and R_2 . If you look at if you look at this circuit from the left of this line, obviously it is a battery VCC supplying a series connection R_2 and R_1 . The drop in R_1 then supplies the base. The base voltage V_{BG} ground, you call this simply V_B is simply the drop at drop across R_1 which is equal to $V_{BE} +$ the drop across R_E .

Now let us see what happens. Suppose I_{CQ} due to some reason increases, what is the current through this? What is the current through R_E ? $I_C + I_B$. This is the current I_B . Now see what happens qualitatively. We shall analyse this quantitatively later. If I_{CQ} increases, then $I_C + I_B$ also increases. If that increases, then what does it have what happens? The drop across R_E , you call this V_E . V_E increases. If V_E increases, then what happens to V_{BE} ? Decreases. Is not it right?

V_{BE} , this drop shall then decrease. If V_{BE} decreases, what happens? I_B . If the diode voltage decreases, I_B decreases and I_C is nothing but $\beta I_B + I_{CEO}$. So if I_B decreases, then what happens to I_C ? I_C decreases. You see, the increasing tendency of I_C is arrested. In other words, there is a feedback mechanism which tends to keep I_C stable and in such a connection, the transistor can never burn down. Thermal runaway is arrested and this is one of the most popular biasing circuits. Next time, we shall make a thorough analysis of this and see the stability of the biasing.