

**Microwave Engineering**  
**Professor Ratnajit Bhattacharjee**  
**Department of Electronics & Electrical Engineering**  
**Indian Institute of Technology Guwahati**  
**Lecture 15**  
**Transmission Line Resonators**

Let us now consider Transmission Line Resonators where we will consider a section of a transmission line, either open or short and we will see that when the length of these sections of transmission lines are chosen appropriately there will exhibit resonance and near the resonant frequency we can model this transmission line resonators either in the form of a series RLC circuit or in the form of an equivalent parallel RLC circuit.

(Refer Slide Time: 01:33)

The transmission line has characteristic impedance  $Z_0$

At  $\omega = \omega_0$        $l = \lambda/2$

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$$

### Transmission Line Resonators


Transmission line sections of various lengths and terminations (open or short) can be used as a resonator.

Let us consider a lossy transmission line of length  $l$  terminated to a short circuit at one end. The transmission line is low loss with very small value of attenuation constant  $\alpha$

The transmission line has characteristic impedance  $Z_0$

At  $\omega = \omega_0$        $l = \lambda/2$
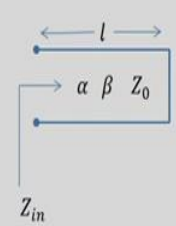
$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$$



So, transmission lines sections of various lengths and terminations open or short can be used as a resonator. Now, let us consider a lossy transmission line of length  $l$  and let us assume that it is terminated to a short circuit at one end. We will also consider the transmission line to be of low loss with very small value of attenuation constant  $\alpha$ . Now, this is shown in the figure we have a transmission line section of length  $l$  and  $\alpha$  is the attenuation constant,  $Z_0$  is the characteristic impedance, and  $\beta$  is the propagation constant.

We are assuming this transmission line to be of low loss type so that  $\alpha$  is very, very small. Now, suppose we choose the line length  $l$  in such a way that at  $\omega = \omega_0$ ,  $l$  is equal to  $\lambda/2$ . So, we are essentially considering a half wavelength short-circuited section of a transmission line. Please note that this half-wavelength will be only at a particular frequency.

If we change the frequency of operation, the physical length of the transmission line will remain the same and it will be depending upon whether the frequency is higher or lower the line length will be longer than  $\lambda/2$  or it will be shorter than  $\lambda/2$ . So, the line length  $l$  is  $\lambda/2$  at  $\omega = \omega_0$ . Now, for such lossy lines we can write  $Z_{in}$  to be equal to  $Z_L + Z_0 \tanh \gamma l$  divided by  $Z_0 + Z_L \tanh \gamma l$ . Now, in our case this  $Z_L$  is 0 we have only these terms left because this becomes 0, this becomes 0 and these two  $Z$  zeros cancel out.

(Refer Slide Time: 04:43)

$$\text{For } Z_L = 0 \quad Z_{in} = Z_0 \tanh \gamma l = Z_0 \tanh(\alpha + j\beta)l$$

$$\text{Therefore, } Z_{in} = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$$

Since we have considered a low loss line,  $\alpha l \ll 1$

$$\tanh \alpha l \cong \alpha l$$

$$\beta l = \frac{\omega l}{v_p} = \frac{\omega_0 l}{v_p} + \frac{\Delta \omega l}{v_p}$$

$$\text{Since } l = \frac{\lambda}{2} \text{ at } \omega = \omega_0, \quad \frac{\omega_0 l}{v_p} = \frac{2\pi f_0 \lambda}{\lambda f_0} \frac{1}{2} = \pi$$

## Transmission Line Resonators

$$\text{For } Z_L = 0 \quad Z_{in} = Z_0 \tanh \gamma l = Z_0 \tanh(\alpha + j\beta)l$$

$$\text{Therefore, } Z_{in} = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$$

Since we have considered a low loss line,  $\alpha l \ll 1$

$$\tanh \alpha l \approx \alpha l$$

$$\beta l = \frac{\omega l}{v_p} = \frac{\omega_0 l}{v_p} + \frac{\Delta \omega l}{v_p}$$

$$\text{Since } l = \frac{\lambda}{2} \text{ at } \omega = \omega_0, \quad \frac{\omega_0 l}{v_p} = \frac{2\pi f_0 \lambda}{\lambda f_0 2} = \pi$$

And therefore when  $Z_L$  equal to 0  $Z_{in}$  is  $Z_0 \tanh \gamma l$ . Now, we can substitute  $\gamma$  as  $\alpha + j\beta$  and therefore  $Z_{in}$  becomes now  $Z_0 \tanh(\alpha + j\beta)l$  and this equation can be expanded as  $Z_{in}$  is equal to  $Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$ .  $\tanh \alpha l$  will become  $\alpha l$  and  $\tan \beta l$  will become  $\frac{\omega l}{v_p}$  and  $\tanh \alpha l$  will become  $\alpha l$ .

Now, we have considered the transmission line to have very low loss. So, in that case we write  $\alpha l$  to be much less compared to 1 and we can approximate  $\tanh \alpha l$  as  $\alpha l$  and similarly  $\beta l$  can be written as  $\frac{\omega l}{v_p}$  and once we substitute  $\omega$  equal to  $\omega_0 + \Delta \omega$  this can be written as  $\frac{\omega_0 l}{v_p} + \frac{\Delta \omega l}{v_p}$ .

Now, since we have  $l$  is equal to  $\frac{\lambda}{2}$  at  $\omega$  equal to  $\omega_0$  this term  $\frac{\omega_0 l}{v_p}$  this becomes  $\pi$  because  $v_p$  will be  $\frac{\lambda}{2}$  into  $f_0$  and  $\omega_0$  can be written as  $2\pi f_0$  and  $l$  is  $\frac{\lambda}{2}$  so we will have  $\frac{\omega_0 l}{v_p}$  is equal to  $\pi$ .

(Refer Slide Time: 07:13)

$$\text{Now, } \beta l = \frac{\omega_0 l}{v_p} + \frac{\Delta \omega l}{v_p} \quad \text{and} \quad \frac{\omega_0 l}{v_p} = \pi$$

$$\text{Therefore, } \beta l = \pi + \frac{\Delta \omega l}{v_p} \quad \text{and} \quad \tan \beta l = \tan \left( \pi + \frac{\Delta \omega l}{v_p} \right) \cong \frac{\Delta \omega l}{v_p}$$

$$\text{Hence, } Z_{in} = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l} \cong Z_0 \frac{\alpha l + j \left( \frac{\Delta \omega l}{v_p} \right)}{1 + j \alpha l \left( \frac{\Delta \omega l}{v_p} \right)}$$

Therefore,  $Z_{in} \cong Z_0 \left( \alpha l + j \frac{\Delta \omega \pi}{\omega_0} \right)$

Comparing with a series resonant circuit for which

$$Z_{in} \cong R + j2\Delta\omega L$$

### Transmission Line Resonators

$$\text{Now, } \beta l = \frac{\omega_0 l}{v_p} + \frac{\Delta \omega l}{v_p} \quad \text{and} \quad \frac{\omega_0 l}{v_p} = \pi$$

$$\text{Therefore, } \beta l = \pi + \frac{\Delta \omega \pi}{\omega_0} \quad \text{and} \quad \tan \beta l = \tan \left( \pi + \frac{\Delta \omega \pi}{\omega_0} \right) \approx \frac{\Delta \omega \pi}{\omega_0}$$

$$\text{Hence, } Z_{in} = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l} \approx Z_0 \frac{\alpha l + j \left( \frac{\Delta \omega \pi}{\omega_0} \right)}{1 + j \alpha l \left( \frac{\Delta \omega \pi}{\omega_0} \right)}$$

$$\text{Therefore, } Z_{in} \approx Z_0 \left( \alpha l + j \frac{\Delta \omega \pi}{\omega_0} \right)$$

$$\text{Comparing with a series resonant circuit for which} \\ Z_{in} \approx R + j2\Delta\omega L$$

So, we have now  $\beta l$  is equal to  $\omega_0 l$  by  $v_p$  plus  $\Delta \omega l$  by  $v_p$  and  $\omega_0 l$  by  $v_p$  is equal to  $\pi$  and therefore we can write  $\beta l$  to be equal to  $\pi$  plus  $\Delta \omega \pi$  by  $\omega_0$  and  $\tan \beta l$  can be written as  $\tan \pi$  plus  $\Delta \omega \pi$  by  $\omega_0$ . Now,  $\Delta \omega$  being very small compared to  $\omega_0$  we can use the approximation first of all  $\tan \pi + \theta$  will become  $\tan \theta$  and then we can use the approximation for small  $\theta$   $\tan \theta$  equal to  $\theta$ .

So, we can write  $\tan \beta l$  to be approximately equal to  $\Delta \omega \pi$  divided by  $\omega_0$ . Hence we can now write  $Z_{in}$  which is  $Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$ . Now, if you substitute  $\tanh \alpha l$  as  $\alpha l$  and  $\tan \beta l$  as  $\Delta \omega \pi$  by  $\omega_0$  we can write  $Z_{in}$  appropriately equal to  $Z_0 \frac{\alpha l + j \frac{\Delta \omega \pi}{\omega_0}}{1 + j \alpha l \frac{\Delta \omega \pi}{\omega_0}}$ .

Now, here you can see in the denominator we have the product of two small terms one is  $\alpha l$  and another is  $\Delta \omega \pi$  by  $\omega_0$ . So, this term can be neglected with respect to 1 and therefore we can write  $Z_{in}$  approximately equal to  $Z_0 \left( \alpha l + j \frac{\Delta \omega \pi}{\omega_0} \right)$ . Now, what we can do? We can compare it with the expression for input

impedance of a series resonant circuit near its resonant frequency so which is given by  $Z_{in}$  equal to  $R$  plus  $j2\delta\omega L$ .

So, if we compare these two this for a  $\lambda/2$  short-circuited transmission line sections and this  $Z_{in}$  is for a series RLC circuit operating near its resonant frequency.

(Refer Slide Time: 10:56)

$$R = Z_0\alpha l \quad \text{and} \quad L = \frac{\pi Z_0}{2\omega_0}$$

Capacitance  $C$  can be found from  $C = \frac{1}{\omega_0^2 L} = \frac{2}{\pi\omega_0 Z_0}$

Unloaded  $Q$  of the resonator  $Q_0 = \frac{\omega_0 L}{R} = \frac{\pi}{2\alpha l}$

**Transmission Line Resonators**

$$R = Z_0\alpha l \quad \text{and} \quad L = \frac{\pi Z_0}{2\omega_0}$$

Capacitance  $C$  can be found from  $C = \frac{1}{\omega_0^2 L} = \frac{2}{\pi\omega_0 Z_0}$

Unloaded  $Q$  of the resonator  $Q_0 = \frac{\omega_0 L}{R} = \frac{\pi}{2\alpha l}$

Then we can write  $R$  equal to  $Z_0\alpha l$  and  $L$  equal to  $\pi Z_0 / 2\omega_0$ , and since  $\omega_0^2 LC = 1$  we can find the capacitance  $C$  as  $1 / \omega_0^2 L$ , and we have already had the expression for  $L$  and this becomes equal to  $2 / \pi\omega_0 Z_0$ . Now, unloaded  $Q$  of the resonator it is given by  $Q_0$  is equal to  $\omega_0 L / R$ .

So, if we substitute  $L$  and  $R$  here  $R$  equal to  $Z_0\alpha l$  and  $L$  equal to  $\pi Z_0 / 2\omega_0$  then we get  $Q_0$  the unloaded  $Q$  of the resonator to be equal to  $\pi / 2\alpha l$ . So, smaller, the value of  $\alpha$  larger will be the value of  $Q$ , and we will have a sharp resonance at  $\omega_0$ . So, you see that if we have a  $\lambda/2$  sections of a transmission line having small amount of loss and the line is short-circuited at one end

then the transmission line section can resonate at a frequency where the line length corresponds to half the wavelength.

(Refer Slide Time: 13:22)

Let us now consider another transmission line resonator which consists of a short-circuited transmission line of length  $\lambda/4$ .

$$l = \frac{\lambda}{4} \text{ at } \omega = \omega_0$$

We have 
$$Z_{in} = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$$

Multiplying the numerator and denominator by  $-j \cot \beta l$

$$Z_{in} = Z_0 \frac{1 - j \tanh \alpha l \cot \beta l}{\tanh \alpha l - j \cot \beta l}$$

### Transmission Line Resonators

Let us now consider another transmission line resonator which consists of a short-circuited transmission line of length  $\lambda/4$ .

$$l = \frac{\lambda}{4} \text{ at } \omega = \omega_0$$

We have 
$$Z_{in} = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$$

Multiplying the numerator and denominator by  $-j \cot \beta l$

$$Z_{in} = Z_0 \frac{1 - j \tanh \alpha l \cot \beta l}{\tanh \alpha l - j \cot \beta l}$$

So, we continue our discussion on transmission line resonators. We consider another type of transmission line resonator. Here, we consider a short-circuited transmission line of length  $\lambda/4$ . So, for this type of transmission line resonator we have at  $\omega = \omega_0$ . The physical length of the transmission line  $l$  is equal to  $\lambda/4$  which means it is a quarter-wave section, short-circuited at one end.

Now, if the line as before is assumed to be slightly lossy that means having an attenuation constant of  $\alpha$  and phase constant  $\beta$  and characteristic impedance  $Z_0$ . So, for such

line we can we have already seen that we can write  $Z_{in}$  equal to  $Z_0 \tanh \alpha l$  plus  $j \tan \beta l$  divided by  $1 + j \tan \beta l \tanh \alpha l$ . Now, what we do? We multiply both the numerator and the denominator by  $\cot \beta l$ .

So, in that case when it is multiplied by  $\cot \beta l$   $j \tan \beta l \cot \beta l$  will give 1 and therefore we can write  $Z_{in}$  is equal to  $Z_0 \tanh \alpha l \cot \beta l$  and then this term will become  $\tanh \alpha l \cot \beta l$  minus 1 into  $j \cot \beta l$  will give  $j \cot \beta l$ . So,  $Z_{in}$  becomes after multiplying by  $\cot \beta l$   $Z_{in}$  becomes  $Z_0 \tanh \alpha l \cot \beta l$  divided by  $\tanh \alpha l \cot \beta l$  minus  $j \cot \beta l$ .

(Refer Slide Time: 16:19)

Let  $\omega = \omega_0 + \Delta\omega$

$$\beta l = \frac{\omega_0 l}{v_p} + \frac{\Delta\omega l}{v_p} = \frac{\pi}{2} + \frac{\pi \Delta\omega}{2\omega_0}$$

Therefore,  $\cot \beta l = -\tan \frac{\pi \Delta\omega}{2\omega_0} \cong -\frac{\pi \Delta\omega}{2\omega_0}$

We have  $Z_{in} = Z_0 \frac{1 - j \tanh \alpha l \cot \beta l}{\tanh \alpha l - j \cot \beta l}$

Therefore,  $Z_{in} = Z_0 \frac{1 + j \alpha l \left( \frac{\pi \Delta\omega}{2\omega_0} \right)}{\alpha l + j \frac{\pi \Delta\omega}{2\omega_0}} \cong \frac{Z_0}{\alpha l + j \frac{\pi \Delta\omega}{2\omega_0}}$

**Transmission Line Resonators**

Let  $\omega = \omega_0 + \Delta\omega$

$$\beta l = \frac{\omega_0 l}{v_p} + \frac{\Delta\omega l}{v_p} = \frac{\pi}{2} + \frac{\pi \Delta\omega}{2\omega_0}$$

Therefore,  $\cot \beta l = -\tan \frac{\pi \Delta\omega}{2\omega_0} \approx -\frac{\pi \Delta\omega}{2\omega_0}$

We have  $Z_{in} = Z_0 \frac{1 - j \tanh \alpha l \cot \beta l}{\tanh \alpha l - j \cot \beta l}$

Therefore,  $Z_{in} = Z_0 \frac{1 + j \alpha l \left( \frac{\pi \Delta\omega}{2\omega_0} \right)}{\alpha l + j \frac{\pi \Delta\omega}{2\omega_0}} \approx \frac{Z_0}{\alpha l + j \frac{\pi \Delta\omega}{2\omega_0}}$

Once again, we consider  $\omega$  to be  $\omega_0 + \Delta\omega$  close to the resonant frequency, and in this case, when it is a  $\lambda/4$  transmission line section  $\beta l$  can be

written as  $\pi/2$  plus  $\pi \Delta \omega$  divided by  $2 \omega_0$ . Now, once we have this expression for  $\beta$  we find that  $\cot \beta$  because of this  $\pi/2$  term it becomes minus  $\tan \pi \Delta \omega$  divided by  $2 \omega_0$ .

Once again since we are assuming  $\Delta \omega$  to be small compared to  $\omega_0$  we can write  $\tan \pi \Delta \omega$  divided by  $2 \omega_0$  to be approximately equal to minus  $\pi \Delta \omega$  divided by  $2 \omega_0$ . And then we already have the expression for  $Z_{in}$ , we can now make appropriate substitutions  $\tanh \alpha$  can be substituted by  $\alpha$  and  $\cot \beta$  we can make substitution minus  $\pi \Delta \omega$  divided by  $2 \omega_0$ .

So, once we do that we get  $Z_{in}$  to be equal to  $Z_0$  plus  $j \alpha \pi \Delta \omega$  divided by  $2 \omega_0$ . So, this minus and this is minus will make it plus and  $\alpha$  again plus  $j \pi \Delta \omega$  divided by  $2 \omega_0$ . Now, here in the numerator once again we have the product of two small terms  $\alpha$  and  $\pi \Delta \omega$  divided by  $2 \omega_0$ . So, this term can be neglected in comparison with 1, and  $Z_{in}$  finally can be approximated as  $Z_0$  divided by  $\alpha$  plus  $j \pi \Delta \omega$  divided by  $2 \omega_0$ .

(Refer Slide Time: 20:02)

$$Z_{in} \cong \frac{Z_0}{\alpha + j \frac{\pi \Delta \omega}{2 \omega_0}} = \frac{1}{\frac{\alpha}{Z_0} + j \frac{\pi \Delta \omega}{2 \omega_0 Z_0}}$$

For a parallel RLC circuit near resonance,

$$Z_{in} \cong \frac{R}{1 + j 2 \Delta \omega RC} = \frac{1}{\frac{1}{R} + j 2 \Delta \omega C}$$

Therefore,  $R = \frac{Z_0}{\alpha}$  and  $C = \frac{\pi}{4 \omega_0 Z_0}$

$$Q_0 = \omega_0 RC = \frac{\pi}{4 \alpha}$$



## Transmission Line Resonators

$$Z_{in} \approx \frac{Z_0}{\alpha l + j \frac{\pi \Delta \omega}{2 \omega_0}} = \frac{1}{\frac{\alpha l}{Z_0} + j \frac{\pi \Delta \omega}{2 \omega_0 Z_0}}$$

For a parallel RLC circuit near resonance,

$$Z_{in} \approx \frac{R}{1 + j 2 \Delta \omega RC} = \frac{1}{\frac{1}{R} + j 2 \Delta \omega C}$$

Therefore,  $R \approx \frac{Z_0}{\alpha l}$  and  $C = \frac{\pi}{4 \omega_0 Z_0}$

$$Q_0 = \omega_0 RC = \frac{\pi}{4 \alpha l}$$

So, this can be further written in this form  $\frac{1}{\alpha l + j \frac{\pi \Delta \omega}{2 \omega_0 Z_0}}$ . Now, we identify that this form is of the input impedance is that of a parallel RLC circuit operating near it is resonance. For a parallel RLC circuit near resonance we have  $Z_{in}$  to be approximately equal to  $\frac{R}{1 + j 2 \Delta \omega RC}$ , which can be put of this form  $\frac{1}{\frac{1}{R} + j 2 \Delta \omega C}$ .

Now, if we equate this corresponding terms then we get  $R$  equal to  $\frac{Z_0}{\alpha l}$  and  $C$  equal to  $\frac{\pi}{4 \omega_0 Z_0}$  and once we have the values for  $R$  and  $C$  we can calculate the value of  $L$  if required and we can also calculate the unloaded  $Q$ .  $Q_0$  is equal to  $\omega_0 RC$  and which is given by  $\frac{\pi}{4 \alpha l}$ . Once again, we see that low  $\alpha l$  we have high values of unloaded  $Q$ .

So, we find that a short-circuited  $\frac{\lambda}{4}$  sections of a transmission line is essentially it can be modeled as a parallel RLC circuit, and the resonant frequency will be determined by the length of the line at which it is  $\frac{\lambda}{4}$ . In this lecture we have studied different types of transmission line resonators. In the next lecture, we will consider another form of resonator, which is waveguide resonators.