


Principles of Signals and Systems
Prof. Aditya K. Jagannatham
Department of Electrical Engineering
Indian Institute of Technology, Kanpur

Lecture – 23

**Laplace Transform – RL Circuit Problem, Unilateral Laplace Transform, RC
Circuit with Initial Conditions**

Hello, welcome to another module in this massive open online course. So, we are looking at example problems for the Laplace transform. Let us do few more or. In fact, one or two more, and then we will go on to a new topic.

(Refer Slide Time: 00:27)

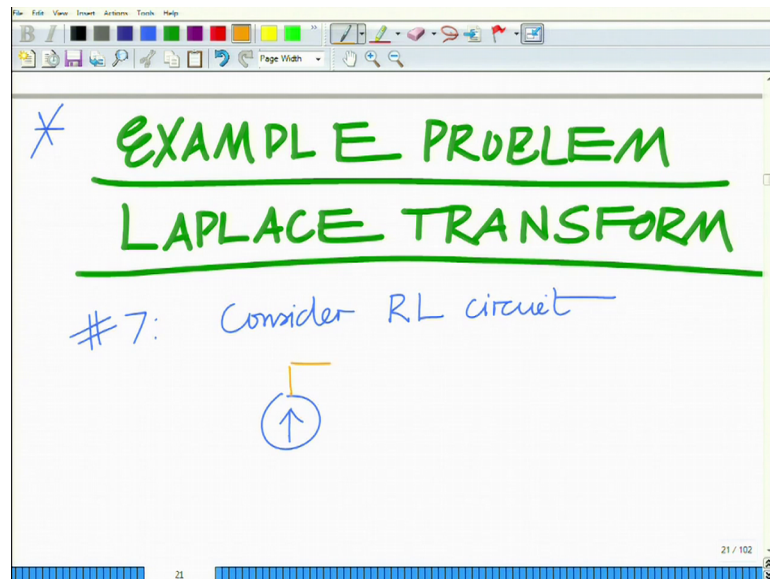

So, I want to start with another example problem or the Laplace transform, and the problem is the following. So, this is role number 7, consider the RL circuit that is given below. So, I have a current source which is connected in parallel with a resistance R and inductor L correct.

(Refer Slide Time: 01:23)

#7: Consider RL circuit

The diagram shows a series RL circuit with an input current $i(t)$ entering from the top. The current through the resistor is $i_R(t)$ and the current through the inductor is $i_L(t) = y(t)$. The voltage across the resistor is $v(t)$. The input current is also labeled as $x(t) = i(t)$.

$$v(t) = L \frac{di_L(t)}{dt}$$

$$i_R(t) R = v(t) = L \frac{di_L(t)}{dt}$$

$$\Rightarrow i_R(t) = \frac{L}{R} \frac{di_L(t)}{dt}$$

And if we call this as output current $i_L(t)$ equals y . And if we call this as $i(t)$ then we have $v(t)$ equals $L \frac{di_L(t)}{dt}$ by dt ok.

And if you call the current through the resistance as $i_R(t)$, we have therefore, by ohms law $i_R(t) R$ equals $v(t)$ equals $L \frac{di_L(t)}{dt}$ which implies $i_R(t) R$ equals $L \frac{di_L(t)}{dt}$ and further we have the $i(t)$ current equals $i_R(t)$ plus $i_L(t)$.

(Refer Slide Time: 02:47)

$$i(t) = i_R(t) + i_L(t)$$

$$i(t) = \frac{L}{R} \frac{di_L(t)}{dt} + i_L(t)$$

$$x(t) \quad x(t) = \frac{L}{R} \frac{d}{dt} y(t) + y(t)$$

$$\Rightarrow X(s) = \frac{L}{R} s Y(s) + Y(s)$$

$$= Y(s) \left(1 + \frac{L}{R} s \right)$$

This is current through the resistance $i_R(t)$ plus current through inductor $i_L(t)$ which is equal to $L \frac{di_L(t)}{dt}$ plus $i_L(t)$ ok.

So, this is my input $i(t)$. So, this is the input output equation. So, if we denote $i(t)$ by $x(t)$ this is my input $x(t)$. So, I have $x(t)$ equals the input which is $i(t)$. And of course, you already said that $i(t)$ is the output that is $y(t)$. So, the input is the source current that is $i(t)$ and the output is the inductor current, output $y(t)$ is the inductor current that is $i_L(t)$.

And. Now, therefore, we have $x(t)$. Writing this in terms of $x(t)$ $y(t)$, we will have $x(t)$ equals L by R $\frac{d}{dt} y(t)$ plus $y(t)$. Now taking the Laplace transform we have $X(s)$ equals L over R . Remember Laplace transform $\frac{d}{dt} y(t)$ is $s Y(s)$ this is $Y(s)$ plus the Laplace transform of $y(t)$ which is $Y(s)$, which is equal to. Well $Y(s)$ into $1 + \frac{L}{R} s$, which means the transfer function. Remember the transfer function, input output transfer function is defined as the ratio of output Laplace transform to input Laplace transform; that is $Y(s)$ over $X(s)$.

Therefore $H(s)$ the Laplace transform of the transfer, all the transfer function is basically Laplace transform.

(Refer Slide Time: 05:09)

$$H(s) = \frac{Y(s)}{X(s)} = \frac{1}{1 + \frac{L}{R}s}$$

$$H(s) = \frac{1}{1 + \frac{L}{R}s}$$

$$= \frac{R/L}{s + R/L}$$

The impulse response or basically the transfer function is basically $Y(s)$ by $X(s)$ equals 1 over $1 + \frac{L}{R}s$. So, we have $H(s)$ equals 1 over $1 + \frac{L}{R}s$, and observe the pole of the system, but this can also be written as R/L divided by $s + R/L$. So, the pole, it has a one pole P_1 equals minus R/L .

(Refer Slide Time: 06:04)

$$\frac{R}{s + \frac{R}{L}} = \frac{\frac{R}{L}}{s + \frac{R}{L}}$$
$$p_1 = -\frac{R}{L}$$
$$\text{Roc: } s > -\frac{R}{L}$$
$$h(t) = \frac{R}{L} e^{-\frac{Rt}{L}} u(t)$$

Therefore Roc, now let us assume a right handed signal. Therefore, Roc is basically. If Roc is basically for right handed signal, Roc is basically s greater than minus R by L , and the corresponding inverse Laplace transform; that is H_t , you can see is basically that is R over L times e raise to minus Rt over L $u(t)$. So, this is the. So, this is the impulse response.

(Refer Slide Time: 07:06)

$$p_1 = -\frac{R}{L}$$
$$\text{Roc: } s > -\frac{R}{L}$$
$$h(t) = \frac{R}{L} e^{-\frac{Rt}{L}} u(t)$$


Impulse Response of RL circuit

This is the impulse response of the RL circuit. So, basically we have found the impulse response of this RL circuit, which is R over L e raise to minus Rt over L times $u(t)$,

assuming that it is a right handed signal and the Roc is real part of s greater than minus R over L all right.

Now, let us proceed on to a different topic which is something that we are going to discuss briefly, and something we did not discuss before; that is the concept of the unilateral Laplace transform. Remember what we have looked at so far, is the concept of bilateral Laplace transform.

(Refer Slide Time: 08:00)

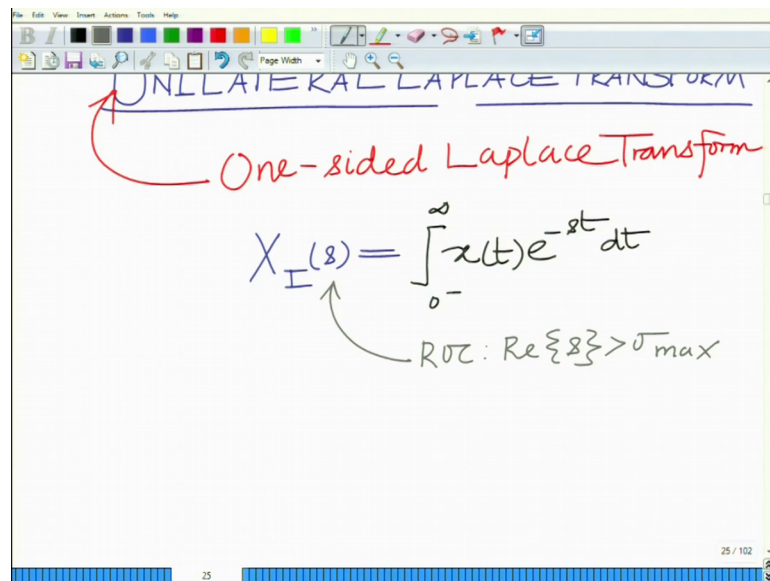

UNILATERAL LAPLACE TRANSFORM

One-sided Laplace Transform

$$X_I(s) = \int_{0^-}^{\infty} x(t)e^{-st} dt$$

ROC: $\text{Re}\{s\} > \sigma_{\max}$

The unilateral Laplace transform, the unilateral Laplace transform or one sided Laplace transform can be defined as follows that is X_I of s equals 0 minus to infinity $x(t) e^{-st} dt$ and therefore.

Now, the Roc. Now you look at this, we are clearly considering a right handed signal there. So, for Roc is of the form when you are looking at the unilateral Roc we are considering a right handed signal. So, Roc will be of the form real part of s greater than σ_{\max} . Now typically this is useful for determining the response of a causal system to a causal input with non zero initial conditions all right.

So, the unilateral Laplace transform or the one sided Laplace transform, as we are going to illustrate, it is basically very useful in scenarios where you have a causal system with a causal input and nonzero initial conditions. So, this is useful for the unilateral Laplace transform, useful for a causal system with a causal input.

(Refer Slide Time: 10:02)

ULT: Use for for causality
with causal input
+ Non-zero initial
conditions.

Properties:

$$x(t) \leftrightarrow X_I(s)$$
$$\frac{dx(t)}{dt} \leftrightarrow sX_I(s) - x(0^-)$$

26 / 102

Remember causal input is non zero only for t greater than or equal to 0 plus where you have nonzero plus where you have nonzero initial conditions all right.

Now, some of the properties of this unilateral transformer as follows; slightly different from those of the bilateral Laplace transform. So, let us say the signal $x(t)$ has unilateral Laplace transform $X_I(s)$, then $\frac{dx(t)}{dt}$. The derivative has a Laplace transform $sX_I(s) - x(0^-)$. So, this is the derivative of $sX_I(s)$ minus the value of the signal x at 0^- . So, this is the derivative of $sX_I(s)$. Remember previously for the bilateral, we simply had the Laplace transform of the derivative of the signal is $sX(s)$.

But here we have $sX_I(s)$, where $X_I(s)$ is a unilateral Laplace transform minus $x(0^-)$ minus there is a value of this signal at 0^- further.

(Refer Slide Time: 11:46)

Properties:

$$x(t) \leftrightarrow X_I(s)$$

$$\frac{dx(t)}{dt} \leftrightarrow sX_I(s) - x(0^-)$$

$$\int_{0^-}^t x(\tau) d\tau \leftrightarrow \frac{X_I(s)}{s}$$

$$\int_{-\infty}^t x(\tau) d\tau \leftrightarrow \frac{X_I(s)}{s} + \frac{1}{s} \int_{-\infty}^{0^-} x(\tau) d\tau$$

If you consider integral 0 minus, integral 0 minus to t x tau d tau; this will have the Laplace transform X I of s divided by s and integral minus infinity to t x tau d, tau will have the Laplace transform X I of s over s plus 1 over s integral minus infinity to 0 minus x tau d tau. So, these are some of the properties of the unilateral transform.

Let us look at an example to understand this better.

(Refer Slide Time: 12:44)

ex: Consider RC circuit

$V_C(0^-) = V_0$ (initial voltage of Capacitor)


$V_s(t) = Vu(t)$

Let us consider the RC circuit below. Consider the RC circuit where you have a voltage source connected across a resistance, and a capacitance and series. So, you have this, let

us say is the Res, the voltage $V_c t$ is the voltage across the capacitor $V R t$ is the voltage across the resistance. Let us say we assume a current of $i t$, let us say the source voltage is given by $V_s t$ ok.

Now, we are given the initial condition. We see 0 minus equals V naught, or remember this is the initial condition, this is the initial voltage of capacitor. Further we are given that the source voltage equals V times $u t$ that is The source voltage is as follows.


(Refer Slide Time: 14:11)

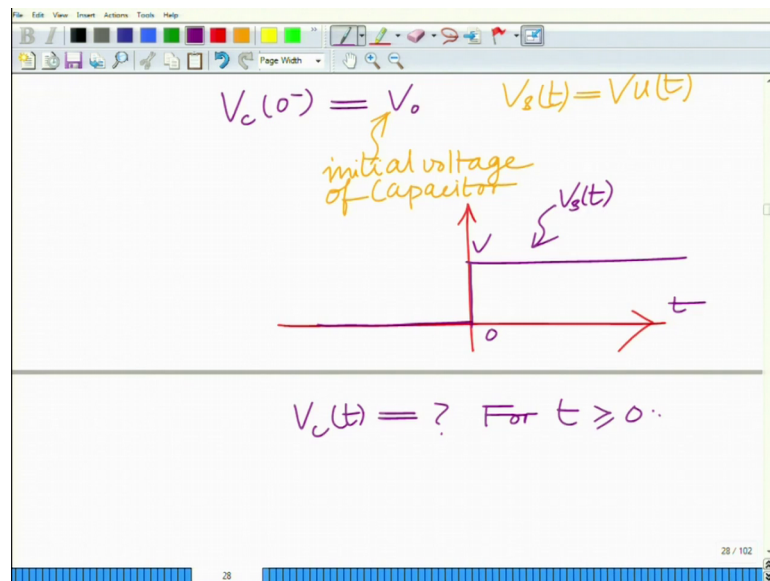

So, we have a step change. You have a step change at t equal to 0. We have step change to V . So, this is basically your $V_s t$ the step function at time t equal to 0, it becomes weak. So, its V times $u t$, and the initial capacitor voltage; that is $V_c t$ at t equal to 0 minus is V naught, the initial cap initial voltage across the capacitor is V naught ok.

Now, we are required to find what is the capacitor voltage for time t greater than or equal to 0. How does the capacitor voltage vary, change as for time t greater than or equal to 0. So, we are required to find what is $V_c t$ equal to for time t greater than equal to 0. Now taking the unit

(Refer Slide Time: 15:14)

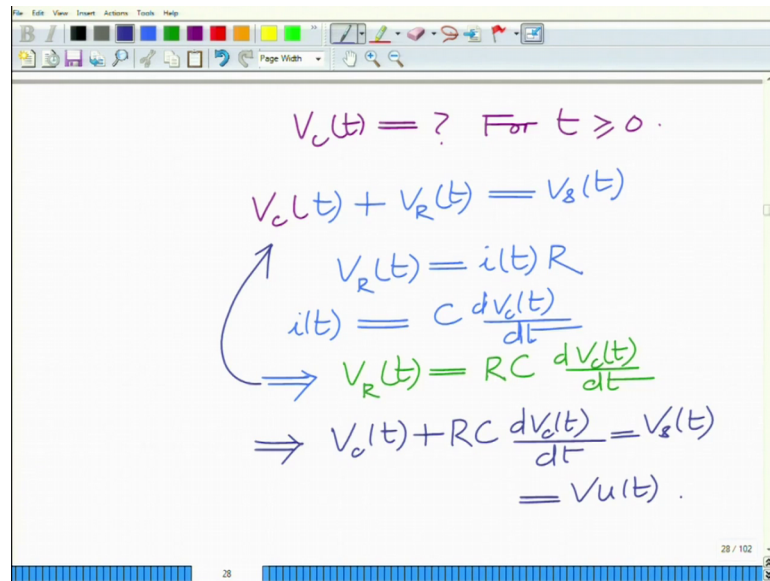
$$\begin{aligned} V_c(t) &= ? \text{ For } t \geq 0. \\ V_c(t) + V_R(t) &= V_s(t) \\ V_R(t) &= i(t)R \\ i(t) &= C \frac{dV_c(t)}{dt} \\ \Rightarrow V_R(t) &= RC \frac{dV_c(t)}{dt} \\ \Rightarrow V_c(t) + RC \frac{dV_c(t)}{dt} &= V_s(t) \\ &= V u(t). \end{aligned}$$

Now what we can write this as from the system; now voltage across the capacitor. Now you can clearly see the voltage across the capacitor plus voltage across the resistance, is equal to the source voltage.

Now, you can see the voltage across the resistance equals i times the resistance, correct i times the resistance, but i equals we have $C \frac{dv}{dt}$ that is C times the derivative of the voltage across the capacitor that is a current, which implies the voltage across the resistance equals $RC \frac{dv}{dt}$, which basically now implies substituting this here, we have $V_c(t) + RC \frac{dV_c(t)}{dt} = V_s(t) = V u(t)$.

Now, we take the one sided Laplace transform on both the side, because we have a system with nonzero initial conditions. So, we are using the one side or the unilateral Laplace transform. So, taking the unilateral Laplace transform.

(Refer Slide Time: 16:57)

The whiteboard shows the following steps:

$$i(t) = C \frac{dv_c(t)}{dt}$$

$$\Rightarrow V_R(t) = RC \frac{dv_c(t)}{dt}$$

$$\Rightarrow V_c(t) + RC \frac{dv_c(t)}{dt} = V_s(t) = Vu(t)$$

Taking ULT,

$$V_c(s) + RC(sV_c(s) - V_c(0^-)) = \frac{V}{s}$$

So, taking the unilateral Laplace transform. The unilateral Laplace transform of $V_c(t)$, let's say is $V_c(s)$ plus the unilateral Laplace transform $dv_c(t)/dt$. As we have seen before is $sV_c(s)$ minus $V_c(0^-)$ which is V_0 equals the Laplace transform of a $Vu(t)$ which is V/s . This implies.

(Refer Slide Time: 17:35)

The whiteboard shows the following steps:

$$\Rightarrow V_c(s) + RC(sV_c(s) - V_0) = \frac{V}{s}$$

$$\Rightarrow V_c(s)(1 + RCs) = RC V_0 + \frac{V}{s}$$

$$\Rightarrow V_c(s) = \frac{RC V_0}{1 + RCs} + \frac{V}{s(1 + RCs)}$$

$$= \frac{V_0}{s + \frac{1}{RC}} + V \left(\frac{1}{s} - \frac{RC}{1 + RCs} \right)$$

That we have Vcs plus $RC Vc s$ minus V_0 equals V/s which implies Vcs into this is $sVcs$, Vcs into $1 + sRC$ or $1 + RCs$. Let's write it that $1 + RCs$ Vcs into

$1 + RCs$ equals RC into V naught plus V by s implies Vcs equals RC V naught by $1 + RCs$ plus V by s into $1 + RCs$.

Now, further simplifying this; this is simply V naught over $s + 1/RC$ plus V into 1 over s minus RC over $1 + RCs$ correct. So, you have this equals.

(Refer Slide Time: 19:18)

The image shows a whiteboard with the following handwritten work:

$$= \frac{V_0}{s + \frac{1}{RC}} + V \left(\frac{1}{s} - \frac{1}{1 + RCs} \right)$$

Taking ILT

$$V_c(t) = V_0 e^{-t/RC} u(t) + V(u(t) - e^{-t/RC} u(t))$$

$$= V_0 e^{-t/RC} u(t) + V(1 - e^{-t/RC}) u(t)$$

Now, again which if you take the inverse Laplace transform you get $V_c(t)$. Now the inverse Laplace transform is V naught over $s + RC$ is V naught e power minus t over RC into $u(t)$ plus V into inverse Laplace transform 1 over s is $u(t)$ minus inverse Laplace transform of RC over $1 + RCs$ is simply e raise to again similar to before e raise to minus R over C $1 - e$ into e raise to minus t over RC $u(t)$.

So, $V_c(t)$ equals this, which is equals to second taking inverse already i taking the inverse Laplace transform. So, this is V naught e raise to minus t over RC plus V $1 - e$ raise to minus t over RC into $u(t)$, which means for t greater than or equal to 0 $V_c(t)$ equals.

(Refer Slide Time: 20:42)

$$= V_0 e^{-t/RC} u(t) + V(1 - e^{-t/RC}) u(t)$$

For $t \geq 0$

$$V_c(t) = V_0 e^{-t/RC} + V(1 - e^{-t/RC})$$

output for $t \geq 0$.

We have $V_c(t)$ equals $V_0 e^{-t/RC} + V(1 - e^{-t/RC})$ for t greater than or equal to 0.

Remember this holds only for $t \geq 0$. So, this is output for t greater than or equal to 0. Therefore, using the inverse Laplace transform from the differential equation of the system, using the concept of the unilateral Laplace transform or basically the one sided Laplace transform, we have been able to find the output for t greater than or equal to 0 for a system with nonzero initial conditions, all right.

So, in this module what we have seen is, we have seen different problems as well as the concept of the unilateral Laplace transform. So, we will stop here and continue in subsequent modules.

Thank you very much.