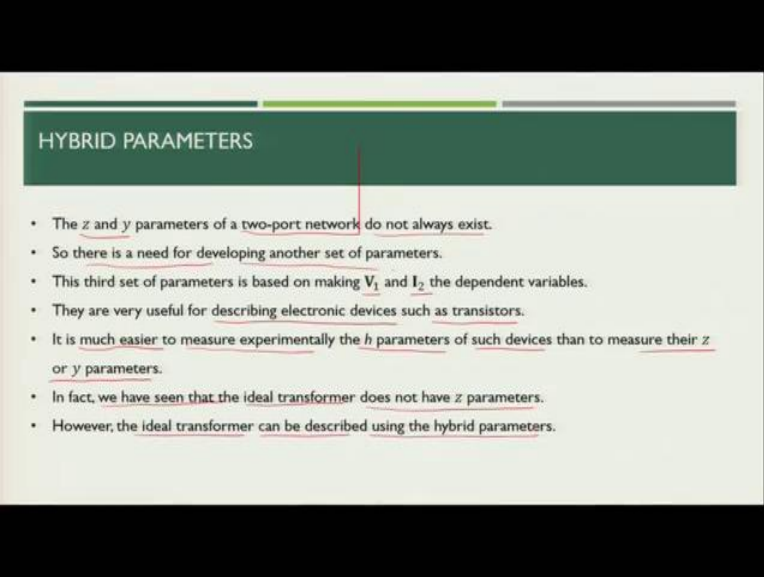


Basic Electric Circuits
Professor Ankush Sharma
Department of Electrical Engineering
Indian Institute of Technology Kanpur
Module 8 - Two Port Network
Lecture 38 - Hybrid Parameters

Namaskar, in last two sessions we discussed about the z parameters and y parameters. In case of z parameters, we established the relationship for V_1 and V_2 that is the voltages at the two ports in terms of the currents. While in case of y parameters we stabilize the relationship for currents at both sides in terms of voltages. Now, third condition may arise when you have, voltage and current as a dependent component. Then in that case what will happen? That will give the new set of parameters which we will discuss in today's session.

(Refer Slide Time: 1:06)



HYBRID PARAMETERS

- The z and y parameters of a two-port network do not always exist.
- So there is a need for developing another set of parameters.
- This third set of parameters is based on making V_1 and I_2 the dependent variables.
- They are very useful for describing electronic devices such as transistors.
- It is much easier to measure experimentally the h parameters of such devices than to measure their z or y parameters.
- In fact, we have seen that the ideal transformer does not have z parameters.
- However, the ideal transformer can be described using the hybrid parameters.

Let us start the discussion of today's lecture, we will discuss about the hybrid parameters in today's session. We have seen z and y parameters, but in case of two port network it is not necessary that you always have a flexibility to find out the z and y parameters. There is a need for developing another set of parameters, wherein you may have the dependent variables as V_1 and I_2 , while the independent variables will be to V_2 and I_1 .

This kind of relationships you will see mostly in the electronic devices such as transistors. In case of transistors, if you have studied, we developed the equivalent model of transistor in terms of h

parameters. In those cases we can use the h parameter variables which we will discuss in today's session.

Now, it is much easier to measure experimentally the h parameters of such devices, then to measure their z and y parameters. That is why we have more interested into the h parameters calculation. So, if you recollect that we discussed that in case of ideal transformers we cannot create the z parameters for that circuit. But in this case the ideal transformer can be described using hybrid parameters.

(Refer Slide Time: 2:46)

- The relation between the terminal voltage and the terminal current can established using the following equations:
$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- ①}$$
$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- ②}$$
- This can alternatively be expressed in matrix form as,
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$
- Here the h terms are known as the hybrid parameters or the h parameters.
- They are called so because they are a hybrid combination of ratios.

Now, how we will define the relationships between the terminal voltages and the current. In case of h parameters, we will say that V_1 that is the input port voltage will be related to input port current and output port voltages in terms of,

$$V_1 = h_{11}I_1 + h_{12}V_2$$

Similarly, output port current that is I_2 will have a relationship between input port current and output port voltage and will define it as,

$$I_2 = h_{21}I_1 + h_{22}V_2$$

These are the two basic equations to find out the h parameters.

Now in matrix form how we will represent? So you will have

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

In summary we can say that we can be present it like a input the dependent vector is equal to h parameter matrix multiplied by independent vector. Now h terms are known as the hybrid parameters or h parameters in this case.

So why they are called is hybrid? Because in this case we have a combination of ratios. So, if you see h_{11} . It will be having the relationship between $\frac{V_1}{I_1}$, while $h_{12} = \frac{V_1}{V_2}$. So, when you see these two equations you will come to know that there is no uniformity in the parameters. These are the hybrid kind of parameters which we have in case of h parameters.

(Refer Slide Time: 4:48)

- The values of the parameters can be evaluated by setting $V_2 = 0$ (output port short-circuited) or $I_1 = 0$ (input port open-circuited).
- The individual parameters are evaluated as follows:
 - If $V_2 = 0$, then
$$h_{11} = \frac{V_1}{I_1}, h_{21} = \frac{I_2}{I_1}$$
 - If $I_1 = 0$, then
$$h_{12} = \frac{V_1}{V_2}, h_{22} = \frac{I_2}{V_2}$$
- The parameters h_{11} , h_{12} , h_{21} , and h_{22} represent an impedance, a voltage gain, a current gain, and an admittance, respectively.
- This is why they are called the hybrid parameters.

- The relation between the terminal voltage and the terminal current can be established using the following equations:

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \quad \text{--- (1)} \\ I_2 &= h_{21}I_1 + h_{22}V_2 \quad \text{--- (2)} \end{aligned}$$
- This can alternatively be expressed in matrix form as,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$
- Here the h terms are known as the hybrid parameters or the h parameters.
- They are called so because they are a hybrid combination of ratios.

How will you find the h parameters? The value parameters can be evaluated by setting $V_2 = 0$. That means you set the output port short circuit or $I_1 = 0$ that is input port open circuit. So, let us state first case in which we set $V_2 = 0$ that means the output port is short circuited. So, if you set $V_2 = 0$ in these two equations what will happen,

$$h_{11} = \frac{V_1}{I_1}, \quad h_{21} = \frac{I_2}{I_1}$$

Now, second case is when you set $I_1 = 0$. So here if you set $I_1 = 0$, h_{12} you will get as V_1 upon V_2 . And h_{22} you will get as I_2 upon V_2 .

$$h_{12} = \frac{V_1}{V_2}, \quad h_{22} = \frac{I_2}{V_2}$$


Now these parameters, what do they represent?

h_{11} represents the impedance because it is the ratio between V_1 and I_1 , h_{12} is the voltage gain because this is a relationship between V_1 and V_2 , h_{21} is the current gain because it is again the ratio between I_2 and I_1 and h_{22} is the admittance because it is ratio between I_2 and V_2 . So now, since we have impedance, voltage gain, current gain and admittance as a parameter, we call them as hybrid parameters.

(Refer Slide Time: 6:44)

- Specifically,
 - h_{11} = Short-circuit input impedance
 - h_{12} = Open-circuit reverse voltage gain
 - h_{21} = Short-circuit forward current gain
 - h_{22} = Open-circuit output admittance
- The h parameters are determined similar to the z or y parameters.
- For reciprocal circuits, $h_{12} = -h_{21}$.
- The hybrid model of a two-port network is as shown in the below figure.

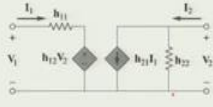$V_1 = h_{11}I_1 + h_{12}V_2$
 $I_2 = h_{21}I_1 + h_{22}V_2$



- The relation between the terminal voltage and the terminal current can be established using the following equations:
$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- (1)}$$
$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- (2)}$$
- This can alternatively be expressed in matrix form as,
$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = [h] \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$
- Here the h terms are known as the hybrid parameters or the h parameters.
- They are called so because they are a hybrid combination of ratios.

So now, you can say that,


- h_{11} = Short-circuit input impedance
- h_{12} = Open-circuit reverse voltage gain
- h_{21} = Short-circuit forward current gain
- h_{22} = Open-circuit output admittance

Now, the h parameters you can determine in a similar way as we determine in case of z or y parameters means you can just write the relationships h parameter equations. And then you can easily find out the h parameters. In case of reciprocal circuits $\mathbf{h}_{12} = -\mathbf{h}_{21}$. So, hybrid model of a two Port network you can define like this. How you will define, how you will draw this kind of circuit?

If you see the first equation which we have $\mathbf{V}_1 = \mathbf{h}_{11}\mathbf{I}_1 + \mathbf{h}_{12}\mathbf{V}_2$, that is $\mathbf{h}_{11}$ multiplied by current flowing through this and then you have $\mathbf{h}_{12}\mathbf{V}_2$ that is dependent voltage source. So, it will become $\mathbf{h}_{12}\mathbf{V}_2$. This is simply a series combination of the resistor and the dependent voltage source that is why you define it in terms of voltage $\mathbf{V}_1$.

Now here, it is a parallel combination so you can straightaway utilize the nodal analysis. So, if you use Kirchhoff's current law, you will get $\mathbf{I}_2 = \mathbf{h}_{21}\mathbf{I}_1 + \mathbf{h}_{22}\mathbf{V}_2$. These two are the same equations which we represented initially to define the h parameters. The same equations can be utilized to draw the hybrid model of a two port network, so this will be your equivalent h parameter circuit for a particular network.

(Refer Slide Time: 9:20)

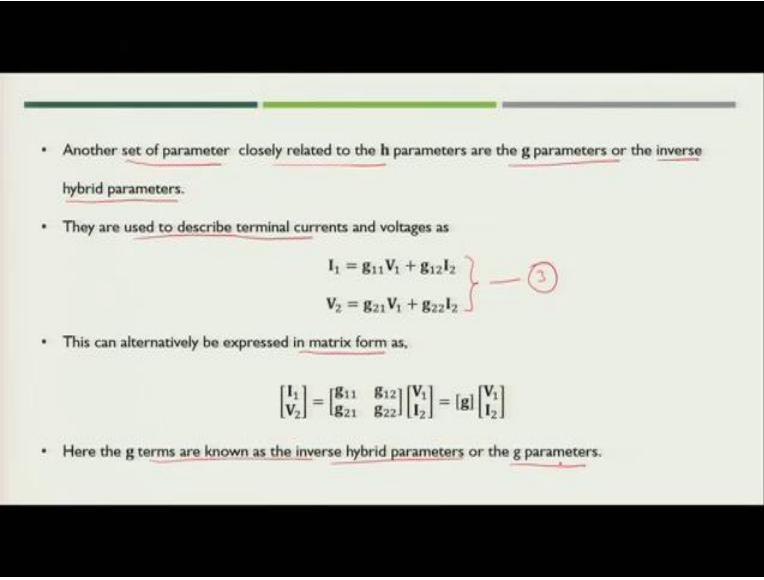

- Another set of parameter closely related to the h parameters are the g parameters or the inverse hybrid parameters.
- They are used to describe terminal currents and voltages as

$$\left. \begin{aligned} \mathbf{I}_1 &= \mathbf{g}_{11}\mathbf{V}_1 + \mathbf{g}_{12}\mathbf{I}_2 \\ \mathbf{V}_2 &= \mathbf{g}_{21}\mathbf{V}_1 + \mathbf{g}_{22}\mathbf{I}_2 \end{aligned} \right\} \text{--- (3)}$$
- This can alternatively be expressed in matrix form as,

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{g}_{11} & \mathbf{g}_{12} \\ \mathbf{g}_{21} & \mathbf{g}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = [\mathbf{g}] \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix}$$
- Here the g terms are known as the inverse hybrid parameters or the g parameters.

Now, there is another set of parameters which are closely related to h parameters. And what they are called? They are called as a g parameter or inverse hybrid parameters. Now in case of h parameters we stabilize the relationship between $\mathbf{V}_1$ and $\mathbf{I}_2$. So $\mathbf{V}_1$ and $\mathbf{I}_2$ were the dependent

variables in case of h parameters. Now, in this case when you are defining the g parameters or you can say the inverse of h parameters, we will have the dependent variables as I_1 and V_2 , independent variable will be V_1 and I_2 .

So now, how you will describe the terminal currents and voltages?

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

This can be another set of equations which will define the g parameters. In matrix form how you can write? You can write as a dependent variable vector,

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [g] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

So, since if you see these are inverse of h parameters, because in case of h parameters we were having V_1 and I_2 as dependent variable, here we are having the opposite of that, that is I_1 and V_2 as dependent variable. So, we will say g as inverse of hybrid parameters or we say in short as g parameters.

(Refer Slide Time: 11:20)

The slide content is as follows:

- The values of the parameters can be evaluated by setting $V_1 = 0$ (input port short-circuited) or $I_2 = 0$ (output port open-circuited).
- The individual parameters are evaluated as follows:
 - If $I_2 = 0$, then

$$g_{11} = \frac{I_1}{V_1}, g_{21} = \frac{V_2}{V_1}$$
 - If $V_1 = 0$, then

$$g_{12} = \frac{I_1}{I_2}, g_{22} = \frac{V_2}{I_2}$$
- The parameters g_{11} , g_{12} , g_{21} , and g_{22} represent an admittance, a current gain, a voltage gain, and an impedance, respectively.

- Another set of parameter closely related to the h parameters are the g parameters or the inverse hybrid parameters.
- They are used to describe terminal currents and voltages as

$$\left. \begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned} \right\} \text{--- (3)}$$
- This can alternatively be expressed in matrix form as,

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [g] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$
- Here the g terms are known as the inverse hybrid parameters or the g parameters.

Now, how you will find out the values of g parameters? The values of these parameters can be evaluated by now setting $V_1 = 0$. That is input ports short circuited. So in case of h parameters we were having $V_2 = 0$ that is output port was short circuited. Here $V_1 = 0$ means input port is short circuited and $I_2 = 0$ that means output port open circuit. In case of h parameters, we set $I_1 = 0$ that is input port open circuited.

Now, if you set $I_2 = 0$, we will get,

$$g_{11} = \frac{I_1}{V_1}, \quad g_{21} = \frac{V_2}{V_1}$$

If you set $V_1 = 0$, then,

$$g_{12} = \frac{I_1}{I_2}, \quad g_{22} = \frac{V_2}{I_2}$$

The parameters g_{11} , g_{12} , g_{21} , and g_{22} represent an admittance, a current gain, a voltage gain, and an impedance, respectively. You can compare them with the h parameters where h11 was impedance, h12 was voltage gain, h21 was current gain and h22 was admittance. Here you will see the parameters are opposite to what we had in case of h parameters.

(Refer Slide Time: 13:35)

- Specifically,
 - g_{11} = Open-circuit input admittance
 - g_{12} = Short-circuit forward current gain
 - g_{21} = Open-circuit reverse voltage gain
 - g_{22} = Short-circuit output impedance
- The g parameters are determined similar to the z or y parameters.
- The inverse hybrid model of a two-port network is as shown in the below figure.

$I_1 = g_{11}V_1 + g_{12}I_2$
 $V_2 = g_{21}V_1 + g_{22}I_2$

- Another set of parameter closely related to the h parameters are the g parameters or the inverse hybrid parameters.
- They are used to describe terminal currents and voltages as
$$\begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned}$$
- This can alternatively be expressed in matrix form as,
$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = [g] \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$
- Here the g terms are known as the inverse hybrid parameters or the g parameters.

Now, you can say that

- g_{11} = Open-circuit input admittance
- g_{12} = Short-circuit forward current gain
- g_{21} = Open-circuit reverse voltage gain
- g_{22} = Short-circuit output impedance


Now, here also you can find out the g parameters similar to what we did in case of z or y parameters. Here the inverse hybrid model that is the g parameter model. You can draw like this. If you see here the current source and the resistances are in parallel so you can use nodal analysis in this case.

If you apply Kirchhoff's current law here, then $\mathbf{I}_1 = \mathbf{g}_{11}\mathbf{V}_1 + \mathbf{g}_{12}\mathbf{I}_2$ that is the dependent current source you have got. This you will get in case of this part of the circuit. In case of second part you will see that the resistances in series with dependent voltage source so you will use Kirchhoff's voltage law. When you use Kirchhoff's voltage law you will write $\mathbf{V}_2 = \mathbf{g}_{21}\mathbf{V}_1 + \mathbf{g}_{22}\mathbf{I}_2$. So now, you will see that these two are the same equations which we initially mentioned in case of g parameters. So, these equations can be used to draw the equivalent circuit for g parameters.

(Refer Slide Time: 15:27)

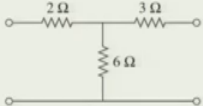EXAMPLE:

❖ Determine the h-parameters for the below circuit?



SOLUTION: The parameters are determined using the equations discussed earlier in the lecture.

Now, let us understand this concept with the help of few examples. Let us take first the example in case of h parameters. So here if you see you have the T circuit which has one 2 ohm resistance, 3 ohm resistance and 6 ohm resistance. Now we need to find out the h parameters, so we will use the basic definition for in case of h parameters.

(Refer Slide Time: 15:54)

• To determine h_{11} and h_{21} , we connect a current source I_1 to the input port and short the output port as in the following figure.

• Since the terminal is shorted, 3 and 6 ohm resistors are in parallel.



$$V_1 = I_1(2 + 3||6) = 4I_1$$

$$h_{11} = \frac{V_1}{I_1} = \frac{4I_1}{I_1} = 4\Omega$$

So we will first determine the h_{11} , h_{21} . How? We will first connect the current source I_1 to the input port and short circuit the output port. So, if you see the updated circuit here you have the T circuit of the, T circuit given in the question. Now, you are making output port short circuit means $V_2 = 0$ in this case and you are applying the current source I_1 to the input port.

Now when you short circuit the output port these 3 ohm and 6 ohm resistance will now be in parallel. So what you can write

$$V_1 = I_1(2 + 3||6) = 4I_1$$

$$h_{11} = \frac{V_1}{I_1} = \frac{4I_1}{I_1} = 4\Omega$$

Now, in the second case what you have to do? Now you will utilize the current division at this point. So, if you see the current flowing in this particular segment that is 3 ohm resistance will be the current which is flowing here will be divided in 3 ohm and 6 ohm resistance so using current division you can find out what is the value of current flowing in the through this particular 3 ohm the resistance. So, what you get using current division? You will get the value of current flowing in this. But here the value of current is also $-I_2$ because the direction of current is opposite.


(Refer Slide Time: 18:12)

- By current division,

$$-I_2 = \frac{6}{6+3} I_1 = \frac{2}{3} I_1$$

$$h_{21} = \frac{I_2}{I_1} = \frac{-\frac{2}{3} I_1}{I_1} = -\frac{2}{3}$$

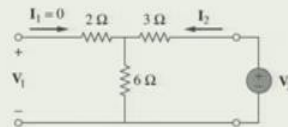- To determine h_{12} and h_{22} , we connect a voltage source V_2 to the output port and open-circuit the input port as in the following figure.



- The 2 ohm resistor is open circuited. Hence, by voltage division


$$V_1 = \frac{6}{6+3} V_2 = \frac{2}{3} V_2$$

$$h_{12} = \frac{V_1}{V_2} = \frac{\frac{2}{3} V_2}{V_2} = \frac{2}{3}$$

- Also,

$$V_2 = I_2(3+6) = 9I_2$$
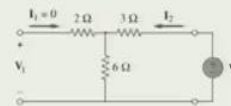
$$h_{22} = \frac{I_2}{V_2} = \frac{I_2}{9I_2} = \frac{1}{9} S$$



You can write

$$-I_2 = \frac{6}{6+3} I_1 = \frac{2}{3} I_1$$

$$h_{21} = \frac{I_2}{I_1} = \frac{-\frac{2}{3} I_1}{I_1} = -\frac{2}{3}$$

Now next, what we have to do? We need to find out the values of $\mathbf{h}_{12}$ and $\mathbf{h}_{22}$. So, what we will do? In this case will connect a voltage source $\mathbf{V}_2$ to the output port and we will keep the input port as open circuit. In this case $\mathbf{I}_1$ will become 0 and we will apply $\mathbf{V}_2$ to the output port. So what will happen now?

So, if you use the Voltage division at this particular point so you will see that the value

$$\mathbf{V}_1 = \frac{6}{6+3} \mathbf{V}_2 = \frac{2}{3} \mathbf{V}_2$$

$$\mathbf{h}_{12} = \frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{\frac{2}{3} \mathbf{V}_2}{\mathbf{V}_2} = \frac{2}{3}$$

Now, also you can say that,

$$\mathbf{V}_2 = \mathbf{I}_2(3+6) = 9\mathbf{I}_2$$


$$\mathbf{h}_{22} = \frac{\mathbf{I}_2}{\mathbf{V}_2} = \frac{\mathbf{I}_2}{9\mathbf{I}_2} = \frac{1}{9} \text{ S}$$

Now, if you see $\mathbf{h}_{12} = 2/3$ and $\mathbf{h}_{21} = -2/3$. So, you can simply say that this circuit is reciprocal circuit.

(Refer Slide Time: 20:48)

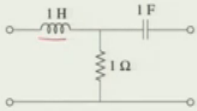EXAMPLE:

✦ Determine g-parameters as function of s for the following circuit?



SOLUTION: The above circuit can be solved using the same procedure discussed in the previous example.

First we need to convert the circuit into s-domain.

Now next, let us try to find the g parameters of the circuit which is given in this figure, here you will see that the circuit is having inductor of one henry capacitor of 1 farad and one resistance of 1 ohm. We have to find the g parameters as a function of s? So, means that we have to convert first this circuit into Laplace domain that is S domain.

(Refer Slide Time: 21:20)

• To determine g_{11} and g_{21} , we connect a voltage source V_1 to the input port and open-circuit the output port as in the following figure.

• Since the terminal is open-circuited, the capacitor need not be considered in calculating I_1 .

$$I_1 = \frac{V_1}{s + 1}$$

$$g_{11} = \frac{I_1}{V_1} = \frac{1}{s + 1}$$

So first we will convert it to Laplace domain that is we will say that 1 henry in s domain we will be s. Capacitor will be represented as 1 by s. And the resistance will remain the same. Now, to find out the value of g_{11} and g_{21} . What we will do? We will connect the voltage source V_1 to the input port and we will open circuit the output port. As we see in this figure. So here now what will happen? I_2 will be zero and we will have current I_1 flowing from the input port.

Now what is the value of I_1 ? I_1 you can simply represent as,

$$I_1 = \frac{V_1}{s + 1}$$

$$g_{11} = \frac{I_1}{V_1} = \frac{1}{s + 1}$$


(Refer Slide Time: 22:33)

- By voltage division,


$$V_2 = \frac{1}{s+1} V_1$$

$$g_{21} = \frac{V_2}{V_1} = \frac{1}{s+1}$$

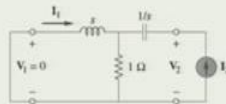- To determine g_{12} and g_{22} , we connect a current source I_2 to the output port and short-circuit the input port as in the following figure.



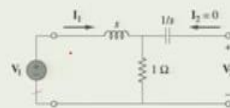- To determine g_{11} and g_{21} , we connect a voltage source V_1 to the input port and open-circuit the output port as in the following figure.
- Since the terminal is open-circuited, the capacitor need not be considered in calculating I_1 .



$$I_1 = \frac{V_1}{s+1}$$

$$g_{11} = \frac{I_1}{V_1} = \frac{1}{s+1}$$

Now next, what do you have to do? You must find out the value of voltage V_2 in terms of V_1 . So you can simply use voltage division here. Because V_2 is applied across 1 ohm resistance, it can be represented in terms of V_1 with the help of voltage division.

So, if you apply voltage division,

$$V_2 = \frac{1}{s+1} V_1$$

$$g_{21} = \frac{V_2}{V_1} = \frac{1}{s+1}$$

Now next, we need to find out g_{12} and g_{22} . We have to connect a current source I_2 to the output port and short circuit the input port. We will short circuit the input port that means $V_1 = 0$ and we will apply I_2 as a current source at the output terminal. Now we need to find out the value of g_{12} and g_{22} .

(Refer Slide Time: 23:44)

- By current division

$$I_1 = -\frac{1}{s+1} I_2$$

$$g_{12} = \frac{I_1}{I_2} = -\frac{1}{s+1}$$

- Also,

$$V_2 = I_2 \left(\frac{1}{s} + s \parallel 1 \right)$$

$$g_{22} = \frac{V_2}{I_2} = \frac{1}{s} + \frac{s}{s+1} = \frac{(s^2+s+1)}{s(s+1)}$$

- By voltage division,

$$V_2 = \frac{1}{s+1} V_1$$

$$g_{21} = \frac{V_2}{V_1} = \frac{1}{s+1}$$

- To determine g_{12} and g_{22} , we connect a current source I_2 to the output port and short-circuit the input port as in the following figure.



- To determine g_{11} and g_{21} , we connect a voltage source V_1 to the input port and open-circuit the output port as in the following figure.
- Since the terminal is open-circuited, the capacitor need not be considered in calculating I_1 .

$$I_1 = \frac{V_1}{s + 1}$$

$$g_{11} = \frac{I_1}{V_1} = \frac{1}{s + 1}$$

So what we will do? We will use the current division. Here if you see the current I_2 is flowing 1 ohm resistance as well as the inductor. So, if you see that the component of current flowing through the inductor the component of I_2 will be nothing but equal to minus of I_1 . So what we have to do? We have to find out the portion of I_2 flowing through the Inductor. So for that we can simply utilize the current division.

So, if you utilize current division,

$$I_1 = -\frac{1}{s + 1} I_2$$

$$g_{12} = \frac{I_1}{I_2} = -\frac{1}{s + 1}$$

Now, we need to find out the relationship between V_2 and I_2 . Value of V_2 is,

$$V_2 = I_2 \left(\frac{1}{s} + s \parallel 1 \right) = 9I_2$$

$$g_{22} = \frac{V_2}{I_2} = \frac{1}{s} + \frac{s}{s + 1} = \frac{(s^2 + s + 1)}{s(s + 1)}$$

So now, whether it is a simple network or if you get the network having that resistance, inductance and capacitance. You can easily find out the parameters that maybe z parameters, y parameters, h

parameters or g parameters. So with this we can close our today's session. In this session we discussed about two important parameters which were h parameters and g parameters. Thank you.