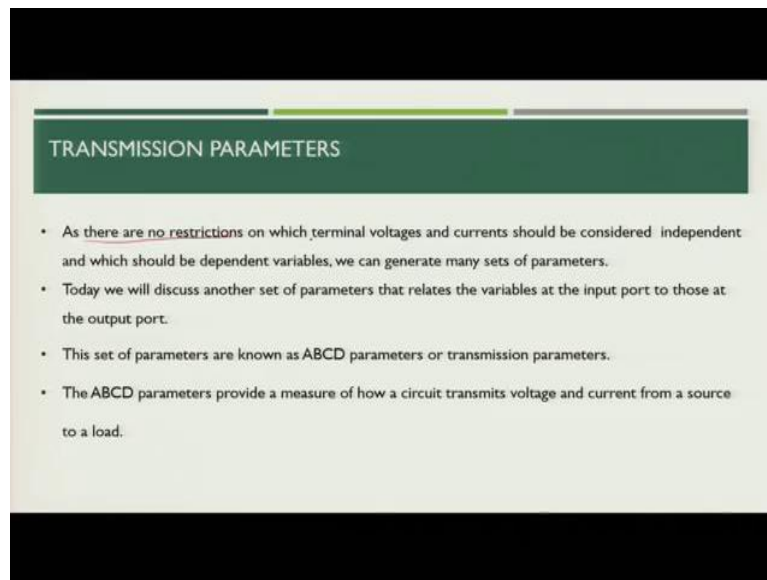


Basic Electric Circuits
Professor Ankush Sharma
Department of Electrical Engineering
Indian Institute of Technology Kanpur
Module 8 - Two Port Network
Lecture 39 - Transmission parameters

Namaskar, so in last few sessions we discussed about a set of parameters, we started with z parameters, then we spoke about y parameters and then we discussed h parameters as well as g parameters. In today's session we will discuss about transmission parameters.

(Refer Slide Time: 0:45)




Let us see what the transmission parameters is. Basically, there are no restrictions on which the terminal voltage and current should be considered independent and which should be dependent. We have 4 variables: V_1 , I_1 and V_2 , I_2 . We can choose any one set of voltage or current as independent parameter and any set we can consider as a dependent parameter.

Based on the choice we can generate many sets of such parameters. We discussed few of the parameters in our previous lectures, so today we will discuss about another set of parameters which relates variables at the input port to those at the output port that means the V_1 , I_1 that is the variable we get at the input port will be related with the output port variable that is V_2 , I_2 .

And these sets of parameters are known as ABCD parameters or you can also say them as transmission parameters. Now ABCD parameter is very important in powered systems because it provides measure of how circuit transmits voltage and current from source to load. So here the relationship between V_1 , I_1 and V_2 , I_2 is important so we will discuss the ABCD parameters today.

(Refer Slide Time: 2:20)

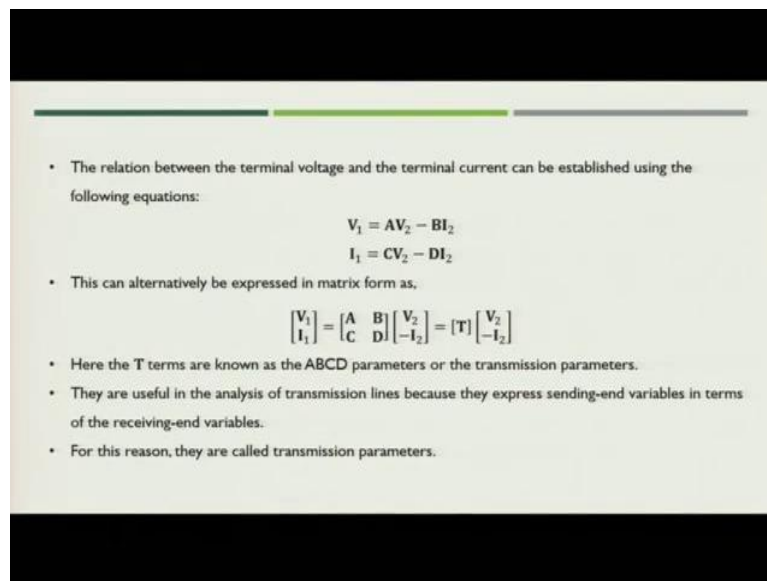

- The relation between the terminal voltage and the terminal current can be established using the following equations:
$$V_1 = AV_2 - BI_2$$
$$I_1 = CV_2 - DI_2$$
- This can alternatively be expressed in matrix form as,
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$
- Here the T terms are known as the ABCD parameters or the transmission parameters.
- They are useful in the analysis of transmission lines because they express sending-end variables in terms of the receiving-end variables.
- For this reason, they are called transmission parameters.

So, how we will relate these ABCD parameters with respect to the circuit variables? The relationship between terminal voltage and terminal current can be stabilised with the help of these two equations. So here the input port voltage that is V_1 can be written in terms of output port voltage and current and it is defined as

$$V_1 = AV_2 - BI_2$$

Similarly, input port current I_1 can be related to V_2 , I_2 and we can write

$$I_1 = CV_2 - DI_2$$

Now in matrix form we can write,


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = [T] \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Now in this case if you see ABCD can be written as capital T and this defines the transmission parameters.

So, either you can write ABCD or you can simply write T, both will represent the same set of ABCD parameters. Now this is very important in the analysis of transmission lines because now they are expressing the sending-end voltages and currents in terms of receiving-end voltage and current so because of this particular property we call them as a transmission parameters.

(Refer Slide Time: 4:17)

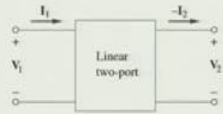- The above equations relate the input variables (V_1 and I_1) to the output variables (V_2 and $-I_2$).
- Notice that in computing the transmission parameters, $-I_2$ is used rather than I_2 , because the current is considered to be leaving the network, as shown in below figure.
- It is so, because in the power systems we consider I_2 as leaving the port.



Now, the above equation which we discussed relate the input variables V_1 and I_1 to output variable V_2 and $-I_2$. So here the important thing is that till now we shown the relationship between V_1 , I_1 and V_2 , I_2 , here we are considering the opposite sign of I_2 because when you see the transmission network you take the simple power system network where the V_1 , I_1 is inside the network and V_2 is the output port voltage and current generally goes out of the circuit.

Because of this specific condition, related to power system network, rather than establishing the relationship between V_1 , I_1 and V_2 , I_2 establishes the relationship between V_1 , I_1 and V_2 , $-I_2$. So, I_2 we generally consider in this direction, but since the load if you connect consumes current rather than providing current so that is why the transmission parameters can best be described by reversing the sign of current I_2 so that is why we use here $-I_2$ rather than I_2 .

(Refer Slide Time: 5:53)

• The values of the parameters can be evaluated by setting $V_2 = 0$ (output port short-circuited) or $I_2 = 0$ (output port open-circuited) in the following equations –

$$V_1 = AV_2 - BI_2$$
$$I_1 = CV_2 - DI_2$$

• The individual parameters are evaluated as follows:

- If $I_2 = 0$, then

$$A = \frac{V_1}{V_2}, C = \frac{I_1}{V_1}$$

- If $V_2 = 0$, then

$$B = -\frac{V_1}{I_2}, D = -\frac{I_1}{I_2}$$

• The parameters A, B, C, and D represent a voltage gain, an impedance, an admittance, and a current gain, respectively.

Now, let us see how we will calculate these parameters. The parameters we can calculate by setting $V_2 = 0$ that means you set the output port as short-circuited or $I_2 = 0$ that means you set output port open circuit. Now, the equations which we saw in terms of ABCD parameters which relates V_1 , I_1 and V_2 , I_2 is like this shown in the slide,

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Now in these equations, if you set $I_2 = 0$ that means you are setting output port as open circuit. In that scenario,

$$A = \frac{V_1}{V_2}, C = \frac{I_1}{V_1}$$

Now, next is the condition when you set $V_2 = 0$ that means you are keeping output port short-circuited, you get,

$$B = -\frac{V_1}{I_2}, D = -\frac{I_1}{I_2}$$

Now, what these parameters are representing? If you see A, A is nothing but a reverse voltage gain, B is nothing but the impedance, C is the admittance and D is current gain.

(Refer Slide Time: 8:20)

- Since the transmission parameters provide a direct relationship between input and output variables, they are very useful in cascaded networks.
- Specifically,
 - A = Open-circuit voltage ratio
 - B = Negative short-circuit transfer impedance
 - C = Open-circuit transfer admittance
 - D = Negative short-circuit current ratio
- The T parameters can also be determined similar to the z or y parameters.
- For reciprocal circuits, $AD - BC = 1$.

So, what we can say that since the transmission parameters provides a direct relationship between input and output variables, they are very useful in cascaded networks that means if you have two networks connected in cascaded fashion so you can say that here the parameters are V_1, I_1 , intermittent parameters you can say V_1', I_1' and output you may have V_2, I_2 as the variables. The transmission parameters will help you to stabilise the relationship in those cases when you have cascaded networks. Analysis of these kind of networks we will see the next lecture when we discuss about the interconnection of various networks, we will see that particular aspect in detail.

For today's lecture we will first discuss the key properties of the transmission parameters, so we will see what are those the properties. First let us see what ABCD defines; A will be your open circuit voltage ratio because this you calculate when you keep output port as open circuit, B is negative short-circuit transfer impedance, C is open circuit transfer admittance and D is again negative short-circuit current ratio.

Now, one of the important properties in case of ABCD parameters is that if you want to see whether the two port network is reciprocal or not, you need to find out with the help of this condition. So, if $AD - BC = 1$, we will say that the circuit is reciprocal. Now, how we will define, determine the values of ABCD? We will define the values of ABCD similar to what we did in case of z, y or in case of h and g parameters, means we will first open circuit the output port and then we will short-circuit the output port and find out the value of ABCD parameters.

(Refer Slide Time: 10:42)

• The last set of parameter is obtained by expressing the variables at the output port in terms of variables at the input port:

$$\begin{aligned} V_2 &= aV_1 - bI_1 \\ I_2 &= cV_1 - dI_1 \end{aligned}$$

• This can alternatively be expressed in matrix form as,

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix} = [t] \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

• Here the parameters are known as the inverse transmission or t-parameters.

• The values of the parameters can be evaluated by setting $V_1 = 0$ (input port short-circuited) or $I_1 = 0$ (input port open-circuited).

Now, next is the opposite of what we discussed till now means the relationship will now be V_2 , I_2 will be related with respect to V_1 , I_1 that means we can also set V_1 , I_1 as independent variables and V_2 , I_2 as dependent variables, in that case the relationship which we get is called as a inverse transmission or inverse T parameters.

We establish this relationship with the help of small abcd because it is opposite to the capital ABCD parameter which we have discussed till now where we establish the relationship of V_1 , I_1 with respect to V_2 , I_2 . In this case the relationship will be V_2 , I_2 with respect to V_1 , I_1 , so here V_1 , I_1 is independent, V_2 , I_2 is dependent.

So, how we will write?

$$V_2 = aV_1 - bI_1$$

$$I_2 = cV_1 - dI_1$$

Alternatively, in the matrix form you can write it like,

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} a & b \\ c & d \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix} = [t] \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

So, we represent this abcd matrix with small t, so we say it as a inverse transmission or a small t parameters. Now, how you will find out the values? You will apply the same criteria which we did in the case of transmission parameters. Here the value of parameters can be evaluated

by now setting $V_1 = 0$ that means (open port is) input port is short-circuited and $I_1 = 0$ that means input port is open circuited.

(Refer Slide Time: 13:07)

The individual parameters are evaluated as follows:

- If $I_1 = 0$, then

$$a = \frac{V_2}{V_1}, c = \frac{I_2}{V_1}$$
- If $V_1 = 0$, then

$$b = -\frac{V_2}{I_1}, d = -\frac{I_2}{I_1}$$
- Specifically:
 - a = Open-circuit voltage ratio
 - b = Negative short-circuit transfer impedance
 - c = Open-circuit transfer admittance
 - d = Negative short-circuit current ratio
- For reciprocal circuits, $ad - bc = 1$.

How you will find the values of parameters? So, when you set $I_1 = 0$, you will get,

$$a = \frac{V_2}{V_1}, c = \frac{I_2}{V_1}$$

Then we will set $V_1 = 0$, to get,

$$b = -\frac{V_2}{I_1}, d = -\frac{I_2}{I_1}$$


So, what you can write? a is nothing but open circuit voltage ratio, what is b ? b is negative short-circuit transfer impedance, because it is basically the relationship ratio between V and I , so it is negative short-circuit transfer impedance, c is open circuit transfer admittance because it is $\frac{I_2}{V_1}$ ratio and then d is negative short-circuit current ratio that is relationship between the ratio between $\frac{I_2}{I_1}$.

So, these small $abcd$ parameters can also be utilised in case of the transmission lines particularly the power systems because here also we get the impact of output variables that is V_2, I_2 on the input variables that is V_1, I_1 . So here we will say that the circuit is reciprocal again if $ad - bc = 1$.

(Refer Slide Time: 15:10)

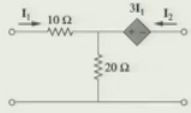EXAMPLE:

❖ Determine the transmission parameters for the below circuit?




SOLUTION: The parameters are determined using the equations discussed earlier in the lecture.

Now, let us a couple of examples to understand these parameters. Let us see there is one circuit as given in the figure, we have two resistances and one dependent voltage source and we need to find out the transmission parameters for this particular circuit so we will use the equations and we will set first voltage the output port as open circuit and then short-circuit to find out the circuit parameters.

(Refer Slide Time: 15:51)

• To determine A and C, we connect a voltage source V_1 to the input port and open the output port as in the following figure.

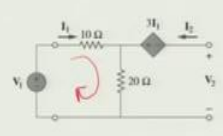
$$V_1 = I_1(10 + 20) = 30I_1$$
$$V_2 = I_1(20 - 3) = 17I_1$$

So now, in first case what we are doing? We are opening the output port and the input port we have a voltage connected that is V_1 . And when we have this particular condition, we put these values in the ABCD equation that is V_1, I_1 equations.

From this figure,

$$V_1 = I_1(10 + 20) = 30I_1$$

$$V_2 = I_1(20 - 3) = 17I_1$$

So, V_1 and V_2 we have got with respect to input current I_1 .

(Refer Slide Time: 17:47)

• Thus,

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = 1.765$$

$$C = \frac{I_1}{V_2} = \frac{I_1}{17I_1} = 0.0588S$$

• To determine B and D, we connect a voltage source V_1 to the input port and short the output port as in the following figure.

So, what you can write now with the help of equations for ABCD parameters, we know that,

$$A = \frac{V_1}{V_2} = \frac{30I_1}{17I_1} = 1.765$$

$$C = \frac{I_1}{V_2} = \frac{I_1}{17I_1} = 0.0588S$$

Now, next we have found the value of A and C, next we need to find out the value of B and D. So for that what we have to do? We have to short-circuit the output port and apply a voltage V_1 in the input port and solve the equations.

(Refer Slide Time: 19:19)

• At node a in the circuit, KCL gives,

$$\frac{V_1 - V_a}{10} - \frac{V_a}{20} + I_2 = 0$$

• But $V_a = 3I_1$ and $I_1 = (V_1 - V_a)/10$. Using these we get,

$$V_a = 3I_1 \text{ and } V_1 = 13I_1$$

• Substituting the above values in the KCL,

$$I_1 - \frac{3I_1}{20} + I_2 = 0 \Rightarrow \frac{17}{20}I_1 = -I_2 \Rightarrow I_1 = -\frac{20}{17}I_2$$

• Therefore,

$$D = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176, \quad B = -\frac{V_1}{I_2} = \frac{-13I_1}{\left(-\frac{17}{20}\right)I_1} = 15.29\Omega$$

You will, if you see the circuit you can apply Kirchhoff current law at this node, let say the voltage at this node is V_a and we apply Kirchhoff current law at this node, so what we can write? We can write the value of $I_1 = (V_1 - V_a)/10$ and the current is going inside, so we are taking current going inside as positive or current going outside as negative. So applying KCL,

$$\frac{V_1 - V_a}{10} - \frac{V_a}{20} + I_2 = 0$$

Now, if you see this circuit you can say that V_a is nothing but equal to voltage the of dependent voltage source because this is the voltage which is applied across the 20 ohms resistance and the voltage which is applied across 20 ohms resistance is nothing but V_a . So, what you can write? You can write $V_a = 3I_1$ and from this section we have already seen that $I_1 = (V_1 - V_a)/10$. So we have these two information in our hand, so we can now say the value of $V_a = 3I_1$ and $V_1 = 13I_1$.

Substituting the above values in the KCL,

$$I_1 - \frac{3I_1}{20} + I_2 = 0 \Rightarrow \frac{17}{20}I_1 = -I_2$$

Therefore,


$$D = -\frac{I_1}{I_2} = \frac{20}{17} = 1.176, \quad B = -\frac{V_1}{I_2} = \frac{-13I_1}{\left(-\frac{17}{20}\right)I_1} = 15.29\Omega$$

So, using the technique of putting output port open circuit and short-circuit one by one you can easily find out the values of ABCD parameter.

(Refer Slide Time: 23:10)

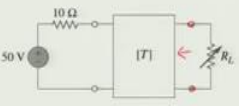EXAMPLE:

✦ The transmission parameters for the below circuit are $\begin{bmatrix} 4 & 20\Omega \\ 0.1S & 2 \end{bmatrix}$. The output port is connected to a variable load for maximum power transfer. Find R_L and maximum power transferred?




SOLUTION: The parameters are determined using the equations discussed earlier in the lecture.

Now, let us see another example where the transmission parameters are given, so here you see the transition parameters in the matrix form, the output port is connected to a variable load for maximum power transfer. Now, what we must do? We need to find out the value of R_L at which maximum power transfer will take place and we need to find out how much maximum power will be transferred.

So, what we will do? We will utilise the same process which we discussed, we will first put output port open circuit and then short-circuit to find out the relationships and when you are required to find out the value of R_L for maximum power transfer, the objective will be to find out the Thevenin equivalent of the circuit which is left to the R_L . This segment needs to be represented as Thevenin equivalent. We will use ABCD parameters and find out the value of V_{Th} and R_{Th} so that we can find out the value of maximum power to be transferred.

(Refer Slide Time: 24:26)

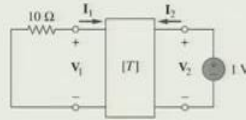
- We need to determine the Thevenin equivalent (Z_{Th} and V_{Th}), at the load or output port.
- We find Z_{Th} using the below circuit.



- Our goal here is to set $Z_{Th} = V_2/I_2$
- This can be found out using the ABCD parameters.

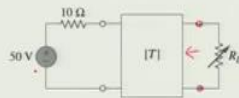EXAMPLE:

- The transmission parameters for the below circuit are $\begin{bmatrix} 4 & 20\Omega \\ 0.1S & 2 \end{bmatrix}$. The output port is connected to a variable load for maximum power transfer. Find R_L and maximum power transferred?



SOLUTION: The parameters are determined using the equations discussed earlier in the lecture.

Now, first what we need to do? We must determine the Thevenin impedance and Thevenin voltage, first let us find out the value of Thevenin impedance. So for that what we have to do? To find out the value of Thevenin impedance we need to short-circuit all the independent voltage source, so you here this independent voltage source we will short-circuit and then to find out the value of Z_{Th} we will apply one voltage at the output port so that we can find the value of V_2 , so when you get the value of V_2 and I_2 you can simply find out the value of Z_{Th} . So this relationship V_2 and I_2 we will get with the help of ABCD parameters.

(Refer Slide Time: 25:20)

• Substituting the given parameters we obtain,

$$V_1 = 4V_2 - 20I_2$$
$$I_1 = 0.1V_2 - 2I_2$$

• At the input port $V_1 = -10I_1$

• Substituting this relation in the first equation, we get,

$$-10I_1 = 4V_2 - 20I_2 \Rightarrow I_1 = -0.4V_2 + 2I_2$$

• Applying the above value to the second equation of the ABCD parameters, we get,

$$-0.4V_2 + 2I_2 = 0.1V_2 - 2I_2 \Rightarrow 0.5V_2 = 4I_2$$
$$Z_{Th} = \frac{V_2}{I_2} = \frac{4}{0.5} = 8\Omega$$

So, if you put the values of A, B, C and D you can simply write

$$V_1 = 4V_2 - 20I_2$$

$$I_1 = 0.1V_2 - 2I_2$$

At the input port $V_1 = -10I_1$

Substituting this relation in the first equation, we get,

$$-10I_1 = 4V_2 - 20I_2 \Rightarrow I_1 = -0.4V_2 + 2I_2$$


Applying the above value to the second equation of the ABCD parameters, we get,

$$-0.4V_2 + 2I_2 = 0.1V_2 - 2I_2 \Rightarrow 0.5V_2 = 4I_2$$

$$Z_{Th} = \frac{V_2}{I_2} = \frac{4}{0.5} = 8\Omega$$

(Refer Slide Time: 26:40)

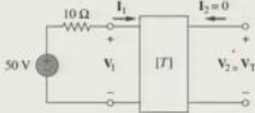- To determine V_{Th} , we use the below circuit.



- At the output $I_2 = 0$ and the input port $V_1 = 50 - 10I_1$
- Applying the above to the ABCD parameter equations,

$$50 - 10I_1 = 4V_2$$

$$I_1 = 0.1V_2 \Rightarrow V_2 = 10I_1$$

Now, next task is we need to find out the value of V_{Th} , so for finding out the value of V_{Th} the value of current $I_2 = 0$ because this port will be open circuited and the input port the value of $V_1 = 50 - 10I_1$.


Now we apply this to ABCD parameter equations so what we can write? We can write

$$50 - 10I_1 = 4V_2$$

$$I_1 = 0.1V_2 \Rightarrow V_2 = 10I_1$$

(Refer Slide Time: 27:49)

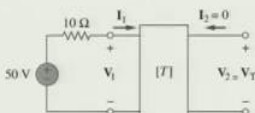- To determine V_{Th} , we use the below circuit.



- At the output $I_2 = 0$ and the input port $V_1 = 50 - 10I_1$
- Applying the above to the ABCD parameter equations,

$$50 - 10I_1 = 4V_2$$

$$I_1 = 0.1V_2 \Rightarrow V_2 = 10I_1$$

$$50 - 10I_1 = 4V_2 \Rightarrow 50 - V_2 = 4V_2$$

$$5\mathbf{V}_2 = 50 \Rightarrow \mathbf{V}_2 = 10$$

Thus,

$$V_{Th} = \mathbf{V}_2 = 10\text{V}$$

For maximum power transfer,

$$R_L = Z_{Th} = 8\Omega$$

The maximum power transfer is therefore,

$$P = I^2 R_L = \left(\frac{V_{Th}}{2R_L} \right)^2 R_L = 3.125\text{W}$$

So, with this we can close our today's session in which we can discussed about the transmission parameter and inverse transmission parameter. In next lecture we will discuss about the interconnection of various two-port networks which we have discussed in last 4 sessions, thank you.