

Course name- Analog VLSI Design (108104193)
Professor – Dr. Imon Mondal
Department – Electrical Engineering
Institute – Indian Institute of Technology Kanpur
Week- 2
Lecture- 8, Module-2

Now, we will come back, we just now saw that starting from first principles and some assumptions, some incremental assumptions, some exact, some assumptions which we just blew out of a hat, we could come up with a desirable IV characteristics of a two-port network, which can give us amplification of power, right. So now, as it turns out, as it turns out, there are two-port network, there are devices, right, which can be, which can be arranged in this form of two-port networks, which have characteristics similar to whatever we just plotted, right. A case in point is a device called MOSFET, right. So, as it turns out, if we, inside this two-port network, we assume that we have a MOSFET and we can further assume that one terminal of the MOSFET is shared between the input and the output and we denote this terminal as V_2 , denote this terminal as V_1 and denote this current as I_1 and denote this current as I_2 , right. Don't bother about the particular symbol as of now, but if we simply denote these currents and voltages as I_1 , I_2 , V_1 , V_2 as shown here, as it turns out, the I_1 , V_1 characteristics, even if before sketching the I_1 , V_1 characteristics, let me simply write that I_1 is equal to 0 for all V_1 and V_2 . This is just how the device is, ok.

So, that makes life pretty simple, if since I_1 is equal to 0, right, so Y_{11} is equal to 0 and Y_{12} equal to 0. So, we do not have to bother about different slopes at different operating points, right, as far as the input characteristics is concerned, right, as far as the slope between I_1 and V_1 and I_1 and V_2 are concerned. However, I_2 is governed by this following equation, simply say that this is equal to some constant β times V_1 minus some constant V_{th} whole square, right. This is as long as V_1 is greater than equal to V_{th} and V_2 is greater than equal to V_1 minus V_{th} .

So, this is just how the current equations are, right. So, if I sketch the I_2 versus V_1 characteristics, right, what will I get? So as long as if I, let us say, I mark out every point V_{th} , all these characteristics is saying is that above, as long as V_1 is more than V_{th} and V_2 satisfies this condition, right, V_2 is greater than V_1 minus V_{th} , then if I keep increasing V_1 , right, I should get a parabolic slope, parabolic looking curve, ok. What happens, this is for let us say certain V_{2q} , V_2 equal to certain V_{2q} . What happens if I, so this will have to also ensure that V_{2q} is greater than equal to $V_1 - V_{th}$ for all range of V_1 that I have plotted it with, plotted the curve for, ok. So, what happens if I change V_2 , what happens if I change V_2 from V_2 equal to V_{2q} plus small V_2 ? What do you think

will happen if we follow the equation that we have just sketched? Note that this equation is independent of, this current I_2 is independent of the voltage V_2 , right.

So whatever happens at V_2 will have no bearing on the current I_2 , which means it will follow the same curve, ok. So as long as these two conditions are met. What about the output characteristics of I_2 versus V_2 ? What is this equation telling you? This equation is telling you that for certain V_1 , so V_1 equal to V_{1q} , right, I will have certain I_2 and the value of I_2 will be say I_{2q} which is equal to $\beta V_{1q} \text{ minus } V_{th} \text{ whole square}$, ok. And this value will be constant as long as, as long as what? This equation is telling you that for certain V_1 , so V_1 equal to V_{1q} , right, I will have certain I_2 and the value of I_2 will be say I_{2q} which is equal to $\beta V_{1q} \text{ minus } V_{th} \text{ whole square}$, ok. And this value will be constant as long as, as long as what? As long as V_2 is, as long as V_2 is greater than $V_1 \text{ minus}$, this is $V_{1q} \text{ minus threshold voltage}$, right.

So at smaller values of, as you decrease V_2 , right, as you decrease V_2 , maybe at some switch or some point here, you meet V_2 equal to $V_{1q} \text{ minus special voltage}$ and the boundary of the V_{1q} . The validity of this equation is, is this, is this line where V_2 is equal to $V_{1q} - V_{th}$, ok. So, what happens if I increase V_1 to V_1 equal to $V_{1q} \text{ plus small } v_1$? What happens then? Will I_2 change? Surely, I_2 is going to change because now I have a new V_1 , right. So I_2 will increase to a different value and what will be this increase? This increase will be equivalent to the increase that you, you plug in that new V_1 into the, into the current equation, right, you plug in the new V_1 into the current equation, and you will get an increase. Or in other words, if V_1 , if you assume that the V_1 is small enough, if you assume the V_1 is small enough where you can neglect the higher order terms, that is if you expand this quadratic, if you expand this whole square term, you will get a square law, you will get a, you will get a square term, you will get a linear term, you will get a constant term, right.

So if you assume that the quadratic terms are small enough to be neglected, this increase, increase in I_2 will be how much? This increase in I_2 will be Y_{21} times V_1 , right. And again, what will be the range of validity for this flat line? This will be L , this new $V_{1Q} \text{ plus } V_1 \text{ minus } V_{th}$, right, okay. Now note that this equation does not tell us anything about what is going to happen, what is going to happen below V_2 , below the condition where you breach this limit of V_2 to be greater than equal to $V_1 \text{ minus } V$, right. As it turns out, as it turns out, there is also a nice flow from expression for that. But I mean, even if we, even without going there, we know that this is going to, this is going to somehow dive, somehow dive into and go to 0, right.

That is all we know at the moment. We do not know the exact equation which will result in this diving, right. But we know that it will, it is going to, it is going to go to 0,

okay. So even before, even before moving on, let me make couple of very important points here. As it turns out, these, this IV characteristics that we have sketched here are particular to a MOSFET.

But note that the IV characteristics that we arrived at, right, the desirable IV characteristics that we arrived at are not particular to a MOSFET. That is particular to any device, right, that is particular to any device that has, that you can make, that you can, that you need to make an amplifier, right. So if you go down the history, and you will see that before MOSFETs, there were BJTs, right. BJTs are still present, they are still used, but not as widely used as BJT, as MOSFETs. But however, still there are BJTs whose input-output characteristics look almost similar to the whatever we see here.


Even before BJTs, there used to be vacuum tubes, right, whose input-output characteristics again, looked almost exactly what we came up with from scratch. Tomorrow, if there are new devices, you will see that you have FinFETs, get all around devices, gallium arsenide, gallium arsenide, and so on and so forth. All of them fundamentally have similar IV characteristics. So, it is not a coincidence that all of them have similar IV characteristics. In fact, the story goes the other way round.

The logic goes the other way round. What is the logic? The logic is in order to get an amplifier which can amplify power, we need these type of, we need devices which have these type of IV characteristics. Now as a circuit designer, if you lay down the law and say that I need these kind of devices which have these kinds of or rather I need devices which have these kinds of IV characteristics, then you go to your, then we go to our device colleagues and ask them, hey see, this is what we need to get a power amplification. Can you make a device and give it to us? They say sure enough, not only one, we can give you different flavors of devices whose IV characteristics look like this. Now note that the devices that I named before, right, right from vacuum tubes to BJTs to MOSFETs to Gallium Arsenide FETs, JFETs and pinFETs and so on, all of them can have completely different underlying physics, can have completely different transport phenomena as to how the current flows inside the device, right.

However, for the purpose of designing a circuit at the level in which this course will concentrate on, you do not need to know how the transport of current or how the transport of the electrons or the holes inside the devices take place, right. All we need to know is the, is the, is the underlying IV characteristics. Now note that these underlying equations of the IV characteristics will also depend on the type of, type of devices that we are, that one is going to use. However, however, they will look similar, they will look, they will look similar in terms of their incremental properties will look similar and what will they look like? They will look like Y_{11} will be close to 0 or exactly 0, Y_{12} will be

close to 0 or exactly 0, Y_{22} will be close to 0 or exactly 0 and Y_{21} has to be very high, right. If you do not have these properties in a device, you cannot make a good amplifier.

Now as it turns out, all the devices that we talked about, right, are also three terminal devices. However, you can make a two-port network with a three terminal device also, right. So, all these devices are three terminal devices, and they have input output characteristics which are, which mimic, which mimic the conditions that we have been discussing till now. In this particular course, we will deal solely with MOSFETs and we will from the next class onwards or from the next lecture onwards, we will concentrate on the operation of a MOSFET under different conditions, under different operating conditions, like what happens if I increase V_1 , what happens if I increase V_2 , what happens if I decrease V_1 or decrease V_2 and what are the particular governing current voltage equations that we need to, that we need to deal with, but in doing so, we should not lose sight or you should not lose sight of the fact that if tomorrow you are given a different device, right, you should not throw up your hands and say I did not study, I did, I mean, the course that I took was only on MOSFETs, so I cannot, I cannot design circuits with these. You should, what you should imbibe is the thing that you should take away from this course is the fact that the first thing that you have to do is something somebody gives you a device is to, is to plot the IV characteristics and see whether in some portion of the IV characteristics are you able to satisfy those four conditions, right, simultaneously, right.

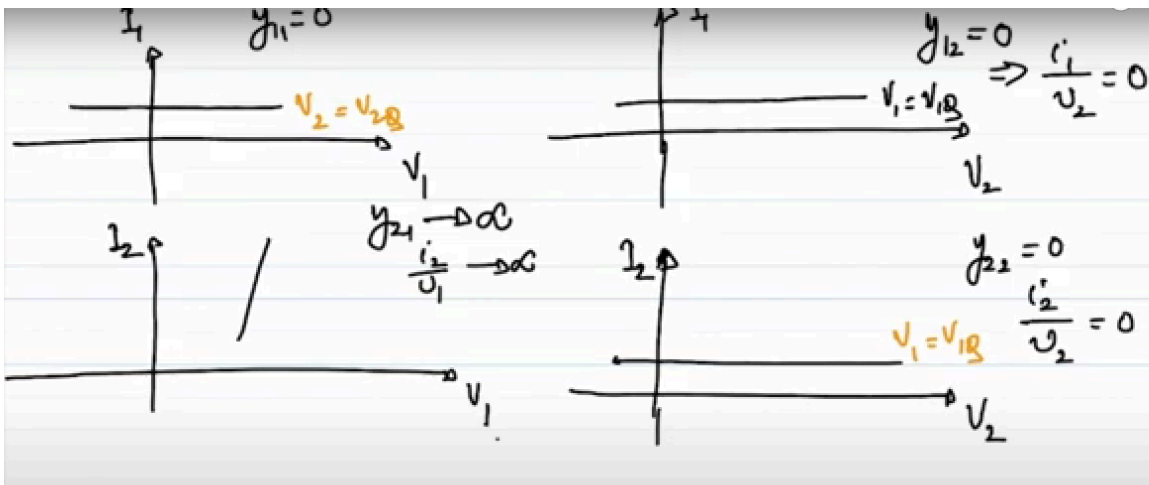

So you should be able to satisfy the conditions of Y_{11} should be equal to 0 or close to 0, Y_{12} should be equal to 0 close to 0, Y_{21} should be as high as possible and again Y_{22} should be close to 0 or equal to 0, right. As long as the new device that you are encountered with satisfy these four conditions, right, you should be able to make a decent amplifier. Now the details of when the current voltage characteristics change from the idealized case will depend on the device physics or on the, which in turn governs the

current voltage equations. Then at the second order level, you need to know the exact current voltage equations which are going to affect your design, right. But as long as you know, as long as you know what your expectations are and the fact that the device that you are dealing with meets your expectations, you should be able to design an amplifier.

And from the next lecture onwards, we will concentrate on designing one such amplifier, right, using MOSFETs. Thank you.