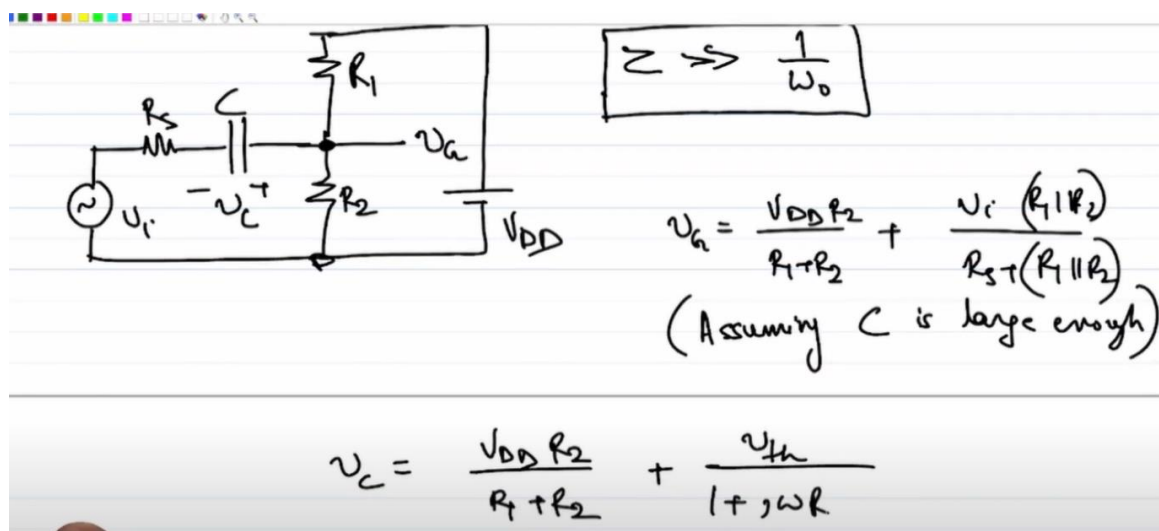


Course name- Analog VLSI Design (108104193)
Professor – Dr. Imon Mondal
Department – Electrical Engineering
Institute – Indian Institute of Technology Kanpur
Week- 5
Lecture- 15, module-02

Welcome back. So, what is the conclusion of whatever we discussed to quickly recap. So, if you have a structure like this, what we want, we want the capacitor to act as a short circuit at the frequency of interest right. And so, what will be the, what will be the voltage at this node, what will be the total voltage v_g , the total voltage v_g will be and I can use superposition because completely linear network, what will be the superposition of this B, we have two sources one is V_{dd} , one is V_i right. So, if I assume in case of superposition, I take one source at a time and de-energize the other source, both are voltage sources, de-energizing a voltage source is essentially equivalent to, is essentially equivalent to shorting it. Let me connect everything together so that it makes a bit more sense right.

So, if I assume that V_i is shorted, what will v_g be? v_g will be V_{dd} times R_2 by R_1 plus R_2 and if I subsequently assume V_{dd} is shorted, what will be v_g ? This will be, if I further assume that the C is large enough to be treated as short circuit, so this will be approximately equal to V_i times R_1 parallel R_2 by R_s plus R_1 parallel R_2 right. This is assuming C is large now right. So, what is the assumption, what is the total voltage across the capacitor? What will be the total voltage that we will see across the capacitor? Let me mark the voltage in this direction, let us say V_c . So, what will be the total voltage across the capacitor? V_c will be again I can do superposition right.



So, what will be, if I assume V_i to be de-energized, V_c will be what? V_c will be simply

V_{DD} times R_2 by R_1 plus R_2 and this is expected because that was the quiescent voltage that we anyways wanted. Now what is the effect of V_i ? Again because I am using superposition, I can short V_{DD} , by short V_{DD} R_1 and R_2 come to come parallel to each other. What will be the voltage then? Voltage across capacitor will be nothing but whatever we saw in the earlier example will be $V_{Thevenin}$ by $V_{Thevenin}$ by $1 + j\omega R_{th} C$ ok. And $V_{Thevenin}$ in our case was V_i right, $V_{Thevenin}$ for the capacitor was V_i and if this is omega naught, if C is much much greater than 1 by omega naught R_{th} right, then we see will be R_2 by R_1 plus R_2 . So, as you see if the if you if we if we follow the rules right, if we if we if follow the sizing rules of the capacitor, what we will see is that the capacitor is only holding is only holding the DC portion of the information right.

So, this is the DC portion of the information and this is the AC portion of the information right. So, this is amplitude or rather this is the response voltage response across the capacitor right, voltage response across the capacitor at steady state. When I say steady state what I mean is that you have your V_i is a sinusoid, you have applied the sinusoid and you have waited for infinite time, no transients we are talking if there is no transient effects that we are talking about here. So, the voltage across the capacitor is V_i by 1 plus or rather the voltage response of the capacitor is V_i by $1 + j\omega R_{th} C$ and this the other one this this one is essentially the bias at that bias voltage of the capacitor is holding right, the DC bias or DC voltage we simply say DC voltage. So, as you see the capacitor is doing two jobs here, one is it is holding the DC voltage across it and also it is allowing the AC voltage to go through ok great.

$$V_C = \boxed{\frac{V_{DD} R_2}{R_1 + R_2}} + \boxed{\frac{V_i}{1 + j\omega R_{th} C}}$$

DC voltage \leftarrow \leftarrow Voltage response across the capacitor @ steady state

If $C \gg \frac{1}{\omega_0 R_{th}}$

$$V_C = \frac{V_{DD} R_2}{R_1 + R_2}$$

So, now that we have the biasing picture at the input side, let us redraw our common source amplifier right. So, what is our common source amplifier now? Let us go to a new page. The common source amplifier now at least at the input side is looks to be sorted. So, this is V_{DD} and this is R_n . So, is I mean seems like if I size C R_1 and R_2 accordingly right, it looks like I mean all our problems are solved we should be and if we take the output, if we take the output from this node it looks like we are good to go right, but the question is are

we? As it turns out there is a slight bit of complication and the complication is again a practical one that remember I told you that there is a problem that you cannot have access to both terminals of a source right.

Similarly, you need not necessarily have access to both terminals of a load because what is this RL? What is this RL? This RL might not be might not be a actual register, this RL might be the input impedance of another stage that it is driving. So, which essentially means that you only have access to one terminal of the load and not the other terminal that you will just connect it to Vdd right. So, essentially the problem is we seldom have access to both terminals of RL ok. So, which means that your RL is just like your source your RL one terminal you can assume it to be implicitly grounded right and you have access to this terminal which means you cannot put RL between the Vdd and the drain of the transistor ok. So, now what should we do? Input side we did something to figure, but what should we do with the output side? Note that the first condition, what is the first condition? The first condition is that we need to ensure that the transistor is in saturation right without that we do not have any story to tell right.


Without that you cannot make the amplifier work like that or you cannot make the transistor work like an amplifier simply because I mean go back to the small signal model of an amplifier the gds or the Y22 or the gds has to be equal to 0. If the transistor is not in saturation that is not possible hence it is a big problem right. So, what is a again if we go back to our drawing boards what is a easiest way of ensuring the transistor is in saturation? One is to say that I will directly connect and that train to train to the Vdd ok right. So, then what should we do with RL? How should I connect how should I connect RL because ultimately what is the what is the incremental equivalent of this? What is the incremental current the increment the what will be the total current of the transistor? Total current will be I_D plus an incremental current right some dI or let me say small i_d . The small i_d will be g_m times V_g right g_m times V_g where s is grounded.

So, it is basically g_m times V_g and if you are done a good job in in biasing the input side V_g will be approximately equal to V_i then essentially the incremental current distilled i_d plus capital i_d plus small i_d or let me say i_{DQ} plus small i_d , but where will this i_d flow? Where will this incremental current flow? This incremental current clearly will flow into the into the Vdd right because incrementally this Vdd is in a short circuit right. So, this i_d will mark i_d with my gender color. So, this clearly this i_d will flow into the Vdd and whatever you do with RL you will not be able to generate any voltage across RL right. So, earlier how do we solve this problem? We put the RL in the path of i_d , we put the RL between the drain and the Vdd. So, the i_d had no other option, but to flow through RL since i_d was flowing through RL it was generating a voltage proportional to i_d and we were we were reading that voltage out, but now as I said since we do not have access to both

terminals of RL we cannot put RL in the in the path of i_d .

So, what is the solution? Ok. So, if this cannot be done this cannot be done firstly I mean firstly the first things first we cannot expect to get anything out of this if drain is connected to Vdd right. If drain is connected to Vdd all the incremental current i_d right this magenta i_d will always go to Vdd. So, we have to first things first we have to prevent that. So, how do you prevent that? How were you preventing it earlier? From drain being shorted to Vdd we prevented that earlier by connecting a resistor in that case it was RL, but in this case let me say it is not RL let me call this R_d I mean nothing innovative D it stands for drain I am connecting it between drain and Vdd.


So, I am calling it calling it R_d ok. So, now this drain what will be the what will be the drain voltage I mean this is nothing, but the common source amplifier with R_d instead of RL. So, what will be the drain voltage here? What will be the total drain voltage here? This will be V_{DD} minus $i_d R$ plus i_d times RL correct ok, but ultimately what do I want? I want I want the i_d to flow into flow into RL right. I want i_d to flow into RL because ultimately I want the voltage to develop across RL right. So, how do you think can you can you suggest a way so that if not the full i_d part of the i_d flows into RL well one way to say is that I can I have one possible way is simply to connect the drain of the transistor to RL right.

 

Then one might be tempted to say that this part of this i_d part of this i_d will flow into RL and part of this i_d will flow into R_d right. So, if not I mean earlier we are not getting anything now we are getting something this might be a this might be a decent solution right, but even before jumping into that conclusion let me let me let me now point you point out a important problem with this with this type of if you simply connect RL to if you simply connect RL to the drain right. So, what is the problem? Let us let us start again from the beginning let us assume the RL was not connected what was the what is the what is the voltage? So, what is the voltage at the drain? The voltage at the drain is V_{DD} minus this right. So, let us let us forget about let us forget about the incremental i_d right. So, the voltage quiescent voltage let me call this V_d .

So, V_{dq} was V_{DD} minus i_{dq} times this is not RL this is R_d I am sorry R_d ok. So, what is

the voltage across R_L ? Let me call it V_{RL} what is V_{RL} ? V_{RLQ} is equal to 0 right if V_{RL} is equal. Now, what will happen if I connect these two? What will happen if I connect these two nodes? If I connect V_d and V_{RL} forget about the incremental forget about the incremental current what about the DC current? What will happen to the DC current? So, clearly some part of the DC current some part of the DC current that was coming out of coming through this will now flow into flow into R_L right. What is the problem? The problem is then the value of V_d will drop the drain voltage will drop because now you are essentially loading the drain you are essentially loading the drain voltage with loading the drain with R_L in the in the biasing picture also right. So, why again why are you loading? Because the moment you are connecting R_L to V_d you are drawing current out of that node right.

 

$$V_{DQ} = V_{DD} - I_{DQ} R_D$$

$$V_{RLQ} = 0$$

R_L is loading M_1 . \therefore DC Q-point will change

So, what is the crux of loading? If you are drawing current out of a node after you have connected a load the load resistance is loading the node. So, here you are using R_L you are loading your common source amplitude right. And what will happen if you load it will draw some current out whatever biasing you had envisaged earlier right after carefully writing out the equations will go for a toss the transistor will might not remain in saturation if you not careful right. So, what is the what is the problem? The problem is R_L is loading M_1 right R_L is loading M_1 therefore dc Q-point will change it is loading in the dc picture as well right ok. So, let us draw this redraw.


So, let us see what is the problem. So, let us forget about i_d for the time small i_d for the time being the problem is this is loading right. So, what is the solution? So, let us say I knew a priori let us say I knew a priori the voltage at V_d is V_{dQ} right. So, let us say I knew this voltage is V_{dQ} and somehow after I figured whatever V_{dQ} was right I put a battery let me do this. So, let us say I knew this voltage is V_{dQ} V_{dQ} equal to i_d I mean V_{DD} minus i_d

Rd right and I somehow I figured out what the battery what the value was and I put a battery V_{DQ} between I mean in series with R_L right.

So, what is the voltage here now? The voltage here now is V_{DQ} right. So, now if I connect these two nodes what is going to happen do you think any current will flow through that blue line to that blue where no right because both sides of the where where at identical potential to start off right. So, there is no need current only flows from a higher potential to lower potential in order to equalize the in an attempt equalize the difference in voltages. Since there is no difference in voltage no current no DC current will flow right. Since no DC current will flow my the quiescent point of the M1 will not get will not get happened right ok great.

So, let me let me make it a slightly better drawing. So, what is the solution that we come up with? The solution that we come up with is put a identify whatever voltage V_D was V_{DQ} and put that put that value would put that put a include a battery of exactly that value V_{DQ} . Now some of you might get angry with me and say that a half the lecture you have told us that I mean I cannot use a floating battery and how come I am using a floating battery certainly. You are absolutely right we cannot use a floating battery, but now we have a replacement. What is the replacement? An infinite capacitor right.


So, instead of using V_{DQ} what will we use? We will use a we will use a capacitor right. So, we will use a capacitor let me call this C_2 and let us assume C_2 tends to right. So, if I use C_2 and I use C_2 tends to infinity right. So, what will be the voltage what will be the voltage across C_2 ? What will be the voltage across C_2 under DC condition right. So, voltage V_{C2Q} that is a V_{C2Q} the q stands for quiescent what will be V_{C2Q} ? So, clearly at DC capacitor is open circuited no current will flow.

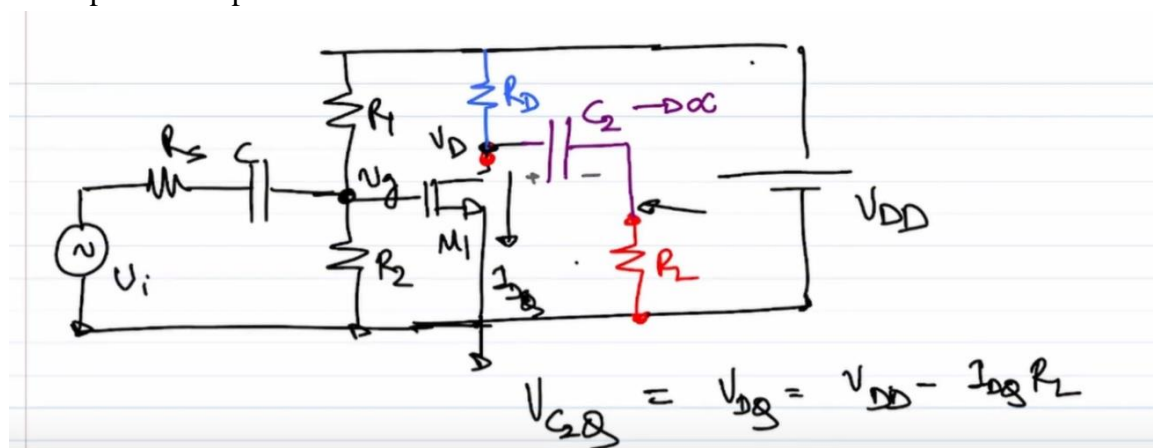

So, what is this voltage? That voltage is 0 what is V_D ? V_D is V_{DQ} right. So, V_{C2Q} is V_{DQ} which is V_{DD} minus $I_{DQ} R_L$ right. So, the so note that by putting a capacitor we are not disturbing the we are not disturbing the quiescent point of the other transistor right. If we can ensure that we are not disturbing the quiescent point of the transistor that is a good start

right. The RL is no longer loading the quiescent point of your a quiescent operation of your transistor ok great.

 So, what about the AC condition right. So, let us sketch the AC equivalent right before we go into the AC condition let us sketch the AC equivalent. Let us assume the gate is at V_g what is the equivalent of the transistor?



The transistor is a g_m a voltage control current source the source is grounded right source is grounded. So, we do not have to bother too much on top I have R_d right. What is what should I do with the other side of the R_d ? Other side of the R_d should be grounded because again V_{dd} right.

So, this grounds from here I go at the drain what do I have? I have a capacitor an infinite capacitor an infinite capacitor in a incremental sense is a is a short circuit right. So, the capacitor shorts then what we end up with we end up with let me use a different color for R_d because that is how I have sketched it in the figure on the top ok. So, what will be the value of this g_m ? It will be g_m times V_{gs} right in this case hence it will be g_m times V_g ok and from across which node am I interested in taking the output? Clearly I am interested in taking the output across R_L right. So, this is my V_o this is V_o ok. So, if that is the case what is the incremental V_o ? So, note that in this case R_L and R_d are in parallel to each other right.

Since R_L and R_d in parallel to each other all the incremental current $g_m g_m V_g$ is flowing out of the parallel combination of R_d and R_L and I am taking by taking the voltage across R_L I am essentially taking the voltage across R_L and R parallel combination of R_L and R_d for the purpose of this analysis right.

$$\begin{aligned}
 v_o &= -g_m v_g (R_D \parallel R_L) \\
 &\approx -g_m v_i (R_D \parallel R_L) \\
 \Rightarrow \boxed{\frac{v_o}{v_i} &= -g_m (R_D \parallel R_L)}
 \end{aligned}$$

So, V_0 becomes equal to minus g_m times V_g R_D parallel R_L ok and if you bias your input side properly this becomes minus g_m times V_i times R_D parallel R_L ok which means the incremental gain V_0 over V_i becomes minus g_m times R_D parallel ok. So, this is so this is clearly this is not as good as minus g_m times R_L which we could have gotten if we had plugged R_L in instead of R_D if we had the option of having access to both terminals of R_L and I could have plugged R_L in between the drain and the and V_{dd} , but we could not do so and because and what was the replacement? The replacement the alternate architecture was to put R_D between V_{dd} and in between V_{dd} and the drain and R_L is grounded right. So, and because now the current is getting shared incremental current is getting shared between note that this incremental current this incremental current is getting shared between R_L and R_D right earlier all the incremental current was going into R_L because the incremental current is getting shared between R_L and R_D we are getting a lower gain ok. So, one final thing let me ask you before we stop again we assumed C_2 to be we assume C_2 to be infinitely large right.

What do you think I mean clearly you cannot again have an infinite capacitor right what do you think will be the value of C_2 or what will be the constraint on the value of C_2 right when if we have to choose a value so as to pass a waveform of frequency ω right. So, essentially what I am asking is we can you figure out what will be the constraint on what will be the what will be the limit of C_2 or what will be the constraint on C_2 just like we figured out the constraint on C_2 at the beginning of this on this page right. So, I hope you can do it yourself I will see you in the next lecture. Thank you.