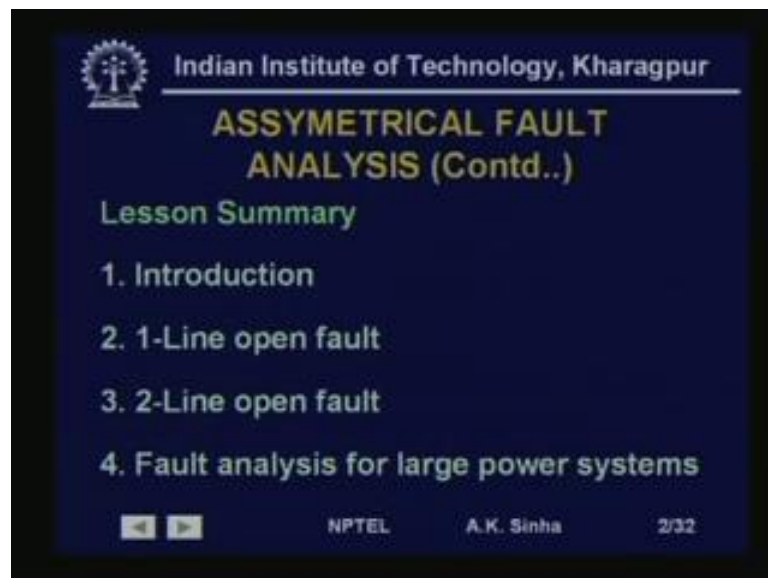


Power System Analysis
Prof. A. K. Sinha
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 29
Unbalanced Fault Analysis (Contd.)


Welcome to lesson 29 on Power System Analysis. In this lesson we will continue with Unbalanced Fault Analysis, the asymmetrical faults that we were considering, and a previous lectures, where the short circuit.

(Refer Slide Time: 01:00)



In this lecture we will consider the open circuit faults. So, here we will start with an introduction. Then we will discuss 1 line open fault and then 2 line open fault. And after that we will discuss a little about fault analysis for large power systems.

(Refer Slide Time: 01:31)

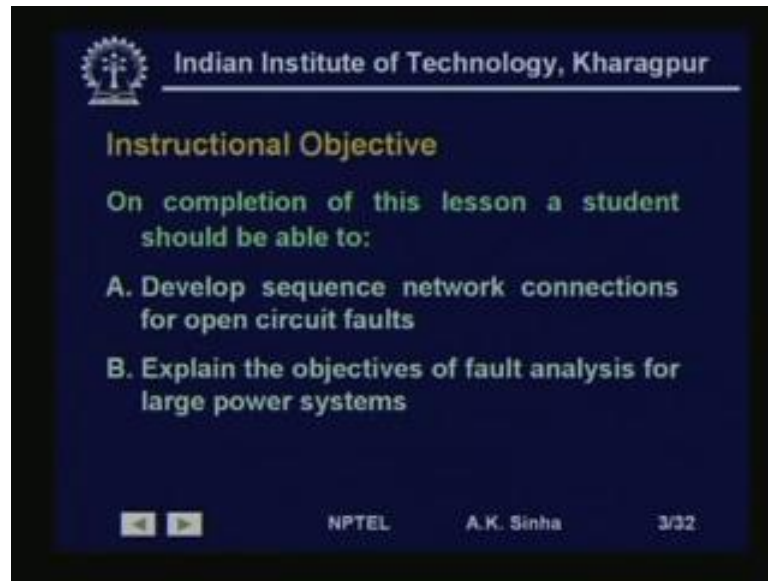

Indian Institute of Technology, Kharagpur

Instructional Objective

On completion of this lesson a student should be able to:

- A. Develop sequence network connections for open circuit faults
- B. Explain the objectives of fault analysis for large power systems

NPTEL A.K. Sinha 3/32

Well, on completion of this lesson you should be able to develop sequence network connections for open circuit faults. And you should be able to explain the objectives of fault analysis for large power systems.

(Refer Slide Time: 01:49)



Indian Institute of Technology, Kharagpur

Types of Faults

L - G Fault	}	→ Asymmetrical Faults
L - L - G		
L - L		
3 ϕ - G	}	→ Symmetrical Faults
1 ϕ - Open		
2 ϕ - Open	}	→ Asymmetrical Faults

NPTEL A.K. Sinha 4/32

As we discussed in a previous lesson, there are different kinds of faults which occur in a power system. Such as line to ground fault or line to line to ground faults and line to line faults these are asymmetrical faults. Similarly, 3 phase to ground faults are symmetrical faults.

All these faults are basically short circuit faults. Whereas, we have other types faults which are basically open circuit faults. Like a single phase open that is 1 line gets open or 2 line gets open. In both these cases the fault again is an asymmetrical fault. Because, the voltage and currents and in all the 3 phases are not balanced asymmetrical.

Now, when we 1 question which comes to mind as we can understand studying the short circuit faults. Because in case of short circuit have a currents are going to flow in the circuit. And we need to protect our equipment from damage because of this heavy currents. What happens in case of open circuit faults. Well open circuit faults in most to the cases will lead to over voltages. And that is why we need to study them, because these over voltages can sometimes cause insulation failure and thereby resulting in a short circuit. So, we need to study these open circuit faults also to make sure that our system design for insulation can take care of the over voltages cause by the open circuit faults.

(Refer Slide Time: 03:44)



Now, how do we simulate these open circuit faults. Well, if you see here we have phase a, b and c in the 3 phases we have impedances Z_a , Z_b and Z_c . Now, we are considering a fault occurs as between these points F and F dash on 2 sides of these impedances. These impedances can be the line impedances themselves and the point F and F dash can be the 2 bus pass.

Or it can be any 2 points, where the line gets broken or there is an open circuit in any equipment. So, here as we have shown phase a is carrying current I_a , phase b is carrying current I_b and phase c is carrying current I_c . The impedances Z_a , Z_b , Z_c or not same and thereby the currents will also be not same. That means, we have asymmetrical operating condition here.

Now, these if we assume Z_a to be infinite very large. We can simulate a fault which is an open circuit on phase a. Similarly, Z_b or Z_c can be made infinite or a very large which will simulate a fault of open circuit of phase b and c. So, in this way if we by making these impedance values very large or infinite we can simulate open circuit faults on this system.

And that is why these open conductor faults or open circuit faults are sometimes called series faults. That means what we are doing is we are introducing a large impedance in series with the circuit and for simulating these faults. Now, what happens in case of these series faults or open conductor faults.

(Refer Slide Time: 05:54)

Indian Institute of Technology, Kharagpur

Currents and voltages in open conductor fault

$$I_p = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}; \quad V_p = \begin{bmatrix} V_{aa'} \\ V_{bb'} \\ V_{cc'} \end{bmatrix}$$

$$I_s = \begin{bmatrix} I_{a1} \\ I_{a2} \\ I_{a0} \end{bmatrix}; \quad V_s = \begin{bmatrix} V_{aa'1} \\ V_{aa'2} \\ V_{aa'0} \end{bmatrix}$$


NPTEL A.K. Sinha 6/32

Let us see how to be defined the currents and voltages in case of open circuit faults or open conductor faults. The currents are in phase variable I_a , I_b and I_c and the voltage across the faulted portion. If you see this across this portion that is between F and F dash of this system. We see the voltages as $v_{aa'}$ $V_{bb'}$ $V_{cc'}$ as seen here that is voltage between a and a dash b and b dash c and c dash and so on.

We can convert this into asymmetrical component variables and we can write this as I_s , which is symmetrical component of for the currents. So, we have I_{a1} I_{a2} I_{a0} as the symmetrical component currents for the system. And V_s is equal to V_{a1} V_{a2} and V_{a0} . So, this is the transformed currents and voltages in the sequence network.

Now, for this system compare to the short circuit that we have done. There is some difference. The difference that we find here is that here we have 2 points a and a' for the faults and all the phases a b and c . That is we have 2 point F and F' in the system, which involve the fault. Whereas, in case of short circuit faults we had seen we had only 1 point F which there the fault had occurred.

(Refer Slide Time: 07:55)

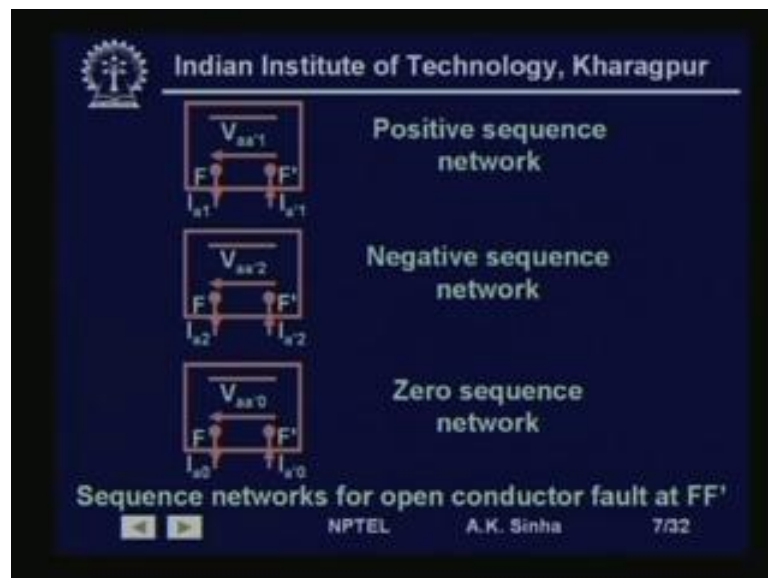


So and trying to obtain the sequence network for this we will also have these 2 points F and F' . So, this is the reference there is the positive sequence network there is there is the reference. And we have F F' as the 2 points of indicating the fault. And voltage between these 2 points is V_{a1} which is the positive sequence voltage. And the current flowing is i_{a1} and entering $I_{a'1}$.

In fact, as we will see these currents will be equal. Similarly the negative sequence we have the reference here. And we have 2 points F and F' where the current I_{a2} is and coming out from F and $I_{a'2}$ is entering F' . Now, in cash of negative sequence network V_{a2} is the voltage between F and F' .

Similarly, we have the zero sequence network reference here 2 points F 1 F dash I a 0 coming out from F I a dash 0 entering F dash and V a a dash 0 is the voltage between F and F dash for this network. Now, what we need to do is we need to find out the connection between the 3 sequence network for different types of fault. But, here what we find is the situation is somewhat more complexes.

Then what we are seen in case of a short circuit here we have 2 points F and F dash. That means, we have to get Thevenin's equivalent between F dash and reference as well as between F 1 reference. That means we have to think of Thevenin's equivalent in terms of 2 port network, because here we have a 2 port network between F dash and the reference and F and reference for each of the sequence network.

(Refer Slide Time: 10:06)

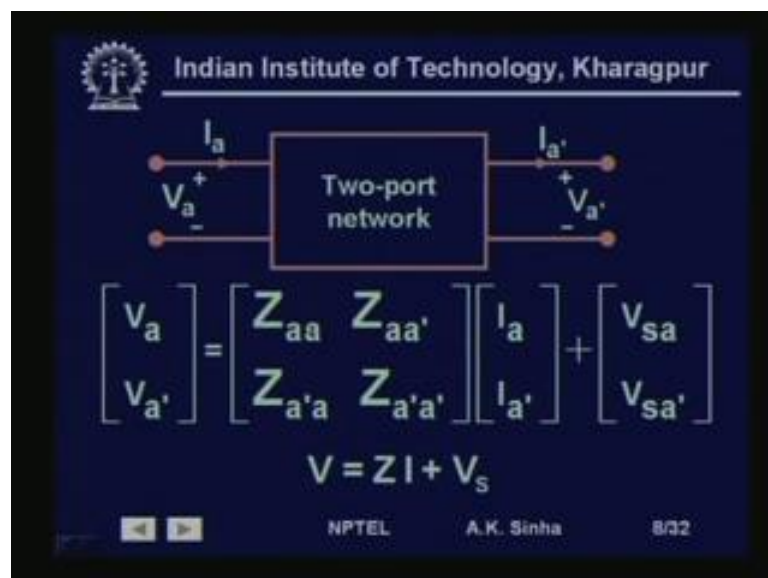

So, we need to take care of this using the theory from 2 port network. So, here I have shown this as a 2 port network, where we have I F flowing n on the input side. So, this side we have I a flowing n and V a is the voltage. And this side I a dash going out and V a dash is the voltage. Now, we can write down the voltage and current relationship for this 2 port network as V a V a dash is equal to Z a a Z a a dash Z a dash a and Z a dash a dash into I a I a dash.

Now this, these impedances are basically called the open circuit impedance for this network. That is you will get this impedance by keeping this open and supplying current

here. If see you was supply 1 ampere current here and you measure the voltage here. Then you will get Z_{a-a} this is Z_{a-a} .

Similarly, if you supply a current here keeping this open. If you measure the voltage here you will get Z_{a-a} . And so in this way we can find out these impedances. And here we have written this V_{s-a} and V_{s-a} . Now, these are basically the voltages or the voltage sources, which are connected in this system, so on this side as well as this side. So, they are taken care by means of this V_{s-a} and V_{s-a} . Therefore, in short we can write this relationship as $V = ZI + V_s$.

(Refer Slide Time: 12:05)

Indian Institute of Technology, Kharagpur

Network external connections impose the condition $-I_{012} = I_{012}$, i.e. $-I_{a1} = I_{a1}$, $-I_{a2} = I_{a2}$ and $-I_{a0} = I_{a0}$. (Current entering the node is +ve)

For +ve sequence network we can write:

$$\begin{bmatrix} V_{a1} \\ V_{a'1} \end{bmatrix} = \begin{bmatrix} Z_{aa1} & Z_{aa'1} \\ Z_{a'a1} & Z_{a'a'1} \end{bmatrix} \begin{bmatrix} -I_{a1} \\ I_{a1} \end{bmatrix} + \begin{bmatrix} V_{sa1} \\ V_{sa'1} \end{bmatrix}$$

$$\begin{bmatrix} V_{a1} \\ V_{a'1} \end{bmatrix} = \begin{bmatrix} V_{sa1} \\ V_{sa'1} \end{bmatrix} - \begin{bmatrix} (Z_{aa1} - Z_{aa'1}) I_{a1} \\ -(Z_{a'a1} \quad Z_{a'a'1}) I_{a1} \end{bmatrix}$$

NPTEL A.K. Sinha 9/32

So, how to be use this 2 port network relationship, in case of our sequence networks. Now, as we have as seen that we have in this case a system, where we have I_{a1} coming out and $I_{a'1}$ going in. Now, in case there is no crossover of wires; that means, the phase are not coming in contact with the other phase. Then we will the external conditions of the system. We will see that the value of I_{a1} and $I_{a'1}$ will be same. That is the current flowing out of the positive sequence network will be same as the flowing in into the positive sequence network at this point F dash. So, the network external connections impose the condition that minus I_{012} is equal to I_{012} dash.

That means the current the sequence currents flowing out of the F point are same as that flowing into the F point. That is minus I_{a1} is equal to this is equal to $I_{a'1}$ minus I_{a1} .


a_2 is equal to I_{a_2} these dashes should come here. And $I_{a_1} - I_{a_0}$ is equal to I_{a_0} I_{a_0} current entering the node is considered positive.

So, current coming out that is from the terminal F have been put as negative here. Therefore, for positive sequence network we can write V_{a_1} and V_{a_1} is equal to $Z_{a_1} I_{a_1} - Z_{a_1} I_{a_1} - Z_{a_1} I_{a_1}$, these are the open circuit impedances for this 2 port network.

That we have and is into minus I_{a_1} because we have put this minus I_{a_1} , because we are taking current entering as positive. So, minus I_{a_1} and plus I_{a_1} , because $I_{a_1} - I_{a_1}$ is basically equal to I_{a_1} . So, here we have this minus I_{a_1} and I_{a_1} here, because the magnitudes are same for both as we have said that next network external connections impose this condition. When there is no crossover of the phase. So, plus V_{s_1} and V_{s_1} , these are the internal voltage sources in the 2 sides of the network. So, this we can write again as $V_{a_1} - V_{a_1}$ is equal to this, we have taken on this side into this. We have simplified this, then we get this $Z_{a_1} - Z_{a_1}$ into I_{a_1} and minus $Z_{a_1} - Z_{a_1} I_{a_1} + Z_{a_1}$ into I_{a_1} .

So, after simplifying if we write this Z_{a_1} into minus $I_{a_1} - Z_{a_1}$ into I_{a_1} . So, minus has been taken here. So, this minus comes here now this $Z_{a_1} - Z_{a_1}$ this is minus here and this minus is missing here. So, minus we have taking here. So, this is positive, because $Z_{a_1} - Z_{a_1} I_{a_1}$ is here, so $Z_{a_1} - Z_{a_1}$ into I_{a_1} . Now, since it is positive this is minus we have taken here. So, minus is here and this will be minus here. So, this becomes plus and then this becomes minus. So, it is finally, minus Z_{a_1} into I_{a_1} .

(Refer Slide Time: 16:27)

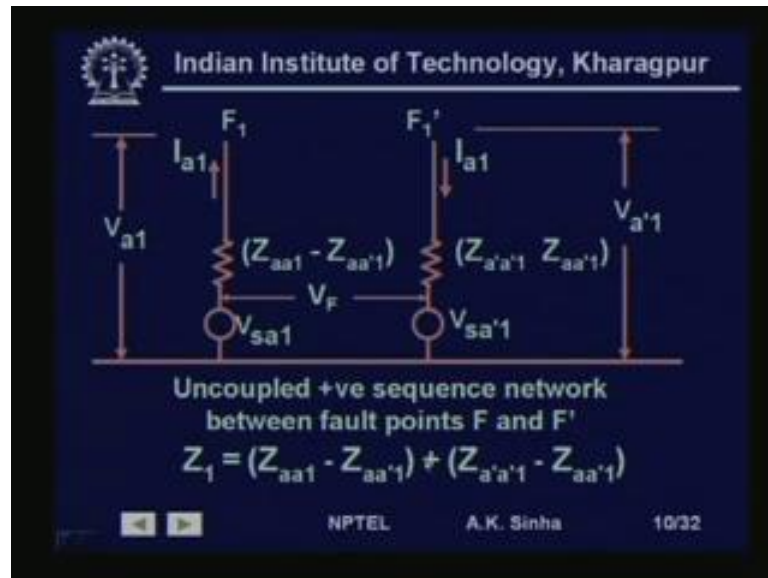

So, this is the relationship that we get which we can write in circuit form like this, where we have V_{sa1} is the voltage of the internal voltages in the system. So, that is put here and we have the impedance $Z_{aa1} - Z_{aa'1}$ as the series impedance connected to this source. And I_{a1} is the current coming out at this point F_1 . Similarly for the other side on the F_1' side.

We have $V_{sa1} - V_{sa'1}$ that is the internal voltage on that side. And the impedances $Z_{aa1} - Z_{aa'1}$ minus $Z_{a'a'1} - Z_{aa'1}$ this minus sign is missing here. So, and the current is entering this node as F_1' and the voltage across this is $V_{a'1}$ and the voltage here is V_{a1} . That is if we remember this we are saying this voltages V_{a1} and this is $V_{a'1}$. So, between reference n point $F_1 - F_1'$.

So, here that is what we get. So, this is and the V_F and the voltage at the fault point which is equal to your $V_{a'1} - V_{a1} - V_{a'1}$ is the voltage, which is coming between these 2 points. That is $V_{a'1}$. So, for the positive sequence and this is the voltage or the open circuit voltage across the fault point, which we get as the Thevenin's equivalent voltage, which will be coming.

So, this is the uncoupled positive sequence network between the fault point F and F' . Here we can write the if we say that the total current, which flows on the first sequence current which flows through the network encounters, Then positive sequence impedance of the network than the positive sequence impedance red one can be seen as this

impedance, and this impedance in series because this is I_{a1} flowing and through this flowing through the other parts of the network comes out like this.

So, the current I_{a1} is seeing this impedance and this impedance in series. So, we get Z_1 as $Z_{a1} - Z_{a1} +$. That is this impedance plus, this impedances plus, this impedance is $Z_{a1} - Z_{a1}$. So, this is what we will get as the total positive sequence impedance for this network.


Similarly, we can get the uncoupled negative sequence network between point F and F dash. For the system in the same way in the impedance in this case will be $Z_2 - Z_{a2} + Z_{a2} - Z_{a2}$ should be here. And the points these are F2 and F2 dash and the current flowing here is I_{a2} . And the current same current after flowing through the parts of the circuit will be entering this point F2 dash as I_{a2} , which is same as I_{a2} this will be entering here.

Now, again since we have said the negative sequence impedance is the impedance offered, but by this network to current negative sequence current flowing into the network. So, this is the negative sequence current flowing into the network. So, the impedance offered by the network to this current will be this impedance plus this impedance. So, we can write Z_2 is equal to $Z_{a2} - Z_{a2} + Z_{a2} - Z_{a2}$. So, this is the total negative sequence impedance seen by the current for the network or this is the negative sequence impedance of the network for this system.

Similarly, we can get the zero sequence network for this F0 and F0 dash points. So, here again the impedance is $Z_0 - Z_{a0} + Z_{a0} - Z_{a0}$. And we see that negative and zero sequence network do not have any voltage sources associated with them, which is what we had seen earlier also. So, here also there will be no such sources.

So, uncoupled zero sequence network between fault points F and F dash is like this. And the impedance offered to zero sequence current by this network will be equal to some of these 2 impedances that is Z_0 is equal to $Z_{a0} - Z_{a0} + Z_{a0} - Z_{a0}$. So, this is the total impedance which will this network we will see.

(Refer Slide Time: 22:08)

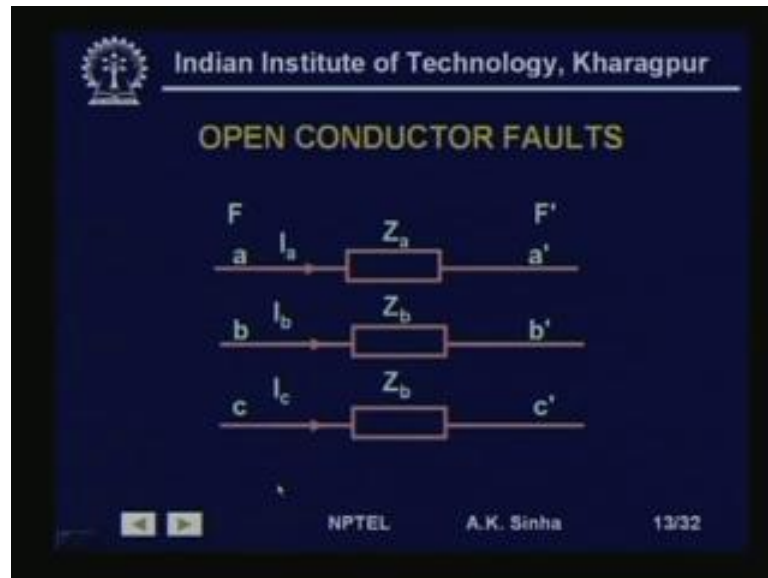

Now, for simulating the open conductor faults since we are simulating only 1 conductor or 2 conductor open faults. In case of 3 conductor open faults we do not need any analysis as such, because in that case there will be no current flowing through the system. System again will be symmetrical open circuit system.

So, a since we are simulating only 1 phase open or 2 phase open. So, what we can do is we can use Z_a as infinity. If we are assuming or we are simulating phase single conductor open that is 1 phase open and. So, phase a open with Z_a infinity or when we are when we are simulating 2 phases open. Then we can assume Z_b to be infinity. So, we do not need to create this for separate Z_a Z_b Z_c .

In fact, we can assume for simulation Z_b and Z_c and equal and Z_a is separate in phase a. So, when we want to simulate for 1 conductor open Z_a can be made infinite where Z_b will be finite. If we want to conductor open Z_b will be infinite and Z_a will be finite. So, this way we can simulate this. Now, let us see with this situation what happens.

(Refer Slide Time: 23:39)

Indian Institute of Technology, Kharagpur

$$\begin{bmatrix} V_{aa'} \\ V_{bb'} \\ V_{cc'} \end{bmatrix} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} - \begin{bmatrix} V_{a'} \\ V_{b'} \\ V_{c'} \end{bmatrix} = \begin{bmatrix} Z_a & 0 & 0 \\ 0 & Z_b & 0 \\ 0 & 0 & Z_c \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$V_{abc} - V_{a'b'c'} = Z_{abc} I_{abc}$$

$$V_{aa'(012)} = V_{012} - V'_{012} = Z_{012} I_{012}$$

$$Z_{012} = A^{-1} Z_{abc} A$$

NPTEL A.K. Sinha 14/32

So, again we can write down the voltage equation for the system as $V_a - V_{a'}$, $V_b - V_{b'}$ and $V_c - V_{c'}$ in phase components. So, this will be equal to $V_a - V_{a'}$, $V_b - V_{b'}$, $V_c - V_{c'}$, which will be equal to $Z_a I_a$, $Z_b I_b$ and $Z_c I_c$.

That is if you see here $V_a - V_{a'}$ will be nothing but $I_a Z_a$ here we are assuming there are no mutual couplings between these phase impedances. So, in this way we can write this relationship in this simple form. That is we can write $V_{abc} - V_{a'b'c'}$ is equal to $Z_{abc} I_{abc}$.

Now, this can also be written in terms of sequence component as $V_{aa'(012)}$ is equal to $V_{012} - V'_{012}$. That is positive sequence voltages at point F and positive sequence voltages at point F'. So, subtraction of these two will be equal to $Z_{012} I_{012}$. Where this Z_{012} as we have seen earlier will be nothing but equal to an inverse Z_{abc} into A where A is the symmetrical component transformation matrix.

So, Z_{012} is equal to $A^{-1} Z_{abc} A$, this is what we will write for this to get this Z_{012} . And then we find that $V_{012} - V'_{012}$ is equal to $Z_{012} I_{012}$. That means the phase quantities are now converted into sequence quantities.

(Refer Slide Time: 25:43)

Indian Institute of Technology, Kharagpur

$$Z_{012} = \frac{1}{3} \begin{bmatrix} Z_a + 2Z_b & Z_a - Z_b & Z_a - Z_b \\ Z_a - Z_b & Z_a + 2Z_b & Z_a - Z_b \\ Z_a - Z_b & Z_a - Z_b & Z_a + 2Z_b \end{bmatrix}$$

$$\begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} - \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} Z_a + 2Z_b & Z_a - Z_b & Z_a - Z_b \\ Z_a - Z_b & Z_a + 2Z_b & Z_a - Z_b \\ Z_a - Z_b & Z_a - Z_b & Z_a + 2Z_b \end{bmatrix} \begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix}$$

NPTEL A.K. Sinha 15/32

Now, if we do this then we find that Z_{012} is equal to $\frac{1}{3}$ into $Z_a + 2Z_b$ $Z_a - Z_b$ $Z_a - Z_b$. So, that is what we are finding that in this case the diagonal elements are equal to $Z_a + 2Z_b$. And all the off diagonal elements are equal to $Z_a - Z_b$ like this is a symmetric matrix with all the diagonal elements having the same value.

And all the off diagonal elements having the same value. The diagonal elements have $Z_a + 2Z_b$. Whereas the off diagonal elements or $Z_a - Z_b$. And of course, this $\frac{1}{3}$ comes, because of the transformation that we have. So, in this case we can write this as V_{a0} is equal to $V_{a0} - V_{a0}$. Similarly, for positive this sequence V_{a1} is equal to $V_{a1} - V_{a1}$ V_{a2} is equal to $V_{a2} - V_{a2}$. This is equal to this Z_{012} into I_{a0} I_{a1} I_{a2} . So, this is what we will get.

(Refer Slide Time: 27:09)

Indian Institute of Technology, Kharagpur

Subtracting row 2 from row 1

$$V_{aa'(0)} - V_{aa'(1)} = Z_b (I_{a0} - I_{a1})$$
$$V_{aa'(0)} - Z_b I_{a0} = V_{aa'(1)} - Z_b I_{a1}$$

Subtracting row 3 from row 2

$$V_{aa'(1)} - V_{aa'(2)} = Z_b (I_{a1} - I_{a2})$$
$$V_{aa'(1)} - Z_b I_{a1} = V_{aa'(2)} - Z_b I_{a2}$$

NPTEL A.K. Sinha 16/32

And if we use this relationship, that is subtracting row 2 from row 1. That is from this row 2 ((Refer Time: 27:14)) if we subtract this is $Z_b I_{a0} - Z_b I_{a1}$ plus $Z_b I_{a1} - Z_b I_{a2}$ this we subtract from row 1. That is $Z_b I_{a0} + Z_b I_{a1} - Z_b I_{a2}$. Then an arranging this we will get $V_{aa'(0)} - V_{aa'(1)}$ is equal to $Z_b I_{a0} - Z_b I_{a1}$.

That is, if we do this subtraction of the row 2 from row 1 this is what we are going to that. And this we will we can write as $Z_b I_{a0} - Z_b I_{a1}$. This term we are taking on this side. Now, this time we are taking on right hand side. So, this becomes positive. So, $V_{aa'(1)} - Z_b I_{a1}$. So, this is what we will get by subtracting row 2 from row 1.

Now, similarly subtracting row 3 from row 2 we will get $V_{aa'(1)} - V_{aa'(2)}$ is equal to $Z_b I_{a1} - Z_b I_{a2}$ which we will give us $V_{aa'(1)} - Z_b I_{a1}$ plus $Z_b I_{a1} - Z_b I_{a2}$ we are taking on this sides. So, it becomes negative, this $V_{aa'(2)} - Z_b I_{a2}$ we are taking on this side. So, it becomes positive minus $Z_b I_{a2}$. So, this is minus $Z_b I_{a2}$. So, these 2 relationships that we are getting here like this.

(Refer Slide Time: 29:05)

Indian Institute of Technology, Kharagpur

or

$$V_{aa'(0)} - Z_b I_{a0} = V_{aa'(1)} - Z_b I_{a1} = V_{aa'(2)} - Z_b I_{a2}$$

Adding row 1 and row 2

$$V_{aa'(0)} + V_{aa'(1)} = \frac{1}{3}(2Z_a + Z_b)(I_{a0} + I_{a1}) + \frac{2}{3}(Z_a - Z_b) I_{a2}$$

Substituting for $V_{aa'(0)}$ and simplifying

$$V_{aa'(1)} - Z_b I_{a1} = \frac{1}{3}(Z_a - Z_b)(I_{a0} + I_{a1} + I_{a2})$$

From above two equations we get the sequence network connection as:

NPTEL A.K. Sinha 17/32

Now, from this what we are seeing $V_{aa'(0)} - Z_b I_{a0}$ is equal to $V_{aa'(1)} - Z_b I_{a1}$ is equal to $V_{aa'(2)} - Z_b I_{a2}$. That is if we see here this term this term $V_{aa'(1)} - Z_b I_{a1}$ is here also. So, which means this term is equal to this term is equal to this term.


So, this is what we are writing here. That is $V_{aa'(0)} - Z_b I_{a0}$ is equal to $V_{aa'(1)} - Z_b I_{a1}$ is equal to $V_{aa'(2)} - Z_b I_{a2}$. Now, adding row 1 and row 2 what we will get. That is again if we go here and add row 1 and row 2 what we are going to get. We will get $V_{aa'(0)} + V_{aa'(1)}$ is equal to $\frac{1}{3}(2Z_a + Z_b)(I_{a0} + I_{a1}) + \frac{2}{3}(Z_a - Z_b) I_{a2}$.

Now, substituting for $V_{aa'(0)}$ and simplifying that is from here we can substitute value by putting this side on this side. And simplifying we will get $V_{aa'(1)} - Z_b I_{a1}$ is equal to $\frac{1}{3}(Z_a - Z_b)(I_{a0} + I_{a1} + I_{a2})$.

That is would we have done is substituting the value of this. Here from this one and then we will get this $V_{aa'(1)} - Z_b I_{a1}$ is equal to this 2. So, from above 2 equations we get the sequence network connections as now what does this say. This is saying $V_{aa'(0)} - Z_b I_{a0}$ is equal to $V_{aa'(1)} - Z_b I_{a1}$ and $V_{aa'(2)} - Z_b I_{a2}$ means this Z_b is connected in series with this negative sequence network positive sequence network and zero sequence network.

And we also have from this that $V_{a'a'2} - Z_b I_{a'2}$ is equal to $\frac{1}{3} Z_b$ minus Z_a minus Z_b into this that is sum of all these 3 currents will also flow through this impedance. So, if we use this, these two this equation and this equation. Then we will get connection of the circuit like this.

(Refer Slide Time: 32:18)

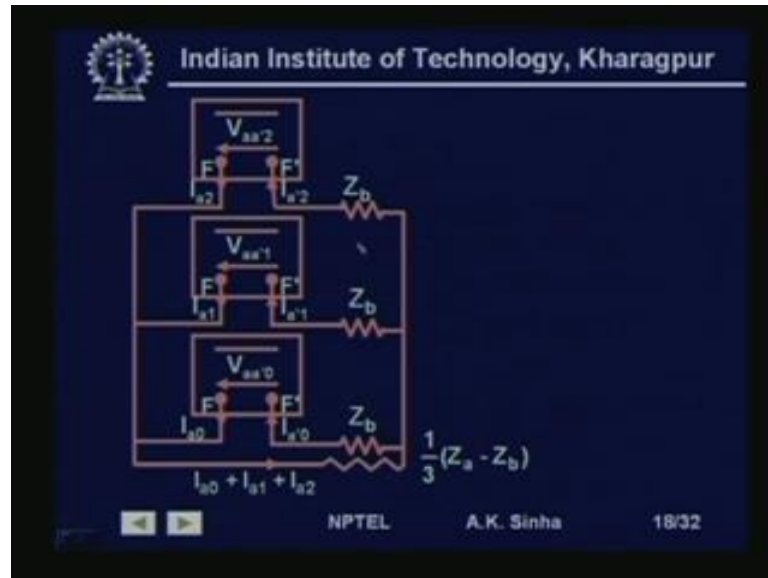


That is $V_{a'a'0}$ in which though the Z_b is connected in series with this. So, $I_{a'0}$ is flowing into this. So, this is $V_{a'a'0} - Z_b I_{a'0}$ is the voltage across these two points. Similarly, $V_{a'a'1} - Z_b I_{a'1}$ is the voltage, which is coming across these two points.

Similarly, $V_{a'a'2} - Z_b I_{a'2}$ is giving as voltage between these two points. So, that is why and these are equal. So, we have connected them. We also see that the current this current is flowing this is $I_{a'2}$, $I_{a'1}$ and $I_{a'0}$ is flowing through the impedance $\frac{1}{3} Z_a$ minus Z_b and this is equal to this voltage which is same as this voltage.

So, this is the circuit that we get in case of this system where we have a Z_a in phase a and Z_b and Z_b in phase b and c respectively. So, this is the sequence network connection that we are getting. Now, if you want to get simulate 1 conductor out or a single phase open. Then we can do that very easily by substituting Z_a is equal to infinity.

(Refer Slide Time: 33:53)

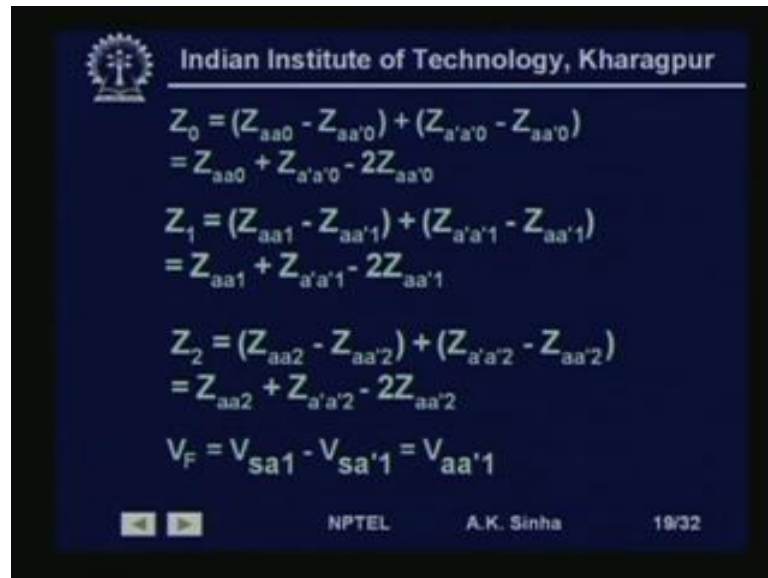

Indian Institute of Technology, Kharagpur

$$Z_0 = (Z_{aa0} - Z_{aa'0}) + (Z_{a'a'0} - Z_{aa'0})$$
$$= Z_{aa0} + Z_{a'a'0} - 2Z_{aa'0}$$
$$Z_1 = (Z_{aa1} - Z_{aa'1}) + (Z_{a'a'1} - Z_{aa'1})$$
$$= Z_{aa1} + Z_{a'a'1} - 2Z_{aa'1}$$
$$Z_2 = (Z_{aa2} - Z_{aa'2}) + (Z_{a'a'2} - Z_{aa'2})$$
$$= Z_{aa2} + Z_{a'a'2} - 2Z_{aa'2}$$
$$V_F = V_{sa1} - V_{sa'1} = V_{aa'1}$$


NPTEL A.K. Sinha 19/32

And Z_b is finite, but before we do that we need to compute the value of Z_0 , Z_1 and Z_2 for the circuit. So, if we see here what is the current which is flowing through that is I_{a1} is flowing through which circuit.

Then we find this Z_b is there and the circuit that we had seen for this positive sequence network that will be there. So, Z_b is in series with that. And similarly for this we will find for Z_2 will be in series with this Z_b . And Z_0 in series with this and of course, $1/3 Z_a$ minus Z_b is in parallel with these.


So, if we do this circuit reduction then we have Z_0 is equal to Z_{aa0} minus $Z_{aa'0}$ plus this. So, this we have seen is equal to this Z_1 we have seen is equal to this Z_2 we have seen is equal to this. That is simply adding this is what we get and V_f is equal to V_{sa1} minus $V_{sa'1}$ this is equal to $V_{aa'1}$, this is what we had seen in this circuit earlier.

(Refer Slide Time: 35:20)

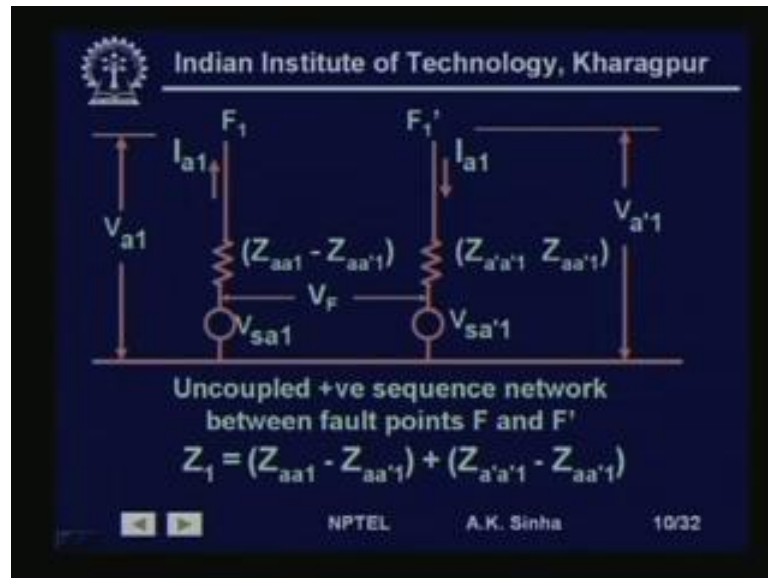

V_f is equal to $V_s - V_{sa1} - V_{sa'1}$ this is what we have seen this is equal to V_f . So, this is what we have. So, V_f is this we have $Z_1 Z_2 Z_0$ ((Refer Time: 35:42)) that we have calculated earlier. So, these can be substituted here.

(Refer Slide Time: 35:45)

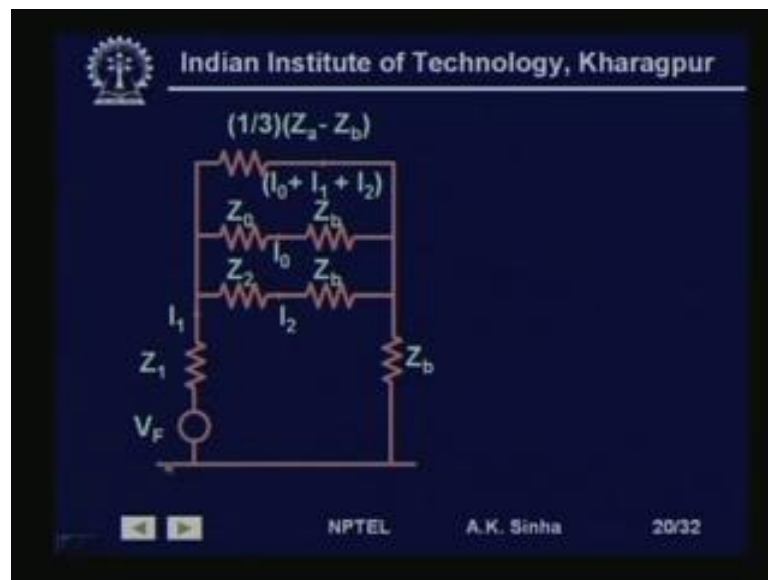

So, we have the complete circuit now like this. $V_f Z_1$ in series with that and we have now this current I_1 flowing through this. And then we have Z_b here and this is the point where we have this. This is the point these two the points of the circuit, and then again if we take zero sequence or negative sequence.

Then we have Z_0 and Z_b in series. So, we have Z_0 and Z_b in series. Similarly, Z_2 and Z_b in series and here I_2 is flowing here I_0 is flowing and here we have I_0 plus I_1 plus I_2 flowing. So, this is I_1 flowing this is I_2 flowing this is I_0 flowing through the circuit and I_1 plus I_2 plus I_0 flowing through the circuit like this. So, this is complete circuit which defines the sequence network connection for the system, where we have an impedance Z_a in phase a and impedance Z_b in phase b as well as phase c.

(Refer Slide Time: 37:11)

Indian Institute of Technology, Kharagpur

$$I_1 = \frac{V_f}{Z_T}; Z_T = Z_1 + Z_0 + Z$$

$$Z = \frac{(Z_0 + Z_b)(Z_2 + Z_b)(Z_2 - Z_b)}{(Z_2 - Z_b)(Z_2 + Z_b) + (Z_2 - Z_b)(Z_2 + Z_b) + 3(Z_0 + Z_b)(Z_2 + Z_b)}$$

$$I_2 = -I_1 Z / (Z_2 + Z_b)$$

$$I_0 = -I_1 Z / (Z_0 + Z_b)$$

NPTEL A.K. Sinha 21/32

Now, as we said we can calculate the positive, negative and zero sequence current for this circuit. So, we can do that I_1 will be equal to V_f by Z_t that is if we see this circuit. V_f is the voltage and this is the total impedance of the circuit is the Z_t and we need to find out what is Z_t .


So, Z_t will be equal to Z_1 plus Z_b that is again if we see this is a Z_1 in series and Z_b in series which I_1 flowing. And this rest of the circuit is again can be reduced in to 1 impedance connected between, these 2 points. So, if we do that that is these 3 impedance arms are in parallel. So, we need to find out and equivalent for these three. So, that is Z and we can write this Z is equal to Z_0 plus Z_b into Z_2 plus Z_b into Z_a minus Z_b divided by Z_a minus Z_b into Z_0 plus Z_b plus Z_a minus Z_b into Z_2 plus Z_b plus 3 times Z_0 plus Z_b into Z_2 plus Z_b .

That is what we have done is ((Refer Time: 38:32)) reduce these 3 arms into a single impedance Z . Then we have Z_1 plus this Z plus Z_b that is equal to Z_t . So, if we do that

then we have this I_1 computed like this. I_2 is the part of current, which is flowing in that. So, this can be written as $\frac{-I_1 Z}{Z_2 + Z_b}$ and I_0 will be $\frac{-I_1 Z}{Z_0 + Z_b}$.


So, since I_1 is flowing and total impedance as we had seen is this impedance is Z . A part of this goes through this rest will go through this. So, we have this ratio coming into picture. So, $\frac{Z}{Z_2 + Z_b}$ and $\frac{Z}{Z_0 + Z_b}$ for I_0 and I_2 we have $\frac{Z}{Z_2 + Z_b}$ part of the current I_1 will be flowing. So, this is how we can calculate the positive negative and zero sequence current flowing into this system.

(Refer Side Time: 39:44)

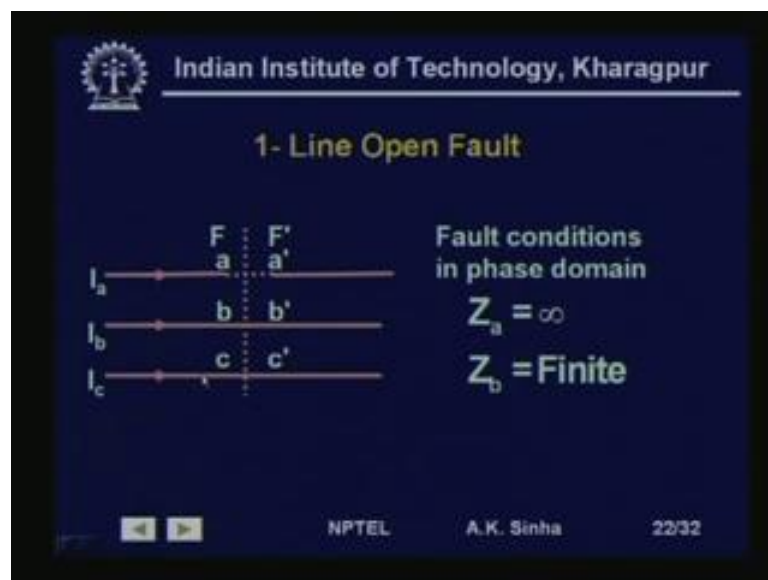

Now, we want to simulate 1 line open for a single phase open fault. Again here as we have seen we have this fault created between 2 points F and F dash. Now, in this case what we have Z_a is infinite. If we see the previous system and Z_b is finite. So, substituting Z_b as finite. So, these 2 lines are connected and we have a finite impedance here infinite impedance here. There is a infinite impedance here because it is open here.

(Refer Slide Time: 40:17)

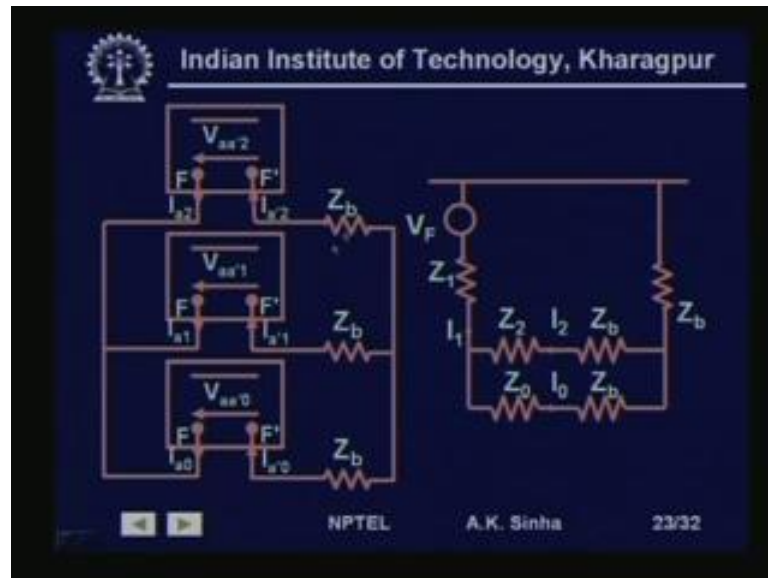

So, with this if you see then what happens if we go back to this circuit. What we find substituting Z_a is equal to infinite means this becomes infinite. So, this is an open circuit, rest of the circuit, we do not have Z_a . So, rest of the circuit remains as the case. So, this is what we get in this case that is this is the system, that we have, where we have Z_a as here.

We have a Z_a minus Z_1 by $3Z_a$ minus Z_b that part is now infinite. So, it is open. So, when we reduce this circuit we reduce it to this form that part here $1/3 Z_a$ minus Z_b is no longer connected parallel that is open. So, this is the total circuit that we have and we can calculate I_1 , I_2 and I_0 for this circuit.

(Refer Slide Time: 41:10)

Indian Institute of Technology, Kharagpur

$$I_1 = \frac{V_f}{Z_T}; Z_T = Z_1 + Z_b + Z$$

$$Z = \frac{(Z_0 + Z_b)(Z_2 + Z_b)}{(Z_0 + Z_2 + 2Z_b)}$$

$$I_2 = -I_1 \cdot Z / (Z_2 + Z_b)$$

$$I_0 = -I_1 \cdot Z / (Z_0 + Z_b)$$

NPTEL A.K. Sinha 24/32

So, we get I_1 is equal to V_f by Z_T and Z_T in this case will be equal to Z_1 plus Z_b plus Z . That is again Z_1 plus Z_b plus Z , which is the parallel of these 2 arms. So, we can do this Z is equal to Z_0 plus Z_b into Z_2 plus Z_b plus divided by Z_0 plus Z_2 plus $2Z_b$. And once we have we know I_1 we can calculate I_2 is equal to minus I_1 into Z by Z_2 plus Z_b and I_0 will be minus I_1 Z divided by Z_0 plus Z_b . And so this way we can compute. All the 3 currents sequence currents and then we can convert them 2 phase values and we can calculate the voltages in the same way.

(Refer Slide Time: 42:05)

Indian Institute of Technology, Kharagpur

2-Line Open Fault

Fault conditions in phase domain

$$Z_b = \infty; Z_a = \text{Finite}$$


$$I_b = I_c = 0$$

$$\begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

NPTEL A.K. Sinha 25/32

Now, for a 2 line open fault that is phase b and c are open. This can be simulated by putting Z_b is equal to infinite and Z_c as finite. That means I_b and I_c in this case is equal to 0. Now, if that is the situation then we can write this $I_0 I_1 I_2$ is equal to 1 by 3 into this is the transformation matrix. That we have inverse and this is $I_a I_b$ and I_c . Now, I_b and I_c are 0. So, what we get we get I_0 is equal to 1 by 3 into $I_a I_1$ is equal to 1 by 3 into $I_a I_2$ is equal to 1 by 3 into I_a these 2 are 0. So, we get 1 by $3 I_a I_a I_a$. So, what does this say. This says that the 3 sequence currents are equal which means the 3 sequence current networks connected in series. So, this is what we will get.

(Refer Slide Time: 43:19)

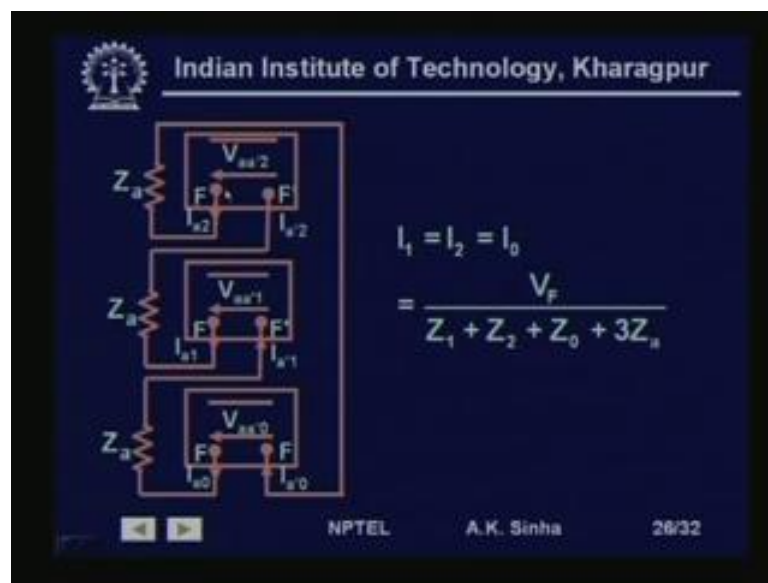

Here the, this is the zero sequence network Z_a is connected in series like this. To F dash then from F again Z is connected to F here and then F dash here and then from F Z_a connected and it comes to this point. So, the 3 networks are in series as such is $Z_a Z_a$ and Z_a connected here therefore, we get I_1 is equal to I_2 is equal to I_0 . This is equal to V_f divided by Z_1 plus Z_2 plus Z_0 plus $3Z_a$.

So, in this case this is how we calculate the current sequence currents. Once we know the sequence currents. We can calculate the sequence voltages at any point and converting them. We will find out the phase voltages at fault point or any another point in the system. So, this is how we can solve open circuit faults using the sequence network connections.

(Refer Slide Time: 44:27)

Indian Institute of Technology, Kharagpur

Algorithm for Analysis of Faulted Power Systems

1. Obtain pre-fault steady state solution of the system (Load Flow study).
2. Assemble systems model consisting of three separate sequence networks with their appropriate impedance values and short all the voltage sources (passive network).
3. Depending on type and location of fault using mathematical description of same make the proper connections for the sequence networks.

NPTEL A.K. Sinha 27/32

So, after this we will summarize whatever we have done. Tell now in case of faulted system analysis how do we carry it out. So, what we do is we will right down the algorithm for analysis of faulted power system. What we do first is obtain pre fault steady state solution of the system. That is the pre fault conditions we find out if we can if we do not know or do not want to these values. Or we have unloaded system that is we have assumed that the system is initially unloaded. Then of course, we know the voltages are one and the currents are zero.

So, but if we want to take into account the loaded system condition at which the fault has occurred. Then we can of course, do a load flow study and find out the voltage and currents in various parts of this system. So, we know that pre faults steady state solution of the system by doing a load flow study.

Now, after this assemble the system models consisting of 3 separate sequence networks. That is we create the 3 sequence networks, positive, negative and zero sequence networks with their appropriate impedances. Which means if we are interested in the fault current immediately after the fault has occurred. Then we get the subtransient impedances, if we are interested in finding out the current after sometime, that is when the breaker opens.

The circuit may be after 2 cycles or 5 cycles like that. Then we may substitute transient impedances instead of the subtransient impedances. And if we are interested in sustain


fault current that is steady state fault current. Then we need to substitute the steady state impedances, which is the synchronous impedances for the machines as such.

So, appropriate impedance value and short all the voltage sources that is we have seen earlier that. What we do is for computing the fault currents using the Thevenin's theorem principle. What we are trying to do is find out the changes caused by introducing this fault.

That is we had seen that fault is acting as a structural change. That is inclusion of an impedance fault impedance into the system. And this we can simulate by using Thevenin's theorem. That is by putting impedance at fault point equal to this impedance in series with the voltage, which is opposite to the open circuit voltage at the fault point

So, that is what we do in this case. So, for this purpose we have already eliminated all the voltage sources. That is the all the generators are shorted and replace by their appropriate impedances. Depending on the type on location of the fault using the mathematical description of the of the same, make proper connection for the sequence network. That is depending on the type of all fault if it is single line to ground fault. Then it all the 3 impedance as 3 sequence networks will be connected in series and so on. So, we need to do that. So, make the proper connections for the sequence network. Then excite the positive sequence network at the fault point.

(Refer Slide Time: 48:27)

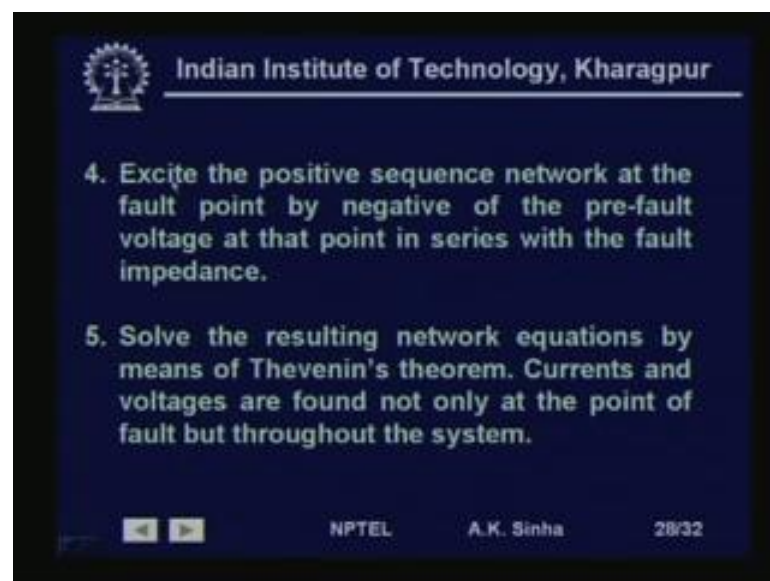

The slide features the IIT Kharagpur logo and name at the top. It contains two numbered steps in white text on a dark blue background. At the bottom, there are navigation icons (back, forward), the text 'NPTEL A.K. Sinha', and the slide number '28/32'.

Indian Institute of Technology, Kharagpur

4. Excite the positive sequence network at the fault point by negative of the pre-fault voltage at that point in series with the fault impedance.
5. Solve the resulting network equations by means of Thevenin's theorem. Currents and voltages are found not only at the point of fault but throughout the system.

NPTEL A.K. Sinha 28/32

As what I said excite the positive sequence network at the fault point by negative of the pre-fault voltage at that point. In series with the fault impedance, this is what the Thevenin's theorem says that .We have reduced the network passive network by shorting all the voltage sources and replacing them by their appropriate impedances

Now, at the fault point we have we connect the voltage source of value which is equal to the negative of the open circuit voltage at that point that we had found using in the Thevenin's theorem. And in series this voltage is connected the series with the fault impedance at the fault point. So, between the fault point and the reference.

So, this is how we do that this when we do this will give us the currents and voltages caused by the introduction of the fault. That is the changes caused by this fault and this can be added or superimposed on the pre-fault values. And therefore, we will get the final values. Solve the resulting network equitation's by means of Thevenin's theorem currents and voltages are found not only for the point of fault, but throughout the system.

So, once we find these changes what we do is we added to the or superimposed on the pre-fault conditions that we have. And then we know the voltages and currents are various points in this system. So, this is the algorithm that we use for solving the faulted system. That is the solving or analyzing the system under fault conditions.

(Refer Slide Time: 50:34)

Indian Institute of Technology, Kharagpur

Short-Circuit Analysis of Large Power Systems

For small systems it is possible to reduce the sequence networks into its Thevenin's equivalent at the fault point.

For large systems it is extremely difficult to obtain such an equivalent.


For large systems we need to develop a systematic and general procedure (algorithm) which is suitable for solution on computer.

NPTEL A.K. Sinha 29/32

However, this does not work very well for large system. Because, here we need to find out the reduce network. Reduce possible network at the fault point, which is very difficult to obtain for large systems So, for small systems it is possible to reduce the sequence network into establish equivalent at the fault point.

But for large system it is extremely difficult to obtain such an equivalent. That is very complex to do that for a large system, which has large number of lines and nodes in the system that is bus wires in the system. For large systems therefore, we need to develop a systematic and general procedure. That is some algorithm which is suitable for solution on computer we need to do this for large systems. And we will see how we do it in detail in the next class. So, what we do before we start analysis large system we need to define the problem or state the problem

(Refer Slid Time: 51:39)

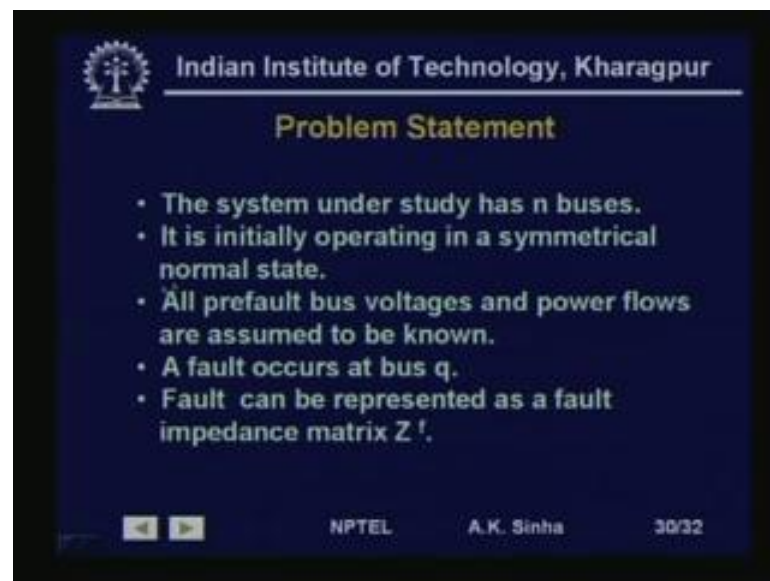

Indian Institute of Technology, Kharagpur

Problem Statement


- The system under study has n buses.
- It is initially operating in a symmetrical normal state.
- All prefault bus voltages and power flows are assumed to be known.
- A fault occurs at bus q .
- Fault can be represented as a fault impedance matrix Z^f .

NPTEL A.K. Sinha 30/32

So, what we do is we say that the system under study has n buses, where n is very any number and large number normally. It is initially operating in a symmetrical normal state. That is what we assumed that initial conditions are steady state conditions all pre-fault bus voltages and power flows are assume to be known.

That is we have done the load flow study. And the know the voltage and power flows at a fault occurs at some bus q . So, any bus it can be any bus q fault can be represented as a fault impedance matrix Z^f . This again we will see how to do it. So, that is if you see the system. We can define this is the n bus power system.

(Refer Slide Time: 52:27)

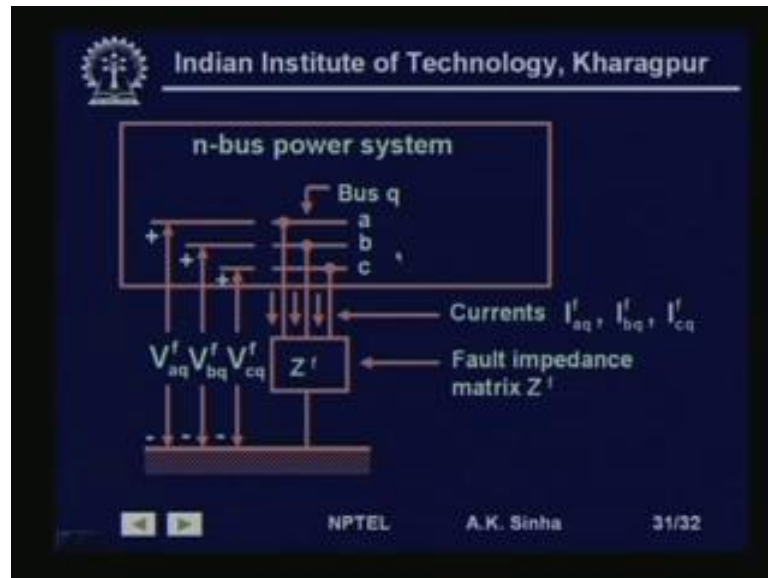

In which we have taken this bus q at which the fault has occurred the fault impedance is Z_f and the a, b, c phase voltages are shown here for the bus q. So, with this we end today. In the next lesson we will talk about how to develop an algorithm for short circuit studies on large power systems.

Thank you very much.

Preview of Next Lecture

Lecture No. # 30

Fault Analysis for Large Power System

Welcome to lesson 30 on Power System Analysis. In these lessons we will discuss Fault Analysis for large power system. We will start with an introduction. Then we will discuss fault analysis for last power system using Y bus matrix.

(Refer Slide Time: 53:32)

Indian Institute of Technology, Kharagpur

ASSYMETRICAL FAULT ANALYSIS (Contd..)

Lesson Summary

1. Introduction
2. Fault analysis using Y_{bus} matrix
3. Fault analysis using Z_{bus} matrix
4. Example

NPTEL A.K. Sinha 2/26

Then we will talk about fault analysis using Z bus matrix and then finally, will solve one example using Z bus matrix.

(Refer Slide Time: 53:43)

Indian Institute of Technology, Kharagpur

Instructional Objective


On completion of this lesson a student should be able to:

- A. Develop algorithm for fault analysis using Y_{bus} method
- B. Explain the difficulties associated with fault analysis using Y_{bus} method
- C. Develop algorithm for fault analysis using Z_{bus} method

NPTEL A.K. Sinha 3/26


Well, the instructional objective for this lesson is that on completion of this lesson, you should be able to develop algorithm for fault analysis using Y bus methods. Explain the difficulties associated with fault analysis using Y bus method. Develop an algorithm for fault analysis using Z bus method.

(Refer Slide Time: 54:10)

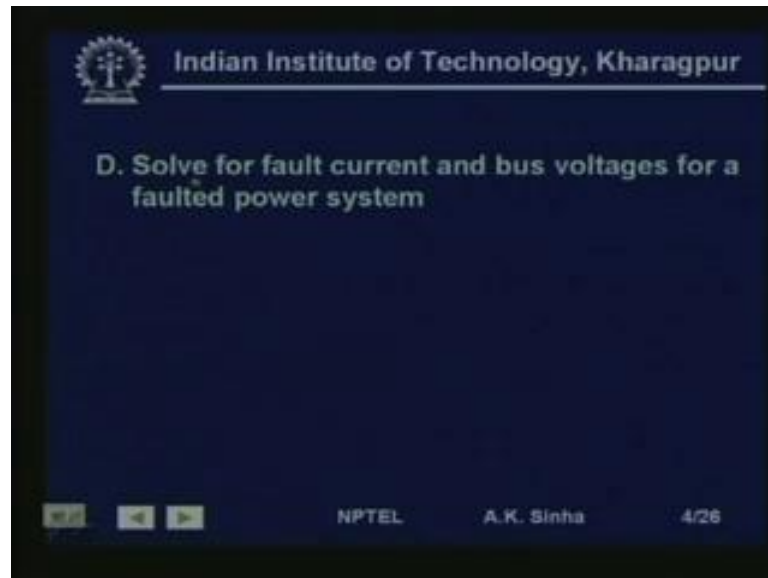

And solve for fault current and bus voltages for a faulted power system using the Z bus method.

(Refer Slide Time: 54:23min)

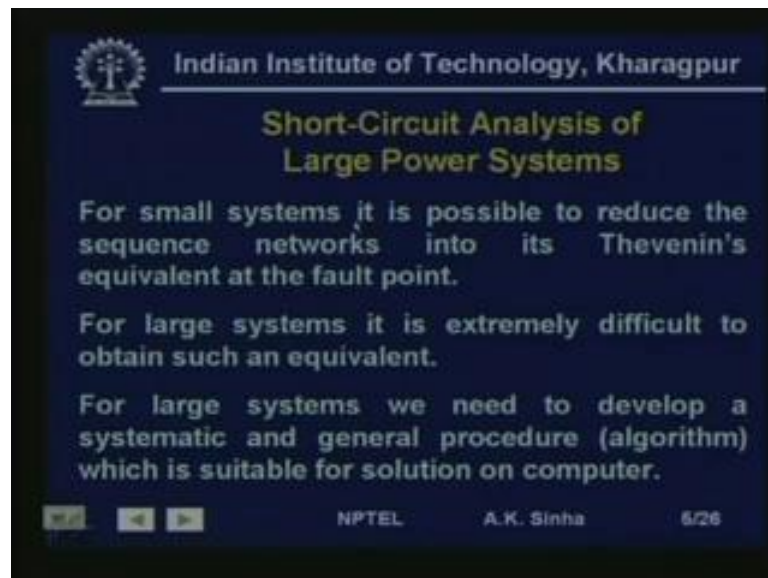


Well as we had discussed in lesson 29. That we can do symmetrical as well as asymmetrical fault analysis using Thevenin's theorem, but when we are trying to do it for a large system, trying to find out the Thevenin's equivalent of the network at the fault point as a very complex job.

For small systems it is possible to reduce the sequence networks into Thevenin's equivalent at the fault point. For large network it is extremely difficult to obtain such an equivalent. Because, you need reduction for very large network with large number of voltage sources in the system.

So, therefore, for these large systems we need some kind of a systematic method to solve this problem using a digital computer. So, we need to develop a systematic and general procedure, which is suitable for solution on a computer.

(Refer Slide Time: 55:31)

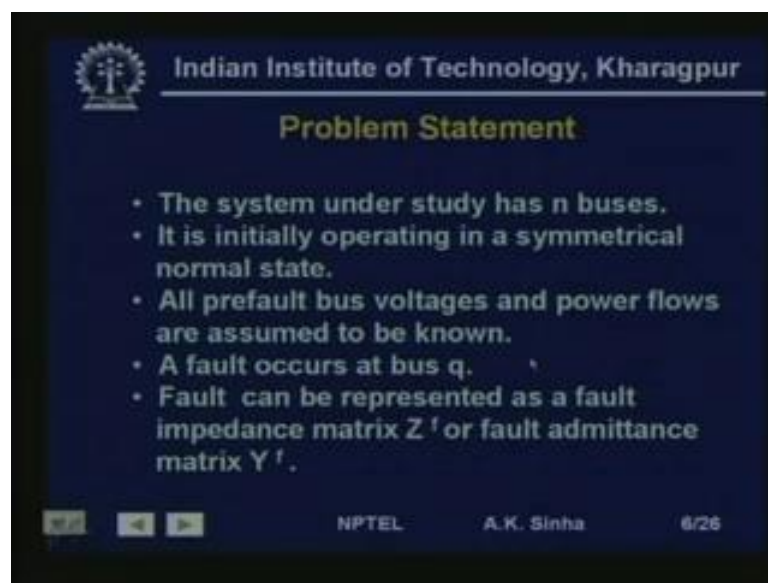

Indian Institute of Technology, Kharagpur

Problem Statement

- The system under study has n buses.
- It is initially operating in a symmetrical normal state.
- All prefault bus voltages and power flows are assumed to be known.
- A fault occurs at bus q .
- Fault can be represented as a fault impedance matrix Z^f or fault admittance matrix Y^f .

NPTEL A.K. Sinha 6/26

Now, how do we go about this. First what we will do is we will define or we will state the problem for a large power system. So, what will do is we will state a general problem in which we will say that system under study has n buses, where n is pretty large. It is initially operating in a symmetrical normal state that is before the fault has occurred. The system is working in a normal state, which is basically operating and a asymmetrical loading condition. So, voltages and currents in the system are normal they are not abnormal. So, node currents are there the system voltage is or the bus voltage is at various places will be very near to their rated values.

(Refer Slide Time: 56:24)

The slide features the IIT Kharagpur logo in the top left corner. The text is centered and reads: "Although this algorithm looks straight forward there are some difficulties associated with this: The algorithm involves inversion of $(n-1) \times (n-1)$ matrix Y_{00} . For finding out the Circuit breaker ratings and relay settings we require calculation of fault currents for faults at different busses. For each of these fault calculations we will require inversion of Y_{00} matrix which will be different in each case. This is computationally very expensive." At the bottom, there are navigation icons (back, forward, search) and the text "NPTEL A.K. Sinha 18/26".

So, this is what will we have written here, that although, this algorithm looks straight forward there are some difficulties associated with this. The algorithm involves inversion of n minus 1 into n minus 1 matrix Y_{00} , for finding out the circuit breaker ratings, and relay settings. We require calculation of fault currents for faults at different busses. That is what we said at various buses we need to compute create the fault, and the find out that the fault currents and the voltages. For each of these fault calculations we will require inversion of Y_{00} matrix which will be different in each case. This is computationally very expensive and this is the main reason Y bus based algorithm for fault analysis is not much prepared. Instead the prepared the steady state bus based algorithm and we will see how this Z bus based algorithm to works.

(Refer Slide Time: 57:27)

Indian Institute of Technology, Kharagpur

Fault Analysis Using Z_{BUS} Method

Using the Thevenin's theorem the postfault Bus voltages are given by

$$V'_{bus} = V^0_{bus} + Z_{bus} I'_{bus}$$
$$I'_{bus} = \begin{bmatrix} 0 \\ 0 \\ \vdots \\ -I' \\ \vdots \\ 0 \end{bmatrix} \leftarrow \text{qth component}$$

NPTEL A.K. Sinha 17/28

So, fault analysis using Z bus method. Now, again we have seen using the Thevenin's theorem the post-fault bus voltages can be returns as V_{bus} as is equal to V_{bus}^0 plus Z_{bus} into I_{bus}^f . Now, what is this I_{bus}^f ? I_{bus}^f is basically the current injections at various points when the fault as occurred.

Now, as we have seen for Thevenin's equivalent, what we have written is that this delta V involves this delta I. This is the because of the changes which have occurred and in case of finding out the changes, we have already eliminated all generating sources. The only source which is available in the system is the voltage source at the fault point. And that is the current I_f and flowing from the bus towards the graph.

So, if we see in terms of current injection at all the other buses except the q th bus is going to be 0 and the q th bus the current injection is nothing but the negative of the fault current, because the fault current is flowing away from the bus to the ground. And since we write these equations in terms of current injections into the bus, therefore we write this as minus I_f .