

Power System Engineering
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 30
Load flow of radial distribution networks (Contd.)


So, I hope you are understanding all these, right? Things are simple, but just try to understand, not here, your, what you call, not much mathematics is there, but before that you, but you have to understand all these things.

(Refer Slide Time: 00:34)

Branch Number (jj)	Sending end node $m_1 = IS(jj)$	Receiving end node $m_2 = IR(jj)$	Nodes beyond branch jj $N(jj, u)$	Total number of nodes beyond branch-jj $N(jj)$
1	1	2	2, 3, 4, 5, 6, 7, 8	7
2	2	3	3, 4, 5, 6, 7, 8	6
3	3	4	4, 5, 6, 7, 8	5
4	4	5	5, 6, 7, 8	4
5	5	6	6, 7, 8	3
6	6	7	7, 8	2
7	7	8	8	1


So similarly, similarly when branch number say, when branch number jj is equal to 3 right. So, what will happen here? Already for jj is equal to 1 and 2, I have told you. So, I think you have understood now. One more, so once more I will tell you, when jj is equal to 3, you have to read all this data, you have to read all this data right. So, when jj is equal to 3 branch number, your m 1 will be is equal to IS jj, there will be IS 3 will be is equal to 3, that is sending inside apart branch 3, and m 2 is equal to IR jj, so m 2 will be equal to IR 3 is equal to your 4.

(Refer Slide Time: 01:10)

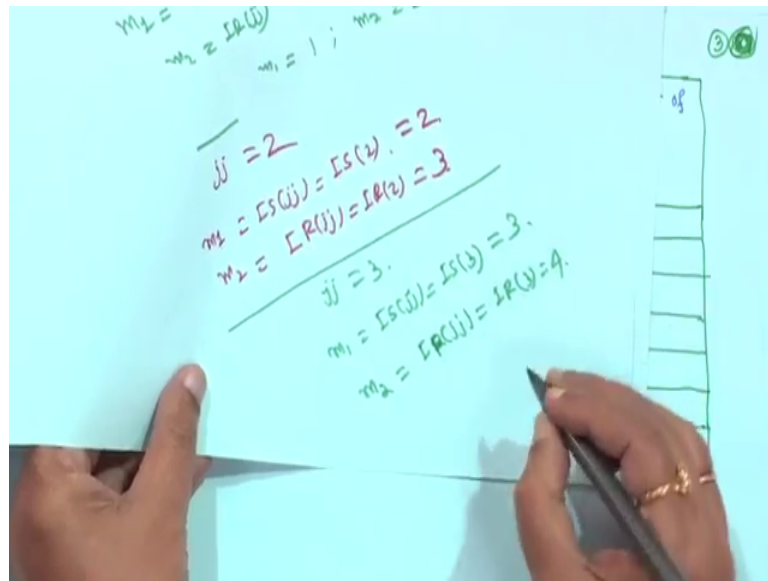

So that means, when jj , when jj is equal to 3, that is branch number 3, m_1 will be equal to IS_{jj} , is equal to IS_3 , that jj is equal to 3, that is equal to 3. So this is 3, and m_2 that is a receiving end node, that is your IS sorry, IR_{jj} , is equal to IR_3 and that is equal to 4. So, receiving end node will be 4.

(Refer Slide Time: 01:46)

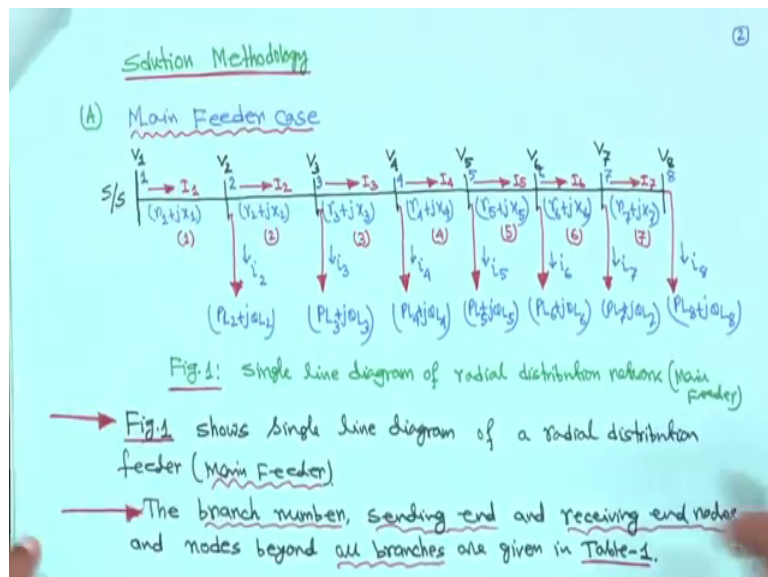

And beyond branch 3, how many nodes are there. So, this is beyond, this is branch 3. So how many nodes are there? If you look, 1, just count, 1, 2, 3, 4, 5. So, here it is 5 total nodes. And how many, what the nodes number? 4, 5, 6, 7, 8. So, node numbers are 4, 5,

6, 7, 8. This is a main feeder simple case, while you take radial branches, things will be different. At that time you will see, how simple it is. Similarly for branch 4, it is branch 4 is 4 to 5, right, branch 4 it is this one, right. So, sending end is branch 4, is your sending end node is 4 receiving end node 5, so 4, 5. And total number of nodes beyond this branch is, node numbers are 5, 6, 7, 8. So 5, beyond this branch it is 5, 6, 7, 8, right, and total nodes are 4.

Similarly for branch 5, branch 6, branch 7 right. Branch 5, for branch 5 this is sending end node, and this is receiving end node, for branch 6 this will be sending end node, this will be receiving end node, for branch 7 this will be sending end node, this will be receiving node right. So, this way you first complete this table branch number, sending end node is jj, we are writing m 1 is equal to IS jj, but you have to read jj, IS jj, then IR jj, nodes beyond branch jj, this one also.

And total number of nodes in jj, beyond branch jj, all these things, first you have to make the table right. This data, this data you have to, your, what you call, you have to, I mean marked your number than network and all the branch number, sending end, receiving end, everything, and accordingly you have to prepare the table, right. This data you have to feed it to the computer, you have to create all these things, but the procedure right. It is not Newton Raphson or Gauss seidel right. So, first you have to make this, data preparation is simple.

(Refer Slide Time: 03:40)

④

$$Z_1 = (r_1 + jx_1); \quad Z_2 = (r_2 + jx_2); \quad Z_3 = (r_3 + jx_3); \quad Z_4 = (r_4 + jx_4)$$

$$Z_5 = (r_5 + jx_5); \quad Z_6 = (r_6 + jx_6); \quad Z_7 = (r_7 + jx_7)$$

Consider branch-1, the receiving-end node voltage can be written as:

$$\rightarrow V(2) = V(1) - I(1) Z(1) \dots (1)$$


Similarly, for branch 2, 3, 4, 5, 6, 7,

$$\left\{ \begin{array}{l} V(3) = V(2) - I(2) Z(2) \dots (2) \\ V(4) = V(3) - I(3) Z(3) \dots (3) \\ V(5) = V(4) - I(4) Z(4) \dots (4) \\ V(6) = V(5) - I(5) Z(5) \dots (5) \\ V(7) = V(6) - I(6) Z(6) \dots (6) \end{array} \right.$$

Next is, your impedance of the branch, these are all given a branch 1, branch 2 r_1 plus jx_1 , r_2 plus jx_2 , and so on, these are given. So, this is actually impedance, we are putting Z_1 is equal to r_1 plus jx_1 , Z_2 r_2 plus jx_2 and so on.

There are 7 branches, because there are 8 nodes so 7 branches. Z_7 is r_7 plus jx_7 right. Now if you consider branch 1, the receiving end node voltage can be written as, consider this branch 1, similarly branch 1, if you look at the table branch 1, sending end node receiving end node right, but from the diagram it is sending end node is branch 2, 1 right, V_2 will be, V_2 will be V_1 minus I_1 into Z_1 , because Z_1 is equal to r_1 plus the x_1 . So, V_2 will be V_1 , I told you V_2 and your suffix 2 and bracket V_2 all are same, Z everything is same. Here I am writing for easy writing, that is why Z_1 , Z_2 this way writing, but everything remains same right, all I told you Z_1 actually same thing.

(Refer Slide Time: 04:43)

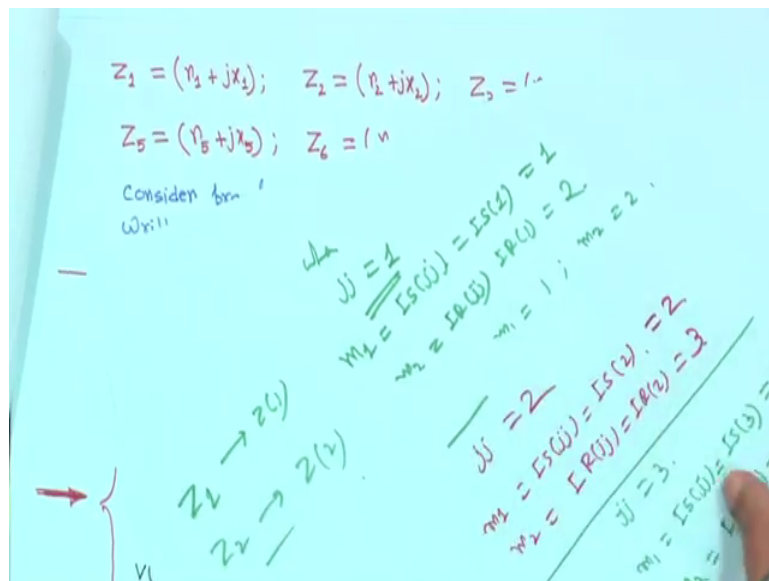

This Z_1 means Z bracket 1, same thing Z_2 means Z bracket 2 same thing right, but this I put it because, coding for the writing and making this slide node. I was thinking from the coding point of view such that, it will be the easy for you to understand right. So, V_2 will be is equal to V_1 minus $I_1 Z_1$, because this is the current flowing through this branch I_1 so V_2 will be v_1 minus, so V_2 is known now because V_1 is known, V_1 is known and say, later I will see how to compute initial values of I_1 , but for the sake of our, your, what you call, understanding, you assume that I_1 is known to you right.

Therefore V_2 is, because z impedance is known for the line right, therefore V_2 , V_1 minus $I_1 Z_1$.

Suppose if I_1 is known, Z_1 is also known, V_1 is a slag by voltage also V_2 is known. Similarly, for branch 2, you can write V_3 is equal to V_2 minus $I_2 Z_2$. So, here, because V_2 is known here, so v_2 will come here, we assume all $I_1, I_2, I_3, I_4, I_5, I_6$ all are known, you assume they all are known, how to compute initial values of i , will come later.

(Refer Slide Time: 05:52)


$Z_5 = (r_5 + jx_5); Z_6 = (r_6 + jx_6); Z_7 = (r_7 + jx_7)$
 Consider branch-1, the receiving-end node voltage can be written as:
 $\rightarrow V(2) = V(1) - I(1) Z(1) \dots (1)$
 Similarly, for branch 2, 3, 4, 5, 6, 7.
 $V(3) = V(2) - I(2) Z(2) \dots (2)$
 $V(4) = V(3) - I(3) Z(3) \dots (3)$
 $\rightarrow V(5) = V(4) - I(4) Z(4) \dots (4)$
 $V(6) = V(5) - I(5) Z(5) \dots (5)$
 $V(7) = V(6) - I(6) Z(6) \dots (6)$
 $V(8) = V(7) - I(7) Z(7) \dots (7)$

But you assume they are known say, therefore V_3 is equal to V_2 minus $I_2 Z_2$ right, similarly V_4 will be V_3 minus $I_3 Z_3$ and so on, because there say, this is, your, what you call, this is a main figure and recursive type of relationship.

Similarly, V_5 is equal to V_4 minus $I_4 Z_4$, V_6 is equal to V_5 minus $I_5 Z_5$, all equation numbers have been given, V_7 is equal to V_6 minus $I_6 Z_6$, and V_8 is equal to V_7 minus $I_7 Z_7$. Once V_2 is computed, substitute where V_3 is evaluated because these are known, we are assuming these are known right. See I think V_3 is computed, these are known so V_4 will be computed and so on, but before computing this V_1, V_2 is equal to V_1 minus $I_1 Z_1$, this the initial value of I_1 we have to compute $I_1, I_2, I_3, I_4, I_5, I_6, I_7$, these initial values we have to compute before we compute this your V_2, V_3 , but for your understanding, first I am writing this equation, after that I will show you how to compute this thing.

But in code when you write, these initial values of I_1, I_2, I_3 all I , capital I values you have to compute, before computing this equations right. As you have 7 equation that is why, in general, if last node is 8 it would have been V_{NV} is equal to $V_{NV} - 1$, and $I_{NV} - 1$, then $Z_{NV} - 1$ right, but anyway as all nodes are there, we have taken like this. So, this I_1, I_2, I_3 we have to compute right, once this is done I mean these equations are written.

(Refer Slide Time: 07:31)

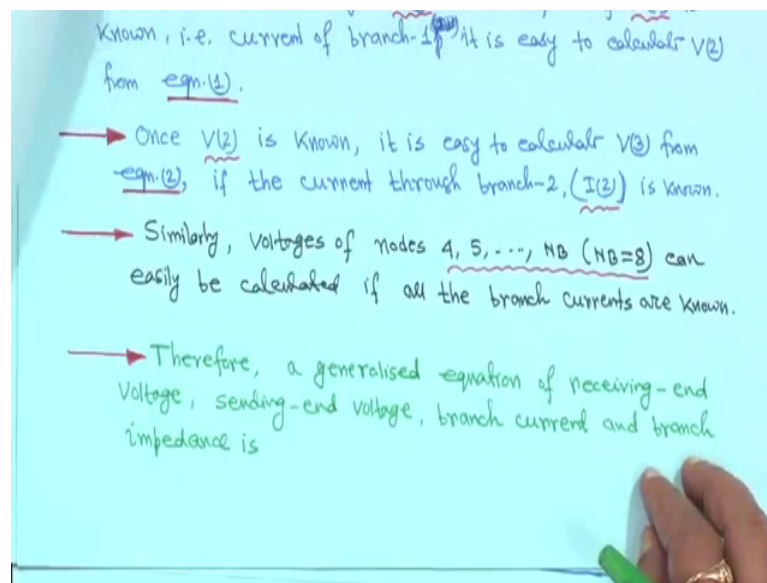


The next one is that, just for you, the other, they will make some matrix form rather than directly, because we have main figure plus main figure with lateral branches, we will come to that, that how to get the solution right, substitution voltage v_1 is known.

So, if I_1 is known; that means, if we know this I_1, I_2 everything, but for the first branch if I_1 is known, say, right. That is current of branch 1, it is easy to compute V_2 from equation 1, V_2 from equation 1, and V_2 can easily computed because if I_1 is known right. Similarly once V_2 is known, it is, V_2 is known, easy to calculate V_3 if I_2 is known because, Z impedances are known for you right.


So, therefore, voltages, similarly voltages are node 4 5 up to node NB, in this case total number of node NB is equal to 8, for this example, I mean the diagram, whatever you have taken we have 8 node. So, NB is equal to 8, can easily be calculated if all the branch currents are known right.

(Refer Slide Time: 08:43)

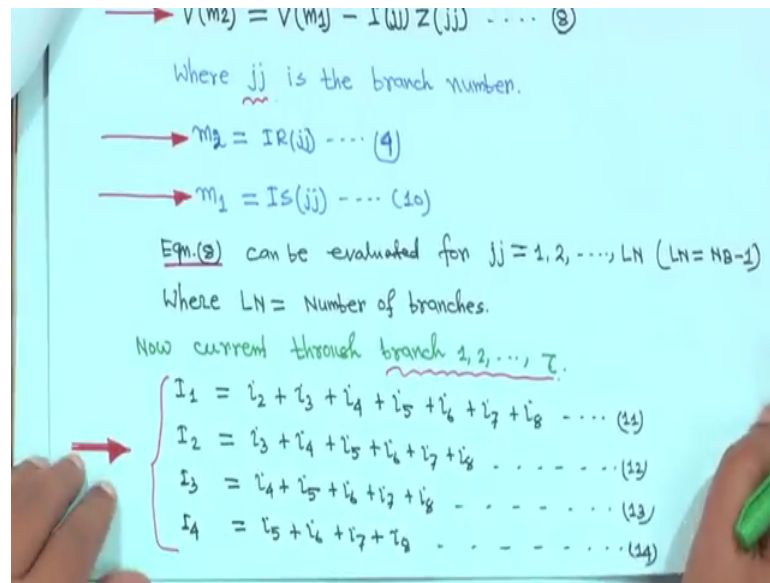

Therefore, a generalized equation of receiving-end Voltage, sending-end Voltage, branch current and branch impedance is, therefore you have to write a generalized equation. So, generalized equation will be $V m 2$ is equal to $V m 1$ minus $I jj Z jj$ right, but $I jj$ is not computed here, you have to do, but how you will do it? When we write the code right, like for j is equal to 1 to LM .

(Refer Slide Time: 08:56)

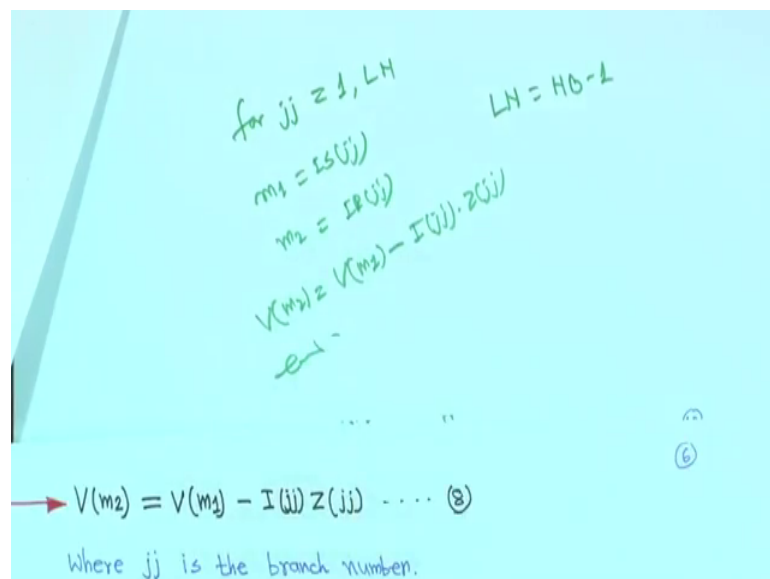

LM is the total number of branches, that is LM actually is equal to NB minus 1 right, NB is the total number of nodes. So, branch number will be one less.

So, it will be $NB - 1$, for jj is equal to 1, LM, then what you define? You define m_1 is equal to sending end node IS jj .

And you define, m_2 is equal to IR_{jj} right, after that you write, V_{m_2} is equal to V_{m_1} minus your I_{jj} into Z_{jj} and LM right. Because this table you are reading, this table, whatever we have made this table, all branch number, sending end node, receiving end node, beyond branch jj and total number of nodes, all you are reading as data, this also will be required later, but m_1 is IS jj into all these things are reading. So, when you write code or something you write for j is equal to 1 to LM, then put m_1 is equal to sending end node IS jj , and automatically after reading this, it will take, those were writing code you know, it will take. And m_2 is equal to IR_{jj} , then you write V_{m_2} is equal to V_{m_1} minus I_{jj} into Z_{jj} this is end.

So this is automatically, all the, your, receiving end voltages for each branch we will be computed. It is always 1, 2, 3, 4 lines only, 5 lines, if you write the code. And your, what you call, you read those data so; that means, here, here in that, here I have not written there here right. So, here I am writing only V_{m_2} is equal to V_{m_1} minus I_{jj} , I told you that how to write the coding part, right.

Where m_2 is equal to IR_{jj} , m_1 is equal to IS jj therefore, equation 8 can be evaluated for jj is equal to 1 to LN, I just told you for jj is equal to 1 to LN, this thing only, this thing only right, where LN is equal to number of branches, that is LN is equal to here I have written that is $NB - 1$. Now you have to, you have to compute the, now, current through branch 1 to 7.

Because you have this diagram, this diagram you have 7 branches 1, 2, 3, 4, 5, 6, 7. Now what is I_1 ? You apply Kirchhoff's first, I_1 is equal to this i_2 , what about the current going to the load? i_2 plus i_3 plus i_4 plus i_5 plus i_6 plus i_7 plus i_8 , this is, you just apply Kirchhoff's first law. So, our I_1 is equal to the current branch 1, 2, up to 7, 7 branches are there.


So, I_1 is equal to, whenever writing here, I am putting suffix, I am not putting in bracket, but when I will see the mathematics I will put them in brackets, but they are same, there should not be any sort of confusion right. So, I_1 is equal to i_2 plus i_3 plus i_4 plus i_5 plus i_6 plus i_7 plus i_8 ; that means, this i_2 , i_3 , i_4 all you have to compute, will come in the next step right, we will come later.

So, this is the equation 11, similarly that branch current I_2 , this is your I_2 , I_2 is equal to actually i_3 plus i_4 plus i_5 plus i_6 plus i_7 plus i_8 .

Because, this is the current I_2 entering into this, entering here. So, this current, will go, basically it is going here only, this current right. So, Kirchhoff's first law again. So, I_2 will be i_3 plus i_4 plus i_5 plus i_6 plus i_7 plus i_8 , this is equation 12. Everything I have made it here, such that you should understand this, right. Then I_3 , this is the branch current, I_3 is equal to i_4 plus i_5 plus i_6 plus i_7 plus i_8 again Kirchhoff's first law. So, it is i_4 plus i_5 plus i_6 plus i_7 this is equation 13 say.

Similarly, branch 4 current, it will be i_5 plus i_6 plus i_7 plus i_8 , it is I_4 is equal to i_5 plus i_6 plus i_7 plus i_8 , this is equation 14 right. Similarly current through branch 5, I mean current through branch 5, I_5 , this one, it will be i_6 , i_7 plus i_8 .

(Refer Slide Time: 13:05)

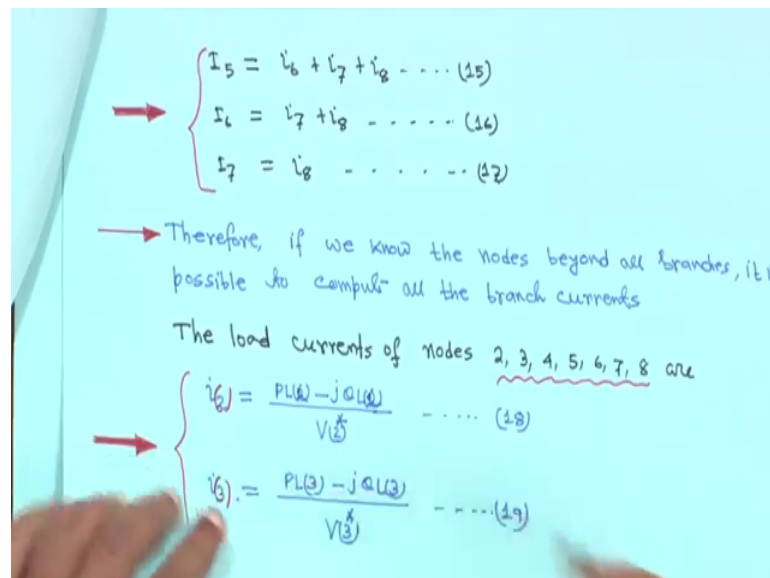

So, I_5 is equal to, your, it is i_6 plus i_7 plus i_8 , this is a question 15. Similarly I_6 is equal to the current through branch, so it will be i_7 plus i_8 Kirchhoff's first law only right, but I am not writing I_6 is equal to i_7 plus your, what you call, your I , your this small I is I_6 also is equal to the small i_7 plus capital I_7 , here also I_1 is equal to capital I_2 plus small i_2 .

But again I_2 is equal to, if you write i_3 plus capital I_3 , ultimately it will be sum of all these, all these currents right. So, what we our objective is, the branch current can be

represented by the load current, but I am not writing I_1 is equal to I_2 plus, a capital I_2 plus small i_2 , do not do that, then you have to write many more equations. So, only this load current right, because this current will be all these things.

So, but if you again put I_2 is equal to I_3 plus i_3 , ultimately we will find I_1 is equal to your, i_2 plus i_3 plus i_5 are to summation of I_8 right. So, do not do that. So, similarly I_6 is equal to your, i_7 plus i_8 this load current.

Ultimately this current is, this current, you can say i_7 plus capital I_7 , but capital I_7 will be small i_8 , ultimately i_7 plus i_8 , same is applicable here. So, do not consider this, I_1 means all this current, Kirchhoff's law, I_1 is equal to capital I_1 is equal to capital I_2 plus small i_2 . Again you will try to put this way, but directly you can put this, ultimately it will be same right, that is why all these things are made. So, similarly capital I_7 that is the last one is equal to small i_8 , because this is the current actually going to the load because no other branches beyond that right. So, it is i_8 . So, and in terms of power, it is given PL_2 plus because this data will be known right.

So, these are all branch current mathematics, I mean simple thing, very simple thing. This last one is equation 17, now therefore, if we move the nodes beyond all branches, it is possible to compute all the branch current; that means, this table, if you know all these nodes beyond all branches, then article, if branch 1 current can be computed; that means, if branch 1, beyond branch 1, these are the node 2, 3, 4, 5, 6, 7, 8.

Therefore, capital I_1 is equal to, it is small i_2 plus i_3 plus i_4 plus i_5 plus i_6 plus i_7 plus i_8 , if you know beyond branch 2, all these your nodes, then it will be capital I_2 , the current, will be small i_3 plus small i_4 plus small i_5 plus small i_6 plus small i_7 plus small i_8 , whatever we have just seen. Similarly all this thing, capital I_7 will be is equal to actually your small i_8 right, sending end, receiving end this way you have moved right.

That is why we have written, capital I_7 is equal to small i_8 ; that means, that is why this is necessary, that nodes beyond branches, this is necessary. You have to make this table, you have to read this data and similarly, but no variable is given, why not given I will come later, how we have given this right. And similarly, total number of nodes this one you have to make it right. So, question is that, this, here I have kept blank, when I will explain at that time, I put something here, at that time, things will be understandable,

right. So now, the load current of node, load currents of your node 2, so look, this is, this is the node had voltage V_2 , this is the V_2 , and this is the load connected PL_2 plus jQL_2 , I_2 is the current going to the load.

So, you know no, from load flow studies, in general p minus j q is equal to V conjugate i , we have studied in our power system analysis load flow studies therefore, you can write PL_2 , when you put in mathematics PL_2 minus jQL_2 is equal to V_2 conjugate into i_2 , that is why we were writing, here I am not putting in this thing, what you call, this one I am putting in bracket, but this one here, I have not put it in bracket, but later I have made it right, later, later, I have made it.

So, what we have done is, later I will give you, this generalized thing is given i_2 is equal to this one PL_2 and your QL_2 , that suffix 2 and bracket 2, all are same, but here I did not put in bracket, later I have generalized, at the time I put them in bracket. So, i_2 is equal to PL_2 minus jQL_2 upon V_2 conjugate, voltage also and putting them in bracket right. If you want, you can make it in bracket no problem, but I have not done it. So, i_3 is equal to PL_3 minus jQL_3 , V_3 conjugate ; that means, here your, your this, this load is connected to that node 3, V_3 is the voltage and i_3 is the current therefore, i_3 is equal to PL_3 minus jQL_3 upon V_3 conjugate, this is equation 19.

(Refer Slide Time: 18:02)

The image shows a list of handwritten equations for load currents at different nodes. A red arrow points to the equations, and a red bracket groups them. The equations are:

$$i_4 = \frac{PL_4 - jQL_4}{V_4^*} \dots (20)$$

$$i_5 = \frac{PL_5 - jQL_5}{V_5^*} \dots (21)$$

$$i_6 = \frac{PL_6 - jQL_6}{V_6^*} \dots (22)$$

$$i_7 = \frac{PL_7 - jQL_7}{V_7^*} \dots (23)$$

$$i_8 = \frac{PL_8 - jQL_8}{V_8^*} \dots (24)$$

Similarly your, all i_4, i_5, i_6, i_7, i_8 all you can compute; that means, that means, i_4 is equal to PL_4 minus jQL_4 upon V_4 conjugate, i_5 is equal to PL_5 minus jQL_5 upon V_5 conjugate, i_6 is equal to PL_6 minus jQL_6 upon V_6 conjugate.

And all the equation numbers are given, i_7 is equal to PL_7 minus jQL_7 upon V_7 conjugate, and i_8 is equal to PL_8 minus jQL_8 , V_8 conjugate.

Now if you want, if you want, here also, this one also you can put in bracket right. If I want to say, this is, this is my i_2 , this is my i_3 in brackets say, all are in bracket say, this is i_4 , this is i_5 , this is i_6 , instead of suffix, I am putting in bracket, actually it is say, i_6 right, this is your i_7 , this is your i_8 right. You can put it like this; that means, in general, in general; that means, $i_2, i_3, i_4, i_5, i_6, i_7, i_8$ all can be computed.

How it will be computed? Because you have to know, because, PL, QL known, but V_2, V_3 all are not known. So, load flow studies you know that your flat voltage start. So, for V_2, V_3 whatever is the slack bus voltage, for all these initial values of V_2, V_3, V_4 , all these voltages will be your consider as the slack bus voltage, initial one, such that initial values of i_2, i_3 all can be computed, we will come to that right.

(Refer Slide Time: 19:27)

The load current of node 'p' is

$$\vec{i}_p = \frac{PL(p) - jQL(p)}{V_p^*} \dots (25), \quad p = 2, 3, \dots, 8$$

OR

$$\vec{i}_p = \frac{PL(p) - jQL(p)}{V(p)} \dots (26), \quad p = 2, 3, \dots, 8$$

From Table-1,
~~Table-1~~ Table-2

Br. No. (i)	Nodes beyond branch-j	Total number of nodes $N(i)$ beyond branch-j
1	2, 3, 4, 5, 6, 7, 8	$N(1) = 7$
2	3, 4, 5, 6, 7, 8	$N(2) = 6$
3	4, 5, 6, 7, 8	$N(3) = 5$
4	5, 6, 7, 8	$N(4) = 4$
5	6, 7, 8	$N(5) = 3$
6	7, 8	$N(6) = 2$
7	8	$N(7) = 1$

Therefore, the load current of say, node p, it can be written as i_p , again I have writing, PL_p minus jQL_p upon your V conjugate p in bracket. So, this one also, if you want you


can put it in bracket, no problem right here, but anyway for general thing, it is p is equal to 2, 3, 8 because it is a currents are at 2, 3, 4.

So, here I am writing, i_p is equal to PL_p minus jQL_p upon V conjugate p , where p is equal to 2, 3, 8. If you put p is equal to 2, you will get i_2 value, if you get p is equal to 3, but initial values are known right now, question is that again I have made this table, you have just understand, very easy actually, very easy right. Now branch number jj 1, 2, 3, 4, 5, 6, 7 right.

There are 7 branches, and nodes beyond branches, all these things where given in the table right, or in this table it is given, all these things are given, all these things are given. So, just rewriting, on the, this sending end, receiving end, not putting in the table 2 right. Only these nodes I am putting, these notes I am putting.

So, these are the nodes are given, and total number of nodes here given, total number of nodes N_{jj} beyond branch jj , it is given 7, 6, 5, 4, 3, 2, 1 in this case; that means, when jj is equal to 1, N_1 is equal to 7, when jj is equal to 2, N_2 is equal to 6, when jj is equal to 3, N_3 is 5 and so on. That is why here, I am writing N_1 is equal to 7, N_2 is equal to 6, and N_3 is equal to 5, N_4 is equal to 4, N_5 is equal to 3, N_6 is equal to 2, and N_7 is equal to 1; that means, this thing we are putting again in better form that this one only, this one and this one same, this one and this one they are same right, and this is the branch number and this is the branch number right. So, this way we were putting, then this is my N_1 , N_2 , N_3 . I hope this is understandable right.

(Refer Slide Time: 21:31)

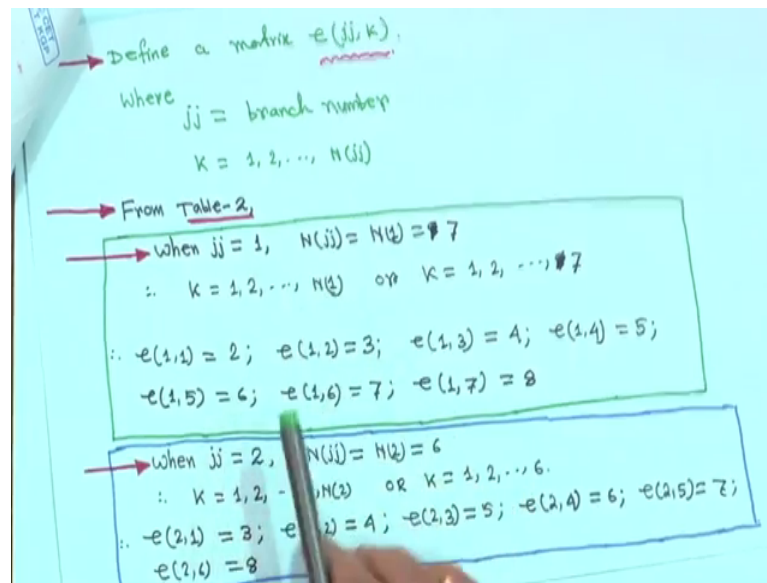

Next one is, now we have to define a matrix $e_{jj, k}$; that means, they are that nodes beyond branch jj , you have to store this in a matrix, in a matrix right. So, here nodes beyond branch jj is given, but this whole matrix you have to store in a matrix form because, you have to read the data in the computer. So, what you have to do is, Newton Raphson's so many things we have seen in algorithm right.

So, here this data you have to store in a computer. So, you have to put this in a, in an array, in a matrix form that will be better.

So, you, what we define? We define a matrix say e is equal to, sorry matrix $e_{jj, k}$ right, your, this is the matrix say jj, k , where jj is the branch number and k will vary from 1, 2, 1, 2 up to N_{jj} right; that means, this thing, these whole thing actually the matrix, it is in the form, these whole thing is a matrix, the here also, here also, these whole thing you put in a matrix right.

Here if we write that thing, that will be actually $e_{jj, k}$ right, this is the whole thing we are putting in a matrix. So, here also it whole thing actually jj, k , this whole thing we will put in a matrix, it will be $e_{jj, k}$. Here I am not writing, but here it is actually $e_{jj, k}$, this way you to make, but how to take it, how to take it, how to put it in an array right.

What we will do is this all, this total number is given nodes beyond branch jj is given right, but let me tell you identification of nodes beyond all branches, algorithm is there, and we know, the, and the identification of branches beyond branch jj , identification algorithm is there right, but I am not here, I, we do not want to make that your, identification algorithm, just if you have the single line diagram will not work, you can prepare the data, and you can easily get the solution by reading this data.

But this node also can be identified by identification algorithm, but that algorithm I thought in the classroom purpose, better not to discuss. So, this thing I have made it of my own, that how to give the data such that your things will easier right. So, identification algorithm is there.

But question is that, we are not showing it here, just we will see that, put this data in an array and see that how things are, things can be computed. So, for example, this matrix; that means, whole data we are keeping in a matrix e_{jjk} . So, this is actually given jj is branch number and k equal to $1, 2, N_{jj}$ for example, when jj is equal to 1 , N_{jj} is equal to $N - 1$, is equal to 7 , because this is the total nodes, the N_{jj} is the total node beyond branch jj . So, you have for j is equal to, jj is equal to 1 , $N - 1$ is 7 because here you have 7 nodes, you mark those 7 nodes right therefore, why I have taken this e_{jjk} matrix, e_{jjk} matrix because, if you, in that case if lateral branches will be there.

So, same matrix e_{jjk} will be used and automatically it will, automatically data, data will be read right. So, for example, when jj is equal to 1 then N_{jj} is equal to $N - 1$ is equal to 7 . And therefore, k is equal to 1 to N_{jj} ; that means, k is equal to $1, 2$ up to $N - 1$ or k is equal to $1, 2$ up to 7 right; that means, that when jj is equal to 1 , it is $e_{1,1}, e_{1,2}, e_{1,3}, e_{1,5}, e_{1,6}, e_{1,7}$; that means, your $e_{1,1}$ read this data, you have to read it, $e_{1,1}$ is equal to 2 .

So, when jj is equal to 1 , $e_{1,1}$ which 2 , then $e_{1,2}$ is equal to 3 , $e_{1,2}$ is equal to 3 , that $e_{1,3}$ is equal to 4 , then $e_{1,3}$ is equal to 4 , then $e_{1,4}$ is equal to 5 , this is the fourth element, $e_{1,4}$ is equal to 5 , is the fifth element, $e_{1,5}$ which equal to 6 this is given, then this is, if this is that you sixth element, $e_{1,6}$ is equal to 7 , $e_{1,6}$ is equal to 7 , this seventh element, $e_{1,7}$ is equal to 8 . So, this is that your $e_{1,1}, e_{1,2},$ up to $e_{1,7}$ because k is varying from 1 to up to N_{jj} and, j you are changing right, j you are changing and; that means this, for jj is equal to 1 , these are the element, these are the data

you have to read in the computer rather than identification algorithm you will find these things quite easier, quite easier right.

When jj is equal to 2, that is N_{jj} is equal to N^2 is 6 ; that means, here if there are 6 numbers, so n^2 is equal to 6 right. Therefore, even jj is equal to 2 means, it will be $e_{2,1}$ because jj is equal to 2, your matrix is your $e_{jj,k}$. So, when jj is equal to 2 into 6 right, because N_{jj} is equal to N^2 is 6 right, and k is varying 1, 2 up to N^2 , or N^2 is equal to 6 1, 2 up to 6, and jj is equal to 2 because your matrix is jj,k right. So, you can write $e_{2,1}$ is equal to 3. So, $e_{2,1}$ is equal to 3 the second row here.

Then $e_{2,2}$ is equal to 4, $e_{2,2}$ is equal to 4, then your $e_{2,3}$, $e_{2,3}$ is equal to 5. Therefore, $e_{2,3}$ is equal to 5, then your $e_{2,4}$ is equal to 6, $e_{2,4}$ this is a fourth element 6, then $e_{2,5}$ is 7, $e_{2,5}$ it is, it is your, what you call, it is 7, $e_{2,5}$ is equal to 7, and then your $e_{2,6}$ is equal to 8, $e_{2,6}$ is equal to 8, this element first you identify, and put this, read this in the computer, all this data $e_{1,1}$ e_{e} or e_{e} matrix we have to read this data in the computer; so, similarly $e_{2,5}$ 7, $e_{2,6}$ 8.

Thank you very much, we will be back.