

Power System Engineering
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture – 36
Load flow of radial distribution networks (Contd.)

So, after second iteration we have just seen that, voltage V2 is 0.98578 angle is of course, in distribution system very small.

(Refer Slide Time: 00:21)

Handwritten calculations on a light blue background:

$$\therefore V_4 = 0.965882 + j0.0062019 - 0.007552 \angle -33.16^\circ \times 1.96 \angle 22.56^\circ$$

$$\therefore V_4 = 0.965882 + j0.0062019 - 0.0148019 \angle -10.6^\circ$$

$$\therefore V_4 = 0.965882 + j0.0062019 - 0.014549 + j0.0027228$$

→ $V_4 = 0.951333 + j0.0089247$

→ $V_4 = 0.95137 \angle 0.54^\circ \text{ pu}$

After 2nd Iteration

$$V_2 = 0.98578 \angle 0.085^\circ \text{ pu}$$

$$V_3 = 0.96590 \angle 0.36^\circ \text{ pu}$$

$$V_4 = 0.95137 \angle 0.54^\circ \text{ pu}$$

So, 0.085-degree V3 is equal to 0.96590 angle 0.36 degree and V4 is equal to 0.95137 angle 0.5 these, are all in per unit, right? All calculations are in per unit, right? Everywhere I have not written per unit. So, here again you can see that all the angles are leading angle and I ask you also that why instead of negative, why this positive angle is coming? Answer is very simple, but you please find out, what is a I mean why it is coming leading angle for this example right?

(Refer Slide Time: 01:06)

Power Loss After 2nd iteration

$$\rightarrow P_s - jQ_s = V_1^* I_1 = 1 \angle 0^\circ \times 0.01922 \angle -35.98^\circ$$

$$\rightarrow P_s - jQ_s = 0.0155748 - j0.011266$$

$$\rightarrow P_s = 0.0155748 \text{ pu} = (0.0155748) \times (\text{MVA})_B \times 1000 \text{ kW}$$

$$\rightarrow P_s = (0.0155748) \times (100) \times 1000 \text{ kW}$$

$$\rightarrow P_s = \underline{1557.48 \text{ kW}}$$

Similarly

$$\rightarrow Q_s = (0.011266) \times (100) \times 1000 \text{ kVAR}$$

$$\rightarrow Q_s = \underline{1126.6 \text{ kVAR}}$$

$$\therefore \text{SP}_{\text{Loss}} = 1557.48 - (400 + 500 + 600) = \underline{57.48 \text{ kW}}$$

$$\text{Loss} = 1126.6 - (300 + 400 + 400) = \underline{26.6 \text{ kVAR}}$$

(Refer Slide Time: 01:18)

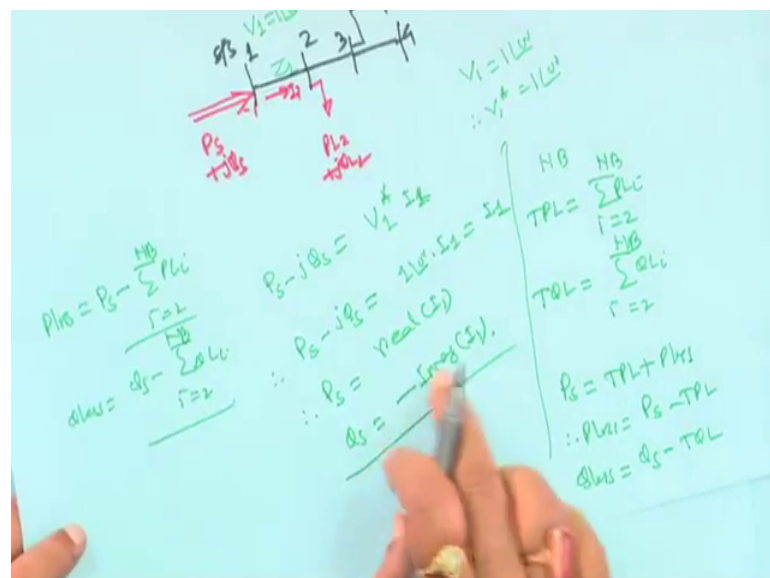


Diagram illustrating power flow and loss calculation in a distribution network.

At node 1 (Substation):

$$P_s - jQ_s = V_1^* I_1$$

$$P_s - jQ_s = 1 \angle 0^\circ \cdot I_1 = I_1 \angle -35.98^\circ$$

$$\therefore P_s = \text{Real}(S), Q_s = -\text{Imag}(S)$$

At node 2:

$$P_2 - jQ_2 = V_2^* I_2$$

$$P_2 - jQ_2 = 1 \angle 0^\circ \cdot I_2 = I_2 \angle -35.98^\circ$$

$$\therefore P_2 = \text{Real}(S), Q_2 = -\text{Imag}(S)$$

At node 3:

$$P_3 - jQ_3 = V_3^* I_3$$

$$P_3 - jQ_3 = 1 \angle 0^\circ \cdot I_3 = I_3 \angle -35.98^\circ$$

$$\therefore P_3 = \text{Real}(S), Q_3 = -\text{Imag}(S)$$

At node 4:

$$P_4 - jQ_4 = V_4^* I_4$$

$$P_4 - jQ_4 = 1 \angle 0^\circ \cdot I_4 = I_4 \angle -35.98^\circ$$

$$\therefore P_4 = \text{Real}(S), Q_4 = -\text{Imag}(S)$$

At node 5:

$$P_5 - jQ_5 = V_5^* I_5$$

$$P_5 - jQ_5 = 1 \angle 0^\circ \cdot I_5 = I_5 \angle -35.98^\circ$$

$$\therefore P_5 = \text{Real}(S), Q_5 = -\text{Imag}(S)$$

At node 6:

$$P_6 - jQ_6 = V_6^* I_6$$

$$P_6 - jQ_6 = 1 \angle 0^\circ \cdot I_6 = I_6 \angle -35.98^\circ$$

$$\therefore P_6 = \text{Real}(S), Q_6 = -\text{Imag}(S)$$

Power loss calculation:

$$P_{\text{Loss}} = P_s - \sum_{i=2}^6 P_i$$

$$Q_{\text{Loss}} = Q_s - \sum_{i=2}^6 Q_i$$

Alternatively, using TPL (Total Power Loss):

$$P_{\text{Loss}} = P_s - \sum_{i=2}^6 P_i$$

$$Q_{\text{Loss}} = Q_s - \sum_{i=2}^6 Q_i$$

Next is that power loss calculation, right? What will be the power loss? There are mainly your 2, 3 ways of computing power losses, right? One is that, suppose you have a distribution network I will show you the 2 different ways, right? At least 2, 3 ways, this suppose you have a power network distribution network like this, this is your substation, this node is 1, suppose this is 2 3 4 5 and 6 this is the distribution network, right? And current flowing through this first branch, very first branch this is you say I 1 everywhere load is there, I mean everywhere for example, here it is P 1 2 plus j Q 1 2 say similarly

here, $P_{l3} + jQ_{l3}$ and so on, everywhere loads are there I am not showing here, but everywhere loads are there.

Suppose net injected power is power coming to the substation, this substation actually power coming from the grid to the substation, suppose it is $P_s + jQ_s$, right? And it is a your impedance of this branch very first branch say it is Z_1 . So, whatever, but from the load flow studies, you know this your how to call that branch current I_1 and this voltage substation voltage is known to you, this voltage is V_1 is equal to in this case one angle 0 we have taken.

So, then this current is also known from the load flow studies, then what you can do is, you can write this equation $P_s - jQ_s$ is equal to $V_1 \text{ conjugate } I_1$ this is the power coming from the grid to a substation. So, you can write that, the I you have studied, in the load flow studies $P_l - jQ_l$ is equal to $V \text{ conjugate } I$. So, $P_s - jQ_s$ is equal to $V_1 \text{ conjugate } I_1$, this is the current this I_1 , right? And the I_1 current is known to you, then V_1 is equal to 1 angle 0 degree therefore, $V_1 \text{ conjugate}$ is also 1 angle 0 degree; that means, my $P_s - jQ_s$ is equal to your 1 angle 0 degree into I_1 is equal to I_1 everything is in per unit therefore, P_s is equal to real part of I_1 , right?

And Q_s is equal to minus imaginary part of I_1 , because it is $P - jQ$. So, $P_s - jQ_s$ is equal to I_1 . So, it is minus imaginary of I_1 ; that means, this P_s and Q_s coming from the grid, are entering into this your what to call substation and; that means, this power is equal to whatever loads are there, whatever suppose you have N_B number of nodes and you have all the $P_l - jQ_l$ is known. So, what will be the then total load.

Say total load will be TPL will be your $\sum_{i=1}^{N_B} (P_{li} - jQ_{li})$ and this is P_{li} this is the total load and total reactive load, this is real power load it is Q_{li} equal to 2, to N_B right; that means, this is the injected power and injected power P_s actually is equal to total power TPL plus total power loss right; that means, P_{loss} is equal to P_s minus total real power load.

Similarly your Q_{loss} is equal to Q_s minus total reactive power load; that means your P_{loss} is equal to the power injected at the substation, that is P_s minus that total TPL right? That is total real power load, this is the P_{loss} and Q_{loss} is equal to Q_s minus $\sum_{i=1}^{N_B} Q_{li}$ this is the power loss, right? So, this is in per unit, whatever you will get P_s or loss everything is in per unit. So, you have chosen 100 MVA base

(Refer Slide Time: 05:32)

$$P_{\text{res}} = P_s - \frac{\sum_{i=1}^N P_{\text{res}}}{\sum_{i=1}^N 1}$$

$$P_{\text{res}} = P_s - \frac{\sum_{i=1}^N P_{\text{res}}}{N}$$

$$P_{\text{res}} = P_s - \frac{P_{\text{res}} \cdot N}{N}$$

$$P_{\text{res}} = P_s - P_{\text{res}}$$

$$2P_{\text{res}} = P_s$$

$$P_{\text{res}} = \frac{P_s}{2}$$

If you multiply it by M V A base then it will be megawatt, then this quantity if you multiply by 1000 it will be kilowatt, right? Therefore, real of I 1 into M V A base into your 1000, that is kilowatt and M V A base is 100; that means, this quantity this whole quantity hold on I am writing here this whole quantity P s, right? Is equal to real of I 1 then into 100 M V A base into 1000 this is kilowatt; that means, P s is equal to real of I 1 into 10 to the power 5 kilowatt.

(Refer Slide Time: 06:05)

$$\begin{aligned}
 P_s &= \{ \text{real}(I_1) \} \times (100) \times (1000) \text{ kW} \\
 \therefore P_s &= \{ \text{real}(I_1) \} \times 10^5 \text{ kW} \\
 Q_s &= -\{ \text{Imag}(I_1) \} \times 10^5 \text{ kVar} \\
 \hline
 P_{\text{loss}} &= P_s (\text{kW}) - TPL (\text{kW}) \\
 Q_{\text{loss}} &= Q_s (\text{kVar}) - TQL (\text{kVar})
 \end{aligned}$$

Similarly, Q_s also will be minus imaginary of I_1 , right? Into 10 to the power 5 kilo hour, right? So, this way this is one way, another way I square unless you can compute. So, this way, you can compute; that means, your power loss that real power loss P_{loss} is equal to, if you put like this that is your P_s , suppose if it is in kilowatt minus total load TPL that is also in kilowatt, that will be P_s loss right that that; that means, TPL sum of all the your real power load, similarly Q_{loss} also it is Q_s , if it is in kilo hour minus TQL then your kilo hour.

So, this is P_{loss} and this is Q_{loss} , right? So, this way you can compute, same way I have made it here for you, that power loss after second iteration, of course this is not exact, because we have to move few for few iterations another 1 or 2. So, here also you are writing P_s minus $j Q_s$ is equal to V_1 conjugate I_1 . So, I told you V_1 is 1 angle 0. So, V_1 conjugate 1 angle 0 and this I_1 is actually g after second iteration we have seen it is 0.01922 angle minus 35.8 degree; that means, P_s minus $j Q_s$ is equal to 0.0155748.

I have taken up to 6 7 decimal places for more accuracy, but for assignment or for exam purpose if something like is there, I will suggest you consider only up to 4 or 5 decimal places, do not go beyond that right? Minus $j 0.011266$ right; that means, P_s will be real of this one is 0.155758 per unit is equal to this is the value, into multiplied by MVA base into 1000 kilowatt just in showed you, but MVA base is 100. So, it is P_s is equal

to 0.0155748 into 100 into 1000 kilowatt, that is total input power to the substation real power 1557.48 kilowatt, right?

Therefore, similarly Q_s will be, this is your Q_s is equal to minus your imaginary of this one. So, didn't generally Q_s will be just compare the real and imaginary. So, Q_s is 0.011266 into base MVA 100 into 1000 kilo hour right? Therefore, Q_s will be 1126.6 kilo hour; that means, this is power input and load is; that means, total power loss P_{loss} is I am writing sum of power loss, previous thing I wrote P_{loss} are $s P_{loss}$ same, sum of power loss is equal to total your power loss that is 1557.48, just now we got this one minus the total load that, $P_L 2$ plus $P_L 3$ plus $P_L 4$. So, it is in kilowatt.

So, 57.48 kilowatt similarly Q_{loss} will be 1126.6 kilowatt minus $Q_L 2$ plus $Q_L 3$ plus $Q_L 4$ whatever load was there. So, loss is coming 26.6 kilo hour, after your second iteration, right? This way loss can be computed. So, here a during the iterative process, I didn't check any convergence thing or anything, because there I have to one more iteration. I request you to do the next iteration, of yourself right? So, that is why iteration means that what we the loss was the difference of the loss in successive iteration and take their absolute value, and if it is less than said 10 to the power minus 3 or minus 4 in terms of kilowatts say, then you assume the solution has converged.

But when we will take I square all loss I will show you also I square all loss for 3, there are 3 branches when I take I square all loss you find there is a difference is there, because it is not a converse solution right? Still one or 2 iteration required.

(Refer Slide Time: 10:44)

Other Technique for Loss Calculation. (56)

$$\rightarrow S_{P_{Loss}} = (|I_1|^2 r_1 + |I_2|^2 r_2 + |I_3|^2 r_3) \times (MVA)_B \times 1000 \text{ KW}$$

$$\therefore S_{P_{Loss}} = \left((0.01922)^2 \times \frac{0.78}{1.21} + (0.01415)^2 \times \frac{1.62}{1.21} + (0.00755)^2 \times \frac{2.19}{1.21} \right) \times 10^5$$

$$\rightarrow S_{P_{Loss}} = \underline{60.94 \text{ KW}}$$

Similarly

$$\rightarrow S_{Q_{Loss}} = (|I_1|^2 x_1 + |I_2|^2 x_2 + |I_3|^2 x_3) \times 10^5 \text{ KVAR}$$

$$\therefore S_{Q_{Loss}} = \left((0.01922)^2 \times \frac{0.45}{1.21} + (0.01415)^2 \times \frac{0.66}{1.21} + (0.00755)^2 \times \frac{1}{1.21} \right) \times 10^5$$

$$\rightarrow S_{Q_{Loss}} = \underline{28.94 \text{ KVAR}}$$

So, another thing is that your I square r. So, there are 3 branches. So, it is mod I 1 square r 1, plus magnitude I 2 square r 2, plus magnitude I 3 square r 3, everything is a per unit multiplied by M V A base multiplied by thousand kilowatt, right? So, magnitude is 0.01922 square and your r 1 is it actually value was 0.78 ohm.

So, I have divided by their base in impedance 1.21, right? Similarly, here also this is the I 2 square this is the magnitude of I 2, all you have calculated after second iteration into this is a exact value of up to 1.62 ohm by base impedance 1.21, similarly here also these the magnitude of current square current square into 2.19 up 1.21, when M V A base is M V A base is 100. So, multiplied by 10 to the power 5 therefore, total power loss here it is coming 60.94 kilowatt, but here it was 57.48 kilowatt.

(Refer Slide Time: 11:40)

$$\begin{aligned} \rightarrow SP_{Loss} &= (|I_1|^2 r_1 + |I_2|^2 r_2 + |I_3|^2 r_3) \times (MVA)_B \times 1000 \text{ KW} \\ \therefore SP_{Loss} &= \left((0.01922)^2 \times \frac{0.78}{1.21} + (0.01415)^2 \times \frac{1.62}{1.21} + (0.007552)^2 \times \frac{2.19}{1.21} \right) \times 10^5 \\ \rightarrow SP_{Loss} &= \underline{60.94 \text{ KW}} \end{aligned}$$

Similarly

$$\begin{aligned} \rightarrow SQ_{Loss} &= (|I_1|^2 x_1 + |I_2|^2 x_2 + |I_3|^2 x_3) \times 10^5 \text{ KVAR} \\ \therefore SQ_{Loss} &= \left((0.01922)^2 \times \frac{0.45}{1.21} + (0.01415)^2 \times \frac{0.66}{1.21} + (0.007552)^2 \times \frac{0.91}{1.21} \right) \times 10^5 \\ \rightarrow SQ_{Loss} &= \underline{28.94 \text{ KVAR}} \end{aligned}$$

What this difference is? Because the solution has not yet converged, when you take say another iteration or another 1 or 2 iterations. So, in solution will converge, you will find the calculating these way this loss or calculating these way this loss both will be same identical right?

Similarly, that total Q loss I there is magnitude I 1 square x 1, I 2 square x 2, plus I 3 square x 3, into 10 to the power 5 kilo hour, right? So, all the I 1s this thing this value is converted to per unit, all it is values and you substitute all this values, all this values are substituted our magnitude of I 1 magnitude of I 2 and magnitude of I 3 and then square, right? And these are all x 1 value it is ohmic values divided by their base impedance 1.21 1.21 into 10 to the power 5.

So, total Q loss is 28.94 kilowatt, but here if you look it is 26.6 kilo hours slight difference is there, because their solution has not yet converged that is why, this is the your how to call this, that is why this difference using this method, but I suggest you do the third iteration, you will find this 2 will be very close to this one and finally, solution will converge right? So, this is actually using your method 1. So, this is the calculation for method 1 load flow.

(Refer Slide Time: 12:59)

Data Same as Example-1 (Method-1)

$$\rightarrow r_1 = \frac{0.78}{1.21} = 0.6446 \text{ pu}; \quad x_1 = \frac{0.45}{1.21} = 0.3719 \text{ pu}$$

$$\rightarrow r_2 = \frac{1.62}{1.21} = 1.3389 \text{ pu}; \quad x_2 = \frac{0.66}{1.21} = 0.5454 \text{ pu}$$

$$\rightarrow r_3 = \frac{2.19}{1.21} = 1.8099 \text{ pu}; \quad x_3 = \frac{0.91}{1.21} = 0.7520 \text{ pu}$$

$$\rightarrow PL_2 = 400 \text{ kW} = 0.40 \text{ MW} = 0.004 \text{ pu};$$

$$\rightarrow QL_2 = 300 \text{ KVAR} = 0.30 \text{ MVAR} = 0.003 \text{ pu};$$

$$PL_3 = 500 \text{ kW} = 0.5 \text{ MW} = 0.005 \text{ pu};$$

$$QL_3 = 400 \text{ KVAR} = 0.4 \text{ MVAR} = 0.004 \text{ pu}$$


$r_1 \rightarrow r(1)$
 $x_1 \rightarrow x(1)$
 $r_2 \rightarrow r(2)$
 $x_2 \rightarrow x(2)$
 $r_3 \rightarrow r(3)$
 $x_3 \rightarrow x(3)$

$PL_2 \rightarrow PL(2)$
 $QL_2 \rightarrow QL(2)$
 $PL_3 \rightarrow PL(3)$
 $QL_3 \rightarrow QL(3)$
 $PL_4 \rightarrow PL(4)$
 $QL_4 \rightarrow QL(4)$

Now, example 2 that is method 2 this is actually, same data we will take for the purpose of comparison same data we will take. So, data same as example 1 or method 1, but here everything rewriting because r_1 is converted to per unit, r_2 r_3 all are converted to per unit, right? Then x_1 x_2 x_3 all are converted to per unit, everything is in per unit and meaning is same r suffix 1 r bracket 1 x 1 is equal to x bracket 1 they are all same that is why, but still I am making it here, that when you are writing mathematics, we are using this one.

If you write code, you will use this one, right? But question is that I am just making it like this, similarly PL_2 QL_2 all up to PL_3 QL_3 PL_4 QL_4 all are same, this PL_2 this PL_2 all are same. So, there should not be any question of confusion, right? So, PL_2 is 400 kilowatt divided by 1000.4 megawatt divide by base M V A. So, 0.004 per unit initially also for example, one all this are given similarly QL_2 is 300 kilowatt is equal to 0.003 per unit similarly PL_3 is 500 kilowatt that is 0.5 megawatt that is 0.005 per unit and QL_3 is equal to 400 kilowatt that is 0.4 megawatt. So, 0.004 per unit, right? And similarly, PL_4 is equal to 600 kilowatt is equal to 0.006 per unit and QL_4 is 400 kilowatt is equal 0.004 per unit, right?

(Refer Slide Time: 14:20)

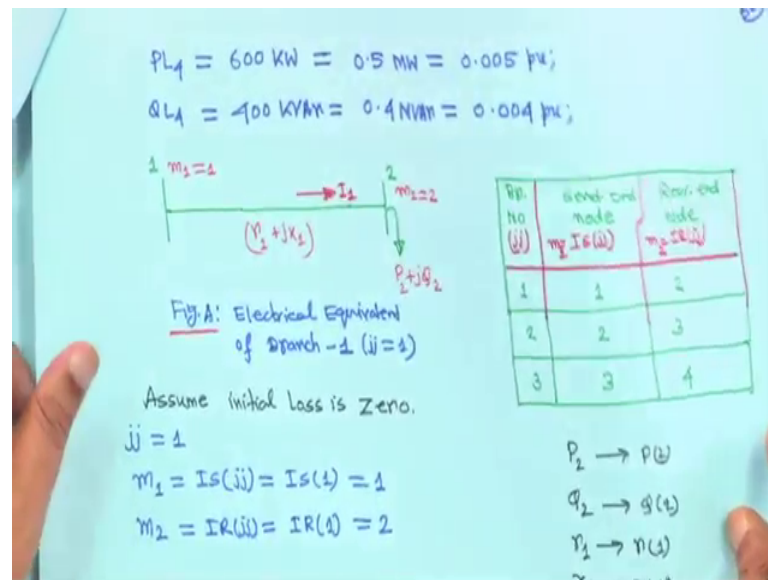

Now, that this the same example for one this a branch number 1 2 3 sending and receiving end, sending and receiving end, sending and receiving end, right? Here also meaning is same P suffix 2 and P bracket 2 all are same, similarly Q 2 r 1 except the everything meaning is same right? That is, they are identical same thing. So, for when is a for second method initially, we have to assume that loss is 0, that mean we assume initial loss is 0 means, that all the all the branch power losses are 0; that means, real power losses and reactive power losses in all the branch you assume initially it is 0 right?

Therefore, for j j is equal to 1, when j j is equal to 1 sending end node is m 1 is 1, m 2 is equal to 2 right? Therefore, m 1 is equal to 1 m 2 is equal to 2 all this things are written here right?

(Refer Slide Time: 15:31)

From Eqn. (68),

$$\rightarrow A_{ij} = P(m_2) P(ij) + Q(m_2) X(ij) - 0.5 |V(m_2)|^2$$

$\rightarrow$ when $ij = 1$

$$m_1 = 1$$

$$m_2 = 2$$

$$\rightarrow A_{11} = P(2) V(1) + Q(2) X(1) - 0.5 |V(2)|^2 \dots \dots (i)$$

$$\rightarrow P(2) = PL_2 + PL_3 + PL_4 = (0.004 + 0.005 + 0.006) = \underline{0.015 \text{ pu}}$$

$$\rightarrow Q(2) = QL_2 + QL_3 + QL_4 = (0.003 + 0.004 + 0.004) = \underline{0.011 \text{ pu}}$$

$$\rightarrow |V(2)| = \underline{1.0 \text{ pu}}$$

$$\rightarrow V(1) = V_2 = \underline{0.6446 \text{ pu}}$$

Then from equation 68 if we go to equation 68. Then you will see equation 68 is this one, we wrote A_{jj} is equal to $P_{m2} r_{jj}$ plus $Q_{m2} x_{jj}$ minus 0.5 into magnitude V_{m1} square, when jj is equal to 1 , just now we have given m_1 is equal to 1 m_2 is equal to 2 ; that means, A_{11} is equal to P_2 , here you substitute here you substitute jj is equal to 1 and m_2 is equal to 2 here and m_1 is equal to 1 here you substitute. So, A_{11} is equal to $P_2 r_{11}$ plus $Q_2 x_{11}$ minus 0.5 magnitude V_1 square this is a equation only numerical equation 1. So, initially loss of all the branches are neglected therefore, total load fed through this node will be PL_2 plus PL_3 plus PL_4 just repeating this.

(Refer Slide Time: 16:20)

$\therefore |I_2|^2 = \frac{(P_2^2 + Q_2^2)}{V_2^2}$

$\therefore V_2^2 |I_2|^2 = \frac{X_2^2 (P_2^2 + Q_2^2)}{V_2^2}$

$P_2 - jQ_2 = V_2^* I_2$

$\therefore I_2 = \frac{P_2 - jQ_2}{V_2^*}$

$\therefore |I_2| = \frac{\sqrt{P_2^2 + Q_2^2}}{V_2}$

$P_2 \rightarrow PR$
 $Q_2 \rightarrow QR$

Look, we have taken a very small example, right? This is the electrically equivalent of branch 1 and 2. So, this is branch 1 I node 1 2 3 4 electrically equivalent this is your branch 1, right? So, here everywhere load is there P L 2 Q L 2 P L 3 Q L 3 P L 4 all this things have been explained before, and this is the branch 1 and this is the branch 2. Then what is the electrical equivalent? It will be P 2 plus j Q 2, right? So, beyond this node this 2 branches are there, but we have assumed losses are 0, then what is the total load fed to this node? It will be P 2 will be here you have load here you have load here you P L 2 plus P L 3 plus P L 4.

Because everywhere that, P L 2 plus j Q L 2 P L 3 plus j Q L 3 plus P L 4 plus j Q L 4 load is there. So, P 2 will be P L 2 then plus P L 3 plus P L 4 similarly, Q 2 will be Q L 2 Q L 3 plus Q L 4 Q L 2 plus Q L 3 plus Q L 4, right? That loss is neglected so; that means, my P 2 will be P L 2 plus P L 3 plus all in per unit, you make 0.004 plus 0.005 plus 0.006, that will be 0.015 per unit, right?

Similarly, Q 2 will be is equal to Q L 2 plus Q L 3 plus Q L 4, is equal to 0.003 plus 0.004 plus 0.004 that is 0.011 per unit, voltage at the substation it is known, because it is 1 angle 0. So, magnitude V 1 is equal to 1 this is known right? And r 1 r 1 is equal to this r 1 I told you this per unit 0.644 per unit and x 1 is equal to x suffix 1 that is 0.3719 per unit. So, all these all these data put here, in this equation and calculate what is the value of a 1?

(Refer Slide Time: 18:22)

$$\begin{aligned}
 \rightarrow A(1) &= 0.015 \times 0.6446 + 0.011 \times 0.3719 - 0.5 \times 1.0^2 \\
 \rightarrow \therefore A(1) &= \underline{-0.4862401} \\
 \text{From eqn. (69), we} \\
 \rightarrow D(ji) &= \left[A^2(ji) - (r^2(ji) + x^2(ji)) (P^2(mj) + Q^2(mj)) \right]^{1/2} \\
 \rightarrow \therefore D(1) &= \left[A^2(1) - (r^2(1) + x^2(1)) (P^2(1) + Q^2(1)) \right]^{1/2} \\
 \rightarrow r^2(1) + x^2(1) &= (0.6446)^2 + (0.3719)^2 = \underline{0.553818} \\
 \rightarrow \therefore D(1) &= \left[(-0.4862401)^2 - (0.553818) \{ (0.015)^2 + (0.011)^2 \} \right]^{1/2} \\
 \rightarrow \therefore D(1) &= \underline{0.486042}
 \end{aligned}$$

So, if you do. So, A_1 will be 0.115 into 0.6446 plus 0.011 into 0.379 minus 0.5 into v_1 square, that is 1 square it will become a 1 will become minus 0.4862401 , right? And similarly, from equation 69, another term was that D_{jj} . So, D_{jj} is equal to a square jj minus r square jj plus x square jj into square m^2 plus Q square m^2 bracket close right? To the power half.

Therefore, jj is equal to 1 therefore, D_1 is equal to a square 1 minus r square 1 plus x square 1 and m^2 is equal to 2 , for jj is equal to 1 therefore, P square 2 plus Q square 2 to the power half therefore, you first you calculate this term, r_1 square plus x_1 square. So, r_1 square plus x_1 square is equal to this 1 , right? 0.6446 square plus 0.3719 square is equal to 0.553818 , I suggest I have taken up to 6 decimal place or so, but for the assignment purpose everything, I will tell you that you should take only up to 3 or 4 decimal place I mean if you for 5538 you can make it approximation 0.554 , right? So, I have taken exact 1 , then D_1 is equal to we have calculated just now A_1 minus 0.4862401 .

So, it is minus 0.4862401 whole square right? Because it is square right? Minus then r square plus r_1 square plus x square you have made it 0.553828 . So, substitute here, and then it is P^2 square 0.015 square plus 0.011 square and to the power half, if you simplify this D_1 will become 0.486042 . So, A_1 is minus of this thing, very close only there sign difference is there, but this term and this term they are very close, right? Up to first 3 decimal places this 2 are almost same right? But there is a negative sign here, every iteration you will find magnitude wise this 2 term will be very close right? But, here it is negative sign.

(Refer Slide Time: 20:42)

From eqn(66)

$$\rightarrow |V(m2)| = [D(jj) - A(jj)]^{1/2}$$

$$\rightarrow |V(2)| = [D(1) - A(1)]^{1/2} = [0.486042 - (-0.486042)]^{1/2}$$

$$\rightarrow |V(2)| = 0.98604 \text{ pu.}$$

Loss of Branch-1

$$\rightarrow P_{Loss(1)} = r(1) \times \frac{(P_1^2 + Q_1^2)}{|V(2)|^2} = \frac{0.6446 \times \{ (0.015)^2 + (0.011)^2 \}}{(0.98604)^2}$$

$$\rightarrow P_{Loss(1)} = 0.00022939 \text{ pu}$$

$$\rightarrow Q_{Loss(1)} = x(1) \times \frac{(P_1^2 + Q_1^2)}{|V(2)|^2} = \frac{0.3719 \times \{ (0.015)^2 + (0.011)^2 \}}{(0.98604)^2}$$

Next is calculation of voltage magnitude. So, from equation 66, we know that voltage magnitude V_{m2} is equal to D_{jj} minus A_{jj} half right, but for jj is equal to 1 m 2 is equal to 2, this is the very first iteration going on. So, V_2 magnitude V_2 is equal to D_1 minus A_1 to the power half, this all this thing continuing for jj is equal to 1, branch 1 A_1 is equal to 1 m 2 is equal to 2, right? So, you substitute that D_1 is 0.486042 minus, this minus and A_1 is minus in bracket it is minus point 0.486042.

So, minus minus plus actually, to the power half if you simplify, magnitude of V_2 will come 0.98604 per unit. So, V magnitude of V_2 is obtained, now once V_2 is obtained. So, loss of branch 1, that is P_{loss1} into $P_1^2 + Q_1^2$ upon V_2^2 square, this also I have showed you right? How to calculate the losses. So, in this diagram this is the current I_1 and this is the voltage magnitude V_2 therefore, this already I have explained, but once again I am showing, $P_2 - jQ_2$ is equal to V_2 conjugate I_1 , right?

Therefore, I_1 is equal to $P_2 - jQ_2$ upon V_2 conjugate therefore, magnitude of I_1 is equal to root over $P_2^2 + Q_2^2$ upon V_2 , right? And therefore, magnitude of I_1 therefore, magnitude of I_1 square is equal to $P_2^2 + Q_2^2$ square right? Divided by V_2 square right or for branch 1 power loss, if you want r_1 then I_1 square is equal to r_1 in bracket, I am putting $P_2^2 + Q_2^2$ square upon V_2 square right?

So, this is real power loss similarly, if you multiply x 1 with this term then that will give you reactive power loss. So, here P_2 everywhere I am telling, this P_2 means this bracket $P_2 Q_2$ means this bracket Q_2 like this right? Therefore, when you compute the your what you call the loss of branch 1, it is p loss 1 that is loss of branch 1 is equal to r_1 into P_2^2 square plus Q_2^2 square upon V_2 magnitude square.

So, r_1 is 0.6446 into P_2 is 0.015, first iteration is going on plus 0.011 square divided by 0.98604 square. So, P loss 1 will be 0.00022939 per unit, right? Similarly, Q loss 1 will be x_1 into P_2^2 square plus Q_2^2 square upon V_2 square. So, it will be 0.3719 0.015 square plus 0.011 square by 0.9860, actually this term remains same only here, it is multiplied by r here it is multiplied by x right? Therefore, Q loss 1 is 0.0013234 per unit, this is per unit only later we will convert to the real unit, because we have to go for the iteration right?

(Refer Slide Time: 24:00)

Handwritten calculations for power flow iteration 2:

- For $jj = 2$
- $m_1 = Is(jj) = Is(2) = 2$
- $m_2 = IR(jj) = IR(2) = 3$
- $P(3) = PL_3 + PL_4 = (0.005 + 0.006) = 0.011 \text{ pu}$
- $Q(3) = QL_3 + QL_4 = (0.004 + 0.004) = 0.008 \text{ pu}$
- $A(2) = P(3)V(2) + Q(3)x(2) - 0.5|V(2)|^2$
- $A(2) = (0.011)(1.3388) + (0.008)(0.5454) - 0.5(0.98604)^2$
- $A(2) = -0.4670474$
- $D(2) = [A(2)^2 - (P(2)^2 + Q(2)^2)]^{1/2}$
- $D(2) = [(-0.4670474)^2 - (0.011)^2 + (0.008)^2]^{1/2}$
- $V(2) = 1.3388 \text{ pu}$
- $x(2) = 0.5454 \text{ pu}$
- $|V(2)| = 0.98604 \text{ pu}$
- $P(2)^2 + Q(2)^2 = 2.0898$

Similarly, first iteration is continuing. So, similarly for jj is equal to 2 m_1 is equal to 2 all this have been explained, and m_2 is equal to 3 therefore, P_3 will be now actually it will be $P_L 3$ plus $P_L 4$, same the total initially loss are all neglected. So, P_3 is equal to $P_L 3$ plus $P_L 4$ and whatever loss you have calculated this is for loss of branch 1 not branch 2 or 3, right? Therefore, $P_L 3$ plus $P_L 4$ is this much 0.011 per unit and your Q_3 is equal to $Q_L 3$ plus $Q_L 4$ that is your 0.008 per unit, right? So now, from the same

equation for j is equal to j is equal to 2, you calculate A^2 now, from this equation only whatever from equation 68, only put j is equal to 2 here only here only right here only.

So, in that case you will get A^2 is equal to $P^3 r^2$ plus $Q^3 x^2$ minus $0.5 V^2$ magnitude square. So, substitute all the values all the values you substitute. So, A^2 will be 0.011 into 0.3388 plus 0.008 0.5454 minus 0.5 and this is the voltage magnitude V^2 square. So, 0.98640 square. So, A^2 is becoming minus 0.4670474 , right? This is A^2 , all $r^2 x^2 V^2 r$ up to square plus x^2 square everything is written here, re calculated and I am writing here.

For such that when you will we you will go through these slide, at that time readily available in front of you, that is why I have written. Similarly, from this equation that again your D j j equation I come that is equation 69, this is your equation 69 these D j j here put j is equal to 2, right? Accordingly, it will be your P or what you call that m^2 is equal to 3, it will be $Q^3 P^3$ square 3 plus Q^3 square 3 and it is r^2 square 2 plus x^2 square 2.

So, D^2 will be a square 2, minus your r^2 square 2 plus your x^2 square 2 in the P^3 square 3 plus Q^3 square 3, to the power half, right? Therefore, put all these values it is D^2 is equal to minus 0.4670474 . When you will do assignment and repeating I am, that we assignment on example, if something is there you will take only up to 3 or 4 decimal not more than that right? Minus this is r^2 square plus x^2 square r^2 square plus x^2 square in per unit I have computed here, I have computed here right? So, substitute and it is your P^3 square plus Q^3 square right? P^3 is given Q^3 is initially given right? So, if you make D^2 will be 0.466633 this is D^2 , right? Then V^3 then magnitude of V^3 it will be your D^2 minus A^2 half to the power half, right?

(Refer Slide Time: 27:07)

$$\rightarrow |V_3| = 0.966271 \text{ pu}$$

Loss of Branch-2

$$\rightarrow P_{\text{Loss}(2)} = R(2) \times \frac{(P_3^2 + Q_3^2)}{|V_3|^2} = 1.3388 \times \frac{(0.011)^2 + (0.008)^2}{(0.966271)^2}$$

$$\rightarrow P_{\text{Loss}(2)} = 0.00026527 \text{ pu}$$

$$\rightarrow Q_{\text{Loss}(2)} = X(2) \times \frac{(P_3^2 + Q_3^2)}{|V_3|^2} = 0.5454 \times \frac{(0.011)^2 + (0.008)^2}{(0.966271)^2}$$

$$\rightarrow Q_{\text{Loss}(2)} = 0.00010806 \text{ pu.}$$

Again, from this, whatever we have computed this voltage equation this is coming, that is I think it is 66, this is equation 66 from this here it is coming from this equation, right? Therefore, your V_3 will be your D_2 minus A_2 to the power half, substitute 0.466633 minus in bracket minus 0.4670 whatever it is 474 to the power half. So, magnitude of V_3 will be 0.966271 per unit, right? Then will be loss of branch 2.

Thank you we will be right.