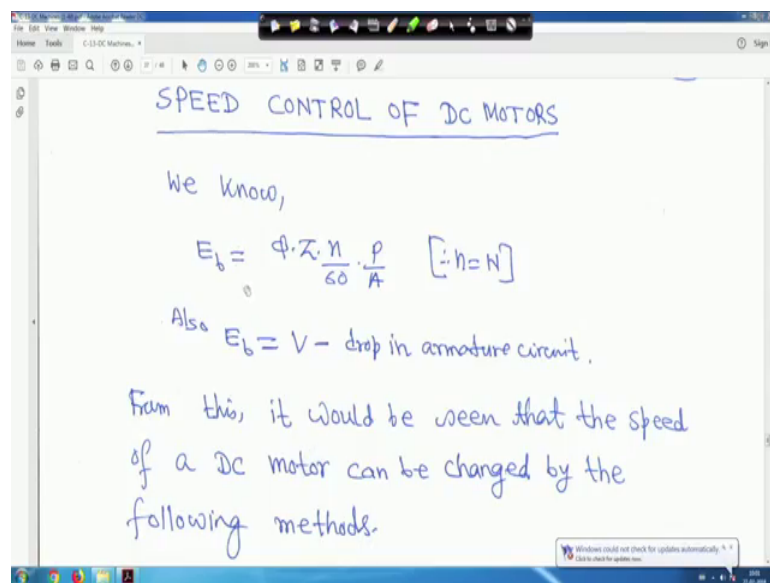


Fundamentals of Electrical Engineering
Prof. Debapriya Das
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur


Lecture – 64
DC Motors (Contd.)

(Refer Slide Time: 00:28)



So this is that last part of this course right. So now, speed control of DC ~~motors~~Motors, you find things are quite simple. So, for example, we know that back Emf is equal to ϕ Z small n upon 60 into P by A somewhere I might have used capital n, but same thing that is why in the bracket it is written small n is equal to capital N. So, no confusion and E b you know that back Emf E b is equal to your V minus the drop in armature circuit, that is the voltage drop in the armature circuit that is i a into r a right.


(Refer Slide Time: 01:05)

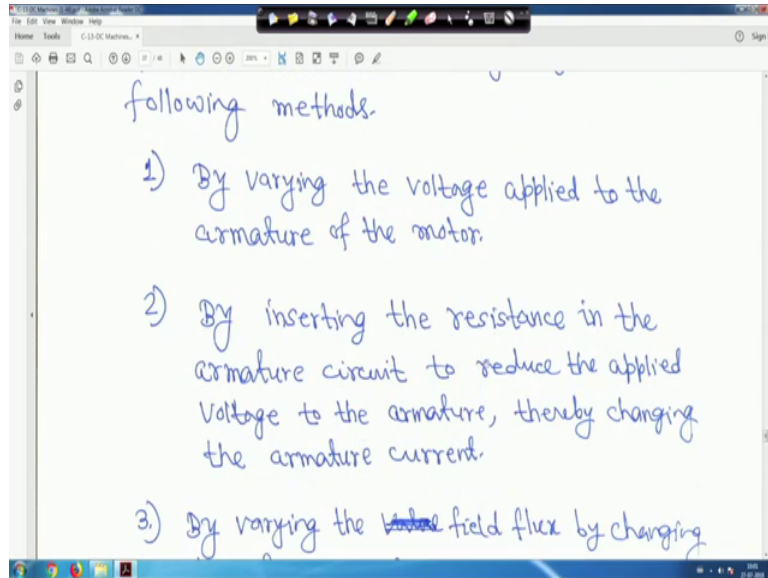

For this it would be seen that the speed of a DC motor can be changed by the following methods. One is by varying the voltage applied to the armature of the motor that is your V_a you can vary that applied voltage.


Another thing is by inserting the resistance in the armature circuit to reduce the applied voltage to the armature, there by changing the armature current right and number 3 is by varying the field flux by changing the field current, these are the 3 different ways of changing the your what you call speed of the DC motor.

(Refer Slide Time: 01:26)

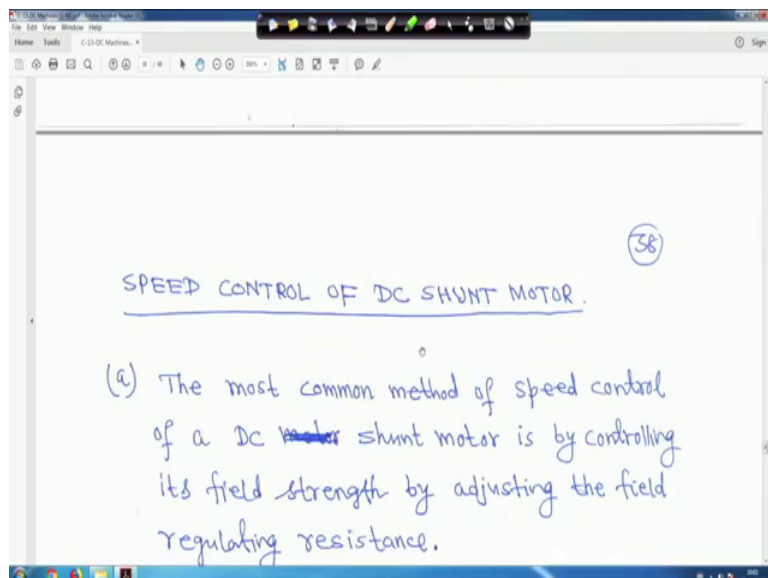

Now, if you look into that the speed control of a DC shunt motor right.

(Refer Slide Time: 01:39)

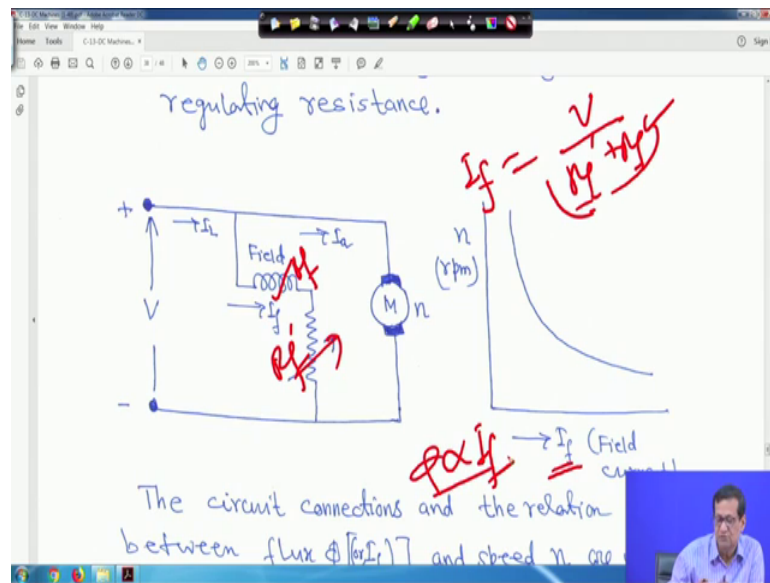

The most common method of speed control of a DC shunt motor is when controlling it is field strength by adjusting the field regulating resistance.

So, if you look into the circuit, that this is your field winding and one additional resistance has been connected right, this is a variable resistance, if I_f you vary this resistance then your, what you call that your field current will vary.

For example, suppose this resistance is R_f right. Suppose, this is your R_{f0} , as say R_{f0} and this field resistance is R_f right. So, when you try to find out what is field current, I_f will be is equal to V upon R_{f0} plus R_f right, this R_{f0} anyway is fixed, this is the field resistance of the circuit of this of this field winding and this R_f dash actually, your what you call that variable resistance. So, if you if you can vary this resistance naturally, the field current will decrease right because, you are adding some resistance field current will decrease.

So, in that way your, what you call; that means, your flux is proportional to the field current. So, naturally that your what you call that flux also will decrease right, but But in that case, we will see the characteristic, how it is if field current decreases speed increases, if I_f field current your increases sorry, if field current your increases, then flux also your increases right in that case, opposite will happen. So, and field basically I_f actually field current ϕ actually proportional to I_f right. So, this you will always keep it in your mind.

So, in that case in that case what will happen? We know this the circuit connections and the relation between flux or ϕ or I_f this can be ϕ or this can be I_f because, flux is proportional to I_f and speed n are shown in figure above.

(Refer Slide Time: 03:19)

The circuit connections and the relation between flux ϕ [I_f] and speed n are shown in the figures above.

In this method, a variable resistance is connected in series with the shunt field and is adjusted to change the field current as required. The speed is inversely prop

In this method a variable resistance is connected in series with the shunt field that is that is in this diagram, this I showed you this is the diagram right.


(Refer Slide Time: 03:28)

In this method, a variable resistance is connected in series with the shunt field and is adjusted to change the field current as required. The speed is inversely proportional to the flux when applied voltage is not changed and back emf can be considered constant.

$$E_b = k \cdot \phi \cdot n$$

$$n \propto \frac{1}{\phi}$$

(Refer Slide Time: 03:42)

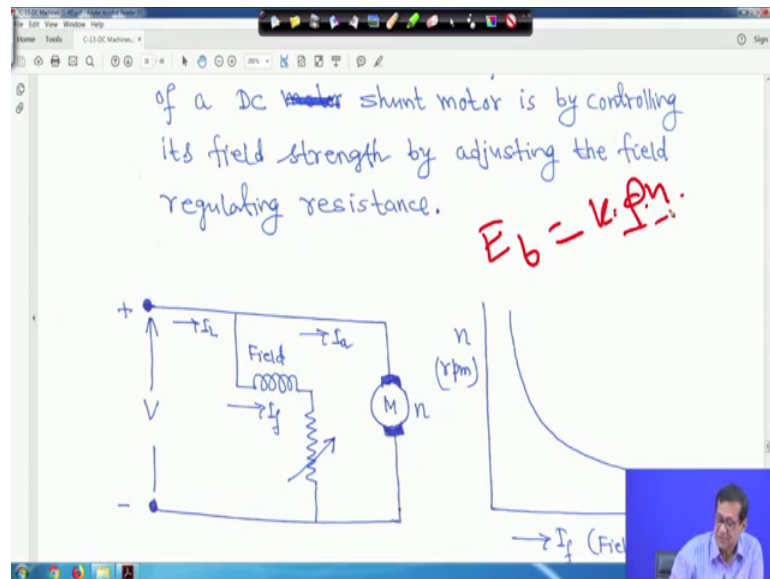

So, this speed is actually inversely proportional to the flux, when the applied voltage is not changed and back Emf can be considered constant that means, this equation.

Your this equation, we know this equation that your E_b is equal to that back Emf is equal to write your K your K into your Φ into n right.

So K is the constant and this is the flux and flux proportional to the I_f if the your what you call that your field current. So, we know this. So here, it is your what you call this is the expression, this is that your E_b is equal to this expression right and if your E_b is equal to then K into Φ into n right. So, here it is written that field the speed inversely proportional to flux, when applied voltage is not changed and back Emf can be considered as constant.

That means your E_b back Emf is equal to K into Φ into n right. So, if you applied voltage constant then E_b , if you can make constant then this then what will happen that n actually, inversely proportional to the your flux right. So, flux is proportional to I_f ; that means, n is inversely proportional to I_f right; that means, if field current increases n decreases and vice versa. So, that is why that is why this characteristic is looks like a your what you call like this one like a rectangular hyperbola right.

So, this is your n rpm and this is your field current right. So, this is the characteristic.

(Refer Slide Time: 05:07)

(39)

Thus, increasing the resistance in the shunt field decreases the shunt field current, hence decreases the flux and increases the speed.

In the same way, decreasing the resistance in the shunt field circuit, increases the shunt field current, hence increases the flux and decreases the speed.

The next is your, thus increasing the resistance in the shunt field decreases the shunt field current hence, decreases the flux and increases the speed because, inversely proportional to it. In the same way, decreasing the resistance in the shunt field circuit increases, the shunt field current hence, increases the flux and decreases the speed right, this is one method.

(Refer Slide Time: 05:24)

2) ARMATURE RESISTANCE CONTROL

In this method, resistance is inserted in series with the armature circuit:


Increase resistance in armature circuit, $I_a(R+r_a)$ drop increases, $E_b = V - I_a(R+r_a)$

The diagram shows a DC motor circuit. A voltage source V is connected to a resistor R in series with the armature circuit. The armature current is I_a . The field winding is connected in parallel with the armature circuit, with field current I_f . The motor terminals are labeled E_b and b .

Another is the that armature resistors resistance control method, in this method resistance actually here, it is inserted in series with the armature circuit with this is your R_a this is

your R that resistance is inserted here and armature resistance I mean, it is your R a small r a right and this is the field current here nothing is there. So, increase the resistance in the armature circuit means the, this is your back Emf. So, if you apply in this circuit kvl you will get E_b is equal to V minus I_a into R plus r_a , r_a is the armature resistance right.

(Refer Slide Time: 06:01)

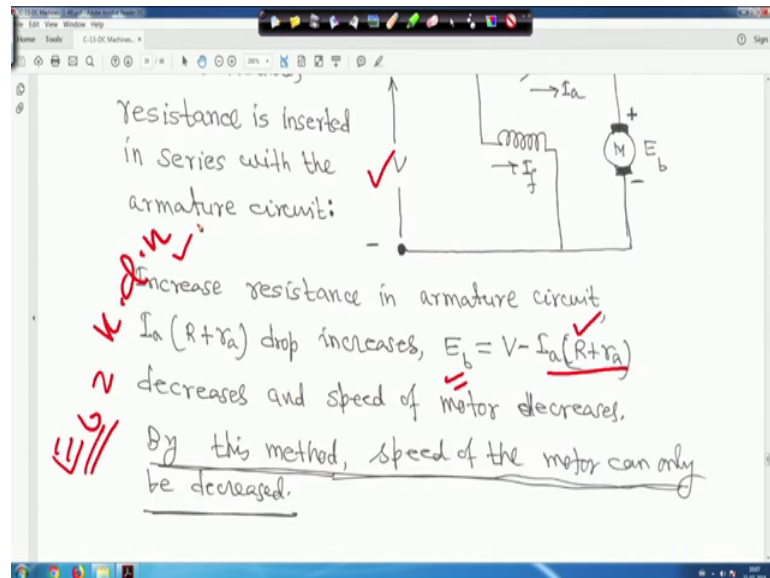

So, therefore, increase the resistance in the armature circuit $I_r a$ that that is your at this if you increase this capital R right then drop increases. therefore Therefore, E_b will decrease right and speed of the motor actually, decreases because, back Emf because your, in this case your E_b back Emf is equal to K into ϕ into n right. So, what is happening here? That because, we have inserted that resistance R. So, this drop will increase therefore, E_b will decrease.

So, in that in that case, your field current I_f remain constant because, nothing is connected here because, this voltage V is remains constant. So, in that case ϕ is also constant. So, your because of the decrease of E_b n or speed also will decrease right. So, almost linearly it should vary. So, in this case what will happen the by this method? The speed of the motor can only be decreased, you cannot increase it, because of this your E_b is decreasing right, you cannot this thing, you can because, you have added r . So, E_b is decreasing. So, by this method only speed can be decrease right. So, this characteristic, you can easily draw.

(Refer Slide Time: 07:13)

SPEED CONTROL OF DC SERIES MOTOR

1) The method used for controlling the speed of a series motor is to vary the field flux by varying the

Speed control of series motor using diverter

Now, second one is that speed control of DC series motor, now this is for shunt. So, nothing is there actually, you put a resistance R capital R and this because of that there will be voltage drop and field current remain constant. So, back Emf will decrease therefore, speed will decrease. So, this method you can only your, what you call, you can only decrease the speed of the machine.

Now, next is your speed control of a DC series motor, DC series motor actually field winding, we have seen is in series with the armature, but what is this that you connect 1 variable resistance, we called diverter that is in parallel to this field winding. So, the way you have studied, your simple parallel circuit for DC circuit analysis. So, as soon as and this is a variable as soon as you connect it, 1 part of the this is the total armature current, this is the total current I_a right the same current is going and the part of the current, it will be flowing through this your I_f and part of the current flowing through the field winding right.

That means I_f plus I_a is equal to capital I suffix a right I_f plus I_f is equal to I_a .

So, by this way part of your basically, you can control this field current by adding a diverter, diverter means part of the current is diverted through this variable resistance, you can vary this. So, this speed control of a series motor, motor using diverter. So, this method used for controlling the speed of the series motor is to vary the field flux by

varying the, your, excitation current because, the excitation current means the field current right.

(Refer Slide Time: 08:41)

the field flux —

by varying the excitation current.


Speed control of series motor using diverter

Here the regulating resistance for the purpose is connected in parallel with the field winding. This is known as diverter. By adjusting the diverter resistance, the field current can be regulated by diverting the desired fraction of the main current.

Here the regulating resistance for the purpose is connected in parallel with the field winding, this is known as diverter by adjusting the diverter resistance, the field current can be regulated by diverting, the desired fraction of the main currents. So, this is main current. So, part of the current can be flowing through this (Refer Time: 08:58) field current will you will decrease right.

So, now this is one way.


(Refer Slide Time: 09:06)

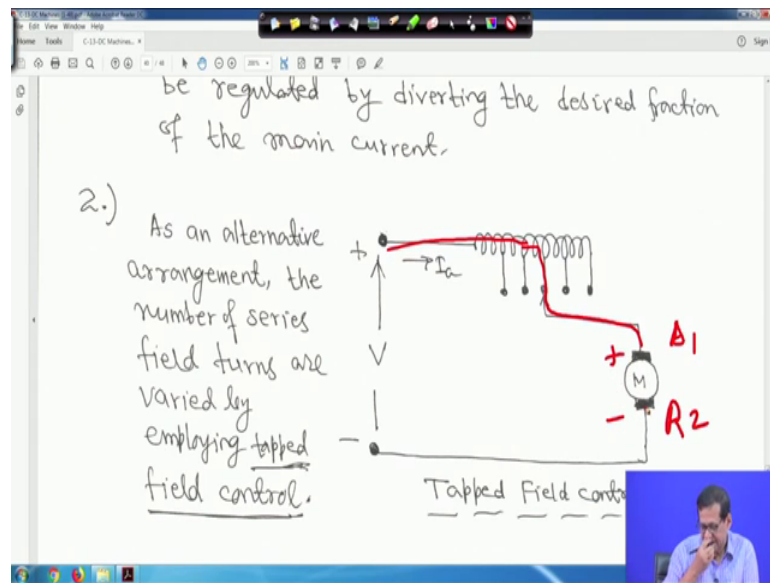

Another way is that as an alternative arrangement, the number of series field turns are varied by employing a tapped field control, in this case what happens? This is a series field, this is basically a series field many places tapped here, it is tapped if you connect this tap naturally, you know what you call ~~this is~~ this is the path, it will follow that your, what you call this your what you call this is the path, this is the path, it will follow right and if you I have not marked here, it is A 1 A 2 right and this is plus minus right.

And ~~this your your~~, what you call by changing this by changing, this tap from here to here, what here to here, you can control the current through so the field right. So, this way also this is called tapped field control, this way also you can control the your what you call that your control the speed of the series motor right. So, details mathematics other thing just keeping at the first year level.

(Refer Slide Time: 10:03)

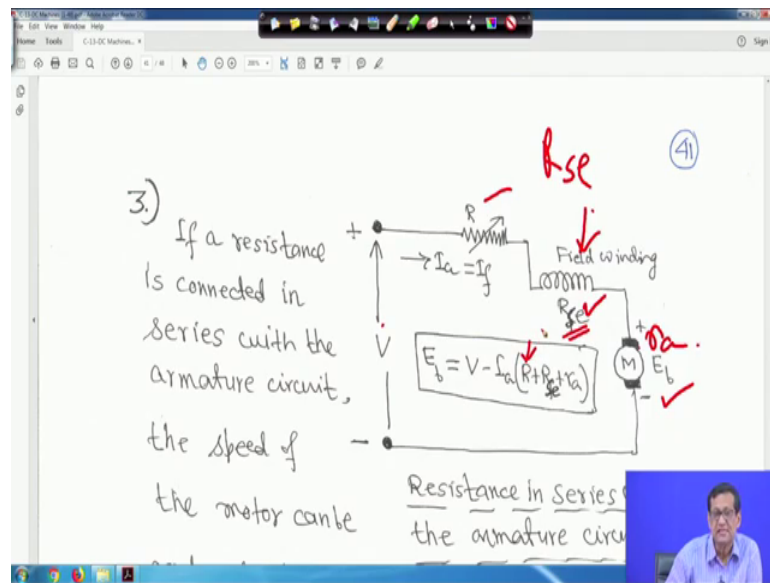

Now, number 3 that if a resistance is connected where, again series motor is connected in series with the armature circuit, the speed of the motor can be reduced by adjusting the resistance as the back EMF I mean here, if you put 1 resistance in series with the field winding because, both are in series I mean series with this is your this one, this one, this resistance this armature is r_a right. So, armature and this is R_{se} this is R_{se} right and this is R .

Therefore back EMF that E_b the back EMF will be V minus I_a into R plus R_{se} plus r_a , this R_{se} is the series field winding resistance here series field winding resistance. So, in that case we are adding 1 resistance R right.

(Refer Slide Time: 10:59)

the speed of the motor can be reduced by adjusting the resistance in the back emf and hence the speed will be reduced by increasing the resistance in the circuit.

Resistance in series with the armature circuit.

REVERSAL OF ROTATION OF DC MOTOR

So, so resist[ance]-. So, in this case:- So, in this case also the speed of the armature can be reduced by R because, if you do so, the back Emf is getting reduced right. So, so by the adjusting the resistance of the back Emf hence, the speed will be your, what you call reduced by increasing the resistance in the circuit. So, if you increase the resistance. So, naturally your back Emf will decrease right. So, in that way speed can be reduced right. So, like your armature control in shunt motor.

(Refer Slide Time: 11:27)


adjusting the resistance in the back emf and hence the speed will be reduced by increasing the resistance in the circuit.

REVERSAL OF ROTATION OF DC MOTOR

A:] shunt motor

The diagram shows a circuit for a shunt motor. It includes a DC voltage source V connected to a shunt field winding with resistance R_f and an armature circuit with resistance R_a . The armature current is labeled I_a . The field winding is connected in parallel with the armature circuit. The motor is represented by a circle with 'M' inside. The field winding is labeled F_1 and F_2 . The armature circuit is labeled A_1 and A_2 .

(Refer Slide Time: 11:30)

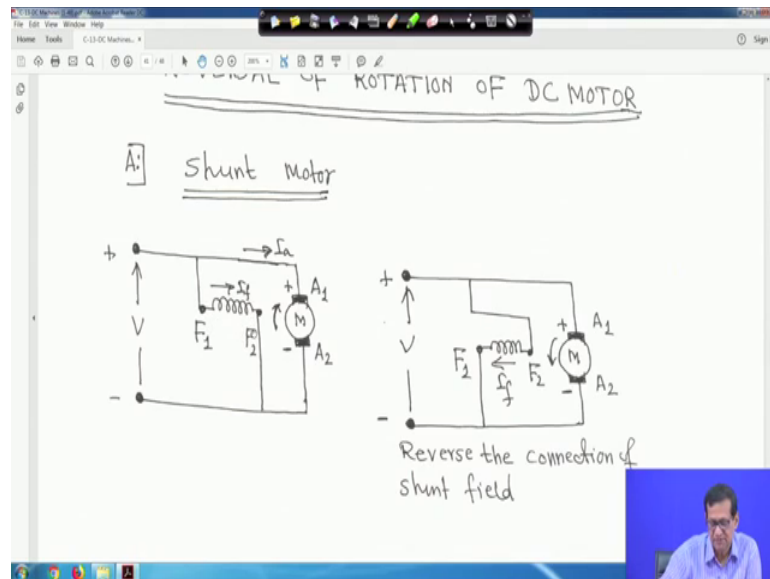


So, next is the reversal of rotation of DC motor or shunt motor.

Suppose this is the connection of the shunt motor F_1 , F_2 is the field terminal, A_1 A_2 armature terminal right. So, if you want to if you want to here also, ~~it~~ It is shown your what you call F_1 F_1 F_2 and this thing now, if you want to interchange the I mean, if you interchange the field terminal then, if you see this diagram F_1 F_2 connected, but now this point is connected here and this point is connected here this is; that means, your direction or this is the earlier, it was your what you call current was flowing in the field from F_1 to F_2 , this connection is flowing F_2 to F_1 and torque is proportional to your product of the your, we have seen that product of your ϕ into I_a right.

And ϕ is proportional to your field current right. So, in that case what will happen as your, that your field winding current is reversed. So, machine will rotate in the opposite direction here, it is shown the in the clockwise direction. So here, it will rotate in the opposite direction, if you reverse the your only field correction right field winding correction.

(Refer Slide Time: 12:36)

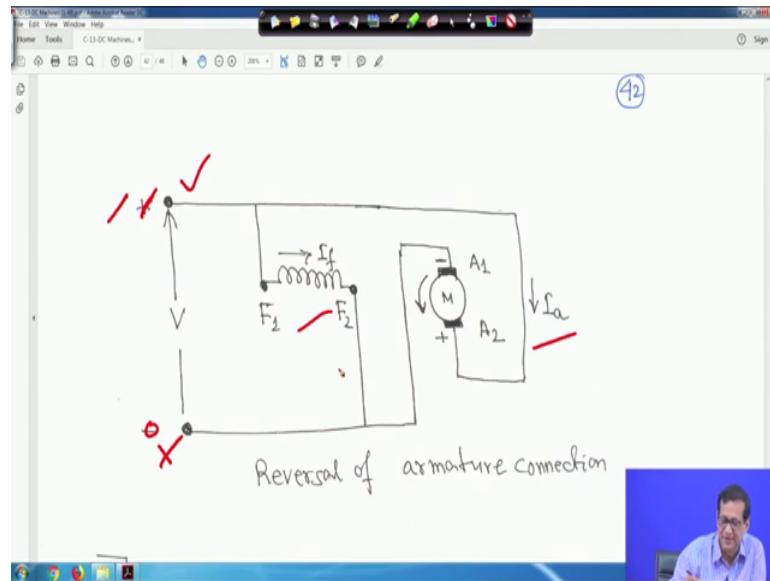


Now, now if you interchange, now the keep the field as it is F 1 F 2, now interchange the armature connection right; that means, plus terminal here I have brought to A 2 and minus 1 I have brought to A 1 I mean here, just we have interchanged these 2, these 2 connection A 1 A 2 reversed in that case your, what you call direction of the armature current is changed, but field current direction remain same. So, machine will rotate in the opposite direction right.

So, your that is either; that means, either you interchange the field connection or you interchange the armature connection such that machine will rotate in the reverse direction, but if you interchange both F 1 F 2 and A 1 A 2 both machine will rotate in the same direction because, torque is proportional to the what you call your ϕ into I_a right product of these 2 right. So in that case, ϕ proportional to I_f ; So, both I_f and armature current direction is changed. So, machine will rotate in the same direction right.

So,—So, in; that means, if you either of this if you interchange machine will rotate in opposite direction, but if you change both then machine will rotate your, what you call in the opposite direction as you saw, if you both you change then machine will rotate in the same direction and another thing is the terminal voltage, if this terminal voltage suppose, this is plus, this is minus, if you interchange this terminal suppose, if I connected to minus and if I connected to plus machine will rotate in the same direction right in your laboratory, you can verify easily right.


Because, if you interchange also both the field current and your current armature current both direction will change:- [Seso](#), ultimately torque is proportional to your ϕ into I_a both your ϕ into I_a ; that means, in generally torque is proportional to product of field current and the armature current. So, both directions are changing. So, machine will rotate in the, what you call in the same direction. So, if you interchange this polarity also it will rotate in the same direction, if you interchange both filed or both field and armature, it will rotate in the same direction, but either field or armature, if you interchange then it will rotate in the reverse direction right. So, this is very simple thing.

(Refer Slide Time: 14:43)

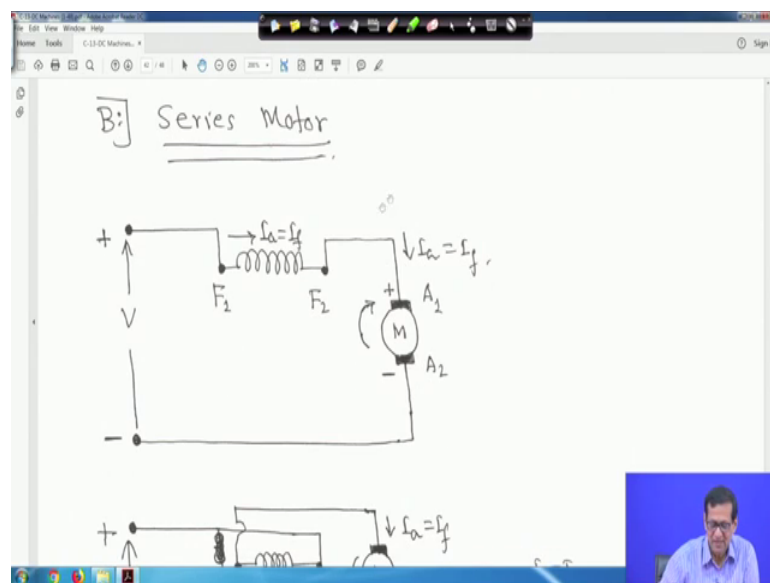

So, now for series motor here also $F_1 F_2$ is there $A_1 A_2$ is there and I_a is equal to field current for series motor also if you inter[change]- reverse the direction of this one, this point is connect to F_2 and this point 2 connected to F_1 then here field current or armature current through, the field winding that from F_1 to F_2 F_1 to F_2 right, if you reverse interchange, this it will move F_2 to F_1 .

(Refer Slide Time: 15:10)

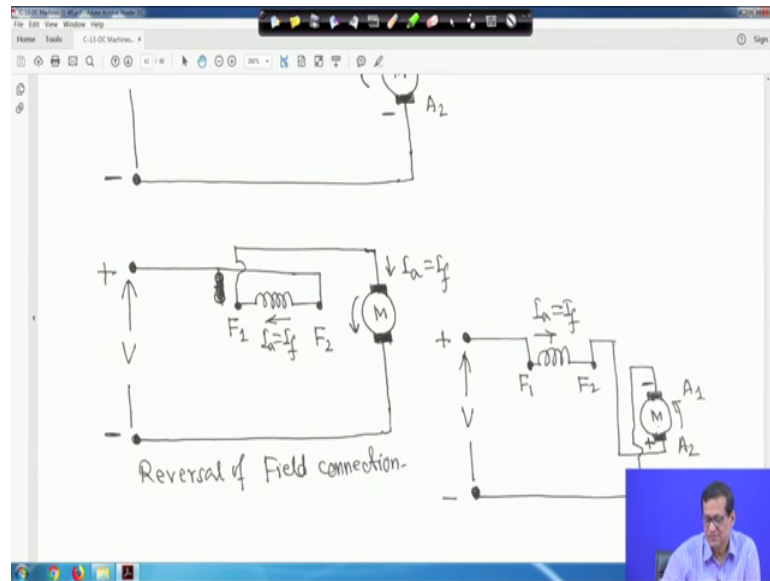

So, this way that your what you call direction of this can be changed here, it is showing your what you call clockwise here, direction is showing anticlockwise because, you are reversing the direction of the field current:- [Similarly](#) similarly, if you reverse the direction of the armature current also in this case. So, the here also, if you when you are reversing then in this case also machine will rotate in the reverse direction, but if you make both then, it will rotate in the same direction, if you interchange the polarity of this supply line also machine will rotate in the same direction right.

(Refer Slide Time: 15:44)

X-3:

A series motor having a resistance of 1Ω between its terminals drives a fan for which the torque is proportional to the square of the speed. At 230 volt, it runs at 300 rpm and takes 15 Amp. The speed of the fan is to be raised to 375 rpm by increasing the voltage. Find the voltage and the current required.

Soln.

Next is an example. So, a series motor having a resistance of 1 Ohm between its terminals drives a fan for which the torque actually is proportional to the square of the speed; that means, $T \propto n^2$ right at 230 volt, it runs at 300 rpm and takes 15 ampere, the speed of the fan is to be raised to 375 rpm sorry, by increasing the voltage, find the voltage and the current required, this is the problem right. So, at 320 volt it runs at 300 rpm and takes 15 ampere, the speed of the fan is to be raised to 375 rpm by increasing the voltage, find the voltage and the current required right.

(Refer Slide Time: 16:25)

Soh.
 We know,
 $T \propto \phi I_a$,
 In series motor, $\phi \propto I_a$,
 $\therefore T \propto I_a^2$ --- (i)
 Also, given that
 $T \propto n^2$ --- (ii)
 If n_1 is the initial speed and I_{a1} is the
 initial current, while n_2 and I_{a2} are s

So, we know that torque actually proportional to ϕI_a . Now the in series motor ϕ is proportional to I_a ; that means, if $\phi \propto I_a$; that means, torque proportional to armature current square.

(Refer Slide Time: 16:39)

In Series motor, $\phi \propto I_a$,
 $\therefore T \propto I_a^2$ --- (i)
Also, given that
 $T \propto n^2$ --- (ii)
If n_1 is the initial speed and I_{a1} is the initial current, while n_2 and I_{a2} are speed and current at the new condition of operation of the motor. Then,

(Refer Slide Time: 16:58)

44
 $\frac{T_1}{T_2} = \left(\frac{I_{a1}}{I_{a2}}\right)^2 = \left(\frac{n_1}{n_2}\right)^2$ --- (iii)
Given that,
 $n_1 = 300 \text{ rpm}, n_2 = 375 \text{ rpm}, I_{a1} = 15 \text{ Amp}$
 $\therefore I_{a2} = I_{a1} \left(\frac{n_2}{n_1}\right) = 15 \left(\frac{375}{300}\right)$
 $\therefore I_{a2} = 18.75 \text{ Amp}$

Now, also given that torque is proportional to n^2 , if n_1 is the initial speed and I_{a1} is the initial current, while n_2 and I_{a2} are speed and current at the new condition of operation of the motor then, we can write because, it is T proportional to n^2 . So, first case if it is T_1 second case torque is T_2 .

Say, then it will be T_1 upon T_2 is equal to I_{a1} upon I_{a2} whole square because, torque is proportional to I_a^2 right and it is given that torque is proportional to n^2 ;

that means, T_1 by T_2 is equal to I_{a1} by I_{a2} whole square is equal to n_1 upon n_2 whole square, this is a equation 3 it is given.

(Refer Slide Time: 17:29)

$$\therefore I_{a2} = I_{a1} \left(\frac{n_2}{n_1} \right) = 15 \left(\frac{375}{300} \right)$$

$$\therefore I_{a2} = 18.75 \text{ Amp}$$

$$E_{b1} = 230 - 15 \times 1 = 215 \text{ volt}$$

Circuit diagram (a) showing a motor with resistance R_{sc} , current $I_{a1} = 15 \text{ Amp}$, voltage $V = 230 \text{ volt}$, and back EMF E_{b1} . A box indicates $R_{sc} + r_a = 1 \Omega$ and $n_1 = 300 \text{ rpm}$.

Now, it is given n_1 is equal 300 rpm, n_2 is equal to 375 rpm and I_{a1} is equal to 15 ampere this is given from which, from these 2 equations from these 2 equations, you can find out I_{a2} will be 18.75 ampere right therefore, the back Emf E_{b1} will 230 minus first phase current was 15. So, 15 into 1 \therefore [Seso](#), 215 volt right and n_1 is 300 ampere and R_{sc} plus r_a , we assume 1 Ohm right total.

(Refer Slide Time: 17:49)

$$E_{b2} = V - 18.75 \times 1$$

$$\therefore E_{b2} = V - 18.75$$

We know $E_b \propto \phi n$

$$\therefore \frac{E_{b1}}{E_{b2}} = \frac{\phi_1 n_1}{\phi_2 n_2} = \frac{I_{a1} n_1}{I_{a2} n_2} = \frac{15 \times 300}{18.75 \times 375} = \frac{215}{V - 18.75}$$

$$\therefore V = 354.65 \text{ Volt}$$

Circuit diagram showing a motor with resistance R_{sc} , current $I_{a2} = 18.75 \text{ Amp}$, voltage $V = ?$, and back EMF E_{b2} . A box indicates $R_{sc} + r_a = 1 \Omega$ and $n_2 = 375 \text{ rpm}$.

-And next is your in the second case, $I_a 2$ is 18.75 ampere and $R_s e$ plus r_a is 1 Ohm, it is given, this is $R_s e$ and this is $n 2$ is 375 rpm therefore, $E_b 2$ is equal to V minus your, 18 70.75 into that r_a plus $R_s e 1$ that is. So, it you will get V minus 18.75, but V we have to determine and we know that back Emf proportional to flux into speed therefore, $E_b 1$ upon $E_b 2$, first condition and second condition you can write $\phi 1 n 1$ upon $\phi 2 n 2$ right is equal to and because, it you can write $I_a 1 n 1$ upon $I_a 2 n 2$.

Because, your flux is proportional to the armature current in series machine series motor, there $\phi 1$ by $\phi 2$ is equal to basically, $I_a 1$ upon $I_a 2$. So, substitute here, it will be $I_a 1 n 1$ upon $I_a 2 n 2$. So, substitute all this value because, all this values are known right. So, and this is $E_b 1$ upon $E_b 2$, $E_b 1$ is 215 volt and $E_b 2$ is this much V minus 18.75. So, this one is equal to this one. So, from which if you solve, you will get V is equal to 350.65 volt right.

Now, next is another example. So, this is the answer. So, simple problem just you have to keep your relationship in your fingertip. So, everything will be solved right.

(Refer Slide Time: 19:11)

Ex-4:

A series motor with negligible field resistance when run at a certain load takes 40 Amp at 500 Volt. If the load torque varies as the cube of the speed, find the resistance necessary to reduce the speed to 80 percent of its original value.

Soln.

Now, next is a series motor with negligible field resistance, when run at a certain load takes 40 ampere at 500 volt, if the load torque varies as the cube of the speed the torque is proportional to n^3 , find the resistance necessary to reduce the speed to 80 percent of it is original value right.

So, if initially it was n , it will be it is it will be $0.8n$ then right. So, you have to find out that your, what you call the resistance necessary right.

(Refer Slide Time: 19:42)

For series motor,
 $T \propto I_a^2$, given that, $T \propto n^3$
 $\therefore \frac{T_1}{T_2} = \left(\frac{I_{a1}}{I_{a2}}\right)^2 = \left(\frac{n_1}{n_2}\right)^3$
 Here, $I_{a1} = 40 \text{ Amp}$, $V = 500 \text{ volt}$, $\left(\frac{n_1}{n_2}\right) = \frac{1}{0.8}$ ✓
 $\therefore \frac{(40)^2}{I_{a2}^2} = \left(\frac{1}{0.8}\right)^3 \therefore I_{a2} = 28.62 \text{ Amp.}$
 Also, $\frac{E_{b1}}{E_{b2}} = \frac{500}{500 - I_{a2}R} = \frac{\Phi_1 n_1}{\Phi_2 n_2} = \frac{I_{a1} n_1}{I_{a2} n_2} = \frac{40 \times 1}{28}$
 $\therefore \frac{500}{500 - I_{a2}R} = 1.747$

So, for series motor torque, we know proportional to armature current square and it is given T proportional to n cube; that means, we can write T_1 by T_2 is equal to I_{a1} upon I_{a2} whole square is equal to n_1 upon n_2 whole cube right first case, second case right.

Now, I_{a1} is given 40 ampere, V is equal to 500 volt and n_1 by n_2 is given 80 percent. So, it will be your, what you call that second case, the speed is 80 percent of the first case because, we are reducing the speed. So, n_1 upon n_2 will be 1 upon 0.8, I mean I mean, it is ~~it is s~~ something like this, it is first case, if first case if it is n , first case if it is n then second case, it is $0.8n$ therefore, n upon $0.8n$ is equal to 1 upon 0.8 that ~~that~~ is written here right.

(Refer Slide Time: 20:37)

Here, $I_{a1} = 40 \text{ Amp}$, $V = 500 \text{ Volt}$, $\left(\frac{n_1}{n_2}\right) = \frac{1}{0.8}$

$$\therefore \frac{(40)^2}{I_{a2}^2} = \left(\frac{1}{0.8}\right)^3 \quad \therefore I_{a2} = 28.62 \text{ Amp.}$$

Also,

$$\frac{E_{b1}}{E_{b2}} = \frac{500}{500 - I_{a2}R} = \frac{\Phi_1 n_1}{\Phi_2 n_2} = \frac{I_{a1} n_1}{I_{a2} n_2} = \frac{40 \times 1}{28.62 \times 0.8}$$

$$\therefore \frac{500}{500 - 28.62R} = 1.747$$

$$\therefore R = 7.47 \Omega$$

So, if; that means, these are the data given. So, 40 square upon I a 2 square is equal to 1 upon 0.8 cube from which, we get I a 2 is equal to 28.62 ampere right. Now also we know E b 1 is 500 volt. First case given, second case some resistance R is inserted. So, 500 minus I a 2 into r is equal to same as before 5 1 n 1 upon phi 2 n 2 is equal to I a 1 n 1 upon I a 2 n 2 same as before is equal to 40 into 1 right, I mean I a 1 is 40 I a 2 is 28.62. So-so 40 upon 28.62 into n 1 upon n 2 actually, 1 upon 0.8 right. So, from which if you solve, you will get R is equal to 7.47 Ohm right. So, this is the answer, this much resistance has to be inserted right.

(Refer Slide Time: 21:29)

EX-5: A 250 volt shunt motor has $r_a = 0.5 \Omega$ and $R_f = 250 \Omega$. When driving a load, the torque of which is constant takes 30 Amp and runs at 500 rpm. It is desired to raise the speed of the motor to 750 rpm. What resistance should be inserted in the shunt field circuit?

Soln.

$r_a = 0.5 \Omega$, $R_f = 250 \Omega$
 $I_{a1} = 30 \text{ Amp}$, $n_1 = 500 \text{ rpm}$

The circuit diagram shows a 250 volt source connected to a shunt motor. The field winding has a resistance $R_f = 250 \Omega$ and the armature has a resistance $r_a = 0.5 \Omega$. The armature current is $I_{a1} = 30 \text{ Amp}$. The motor is represented by a circle with a plus sign and a minus sign, and the back EMF is labeled E_{b1} .

So, next is a 250 volt shunt motor has r_a is equal to 0.5 Ohm and R_f field resistance 250 Ohm, when driving a load the torque of which is constant takes torque is given constant takes 30 ampere and runs at 500 rpm, it is desired to raise the speed of the motor to 750 rpm. So, 500 to 750, you have to raise the speed, what resistance should be inserted in? The shunt field circuit right.

So initially, when this initially there was 1 resistance in the circuit. So, r_a is 0.5, R_f 250, I_a 30 ampere, n 500 rpm right. So, everything is given. So, given that the torque of torque of the load is constant.

(Refer Slide Time: 22:12)

Soln.

$r_a = 0.5\Omega$, $R_f = 250\Omega$,
 $I_{a1} = 30\text{ Amp}$; $n_1 = 500\text{ rpm}$

Given that the torque of the load = constant

$E_{b1} = V - I_{a1} r_a = 250 - 30 \times 0.5$
 $\therefore E_{b1} = 235\text{ volt} \dots (1)$

When running at 750 rpm, let the current through

(a)

So, torque is a constant and back Emf in the first case E_{b1} will be V minus $I_{a1} r_a$. So, V 250, I_{a1} 30 and r_a 0.5; So, 230 fie volt right in the first case.

Now, in the second case, we have to raise the speed to 750 rpm. So, a resistance R had been inserted here, we have to find out, what is the R ? When running at 750 rpm, let the current through the armature be I_{a2} at that time it is I_{a2} right so; that means, E_{b2} is equal to V minus $I_{a2} r_a$.

(Refer Slide Time: 22:40)

When running at 750 rpm,
let the current through
the armature be I_{a2} .

$$\therefore E_{b2} = V - I_{a2} r_a$$

$$\therefore E_{b2} = (250 - 0.5 I_{a2}) \quad \text{--- (i)}$$

We know, $E_b \propto \phi n$.

$$\therefore \frac{E_{b1}}{E_{b2}} = \frac{\phi_1 n_1}{\phi_2 n_2} = \frac{500 \phi_1}{750 \phi_2} = \frac{2 \phi_1}{3 \phi_2} \quad \text{--- (ii)}$$

So, r_a is 0.5 Ohm therefore, E_{b2} is equal to 250 minus 0.5, I_{a2} right, this is the circuit diagram for the second case.

-Now, we know that back EMF is proportional to ϕ into n or is same as before, we can write E_{b1} upon E_{b2} is equal to $\phi_1 n_1$ upon $\phi_2 n_2$ right. So, if you if an n_1 is 500 rpm first case and n_2 is the 750. So, 500 upon 750 into ϕ_1 by ϕ_2 that is $2 \phi_1$ upon $3 \phi_2$, this is equation 3 right.

(Refer Slide Time: 23:12)

Also, $T \propto \phi I_a$

$$\therefore \text{But torque is constant, i.e., } T_1 = T_2$$

$$\therefore \phi_1 I_{a1} = \phi_2 I_{a2}$$

$$\therefore \frac{\phi_1}{\phi_2} = \frac{I_{a2}}{I_{a1}} = \frac{I_{a2}}{30} \quad \text{--- (iv)}$$

\therefore From Eqns. (1), (2), (3) and (4), we get

$$\frac{235}{250} = \frac{2}{3} \times \frac{I_{a2}}{30}$$

Now, torque is given that proportional to phi into I a, but torque remain constant, but torque both the cases torque remain constant. So, T 1 is equal to T 2; that means, for; that means, phi 1 into I 1 I a 1 is equal to phi 2 into I a 2 because, torque, this torque remain constant therefore, first case if it is phi 1 I a 1 second case, it is phi 2 I a 2 from which, we get phi 1 upon phi 2 is equal to I a 2 upon I 1 is equal to I a 2 upon 30 because, I a 1 is equal to 30 ampere right.

Therefore, from equation 1, 2, 3, 4 right.

(Refer Slide Time: 23:48)

$$\therefore \phi_1 I_{a1} = \phi_2 I_{a2}$$

$$\therefore \frac{\phi_1}{\phi_2} = \frac{I_{a2}}{I_{a1}} = \frac{I_{a2}}{30} \quad \text{--- (iv)}$$

$$\therefore \text{From Eqns. (i), (ii), (iii) and (iv), we get}$$

$$\frac{235}{250 - 0.5 I_{a2}} = \frac{2}{3} \times \frac{I_{a2}}{30}$$

$$\therefore I_{a2} = 46 \text{ Amp}$$

From Fig. 1.1

Therefore, from equation 1, 2, 3, 4 right So, actually this is your, what you call, this one will be italic right, this one actually, it is actually equation 1. This is your equation 2, this is equation 3 and this is equation 4 actually, this way some correction right. So, if you from equation 1, 2 and 3, 4 you substitute all these things. So, you will get, you will get your what you call that your 235 upon 250 minus 0.5, I a I a 2 is equal to 2 third into I a 2 by 30. So, if you solve this quadratic equation, 1 solution may not be feasible and answer will be I a 2 is equal to 46 ampere right. So, little bit practice is necessary.

(Refer Slide Time: 24:33)

From Fig(a),

$$I_{f1} = \frac{250}{250} = 1 \text{ Amp}$$
 From Fig(b),

$$I_{f2} = \frac{250}{R+R_f} = \frac{250}{(R+250)} \text{ Amp.}$$
 From Eqn(4),

$$\phi_1 I_{a1} = \phi_2 I_{a2}$$

$$\therefore \frac{\phi_1}{\phi_2} = \frac{I_{f1}}{I_{f2}} = \frac{I_{a2}}{I_{a1}} = \frac{46}{30}$$

$$\therefore \frac{1}{I_{f2}} = \frac{46}{30}$$

So, now from figure a:- [Soso](#), as you as from figure a, we get I f 1 is equal to 250 upon 51 ampere because, if you look into this figure, this is your 250 volt and this is 250. So, for first case, field current was 1 ampere 250 upon 250 and in the second case, circuit the figure a the field current I f 1 will be 250 upon 251 ampere, but second case, I f 2 will be 250 upon R plus f R f.

(Refer Slide Time: 25:05)

From Eqn(4),

$$\phi_1 I_{a1} = \phi_2 I_{a2}$$

$$\therefore \frac{\phi_1}{\phi_2} = \frac{I_{f1}}{I_{f2}} = \frac{I_{a2}}{I_{a1}} = \frac{46}{30}$$

$$\therefore \frac{1}{I_{f2}} = \frac{46}{30}$$

$$\therefore I_{f2} = \frac{250}{R+250} = \frac{30}{46}$$

$$\therefore R = 134 \text{ } \Omega \text{ } \text{Amp.}$$

So, 250 upon R plus 250 ampere. Now, equation 4. So, phi 1 I a 1 is equal to phi 2 I a 2. So, we know that flux is proportional to the field current. So, we can make phi 1 upon

phi 2 is equal to I f 1 upon I f 2 is equal to your, I a 2 upon I a 1, substitute I a 2 is 46, we got I a 1 30. So, 1 upon I f 2 is equal to 46 upon 30, but I f 2 is equal to 250 upon R plus 250 right. So, is equal to this 46 divided by 30. So, it will be 30 by 46. So, after solving this for R, you will get R is equal to 134 Ohm, this is your answer right.

(Refer Slide Time: 25:45)

Ex-6: A six pole lap-connected 230 Volt ⁽⁴⁸⁾ shunt motor has 410 armature conductors. It takes 41 Amp on full-load. The flux per pole is 0.05 Wb. Given that $r_a = 0.1 \Omega$, $R_f = 32 \Omega$ and ~~brush~~ contact drop per brush = 1 volt. Determine the speed of the motor at full-load.

Soln.

$I_a = 41 \text{ amp}$ $I_a = 40 \text{ Amp}$

So, next is that example 6. A six pole lap connected 230 volt shunt motor has 410 armature conductors, it takes 41 ampere on full load, the flux per pole is 0.05 weber given that r_a is equal to 0.1 Ohm field resistance R_f 32 Ohm and contact drop per brush is given 1 volt. So, 2 brushes will be there. So generally, it will be total will be 2 volt right, it is given per brush determine the speed of the motor at full load.

(Refer Slide Time: 26:16)

Soln.

$P = 6$
 $A = 6$
 $Z = 410$
 $I_L = 41 \text{ Amp}$
 $\phi = 0.05 \text{ Wb}$
 $r_a = 0.1 \Omega$
 $V = 230 \text{ Volt}$, $R_f = 230 \Omega$, $\therefore I_f = \frac{V}{R_f} = \frac{230}{230} = 1 \text{ Amp}$
 $\therefore I_a = I_L - I_f = 41 - 1 = 40 \text{ Amp}$

So, it is given lap connected pole is equal to 6. So, therefore, for lap connection parallel path will be A is equal to P is equal to 6 right. So, Z is equal to given 410, that number of conductor that this current I_L is given 41 ampere, flux is given 0.05, weber r a armature resistance is given 0.1 Ohm, terminal voltage V is given 230 volt, R f is given 230 Ohm therefore, all this everything, you put here and there are 2 brushes. So, delta E will be 1 into 2: SoSo, 2 volt right. So, what will happen? First, you find the field current.

I_f is equal to look at the cursor V upon R f that is 230 upon 230 is equal to 1 ampere right.

(Refer Slide Time: 27:00)

$r_a = 0.1 \Omega$
 $V = 230 \text{ Volt}, R_f = 230 \Omega, \therefore I_f = \frac{V}{R_f} = \frac{230}{230} = 1 \text{ Amp}$
 $\therefore I_a = I_L - I_f = 41 - 1 = 40 \text{ Amp.}$
 $\therefore E_b = V - I_a r_a - \Delta E = 230 - 40 \times 0.1 - 2$
 $\therefore E_b = 224 \text{ Volt} = \frac{\phi \cdot Z \cdot n \cdot p}{60 \cdot A}$
 $\therefore 0.05 \times 410 \times \frac{n}{60} \times \frac{6}{6} = 224$
 $\therefore n = 655.6 \text{ rpm Ans.}$

Now armature current, this I_a at this point, you apply kcl. So, I_a will be I_L minus I_f . So, 41 minus 1. So, 40 ampere, now in this case, the brush contact drop is given per brush 1 volt. So, E_b you know V minus $I_a r_a$, but keep it in your mind also this drop has to be subtracted minus ΔE , you may right such that, there should not be any small error.

So, but ΔE will be 2 volt because, per brush 1 volt that is why, it is written 1 into 2. Look at the cursor, 1 into 2 volt right so; that means, means 230 minus 40 into 0.1 minus 2. So, now, we also know that E_b is equal to 224 volt and we also know E_b is equal to $\frac{\phi \cdot Z \cdot n \cdot p}{60 \cdot A}$. So, it will be ϕ is 0.05 weber Z is 410, n by 60, p is lap connection. So, A is equal to P . So, 6 by 6 is equal to 224.

Therefore n is equal to 655.6 rpm right. So, this is the answer. So, this problems are very simple problem, only you have to keep little bit in your mind with this course, I mean whatever little bit, we discussed this course will be is completed right. So, particularly at the first year level that is a single phase transformer has been covered right and induction machine and DC motor just, I have touched, I have not gone through the details considering that, you may be in the first year right or anybody can take this course, but it is just basic thing, we have discussed right not nothing is in detail.

And induction machine also because, most of the time, we have spent for deriving the equivalent circuit right, but starting of induction machine or starting of DC machine, we

have not touched or many other things, we have not touched thinking that, you are just learning this. So, just those, who will be listening this last lecture right. So, my suggestion is the practice few problems, I mean take any book, I mean, you can take any good book and you just try right with this.

Thank you very much.