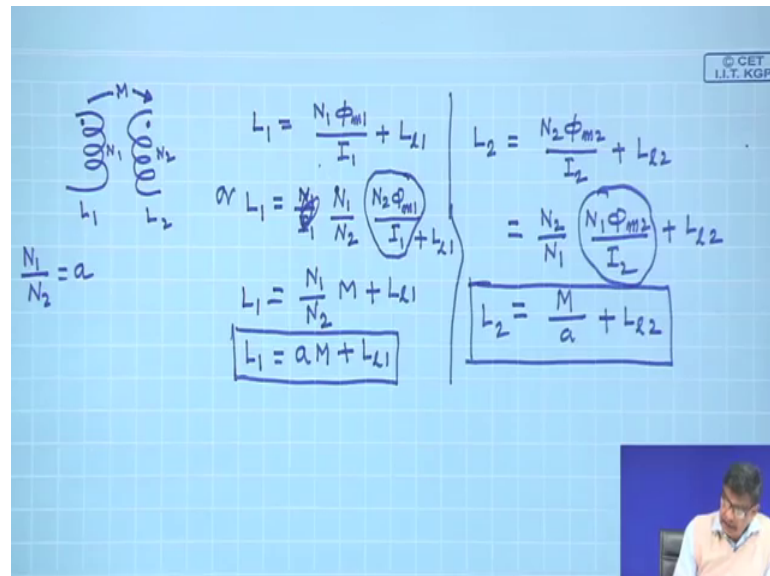


Electrical Machines - II
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture – 03
Equivalent Circuit from Circuit KVL Equations

(Refer Slide Time: 00:29)



Welcome to the 3rd unit of this lecture, you recall that we were discussing about the coupled coils, which I will draw simply like this. And this coupled coils have self-inductance L_1 , L_2 , number of turns N_1 , N_2 . And the mutual inductance between them is M , this is the thing.


And the magnetic circuit, I am not drawing that means the core I am not drawing. You recall that the expression of the self-inductance, we got as $N_1 \phi_{m1} / I_1$, in our 1st unit we have discussed about this, and this is the leakage inductance that is the 1st lecture with this expression I am writing. And similarly L_2 , we got as $N_2 \phi_{m2} / I_2$ plus L_{l2} , these are leakage inductances ok.

Now, this self-inductance can be expressed in terms of leakage inductance as well as this term. But, this term can be nicely simplified in terms of mutual inductance term. How to do it? This or I can write L_1 is equal to N_1 and then what I will do N_1 by I_1 I will write and I am sorry what I will do is this, I will multiply and divide by N_2 . So, this can be as $N_2 \phi_{m1} / I_1$ plus L_{l1} multiply and divide by N_2 , you get this.

Now, you can certainly recognize this term. This is what coil 1 is energized with I_1 current, ϕ_{m1} is the mutual flux created by coil one. So, N_2 into ϕ_{m1} by I_1 is nothing but mutual inductance. So, this is N_1 by N_2 into M plus L_{11} , this is the self-inductance. And if we say that the turns ratio let us define this to be small a , then L_{11} is nothing but a into M plus L_{11} . This is in terms of mutual inductance and leakage inductance, self-inductance will look like.

In the same way, if you look at L_2 what you do is this, you divide by N_1 and multiply with N_1 , then we can recognize this to be once again mutual inductance. Since, there is no difference between m_{12} and m_{21} so, this can be then written as M by a this N_1 by N_2 is 1 by N N_2 by N_1 plus L_{12} . And mind you this I_1 and I_2 are the currents considered I considered DC current one excited at a one time, but in any case this is the thing. Now, these things, we will use to derive the equivalent circuit.

(Refer Slide Time: 05:15)

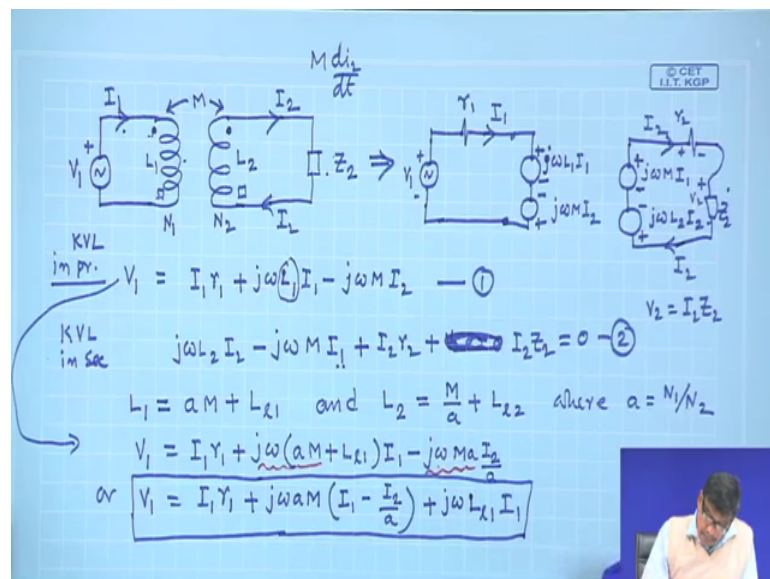

And to do that in my last class, I was telling that you consider these two couple coils and consider that you have applied an AC voltage, which is whose RMS value is V_1 and this is I_1 is the AC current drawn by this coil having turns N_1 . And these are having mutual inductance M and self-inductance L_1 and self-inductance L_2 . And this side on the secondary side, we will connect some impedance Z_2 . These are all complex number Z_2 , V_1 , I_1 and this current is suppose I_2 .

Now, this circuit this is a very important step, it can be drawn like this V_1 applied voltage. And let us assume the winding is having a resistance that is r_1 . And then you have two sources of EMF here, because both the coils are carrying current one is and polarity is important. $L_1 \frac{di_1}{dt}$ in time domain terms, which comes out to be $j\omega L_1 I_1$. Then you have another voltage drop here whose polarity will be like this, because I_2 is entering here.

These two are also can be parallely thought of a dot. So, current entering here will have polarity of the induced voltage in the other coil as this plus, this minus. And the value of these in time domain is $M \frac{di_2}{dt}$, but $\frac{d}{dt}$ if you substitute $j\omega$, small i_2 have a phasor capital I_2 , so this will be $j\omega M I_2$, this is this side.

Similarly, the other side what will be the things, other side between these two terminals, there will be two sources of EMF. One is I_2 is entering through this, therefore the self-inductance drop $j\omega L_2 I_2$. And then the mutual inductance, because primary winding 2 is carrying a current of I_1 this is dot, this is dot. Current is entering through the dot, so other dot is plus.

So, the polarity of this voltage will be this mind you this is $I_1 I_1$, and this is minus and this is $j\omega M I_1$. And then of course if winding is having a resistance, you are having r_2 . And then you have this Z_2 current, I think I move it a bit this side this is the thing that is two voltages are there because of self-inductance and because of mutual inductance r_2 and Z_2 and this is how I have said the current direction I_2 .

And on the side there is no voltage source connected, but anyway this voltage let me call is to V_2 terminal voltage, where V_2 is obviously equal to I_2 into Z_2 ok. So, when both the coils are carrying current, this is the scenario I get it. Now, what I will do is this, I will write down the as I told you simply write down the KVL equations in both the loops. So, first this side KVL equation is see applied voltage V_1 will be equal to I_1 into r_1 plus $j\omega L_1 I_1$ and then minus $j\omega M I_2$, and you are back here. So, this is the 1st equation, similarly so KVL in primary.

Similarly, similarly let us write down KVL equation in secondary, mind you all these quantities are phasors. KVL in secondary will be there is no external voltage connected. So, we start from any point we like and sum of all the voltages. So, suppose from plus to minus this voltage is $j\omega L_2 I_2$, so plus to minus I am writing plus. So, then I must

write $j\omega MI_1$ and this drop is also plus to minus that I am writing plus plus $I_2 r_2$, and this plus to minus so once again V_2 is that correct.

So, plus to minus $j\omega$ plus to minus if I am going and this is equal to 0 let us write plus there. So, $j\omega L_2$, then minus it is minus to plus $j\omega MI_1$ because of this coil current, there is additional voltage here. Then plus $I_2 r_2$ once again plus to minus and plus to minus v_2 and this V_2 is of course $I_2 Z_2$ I can write like that $Z_2 I_2$ that is all. So, this is the thing. So, these are the two basic equations 1 and 2.

Now, we will use this knowledge that L_1 in our last lecture, we have found out that L_1 is equal to aM plus L_{11} . And L_2 is equal to M by a plus L_{22} , where a is equal to N_1 by N_2 is not it, this is the thing. So, let us take the 1st equation and for this L_1 , we will now put this expression that is V_1 applied voltage is equal to resistance drop $I_1 r_1$ plus $j\omega$ for capital L_1 , I will write aM plus L_{11} into I_1 and minus $j\omega M$.

Now, $j\omega MI_2$ is there I_2 . What I will do this, I will just divide by small a and multiply by a , so it remains $j\omega MI_2$. This is the trick I have applied here, division will be clear, why it is done. Then or V_1 is equal to I_1 into r_1 plus $j\omega aM$, you see $j\omega aM$ occurs here and also occurs here. So, I can combine these two terms, and write $j\omega aM$ into I_1 and minus I_2 by a . This I can do, these two I can do, and then plus $j\omega L_{11}$ into I_1 you know this is what it comes out that is all.

(Refer Slide Time: 15:59)

from KVL equⁿ of 2nd coil:- $L_2 = \frac{M}{a} + L_{22}$

$$j\omega L_2 I_2 - j\omega M I_1 + I_2 r_2 + I_2 Z_2 = 0$$

$$\text{or } j\omega \left(\frac{M}{a} + L_{22} \right) \frac{I_2}{a} a - j\omega M I_1 + \frac{I_2}{a} a r_2 + \frac{I_2}{a} a Z_2 = 0$$

$I_2 \rightarrow \frac{I_2}{a}$

$$\text{or } j\omega \left(M + aL_{22} \right) \frac{I_2}{a} - j\omega M I_1 + \frac{I_2}{a} a r_2 + \frac{I_2}{a} a Z_2 = 0$$

Multiply both sides by 'a'.

$$\text{or } j\omega (aM + a^2 L_{22}) \frac{I_2}{a} - j\omega a M I_1 + \frac{I_2}{a} a^2 r_2 + \frac{I_2}{a} a^2 Z_2 = 0$$

Now, let us similarly play with the 2nd equation 2nd KVL equation that is the KVL equation of the 2nd coil, which we have already got. So, from KVL equation of 2nd coil. We have got $j\omega L_2 I_2$ that is this equation, I wrote in the previous page, this equation I am now taking $j\omega L_2 I_2$ minus $j\omega M I_1$, hopefully I have written the polarities correctly plus $I_2 Z_2$ is equal to 0.

Then what I am going to do is recall that L_2 is equal to M by a plus L_{12} L_2 is equal to M by a plus L_{12} , so that thing I will put plug in for L_2 here that is M by a plus L_{12} this into I_2 . And wherever I_2 is there, you do this thing I_2 by a into a. So, this term is this term. Minus $j\omega M I_1$ and then plus I_2 once again do like this, I_2 by a into a r_2 , wherever I_2 is there try to modify it to I_2 by a. But, you cannot just divide by a, if you divide you have to multiply by a that is what exactly I am doing it. So, this term is this term and plus I_2 by a into a Z_2 and this is equal to 0, this is the thing is not.

Now, or $j\omega$ this small a you push it inside, so that it will be M plus a L_{12} into I_2 by a minus $j\omega M$, wherever I_1 is there do not disturb it plus this I have not done anything I_2 by a a into r_2 plus I_2 by a into a into Z_2 is equal to 0, mind you are all complex numbers. Now, what I will be doing is I will be multiply both sides by turns ratio a. So, if you multiply, then it will become or $j\omega$ this a you push it inside, it will be a M plus a square L_{12} into I_2 by a minus $j\omega a M I_1$ plus I_2 by a into a square into r_2 plus I_2 by a into a square into Z_2 and this is equal to 0.

So, what are the things I have done, secondary coil KVL equation I have written, wherever so and then I have substituted for L_2 ; L_2 I have expressed in terms of mutual inductance and leakage inductance. What is the reason for that, because in the transformer equivalent circuit I know there is no term representing capital L_1 self-inductance is absent.


It is expressed in terms of mutual inductance terms and L_{12} , so that is the reason L_2 I have replaced by expressed it in terms of mutual inductance and leakage inductance and put it here. And wherever I_2 is there, I am simply telling that you divide by a multiply by a, so that I_2 is written minus $j\omega M I_1$ do not disturb and then plus I_2 by a into a r_2 plus I_2 by a into a Z_2 is equal to 0.

And then in the next step what I am telling the say you have put it inside, so it has become a a cancels. So, M plus this, then you multiply both sides by small a. So, $j\omega$

this small a you put it inside, so a M plus square L 1 2 etcetera minus j omega a M I 1 plus I 2 by a a square r 2 plus I 2 by a a square Z 2. So, this is the 2nd equation. So, these two equations are now like this is one and this is one.

And we are done and in equivalent circuit now can be drawn, let us see how. So, these two equations we will keep in mind. So, these are the two equations. This is the primary side equation this is the primary side equation, this is the secondary side equation. Let us see, how it helps us to write down.

(Refer Slide Time: 23:29)

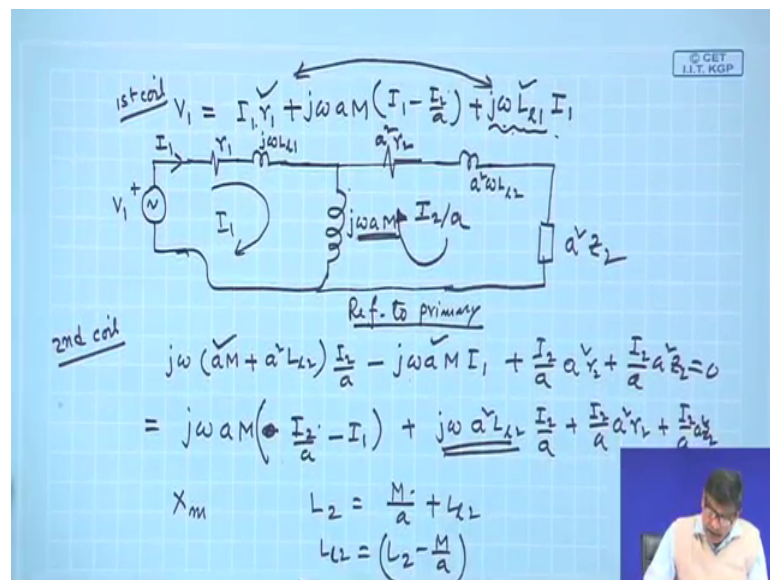

Suppose, I want to draw a circuit diagram or let me write here. So, the first KVL equation, we have got re-write V 1 is equal to I 1 r 1 plus j omega a M into I 1 minus I 2 by a and plus j omega L 1 1 leakage inductance I 1. Now, this can be drawn like this, because I know the terms this is my V 1 and this is my I 1 earlier it was coupled coils, now I am telling ok, there is a resistance here I 1 r 1 draw, then there is I 1 into j omega L 1 1.

These two terms, you combine. So, r 1 plus j omega L 1 1 leakage inductance drop so, this drop plus this drop. Then there is another drop, which is occurring in a inductance coil, it is not transformer coil. Now, I am trying to translate this in terms of circuit and I will tell it is a reactance of value j omega a M and I close it. So, this is I 1 is it correct.

If somebody says it means this, no because of the fact so I have taken this term this term and $j\omega M I_1$ that is fine. But, there is a term $-I_2$ by a into $j\omega M$, so how to do it.

So, what I will do, I will write I_2 by a here. And in this loop what is there I do not know, suppose a current source I_2 by a here, then of course everything is fine so far as primary coil is concerned, because V_1 is equal to $I_1 r_1$ plus $j\omega L_1 I_1$ plus $j\omega M I_1$, then mesh analysis I know there is another loop here existing, which is providing you this current I_2 by a flowing in the opposite direction, so that will be $-j\omega M I_1$ into I_2 by a, then it is fine I mean primary coil.

Similarly, now the question is what is here in this side ok. 2nd equation will help me to do that. The 2nd equation if you recall, it was this was the first loop 1st coil KVL. 2nd coil KVL, we have already got. 2nd coil KVL was $j\omega M I_1$ plus a square $L_2 I_2$ into I_2 by a minus $j\omega M I_1$ plus I_2 by a square r_2 plus I_2 by a square Z_2 is equal to 0.

Therefore, the 2nd KVL equation is telling me that this voltage drop that is $j\omega M I_1$ into I_2 by a minus $j\omega M I_1$ into this so this can be written as $j\omega M I_1$ minus again I_2 by a this first term I am taken in minus I_1 plus $j\omega L_2 I_2$ by a and then you write this I_2 by a a square r_2 and then plus I_2 by a a square Z_2 and that is equal to 0.

So, you see this voltage drop I_2 by a into $j\omega M I_1$ is taking place here. And then minus $j\omega M I_1$ into I_1 is in the opposite sense. So, I_2 by a minus I_1 mesh analysis, then what you have got. Then you have got the resistance from r_2 whose value is a square r_2 a square r_2 in to I_2 by a plus the leakage reactance drop, whose value is I_2 by a is this term a square ωL_2 a square ωL_2 into I_2 by a is this term.

And then this drop, whose value is a square into Z_2 is it not. So, I have played with these two KVL equations and that I did this circuit this is your mesh current, you must be familiar with mesh current equations. So, you now see both the loop equations are very nicely satisfied. And the equivalent circuit of a transformer, referred to the primary is obtained.

And this circuit was obtained by considering several physical things this way that way. But, I now get if the turns ratio is there, the secondary impedances must be multiplied by

a square that thing has come this thing. Generally, now also it gives me a better physical inside. For example, the magnetizing reactance X_m what about is drawing, I find they refer to the primary. It is not M it is a into M multiplied by $j\omega$.

The leakage inductance L_{l1} , whatever is coming that we have found out how it is related that is you recall L_2 is equal to M by a plus L_{l2} . So, L_{l2} is nothing but the difference of these two numbers. Are you getting? So, today, I am stopping here, but please go through it, it is a circuit approach to arrive at the equivalent circuit of a transformer in a very decent and nice ways.

Thank you.