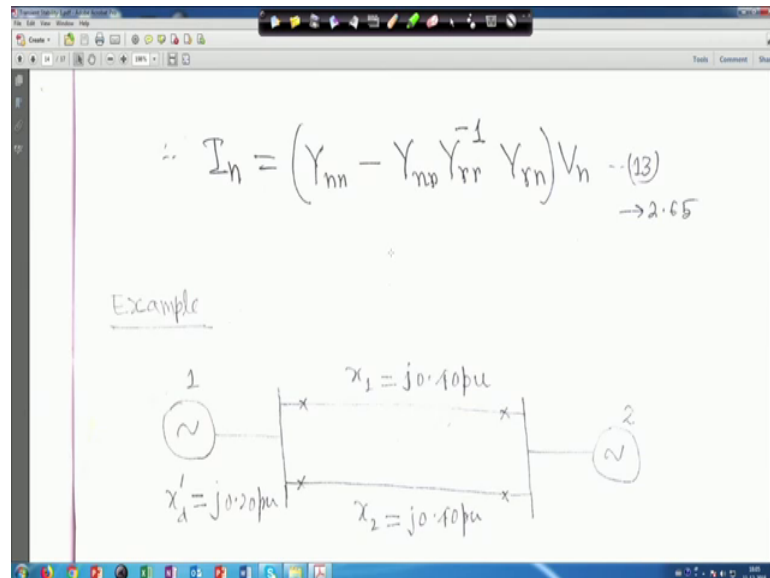


Power System Dynamics, Control and Monitoring
Prof. Debapriya Das
Department of Electrical Engineering
National Institute of Technology, Kharagpur

Lecture - 29
Transient stability (Contd.)

(Refer Slide Time: 00:29)



Ok. In the previous class we have finished this one that I_n is equal to bracket Y_{nn} minus Y_{nr} into Y_{rr} inverse into Y_{rn} bracket close then multiplied by V_n , this is equation-13 right. Now, we will take one example right. This example is your double circuit line right, the problem is something like this is double circuit line. For the generator one that x_d dash is given right $j 0.2$ per unit. And is a double circuit line x_1 is given $j 0.40$ per unit, this is also $x_2 j 0.40$ unit. And of course this is another generator, but x_d is not given right.

So, in this problem we have to find out prefault, then fault, and then post fault admittance matrix right. And fault has occurred actually three phase fault has occurred in that your middle of the line it is the middle of the line that we will see later right. So, we have to find out that your what you call that what you call that reduced your what you call that admittance matrix right.

So, in this case so in this case now prefault case. So, these are these are all reactances given in per unit. So, first you convert it to admittance, then reciprocal of it, so x_d dash

will be $1 \text{ upon } j \ 0.20$, so it is $\text{minus } j \ 5 \text{ per unit right}$. And bus number here where generator here generator-1, and generator-2 is given, but from this problem we have to we have to create that your bus. So, this is this $x \ d \ \text{dash}$ is given. So, this is as that is why the generator terminal bus is marked as one right.


And then this $x \ d \ \text{dash}$ is given point $j \ 0.20$ that means, you have to take the reciprocal of this, because this will become admittance, so it is $\text{minus } j \ 5 \text{ per unit}$. Similarly, for this one that $j \ 0.40$ and $j \ 0.40$, so $1 \ \text{upon } j \ 0.40$, so $\text{minus } j \ \text{point } 2.5 \text{ per unit}$ similarly, here also it is written at the bottom just hold on right.

So, in this case here also it is $\text{minus } j \ \text{your } 0.25 \ \text{per } 2.5 \ \text{per unit right}$. And this is the here no $x \ d \ \text{dash}$ is given, so this bus is marked as bus-2, and this is marked as a bus-3. And this is one, because $x \ d \ \text{dash}$ was given. So, all these things are actually are in per unit, and these are all admittance values these are all admittance values right.

Now, when we when we calculate this thing, you know that when you found that your Y matrix for prefault you have three bus. So, in general that Y matrix per prefault will be capital $Y_{11} \ Y_{12} \ Y_{13}$ right, then $Y_{21} \ Y_{22} \ Y_{23}$ right, and then Y_{31} capital Y_{32} then capital Y_{33} , this was studied from the load flow studies. So, same thing is here right. So, first is you find out small y_1 , and small when we represent this one first we find small y , and off diagonal we will take minus of the small y right.

So, in this case for in this in this case, suppose you are trying to find out all these your what you call small y values Y_{11} , then your Y_{13} all sort of things. If you take Y_{11} right Y_{11} , it is $\text{minus } j \ 5 \ \text{per unit}$ for this one right. Similarly, if you take Y_{13} , it will be minus your what you call $j \ 5 \ \text{per unit}$, because no charges what you call no charging admittances are considered here or no load is given here right.

(Refer Slide Time: 04:12)

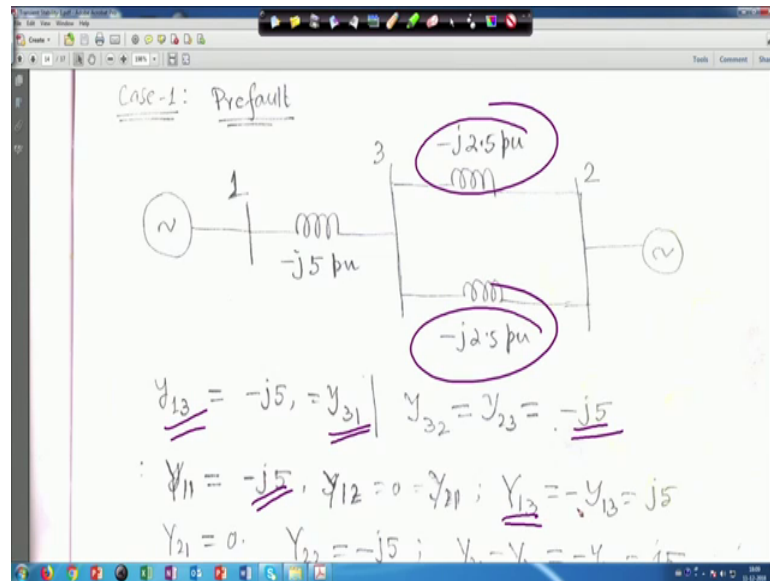

So, in this case what will happen that if you look into this that Y_{11} that is Y_{11} right I told you, it is small y_{13} is equal to minus $j5$ is equal to y_{31} right. Similarly, y_{32} if you take y_{32} is equal to y_{23} minus $j5$, because this is admittance, so minus $j2.5$ this is also admittance minus $j2.5$ they are in parallel, so it will added, because it is admittance right. So, y_{32} is equal to y_{23} that is minus $j2.5$ minus $j2.5$, so total is minus $j5$ right.

Similarly, Y_{11} it will be simply minus $j5$ right. And Y_{12} is equal to no connection between 1 and 1, so $Y_{12} = 0$ is equal to Y_{21} right. And similarly, your now capital Y_{13} is basically minus of that small y , so minus y_{13} , so it is $j5$ right. So, this you know from your load flow studies for forming bus admittance matrix right.

(Refer Slide Time: 05:16)

$$Y_{13} = -j5, Y_{31} = j5; Y_{32} = Y_{23} = -j5$$

$$Y_{11} = -j5, Y_{12} = 0 = Y_{21}; Y_{13} = -Y_{31} = j5$$

$$Y_{21} = 0, Y_{22} = -j5; Y_{23} = Y_{32} = -Y_{32} = j5$$

$$Y_{31} = -Y_{31} = j5; Y_{32} = j5; Y_{33} = -j5 - j5 = -j10$$

Similarly, capital Y 2 1 is 0, capital Y 2 2 will be minus j 5, similarly capital Y 2 3 is equal to capital Y 3 2 is equal to minus small y 3 2 is equal to j 5 right. And Y 3 1 is equal to capital Y 3 1 will be minus small y 3 1 is equal to j 5 right. And capital Y 3 2 will be j 5, and Y 3 3 will be minus j 5 minus j 5 is equal to minus j 10, it is actually minus j 10 right minus j 5 minus j 5 right.

So, if you if you look into look in the diagram that is Y 3 3 that is Y 3, so Y 3 3 will be this one your this one this minus your say I am just making it is minus j 5 right. And another thing is that these two are in parallel. So, their equivalent is minus j 5, so is equal to minus j 10 per unit right, so that means, this is your Y 3 3.

(Refer Slide Time: 06:26)

$$Y = \begin{bmatrix} 1 & -j5 & 0 & j5 \\ 2 & Y_{nn} & -j5 & Y_{nr} \\ 3 & j5 & Y_{rn} & j5 \\ & & & Y_{rr} - j10 \end{bmatrix} \quad n = \underline{\underline{2}} \quad (15)$$

Therefore, prefault bus matrix is minus $j5$ 0 $j5$ 0 minus $j5$ $j5$ and $j5$ $j5$ minus $j0$, but we have two machines. So, this is your three bus problems. So, this is 1, this is 2, this is 3 right you have three machines. But, we have to reduce the Y matrix in the n into n , because n is equal to here 2, because we have two machines that is why this is partition right. And this matrix we will call that is your Y_{nn} that is Y_{nn} means this is 2 2 your number of machines are two, so you represent Y_{nn} . And this is your Y_{nr} right, and this is Y_{rn} , and this is Y_{rr} right; this we have seen this one before right.

(Refer Slide Time: 07:19)

$$[j5 \quad j5 \quad -j10]$$

$$Y_{nn} = \begin{bmatrix} -j5 & 0 \\ 0 & -j5 \end{bmatrix}$$

$$Y_{nr} = \begin{bmatrix} j5 \\ j5 \end{bmatrix}, \quad Y_{rn} = [j5 \quad j5]$$

So, now you have to reduce it into 2 into 2 matrix. So, if we follow this using this so this is my Y_{nn} I told you, and this is Y_{nr} , and this is Y_{rn} , and Y_{rr} simply is a single element right, this is single element.

(Refer Slide Time: 07:30)


$$Y_{rr} = [-j10]$$

$$Y' = Y_{nn} - Y_{nr} Y_{rr}^{-1} Y_{rn}$$

$$\therefore Y' = \begin{bmatrix} -j2.5 & j2.5 \\ j2.5 & -j2.5 \end{bmatrix} \quad 2 \times 2$$

So, if we put all these things here right here, so Y' will be what you call if you put and substitute, so Y' will be minus $j 2.5$ $j 2.5$ $j 2.5$ minus $j 2.5$ right. So, this is actually this matrix is generally a symmetric matrix or three phase fault right, so because Y_{12} is equal to Y_{21} . This is of course this is a simply 2 into 2 matrix right, so this is your prefault matrix.

(Refer Slide Time: 08:03)

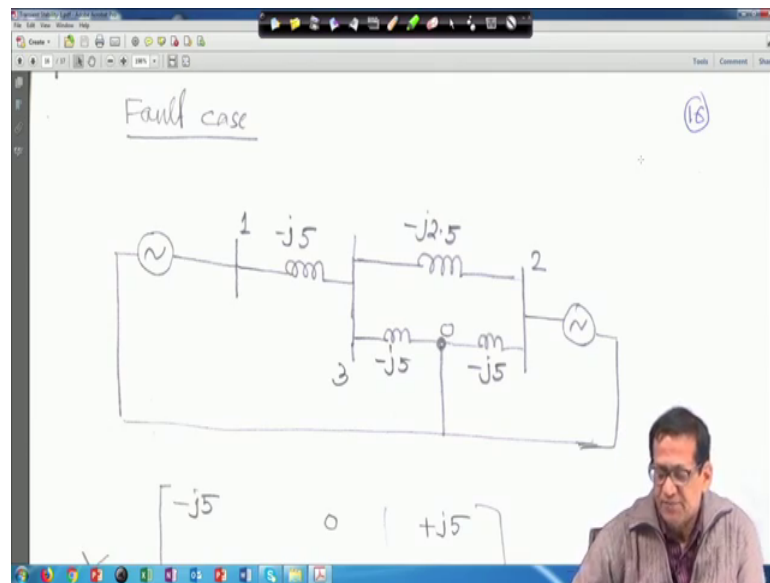

Now, next is next is fault case. Now, three phase fault has occurred in the middle of the line. So, if it is three phase fault has occurred in the middle of the line, you go one of I will go back to the diagram right. So, fault has occurred in the middle of the line say in the middle of the line the fault has occurred, better we will go to the original diagram right.

So, here we will come. So, fault has occurred in the middle of the line. If it is in the middle of the line, this side it will be your this reactance will be half, so this side it will be 0.2, and this side also it will be 0.2 right. So, when fault has occurred, when you replace with the admittance this will be minus $j5$, and this side also will be minus $j5$ per unit right, so that means just hold on, so that means your this diagram when fault has occurred.

(Refer Slide Time: 09:01)

$$Y = \begin{bmatrix} -j5 & 0 & +j5 \\ 0 & -j7.5 & j2.5 \\ j5 & j2.5 & -j12.5 \end{bmatrix}$$

So, that is why this is actually your minus $j 5$ that is why this is minus $j 5$, this is and the three phase fault has occurred right. So, if you construct the Y matrix, it will be minus $j 5$, because this is minus $j 5$ Y_{11} , Y_{12} is 0, and Y_{13} that is your it is minus your of small y_{13} , so it will be plus $j 5$, this you know from your load flows studies.

So, similarly let me move little bit up. So, similarly Y_{21} is 0, Y_{21} no connection between 2 and 1, Y_{21} 0 and Y_{22} Y_{22} means that this one that this one will be added, and fault has occurred here, and then this one will added. So, it will be minus $j 5$, and minus $j 2.5$. So, it will be minus $j 7.5$ right.

And why your what you call 23 will be simply as your what you call that minus your class $j 2.5$ right, because your this thing your that minus of y small minus small y_{23} right. So, if you look into that that 2 to 3 , then 2 to 3 that means this is bus number-3 only this one will come, because fault has occurred. So, please do not consider this one right this side. This side should not be considered only 2 to 3 . So, it is minus small y to 3 , so that is why it is plus $j 2.5$ right.

Similarly, similarly when we will come Y_{31} Y_{31} it is simply minus $j 5$, because plus $j 5$ because it a skew symmetric matrix, then Y_{32} same philosophy Y_{23} is equal to Y_{32} , it will be $j 2.5$. And when it will Y_{33} when it will be Y_{33} , then this one will be added, this one will be added, and this one will be added right.

So, in that case it will be combined as 12.5, because the minus j 5 minus j 5 and minus j 2.5, so minus j 12.5, so that is why that is why this is j 5 j 2.5 and minus j 12.5 right. And this is your what you call that simply this is during fault simply, we will partition simply we will partition right. And this is your Y_{nn} , and this is your Y_{nr} , this is your Y_{rn} , and this is your Y_{rr} it is single element.

(Refer Slide Time: 11:47)


$$\begin{bmatrix} j5 & j2.5 & -j12.5 \\ \dots & \dots & \dots \end{bmatrix}$$

$$Y_{2 \times 2} = \begin{bmatrix} -j3 & j1 \\ j1 & -j7 \end{bmatrix} \leftarrow \text{during fault}$$

And follow the same procedure, same formula used and if you compute then if you if that matrix was matrix reduction right reduce matrix, then final answer will be your this much that $Y_{2 \times 2}$ matrix will be minus j 3 j 1 j 1 minus j 7. This is also symmetric matrix, because Y_{12} is equal to Y_{21} right. So, this matrix this matrix is that is your during fault right this is during fault right.


So, next one is that your post fault. Post fault means, that this line when fault is cleared right, we will go back to we will go back to the diagram that when fault is cleared right, suppose this line it is actually removed; now it has become a single circuit line. So, in that case this one and this one will be there but this is removed right, during when fault is cleared, so that means, we will go back to this and in post fault condition.

(Refer Slide Time: 12:46)

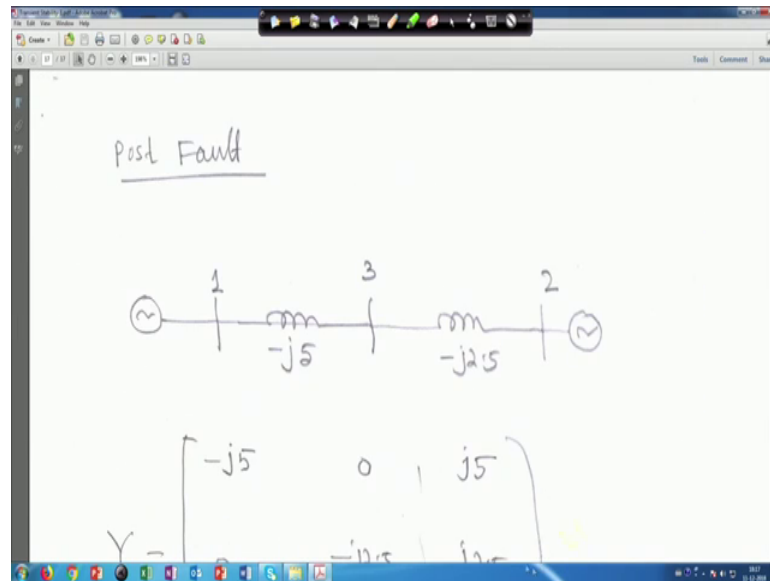

So, this is post fault, so that line is not there.

(Refer Slide Time: 12:53)

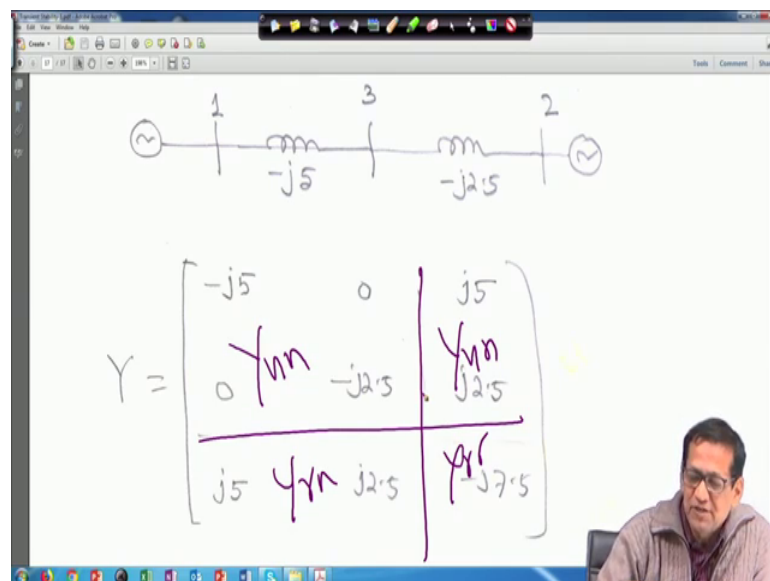


So, 1, 3 and 1, 2, 3, and it is easily you can compute the looking at this network, simply you can compute that your bus admittance matrix right. And your and again you will partition, because it is a 2 into 2 right it is a bus. And so this is your Y_{nn} that is $Y_{2 \times 2}$, this is Y_{nr} , this is Y_{rn} and this is Y_{rr} right. And for following the same equation, you just go for matrix reduction.

(Refer Slide Time: 13:24)

$$Y = \begin{bmatrix} 0 & -j2.5 & j2.5 \\ j5 & j2.5 & -j7.5 \end{bmatrix}$$
$$Y_{2 \times 2} = \begin{bmatrix} -j1.667 & j1.667 \\ j1.667 & -j1.667 \end{bmatrix}$$

So, if you do so if you do so, it will be your what you call this will be the answer right. So, I have not only one step of first one, the prefault case I showed the calculation, but this one you can easily do it, but this will be a symmetric matrix. If you do not get symmetric matrix, then somewhere might have your what you call you might have done wrong calculations right, generally it is a symmetric matrix. So, we will go to another example just hold on.

(Refer Slide Time: 13:49)

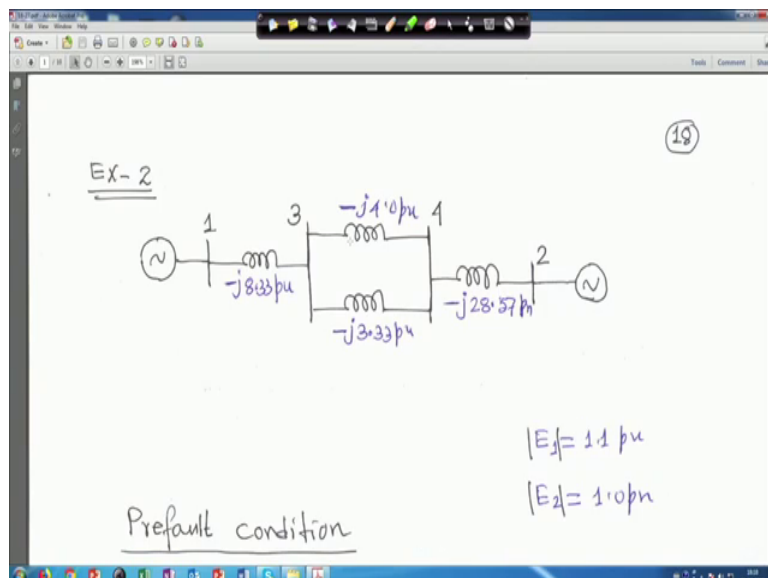

So, we will take another example. So, in this case these example these example that you are two generators are there two generators are there, but this side also all these x d dash all these things that it has this these are all given in admittance. I mean all these parameters that x d 1, dash x d 2 dash line parameters all have been converted to your admittances. So, these are these are all these values, these value, these value, these value, and these value. They are actually admittances right, so this is given. And another thing is given that your magnitude of E 1 voltage E 1 for this bus that your 1.1 per unit and magnitude of E 2 is given 1.0 per unit right, and this is E 1, this is E 2.

And then that pre-fault condition if you just form that your Y matrix right, if you form the Y matrix, so you have 4 bus 1, 2, 3, 4 four bus right. And this voltage E 1, E 2, it is the generator terminal voltage bind the transient reactance, but this is this we have converted to admittance the admittance, but these two are actually transient reactance, you have converted to admittance. And this voltage E 1, and this voltage E 2, basically this is the voltage magnitude right that is bind your transient reactance. So, this is your pre-fault condition Y matrix will just looking at this, you can easily make it right. So, this is my pre-fault condition.

(Refer Slide Time: 15:20)

Pre-fault condition

Full Y matrix

$$= \begin{bmatrix} -j8.33 & 0.0 & j8.33 & 0.0 \\ 0.0 & -j28.57 & 0.0 & j28.57 \\ j8.33 & 0.0 & -j15.57 & j7.33 \\ 0.0 & j28.57 & j7.33 & -j35.9 \end{bmatrix}$$


Since there are two generators in the

That is the matrix order will be 4 into 4, because we have 4-bus system, finally we have to reduce it to 2 into 2. And we have to find out the power delivered pre-fault and post fault, during fault and post fault conditions that is why these two voltage magnitudes are

given say right. So, looking at this looking at this you can easily call these are all admittances right. Looking at this you can easily your what you call you can construct the Y matrix. So, Y matrix actually it is full Y matrix it is prefault condition, this is 4 into 4 matrix right. So, easily you can make it or small y you can calculate, small y 1 1, y 1 2, y 1 3 like this up to your y 4 1, y 4 2, y 4 3, y 4 4 small one. And capital one is equal to the sum of our small one and off diagonal will be minus of small one right. So, this way you can construct the full matrix.


After this we partitioned it, we have partitioned it right. And this is your in this case for this example this is your Y_{nn} , now it is Y_{nr} , it is 2 into 2 matrix. So, all are 2 into 2 matrix, this is Y_{rn} also 2 into 2 matrix right. And this is your Y_{rr} it is also 2 into 2 matrix right. And if you if you look into that, these two matrix are same j 8.33, j two eight 28.57, this is also j 8.33, and j 28.57 right. So, using this same formula right that your bus reduction same formula. So, since there are two generators in the system, the reduced matrix will be of order of 2 into 2 right.

(Refer Slide Time: 17:01)

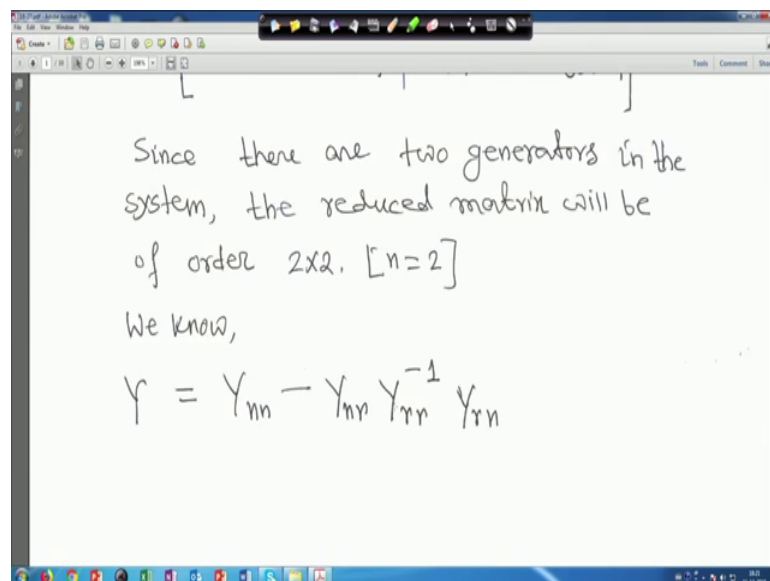

So, we know this thing that Y is equal to Y_{nn} minus Y_{nr} , then Y_{rr} inverse into Y_{rn} this you know. So, we will substitute all I told you that Y_{nn} , Y_{nr} , Y_{rn} , Y_{rr} .

(Refer Slide Time: 17:17)

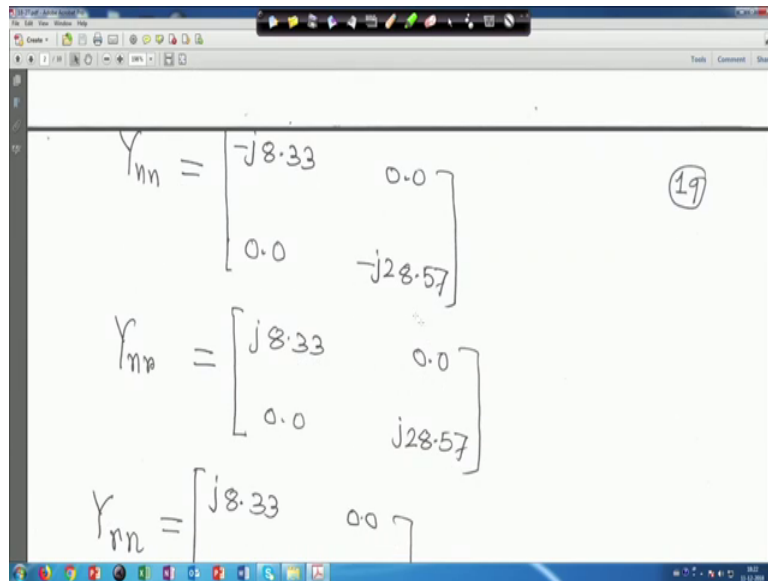


Handwritten equations on a whiteboard:

$$Y_{nn} = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & -j28.57 \end{bmatrix} \quad (19)$$
$$Y_{nr} = \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$$
$$Y_{rn} = \begin{bmatrix} j8.33 & 0.0 \end{bmatrix}$$

If you substitute all, so Y_{nn} I told you this is Y_{nn} , this is Y_{rr} right and this is Y_{rn} .

(Refer Slide Time: 17:24)

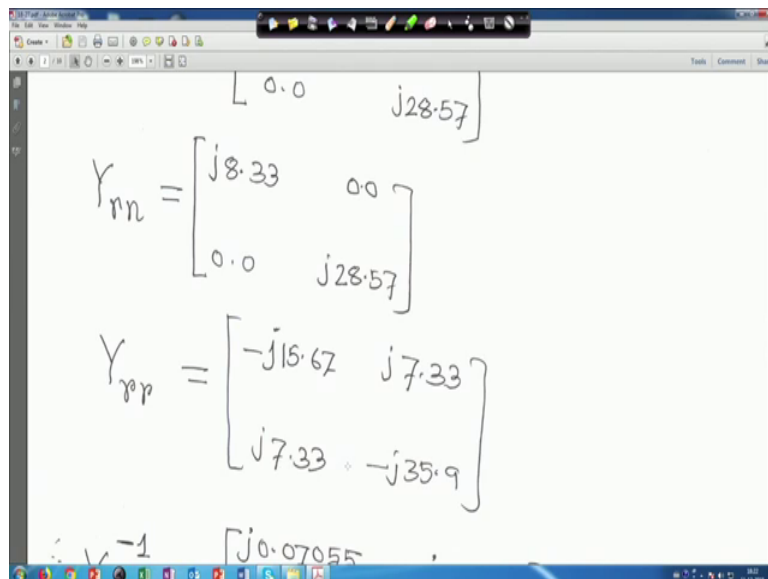

Handwritten equations on a whiteboard:

$$Y_{rn} = \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$$
$$Y_{rp} = \begin{bmatrix} -j15.67 & j7.33 \\ j7.33 & -j35.9 \end{bmatrix}$$
$$V^{-1} = \begin{bmatrix} j0.07055 \end{bmatrix}$$

And this is Y_{rr} right.

(Refer Slide Time: 17:26)

$$Y_{pp} = \begin{bmatrix} -j15.67 & j7.33 \\ j7.33 & -j35.9 \end{bmatrix}$$

$$\therefore Y_{pp}^{-1} = \begin{bmatrix} j0.07055 & j0.0144 \\ j0.0144 & j0.03079 \end{bmatrix}$$

$$Y = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & -j28.57 \end{bmatrix}$$

And if this is Y_{rr} , if you invert this matrix, if you invert this matrix then it will be like this right. So, it is a 2 into 2 matrix. You can easily invert it. You take j common and just simply you invert that one that is all, and multiplied by j again right.

(Refer Slide Time: 17:50)

$$Y = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & -j28.57 \end{bmatrix} - \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix} \begin{bmatrix} j0.07055 & j0.0144 \\ j0.0144 & j0.03079 \end{bmatrix} \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$$

So, once you have done this right, then Y is equal to this is your Y_{nn} minus i mean I mean here Y_{nn} minus Y_{nr} , then Y_{rr} inverse Y_{rn} right. So, here you here this is your what you call this is your Y_{nn} right; and this is Y_{nr} ; this is your Y_{rr} inverse and this

is Y r n right. And you multiply these three matrix. And whatever you will get, you subtract from this matrix right.

(Refer Slide Time: 18:29)

$$\therefore Y = \begin{bmatrix} -j3.435 & \underline{j3.427} \\ \underline{j3.427} & -j3.44 \end{bmatrix} \quad (20) \quad 2 \times 2$$

Now power transmitted from bus-1 to bus-2 is given by
 $P_e = |E_1| |E_2| |Y_{12}| \sin \delta$

Then you will get that your what you call that 2 into 2 matrix that is your Y is equal to minus j 3.435 then j 3.427 j 3.427 and minus j 3.444 right. That means this matrix also symmetric matrix, because Y 1 2 is equal to Y 2 1. This is your prefault that is 2 into 2 bus reduction matrix that is your reduced matrix that is your 2 into 2 now. Now, power transmitted from bus 1 to 2, bus-2.

(Refer Slide Time: 19:03)

$$\begin{bmatrix} j3.427 & -j3.44 \end{bmatrix}$$

Now power transmitted from bus-1 to bus-2 is given by
 $P_e = |E_1| |E_2| |Y_{12}| \sin \delta$

$\therefore P_e = 1.1 \times 1.0 \times 3.427 \sin \delta = 3.7697 \sin \delta$

During Fault condition

So, that is we know this equation from bus-1 to bus-2 after deduction that P_e is equal to $\text{mod } E_1 \text{ mod } E_2 Y_{12} \sin \delta$. So, E_1 , E_2 values are given in initially I told you. And Y_{12} that is your this one magnitude of this one that is your this is my Y_{12} . So, magnitude of Y_{12} is equal to 3.427 right. So, here you will substitute, then initially I told you E_1 and W_2 values are given.

(Refer Slide Time: 19:37)

The image shows a whiteboard with handwritten mathematical equations and text. The equations are:

$$P_e = |E_1| |E_2| |Y_{12}| \sin \delta$$

$$\therefore P_e = 1.1 \times 1.0 \times 3.427 \sin \delta = 3.7697 \sin \delta$$

Below the equations, the text reads:

During Fault Condition

Since there is a three phase fault on bus-3, therefore, voltage of bus-3 will be zero and hence elements corresponding to 2-3 are zero.

So, that means, during your prefault condition that P_e is equal to 1.1 into 1.0 into 3.427 sin delta. So, this is actually 3.7697 sin delta. This is your prefault condition right. Now, during fault condition, so since there is a three phase fault on bus-3 that means, if you go back to the, we will go back to the diagram. So, at there is a there is a three phase fault at this bus, at this bus, there is a three phase fault right. So, at this bus, there is a three phase fault. So, in that case what will happen, the straightforward what we will do if three phase fault has a occurred in that bus.

(Refer Slide Time: 20:24)

Corresponding to 3rd row and column will be absent.

The full matrix during fault will be

$$\begin{bmatrix} -j8.33 & 0.0 & 0.0 \\ 0.0 & -j28.57 & j28.57 \\ 0.0 & j28.57 & -j35.9 \end{bmatrix}$$

So, what we will do that here right. So, therefore, voltage of bus-3 will be 0, because three phase fault occurred at bus, hence the element corresponding to third row and third column will be absent. I mean they will be 0, that means, from this matrix from this matrix right, this matrix fault has occurred at bus-3 right, at bus-3 that means, the third row this third row and this third column it should not be there.

So, basically matrix, matrix will be reduced to that your 3 into 3, after that we will reduce that means, all these elements will be 0 during fault right. So, the I mean it will not be there all will be 0 0, and here also all will be 0 0. So, this should be removed, and this should be removed. So, this one, this one, this one will be there; this one, this one, this one will be there; and this one, this one and this one will be there. That means, matrix first will come down to 3 into 3; after that we will reduce it to 2 into 2 right.

So, because fault has occurred at bus-3, so your bus voltage three I mean voltage at bus-3 will be your 0, therefore third row and third column will be eliminated from that matrix. If you do so, if you do so, then this matrix will be 3 into 3 matrix will be during fault condition, then this is the matrix right, because that row and column third row and third column have been eliminated. So, in that case, what will happen, this is now my Y_{nn} , and this is now Y_{nr} and this is Y_{rn} and this is Y_{rr} . So, it is single element for this one right.

And we will bring it down to 2 into 2 matrix using the same relationship that is $Y_{nn} - Y_{nr} Y_{rr}^{-1} Y_{rn}$ right. So, in that case your if you do so, so Y_{nn} is equal to this much I told you, Y_{nr} will be this much, Y_{rn} will be this much and Y_{rr} is single element right. And you know this formula you know this formula. So, simply we will substitute, and you just simplify you substitute and simplify.

(Refer Slide Time: 22:37)

The whiteboard shows the following derivations:

$$Y = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & -j28.57 \end{bmatrix} - \begin{bmatrix} 0.0 \\ j28.57 \end{bmatrix} \frac{1}{(-j38.9)} \begin{bmatrix} 0.0 & j28.57 \end{bmatrix}$$

$$\therefore Y = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & -j5.83 \end{bmatrix} \quad Y_{12} = 0$$


$$P_e = |E_1| |E_2| |Y_{12}| \sin \delta = 1.1 \times 1.0 \times 0.0 \sin \delta = 0.0$$

If you do so you will get that it is your minus j 8.33, 0, this is 0, and this is minus j 5.83 right that means, my Y_{12} is actually is equal to 0. That means, during fault condition it is $P_e = |E_1| |E_2| |Y_{12}| \sin \delta$. Ultimately we are bringing it down that your what you call that matrix reduction that is number of machines right in terms of number of machines the Y bus matrix order. So, basically $|E_1| |E_2| |Y_{12}| \sin \delta$ are all magnitude, but Y_{12} is 0. So, during fault that power is 0, power delivered will be 0. This is matching with that. By chance if you this is small example by chance it does not it is only what you call two machine case right, and power you are only considering the power transform from 1 to 2. So, $|E_1| |E_2| |Y_{12}| \sin \delta$ right, so this is 0.

So, next one is that your post fault condition. We will not one thing I would like to tell that we will not show you any swing equation or these simulation thing, because this I mean this course itself is a mathematical course full of mathematics. And if I show you swing equations and that coding and other thing, then it will consume lot of time and it is


not a classroom exercise. So, whatever I have planned that things which can be solved in the classroom right.

(Refer Slide Time: 24:08)

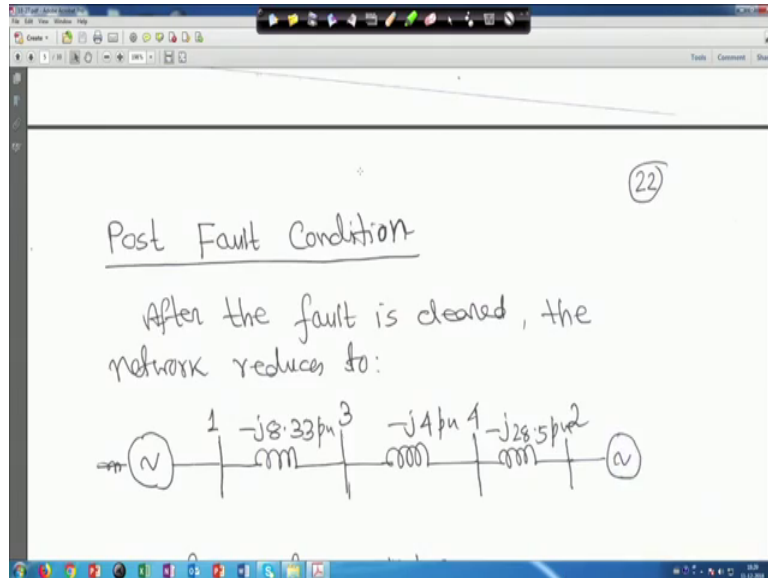

So, next one is that post fault condition. Actually during post fault condition that if you if you come back to this the condition for post fault is that just let me go to the diagram right here. For post fault conditions, when fault is clear, this line is out right. So, this line, this line and this line is there, these three lines are there right. So, this line is out when fault is cleared say. So, so in that case, in that case, just hold on let me go to that right.

(Refer Slide Time: 24:50)

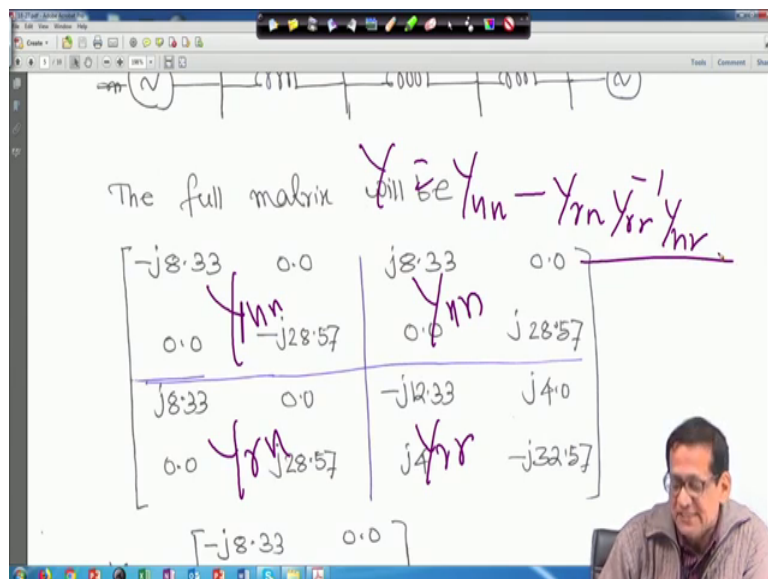

So, in that case we would simply construct, again it will be now 4 into 4 matrix right. So, you can easily construct that Y matrix 4 into 4 Y matrix. So, full matrix will be now it will be only during fault condition first row and first column are eliminated, because fault occurred at bus-3 right. So, that bus voltage three is 0. But for post fault when that line is removed right, and this is that your network diagram. And if you construct the Y matrix, it will be like this and you partition right you partition right.

So, this is your again this is 2 into 2 matrix Y_{nn} , this is your Y_{nr} , this is your Y_{rn} and this is your Y_{rr} right. So, and you use that same relationship that your Y in general Y is equal to Y_{nn} minus Y_{nr} then Y_{rr} inverse, then Y_{rn} right, you use the same relationship, then you will get, then it will be reduced to 2 into 2 matrix right.

(Refer Slide Time: 25:51)


$$\begin{bmatrix} j8.33 & 0.0 & -j2.33 & j4.0 \\ 0.0 & j28.57 & j4 & -j32.57 \end{bmatrix}$$

$$Y_{nn} = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & -j28.57 \end{bmatrix}$$

$$Y_{rr} = \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$$

So, this is Y_{nn} , this is Y_{nr} .


(Refer Slide Time: 25:54)

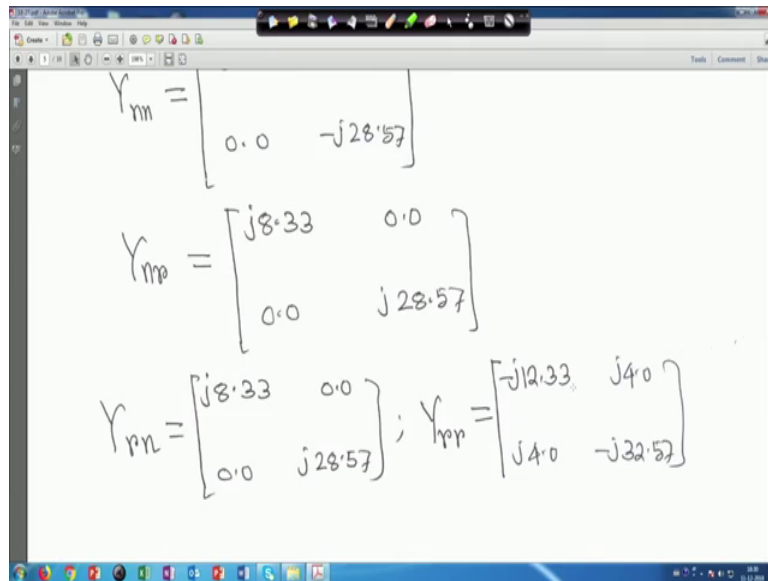

A screenshot of a whiteboard showing three handwritten matrices. The first matrix is $Y_{nn} = \begin{bmatrix} 0.0 & -j28.57 \end{bmatrix}$. The second matrix is $Y_{mp} = \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$. The third matrix is $Y_{pn} = \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$; followed by a semicolon and $Y_{pp} = \begin{bmatrix} -j12.33 & j4.0 \\ j4.0 & -j32.57 \end{bmatrix}$.

And this is Y_{rn} and this is Y_{rr} right you have to invert that Y_{rr} right.

(Refer Slide Time: 26:01)

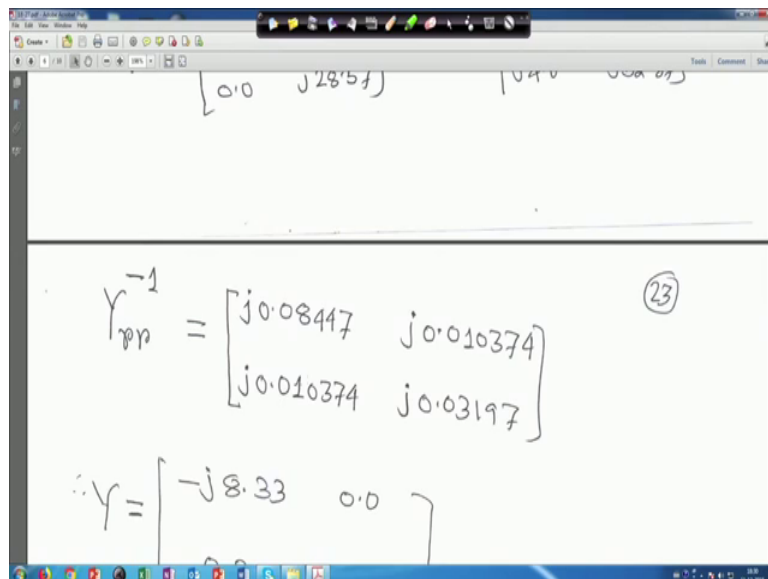

A screenshot of a whiteboard showing the inverse of the Y_{pp} matrix and the resulting Y matrix. The inverse matrix is $Y_{pp}^{-1} = \begin{bmatrix} j0.08447 & j0.010374 \\ j0.010374 & j0.03197 \end{bmatrix}$ with a circled '23' to its right. Below it, the resulting matrix is $\therefore Y = \begin{bmatrix} -j8.33 & 0.0 \end{bmatrix}$.

If you do so, so Y_{rr} inverse will be this much right, I mean this is my Y_{rr} and it is invert 2 into 2 matrix simply you can invert it right.

(Refer Slide Time: 26:11)

Handwritten mathematical derivation on a whiteboard:

$$[j0.010374 \quad j0.03197]$$

$$\therefore Y = \begin{bmatrix} -j8.33 & 0.0 \\ 0.0 & Y_{nn} \\ & j28.57 \end{bmatrix}$$

$$- \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix} \begin{bmatrix} j0.08447 & j0.010374 \\ j0.010374 & j0.03197 \end{bmatrix} \begin{bmatrix} j8.33 & 0.0 \\ 0.0 & j28.57 \end{bmatrix}$$

Labels in purple ink: Y_{nr} , Y_{rn} , Y_{nn} .

$$\therefore X_r \quad Y = ?$$

And then this is your Y this is your Y n n, this is this is your that Y n n that 2 into 2 matrix right. This is Y n r, this is your Y r r inverse and this is your Y r n right. And you multiply all and simplify.

(Refer Slide Time: 26:32)

Handwritten mathematical derivation on a whiteboard:

$$\therefore X_r \quad Y = ?$$

$$|Y_{12}| = 2.4679$$

$$\therefore P_e = |E_1||E_2||Y_{12}| \sin \delta$$

$$\therefore P_e = 1.1 \times 1.0 \times 2.4679 \sin \delta$$

$$\therefore P_e = 2.7147 \sin \delta$$

So, here this one your what you call I did not this is this is an exercise for you. I did not compute or I did not give the answer right, answer you will do it. Only thing is that Y 1 2 is equal to Y 2 1. So, Y 1 2 that I have written here that I have written here but you please find out what is Y 1 1 is equal to how much, and Y 2 2 is equal to how much you

multiply and subtract that from Y_{nn} right. And in this case P_e will be $E_1 E_2 Y_{12} \sin \delta$, this way when you compute you will get $Y_{12} 2.4679$ right. So, that means, my P_e will be that $E_1 1.1 E_2$ one point 2.1 thing I have list here, it is into $\sin \delta$ right. And P_e is equal to 2.71 power transferred that from 1 to 27147 $\sin \delta$ right.

So, thank you very much. We will be back again.