

Electrical Measurement And Electronic Instruments
Prof. Avishek Chatterjee
Department of Electrical Engineering
Indian Institute of Technology, Kharagpur

Lecture - 36
Co-ordinate potentiometer

Welcome, we are studying potentiometers AC potentiometers particularly and the important issue about AC potentiometer is that, the phase angle of the unknown source matters ok. So, we have seen, how to take care of these phase angle using a polar potentiometer and we are going to see another type of potentiometer, which is coordinate potentiometer with which we can again measure unknown AC voltages with arbitrary phase angle.

(Refer Slide Time: 01:23)

Coordinate Potentiometer

An AC voltage can be represented as a complex phasor

Complex number $\begin{cases} a+ib \equiv \text{Coordinate potentiometer} \\ r \angle \theta \equiv \text{Polar potentiometer} \end{cases}$

I_1 I_2

Before we come to this let me motivate you by saying that an AC voltage can be represented as a complex phasor that you know, a complex number. Now, a complex number can be represented in two forms, one is

$A+iB$ and $r \text{ angle } \theta$


So, we can represent a complex number in two forms. The polar potentiometer measures the unknown voltage in this form magnitude and phase angle. The phase angle is read from the dial of the phase shifter and the magnitude from the length at which the null point is

obtained. So, this is the motivation or this representation is the motivation behind polar potentiometer because this is also called polar form of polar representation of a complex number and this is this is the motivation of today's topic coordinate potentiometer.

So, today the potentiometer that we will see, we will measure the unknown voltage in this form a plus i b. So, basically we need two potentiometers; one to measure the real part of a complex voltage another to measure the imaginary part so to say. So, we need two potentiometers. So, let me draw them like this, this is one potentiometer wire and this is another potentiometer wire. Now, the way we will do it is this. So, we will supply two I mean we will apply two voltages of course, two AC voltages in a one here another here in a way so that these two currents say this current and this current call it I_1 and I_2 they are at 90 degree phase angle.

So, I mean this is not what I am drawing now is not the complete picture, but just to motivate you for now. Let me have just two voltage sources such that the two currents are 90 degree out of phase. So, we have to somehow.

(Refer Slide Time: 05:55)

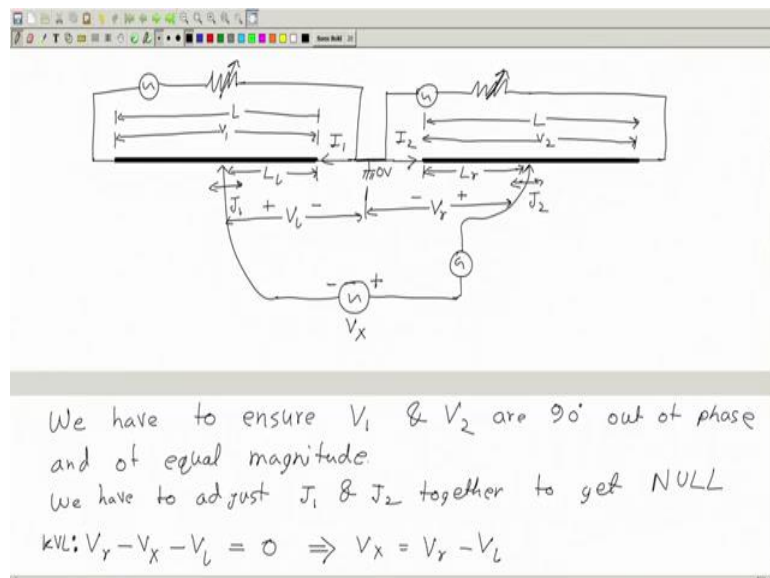

So, somehow, we have to ensure I_1 and I_2 are 90 degree out of phase and of equal magnitude. So, then it will actually mean that. So, this two are identical potentiometer wires.

So, the length of this and the length of this maybe are same. they are full their resistance per unit length may be same. So, if we can adjust I_1 and I_2 to have 90 degree phase angle then we can ensure that the voltage drop in this wire and this wire they are also 90 degree out of phase and the voltage drop per unit length will also be same. So, this will actually ensure ok, let me write it directly. So, we have to ensure that voltage call this voltage V_1 and this V_2 , lengths are same the potentiometers have same length.

So, let us ensure that V_1 and V_2 are 90 degree out of phase and with equal magnitude, for that basically you have to adjust this I_1 and I_2 somehow you have to adjust this here and here to make I_1 and I_2 such that V_1 and V_2 , 90 degree out of phase and of equal magnitude. Now, let me have the unknown source. So, the unknown source is here V_x , x means unknown and what we will do is we will connect two jockey like this one it through a galvanometer, one here another here and let me short these two terminals.

So, these two terminals are shorted, you can take this point as the reference for calculation; this is the reference point. So, now we have to adjust this and this during the measurement to get a null in this galvanometer. So, during measurement, we have to adjust both call this J_1 jockey one and J_2 we have to adjust J_1 and J_2 together to get null here in this galvanometer so; that means, no current should flow through this. When is that possible? That is possible only if this in this circuit, the voltage total voltage is 0.

Now, if this let me call this voltage from here to here, from this reference point up to this side call this V_1 and call this voltage as V_r then what can we say and the reference direction so this is 0 side. So, V_r is measured like this, V_1 is measured like this, V_1 is measured with respect to this point, V_r is also measured with respect to this point. So, then we can say and V_x let me take the reference of V_x like this for example.

So, then we can write applying KVL starting from here. So, we have V_r so this is

KVL: $V_r - V_x - V_L = 0$, right. V_r rise, V_x drop, V_L drop. So, So, then this implies

$$V_x = V_r - V_L = \frac{V_2}{L} Lr - \frac{V_1}{L} L_L = i \frac{V_2}{L} Lr - \frac{V_1}{L} L_L$$

Now, what is V_L ? V_1 will be. So, if this length is capital L here also it is capital L and this length from. So, here to so, here to here.

This length, call it L_1 for left and here length right left and right potentiometer.

(Refer Slide Time: 12:31)

We have to ensure V_1 & V_2 are 90° out of phase and of equal magnitude $\Rightarrow V_2 = \pm iV$ (\pm sign to be decided)
We have to adjust J_1 & J_2 together to get NULL

KVL: $V_r - V_x - V_L = 0 \Rightarrow V_x = V_r - V_L = \frac{V_2}{L} L_r - \frac{V_1}{L} L_c$
 $V_x = j\frac{V_2}{L} L_r - \frac{V_1}{L} L_c$

How to obtain/ensure that $\|V_1\| = \|V_2\|$
angle between V_1 & $V_2 = 90^\circ$?


$J = \sqrt{-1}$

$$V_2 = \pm iV$$

So, you must understand this much before we proceed further and talk about more details like how to get these two currents these two voltages 90 degree out of phase, how to ensure that yes, they are exactly 90 degree out of phase, their magnitudes are same.

So, we will talk about this, but before that you may take a pause and make sure that you have understood up to this. If you have understood then let us proceed and ask, how to ensure or how to obtain or ensure that magnitude of V_1 is same as the magnitude of V_2 and the angle between V_1 and V_2 is 90 degree. So, this is the question of. So, what we will do is this.

(Refer Slide Time: 16:29)

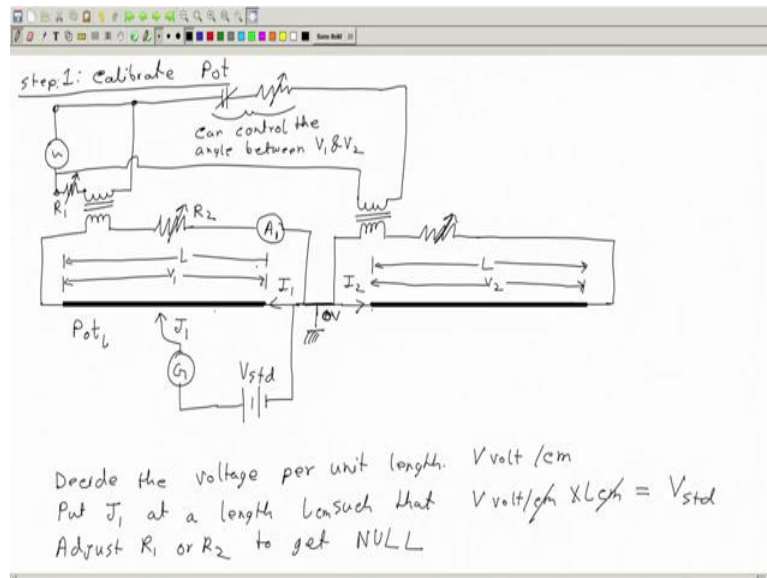

Just like we did it for the polar potentiometer, we will take a source and supply this side and this side with one side through a capacitor, resistor something to change the phase angle of the respective current between the respective currents. So, what we will do is this, let me first put say a transformer here.

So, this is a transformer and let me supply this transformer like this. If you want to control the current or the voltage of this and we finally, we have to control this voltage the magnitude of this voltage. So, we may need to put some resistance, you can put it here, you can also put it in the secondary side. So, by controlling this resistance also you can control this current and thereby this voltage; you can have a resistance here as well.

So, in principle both are ok and here this side we will again let me take a transformer, but let me feed this through variable capacitor, resistor or some sort of impedance with which you can control the phase angle of this current and thereby the phase angle of the secondary voltage there by this current and so this voltage.

Now, so this is this can control the magnitude and phase angle between the V_1 and V_2 can control the angle between V_1 and V_2 . So, you have to adjust this until and unless you get these two voltages V_1 and V_2 at 90 degree out of phase and same magnitude. So, this is the control how you can control, how you can change the angle, but the next question is more important question, how do we know that we are at the desired condition that we

have obtained correct phase angle and correct magnitude? How do we test that? So, for that; so, the way we will do it like this.

So, let me tell you the entire procedure how to use it starting from the calibration. So, let me tell you the entire procedure in detail. So, first step is to calibrate steps. So, step 1, calibrate this potentiometer call this Pot L, Pot L left potentiometer calibrate Pot L, how? So, for that we need a standard cell DC standard cell. So, what we will do. So, let me make several copies of this.


So, step 1 is calibration of potentiometer 1 for that let me. So, we do not need this unknown source right now. So, let me erase this unknown source. So, what we have to do? We have to connect the standard cell if we are taking this as the reference point.

So, let us connect this standard cell like this through a galvanometer and so, first decide the suitable length where you want to get the null. So, that is decided by the choice of voltage per unit length that you that and that in turn depends on the magnitude of the unknown voltage, you should have an idea of the magnitude of the unknown voltage. So, you decide. So, decide the voltage per unit length, accordingly put the jockey call this J 1 then put jockey J 1 at a length. So, from left, this is now from the right side ok. So, put jockey at a length call it l such that.

$$V_{\text{volt/cm}} \times L_{\text{cm}} = V_{\text{std}}$$


then adjust say this resistance or this resistance call this one R 1, R 2 adjust R 1 or R 2 or both to get null ok; that means, the potentiometer 1 or potentiometer 1 is calibrated calibration is over, but of course, we need to record the value of this ammeter here.

(Refer Slide Time: 26:11)

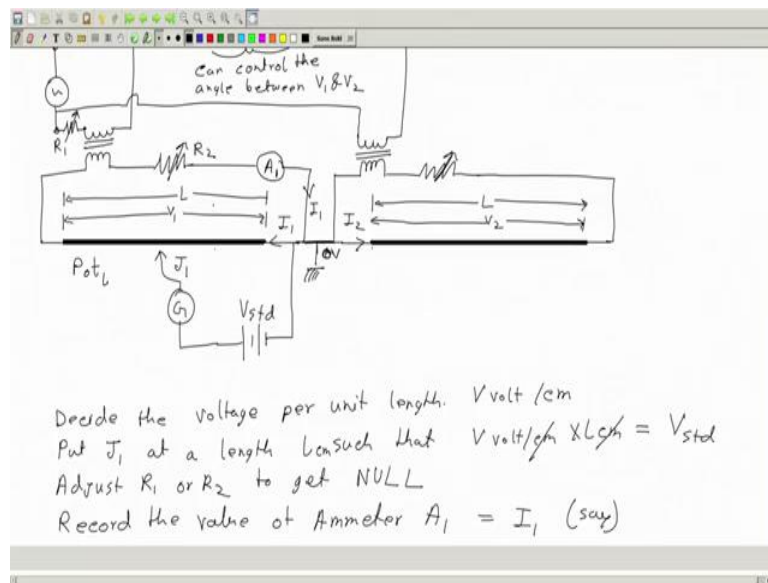

So, record the value of ammeter A1 say this is equal to I 1. So, note this value and then the calibration of potentiometer1 is done.

(Refer Slide Time: 26:43)

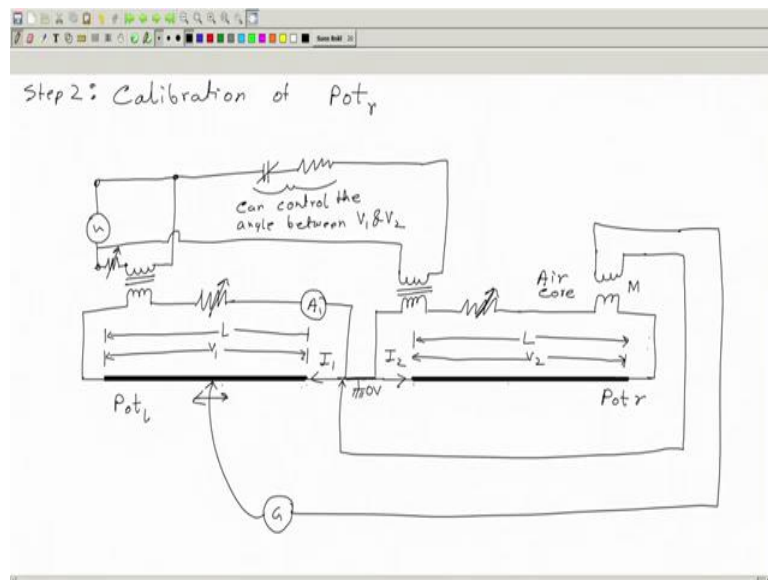


Now next step is calibration of potentiometer2. We call it Pot r. So, this is Pot r right Pot 1, Pot r. Now, for that what we will do and then we have this ammeter A1 of course, and here we will put a new equipment, what is that? That is going to be air core transformer, important that this should be air core. So, I am not drawing any core. So, this is air core transformer and so, if any current is flowing here then we will have some voltage induced

in the secondary, this voltage we will bring and connect one side here, another side through the galvanometer we will connect it here.

This is movable ok. Now, we need to know the mutual inductance of this transformer or; that means, between these (Refer Time: 29:14).

(Refer Slide Time: 29:35)

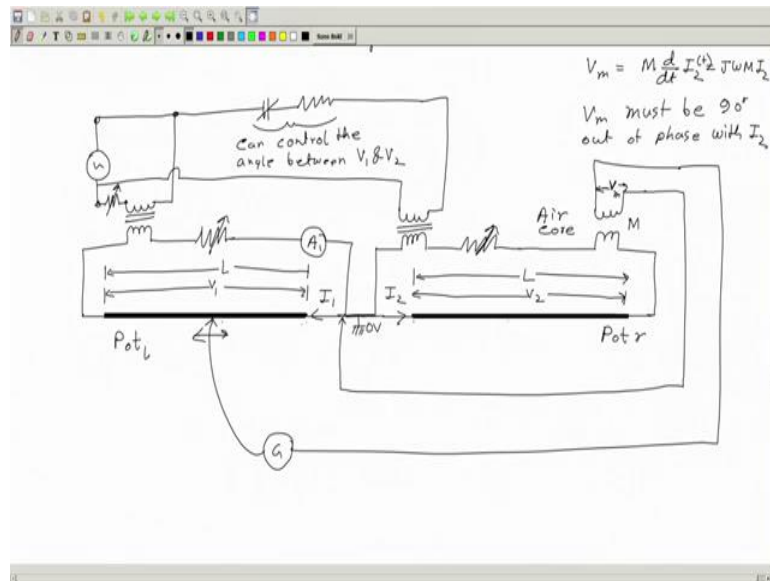


And now observe that this voltage in the secondary, call this V_m . This voltage in the secondary is at 90 degree with the current which is flowing here or here I_2 . V_m must be 90 degree out of phase with I_2 , why? Because, what is V_m ?

$$V_m = M \times \frac{dI_2}{dt} = j\omega M I_2$$

So, V_m is 90 degree out of phase from this current.

(Refer Slide Time: 31:03)

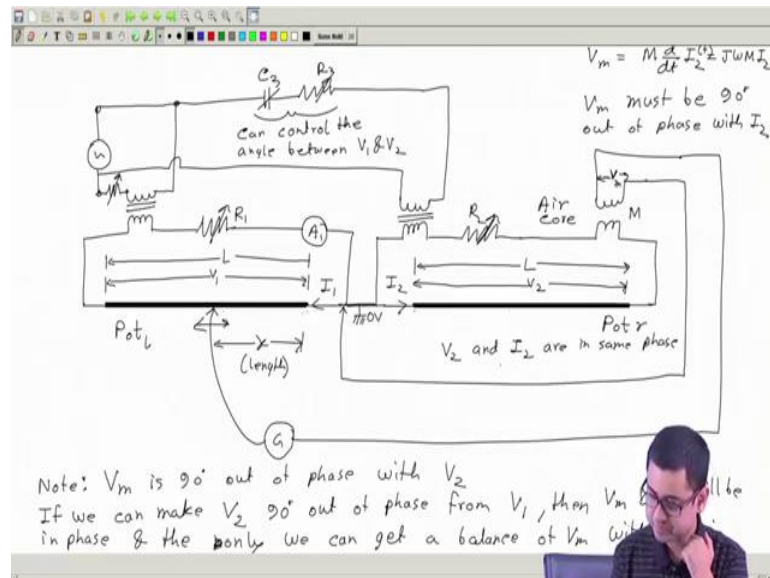

Now, this voltage V_2 , V_2 is in phase with I_2 . V_2 and I_2 are in same phase, why? Because this wire is resistive since the circuit is resistive. So, V_2 is nothing but I_2 multiplied by some resistance. So, V_2 and I_2 are in same phase and V_m and I_2 are 90 degree out of phase. Now, these two facts together, what does it imply? V_m and V_2 they will be 90 degree out of phase.


So, this fact that V_m is 90 degree out of phase from I_2 , but I_2 is in same phase with V_2 this implies that V_m is 90 degree out of phase with V_2 . Now, if we can make V_2 90 degree out of phase from V_1 , if we can make V_2 90 degree out of phase from V_1 then V_m and V_1 will be in same phase same or 180 degree out of phase.

So, will be in phase ok. Because, if we can make V_2 90 degree from V_1 , V_2 is 90 degree from V_1 and V_m is 90 degree from V_2 ; that means, V_1 and V_m will be either in 0 degree or 180 degree and then only we can get a balance here by moving this jokey. So, here actually we are bringing this V_m to potentiometer1 and measuring this V_m using potentiometer1 or potentiometer 1 and we can get a balance or null only if we can make V_2 90 degree out of phase of V_m . And then only we can get a balance of V_m with potentiometer L.

So, if we do not get any balance, if we fail to get any balance for any position of this jokey; that means, V_m is that means, V_m is not in phase with V_1 which in turn will mean V_2

is not at 90 degree with V 1 and then we have to adjust these things this capacitance, this resistance so that V 2 is 90 degree out of phase from V 1.

(Refer Slide Time: 35:19)

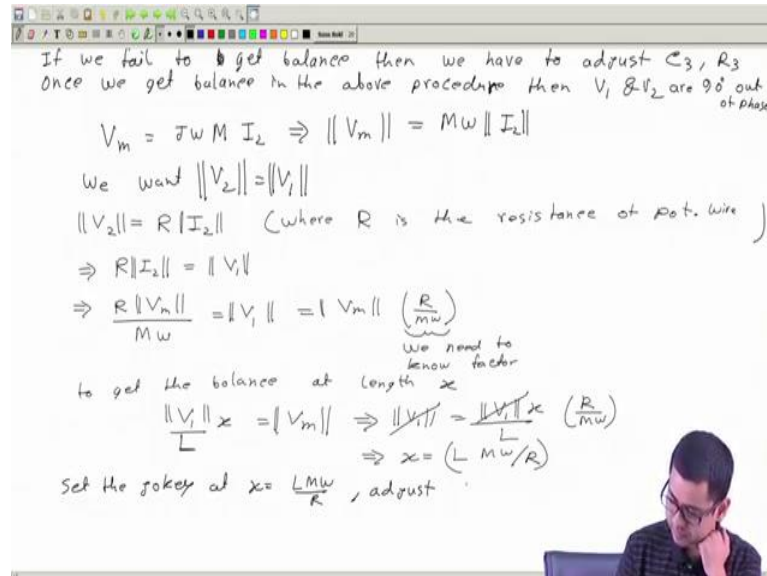

So, let me write. So, if we fail to get balance then we have to adjust this capacitor call that C 3 R 3, C 3 and R 3 and once we adjust it so that we get a balance, that ensures V 2 and V 1 are 90 degree out of phase.

Once we get balance above in the above procedure then V 1 and V 2 are 90 degree out of phase as desired ok. And also, also if we know the value of M if we know the; so, if we know the value of M then from V m we can estimate this current I 2. If we know the value of V m then we can estimate the value of this current I2 from V m and then from that we can estimate the value of V 2, if we know the resistance of this wire ok. So, now say if this is M then from the value of V m, how can we get the value of I 2?

I 2 is so let us write

$$V_m = j \omega M I_2$$

$$\|V_m\| = \omega M \|I_2\|$$

$$\|V_2\| = R \|I_2\|$$

$$R \|I_2\| = \|V_1\|$$

$$\frac{R||V_m||}{M\omega} = ||V_1||$$

So, if we know this factor; so, we need to know this factor or maybe the potentiometer manufacturer or the seller will give us this factor for a particular value of omega. Then, we know that for which length here; so, for what value of this length call this l what call this x; I might have used l many a times, call this x this length.

So, what will be the value of this x? So, we can write that; so, this since we are getting V m, V m here and we want to get a balance.

(Refer Slide Time: 42:19)

$$||V_2|| = R ||I_2||$$
 (where R is the resistance of pot. wire)

$$\Rightarrow R ||I_2|| = ||V_1||$$

$$\Rightarrow \frac{R ||V_m||}{M\omega} = ||V_1|| = ||V_m|| \left(\frac{R}{M\omega} \right)$$

We need to know factor

to get the balance at length x

$$\frac{||V_1||}{L} x = ||V_m|| \Rightarrow ||V_1|| = \frac{||V_m||}{L} x \left(\frac{R}{M\omega} \right)$$

$$\Rightarrow x = \left(L \frac{M\omega}{R} \right)$$

A diagram of a potentiometer circuit is shown at the bottom, consisting of a long wire with a sliding contact (jockey) and a galvanometer connected to it.

$$\frac{||V_1||}{L} x = ||V_m||$$

$$||V_1|| = \frac{||V_1||}{L} x \left(\frac{R}{M\omega} \right)$$

$$X = L \frac{M\omega}{R}$$

So, what we have to do is; we have to put the jockey at this particular length x and adjust these values these two values or you can also adjust this resistance to control the total current ok, call this R 1 R 2. So, x is obtained like this. Now; so, what we have to do is; set the jockey at $X = L \frac{M\omega}{R}$

ok, this factor $M \omega$ by R should be known. So, set the jokey there and adjust, what we can adjust? We can adjust C_3 , R_3 , R_2 .


(Refer Slide Time: 45:05)

$$V_m = \omega M I_2 \Rightarrow \|V_m\| = M \omega \|I_2\|$$
 We want $\|V_2\| = \|V_1\|$
 $\|V_2\| = R \|I_2\|$ (where R is the resistance of pot. wire)
 $\Rightarrow R \|I_2\| = \|V_1\|$
 $\Rightarrow \frac{R \|V_m\|}{M \omega} = \|V_1\| = \|V_m\| \left(\frac{R}{M \omega} \right)$
 to get the balance at length x We need to know factor
 $\frac{\|V_1\| x}{L} = \|V_m\| \Rightarrow \|V_1\| = \frac{\|V_m\| x}{L} \left(\frac{R}{M \omega} \right)$
 $\Rightarrow x = \left(L \frac{M \omega}{R} \right)$
 Set the jokey at $x = \frac{L M \omega}{R}$, adjust C_3, R_3, R_2 to get balance
 (Do not move the jokey, Do not change I_1)

Adjust C_3 , R_3 , R_2 to get balance. Do not move the jokey at this point, do not change anything in the first potentiometer, do not change R_1 or this resistance. Do not change anything or in one words do not change this current I_1 which is fixed in the first step. Do not change I_1 , this is most important.


Once we get the balance, the calibration of the second potentiometer is over; that means we have made sure the voltage V_2 is in same phase out of phase from V_1 and same magnitude like V_1 . So, this is step 2, over.

(Refer Slide Time: 46:22)

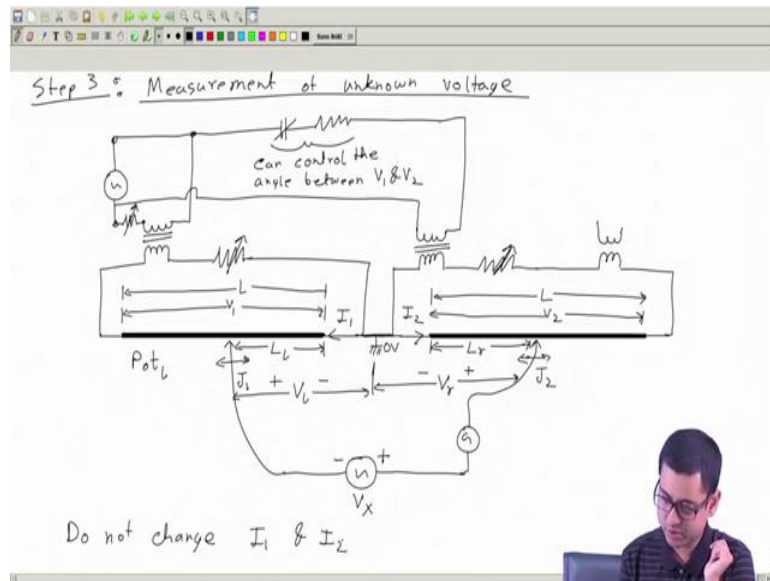

Now, final step step 3. This is the measurement of unknown voltage. So, in this phase we will still have this of course, this is always there. Here also we will have this, although we are not using it. So, you can keep it open. Here also you are not going to in this measurement phase, we are not going to use it you can keep it open, but and now we will connect the V_x and we will have two jokeys.

(Refer Slide Time: 47:41)

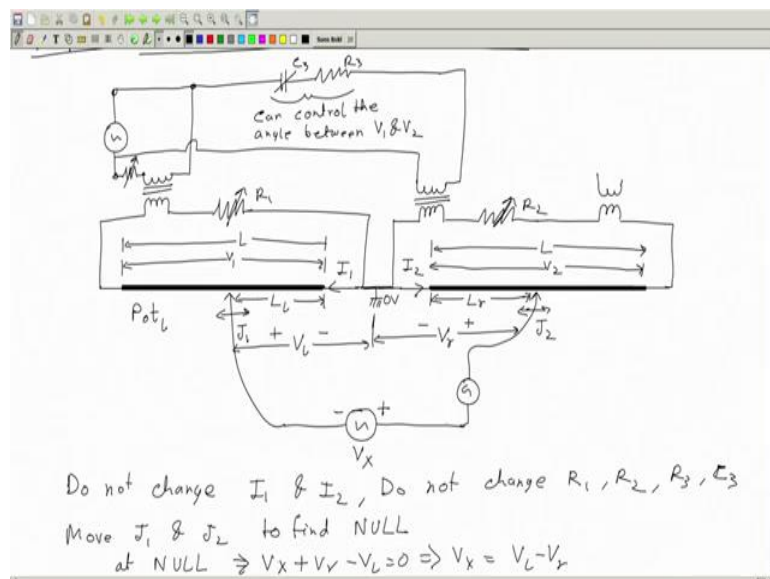

So, do not change I_1 and I_2 ; that means do not change anything. So, this is R_1 , this is R_2 , C_3 , R_3 ok. So, do not change any of these; R_1 , R_2 , R_3 or C_3 do not change any of

these. Move the position of J 1 and J 2 to find null and once we have the null then we can write that. So, at null, we can write that V_x is equal to V_x is how much this is. So, we can write once again the KVL; $V_x + V_r - V_L = 0$,

$$V_x = V_L - V_r$$

So, that is the process that is the total entire process. So, maybe I recap a bit V_1 from here sorry V_x from here is this. So, let me write j to be consistent j means root over minus 1. So, now you can put this value here for V_1 and V_r . So, you will get V_x and we are done.

So, let me just conclude this video by summarizing it in brief. So, what we have to do is first decide the per unit length voltage that we want to have then we have to set the standard, connect the standard cell to the potentiometer keeping in mind the chosen value of voltage per unit length, find the null that is calibration of potentiometer 1.

Then using the air core transformer, we have to calibrate the second potentiometer. Once again, we have to first decide at which point the null should be obtained, put the jockey at that position, adjust the capacitance and resistors to change the phase angle and magnitude of the second potentiometer, once we get the null we are done. Phase 3 last phase, connect the unknown voltage across the two potentiometers together, adjust the two jockeys, do not change anything that can change the current in either potentiometer 1 or potentiometer 2. Change only the two jockeys, find the null and from the lengths get the voltage.

So, one small but important thing which I forgot to mention before is why we use air core transformer here? Why not iron core transformer? Ok. This is because in case of iron core transformer, the flux is not exactly in the same phase with the primary current, there is a small delay which we call the hysteresis lag due to which the flux generated by this primary coil which is this I_2 and the; so, I_2 and flux they will have a small lag between them.

Therefore, this volt secondary voltage V_m will also not will not be exactly at 90 degree from the current I_2 ok, but in case of air core there is no hysteresis lag and that is why, this transformer must be air core that is important. Another small thing you observe that the, that the voltage induced in the secondary is the voltage here is V_m and at the null condition when there is no current in the secondary circuit then there is no voltage drop also in the secondary.

So, therefore, the voltage that we are getting here is strictly V_m , there is no voltage drop at all in the secondary this is also a nice thing; nice and obvious thing. So, the voltage that we are measuring that or that is coming here is exactly 90 degree out of phase from the from the; this current I_2 . So, this is also important. So, since we are dealing with the subject of measurement where accuracy is very crucial important, these minute things must be remembered that we should not use a iron core transformer here.

Thank you.