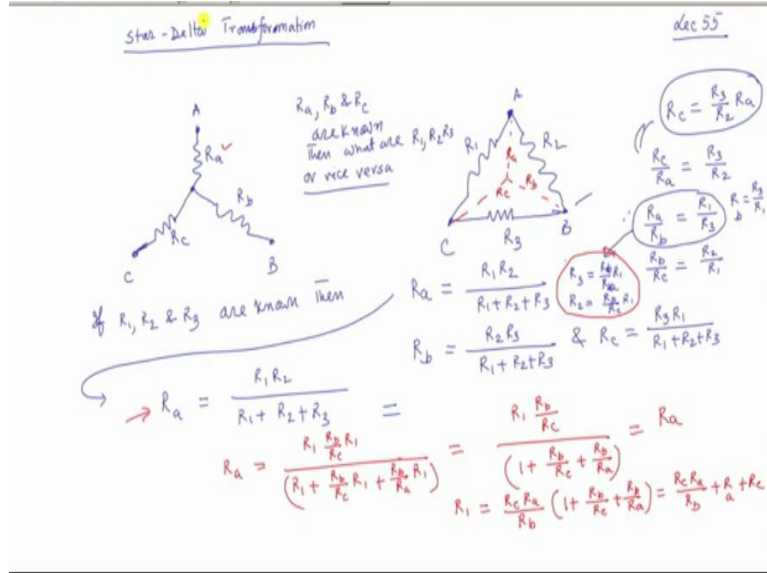


Network Analysis
Prof. Tapas Kumar Bhattacharya
Department of Electrical Engineering
Indian Institute of Technology – Kharagpur

Lecture 55
Star-Delta and Delta-Star Transformation

(Refer Slide Time: 00:19)



So let us start with star-delta formation in lecture 55 and this is the thing we have done for star delta transformation, that is if you know, this R_1, R_2, R_3 in delta fashion at A, B and C, then you can replace R_1, R_2, R_3 by some star connected loads R_a, R_b, R_c and these R_a, R_b, R_c if you know the values of R_1, R_2, R_3 , then R_a, R_b , and R_c can be found out, okay. Also, now I want to find out the reverse formula that is if R_a, R_b, R_c are known, then what should be R_1, R_2 and R_3 .

So to find this out, what we do here is this one. That is in lecture 55, you see if you take this ratio, R_a by R_b which are the 3 values is known, it comes to that. Now what we will be doing is we will express R_2 and R_1 . Let me write these ratios very clearly that is we have got these ratio, R_c is equal to R_3 by R_2 into R_a , therefore and another important ratio is this one. Therefore, for example, from these, I express R_3 in terms of R_a by R_b into R_1 , I can write it like this.


Similarly, I would express R_2 in terms of R_1 , R_2 by R_1 is this. So it will be R_B by R_C into R_1 , R_3 is equal to R_B by R_A , thank you, R_B by R_A . So these 2, I have expressed R_3 and R_2 in terms of R_1 , then I go to say, this equation which has already been established and I will say that R_A is equal to from this; R_1 into R_2 , so R_1 , I will express everything in terms of R_1 here, R_2 and R_3 in terms of R_1 .

So that on the right hand side only R_1 and R_A , R_B , R_C will be there. So I will be able to express R_1 in terms of R_A , R_B , R_C . So R_1 and for R_2 , I will write R_B by R_C into R_1 , this I will write, divided by this is R_1 is there plus for R_2 , I will write R_B by R_C into R_1 plus R_3 , but for R_3 , I will write R_B by R_A into R_1 , like this, this I can write, then you see that there are R_1 square on the top and one R_1 will come out.

So this will be equal to; if I clean this up, so this will be equal to R_1 into R_B by R_C , one R_1 will go and it will be 1 plus R_B by R_C plus R_B by R_A . This will be the thing and that I am telling it is equal to R_A . Therefore, if I take all these things to the right hand side, keeping R_1 on the left hand side, I will get R_1 is equal to R_C into R_A by R_B and whole into 1 plus R_B by R_C plus R_B by R_A , that is over.

But you push it this inside, then what you will be getting? You will be getting R_C R_A first term by R_B plus 1 plus, this R_B and R_C will cancel out, you will get R_A here and the third term will be R_B and R_A will cancel out plus R_C and you are done. So R_1 , the value of R_1 will be equal to R_A plus R_C plus product of these 2 divided by the third one.

(Refer Slide Time: 06:29)

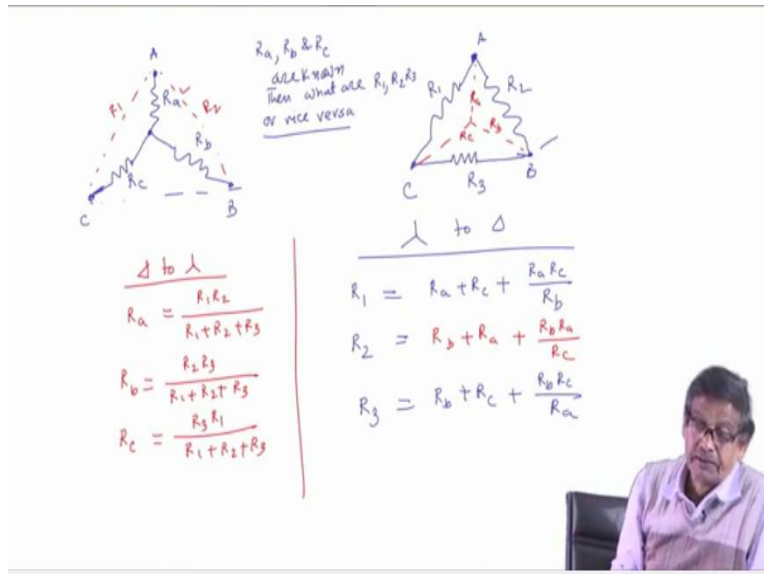


Therefore, it is still there. So finally, this is the thing. Therefore, if the equivalence between these 2 circuits we have already seen for delta to star transformation, delta to star, first we derived that is these that R_A is equal to $R_1 R_2$ divided by R_1 plus R_2 plus R_3 . R_B was equal to R_B is this resistance, $R_2 R_3$ divided by R_1 plus R_2 plus R_3 . They could be also impedances, do not worry, R_C equal to $R_3 R_1$ divided by R_1 plus R_2 plus R_3 .

So if the delta values of resistances are given, equivalence star can be made at those 3 points A, B, C and for star to delta transformation, that is you know the value of R_A , R_B , R_C , then what should be this R_1 ? This is here the R_1 should come, so it is easy to remember. R_1 will be equal to the sum of the adjacent resistance that is R_A plus R_C plus $R_A R_C$ divided by R_B , product of these 2 divided by the third one.

Similarly, for this I have done and similarly, for the other I will be, in the similar way, I will be able to do that. R_2 that is this resistance, that is R_2 will be how much? R_A plus R_B adjacent resistances sum of them, R_B plus R_A divided by $R_B R_A$ by R_C and finally, R_3 will be, R_3 is this one, so it will be R_B plus R_C plus $R_B R_C$ by R_A . So when it will be necessary? For example, if you have a circuit like this.

(Refer Slide Time: 09:37)

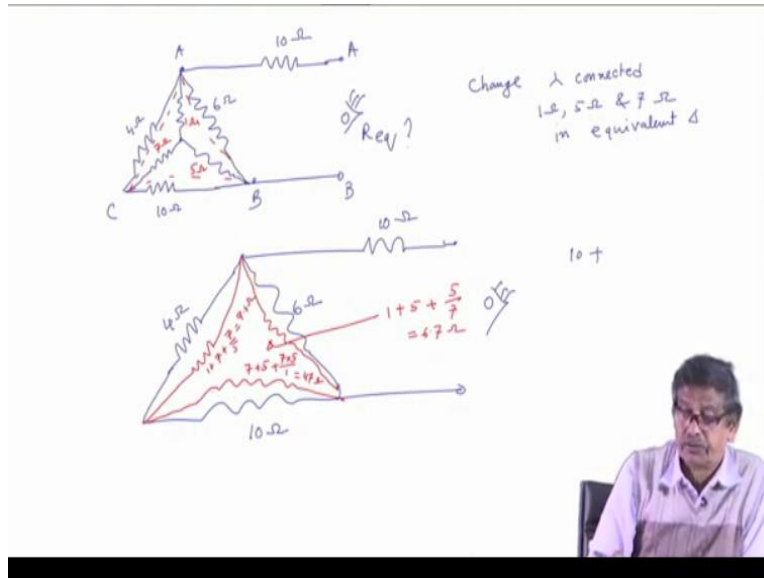

Suppose, I say that you have 3 resistances. Now I am coming to a problem, what I am asking to tell you and there are 3 resistances connected, just a simple example. Suppose, these values are known; 4 ohm, 6 ohm, 10 ohm, this is how 6 resistances are connected and this is a 1 ohm, 5 ohm and 7 ohm, it is there. Now, you have a circuit like this. Another resistance is a 10 ohm.

Suppose, I ask you what is the equivalent impedance looking from the points A and B which you are supposed to do after replacing the sources in any network to find out R Thevenin's or z Thevenin's. Now, here the knowledge of simple series-parallel equivalent resistance formula will not work because the resistance value RAB be will be 10 plus the equivalent resistance of this network between these 2 points and that is very difficult to find out.

Because I do not know this 1 ohm, whether it is in series with 6 ohm or in parallel, no, I am not sure, similarly 4 ohm, then what I will be doing is this, I will be changing, these 3 points are fixed, this is A, this is B, this is C. Question is what is R equivalent? So what I will do? I will replace this delta connected resistances, 4 ohm, 6 ohm and 10 ohm in points A, B and C by an equivalent star I can do or I can change this star to equivalent delta.

So change star connected 1 ohm, 5 ohm and 7 ohm in equivalent delta. So how it will look like? So there were this 4 ohm, 6 ohm and this 10 ohm is there, this I am not disturbing, 10 ohm is there. Here was some additional resistances, 10 ohm connected here. So let this remain, 4 ohm, 6

ohm and 10 ohm. Now this 1, 7, this I will replace it by the equivalent delta here. Another resistance will come there, another resistance will come there, another resistance will come there.

And then I will replace, forget about this star connected 1 ohm, 7 ohm and 5 ohm, so what will be this additional resistance across ABC? There will be this resistance and what will be the value of this? It will be 1 plus 7 star to delta; 1 plus 7 plus 7 by 5, is it not? RA this plus this, plus this into this, divided by the third one, 5 ohm, how much it is? Some value will come, is it coming 9.4, so let us put it. Similarly, this I will replace by a resistance here.

What will be this value? It will be 7 plus 5, let me write 7 plus 5 plus 7 into 5 divided by 1, 47, whatever it is and finally here there will be another resistance connected between these 2 points and this resistance value will be this one. If I write it here, it will be 1 plus 5, so much ohm, 1 ohm plus 5 ohm plus 5 by 7, 6.7 ohm or so. Now I will not carry on with this calculation, I just told you this is this portion.

Then I have been asked to calculate the equivalent resistance of these, then you see this 6 ohm and this red resistance are in parallel, formula can be applied. These 2 are in parallel. I can easily calculate, these 2 are in parallel. Then this and this will be in series and this equivalent resistance can be easily calculated, which will be 10 plus this equivalent resistance between these 2 points.

It is just to tell you that in some situations, when we cannot make out whether the resistances or impedances are really in series or in parallel the star delta transformations or delta star transformation are very useful. That is how it has been pointed out. I hope you have understood it. See problems to find out equivalent impedance, when the resistances are connected in an awkward fashion. Today now, what I am planning to do is to start another interesting theorem and that is called the Tellegen's theorem okay.

(Refer Slide Time: 16:27)

Tellegen's Theorem :-

delivered: $v_1 i_1$

Absorbed:

$$v_2 i_2 + v_4 i_4 + v_5 i_5 + v_6 i_6 + v_7 i_7$$

or $v_1 (-i_1) + v_2 i_2 + v_4 i_4 + v_5 i_5 + v_6 i_6 + v_7 i_7 = 0$

Power absorbed by v_1

Based Power delivered by each element

$$v_1 i_1 + v_2 (-i_2) + v_4 (-i_4) + v_5 (-i_5) + v_6 (-i_6) + v_7 (-i_7) = 0$$

-08:08

So let us start that, at least the idea, Tellegen's theorem. Tellegen's theorem is a very interesting theorem. It is only applicable, but before we start really Tellegen's theorem, you please try to recall that in any network, there may be sources, there may be several impedances connected like this. Suppose, you have a network like this, then in this network, there will be several elements connected and you can have another elements connected here in between these two.

Suppose, you are considering this network, these elements is could be also source, this is another element, another source here but whatever it is, in this network suppose, I say the voltage across each element, I will call it some value say, v_1 , voltage across this element v_2 , understood, this is suppose, v_3 what not, v_3 and so on and v_4 , v_5 , v_6 and v_7 and also arbitrarily, if I assume the currents; i_1 , i_2 , i_3 , and say, i_4 , say i_6 , i_7 , i_5 , this way I have done it.

This of course, you must understand in this diagram, this i_3 and i_1 are same. So let us consider only one element in this branch, they can be combined. So there is nothing like this one, but what I am trying to tell, given a network I will be able to calculate the voltage across each element. That element could be an impedance as well as an source and also I am able to calculate the voltage across each element.

Now in a network if you calculate the product of voltage and current and sum them up for all the elements, it will come out to be 0, okay. That is precisely whatever I am trying to tell. For

example, I say that what is the power delivered by this element? This will be $v_1 i_1$, this element, after I have assumed, so delivered, I was writing like that delivered and here I will write absorbed and once you have assigned the voltage polarities and the current, do not play with that.

So this is the it is delivering power, what about element doing? Element 2 is absorbing power, because current is entering through plus, so it will be $v_2 i_2$, element 2; it is absorbing power. Element 3 of course nothing, element 3, here it is element 4, it is also absorbing power, $v_4 i_4$ and element 5 is also absorbing power, so power absorbed is given by the $v_5 i_5$ and element 6 is also absorbing power, $v_6 i_6$, element 7 also absorbing power, $v_7 i_7$, is it not.

So how many elements are there? 1, 2, 3, 4, 5, 6; 1, 2, 3, 4, 5, another is left out; $v_1 i_1$ is another element, therefore I will say that in this network, this equation is correct, $v_1 i_1$ delivered is equal to $v_2 i_2$, if I miss the terms, you please tell me, plus $v_4 i_4$ plus $v_5 i_5$ plus $v_6 i_6$ plus $v_7 i_7$. This we have learnt in any network it has to happen. It has to happen at all times even if there are time varying.

So volt-ampere supplied, power supplied instantaneous must be equal to some of all the powers of other elements. Now this equation also I could write it like this, that v_1 minus i_1 , I will bring this term to write plus $v_2 i_2$ plus $v_4 i_4$ plus $v_5 i_5$ plus $v_6 i_6$ plus $v_7 i_7$. In that case, I will tell that I have written all the elements as if they are absorbing power. Total power absorbed by this network v_1 , how much power it is absorbing; v_1 and minus i_1 is entering through plus.

So v_1 minus i_1 is the power absorbed by this source, $v_2 i_2$ and why negative sign, because we know to absorb power through the plus current must enter. But since I have assigned current along the leaving the positive terminal, therefore, I have every right to say that minus i_1 is going towards positive and calculate this and then you tell that power absorbed by v_1 , which will come out to be negative. That means, it is really delivering power.

Power absorbed by v_1 and these are of course, all power absorbed. So this way I can write. Therefore, henceforth what I will do? In networks, I will assign the currents and voltages and always calculate power absorbed by different elements. I am sure that some of the terms will


become negative. Let it will become, but mathematically that is also correct. So remember that in any network, this is one of the conventions, better follow.

Instead of separately keeping track of power absorbed, power delivered, always try to make a habit, okay how much power is absorbed by each of the elements. In that sense, I will write it and that sum has to become equal to 0 from this I get. One could also say that I will always calculate power delivered by the network, so power absorbed, same equation could be written based on power delivered by each element with that concept, each element as if delivered powers.

Then I will write $v_1 i_1$ it is really delivering, but $v_2 i_2$, how much it is delivering, v_2 minus i_2 plus v_2 into, then I should not write plus i_2 , because in language I am written delivering, v_2 minus i_2 plus v_4 minus i_4 plus v_5 minus i_5 plus v_6 minus i_6 plus v_7 minus i_7 and this will be 0. In fact, this is the same equation I have written. I have just changed the side of each terms to the right. So you will be writing the correct equations.

No matter, whether you are calculating it considering all the elements to be absorbing power or delivering power. So I will assume all the elements are absorbing power. Now, this is not Tellegen's theorem, this is known, in a circuit and with numbers I can very neatly write down and clearly write down, which are the elements, which are actually absorbing power, which are the elements which are delivering power. We have discussed it in length.

(Refer Slide Time: 26:52)

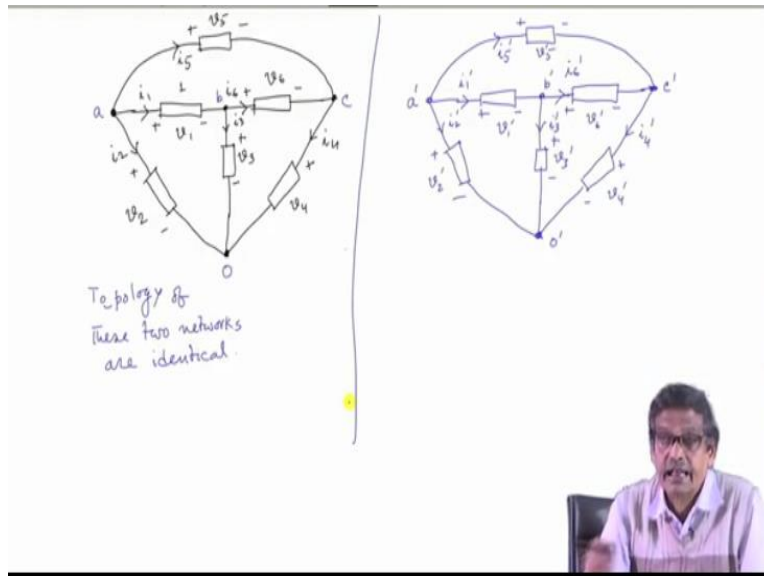

Now, what the Tellegen's theorem tells us that suppose, you have a network. Now let me be a bit methodical in telling the about the Tellegen's theorem. Suppose, consider a network like this and here also another element is there and there is also an element connected here, in general I am telling. So it is a network and these boxes are elements. Some of them could be sources as well, I do not mind, so source I am not drawing separately.

Now, what I will tell that, I will name the elements. For example, this element I will call element 1, voltage across it I will write v_1 and i_1 , quite arbitrarily, this is my prerogative in solving network, you assume polarity and current in whichever fashion you like, but once you assign that write down correct KVL and KCL okay. So let this be element 1, let this be element 2, whose voltage at any time is assumed to be with this polarity and current is assumed to be i_2 .

Let this be element 3, v_3 , this is i_3 . Let this be element 4, voltage across it is v_4 and current is suppose i_4 and in this direction and then this is suppose element 5, v_5 and current is flowing i_5 and this is the voltage across the element with this polarity v_6 and current is i_6 , I can do that, is it not. How many nodes are there in the circuit? 1, 2, 3, and 4 and let me name the nodes as a, b, c, and let this node be called o.

Say reference node with respect to that, I will calculate all the voltages. So, have you understood this thing? This is very important, a general network I have taken and in each branch there may

be 2 series elements, I have combined them and I am calling one element is connected. One of these boxes must have been the source, otherwise how current will survive, okay. So this is a network and this is the topology of the network.

Now I draw a similar network; structurally similar network like this. I have drawn another network, now this network geometrically or topologically they are identical okay, same type, 3 loops, 4 nodes and so on, but only thing these elements could be totally different from these elements. Another network for example, here there was a resistance, here maybe there is an inductance, here there was a source; source is there.

So these 2 networks are totally different networks except for the fact that their topologies are identical. Topology of these 2 networks are identical, got the point and this network is seen separate. I will name their thing with dashed element, a dashed, this node is b dashed, this node is c dashed and this node I will call o dashed, like that I can write. Similarly the voltage and current assumed across each element in this network, I will follow the same rule as I have done here.

For example, I will say this is the voltage across the element, in this dashed network and I will say the voltage across it is v_2 dashed and the current is i_2 dashed. For this element, I will say the voltage across this network is v_1 dashed and current is i_1 dashed. This was plus minus v_5 . This is the voltage across this element current is i_5 dashed. This is v_5 dashed. This is also plus minus v_6 dashed and the current in the same direction I will show, i_6 dashed.

And this is plus minus v_4 dashed and the current is i_4 dashed and plus minus this is v_3 dashed and the current is i_3 dashed. So these 2 networks have otherwise totally different network. Elements may be different only they are structurally same, same topology and with different elements, but the voltage across each element, their polarities I have assumed in the same way as I have done here.

Obviously, the currents i_1 dashed, i_2 dashed, i_3 dashed, i_4 dashed will be decided by what are the sources present here, what are the impedances, they will decide the current, loop equations

this, that you solve and that is supposed to be different from i_1, i_2, i_3, i_4, i_5 . Similar is the case with the voltage across each element that is v_1, v_2, v_3, v_4, v_5 . They are naturally expected to be different from v_1 dashed, v_2 dashed, v_3 dashed, v_4 dashed and so on, is it not. So Tellegen's theorem talks about 2 networks; 2 or more networks which have got same topology and we will continue with this in this next lecture. Thank you.