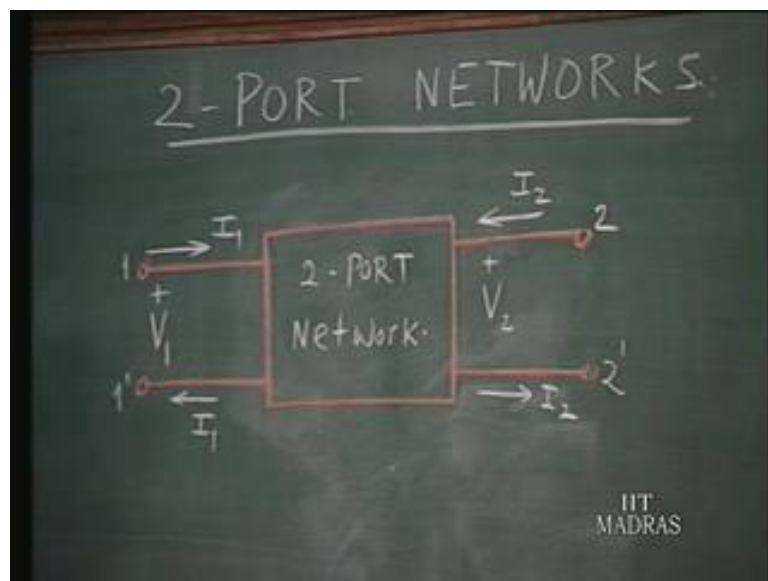


Network and Systems
Prof. V. G. K. Murti
Department of Electrical Engineering
Indian Institution of Technology, Madras

Lecture 31
Network Functions (2)
2-port network parameters
Reciprocal 2-port networks

In the last lecture, we discussed the network functions associated with 1 port networks the driving point impedance functions the driving point admittance function. Now, let us check the configuration of 2 port network which has got 2 terminal pairs 1 and 1 prime are the terminals associated with port 1, 2 and 2 prime are the terminals associated with port 2.

(Refer Slide Time 01:37)



The conventional reference signs for the port voltages and currents are given in this manner. Port current I_1 enters the network to the positive reference for port 1 V_1 . And the port current I_2 enters the network with the positive terminal I mean the positive reference sign for the voltage at port 2. This is the conventional way of taking these polarities of the voltages and currents. And the port concept ensures that if the current I_1 enters the terminal 1, the same current must leave to the terminal 1 prime.

And like wise, current entering terminal 2 must leave the network through terminal 2 prime. Now, we have four variables to deal with V_1 V_2 I_1 and I_2 . So, any two of these are linearly related to other two by virtue of the linear time invariant property of the network. So, depending upon the particular occasion context we take two of them as the excitation functions and the other two as the response functions.

So, you have choice of taking any two as the excitation function and other as the response function and depending upon the pair that you take as the excitation function, you get different types of parameters which describe this 2 port network. We will take up to start with a particular set of parameters called short circuit admittance parameters. This is one way of choosing two of as the input quantity and two as the response quantity.

(Refer Slide Time 04:26)

Short circuit Admittance Parameters

$$I_1(s) = y_{11}(s)V_1(s) + y_{12}(s)V_2(s)$$

$$I_2(s) = y_{21}(s)V_1(s) + y_{22}(s)V_2(s)$$

IIT
MADRAS

Here, we treat I_1 and I_2 as the response quantities and V_1 and V_2 as the input quantities. So, I_1 of s is linearly related to 2 the input quantities V_1 and V_2 and the proportionality constants for that are written as y_{11} of s times V_1 of s plus y_{12} of s times V_2 of s . So, the response in this the response of current I_1 is really related to the input quantities V_1 and V_2 by the proportionality constants y_{11} of s and y_{12} of s .

Similarly, I_2 of s is y_{21} of s times V_1 of s plus y_{22} of s times V_2 of s . So, the network now is characterized by four parameters y_{11} y_{12} y_{21} and y_{22} . They are called short circuited admittance parameters. Because dimensionally, they are

admittances because the ratio of current to a voltage and these are the four parameters are called short circuited admittance parameters.

(Refer Slide Time 04:48)

$$\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} y_{11}(s) & y_{12}(s) \\ y_{21}(s) & y_{22}(s) \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

IIT
MADRAS

In matrix form the same set can be written in very convenient fashion I_1 of s I_2 of s is obtained as the y_{11} of s y_{12} of s y_{21} of s y_{22} of s multiply it V_1 of s V_2 of s . So that is the convenient way in writing down the parameters in matrix form relating the currents to voltages.

(Refer Slide Time 05:33)

$$y_{11}(s) = \frac{I_1(s)}{V_1(s)} \Big|_{V_2=0}$$

$$y_{21}(s) = \frac{I_2(s)}{V_1(s)} \Big|_{V_2=0}$$


The diagram shows a two-port network with input terminals 1-1' and output terminals 2-2'. A voltage source V_1 is applied across terminals 1-1', and the current entering terminal 1 is I_1 . The output terminals 2-2' are short-circuited, so $V_2 = 0$. The current leaving terminal 2 is I_2 . The admittance parameter y_{11} is indicated as the ratio of I_1 to V_1 under these conditions.

IIT
MADRAS

If you observe that if I want to define y_{11} of s , (Refer Slide Time 04:26) if I want to find out what y_{11} of s is I have to write y_{11} of s is the ratio of I_1 of s to V_1 of s when V_2 is 0. Suppose I forced $V_2 = 0$ by short circuiting these two terminals and (Refer Slide Time 04:26) measure the current I_1 of s in response to excitation V_1 of s the ratio of I_1 of s to V_1 of s is y_{11} of s .

Therefore, I_1 of s is written as I_1 by V_1 of s and V_2 is 0; that means, you are short circuiting the output port 2 2 prime. This is 1 1 prime and we are measuring this admittance. You are connecting a voltage source V_1 and measuring the current here. Now let us see, what is the y_{21} of s ? y_{21} of s (Refer Slide Time 04:26) is the ratio of I_2 to V_1 when V_2 is 0. Once again in this equation if you force V_2 to 0 y_{21} of s is I_2 of s for V_1 of s . So, at the same excitation conditions this current I_2 to this V_1 is your y_{21} of s .

(Refer Slide Time 07:14)

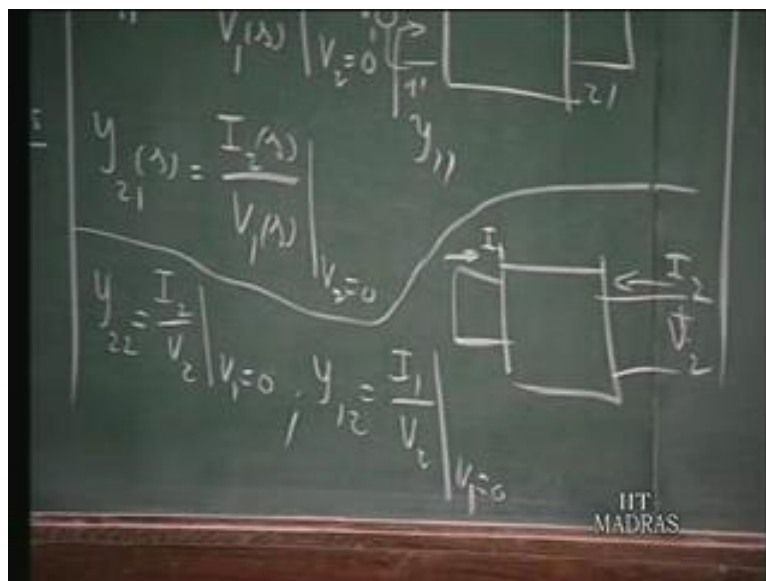

Now, suppose I want to find out y_{12} of s and y_{22} of s . So, y_{22} I will drop the functional notation s within brackets to simplify my writing y_{22} is I_2 by V_2 , when V_1 is 0. So, I_2 by V_2 at $V_1 = 0$; that means, the experiment that you suggested is in this 2 port network you short circuit this and you apply a certain voltage V_2 and measure I_2 the ratio of these two is Y_{22} of s .

And in the same experiment, if you find out the ratio of I_1 to V_2 I_1 to V_2 when V_1 is 0 I_1 to V_2 is Y_{12} Y_{12} therefore, Y_{12} is ratio of I_1 to v_2 by at $V_1 = 0$. So, you have

these four individual parameters can be calculated or can be defined as the ratio of excitation to the Laplace transform to excitation in Laplace transform response under these terminal conditions.

(Refer Slide Time 08:31)

$S:$ y_{11}, y_{22} : d.p. admittances
 y_{12}, y_{21} : Transfer admittances

$$\begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} y_{11}(s) & y_{12}(s) \\ y_{21}(s) & y_{22}(s) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

IIT
MADRAS

Now, y_{11} and y_{22} are called driving point admittances, because the response. And the input at the same location associate the same terminal pair either in the case of y_{11} or in the case of y_{22} I_2 or V_2 .

On the other hand y_{12} and y_{21} are called transfer equations, because the response location is different from the excitation location. Strictly as I said these are called driving point admittance function transfer admittance function. But to simplify our referring to them, we simple refer to them as admittances driving point admittances and transfer admittances.

One thing you should notice is there is the particular order of the subscripts which is important (Refer Slide Time 05:33) when you are calculating y_{21} it is I_2 by V_1 , the first subscript refers to the response location. All our network functions are the response that side, Laplace transforms with response to Laplace transform in the excitation. The first subscript here refers to the response location, the second subscript to the excitation location y_{21} .

There are driving point function both the response and excitation at the same location. Therefore, you have the same subscript y_{11} . Similarly, y_{22} (Refer Slide Time 07:14) look for y_{12} the response location is I₁ port 1. The excitation is at port 2. So, I₁ by the V_2 and this is y_{12} . So, there is an order in writing out the subscripts the first subscript refers to the response location.

The second subscript to the excitation location and that is also in accordance with this matrix. Matrix notations the first subscript use the row address. The second subscript refers the column address and that is exactly the, what we have here also. So, there is some consistency in writing down these equations and that we should keep in mind when defining the other parameters.

Another point to keep in mind is we use the lower case letters for this y 's not the capital letters, but the lower case letters small y and later all will be small z . Because, these are all admittances defined under certain normalized conditions. The general admittances with the other types of tabulations can be used capital letters. But, when you are using specifically for short circuit conditions they are called the lower case letters. Therefore to be must you must keep that in mind y_{11} y_{21} y_{12} y_{22} use small y 's.

Now in all these definitions here, you observe that the natural form of the network is when both ports are short circuited. This we have introducing a voltage V_1 here. And when this V_1 is destroyed or deactivated it may reduce to 0, this is short circuited and this is also a short circuited. Similarly, here you are finding the response of I₁ and I₂ when a voltage is introduced here.


So, when the voltage is removed or made equal to 0, both the ports are short circuited. So, these are the parameters measured under the short circuit conditions of the network both ports are short circuited. Therefore, they are called the short circuit admittance parameters. That is the reason why we call them short circuit admittance parameters.

(Refer Slide Time 01:37) Because, we assume that the natural form of the network is like this. Are we introducing a voltage source here and measuring the response. Similarly, you introduce a voltage source V_2 and measuring responses. So, the natural form of the network is both ports are short circuited. And therefore, the poles of all these network functions y_{11} y_{12} y_{21} y_{22} turn out to be the natural frequencies of the 2 port network when both the ports are short circuited.

And with our with minor exceptions here and there which may come out as a result the cancellation of common factors with numerators and denominators except for that fact. All these functions will have the same denominator polynomial. Because, they represent the natural frequencies of the network under short circuit conditions, therefore when you calculate y_{11} y_{12} y_{21} and y_{22} , you will find that the denominator polynomial all these function is one at the same. It is only the numerator which must be aware.

Now, how do we calculate this y_{11} y_{12} y_{21} and y_{22} for simple networks, you can use these definitions and find out y_{11} y_{12} y_{21} using these definitions.

(Refer Slide Time 13:31)

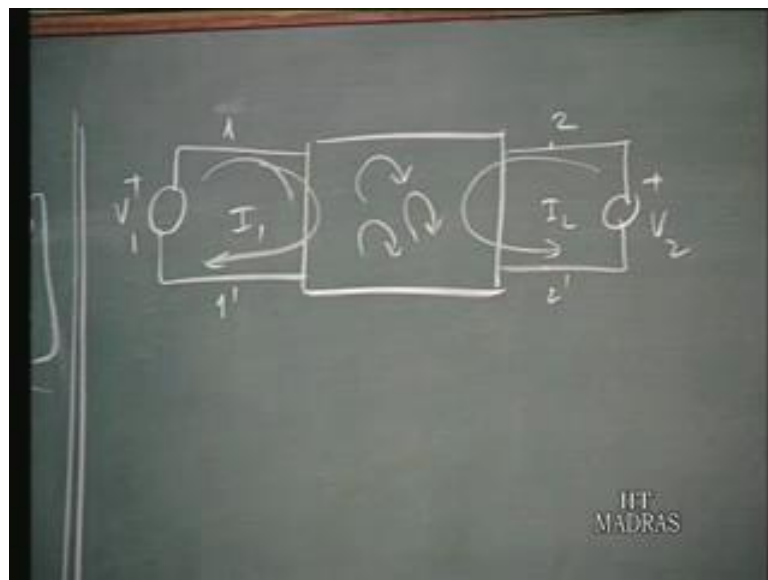

In a more general case suppose I have a 2 port network here. You connect a voltage source V_1 another voltage source V_2 here. And you perform the loop analysis. So through the network, you have this loop current I_1 through this you have loop current I_2 . And therefore may be internal loops here depending upon the structure of the network.

(Refer Slide Time 14:07)

$$\begin{bmatrix} Z_{11} & \dots & Z_{1m} \\ Z_{21} & \dots & Z_{2m} \\ \vdots & & \vdots \\ Z_{m1} & \dots & Z_{mm} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_m \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ 0 \\ \vdots \\ 0 \end{bmatrix}$$

So, you can write the loop equations of this network, we have say Z_{11} say there are m loops Z_{21} Z_{2m} Z_{m1} Z_{mm} . These are the loop equation I_1 I_2 I_m as far as the forcing function is concerned, you have the sources only in this loop quadrants two. Because internally, it is suppose to be a passive network linear time invariant network no independent source are present. Therefore, we have V_1 of s and V_2 of s here for the second loop all the others are 0s.

(Refer Slide Time 15:01)

$$I_1 = V_1 \left(\frac{\Delta_{11}}{\Delta_m} \right) + V_2 \left(\frac{\Delta_{21}}{\Delta_m} \right)$$

$$I_2 = V_1 \left(\frac{\Delta_{12}}{\Delta_m} \right) + V_2 \left(\frac{\Delta_{22}}{\Delta_m} \right)$$

So, from this you can calculate I_1 and I_2 by taking the ratio of the appropriate determinants. And if you do that you will get what I_1 equals V_1 times Δ_{11} by Δ_m , where Δ_m is the mesh based a system determinant and Δ_{11} is the co factor plus V_2 times Δ_{21} by Δ_m . That is you replace the when you calculating I_1 you replace that in first column by this column V_1 V_2 and 0 and when you expand that you will get this.

And similarly, I_2 will be V_2 Δ_{12} by Δ_m and V_1 times Δ_{22} by Δ_m . So, it is clear that this will be the y_{11} and this will be y_{12} this will be y_{21} and this will become y_{22} . So, you can calculate can write down the loop equations of the network in general terms of generalized impedances and calculate the ratio of the appropriate co factor to the mesh based system determinant and that will give you y_{11} y_{12} y_{21} y_{22} in a general case.


(Refer Slide Time 01:37) I mentioned earlier that out of this four quantities V_1 V_2 and I_1 and I_2 . We can take any two as an excitation quantities and take the other two as responses. Let us, now consider that the currents are excitations and voltages as the responses.

(Refer Slide Time 16:41)

The image shows a chalkboard with two equations written in white chalk. At the top, the current I_1 is written. The first equation is $V_1(s) = Z_{11}(s)I_1(s) + Z_{12}(s)I_2(s)$. The second equation is $V_2(s) = Z_{21}(s)I_1(s) + Z_{22}(s)I_2(s)$. In the bottom right corner, the text 'IIT MADRAS' is visible.

Therefore, I can write V_1 of s as an impedance Z_{11} of s multiplied by I_1 of s plus another impedance Z_{12} of s multiplied by I_2 of s . And similarly, the second voltage is Z_{21} of s times I_1 of s plus Z_{22} of s times I_2 of s .


(Refer Slide Time 17:18)

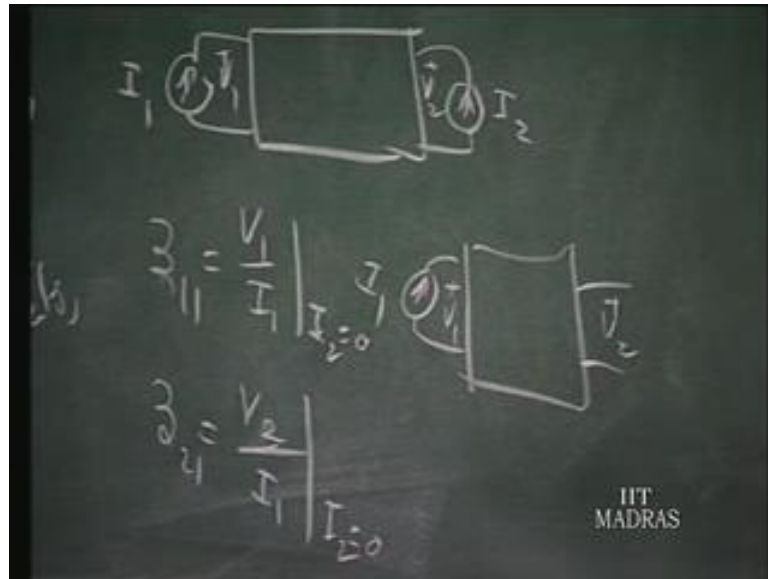

Now, we know have the voltage s as the response quantities and currents and the inputs; that means essentially, what we are thinking of is a network with few current excitations I_2 I_1 and V_1 and V_2 are the response quantities. So, these are called open circuit impedance parameters, for example if I want to measure z_{11} all I have to do is z_{11} is the ratio of V_1 to I_1 when I_2 is 0. Similarly, z_{21} is V_2 by I_1 , when I_2 equal to 0; that means, you are now thinking of a situation where a current I_1 is led in and you are measuring out the responses V_1 and V_2 .

The ratio of V_2 to I_1 is z_{21} the ratio V_1 to I_1 is z_{11} . (Refer Slide Time 04:26) So naturally, you get a similar set of defining relations for z_{12} and z_{22} for z_{12} z_{22} . We have to find out you have to make I_1 0.

(Refer Slide Time 1832)

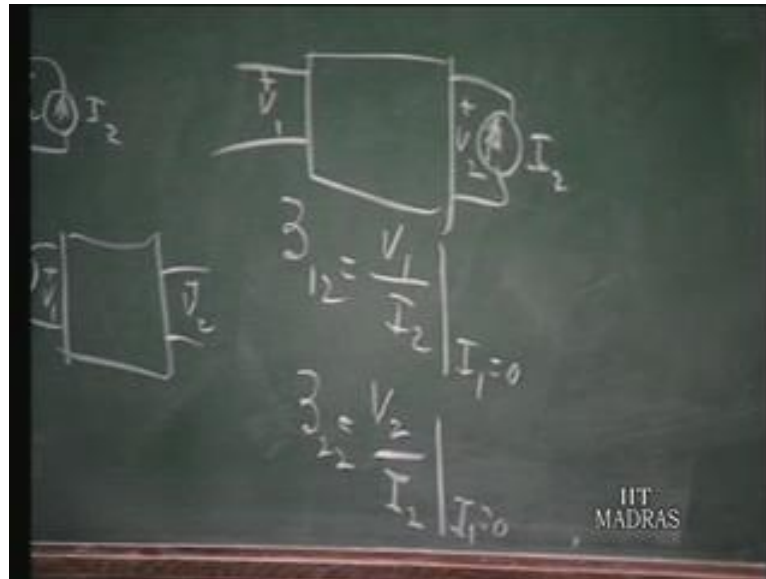

Therefore, you should make $I_1 = 0$ and introduce a current I_2 here. And this is the response V_2 and this is response V_1 z_{12} is V_1 divided by I_2 . When I_1 is 0 and z_{22} is V_2 divided by I_2 when I_1 is 0. So, these definitions are completely in parallel with it defining relationship for the y parameters except now the currents are the excitations sources.


And therefore, we also observe that if this current I_1 is made equal to 0 both the terminals are open. Similarly, when I_2 is made equal to 0 then both of them; that means, these are network functions whose poles represent the natural frequencies of the network when the both the ports are open circuited. So, the raw form of the network is that this is both terminals are open. And you have connect a current source the soldering type of entry for the two currents and finding out the responses.

Whereas, in the short circuit parameters the raw or the natural form is the short circuited and we are introducing a voltage source in that the pliers of the entry at the voltage source. So, we have these are called open circuit impedance parameters. And naturally z_{11} and z_{22} are the driving point impedances because V_1 / I_1 V_2 / I_2 are individually measured in the same pair of terminals. So, Z_{11} and Z_{22} are the open circuit driving point impedance functions z_{12} and z_{21} are the open circuit transfer impedance functions.

So, to summarize the z parameters represent the network functions defined under open circuit conditions. By introducing current sources, when the current sources are open removed then the 2 ports are open circuited. There the poles of all this network function represent the natural frequencies. The network under open circuit conditions Z_{11} and Z_{22} are the driving point impedance functions, z_{21} and z_{12} are the transfer impedance functions.

And we can define them in this fashion are individually and need not to find out these parameters for a general network. We can do the loop current in the node voltage method of analysis. You can introduce a current source here make this a latter node point of the response for V_1 V_2 . And then, you can perform the node analysis and get the values of z_{11} z_{21} z_{12} and z_{22} in more or less similar fashion as what we are demonstrated for the case of admittance functions.


(Refer Slide Time 21:38)

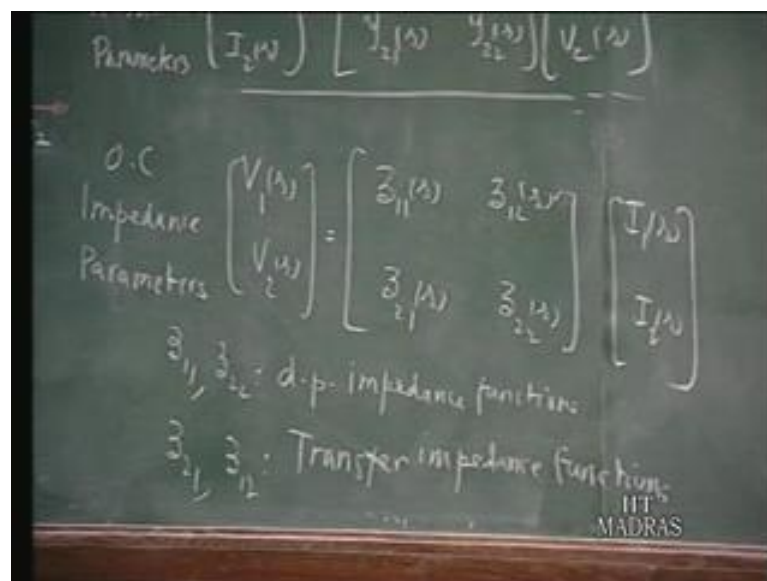

So, let me write this table here in this table, we have already discussed given the matrix relation short circuit admittance short circuit admittance parameters are called y parameters. In the similar fashion we can write V_1 of s and V_2 of s as z_{11} of s z_{12} of s z_{21} of s z_{22} of s and I_1 of s I_2 of s . These are called open circuit impedance parameters. Again z_{11} and z_{22} are the driving point impedance functions open circuit driving point impedance functions, where as z_{21} and z_{12} are the transfer impedance functions.

Now looking at these two, after all you have a matrix relation the currents are given in terms of voltages. (Refer Slide Time 08:31) So, voltages suppose from this you want express voltage in terms of currents you have to invert this matrix and write $V_1 V_2$ is this matrix inverse times $I_1 I_2$. So, one can expect that this entire matrix here is the inverse of this matrix. So, the inverse of this matrix is the inverse of the matrix is this. So, z and y matrices are inverses of each other that does not mean that y_{11} is the inverse of z_{11} .

(Refer Slide Time 23:53)

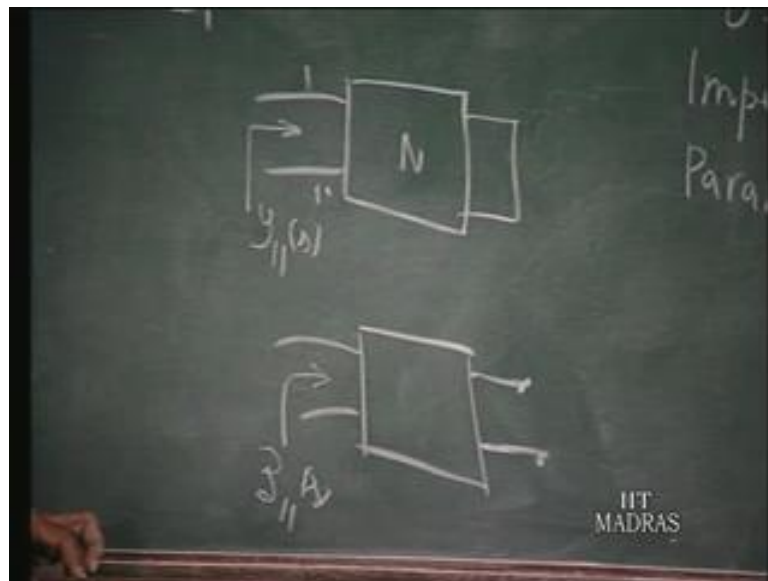

Look at the definition of Y_{11} , how do you define Y_{11} is the ratio of I_1 to V_1 when V_2 is 0. So, you short circuit this and measure this admittance and that is y_{11} of s , how do you define z_{11} it is the ratio of V_1 to I_1 when I_2 is 0, so the you are keeping this open circuit at. And measuring these impedance that is z_{11} of s . So, the network in which this admittance is measured and the networks in which this impedance are measured are different.

This N have other terminals as short circuited here the two terminals are kept open circuited. Because of this reason, z_{11} is not necessarily equal to $1/y_{11}$. So, the short circuit driving point admittance at port 1 is not the reciprocal or the open circuit driving point impedance at port 1.

These two are not reciprocally related, but this entire matrix is the inverse of this matrix. So, you can show that z_{11} is related to all the y parameters in some fashion you can

invert the matrix and find out. But individually, y_{11} is not equal to $1/z_{11}$, because the two networks are different.

(Refer Slide Time 25:21)

Hybrid Parameters

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Inverse hybrid parameters


$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

IIT
MADRAS

Now, apart from these two basic matrices, you have various other types of matrices which I would like to talk about now. You can express V_1 and I_2 in terms of I_1 and V_2 . So, it will be $h_{11} \ h_{12} \ h_{21} \ h_{22}$ times I_1 and V_2 . Again I am dropping the functional notation for the convenience. You can also express I_1 and V_2 in terms of V_1 and I_2 . Normally, these are referred as $g_{11} \ g_{12} \ g_{21} \ g_{22}$. These are called hybrid parameters h parameters are hybrid parameters commonly used in transistor work.

The reason, why they are called hybrid they are mixed variable? Because, you are not talking about both the input quantities as the voltage are currents I_1 is a current other is a voltage response also one is voltage other is current. So, therefore, they are mixed variables they are called hybrid parameters. These are called inverse hybrid parameters h parameters or inverse h parameters.

(Refer Slide Time 26:52)

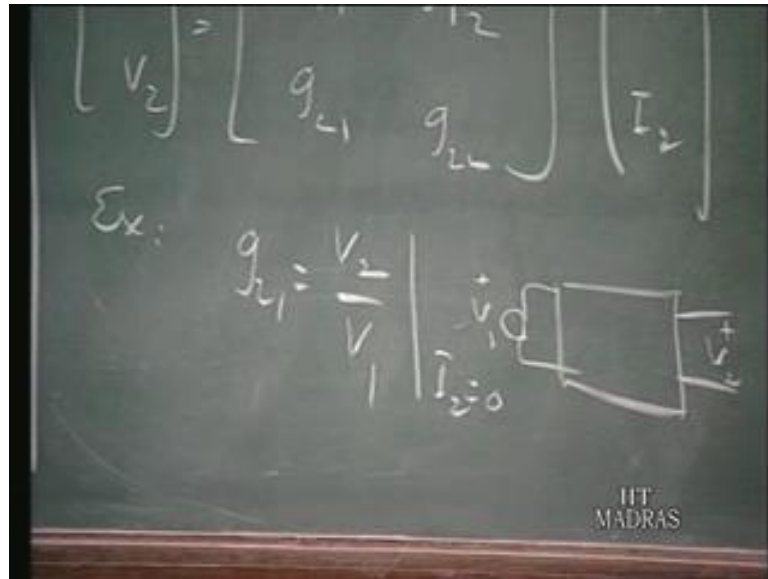


And once again, you can define example if I want to find out what g_{21} is V_2 over V_1 when I_2 is 0. Because, V_2 is $g_{21} V_1$ plus $g_{22} I_2$, therefore when make I_2 equal to 0, V_2 equal g_{21} times V_1 . So like this, you should be able to define each one of these parameters with the appropriate terminal conditions.

Now, you observe that this is the ratio of the response when $I_2 = 0$ and you are measuring the V_2 over with a particular excitation. So in the in defining, this g type parameters this the x pattern of excitation and response that you are having. So, the natural form of the network is when V_1 is 0, this port is short circuited and the other port is open. So, in this hybrid parameters it turns out that 1 port is open circuit the other port is short circuited.

Therefore, the poles here represent the natural frequencies when 1 port is open circuit the other is short circuited, whereas here both the ports are short circuited. This is the case where both the ports are open circuited. If the case hybrid parameters 1 of the ports will be open circuited, the other is short circuited. And the natural frequencies under those conditions will be the poles at the appropriate networks functions here.


(Refer Slide Time 28:18)

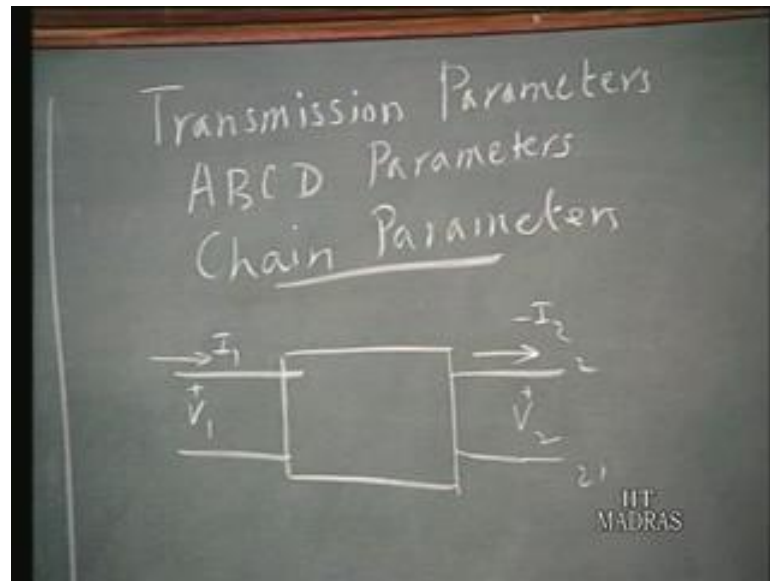

In addition you also have another important category of parameters which go by the name transmission parameters also called ABCD parameters sometimes called chain parameters. Here, assume that this is the transmission line and you are talking about the output of the transmission line. This current is minus I_2 , because we are we are defining the port I_2 as leading inwards. Therefore, $2' 2$ prime this the voltage and current that is being fed from the at the output end.

And the receiving end here, at the transmission line let us say V_1 and I_1 are the voltage and current. So, we can think of V_1 and I_1 are the quantities at the sending end and V_2 and I_2 are quantities at receiving end like a transmission line. The current is going out of transmission line this is terminal voltage at the receiving end. The terminal voltage and current will sending in.

(Refer Slide Time 29:35)

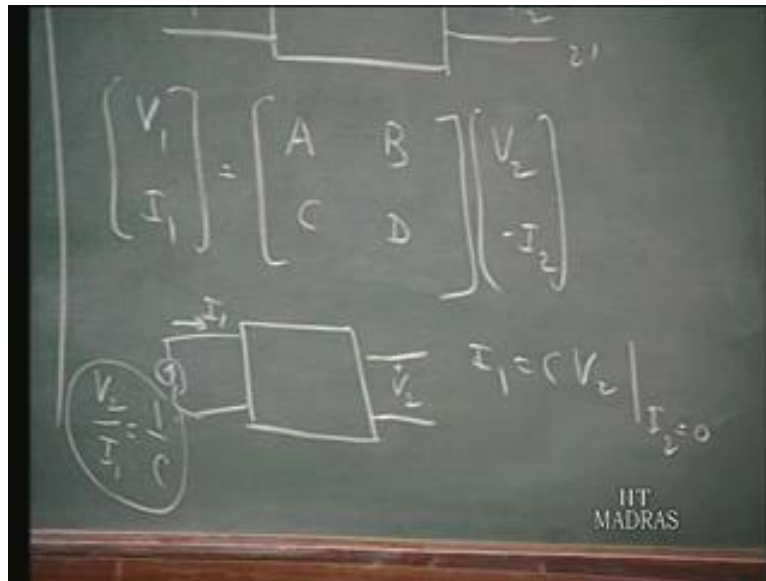

So, if you express V_1 and I_1 in terms of the receiving end quantities V_2 and minus I_2 . Then, these are related like parameters ABCD again ABCD a function surface at general case and this is called ABCD parameters. So that is how these are defined. Now let us see, how do you find out C? C is the ratio of I_1 to V_2 when I_2 is 0. So, I_2 is 0, this is kept open circuited and is the ratio of V_2 to I_1 .

So, the ratio V_2 to I_1 is equal to $\frac{1}{C}$ where I_2 is 0, I_1 equals $\frac{1}{C} V_2$ when I_2 is 0. So normally, when you define any network function you write C equals I_1 by V_2 . You can think of V_2 as an excitation, but unfortunately here I_2 is forced to be 0. Therefore, you cannot think of a connecting a voltage source and again make sure that I_2 is 0. Therefore, you have to think of a current source here, I_1 that is the input and your measuring the V_2 .

Therefore V_2 by I_1 the response to the input V_2 by I_1 turns out to be therefore, $\frac{1}{C}$. So, in the case of this chain parameters, these ABCD values do not turn out to be the network function in our standard format in the ratio of the Laplace transform of the response to the Laplace transform of the input. It turns out that in this particular case of the chain parameters, the reciprocals of these quantities $\frac{1}{C}$ $\frac{1}{A}$ $\frac{1}{B}$ $\frac{1}{D}$ turn out to be the network functions.

In our conventional sense at the Laplace transform of the response to Laplace transform of the input. Because, C normally would be assumed to be I_1 by V_2 and V_2 being the

response, but V_2 is the input. If V_2 is the input we cannot force the current also to be 0, because we cannot connect a voltage source here and then demand that current I_2 is 0.

So, it turns out that as far as the ABCD parameters are concerned it is the reciprocal of the ABCD's which are the conventional network functions. But, we use this ABCD also in network functions in this relationship. But they deviate from our standard definition of a network function. Now in all these cases in all these; that means, we have a essentially five important sets of parameters. Actually, we can have a 6th set also we can expect V_2 and I_2 in terms of V_1 and I_1 that is the inverse of this matrix that becomes 6.

(Refer Slide Time 01:37) After all we have four quantities here V_1 V_2 and I_1 I_2 , you can select a pair of two quantities from four in six different ways. So, you have 1 2 3 4 5 and the, if you take inverse of this you get a sixth set of parameters. But, we normally that is not done that is not very important.

These are the five sets of parameters which are important the short circuit admittance matrices, the open circuit impedance matrices, the hybrid parameters, the inverse hybrid parameters and the chain parameters. The importance of the chain parameters are why you call them chain parameters it will be brought out later. And in the both y matrix z matrix h matrix and g matrix, we use the lower case letters, because they are under standardized terminating conditions It is conventional to use the lower case letters.

As far as the ABCD parameters are concerned, it is a conventional to write them by capital letters A B C and D. It is also important for us to recognize the dimensions of the each one of these quantities. As far as y and z are concerned (Refer Slide Time 25:21) their impedance and admittance is no problem at all h_{11} as the dimensions of resistance or impedance because V_1 h_{11} is V_1 divided by I_1 when V_2 is 0. Therefore this has the dimension of impedance h_{12} V_1 divided by V_2 where I_1 is 0 that has a dimension.

It is dimensionless it is a ratio likewise this is a ratio this has the dimensions of an admittance. Similarly, (Refer Slide Time 25:21) g_{11} has the dimensions of an admittance, g_{12} has the dimensions as the ratio no dimension at all g_{21} is dimension less g_{22} has the dimension of a impedance. Likewise, you can associate the dimensions with each one of these.

So, important thing is for us you must have the familiarity with these, but you must be able to define each one of these parameters in any one of these sets like in this fashion. You must know the dimensions of the quantities that are involved. And further more by manipulating this equations, (Refer Slide Time 08:31) if somebody gives us the admittance parameters of a 1 port 2 port network from these y parameters should be able to derive any other set of parameters.

So, after all from this you have to write down two equation I for I 1 and I 2 in terms of V 1 and V 2. And using those two equations you can manipulate this equations to express I 1 V 2 in terms of V 1 I 2 by manipulating these equations. (Refer Slide Time 25:21) Therefore, in other words given y parameters we should be able to get g parameters in 2 port parallel network given y parameters you should be able to get h parameters and so on and so forth.

So, you should be able to manipulate these equations and find out one set of parameters from any given set. And that is straight forward it is not very difficult I mean tables are set up there is available in textbooks. But, we do not have to read always use these tables we should be able to deduce one set of parameters from the other by manipulating these equations. one or two examples you work out little later.

So, at this point of time, let us now look at these, let us take one or two examples to illustrate these ideas which we have discussed just now. That is to derive one set of parameters from the other set. And then, we will try to work out some other examples using these various parameters.

(Refer Slide Time 36:04)

Express h parameters
in terms of y-parameters.

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \quad \left| \quad \begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$

IIT
MADRAS

Let us, now take an example express h parameters in terms of y parameters. Suppose that is the question that is asked. You recall that h parameters have this form $h_{11} I_1 + h_{12} V_2$. And I_2 equals $h_{21} I_1 + h_{22} V_2$. But, y parameters have the form I_1 equals $y_{11} V_1 + y_{12} V_2$ and I_2 have the form $y_{21} V_1 + y_{22} V_2$. So, now we have to express V_1 and I_1 in terms of I_1 and V_2 .

(Refer Slide Time 37:09)

$$V_1 = \frac{I_1}{y_{11}} - \frac{y_{12}}{y_{11}} V_2$$

$$I_2 = y_{21} \left[\frac{I_1}{y_{11}} - \frac{y_{12}}{y_{11}} V_2 \right] + y_{22} V_2$$

$$= \frac{y_{21}}{y_{11}} I_1 + \left(y_{22} - \frac{y_{12} y_{21}}{y_{11}} \right) V_2$$

$$h_{11} = \frac{1}{y_{11}}, \quad h_{12} = -\frac{y_{12}}{y_{11}}$$

$$h_{21} = \frac{y_{21}}{y_{11}}, \quad h_{22} = y_{22} - \frac{y_{12} y_{21}}{y_{11}} = \frac{\Delta}{y_{11}}$$

$$\Delta = y_{11} y_{22} - y_{12} y_{21}$$

IIT
MADRAS

Therefore, we have to find out from this V_1 equals from this I_1 by $y_{11} V_1$ equals I_1 by y_{11} minus y_{12} by $y_{11} V_2$. That is what we are having? I_1 by Y_{11} minus Y_{12}


by $Y_{11} V_2$ so; that means, that particular equation is in accordance with this form. So, so we already have $h_{11} h_{12}$. As far as I_2 is concerned, we express I_2 in terms of I_1 and V_2 . But, we have I_2 expressed in terms of V_1 and V_2 .

But, V_1 expression we already know, so substitute this here. So, you get I_2 equals y_{21} times for V_1 we substitute this expression I_1 divided by y_{11} minus Y_{12} by Y_{11} times V_2 plus $y_{22} V_2$. So, we have now expressed I_2 in terms of I_1 and V_2 ; that means, this will be y_{21} divided by y_{11} times I_1 plus y_{22} this is starting from this $y_{21} y_{22}$ divided by y_{11} times V_2 .

So, we have expressed V_1 and I_2 in terms of I_1 and V_2 . So, from this we can readily see that h_{11} is 1 over y_{11} h_{12} here minus y_{12} over y_{11} , h_{21} equals y_{21} over y_{11} and h_{22} is this quantity y_{22} minus $y_{12} y_{21}$ divided by y_{11} . That is what we have added. So, this you can write this if you have a common denominator this is Δy divided by y_{11} plus Δy is the determinant of the y matrix $y_{11} Y_{22}$ minus $y_{12} Y_{21}$.

That is you have the y matrix is this $y_{11} y_{12}$, $y_{21} y_{22}$. So, if you take the determinant of this matrix this will be $y_{11} y_{22}$ minus $y_{12} y_{21}$ and that is what we are having here Δy by y_{11} . So, in this way you should be able to convert one set of parameter into ((Refer time: 39:56)).

(Refer Slide Time 40:17)

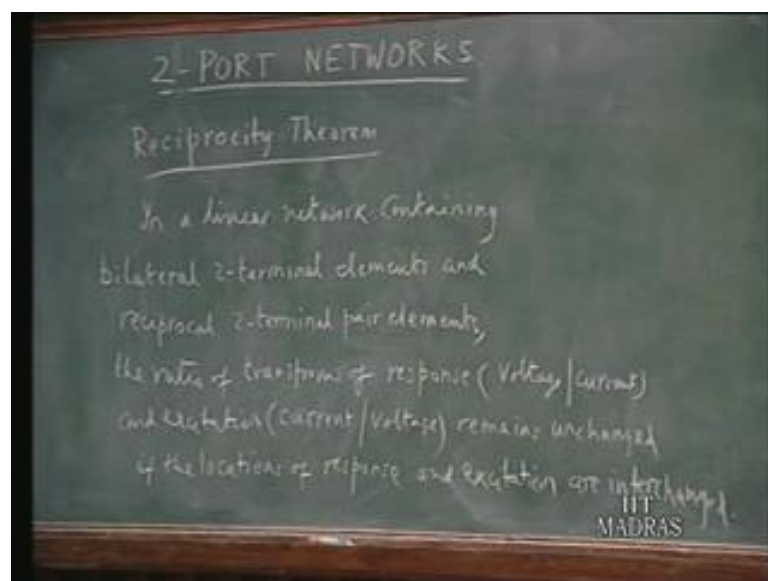


We shall now consider some restrictions imposed on these parameters by a network which is called a reciprocal network. A reciprocal network is a network which satisfies the reciprocity theorem. What is the reciprocity theorem? The reciprocity theorem states that in a linear network containing bilateral 2-terminal elements and reciprocal 2-terminal pair elements.

The ratio of response to excitation, where response means either voltage or current and excitation may be current or voltage. The ratio of response to excitation remains unchanged or remains the same, if the location of response and excitation are interchanged, if the locations of response and excitation are interchanged.

First of all let us see, what this means? We are talking about a linear network containing 2-terminal elements, bilateral 2-terminal elements; that means, the ratio of voltage to current in the form of the relationship remains the same, whether the current is in one direction or the other.

All over or else the elements are bilateral 2-terminal elements, reciprocal, 2-terminal pair elements; that means, you have 2-terminal pairs, your mutual inductance m_{12} is the same as m_{21} . So, these elements are called reciprocal 2-terminal elements. So if you have RLCM elements, the ratio of response to excitation will remain the same if the locations are interchanged; that means, let us take an example.

(Refer Slide Time 43:20)

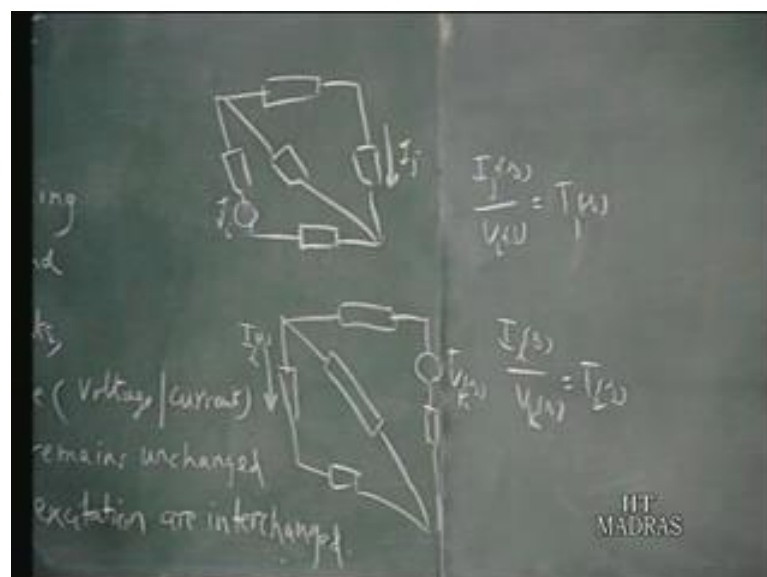

Suppose, I have a network like this suppose I inter I put a voltage source V_i here and measure the current here I_j . So, I am finding out the current here in response to an excitation introduced here. So, I get I_j of s over V_i of s. So, let us say this a one particular transfer ratio, transfer function T_1 of s. Now, if I interchange that; that means, I am measuring the current here by introducing a voltage source here. Suppose I reverse this, I introduce a voltage here say V_k of s.

And then, I measure the response here I_l of s. So now, where I have originally the excitation point I need to finding out the response and where I was earlier measuring the response I am introducing the voltage here. So, I_l of s divided by V_k of s let us is T_2 of s. So, this another transfer function the reciprocity theorem tells us that these two ratios are the same, because the response ratio the ratio of response to the excitation remains the same, when their locations are interchanged.


In viewing this, we must be careful that this current is entering that point as far the source is concerned this point is also entering that point. As far as the this source is concerned. So, you must have some consistency in the symmetry in the reference sides that is important.

And secondly, I purposely write response voltage current here and reverse the order here. So, when you are measuring the ratio response to excitation. You must take the response if its voltage the excitation is the current if the response is current voltage is response excitation is voltage. It does not work out when both the responses are voltage. But, response and excitation are voltages both the response and the excitation are currents.

We will illustrate that little later why it is so. So, one must be a current, the other must be a voltage that is important. And any network which satisfies this is called a reciprocal network. So, a reciprocity theorem is applicable to the types of networks which contain these elements. So, we should be also be familiar, what types of elements will not have reciprocity theorem satisfied. If you have linear dependent sources, control sources and so on. It does not satisfy reciprocity theorem.


So, the types of networks for a another element which some of you may be familiar with what is called a generator? It is an anti reciprocal 2-terminal pair element that also it does not is not will not satisfy reciprocity theorem. So, reciprocity theorem is valid as essentially for RLC networks with mutual inductances also present.

(Refer Slide Time 46:26)

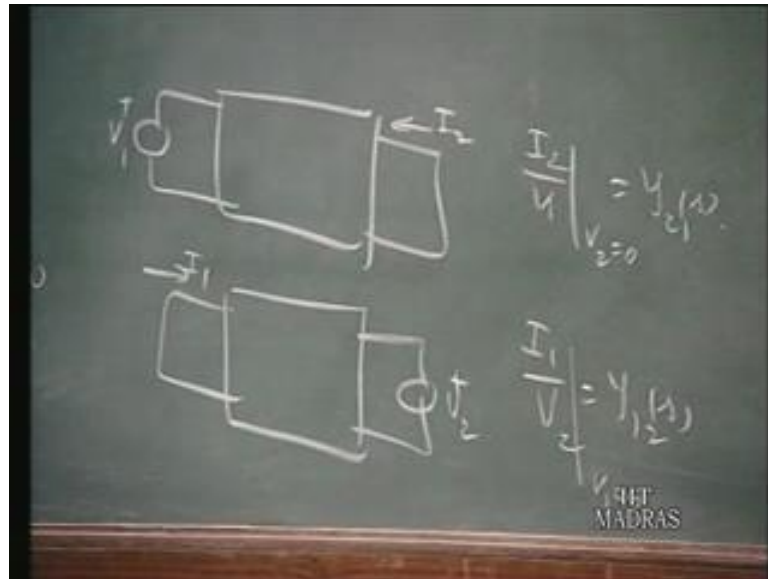

As an obvious of this, what we have here is? Suppose I have 2 port network and let us say this is the raw form of the network. This is a basic network, if I introduce a voltage source here, V_1 and measure the current here I_2 . So, this is I_2 by V_1 when V_2 is 0, this we call this as y_{21} of s we know that.

(Refer Slide Time 47:22)

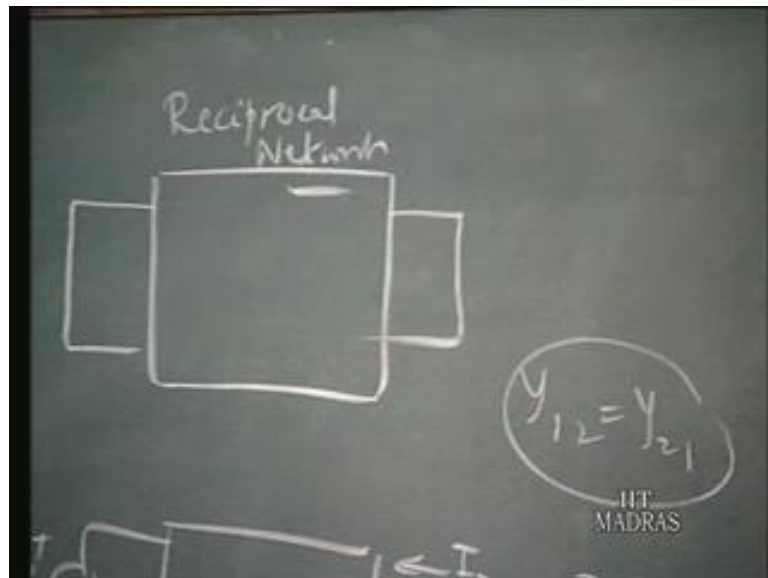

Now in this raw form of the network, suppose I introduce a voltage here V_2 and measure the current response here I_1 . Then, I_1 by V_2 is y_{12} of s, this is what we say when V_1 is 0, this 1 how we define. So, if this is reciprocal network y_{12} must be the

same as y_{21} . So, if this is the reciprocal network it satisfies the reciprocity theorem y_{12} is equal to y_{21} .

(Refer Slide Time 47:39)

Reciprocity

$$y_{12} = y_{21}$$

$$z_{21} = z_{12}$$

$$h_{12} = -h_{21}$$

IIT MADRAS

Similarly, it can be shown that for a reciprocal network; that means, the 2 port is a reciprocal of course. We know that y_{12} is equal to y_{21} . Similarly, it can be shown that z_{21} is equal to z_{12} and it can be shown that h_{12} equals minus h_{21} . Again h_{12} and h_{21} can be expressed in terms of z parameters and this can be shown.

(Refer Slide Time 48:05)

$$h_{12} = -h_{21}$$

$$AD - BC = 1$$

$$\frac{1}{C} = z_{21}$$

$$z_{12} = \frac{AD - BC}{C}$$

IIT MADRAS

And similarly, $AD - BC$ for a reciprocal network is equal to 1, this comes from the fact that $\frac{1}{C}$ happens to be z_{21} and z_{12} happens to be $\frac{AD - BC}{C}$. So; that means, $AD - BC$ by C this is $AD - BC$ by C . So, for a reciprocal network these two must be equal. Therefore, $AD - BC$ is equal to 1. So, this is the consequence of reciprocity as far the parameters are concerned.

So in this lecture, we have introduced ourselves to the various sets of parameters characterizing a 2 port network. These are the z parameters, the y parameters the hybrid parameters h , the inverse hybrid parameters g parameters and the transmission parameters ABCD parameters. We saw that they these two those are independent specifications one set of specifications can be obtained from the other.

We should be able to convert one set of parameters into any one of the other required sets. And we also saw an example, where this such a transformations can be done. Next, we consider the case of reciprocal 2 port network which basically consist of RLCM elements. In such cases, we have additional constraints on the parameters in any individual set.

Basically, the z parameter that two the transfer impedance parameters must be the same, in the case of short circuit admittance parameters the two transfer impedances must be the same. In the hybrid parameters h_{12} must be equal to minus h_{21} and in the case of ABCD parameters $AD - BC$ equals to 1; that means, the determinant of the ABCD matrix must be equal to 1.

These are all equivalent conditions; we will study some additional properties of these parameters. And then, the how for particular configurations one set of parameters is easier to calculate than the others. All these questions will be taken up in the next lecture.