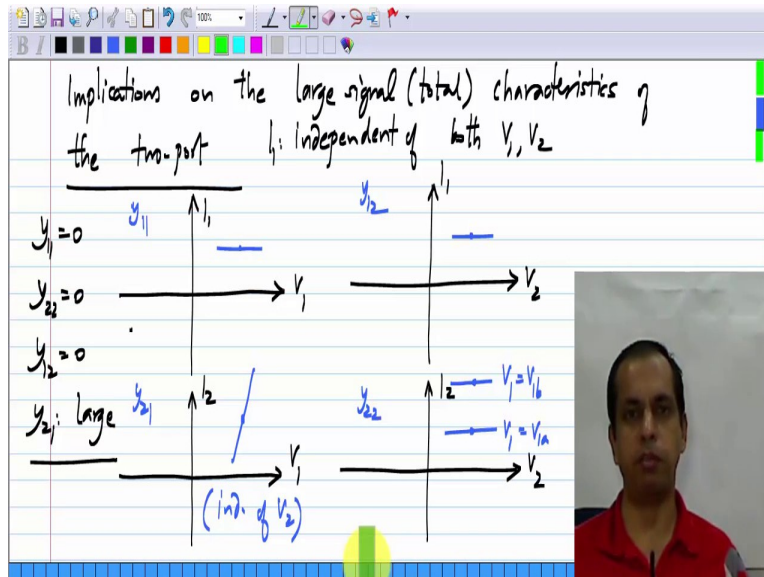


**Analog Circuits**  
**Prof. Nagendra Krishnapura**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Module - 02**  
**Lecture - 03**

(Refer Slide Time: 00:04)



Now let us see what the implications are on the large signal that is total characteristics of the two-port. What do we have now, we have  $y_{11}$  equal zero,  $y_{22}$  equal zero,  $y_{12}$  equal zero and  $y_{21}$  should as large as possible. Now the large signal characteristic can be described by these four graphs, where one of the variable is on the x axis and the other variable is fixed or it's varied as parameter. Now, these small signals parameters are the slopes of these characteristics. For instance, the slope of  $I_1$  versus  $V_1$  is  $y_{11}$ ; slope of  $I_1$  versus  $V_2$  is  $y_{12}$ ; slope of  $I_2$  versus  $V_1$  is  $y_{21}$ , and slope of  $I_2$  versus  $V_2$  is  $y_{22}$ .

Now what does it mean to have  $y_{11}$  equals zero, by the way these are only around some operating point. You have to choose the operating point correctly, because the total characteristic of the nonlinear ah device can be anything, it is around some operating point that we need to have these constraints. So what does it mean to have  $y_{11}$  equal to zero, it means that these characteristics  $I_1$  versus  $V_1$  are flat around some operating point. So let say this is the operating point here, then that means that the slope of  $I_1$  versus  $V_1$  is zero. And similarly because  $y_{12}$  is zero, slope of  $I_1$

versus  $V_2$  is also zero. Now  $V_1$  and  $V_2$  are the only variables, so what does it mean here around some operating point  $y_{11}$  is zero that is the variation of  $I_1$  with  $V_1$  is negligible, it is zero. The variation of  $I_1$  versus  $V_2$  is also zero, because  $y_{12}$  is zero, so this means that this current  $I_1$  is constant that is it is independent of  $V_1$  and  $V_2$  around some operating points, so that's what it is implied by these two small signal parameters.

Again it has to be remembered that this needs to be true only around at certain operating point, it does not have to be true everywhere. If it is true around at certain operating point, we have to choose that operating point. And similarly  $y_{21}$  is very large, so what does it mean the variation of  $I_2$  versus  $V_1$ , the slope of  $I_2$  versus  $V_1$  has to be very large around some operating point. It has to be as steep as possible. And  $y_{22}$  is also zero, so that means that  $I_2$  versus  $V_2$  that has a characteristic like that around the operating point. So what it says is that  $I_2$  versus  $V_1$  has to be very steep, whereas  $I_2$  versus  $V_2$  has to be very shallow that is  $I_2$  should not depend on  $V_2$  at all around some operating point.

I also said that basically these graphs are as drawn for instance  $I_2$  versus  $V_1$  is drawn with  $V_2$  as a parameter, because  $I_2$  does not change with  $V_2$ , so essentially this characteristic  $I_2$  versus  $V_1$  should be independent of  $V_2$ . Because clearly around this operating point we know that  $I_2$  is not changing with  $V_2$ . On the other hand, for this graph  $I_2$  versus  $V_2$ ,  $V_1$  is the parameter; and we know that  $I_2$  changes very sharply with  $V_1$ , in order to have a very large  $y_{21}$ . So if you draw a parametric plot here, so for a particular value of  $V_1$ , you will have this. For another value of  $V_1$ , we will have a very different current, but it will still be flat that is it is independent of  $V_2$ . So if  $V_1$  is  $V_1$ , the current will be different but the variation of  $I_2$  versus  $V_2$  will be flat, that is this slope will be zero.

So what we have done is to evaluate the constraints on small signal parameters, and from that infer what the large signal parameters have to be. And these are good characteristics of amplifiers, regardless of what device you build. For instance, if you are trying to invent a new device, you have to invent a device which follows these things in order to maximize the gain. Of course, instead of choosing  $y$  parameters, you can choose some other parameters and try to maximize the gain according to that parameters, but the qualitative characteristic will be the same; meaning these characteristics these parameters  $11$ ,  $12$ , and  $22$  will be nearly zero, and the characteristic two

one will be very sharply varying. So all it means is that the second port must respond strongly to the first port and all other responses must be very small. I hope this part is clear, you will actually see later that the real devices that we have like the MOS transistor or the bipolar transistor do conform to this in their idealized form, so that is why we choose to go like this, but it also gives you sort of generalization, you do not have to stick to bipolar transistors or MOS transistors, any other device comes along just by looking at the characteristic, you should be able to say if it will make a good amplifier device or not.