

Analog Circuits
Prof. Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology, Madras

Module - 03
Lecture – 04

Now, we understand the common source amplifier, and also the limitation caused by the transistor output conductance and so on. Now, in this lesson we will look at some practical aspects of a common source amplifier and in general any amplifier. The point is that the parameters of a transistor, or in general any active device semiconductor device vary quite a lot, that is if you realize a lot of transistors and you nominally intend to have the same current factor and same threshold voltage and so on. In reality they will come out to be different from each other, and also it different from one manufacturing batch to another. And also like many semiconductor characteristics, these things are a strong function of temperature. Now, these will have some effect on the amplifier performance, we will first see what that is and try to come up with techniques that fixed these things to the extent possible.

So, let say the transistor is operating at some operating point; it has some V_{GS} , some V_{DS} , and a certain I_D . Now the small signal parameters of this g_m , we know it is $\mu_n C_{ox} W$ by $L (V_{GS} - V_T)$. Again I am ignoring the one plus λV_{DS} term. And also the output conductance g_{ds} is λI_D . So, these are the parameters of the small signal equivalent circuit. In the small signal circuit, we will have the $g_m V_{GS}$, where this is the incremental V_{GS} ; and we have the conductance g_{ds} . Now, how did we setup the operating point in our common source amplifier. Basically, we wanted a certain g_m , and from that we found the V_{GS} , and the way we fixed the operating point was to fix V_{GS} to the desired value. So, if you recall our circuit looked like this, I am not drawing the complete circuit, but only the part that fix is V_{GS} . And in our particular example, we had a 23 volts supply and an appropriate ratio of resistors such that the operating point V_{GS} was equal to 3 volts. We fixed V_{GS} to 3 volts.

So, now let see what happens with this type of setting up of the operating point. So, g_m is $\mu_n C_{ox} W$ by $L (V_{GS} - V_T)$; and as usual I will consider the threshold voltage to be 1 volt, and $\mu_n C_{ox} W$ by L to be 100 microampere per volt square. Now in our circuit, this is fixed at

three volts. So clearly, if you calculate this, this will come out to be 200 micro Siemens, which is what we wanted. Now, it turns out the threshold voltage of a transistor can vary considerably. So, let say it varies from 0.8 volts to 1.2 volts; it can vary by even more than that.

So, if V_T happens to be 0.8 volts, and let say the current factor does not change at all. What happens, this $V_{GS} - V_T$ will be three volts minus 0.8, which is two point two volts. So, this g_m will turn out to be two twenty micro Siemens. So, I hope it is clear what I am doing here. In our circuit, V_{GS} is fixed; and we thought that V_T was one volt for our transistor, but who knows when you buy many transistors, it could be 0.8 volts or even smaller. So, if you do apply the same formula with V_T being point eight volt, you will get 220 micro Siemens.

And similarly, if V_T is 1.2 volts, $V_{GS} - V_T$ is smaller than what is required, it is one point eight volts, and g_m will be 180 micro Siemens. So, you can see that instead of two hundred, we are getting either 220 or 180 or some value in between. Now, we have not even taken into account the variations in $\mu_n C_{ox}$. So if $\mu_n C_{ox}$ varies by let us say plus ten percent, if it is higher by ten percent then g_m will also be higher by 10 percent. And similarly if this value is lower by 10 percent, the g_m will also be lower by 10 percent and so on.

Basically, g_m is proportional to $\mu_n C_{ox} W/L$, and any variations in $\mu_n C_{ox}$, by the way like I said μ_n is mobility of the semiconductor and that varies quite a bit with temperature. So, there are couple of things here, one is that the value of V_T may not be known exactly; one possible way though tedious is to when you buy transistor you somehow measure V_T and then you design your amplifier. Even that does not solve your problem, because over temperature things will vary. So, let us say you measure it at room temperature, let us take this particular case; V_T is only 0.8 volt, so to get 200 micro Siemens, you calculate whatever V_{GS} is required, and then apply that V_{GS} , and that does not help, because if V_T changes with temperature, this g_m will shift, change with temperature and so on. And similarly as current factor changes with temperature, g_m will change with temperature. So, we need to have a more robust way of setting up the operating point, so that the g_m does not vary as much as it does now.