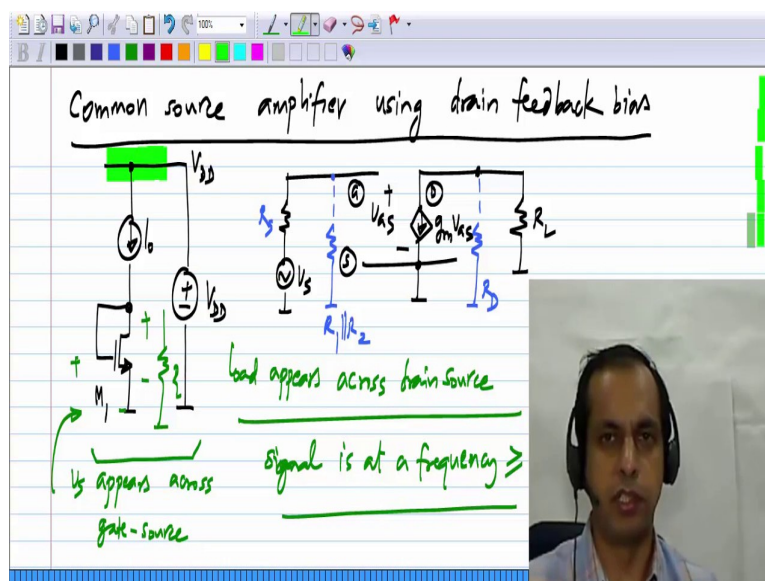


**Analog Circuits**  
**Prof. Nagendra Krishnapura**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Module - 03**  
**Lecture – 10**

(Refer Slide Time: 00:27)



We now know the technique of drain feedback biasing, but our aim is to realize a common source amplifier with smaller gain sensitivity. So, what we have to do is to marry the drain feedback bias with the small signal picture of the common source amplifier and come up with the circuit, which behaves like a common source amplifier in the incremental small signal picture, but its biasing is based on drain feedback. Now, drain feedback bias has this arrangement, the desired drain current  $I_0$  is connected that way and the drain voltage is fed back to the gate, let me call this MOS transistor  $M_1$  and this is  $V_{DD}$ , which really means that the supply voltage  $V_{DD}$  is connected between this upper rail and ground. So, it is quite common to show sometimes just the line that is marked  $V_{DD}$ , it means that there is a battery of value  $V_{DD}$  between this point and ground.


Now, what is the common source amplifier? common source amplifier is one where I have a signal source, and I have my transistor, gate, drain and source. And this is the control source inside the transistor  $g_m V_{GS}$ , where the  $V_{GS}$  is the gate source voltage.

The source is grounded and the load is connected between drain and ground, this is the essence of the common source amplifier. Now, of course, we could have extra components, first of all, we could have capacitors, which are useful for adding some value of bias to the signal, assuming that the signal is above a certain frequency. Also, we may have other resistors useful for biasing. If you recall the old circuit, we had  $R_1$  parallel  $R_2$  over here, and then we had the drain bias resistor  $R_D$  over there. These may or may not be there that depends on the exact biasing arrangements. But the stuff that I have shown in black that is the common source amplifier.

So, somehow we have to make sure that this signal  $V_s$  or most of it appears across this gate source. And then we have a load resistance  $R_L$ , and this  $R_L$  must appear across drain source. Now, of course, this must happen without disturbing the bias. So, let us try to do this. We already know all the principles we need for this. We know how to add signal to bias. As usual, we will assume that the signal is at a frequency greater than or equal to some  $\omega_0$ . So, we do not have dc signals. So, in this case, you can use ac coupling techniques, we can use a capacitor to couple the signal and we know how to calculate the value of the capacitor.

So, given this, we can proceed with trying to turn this into a common source amplifier, so let us do that. As usual, I would encourage you to think through the steps yourself, to find out exactly how to do it, and it is fun, this is how you invent circuits. This circuit we are going to come up with is already well known, but later when you become more experienced, you can come up with new circuits and that is why a chain of logical reasoning just as this one. So, you know certain building blocks and you put together those building blocks to make more complex circuits.

(Refer Slide Time: 04:36)

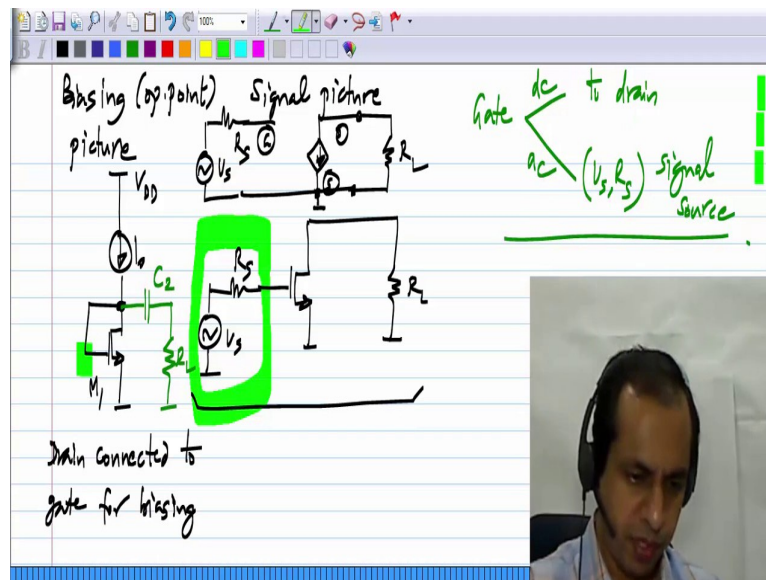

So, we have the biasing picture or setting up of the operating point and in that, I will continue to show it like this. Please understand that there is a battery between this point and ground. This is  $M_1$ ; so the essential feature here is that drain is connected to the gate for biasing. And the signal picture, I will show a MOS transistor instead of its small signal picture, I could also show that. Let me show both and later depending on convenience, I will show only one or the other. This is the small signal picture, what should happen, this source should be grounded in this small signal picture and the source  $V_s$  must appear here. This is the gate, this is the drain, this is the source and  $R_L$  must appear over there. And of course, the transistor has to remain in saturation, but that is guaranteed by this biasing arrangements. Because in this case,  $V_{DS}$  equals  $V_{GS}$  and it is definitely more than  $V_{GS}$  minus  $V_T$  as long as the threshold voltage  $V_T$  is positive.


Or if I draw it with the MOS symbol and have  $V_s$  and  $R_s$  appearing across the gate source, and  $R_L$  appearing over here, this is in the small signal incremental picture. Now, first let us try connecting the load resistor. The load resistor must appear between drain and ground or it must be connected to the drain. So, let me take the load resistor  $R_L$ , which could be grounded. This was explained earlier while discussing the original common source amplifier.  $R_L$  is the representation of whatever follows it may not be a physical resistor, so one side of it is grounded.

Now, what do I do? It has to get connected to the drain so the first naive attempt is to simply connect it to the drain like that. Now, please think about what problems this could have. One problem that is immediately evident is that we wanted this current  $I_0$  to flow through the drain of the transistor, the drain current has to be equal to  $I_0$ . But, in this case, what happens I have a certain value of operating point drain source voltage  $V_{DS}$ , and that appears across  $R_L$ , so  $V_{DS}$  by  $R_L$  will flow that way. So, the current in steady state, this drain current will not be equal to  $I_0$ , but it will be equal to  $I_0$  minus  $V_{DS}$  by  $R_L$ . So, this is an unnecessary complication, you do not want this  $R_L$  to draw any operating point current, it is totally useless. There is no point in doing that.

So, what do we have to do, we have to connect it differently, we cannot connect it directly. So, somehow only for signals it should appear across this. And that is easy if this signal is above a certain frequency  $\omega_0$ . So, this is known as ac coupling and the way we connect  $R_L$  to the transistor is exactly the same as our original common source amplifier. We connect it through a capacitor. So, that if the capacitance is very large, then all of the signal voltage  $V_{DS}$  will appear across  $R_L$ , but the dc here is blocked. So, sometimes this is also known as dc blocking capacitor. The operating point here will be  $V_{GS}$ , whatever the  $V_{GS}$  is; it is given by ( $V_t + \sqrt{2k_n I_0}$ ), as we have evaluated earlier. The operating point voltage here is zero, and the difference would be dropped across the capacitor. So, let me call this  $C_2$ , following my original notation.

Now, what should I do about the gate? The gate voltage must get connected to the drain for dc biasing, but it should get connected to this source combination of  $V_s$  and  $R_s$  for signal, for ac. For dc, it should go to the drain; and for ac, it must go to  $V_s$   $R_s$ , basically the signal source. How do we arrange this? This is again something that we know. We know how to add a certain dc to a certain ac signal source, that is we want a terminal to be connected to terminal A for dc, and terminal B for ac, we know how to do that. This is exactly what we did earlier also.

(Refer Slide Time: 10:12)

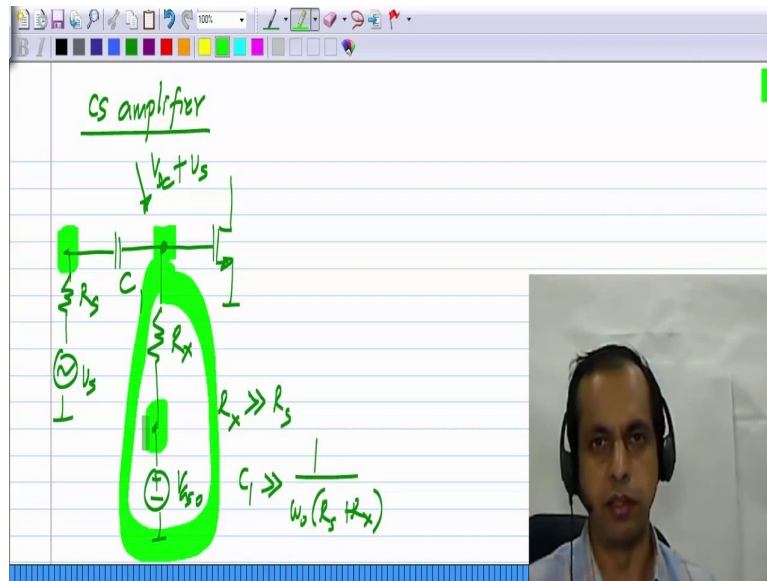

In case of the common source amplifier, if you recall the gate, I would not show the complete picture on the drain side, but the gate we have to get  $V_{dc} + V_s$ . So, what did we do? We have the signal source  $V_s$  and we have the dc source  $V_{GS0}$ , whatever the quiescent value, the operating point value of  $V_{GS}$  is. How did we do this? So we connected  $V_{GS0}$  through some resistor and the signal source through a capacitor. Now, of course, we have to satisfy some more conditions. This  $R_x$  has to be much more than  $R_s$  so that all of  $V_s$  appears here and

$$\omega_0 \ll \frac{1}{R_s + R_x} \quad \text{and so on. So, this was the essential idea. Now, of course, in the common}$$


$$C_1 \gg \frac{1}{\omega_0}$$

source amplifier, we did not have a separate source  $V_{GS0}$ , this itself was derived from a voltage divider powered by the supply voltage  $V_{DD}$ . But now the idea is exactly the same, the gate has to get connected to something for ac and something else for dc.

So, what we do is the following. Let me show this broken here. This point should get connected to the drain for dc. I connected through a resistor, let me just call it  $R_G$ . At the same time, you should also get connected to the signal source for ac. So, I connect it to the signal source through a capacitor  $C_1$ . And now we have to make sure that this  $C_1$  is much larger than something and we have this  $R_G$ , we have to find out the effect of that and so on. So, what we have done is to use the principle of ac coupling to connect the signal source to the gate source

and the load  $R_L$  to the drain source. So, I hope the logic is very clear, if not please replay the lecture and follow the logic once more, it is very important that you understand the logic behind every step of this.

(Refer Slide Time: 12:53)

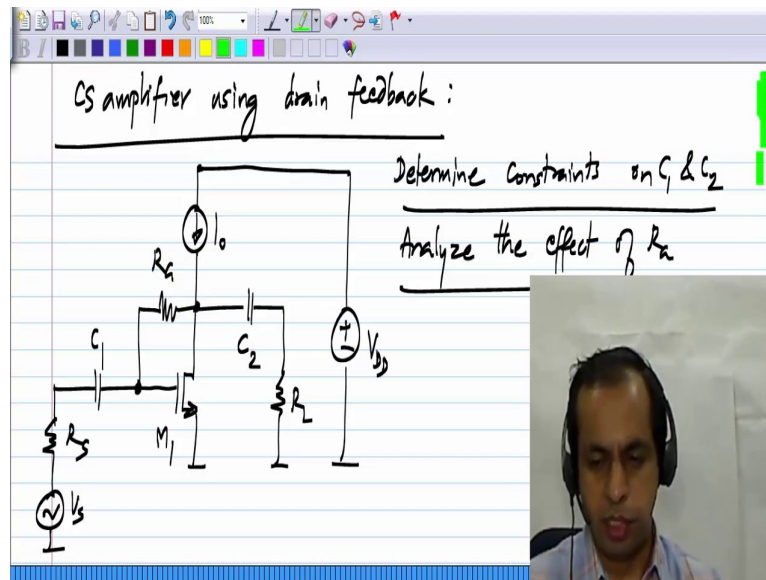

So, the common source amplifier using drain feedback. I will show the complete picture here. So, we have a current source  $I_0$ , the feedback to the gate is provided through  $R_G$  and that is ok, because no dc flows into the gate, so there will no dc voltage drop across  $R_G$ . Earlier, when we were coming up with the biasing arrangement, we had connected the drain directly to the gate, now we connected through an  $R_G$ , but it makes no difference at all, because no dc flows through the gate. And the signal source is connected to the gate source via  $C_1$ , the load resistance  $R_L$  is connected to the drain source via  $C_2$ . So, this is the topology. Like I said hopefully you understand all the logical steps leading to this.

Now, we have to, of course, go and analyze this use our circuit analysis skills and analyze the effect of everything. So, we need to determine constraints on  $C_1$  and  $C_2$  just like before. Also, we have to analyze the effect of  $R_G$ , because  $R_G$  is not a component that is in the basic common source amplifier. So, if you look at this, this is the basic common source amplifier, it has the transistor, signal source and load; that is all. The  $R_G$  is something extra, it is similar to the bias resistor we have in the original common source amplifier topology, we had  $R_1$  and  $R_2$  on the gate side, and drain bias resistor  $R_D$ , and we analyzed the effect of that and so what happens. So, similarly we have to do it here, we have to find the effect of  $R_G$  and see what is

the good value so that it does not significantly or adversely affect the common source amplifier.