

**Analog Circuits**  
**Prof. Nagendra Krishnapura**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Module - 04**

**Lecture – 08**

(Refer Slide Time: 00:21)

Sense @ drain, feedback to source

$I_D > I_0$ , we must reduce  $V_{GS}$

$V_{GS} = V_{G0} - V_S \Rightarrow$  increase  $V_S$

$V_S$  reduces

-negative incremental gain

If  $V_S$  reduces  $\Rightarrow I_D > I_0 \Rightarrow V_S$  must increase

" increases  $\Rightarrow I_D < I_0 \Rightarrow$  " decrease

So, far we have discussed two types of biasing a transistor at a desired current. In one case, we sense the difference between desired and actual currents at the drain terminal and feedback to the gate; in the other case, we sense the difference at the source terminal and feedback to the source. There are two more varieties that are possible. One of them is to sense at the drain and feedback to the source terminal. So, let us say we have the transistor, and because we are feeding back to the source terminal, we keep the gate at a fixed voltage  $V_{G0}$ . Now, we want to sense the current difference at the drain, so we have  $I_D$ , so to be able to sense the current difference, we connect a current source  $I_0$ . This gate connected to the supply some voltage.

And now I will come back what happens to the drain node, but this is the source voltage  $V_s$ , so if  $I_D$  is more than  $I_0$  that is the actual drain current is more than the desired current then we must reduce  $V_{GS}$ . If we reduce  $V_{GS}$  then the drain current will come down. Now,  $V_{GS}$  equals  $V_{G0} - V_s$ , so this means that to reduce  $V_{GS}$ , we must increase  $V_s$ . And similarly, if  $I_D$  is too small, if  $I_D$  is smaller than  $I_0$  then we must increase the drain current and we do that by reducing the value of  $V_s$ . So, this is the action what we want at the source. Now, what really


happens at the drain? The difference between  $I_0$  and  $I_D$  flows into this capacitor  $C_p$ , which consists of the parasitic capacitance at this node. Now, if  $I_D$  is too large that is  $I_D$  is larger than  $I_0$  then this current will be negative, current will be drawn out of the top lead of this capacitor. So, if  $I_D$  is more than  $I_0$  then the drain voltage  $V_D$  reduces. And the opposite happens if  $I_D$  is less than  $I_0$  then the drain voltage would increase.

Now, you see that  $V_D$  reducing is an indication that the drain current is larger than what is required. And in that case, we must actually increase  $V_s$ . So, the sense of change we want at the source is opposite of what is happening at the drain. So, if  $V_D$  reduces, we must increase  $V_s$ ; and if  $V_D$  increases, we must reduce  $V_s$ .  $V_D$  reduces this means that  $I_D$  is greater than  $I_0$  and this means that  $V_s$  must increase. And similarly, if  $V_D$  increases this means that  $I_D$  is smaller than  $I_0$  and this must decrease. So, how do we accomplish this? What we really meant is some block which takes its input, which is the drain voltage and gives an output, which is the source voltage. And also it must have this behavior, that is if  $V_D$  reduces,  $V_s$  must increase and so on.

So, let say these are the input and output terminals of this block whatever that is, then the output versus input that is the voltage at the output versus the voltage at the input should have a characteristic like this, which means if this  $V_{in}$  increases,  $V_{out}$  what is driven to the source which actually decreases. In other words, it must have a negative incremental gain. So, you must drive the source using an amplifier or some block, which is driven by the drain voltage and this must have a negative incremental gain so that the sense of variation is as shown here. So, this is slightly more complicated than our original case. The very first case we discussed, we sensed at the drain and fed back to the gate; the sense of variation we wanted at the gate was exactly the kind of variation we were getting at the drain.

So, we could connect it with a positive incremental gain in general; and even a direct connection was ok. Whereas, in this case, the direct connection will certainly not work; and you do need a negative incremental gain between the drain and the source. So, because this is slightly more complicated, we normally would not use this for a simple common source amplifier, but these structures do occur in many places in circuits. I will show you one example of how to accomplish this.

(Refer Slide Time: 05:36)

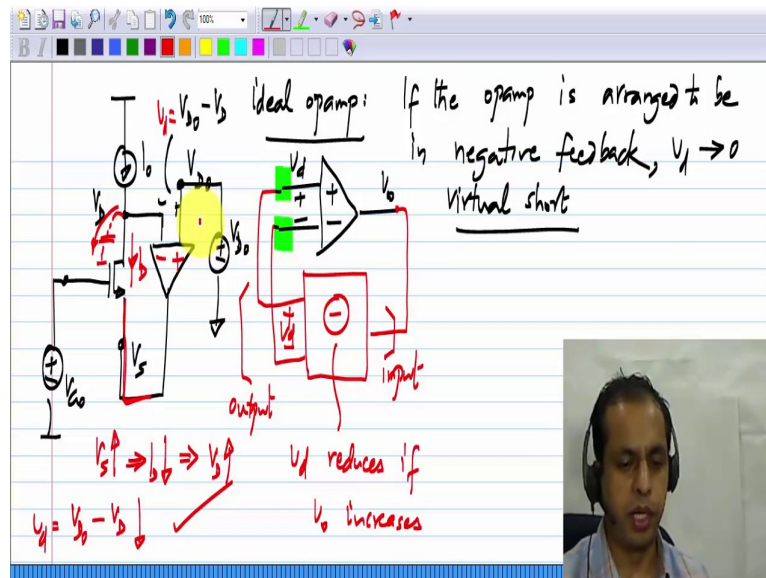

This is at  $V_{G0}$ , some bias voltage at the gate; and this is  $I_0$ . Like I said I should take this, make it go through a negative incremental gain and drive the source. There are many, many options possible. What I will use one particular option using an op amp and I assume that you are familiar with the concept of an ideal op amp. If not, please go through the relevant lecture material from basic electrical circuits. The ideal op amp, I will describe it very, very briefly here; it has an input  $V_d$  between two terminals; it has two input terminals and the difference voltage is called  $V_d$ . The input terminals are marked with plus and minus, and this is the difference voltage and the output voltage  $V_o$ .

Now, what it means is if the op amp is arranged to be in negative feedback, what does that mean? There is some circuitry around the op amp, you cannot use the op amp just by itself without anything else. So, there is some circuitry around the op amp,  $V_o$  gets connected to that, and the input terminals of the op amp also get connected to that. What is the meaning of negative feedback, it means that the action of this circuit whatever is the rest of the circuit is such that  $V_d$  reduces if  $V_o$  increases. In other words, this stuff has a negative incremental gain, it does not have to be actually a gain. All it has to do is to make sure that  $V_d$ , which is the output of this block, as far as this block is concerned, you can think of this as the output and this as the input. And this block should be such that its output reduces if the input increases, that is this  $V_d$  must reduce as  $V_o$  increase through the feedback circuit.

If that the case, then in case of an ideal op amp,  $V_d$  goes to zero that is the difference between these two terminals will be forced to zero by the op amp. And this concept of  $V_d$  being forced to zero, this is known as the virtual short. Now, if two nodes are shorted to each other; obviously, there will be at the same voltage. In the case of an op amp, operating in negative feedback, these two terminals are not shorted together, there is no wire connecting them. But this op amp and the negative feedback together will force these two voltages to be exactly the same and that is what the ideal op amp does. In case of real op amp,  $V_d$  will become very, very small, but not exactly zero; in case of an ideal op amp, it becomes zero. These things are described in more details in basic electrical circuits or you can use some of the text books that you may have which described the op amp.

So, I am going to use this block to complete the feedback. What I did was I took the drain voltage, fed it to one of the inputs of the op amp, and drive the source with the output of the op amp. And the other input of the op amp, I call it  $V_{d0}$ . Basically, it is some fixed bias voltage as far as I am concerned right now, this is  $V_{d0}$ . Now, how should the circuit be configured? Obviously, first of all, we already know that the incremental gain from the drain to the source must be negative. So, this appears to be the negative terminal so that is what it should be the terminal on the left side is the negative terminal. You can also examine it from the viewpoint of the op amp and you will reach exactly the same conclusion.

So, what must happen is that if  $V_d$  increases,  $V_s$  must reduce so that tells you that the sense of the op amp must be like that. Now, going by what I described to you just about the op amp, the difference voltage in this polarity is  $V_{D0} - V_D$ . And I will now analyze the rest of the circuit, that is from this point onwards this is the output of the op amp that I call  $V_s$ . Now, what happens if  $V_s$  increases, this  $I_D$  here will actually reduce, because the gate source voltage reduces; and in that case,  $I_0$  minus  $I_D$  will flow into this capacitor and raise the drain voltage, the drain voltage increases. And the difference voltage of the op amp, if the signs of the op amp were like that the difference in voltage of the op amp is  $V_{D0} - V_D$  and this will fall down. So, it is in the correct sense for negative feedback.

The way you evaluate the op amp signs for the negative feedback is you assume some sort of signs and then you work around and then see if this difference voltage reduces as  $V_o$  increases. So, if I choose the signs to be like that then as  $V_s$  increases,  $I_D$  will fall down which will make the drain voltage increase, which will make the difference voltage  $V_d$ , this  $V_d$  here, decrease. So, it is in negative feedback. So, the correct signs of the op amp are like that. So,

this is the way of biasing a transistor at constant current  $I_0$  by sensing at the drain and feeding back to the source.