

**Analog Circuits**  
**Prof. Nagendra Krishnapura**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Module - 05**

**Lecture – 12**

(Refer Slide Time: 00:05)

Current controlled current source (CCCS)

$i_o = k i_i ; k=1 \quad i_o = i_i \quad \text{Current buffer}$

$R_i \rightarrow 0 ; R_o \rightarrow \infty$


$i_o = i_i \cdot \frac{R_s}{R_s + R_L}$

Now, we will take up another type of controlled source, which is the current controlled current source. And just like with the voltage controlled voltage source, we will make the gain of the current controlled current source to be one, that is in general a current controlled current source should have an output current which is some constant  $k$  times the input current, and this should be independent of the impedance of the source which is driving the current controlled current source and also the load resistance. For that to happen, it should offer a very small input resistance tending to zero, and a very high output resistance. Now, because of the way the MOS transistor is, which has a common terminal between control and controlling side that is the source terminal is common to the two sides, it turns out that we can only realize  $k$  equals one.

So, we will try to realize  $i_o = i_i$ . Again as with the case of the voltage controlled voltage source, although there is no gain, this is still useful as a current buffer, meaning let say we had an imperfect current source  $i_i$  in parallel with some source resistance  $R_s$ . And if you have a load resistance  $R_L$ , if you connect it directly, the load current will be just a fraction of the input current. And how much this fraction is depends on the ratio  $R_s$  to  $R_L$ . Now, if you use a

current buffer, this is a current buffer, it will have a very low input resistance meaning all of that current will go into the input and the output current will be exactly equal to the input. So, regardless of the values of  $R_S$  and  $R_L$ , the output current – the current in the load will be equal to the input current, so that is the use of it. And we will realize this using a MOS transistor.

(Refer Slide Time: 02:51)

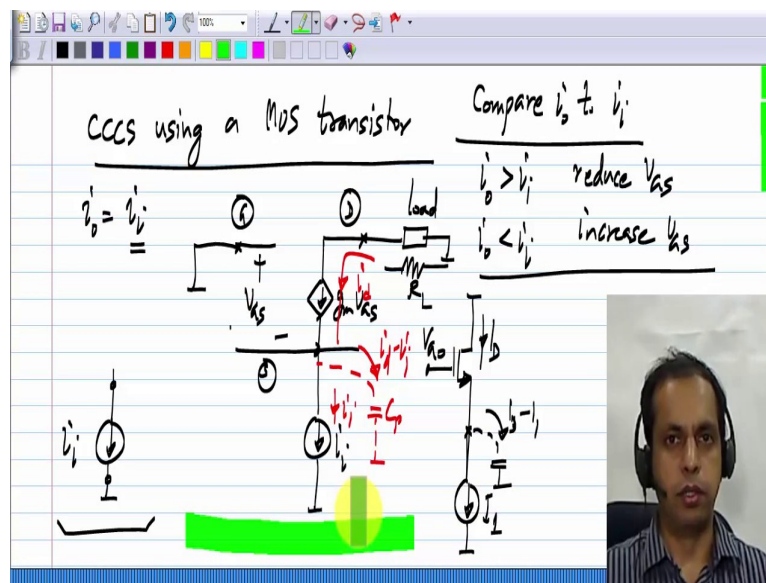

So, we want  $i_o = i_i$ , when we say there is an input current; obviously, we mean that there is a current source whose value is  $i_i$ ; and of course, it could be non-ideal. In fact, it is expected to be non-ideal. And it will have a resistance in parallel with it which is  $R_S$ . Recall that our representation for a voltage input is a voltage source  $v_i$  in series with resistance  $R_S$ , equivalently you can think if it is a current source  $i_i$  in parallel with  $R_S$ . So, this is our input. Now, in the initial discussion, just to make that drawing I will omit  $R_S$ . Although later I will put it in and analyze its effect.

Now, I want  $i_o = i_i$ . And what is this  $i_o$ , we have the MOS transistor with its gate, drain and source terminals. This is  $v_{gs}$ , and this current is  $g_m v_{gs}$ . And the incremental drain current flows from drain to source, and that will be the output current  $i_o$ , so that is where a current flows in a MOS transistor, and that has to be the output current of our circuit. So, this current flows from drain to source. Now, what we do in order to realize a current controlled current source, we have to compare the  $i_o$  the output current to  $i_i$ . And if  $i_o > i_i$ , we have to reduce  $v_{gs}$ ; and if  $i_o < i_i$ , we have to increase  $v_{gs}$ . Now, eventually the output current of this block must be

connected to a load, so the current flows from drain to source, we could connect the load to one of these terminals, and do this comparison at the other terminal.

Now, if you have been kind of following closely and you recall what we have done in earlier lecture, you see that we have actually done this already. What we are saying is that the drain current of the MOS transistor  $i_d$  here let me rename this  $i_d$ , we want to make it equal to  $i_d$  or  $i_o=i_i$ . Now, where have we done this before, we have made the drain bias current of a MOS transistor equal to the given current  $i_o$ , that we have already done. So, we have done it for the sake of biasing, now we will do it for signals. Now, it turns out that the most convenient way of doing it for signals is to essentially copy the source feedback biasing.

What do we do here, we had a certain drain current  $I_D$ , and we want to make it equal to a given current source let me call it just to not confuse with other  $i_o$ , let me call this  $I_1$ , we want it to make  $I_D=I_1$ , we connected these two together, so that the difference flows into a parasitic capacitor. And if  $I_D$  is more than  $I_1$ , it increases the source voltage, thereby reducing the value of  $I_D$ . The gate is connected to a fixed voltage. And if  $I_D$  is less than  $I_1$ , current will be drawn out of the capacitor, the source voltage will fall down,  $V_{GS}$  will increase and the current will increase. Now, this is a convenient way of doing it with signals as well.

So, what we have to do, the drain current of the MOS transistor is flowing like that. And we connect our desired current, in this case, it is the input current, so we call it  $i_i$  there. So, what happens, we have  $i_i$  over here, and  $i_d$  over there; the gate is connected to small signal ground. Here it is connected to some fixed voltage, but in this case, we just connect it to ground. Now, what happens, you can imagine exactly the same thing happening as earlier, you can imagine a parasitic capacitance here, and this difference  $i_d - i_i$  will flow into that one. And what happens if initially  $i_d$  was too small, then this current will be negative, so current will be pulled out of  $C_p$ , the source voltage will fall down,  $v_{gs}$  will increase and  $i_d$  will increase. And exactly the opposite happens if  $i_d$  is too large.

Now,  $i_d$  is flowing from drain to source, so we can use the part that is flowing out of the drain to connect it to a load, that is a load and for illustration you can imagine that it is a resistance, so that is all that is there to it. In this case, I did not discuss this scheme in too much detail, but making the output current or drain current of a transistor to a given current  $i_i$ , we already done it before for the sake of biasing. Here we have made this total current  $I_D$  equal to this given current  $I_1$ .

Now, what applies for total current definitely applies for incremental currents and we used exactly the same scheme. The negative feedback action must be pretty obvious by looking at how much current flows into this  $C_p$  and it depends on the difference  $i_d - i_i$ . So, this is our current buffer or current controlled current source; or at least this is our attempt at getting one such block. Now, you can see that in steady state, no currents flow through the capacitor and all of these  $i_i$  will flow through here. What it really means is that  $v_{gs}$  will adjust itself so that the current flowing here  $g_m$  times  $v_{gs}$  equals  $i_i$ . Now, we can analyze it further to see whether it really does that and also to see what its input and output resistances are.