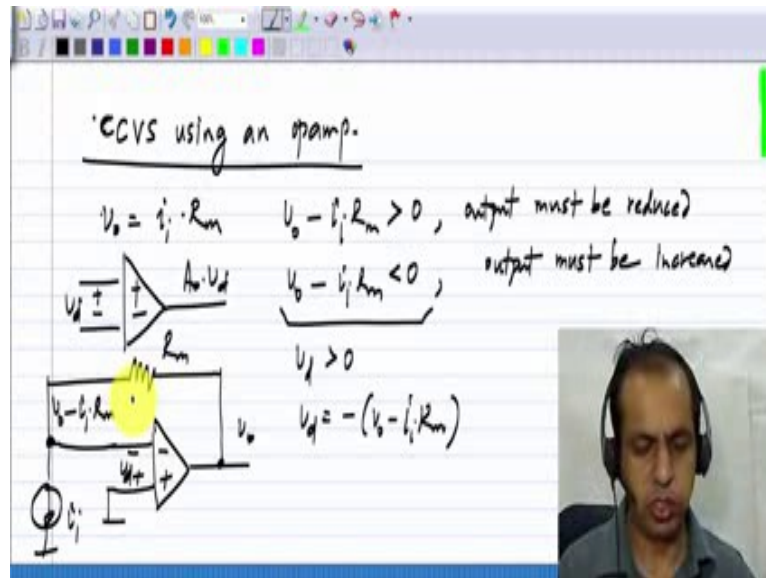


**Analog Circuits**  
**Prof. Nagendra Krishnapura**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Module - 06**

**Lecture – 06**

(Reference time: 00:09)



Now, we will implement a current controlled voltage source using an op amp which is modeled as a voltage controlled voltage source. A current controlled voltage source obeys the relationship output voltage  $V_o = (i_i * R_m)$ , which is the trans resistance or trans impedance of the current controlled voltage source. Just like in the case of current controlled voltage source using a MOS transistor, we define an error voltage  $V_o - (i_i * R_m)$ . And if this happens to be more than zero it means that the output voltage is higher than what is desired. The output must be reduced. And similarly, if this is less than zero, output must be increased.

If you consider an op amp, which we model as a voltage controlled voltage source, there is the input voltage difference  $V_d$ , and the output is some  $A_o * V_d$ , and  $A_o$  is the large number or you would like it to be a large number. Now, how does this work, if  $V_d$  is positive, the output will be driven to a large positive value; if  $V_d$  is negative, it will be driven to large negative value so that means that to reduce the output voltage, you have to make  $V_d$  more negative that is we have to reduce  $V_d$  or we have to make it more negative than what it currently is. And similarly, to increase the output  $V_d$  must be made more positive. Now, here you see that if the

error voltage  $V_o - (i_i * R_m)$  is less than zero, the output must be increased. So, putting the two together, you see that when  $V_o - (i_i * R_m)$  less than zero,  $V_d$  must actually be greater than zero;  $V_d$  is the input difference voltage of the op amp with the signs define like this.

So, if this is the output voltage, and this is  $V_d$ , I would like  $V_d$  to be  $-(V_o - (i_i * R_m))$  so that the action described here can happen. If  $V_d = -(V_o - (i_i * R_m))$  what happens is that when  $V_d < 0$ , the output will be further reduce to negative values, so that is not what you want. So,  $V_d$  has to be equal to  $-(V_o - (i_i * R_m))$ . Now how do we obtain this  $-(V_o - (i_i * R_m))$ ; just like  $V_d$  in the case of the transistor current controlled voltage source, if this is the output node, and this is the input current source then if I connect  $R_m$  like that the voltage here will be  $(V_o - (i_i * R_m))$ . And we want that to be equal to  $-V_d$ . So, convenient way to do that is you connected to this ground and connect it here. So, now, you can see that  $-V_d$  equals  $(V_o - (i_i * R_m))$ .

(Refer, slide Time: 04:03)

CCVS using an opamp:

$$\frac{V_o}{i_i} = \frac{R_m}{1 + \frac{1}{A_o}} \approx R_m \text{ if } A_o \rightarrow \infty$$


$V_o = A_o V_d$   
 $i_d = \frac{V_o}{A_o}$   
 $V_o - i_i R_m = -V_d = \frac{V_o}{A_o}$

So, a current controlled voltage source using an op amp, it looks like this. So, this is  $V_o$ , this is  $R_m$  and this is  $i_i$ . Of course, the input source can have an internal resistance  $R_s$ . Now the op amp is modelled as a voltage controlled voltage source that means that if this voltage is  $V_d$ , the output voltage  $V_o$  is  $A_o * V_d$ . Let us analyse what exactly we get from this. And for simplicity, I will not include  $R_s$ , but you can include it and analyse it and see what you get out of it.

In this case, we know that this  $V_d$  here, this voltage has to be  $(V_o - (i_i * R_m))$ , because this current has to flow into the resistance nothing goes into the op amp. We assumes that the

input resistance of the op amp itself is infinite. So, now, this is equal to  $-V_d$  and from this we can see that  $V_d = V_o / A_o$  which is  $V_o / A_o$ . From this, we see that  $V_o / i_i$  equals  $(R_m / (1 + (1 / A_o)))$ . Now, this is the desired ratio between the output voltage and the input current and we have something extra in the denominator, but the denominator reduces to unity and this ratio goes to  $R_m$ , if  $A_o \rightarrow \infty$ . If the gain of the op amp is infinite then we get exactly what we want. So, this is the current controlled voltage source using an op amp.

(Refer Slide Time: 06:39)

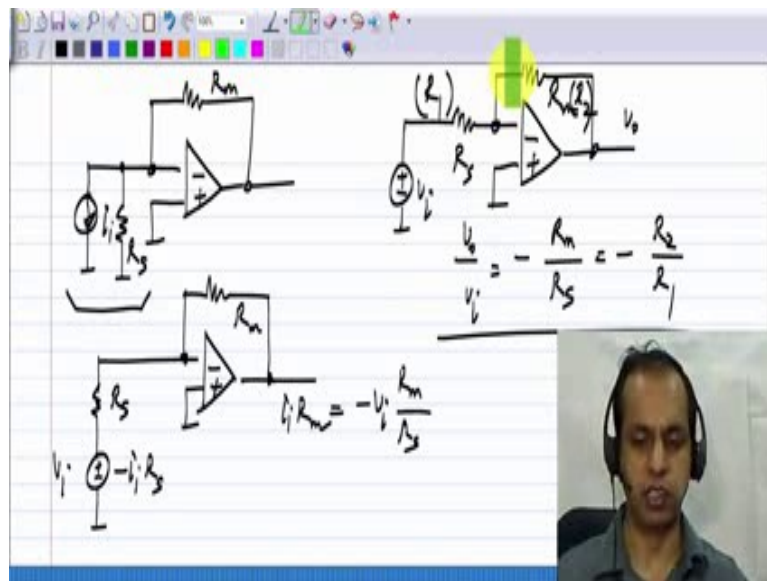


Now, just like in many other current controlled devices, many times such a device is used actually with a voltage input that is imagine that we had the current controlled voltage source  $R_m$ , and this is the source resistance  $R_s$ . We can convert the parallel combination into a series combination of  $R_s$  and a voltage which is  $-i_i R_s$ , and this drives current controlled voltage source. Now, once we have the circuit, we can forget that we ever started from a current source; we can just think of this as the voltage source  $V_i$ . And draw it like this, where we have some resistance  $R_s$  in series with input source. Now, we can forget about the factor this was the internal resistance of the current source. We have some voltage source, and we have resistance here in series and we have some resistance  $R_m$  over there. The output voltage here is  $i_i * R_m$  which can also be written as  $-V_i * (R_m / R_s)$ .

So, if this is  $V_o$ ,  $V_o / V_i$  will be  $-(R_m / R_s)$ . Of course, usually these are not denoted  $R_m$  and  $R_s$  if you are not using them as a trans impedance amplifier. We just call them  $R_1$ ,  $R_2$  in that case they become  $-(R_2 / R_1)$ . So, this is nothing but a current controlled voltage source driven by

a series combination of voltage source and resistor. Many times it is use like that. In this case, you do see that a gain depends on  $R_s$ , which is in series with voltage source. This is not a voltage controlled voltage source, because in a voltage controlled voltage source the gain  $V_o/V_i$  should not depend on the internal resistance of  $V_i$ . Now for instance, if there is another resistance here that appears in series with this and the gain will depends on that resistance. So, this is the current controlled voltage source driven by a voltage source in series with its internal resistance.

(Refer Slide Time: 09:24)

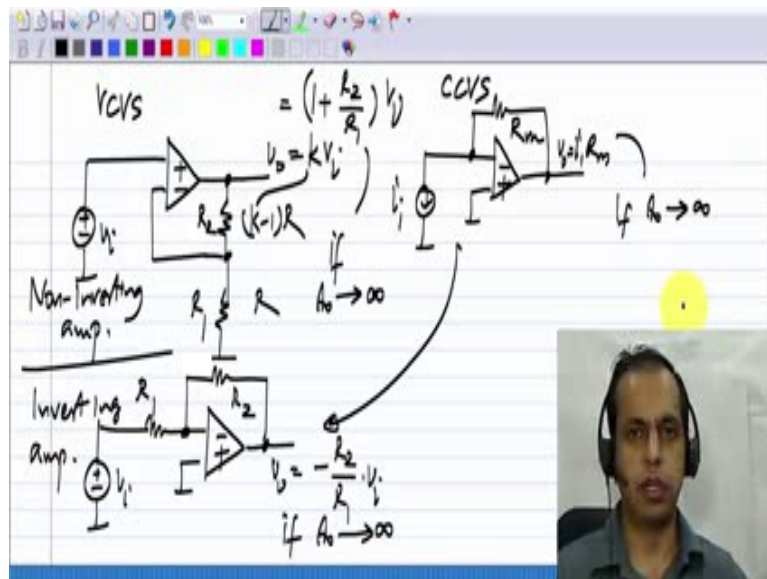

So, now we have seen two circuits - voltage controlled voltage source using an op amp which looks like this, and the current controlled voltage source using an op amp which looks like that. And in case of voltage controlled voltage source, the output will be exactly  $k * V_i$ ; where this  $k$  is given by the resistor ratio. If this is  $(K - 1)*R$  and  $R$ ,  $K$  is what appears there. or , if you call these  $R_2$  and  $R_1$ , this will be  $( 1 + ( R_2 / R_1 ) ) * V_i$ . In this case, the output voltage will be  $i_i * R_m$ ; now these are true if the gain of the op amp goes to infinity.

So, an op amp whose gain is infinity, it is known an ideal op amp. And in case of an ideal op amp, the gain of this will be  $( 1 + ( R_2 / R_1 ) )$ , the gain of this will be  $R_m$ . And a variant of this which can be driven with voltage source is  $V_i R_1 R_2$ . Here the output will be  $( R_2 / R_1 ) * V_i$ , if the gain of op amp is infinite. Now of course, these two circuits are very likely very familiar to you and they are nothing but the classic non inverting amplifier, and the inverting amplifier, so that is how we can realise control sources using an op amp as well. So, we can

also realise control sources using an op amp; we have seen how to make a voltage controlled voltage source as well as the current controlled voltage source.