


Digital IC Design
Prof. Janakiraman Viraraghavan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture - 25
NMOS Transistor ON Resistance and Fall Delay

So, the idea is we have derived equations for the currents of the transistor, we know how the transistor behaves with various voltages and stuff like that that is fine. But, how are we going to use this transistor, invariably we are going to only use this transistor either to charge a capacitor or discharge a capacitor.

This entire course is all about that how fast you can charge the capacitor, how fast you can discharge the capacitor right. This capacitance can be because of its own parasitic capacitance like, I will discuss today or it can be because of a load capacitance right, so I have a capacitance discharging.

(Refer Slide Time: 00:51)

 

So, if I have an a logic inverter driving a load capacitance right this inverter is going to either charge this capacitor or discharge this capacitor, and the delay of the gate is determined by how fast this action can happen ok. So, I also told you that delay is defined as the time it takes for the input to go to 50 percent right from there till the time the output reaches 50 percent ok.

So, if this is my $V_{DD}/2$ and this also is $V_{DD}/2$, then the delay of the gate is defined exactly as this delay ok, this is the delay and we want to estimate this ok. So, the simplified picture is we have a capacitor C_L and an n mos is going to discharge it, we will see why and n mos cannot charge the capacitor or a p mos cannot discharge a capacitor we look at it later ok.

But for now let us just look at this picture, the capacitor is charged V_C of 0 minus equals V_{DD} . So, this inverter is going to now discharge the capacitor through an n mos transistor ok. So, this voltage V_{naught} is going to fall from V_{DD} to $V_{DD}/2$, because of the delay

definition that is why $V_{DD}/2$ is a very sacrosanct number, I am not worried about taking it all the way to 0 ok.

Now, we have to make some assumptions to simplify our analysis otherwise it becomes very difficult. So, if for example, you the input is going to rise slowly like this, then that delay becomes a little hard to handle right. If it becomes a ramp function then I have to see when the delayed when the device turns on when it goes into linear, saturation all that it's it is very painful to do that. So, we have to make some approximations to get a first order number and then we will incorporate this input see also later on.

So, the assumption we are going to make is the input rises instantaneously to V_{DD} ok, 0 to V_{DD} instantaneous ok. So, if at 0 plus the gate is at V_{DD} my v_{out} is also at V_{DD} right and 0 plus just after write down it on in what region of operation will my transistor be in saturation region or velocity saturation right. Because V_{GS} is equal to V_{DD} ; obviously, V_{DS} has to be greater than $V_{GS} - V_T$ you are removing some quantity from there therefore, the transistor is in saturation region ok.


So, the currents look like this I_D and this is V_{naught} , so right this is my points where it is V_{DD} . This is V_{DD} and somewhere here is $V_{DD}/2$, I am assuming V_{DD} is large enough such that it is to the right $V_{DD}/2$ is to the right of $V_{DD}/2$ $V_{D SAT}$ ok. So, that I do not have to deal with a change in region of operation ok, so this is an assumption.

So, what is the equation of the current I_{DS} ? Let us say its velocity saturated it is $K_n' W/L$ into $V_{D SAT}$ n into V . What is V_{GS} ? V_{DD} right $V_{DD} - V_{Tn} - V_{D SAT}$ n by 2 into 1 plus λV_{naught} . Suppose is a long channel device then this would be in saturation where this would just be $K_n' W/L$ $V_{GS} - V_T$ $V_{DD} - V_T$ is the whole square ok.

So, let me not worry about all that I will just write this as I_{naught} into 1 plus λV_{naught} ok. Whether it is velocity saturated or not or it is in saturation I_{naught} is independent of V_{naught} that is the only thing I am worried about ok. So, now just look at the picture the

V_{naught} is coming down, its being the capacitors discharging right V_{naught} is just the voltage across the capacitor and the voltage is coming down.

(Refer Slide Time: 06:46)
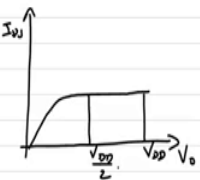
$$\begin{aligned}
 R(V_0) &= \frac{V_0}{I_0(1+\lambda V_0)} \\
 R_{eq} &= \frac{1}{(V_f - V_i)} \int_{V_i}^{V_f} R(V_0) dV_0 \sim \frac{1}{(-V_{DD}/2)} \int_{V_{DD}}^{V_{DD}/2} \frac{V_0}{I_0} (1 - \lambda V_0) dV_0 \\
 &= \frac{1}{I_0} \cdot \frac{2}{V_{DD}} \int_{V_{DD}}^{V_{DD}/2} V_0 (1 - \lambda V_0) dV_0 \\
 &= \frac{3}{4} \frac{V_{DD}}{I_0} - \frac{1}{12} \frac{\lambda V_{DD}^2}{I_0} \\
 \Rightarrow R_{eq} &= \frac{3}{4} \frac{V_{DD}}{I_0} \quad (\text{if } \lambda = 0)
 \end{aligned}$$


So, if you look at the resistance, it now becomes a function of V_{naught} ok, so last class somebody asked me why do not you do a derivative out here. See in analog it is to do a derivative because, you fix your bias somewhere here and then you will do some sort of a small signal analysis over that bias point.

So, in some sense we have linearized this whole thing here, so when you do a Taylor series there you going to take a derivative and then you expand it in terms of the input variables. So, therefore, you take derivatives there, but here I am actually discharging it from V_{DD} to V_{DD} by 2 it such a large range right.

So, I cannot do that small signal also taking derivative here, I have to find some other way of finding the resistance average resistance, now which is a function of v_{naught} right. So, R of V_{naught} is simply what V_{naught} by I_{naught} into $1 + \lambda V_{naught}$. Now, I have a function f of x that is going from a to b , I want to find what is the average value, what do you do you just integrate and divide by the x_2 minus x_1 right that is all I am doing here.

So, I am saying that $R_{equivalent}$ is defined as V_{final} minus $V_{initial}$ into $V_{initial}$ to V_{final} of R of V_{naught} d V_{naught} that is my that is what I am defining as the average resistance ok. So, this I will now write as minus V_{DD} by 2, because V_f is V_{DD} by 2 V_i is V_{DD} . And, so I am going to write this as V_{DD} to V_{DD} by 2 into V_{naught} by I_{naught} write that $1 + \lambda v_{naught}$ I am going to write as a Taylor series because λ is very small ok. I can expand this approximately as $1 - \lambda V_{naught}$ ok, maybe I should put an approximate here d V_{naught} .

Of course, now I_{naught} is a constant, so I will just write into 2 by V_{DD} into V_{naught} into $1 - \lambda V_{naught}$ d V_{naught} right. So, what did we get the answer here you solve the integration and you just get what $\frac{3}{4} V_{DD}$ by I_{naught} minus $\frac{7}{12} \lambda$ into V_{DD} squared by I_{naught} right this is what we got fine.


So, if it is going to have channel length modulation then this is the only way you can do it, because there is a variation of resistance all through because of that $1 + \lambda V_{naught}$ right. So, now, the interesting thing is if it is a long channel device, then λ is equal to 0 ok.

So, implies $R_{equivalent}$ is $\frac{3}{4} V_{DD}$ by I_{naught} is λ equal to 0 ok. So, the point I was trying to make last time is we found an equivalent R right, why are we finding equivalent R ? Because, I can now treat this as an RC discharge and I can evaluate delays in terms of the time constant of that RC network ok. But, if λ equal to 0 then this is just like a constant current source discharging my capacitor, why is it a constant current source? Because, there is no dependence on V_{naught} .

Now, if λ equal to 0 the current basically just becomes a I_D versus V_{naught} ; this simply become the flat line and this is my region of operation from V_{DD} to $V_{DD} - 2V_{th}$ ok. And of course, now I do not have to worry about V_{Dsat} , because this will always be in this thing you know you have to still worry about it.

You have to make sure the V_{th} is above some number below some number for it to be in saturation region all through ok, so assume V_{DD} is high enough there is no problem. So, this is now like a constant current source discharging the capacitor ok, so we did the same calculation in method 2.

(Refer Slide Time: 11:59)

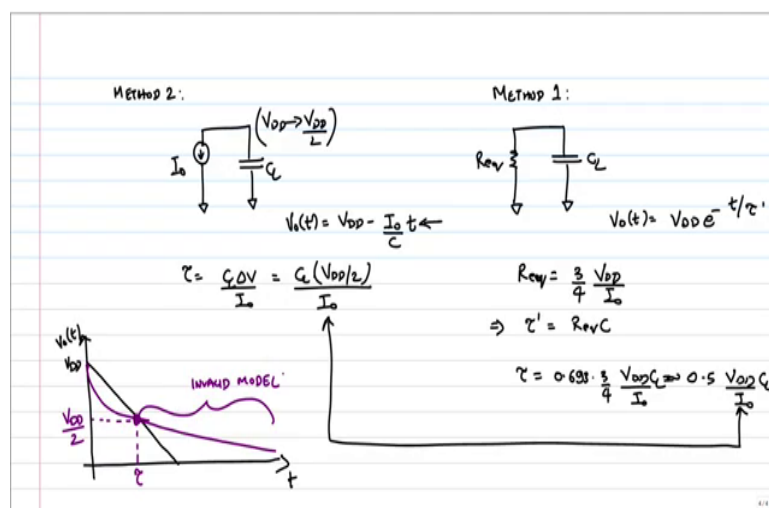

So, it is a constant current source discharging my capacitor; method 1 is you had a thing like this R_{eq} equivalent into and C_L . Now, what is the time it is going to take two and what is this current is I_{naught} by the way if λ equal to 0 this current is just I_{naught} . What is the

time it is going to take to discharge from V_{DD} to $V_{DD}/2$? If it is a constant current source discharge $C \Delta V$ by I right.

So, the time is $C \Delta V$ by I naught C_L right, C_L into $V_{DD}/2$ divided by I naught. Here the R equivalent was $3/4 V_{DD}$ by I naught which implies that the time constant of this RC network right let me call it τ_{prime} is R equivalent into C . Now, the delay of this thing to come from V_{DD} to $V_{DD}/2$ is 0.693 times the time constant, so this is 0.693 into $3/4 V_{DD}$ by I naught right.

So, this is approximately again we will get 0.5 1 or 5 2 or something like that, I naught into C_L , now these two answers indeed do match right. Now; obviously, if λ is 0 then the constant current source model is the right model, because the transistor is a current source ok. So, if you look at the model that we are using for delay ok. This guy is if you look at this V naught of t it will start from V_{DD} and then go linearly right.

What is this? $C dV/dt$ equal to I , so I naught by C into t whereas, this guy if you see V naught of t this $V_{DD} e^{-t/\tau_{prime}}$. So, the 2 models actually follow different equations with respect to time, but this one is more accurate ok. So, if you look at V naught of t versus t , you have a straight line like this for method 2, the method 1 is going to look like this asymptotically it will go down to this thing.

So, this is my delay τ and this is $V_{DD}/2$, so the two models give the same answer at that particular instant of time, any other instant the two models are different right. The delays are the same, question why do you why do we even want to do it to the resistance method? One is of course; if there is channel length modulation then this current source thing fails.

I have to now if you can of course; solve this from first principles by saying that I equal to $\mu C_{ox} W (V_{GS} - V_{th}) V_{DS}$ minus $C dV/dt$. And use the equation of the you know make I dependent on V and solve the differential equation then its fine. Otherwise I need to do it through this resistance method which is a reasonable approximation; because all I am worried about is that delay act when it comes to V_{DD} , this is the only point of interest in this model for me.

So, if you ask me which is better it does really does not matter right, and I also pointed out that beyond this both the models are actually not valid. Because when it drops below V_{DD} by 2 and eventually goes below $V_{D\text{sat}}$, the transistors goes into a linear region of operation right and there the equation itself changes.

So, when I do that resistance calculation it will go into a different region of operation altogether. So, that is not even worth sort of going through all the way down to 0 with that equation because it is not of interest to us ok. So, beyond this invalid model, the reason I am pointing this out is you will see that we use certain models in this course which are valid only in certain regions of operation.

Outside that region of operation if you ask me what the value of the model is I would say I do not care, because the model is not even meant to handle that region of operation that is the point I am trying to drive home here. Any questions? So, the other thing is of course, later when I start putting transistors in series or in parallel. Then I it is very easy for me to reduce that network using series parallel resistance combinations if I know R equivalent current source model I cannot do that. Any questions here? Ok.

(Refer Slide Time: 18:00)


$$R_{eq} = \frac{3}{4} \frac{V_{DD}}{I_0}$$

$$I_0 = \begin{cases} K_n' \frac{W}{L} V_{DSAT} n \left[(V_{DD} - V_{TN}) - \frac{V_{DSAT} n}{2} \right] & \text{velocity saturation (SC)} \\ \frac{1}{2} K_n' \frac{W}{L} (V_{DD} - V_T)^2 & \text{SAT (LONG)} \end{cases}$$

$$R_{eq} \propto \frac{1}{W}$$

if V_{DD} LARGE ie $V_{DD} - V_{TN} - \frac{V_{DSAT} n}{2} \sim V_{DD}$

R_{eq} not a fn of V_{DD}



So, let us look at this equation a little more closely R_{eq} equivalent is 3 by 4, I leave out this lambda parameter I naught ok. If it is velocity saturated then I naught is equal to $K_n' W$ by $L V_{DSAT} n$ into $V_{DD} - V_{TN} - V_{DSAT} n$ by 2 ok. If it is a long channel device and it enters saturation region then it is just $K_n' W$ by L into $V_{DD} - V_T$ whole squared and half right.

This is saturation velocity saturation it does not matter, so this is a long device this is a short channel device ok. So, look at this equation of R_{eq} equivalent now right, clearly it is going to be inversely proportional to W 1 over W , because I naught is sitting below right. So, therefore, if I double the width of a transistor then the resistance of the transistor drops by a factor of 2 right, or the resistance becomes 50; 50 percent of what it was earlier.

So, this is one key technique that we will use if you want to reduce your resistance then you up size the transistor and that is what this equation is also telling us right. Now, what happens if V_{DD} is very large? Suppose V_{DD} is very large such that $V_{DD} \text{ minus } V_{Tn} \text{ minus } V_{D \text{ SAT } n}$ by 3 right or V_{DD} is very large compared to V_t then what will happen? Yeah? If its velocity saturated and V_{DD} is very large what happens to the $R_{\text{equivalent}}$ as a function of V_{DD} . Yeah?

But there is also an inverse dependence on $1 \text{ by } V_{DD} \text{ minus } V_{Tn} \text{ minus } V_{D \text{ SAT } n}$ no. So, if we are V_{DD} is large right, what does large mean? That is $V_{DD} \text{ minus } V_{Tn} \text{ minus } V_{D \text{ SAT } n}$ by 2 is nearly V_{DD} right. This is just a first order thing, this show you that $R_{\text{equivalent}}$ then is not a function of V_{DD} .

So, if I have a 180 nanometer device and I operate it from one you know 1.8 volt down to 1.5 volt, then the $R_{\text{equivalent}}$ will not change much there ok. On the other hand if your V_{DD} is very small, then of course; these things cannot be neglected and that has a more complicated relationship with V_{DD} . In this course we are going to deal only with higher V_{DD} s, we are not going to bring down the V_{DD} close to suppress hold or even low voltage operations ok.