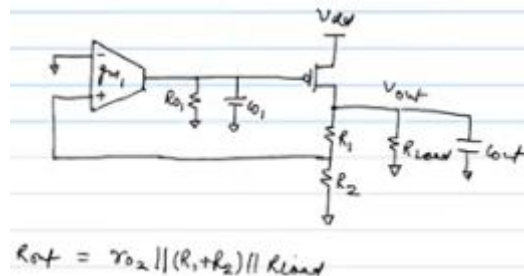


Power Management Integrated Circuits
Dr. Qadeer Ahmad Khan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 24
Line Regulation and PSRR of PMOS LDO

- Line Regulation is the ratio of small-signal changes in V_{out} to small-signal changes in V_{dd} at DC.

$$\text{Line Regulation (dc)} = \frac{\partial V_{out}}{\partial V_{dd}}$$



- The line regulation of the PMOS LDO is $1/(\beta g_{m1} R_{o1})$, i.e. the line regulation depends on the feedback factor β and on the gain of the error amplifier $g_{m1} R_{o1}$. It is independent of the gain of the output stage.
- Assuming that the error amplifier pole $\omega_{p1} = 1/(R_{o1} C_{o1})$ is dominant, the capacitor C_{out} can be neglected while finding the PSRR at frequencies $\omega < \omega_{ugb}$ since $\omega_{p2} = 1/(R_{out} C_{out})$ lies beyond ω_{ugb} .
- Approximate expression of the PSRR at frequencies $\omega < \omega_{ugb}$:

$$\omega_{p1} = \frac{1}{R_{o1} C_{o1}}$$

$$\& A_0 = g_{m1} R_{o1} g_{m2} R_{o2}$$

$$L A (dc) = \beta A_0$$

$$\frac{V_{out}(s)}{V_{dd}(s)} = \frac{1}{\beta g_{m1} R_{o1}} \frac{1 + s/\omega_{p1}}{1 + s/\beta A_0 \omega_{p1}}$$