

Power Management Integrated Circuits
Dr. Qadeer Ahmad Khan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture - 32
Introduction to Switching Regulators

So, so far we looked at linear regulators or LDOs, where we know that your control signal is an analog signal V_{CTRL} . The difference between switching regulator and linear regulator is that here the control is the duty cycle which is a basically a pulse-width modulated signal which regulates your output.

(Refer Slide Time: 00:41)



Switching Regulators

- works on the principle of Pulse Width Modulation (PWM)
- offers higher efficiency across wide V_{out}/V_{in} range
- can buck (step down), boost (step-up) or invert input power supply

V_{in} → Switching Regulator → V_{out}

- $V_{out} < V_{in}$
- $V_{out} > V_{in}$
- $V_{out} < 0$ (negative or inverting)



So, it works on the principle of Pulse Width Modulation or PWM. And, this we already looked at, that it offers higher efficiency across wide V_{out} over V_{in} range, ok. Can buck, which is nothing but step-down, boost, step-up or invert input power supply, which means, if we have a switching regulator and if this is your V_{dd} and this is your V_{out} . Means V_{out} could be less than V_{dd} , V_{out} could be greater than V_{dd} or V_{out} could be less than 0, which is negative or inverting.

(Refer Slide Time: 03:47)

NPTEL

1.2.4.4.4

→ $V_{ref} < V_{ref}$

→ $V_{ref} > V_{ref}$

→ $V_{ref} < 0$ (negative or inverting)

If 3dB cutoff of LFF is $\ll \frac{1}{T_{on}}$
then all harmonics are filtered out and we get only DC component of V_{ref}

EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of Electrical Engineering, IIT Madras

So, how does it work? So, let us say if I have this PWM signal with the period of let us say T_{sw} and I call this T_{on} and this is T_{off} . If you take the Fourier transform of this, how will it look like, spectrum? What all components you will have?

A sine you will have, but how will you plot it on frequency? If this is your frequency and this is your amplitude, what is the first component it will have?

It will have a DC component. So, so, let me draw. So, your 1 over ... then and so on. So, which one will be the significant? DC will be the significant component. And, rest of the harmonics will have a smaller component so, it may be like this. In fact, some of them might be more than the, so, odd or even harmonics if you look at, it's not necessary that it will keep decreasing, but it depends on your duty cycle actually. So, the expression is not straightforward here, when you take the Fourier transform of a triangular signal or any other or the Fourier series when you look at it. So, and if it is a perfect square wave then it will have only odd component. But, if it's duty cycle is not uniform then we will have both odd and even. So, what am I interested in? Output.

What output I would like to have? I want a DC ok. So, which means if I have a filter, very low bandwidth filter, which is a cutoff, which means if this is your low-pass filter. So, if 3 dB

cutoff of LPF is much much less than $1/T_{sw}$, then all harmonics are filtered out and we get only DC component at V_{out} ok.

(Refer Slide Time: 08:14)

NPTEL Integrated Circuits and Systems Group, Department of EE, IIT Madras

LPF

$V_{out} = \frac{T_m}{T_{sw}} \times V_{dd} = D \cdot V_{dd}$

LPF

V_d R C V_{out} I_{load}

$R \gg T_{sw}$

$T_{sw} = 1\text{ms}$

R should be much smaller to supply higher load current

$R = 100\text{m}\Omega$

$I_{load} = 1\text{A}$

Which means, if this is your LPF which will have something like this, this is your PWM signal and this is V_{out} . So, what do you get here? So, DC with very small ripple, ok. How do we implement this filter? And what, by the way, what is the DC component? V_{out} equal to.

So, that will be the average value of that. So, average of that will be T_{on} over T_{sw} multiplied by V_{dd} , which is nothing but duty cycle times V_{dd} . So, how do you implement this filter? What could be the possible ways of implementing this filter?

RC? Ok, let us see RC. In this, RC time constant is much much larger than T_{sw} . So, this is your V_{dd} , this is your V_{out} . Now, I have a load here, what will be the drop here?

I_{load} ; I_{load} into R which means what is V_{out} ? V_{dd} minus I_{load} into R and D times basically ... correct. So now, let us say, what should be the value of this resistor? What will be the value of this resistor?

Student: T_{sw} by C .

No, but you are putting a load here and that is driving load. How can you make it, so let us say you put a one even 1 ohm you put, 1 amp you draw, 1 volt is directly dropped at resistor

output. If we keep increasing that R, you will not get anything at the output, everything will get dropped at our resistor.

So, if now let us take an example. So, let us say your T sw is 1 microsecond; so, which means R should be much smaller to supply higher load current. So, let us say R you make 100 milliohm, I load is 1 amp.

(Refer Slide Time: 12:48)

NPTEL

R should be much smaller to supply higher load current

$R = 100\text{m}\Omega$

$I_{\text{load}} = 1\text{A}$

ICS

EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

$RC = 10 \times T_{\text{sw}}$

$C = \frac{10 \times 1\mu\text{s}}{0.1} = 100\mu\text{F}$

So, you will drop only 100 millivolt which is ok. Now see, let us say you want RC time constant, let us say I want 10 times of T sw; let us calculate the value of C. 10 into 1 micro over 0.1. What is this value?

100 microfarad and even this 10 times I am considering, it is on the lower side actually, usually you would like to have time constant even much larger, so that your ripple can further reduce. So, 100 microfarad is not a small cap, it is a huge cap actually. So, it is not feasible to implement with RC because it will require a very large cap which is not practical actually. So, what else can we do?

(Refer Slide Time: 14:12)

NPTEL

EE6069 POWER MANAGEMENT INTEGRATED CIRCUITS
Integrated Circuits and Systems Group, Department of EE, IIT Madras

$RC = 10 \times T_{sw}$

$C = \frac{10 \times 1\mu}{0.1} = 100\mu F$

RC filter is not practical due to large C
so we use LC filter

$V_{out} = D \cdot V_{dd}$

ideally L is lossless


So, RC filter is not practical due to large C ok. So, what do we do? So, we use LC filter. So, ideally L is lossless. So, you will not drop anything, when you draw the load, I load. So, V out equal to D times V dd. So, there are two advantages here; one is to reduce losses and for the same ripple your value of C required will be much smaller because it is a second order filter ok.

So, you get minus 40 dB per decade instead of minus 20 dB per decade like in RC. So, it gives a second order filter and order of microhenry will give you a much better time constant or you can say your cutoff will be much lower. So, now, let us so, let us see if I can derive this V out equal to D times V dd. So, let us go with this principle.

(Refer Slide Time: 16:37)



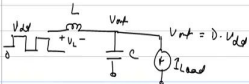... from the previous slide to design C
So we use LC filter



ideally L is lossless

$$V_L = L \frac{dI_L}{dt}$$


$$\Delta I_L = \frac{1}{L} V_L \times dt$$

$$\Delta I_L = \frac{1}{L} V_L dt$$

during T_{on}

$$\Delta I_L = \frac{V_{dd} - V_{out}}{L} \times T_{on} \quad (\text{slope} = \frac{V_{dd} - V_{out}}{L})$$

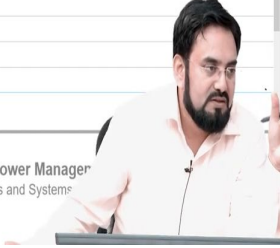
EE5325 Power Manager
Integrated Circuits and Systems



So, V_L equal to, so if this is plus minus V_L this is V_{out} . So, V_L equals $L \frac{dI_L}{dt}$. So, if I want to find the small signal current, what will be that? What will be the small signal current?

So, $\frac{1}{L} V_L \times dt$ ok, correct, I am looking at a small signal. So, if I look at delta component only; so can I write ΔI_L equal to $\frac{1}{L} V_L dt$. So, during T_{on} your ΔI_L will be, what is what is the voltage across your inductor?

V_{dd} minus V_{out} over L multiplied T_{on} . So, this is your current slope. So, this is the slope at which your current will rise and depending upon for how long it is on, that will define your peak. During off time.

(Refer Slide Time: 18:42)




NPTEL

EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

$$\Delta I_L = \frac{V_{out}(1-D)}{L} \times T_{sw}$$
 adding off time

$$\Delta I_L = -\frac{V_{out}}{L} T_{off}$$


$$= -\frac{V_{out}}{L} (1-D) T_{sw}$$

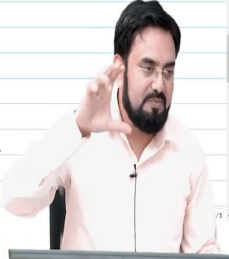

Minus V_{out} over V_L into T_{off} correct. And, let, yeah, wait let us fix it. So, this one ΔI_L can I write like this? $V_{dd} (1-D)$ over L , ok. So, you take V_{dd} common. V_{out} by V_{dd} is nothing but D , duty cycle and T_{on} is.

Duty cycle times T_{sw} , ok, and this one can be written as ... over L into $1-D$, correct, because T_{on} plus T_{off} over T is nothing but ... it is one, so you just break that. So, your D , sorry, the T_{off} will be $1-D$ times T_{sw} , if T_{on} is D times T_{sw} . Now, if you replace this V_{out} by D times V_{dd} , the ripple amount, the peak current will remain the same in both cases ok. So, whether you use this formula, using V_{out} or using V_{in} , ultimately your ΔI_L or peak-to-peak ripple current would remain the same.

(Refer Slide Time: 21:09)

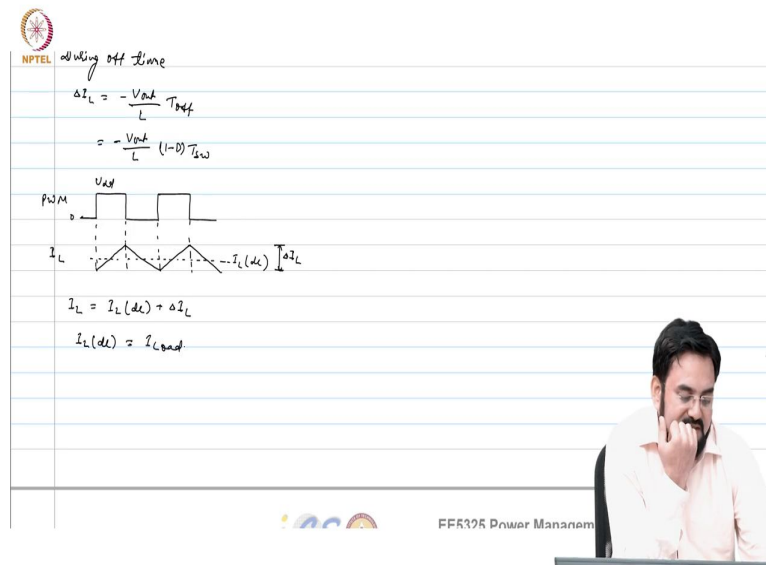

So, if you want to draw the current waveform, if this is going 0 to V_{dd} , if this is your PWM signal, then your I_L or inductor current will look like this and this will be nothing, but I_L DC. So, what you have and this is your ΔI_L . So, your inductor current consists of I_L DC plus ΔI_L and I_L DC is nothing, but I_{load} ok. So, your average current, inductor average current will be same as your load current if your output is constant. So, in the steady-state, your inductor current will settle to I_{load} and output will settle to D times V_{dd} .