

Power Management Integrated Circuits
Dr. Qadeer Ahmad Khan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture - 47

Stability Analysis of Voltage-Mode Buck Converter - Part 2

⑤ LC filter

$$H_{LC}(s) = \frac{V_O(s)}{V_{SW}(s)}$$

$$\frac{V_O}{V_{SW}} = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{Y_2 Z_1 + 1} = \frac{1}{\left(sC + \frac{1}{R_{load}}\right)(sL + R_{loss}) + 1}$$

5. LC filter :

The circuit of the LC filter is in the above image. The input and output of the LC filter are V_{SW} and V_O respectively. R_{LOSS} is the combined resistance of the switches and inductor resistance. The transfer function of the LC filter will be :

$$H_{LC}(s) = \frac{V_O(s)}{V_{SW}(s)}$$

$$= \frac{1}{s^2 LC + R_{loss} C s + \frac{L}{R_{load}} s + \frac{R_{loss}}{R_{load}} + 1}$$

$$= \frac{1/LC}{s^2 + s \left(\frac{R_{loss}}{L} + \frac{1}{R_{load} C} \right) + \left(\frac{R_{loss}}{R_{load}} + 1 \right) \frac{1}{LC}}$$

$$R_{loss} \ll R_{load}$$

$$H_{LC}(s) = \frac{1/LC}{s^2 + s \left(\frac{R_{loss}}{L} + \frac{1}{R_{load} C} \right) + \frac{1}{LC}}$$

The final transfer function of the LC filter will be (derivation is shown in the above images) :

$$H_{LC}(s) = \frac{1/LC}{s^2 + s \left(\frac{R_{LOSS}}{L} + \frac{1}{R_{LOAD} C} \right) + \frac{1}{LC} \left(1 + \frac{R_{LOSS}}{R_{LOAD}} \right)}$$

Assuming $R_{LOSS} \ll R_{LOAD}$ then we can approximate above transfer function as :

$$H_{LC}(s) = \frac{1/LC}{s^2 + s \left(\frac{R_{LOSS}}{L} + \frac{1}{R_{LOAD} C} \right) + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$


$$\frac{\omega_0}{Q_0} = \frac{R_{loss}}{L} + \frac{1}{R_{load} C}$$

$$Q_0 = \frac{\omega_0}{\frac{R_{loss}}{L} + \frac{1}{R_{load} C}} = \frac{1/\sqrt{LC}}{\frac{C R_{loss} + L/R_{load}}{LC}}$$

The above equation is the standard second-order low pass filter.

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
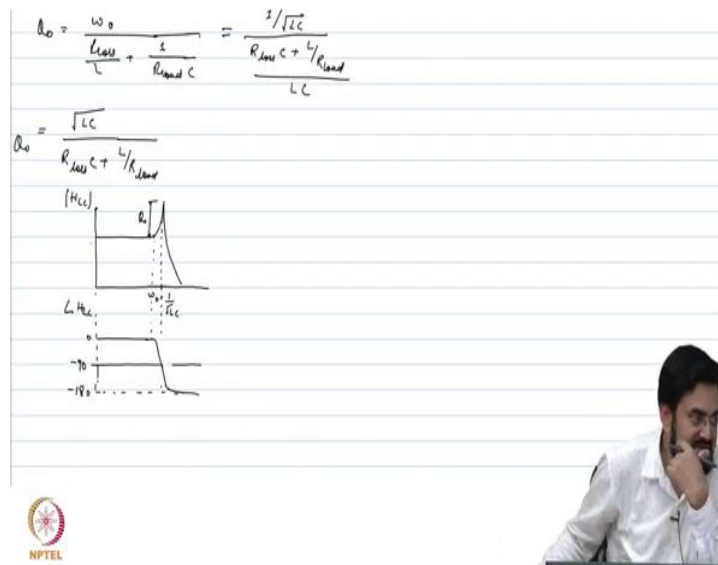
$$Q_0 = \frac{\omega_0}{\frac{R_{LOSS}}{L} + \frac{1}{R_{LOAD}C}}$$



After substituting the value of ω_0 in Q_0 , we get:

$$Q_0 = \frac{\sqrt{LC}}{R_{LOSS}C + \frac{L}{R_{LOAD}}}$$

The magnitude plot of H_{LC} will look like a second-order low pass filter and will have a peaking of magnitude Q_0 at ω_0 . The phase will fall very sharply from 0° to 180° around ω_0 because of a very high Q . So the worst-case condition for phase shift will be for maximum Q . Q is maximum at no-load condition.

At no load, R_{LOAD} will be infinity. So, we can assume that the R_{LOAD} term in the denominator of Q_0 zero.

$$Q_{0-max} = \frac{\sqrt{LC}}{R_{LOSS}C} = \frac{1}{R_{LOSS}} \sqrt{\frac{L}{C}}$$


There is a trade-off here in between efficiency and stability because if we are looking for higher efficiency, we have to reduce R_{LOSS} but then Q_{0-max} will increase and phase shift will be very sharp at ω_0 .

We know that as long as the product of L and C remains constant then ripple voltage will not change. Q_{0-max} will reduce when we choose smaller L and larger C and we will also get a better transient response. Poles will be near $j\omega$ when we have a high value of Q in a second-order system and we will get more ringing in the output.

no. of poles when $R_{load} = \infty$ (no load)

$$Q_{o, max} = \frac{\sqrt{LC}}{R_{load}C} = \frac{s}{R_{load}} \sqrt{\frac{L}{C}}$$

Small Signal Model of a buck converter

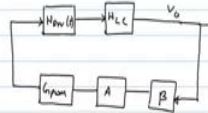

The diagram shows a small-signal model of a buck converter. It consists of a forward path with two blocks in series: H_{MVA} and H_{LC} , followed by the output voltage V_o . The feedback path consists of three blocks in series: G_{FB} , A , and B , which are connected back to the input of the H_{MVA} block.

 NPTEL



The small-signal model of the buck converter is shown in the above image.