

Power Management Integrated Circuits
Dr. Qadeer Ahmad Khan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture – 83
Tri-Mode Buck-Boost Converter (Buck, Buck-Boost and Boost)

(Refer Slide Time: 00:16)



For $V_o < V_{dd}$
 $D < 0.5 \rightarrow$ Buck Mode

For $V_o = V_{dd}$
 $D = 0.5 \rightarrow$ Buck-Boost

For $V_o > V_{dd}$
 $D > 0.5 \rightarrow$ Boost

$D = 0.4$

$V_o = \frac{0.4}{0.6} V_{dd} = 0.67 V_{dd}$

$I_L = \frac{I_{load}}{1-D} = \frac{I_{load}}{0.6} = 1.67 I_{load}$

controlling S_1, S_2 & S_3, S_4 : with single PWM is not efficient
 $(I_L = \frac{I_{load}}{1-D})$

So we need to control S_1, S_2 and S_3, S_4 independently

$S_1, S_2 \rightarrow$ D buck

$S_3, S_4 \rightarrow$ D boost



So, controlling S_1, S_2 and S_3, S_4 with a single PWM is not efficient. Why not sufficient? Because I_L is equal to I_{load} over 1 minus D . So the current will always be higher than load no matter whether you operate in buck or boost. So, we need to control S_1, S_2 independently, I will call it D buck; S_3, S_4 , D boost.

Now, what will be the expression? V_{out} equal to D buck over 1 minus D boost into V_{dd} . Now, if I want V_{out} equal to V_{dd} , what will be the D buck and D boost? You can have infinite combinations, correct.


0.5 , we can make both; then again you will end up having the same thing which you had earlier. Now if I make D buck equal to 0.9 and D boost equal to 0.1 then V_{out} equal to V_{dd} . What is the inductor current I_L ? How much? 1 over 1 minus 0.1 , pretty close to 1.1 ; I_{load} only a 10 percent increase. In the other case, it was a $2x$ increase. So, how do we control this?

So, there are three modes and this is called tri-mode buck-boost. Instead of operating all the four switches simultaneously, we operate them based on in which region we are ok.

(Refer Slide Time: 03:41)



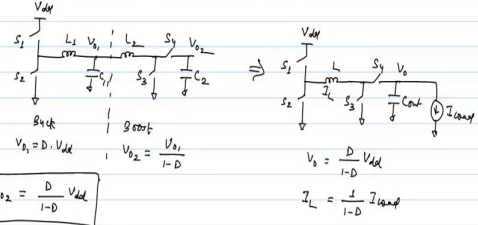$V_o = V_{dd}$
 $Buck-Boost = Buck + Boost$



$V_{b1} = D \cdot V_{dd}$
 $V_{b2} = \frac{V_{b1}}{1-D}$
 $V_o = \frac{D}{1-D} V_{dd}$
 $I_L = \frac{I_{load}}{1-D}$


EE5325 Power Management
Integrated Circuits and Systems Group

So, we divide them in three regions: buck mode, buck-boost mode and boost mode. Tell me what will be the states of the switches in buck mode? You have the circuit here, let me copy it. What will be the state of the switches?

(Refer Slide Time: 04:17)



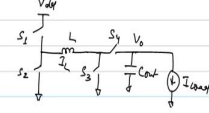$D_{buck} = 0.9$ & $D_{boost} = 0.1$
 $V_o = V_{dd}$
 $I_L = \frac{1}{1-0.1} I_{load} \approx 1.1 I_{load} \rightarrow \text{more efficient.}$



Tri-Mode Buck-Boost


Buck Mode ($V_o < V_{dd}$)	Buck-Boost Mode ($V_o = V_{dd}$)	Boost Mode
$S_3 = OFF, S_4 = ON$	$S_1 = ON, S_2 = OFF$	$S_1 = ON, S_2 = OFF$
$S_1, S_3 \rightarrow PWM_{buck}$	$S_3, S_4 \rightarrow PWM_{boost}$	$S_3, S_4 \rightarrow PWM_{boost}$
$D = D_{buck}$	$V_o = \frac{D_{buck}}{1-D_{boost}} V_{dd}$	$V_o = \frac{V_{dd}}{1-D_{boost}}$

EE5325 Power Management
Integrated Circuits and Systems Group

All 4 switches will be operating in buck-boost mode. So, in this case your V_{out} is D buck times V_{dd} . So, $S1$ $S2$ will be PWM buck. $S3$ $S4$ will be PWM boost. V_{out} will be D buck over $1 - D$ boost V_{dd} . What about this case?

$S1$ is always on; $S2$ is always off. Now, it is looking like a conventional boost converter where $S3$ $S4$ is PWM boost and your V_{out} is V_{dd} over $1 - D$ boost ok. So, how do we decide when to enter which mode? So, we always define maximum and minimum duty cycle.

(Refer Slide Time: 07:40)

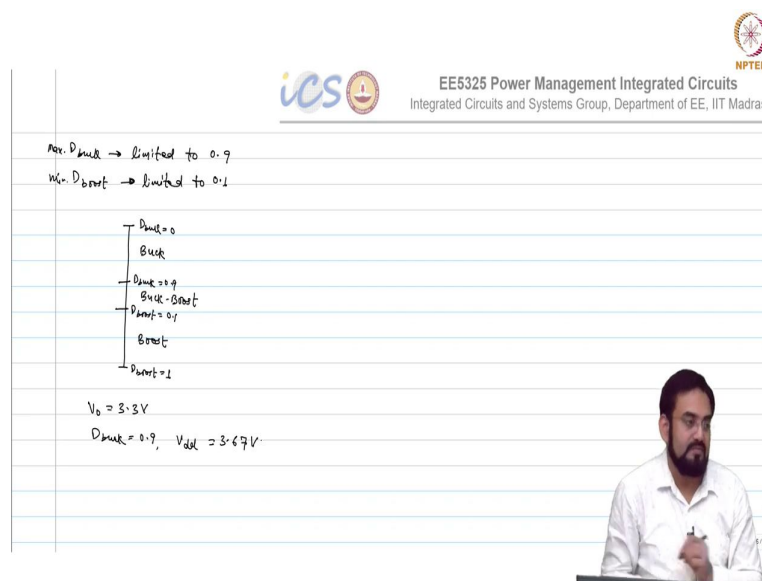

ICS NPTEL EE5325 Power Management Integrated Circuits
Integrated Circuits and Systems Group, Department of EE, IIT Madras

Max. $D_{buck} \rightarrow$ limited to 0.9
Min. $D_{boost} \rightarrow$ limited to 0.1

$D_{buck} = 0$
 Buck
 $D_{buck} = 0.9$
 Buck-Boost
 $D_{boost} = 0.1$
 Boost
 $D_{boost} = 1$

$V_o = 3.3V$
 $D_{buck} = 0.9, V_{dd} = 3.67V$

So, when you hit the boundary let us say my D_{buck} is limited to 0.9 D_{buck} max and minimum d_{boost} is limited to 0.1 ok. So, you do not really need to look at the output because this duty cycle may vary for the same output depending upon the losses.

So, output will not tell you exactly the same thing. Let us say you have no load condition under load condition, the duty cycle will be different for the same output. So, in reality you have to look at the duty cycle when it is saturating. So, now, you have. So, this is let us say D_{buck} equal to 0.9, D_{boost} equal to 0.1 ok; D_{boost} equal to 1 and D_{buck} equal to 0. So, this is your buck region.

Now the duty cycle is saturated to 0.9 ok. When the duty cycle is saturated to 0.9, then you have no option, but to enter buck boost and here boost. So, why can't we enter directly from buck to boost? Can we do that?

What will happen to the output? What is the output in case of 0.9 D buck 0.9? Let us forget about the losses, just ideal condition. What is the output in case of D boost 0.1?

Roughly 20 percent increase in the output. So, let us say I am operating at so, let us let us take an example. Let us say V_{dd} equal to 5 volt. So, and sorry, V_{out} equal to let us say 1.2 volt and D is 0.9, D buck 0.9. So, what will be the V_{dd} ? $1.2 / 0.9$. How much or let me take a better example? Because, the devices you are using are 1.8 volt. So, input hardly changes. So, most of the input when it is changing you will see with the battery voltage; lithium-ion battery.

So, let us take the example of a lithium-ion battery. So, let us say my this is 3.3 volt and no so, what is the V_{dd} here or battery voltage? $3.3 / 0.9$ which is 3.67 correct. Now I am going directly from here to 10 percent. So, your V_{dd} is not changing. Let us say you are operating at V_{dd} equal to 3.6 volt, my output is very well regulated at 3.3 volt. My duty cycle is saturated. Now I directly jump to boost ok.

(Refer Slide Time: 14:28)



Min. $D_{boost} \rightarrow$ limited to 0.1

$D_{buck} = 0$
 Buck
 $D_{buck} = 0.9$
 Buck-Boost
 $D_{boost} = 0.1$
 Boost
 $D_{boost} = 1$

$V_o = 3.3V$

$D_{buck} = 0.9, V_{dd} = 3.67V$

Boost Mode

Min $D_{boost} = 0.1, V_o = \frac{3.67}{1-0.1} = 4.07V$



So, boost mode D boost. This is the minimum duty cycle; I cannot achieve less than this. So, I have to operate at 0.1 ok. So, what will be the V_{out} ? Because my V_{dd} is not changing. 4 volt ok. So, your output will jump to 4 volt from 3.3 volt which is a difference of 700 millivolt. Let us say you have a feedback loop and everything ok. The feedback will try to recover ok, but how will the feedback recover? In this case, you have a boost mode; so, it will go to the buck mode again and it will go back and forth and ultimately you will get a large ripple in the output. So, it does not make sense to jump directly to boost mode, but to go to buck-boost first.