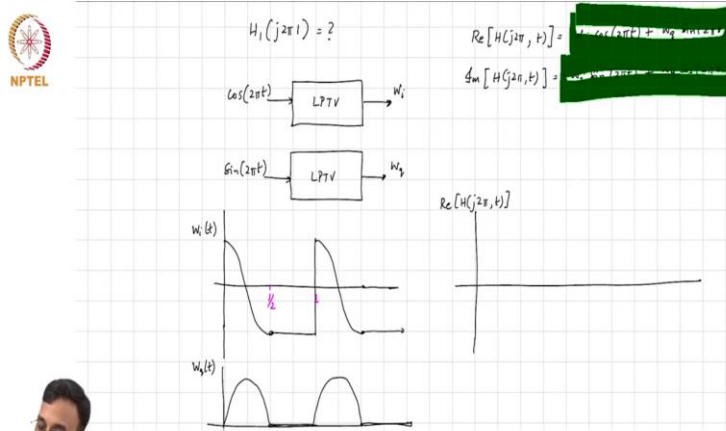


Introduction to Time-Varying Electrical Networks
Professor Shanthi Pavan
Department of Electrical Engineering
Indian Institute of Technology, Madras
Lecture 40
Analysis of an example LPTV Network- part 2

(Refer Slide Time: 00:16)



And the question is what do we do about H say 1 of $j 2 \pi 1$? How do we figure this out? Which there are I do not should I give a \cos or should I give \sin or should I give both? What is the meaning of giving what is j ? It is something imaginary. So, we have already covered this extensively in class; so we do two experiments. So, we have this our unknown system, and we give $\cos 2 \pi t$; you call this W_i . And then you have $\sin 2 \pi t$, you get W_q ; and what is real part of H of $j 2 \pi f$ comma t ? Is nothing but W_i times. Real part of H is?

Student: (())(02:03)

Professor: W_i times $\cos 2 \pi f_s$ times t or by $2 \pi f_s$ times t ; because I am in this case, I am exciting the input with the I am exciting the system with an input at f_s . Does make sense? So, this is $\cos W_i$ times, so f_s is 1 ; so, $\cos 2 \pi t$ plus plus $W_q \sin 2 \pi t$. And imaginary part of H is W ; W what? $i \sin 2 \pi t$ minus $W_q \cos 2 \pi t$. I am sure this is correct and not look back into your notes is correct; minus must be here and plus must be here. How do so this will because our

system is LPTV, what you when you plot this waveform; what do you expect to see? What kind of waveform?

You should get this is nothing, but the gain experienced by the sinusoid. So, the waveforms that you see for real and imaginary part of H will be periodic; and they will be periodic with what frequency? f_s . And is that because the input is fed at f_s , so what; the input also happens to be at f_s . The even if the input was an arbitrary frequency; you will find that these two will be periodic with f_s .

And that is because the system is varying with the frequency f_s ; so, so now let us actually do it. So, if we put $\cos 2\pi f_s t$, how will W_i look like? Let us assume that the g of t is like this; it is very high 0 . So, and this goes from 0 to sorry this is half a second I guess right now sorry $2\pi f_s$; this is half a second, this is one second. Yes, so can you please help me plot W_i of t .

Student: () (05:44)


Professor: It follows.

Student: Follows the $\cos 2\pi f_s t$.

Professor: Very good, so basically it starts here, it follows you would assume that this is cosine. I am going to get rid of this to reduce clutter and then what happens? Then here the capacity. The switch is open remains flat then what happens again? Does this, remains flat and so on. And what comment can you make about W_q of t ?

Multiply this by; this is \sin during half cycle becomes 0 , \sin becomes 0 and so on. But this is not this is not the job done; what do we need to do? To find the real part of H of $j 2\pi$ comma t . What do we do? We need to multiply W_i by $\cos 2\pi f_s t$, which is multiplying W_i by the same waveform. And W_q by W_q by $\sin 2\pi f_s t$; so, what do you think we will have in the first quadrant in the first half second?

(Refer Slide Time: 07:54)

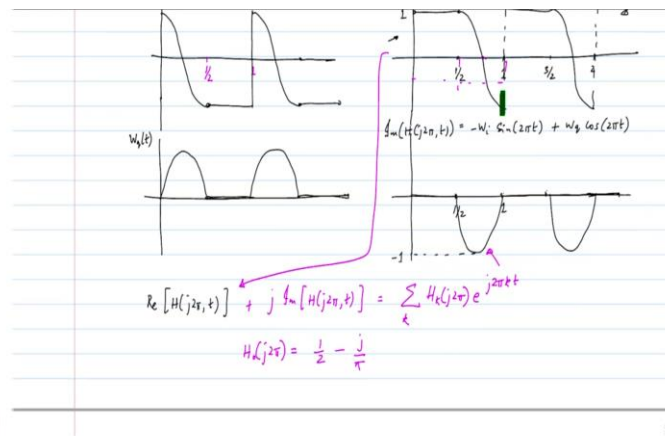


It is nothing but when in the in the first half a second, you have cos square t plus sin square t, sine square 2 pi t. And therefore, that is going to be 1 and what about in the region half to 1? So, W_i times cos. W_q is 0 anyway, so we do not worry about it; so, what happens what comment can we make about this guy now? Minus cos 2 pi. So, that how will that look? That will look like this; that make sense folks; and then again it gets back to, like sense people. And what comment can you make about the imaginary part? Which is minus W_i sin 2 pi t plus W_q cos 2 pi t; all this look like.

So, W_i into sin plus W_q into cos that will simply be 0. In half to 1, it will be W_i is minus 1 will be sin. It is the sorry this this was minus W_i sin 2 pi; so sorry is it negative. So, it is minus W_i cos 2 pi sin 2 pi t, plus W_q cos 2 pi t; and of course, W_q is 0, this in this part. So, W_i is minus 1 minus W_i is 1, so in this it should be.

So, remember this real part of H of j 2 pi comma t is is this waveform here; and you expand this as a fourier series. And you will get some if you do this plus j imaginary H of j 2 pi comma t; what you will get is sigma over k H_k of j 2 pi, e to the j 2 pi k times t. So, H I am sorry I think I have goofed, so basically H_0 of j 2 pi is nothing but the dc value of of these waveforms. And what should H_0 be therefore? dc by the real part is is half; and dc value of the imaginary part is half minus j by pi. So, let us see if that makes sense.

(Refer Slide Time: 13:31)

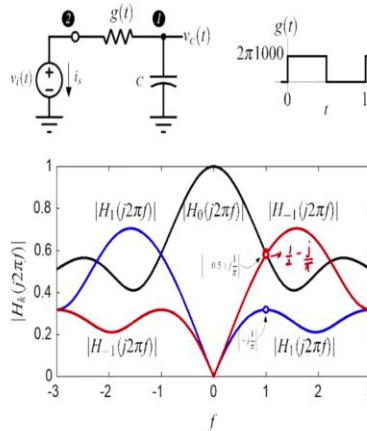

So, it is this is this value here, it happens to be half minus j by π . Now, H so the magnitude is what you call? Square root of one fourth plus one by π square. Now, the next thing I would like to draw your attention to the following.