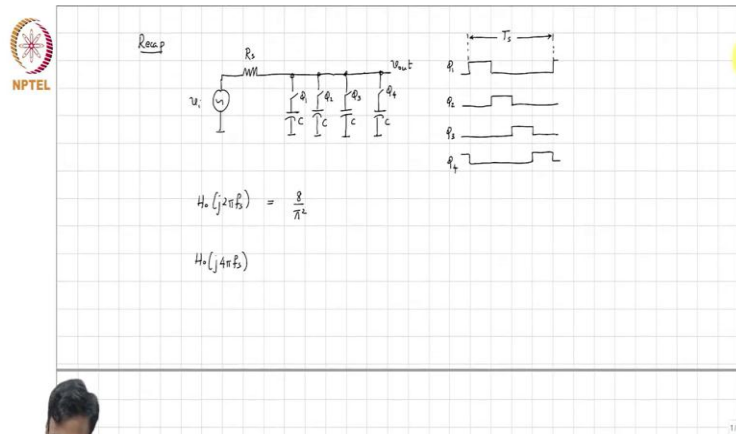


Introduction to Time - Varying Electrical Networks
Professor Shanthi Pavan
Department of Electrical Engineering
Indian Institute of Technology Madras
Lecture 53
Computing $H_0(j2\pi f_s)$ for a 4-path filter


(Refer Slide Time: 0:20)



A quick recap of what we were doing yesterday, we were looking at what is called N-path filter example of which, so you have four identical capacitors and these are the clock waveforms and this is T_s , this is a 25 percent each one of these clocks this is ϕ_1 , ϕ_2 , ϕ_3 and ϕ_4 , each one of these waveforms is a 25 percent intuitive cycle clock.

And we were yesterday we spent a lot of time and figure out what H_0 of $j2\pi f_s$ was and we found that that is equal to 8 by π^2 . Today let us continue and try and figure out what is H_0 of $j4\pi f_s$ which is the zeroth order harmonic transfer function at when the input frequency is $2f_s$ when it is twice the input the switching frequency.

(Refer Slide Time: 3:31)



$w_i(t) = 0$

$\cos(4\pi f_s t)$

R_s

$\frac{1}{C}$ $\frac{1}{C}$ $\frac{1}{C}$ $\frac{1}{C}$

ϕ_1 ϕ_2 ϕ_3 ϕ_4

0 0 0 0

T_s

$R_c [H_c(j2\pi 2f_s)] = \text{Av} \{ W_i \cos(4\pi f_s t) + W_q \sin(4\pi f_s t) \}$

$= \text{Av} \{ W_q \sin(4\pi f_s t) \} = \frac{A}{\pi^2}$

$H_c(j4\pi f_s) = \frac{A}{\pi^2}$

$W_q \sin(4\pi f_s t)$ $\text{Period} = \frac{T_s}{4}$

$\int_{-T_s/4}^{T_s/4} W_q \sin(4\pi f_s t) dt = 0 \rightarrow \text{Period} = \frac{T_s}{4}$

$w_q(t)$

$\sin(4\pi f_s t)$

R_s

$\frac{1}{C}$ $\frac{1}{C}$ $\frac{1}{C}$ $\frac{1}{C}$

ϕ_1 ϕ_2 ϕ_3 ϕ_4

$\frac{2}{\pi}$ $-\frac{2}{\pi}$ $\frac{2}{\pi}$ $-\frac{2}{\pi}$

T_s

$W_i \cos(4\pi f_s t)$

$\int_{-T_s/4}^{T_s/4} W_i \cos(4\pi f_s t) dt = 0 \rightarrow \text{Period} = \frac{T_s}{4}$

So, to do that let me copy this over, as usual we put in $\cos 2\pi$; $\cos 4\pi f_s$ times t and $\sin 4\pi f_s$ times t this is w_i of t and this is w_q of t . And what are the voltages on this capacitor? Well the, if you have an input which is at twice the switching frequency then in one quarter of the clock period you basically have one half of the input cycle, then, so this is T_s , so this is $\cos \omega t$.

So, during the first capacitor is going to average out this part of the waveform and therefore the average here is going to be 0, second capacitor is going to average out that part of the waveform and so therefore that is going to be 0, and similarly the third capacitor and the fourth capacitor all will have 0 voltage across them, so w_i of t is 0.

Remember w_i of t is simply the voltage across the first capacitor during ϕ_1 , the second capacitor during ϕ_2 and so on and therefore w_i of t is 0. What comment can we make about w_q of t ? Well, that is T_s , so that is a $\sin 4\pi f_s t$, the first capacitor is going to average this part of the waveform and that is therefore going to be 2 by π , the second one is going to do, is going to have a voltage which is, so this I am going to mark the voltages down, so this voltage will be 2 by π , this will be minus 2 by π , this will be plus 2 by π and this will be minus 2 by π .

And remember H the real part of H_0 of $j 2\pi$ times $2 f_s$ times t , I am sorry is simply the average value of $w_i \cos 4\pi f_s$ times t , w plus $w_q \sin 4\pi f_s$ times t , which therefore w_i being 0 is nothing but the average value of $w_q \sin 4\pi f_s$ times. So, w_q is going to be a waveform like this, so it is 2 by π minus 2 by π so this is T_s .

And so $W_q \sin 4 \pi f_s \text{ times } t$ is going to be, is going to be this, this and therefore what comment can we make about the average? So, this is $2 \text{ by } \pi$ actually I made a small error, 4 multiply by \sin , this should be, so what should, what would be the average value of that waveform? $4 \text{ by } \pi \text{ square}$ and one thing that is apparent is that this waveform is periodic with respect, what is the period of this $W_q \sin 4 \pi f_s$?

The period is, period is $T_s \text{ by } 4$ which makes sense because this is a, we knew already that it is an LPTV system and with 4 paths and therefore even though the switching frequency is f_s it behaves like an LPTV system with switching frequency $4 f_s$. Now, what comment can we make about the imaginary part of, this is simply the average value of $W_q \cos 4 \pi f_s \text{ times } t$ minus $W_i \sin 4 \pi f_s \text{ times } t$, this we know to be 0 , so this is nothing but the average value of $W_q \cos 4 \pi f_s \text{ times } t$.

And what, how will that look like? So, we know W_q is like this, if we plot $W_q \text{ times } \cos 4 \pi f_s \text{ times } t$. Well, this is going to be a something like that, the second half is going to be something like that, and therefore what comment can we make about the average, of the blue waveform is 0 . Again, we notice that the period is $T_s \text{ by } 4$. So, $H_{\text{sub } 0} \text{ of } j 4 \pi f_s$ is nothing but $4 \text{ over } \pi \text{ square}$.

And so it turns out, I mean then similarly you can go and do it for all integral multiples of f_s and it will turn out that there will be peaks in the transfer function at multiples of, integer multiples of f_s . So, at f_s you have a peak, at $2f_s$ you have a peak, at $3f_s$ you have a peak and so on. And what comment can you make about the peak at, the magnitude of the gain at $4f_s$ versus, at $2f_s$ versus f_s ?

At f_s the gain was $8 \text{ by } \pi \text{ square}$, at $2f_s$ it is $4 \text{ by } \pi \text{ square}$ and likewise it turns out that at higher and higher frequencies, intuitively that makes sense because as frequencies get higher and higher what will happen is that you will be averaging out the sinusoid over what, I mean over $T_s \text{ by } 4$, over period $T_s \text{ by } 4$, but there you will have larger and larger number of integral number of cycles, so only the fractional cycle is what you will, which is what will remain. And therefore, its value will keep decreasing, and.