

**Analog Electronic Circuits**  
**Prof. Shanthi Pavan**  
**Department of Electrical Engineering**  
**Indian Institute of Technology, Madras**

**Lecture - 22**  
**Negative Feedback Continued**

(Refer Slide Time: 00:18)

Lecture 11

$$\frac{V_o}{V_i} = \frac{1}{F} \frac{Lg}{1+Lg} \quad Lg = Af$$

$$\frac{V_e}{V_i} = \frac{1}{1+Lg}$$

Alright people, good evening and welcome to Analog Electronic Circuits. This is lecture 11. So, in the last class we were looking at the basic negative feedback loop where you have a feedback block, forward amplifier, this is  $V_i$  this is  $V_o$ . And we set that,

$$\frac{V_o}{V_{in}} = \frac{1}{f} \frac{Af}{1+Af}$$

where, this loop gain is  $Af$  and is physically interpreted as the gain that you get when you break open the loop.

You know excite one side and see what comes back on the other side and what comes back is  $Af$  in magnitude and must be in the opposite direction. The opposite direction is needed for negative feedback and as we said analogy for negative feedback is like the legal system in any country if the laws are strict and the implementation is strict, then people will tend to commit fewer crimes.

And so, if  $Af$ , the loop gain goes to infinity then the error voltage  $V_e/V_i$  is nothing but  $1/(1 + \text{loop gain})$ , again loop gain is  $Af$ . So, if loop gain tends to infinity, it basically means that the

error voltage is 0. So, again coming back to our social analogy, it basically means that if crime in society is 0, it does not mean that people are honest. It just means that the laws are so strict that the penalty for being dishonest is so high that you dare not commit a crime, alright. So, that is just like how the error voltage is 0.

The error voltage is 0 because the forward amplifier gain is infinite. The moment the amplifier gain becomes small that error voltage is no longer 0, alright. And under the condition that you have a very large loop gain, the closed loop gain which is  $V_o/V_i$  as you can see is largely independent of the loop gain itself correct and the closed loop gain is simply  $1/f$  and is governed by the feedback block, alright.

So, it turns out that this is a great way of realizing amplifiers with very stable gain. For example, let us say you wanted to realize a gain of 2. We already have seen a common source amplifier. Its gain is  $-g_m R_L$  and nothing prevents us from choosing  $R_L = 2/g_m$  so that you get a gain of -2, alright.

But what are the problems with this kind of amplifier? Well temperature changes,  $g_m$  will change which basically means that  $g_m R_L$  will change and so, therefore, this way of realizing gain is not robust. Now if we realize that using negative feedback if we wanted to realize a gain of two using a negative feedback loop what should  $f$  be?  $f$  should be half, correct. So, if  $f$  has to be half, what is the easiest way of getting  $f$  equal to half?

Student: basically, potential divider.

Yeah, just basically use a potential divider now if temperature varies what comment can you make about the values of the resistors? The values of the resistors will change, but these are we are looking for a resistor ratio and therefore, even though the individual resistance is changed both of them will change in the same manner and therefore, the ratio is very very robust even though the individual values of the resistances are not.

So, therefore, the situation boils down, because if we are able to realize a negative feedback loop with a large loop gain then all that we need to do to make the performance robust is make sure that the feedback block whatever it is, its properties are very well controlled. And fortunately if you want a closed loop gain then the feedback factor must be smaller than 1 which is easy to realize using some kind of passive element and the forward amplifiers gain which is needed to be very large. It will be realized using some kind of transistor network.

The transistors and networks of transistors as we will see going forward are very good at giving you a lot of gain, but that gain also changes a lot over temperature and supply voltage change and all that stuff. So, but fortunately as you can see thanks to negative feedback if that gain is large enough.

The sensitivity of the closed loop gain or the input output  $V_o/V_i$  to changes in the gain of the forward amplifier is actually very very low. For example, if the loop gain is a 1000 what is the closed loop gain its  $1/f \times 1000/1000$  and 1 which is  $1/f \times 0.999$ .

Now let us say the loop gain for some reason went down from 1000 to 500 that is either a 50 percent change. If you want to be conservative or it is a hundred percent change if you use a different denominator. You can see that you have a huge change in gain, but the closed loop gain is still  $1/f \times (500/501)$  which is only changes in the third decimal place.

So, a 100 percent change in the gain has only changed the closed loop gain by some point, something percent, alright. So, just like money, if you have enough of it then you do not have to worry about it, correct, just like that in a negative feedback loop if you have enough loop gain you do not have to worry about how much loop gain you have.

So, having seen that now let us put this principle to some use and see some of these are circuits that we are very very familiar with. And as we saw last time, it makes business sense to sell that part as a separate building block so that users can put their favourite feedback factor and get whatever gain they want, closed loop gain they want. And that is the operational amplifier, which is basically a voltage controlled voltage source whose gain is ideally infinity, but in reality it is a large number. It is not typically if you go and pick up an off the shelf op-amp. It is not uncommon to get a gain of maybe  $10^7$ ,  $10^8$  that sort of thing. So, if the op-amp is enclosed inside a negative feedback loop we saw that the error voltage must be 0.

So, the difference between the two input terminals of an op-amp must be 0 if it is enclosed inside a negative feedback loop, which is the virtual short that you are very familiar with. So, now, let's say you want a voltage amplifier with a gain of 2. What will we do? This is our op-amp. What do we do?

Well, that is very straightforward. We just identify just there at the block diagram we want a feedback block with a gain of?

Student: 1.

Half. So, you put R there, you put another R there. So, this is  $V_o$  and this is  $V_o/2$ , and this is  $V_i$ . So, if the op-amps gain is infinity then clearly this difference is 0. That basically means this is  $V_i$  which is the same as  $V_o$  by 0 which basically means that well the output is twice the input. This is all a very well known circuit from your childhood days. So, it is not something particularly new. Now, let's say you had never seen the circuit before and you wanted to figure out what the signs of the op-amp must be. So, what do you do? Well, you don't know the science. So, what do you do?

(Refer Slide Time: 10:50)

Lecture 11

$$\frac{V_o}{V_i} = \frac{1}{f} \cdot \frac{LG}{1 + LG} \quad LG = Af$$
$$\frac{V_o}{V_i} = \frac{1}{1 + LG}$$

You break the loop somewhere and you yank one side of the loop up here. So, what happens to this node here? What direction does it go? Let's assume some random signs like that. So, if this goes up, that goes up. If that goes up and for this choice of signs this also goes up and so, what comes back is of course, larger than what you put in, but is it in the?

Student: Same direction.

Same direction. So, therefore, this is?

Student: Positive feedback.

Positive feedback and therefore, that is not good as far as making a closed loop amplifier is concerned. So, what should we do?

(Refer Slide Time: 11:37)

The slide, titled "Lecture 11", features an NPTEL logo in the top right corner. It contains several diagrams and equations. At the top left, a feedback loop around an op-amp is circled in green. To its right are the equations:  $\frac{V_o}{V_i} = \frac{1}{f} \frac{Lg}{1+Lg}$  and  $Lg = Af$ . Below these are  $\frac{V_o}{V_i} = \frac{1}{1+Lg}$  and  $V_o = I_{in}R$ . On the left, there are two op-amp circuit diagrams: one with a feedback resistor and one with a feedback resistor and a load resistor. In the center, there is a circuit diagram showing a current source  $I_{in}$  in series with a resistor  $R$ , with the output voltage  $V_o$  across the resistor. To the right, there is a circuit diagram showing a current source  $I_{in}$  in series with a resistor  $R$  and a load resistor  $R_L$ , with the output voltage  $V_o$  across the load resistor.

Flip the signs on the op-amps. So, that becomes alright. So, now, let us do another example again, something that you are most likely to be familiar with. Let's say we want an output. We want to make a current controlled voltage source. So, let say we want  $V_o$ , that is some In times some number. So, it is a current control voltage source. So, controlling that proportionality factor will have dimensions of resistance.

So, that is basically what is often called a trans resistance amplifier. So, again we would like to use negative feedback. So, in principle what are we going to do? Let us say you are in a lab and you are given a current  $I_{in}$ . So, let us say you are given some current  $I_{in}$  and I need to generate  $I_{in}R$  what will I do? So, well one idea is to put a resistor here and this gives me?

Student:  $I_{in}R$ .

$I_{in}R$ , my job is done and what is the problem with this? Is this a current controlled voltage source? The test for a voltage source is that you change the load resistance and the output voltage should not?

Student: Should not change.

Should not change, correct? So, here the idea that we first had was to take that current pump to a resistor  $R$  to get this  $I_{in}R$ . We said now I am done, let me go home. So, is this a current control voltage source, why? Well, if I put a load resistor the voltage instead of being  $I_{in}R$  becomes  $I_{in} (R // R_L)$ . So, therefore, it is not a voltage source. So, that is no good. So, you are

in a lab now you have a current source  $I_{in}$  and I told you to produce a voltage  $I_{in}R$ . What will you need and how will we go about doing this? You have a variable voltage source. You want to make the fact that you have a voltage source with a knob alright. That already means that by definition whatever  $R_L$  you put the voltage will be whatever you put there, whatever voltage  $V_x$  is there, whatever  $R_L$  you put across it, the voltage will remain  $V_x$ . So, we have solved that part of the problem. So, you have a variable voltage source with the knob you have seen in the lab. Now I am telling you to make that voltage source equal to?

Student: R.

(Refer Slide Time: 14:53)

The slide, titled "Lecture 11", features an NPTEL logo in the top right corner. It contains several diagrams and equations:

- A feedback loop diagram of an op-amp with a voltage source  $V_o$  and a feedback resistor. A green circle highlights the feedback loop.
- The equation  $\frac{V_o}{V_i} = \frac{1}{f} \cdot \frac{LG}{1+LG}$  with  $LG = Af$ .
- The equation  $\frac{V_o}{V_i} = \frac{1}{1+LG}$ .
- Text: "If  $V_x > I_{in}R$ , must  $V_x \downarrow$ " and " $V_x < I_{in}R$ , must  $V_x \uparrow$ ".
- The equation  $V_o = I_{in}R$ .
- A circuit diagram showing a current source  $I_{in}$  connected to a resistor  $R$  and a load resistor  $R_L$ . A voltmeter  $V_1$  is connected across  $R$ , and another voltmeter  $V_x$  is connected across  $R_L$ .

In the bottom left corner, there is a video feed of a man in a pink shirt, likely the lecturer, looking at the camera.

$I_{in}R$ . So, what will I do? So, what you are telling me therefore, is you generate  $I_{in}R$  somehow and the easy way to generate is simply pump in the current into a resistor then generate that resistor that  $I_{in}R$ . Tell me clearly what I should do this is  $V_x$  there is  $I_{in}R$ . Now what do we do? You put a voltmeter here that is a voltmeter. So, you have to put another voltmeter here. So basically, you measure you compare  $V_x$  with  $V_1$  which is?

Student:  $I_{in}R$ .

$I_{in}R$ . If  $V_x$  is greater than  $I_{in}R$  it basically means that you must?

Student: Reduce the  $V_x$

Reduce  $V_x$ . If  $V_x$  is less than  $I_{in}R$ , you must?

Student: Must increase  $V$ .

Must increase  $V$ , alright and how will you increase  $V_x$ . You basically turn the knob this much you understand, clear? Is this basic idea clear to people? So, what are we comparing therefore? We are comparing two voltages  $V_x$  and?

Student:  $I_{in} R$ .

$I_{in} R$ . Eventually when you are done the output voltage  $V_x$  will be exactly equal to  $I_{in} R$  regardless of what  $R_L$  you put and therefore, this is a what kind of control source?

Student: Current controlled voltage source.

Now there is a slight problem in the sense that there are two volt meters. Can somebody think of getting rid of 1 volt meter? Yeah, well it is pretty straight forward. We are only not interested in the individual voltages.

$V_x$  and  $V_1$  are we only interested in?

Student: Difference.

Difference. So, then the next thing is to say we do not really need that stuff.

(Refer Slide Time: 18:03)

Lecture 11

$\frac{V_0}{V_1} = \frac{1}{f} \cdot \frac{Lg}{1+Lg}$   $Lg = Af$

$\frac{V_0}{V_1} = \frac{1}{1+Lg}$

If  $V_x > I_{in} R$ , must  $V_x \downarrow$   
If  $V_x < I_{in} R$ , must  $V_x \uparrow$

$V_0 = I_{in} R$

$V_x - I_{in} R$

We can just put a voltmeter between these two terms, does that make sense? So, we are comparing two voltages and what is the meaning of compare?

A comparing  $V_x$  and  $I_{in} R$ . So, the meaning of compare is finding the difference and what physical principle will you use to find the difference between two voltages?

Ok. If you want to compare two voltages, what physical principle will we use?

Student: KVL.

So, how will we subtract therefore, we therefore, need to find  $V_x - I_{in}R$ . So, can you tell me how we can find this quantity  $V_x - I_{in}R$ ?

(Refer Slide Time: 19:13)

Lecture 11

NPTEL

$$\frac{V_o}{V_i} = \frac{1}{1 + LG} \quad LG = Af$$

$$\frac{V_o}{V_i} = \frac{1}{1 + LG}$$

if  $V_x - I_{in}R > 0$ , must  $V_x \downarrow$   
if  $V_x - I_{in}R < 0$ , must  $V_x \uparrow$

$$V_o = I_{in}R$$

So, in other words, if  $V_x - I_{in} R$  is greater than 0, it means that  $V_x$  is too high and  $V_x$  must therefore, be reduced. And if  $V_x - I_{in}R$  is less than 0, it means that  $V_x$  is too small and must be increased, alright. So, now, how will I find this quantity?  $V_x - I_{in}R$ . So, in other words, I need to compare  $V_x - I_{in} R$  with 0, correct. So, any suggestions on how I can find  $V_x - I_{in}R$ ? How can I generate that voltage  $V_x - I_{in}R$ .

Yeah. So, basically you recognize that you simply connect a resistance  $R$  in at the output of  $V_x$  and then pull a current  $I_{in}$  like this. What is this potential?



Student:  $V_x - I_{in}R$  and if this potential is greater than 0, you must reduce  $V_x$ . If this potential is less than 0 we must increase  $V_x$ , is this clear? So, therefore,  $V_x$  is a voltage source which is controlled by voltage. What is  $V$ ? What are the dimensions of  $V_x - I_{in}R$ ?

Student: Voltage.

So, that  $V_x$  is controlled by another voltage and if we want that  $V_x - I_{in}R$  to be equal to 0. So, in other words even if we sense that this  $V_x - I_{in}R$  is infinitesimally greater than 0, what must we do? We must kick that  $V_x$  so, hard that it should go to 0. I mean  $V_x$  should be kicked so hard in the negative direction so that the error goes to 0. So, what comment can you make? So, this is clearly a voltage control voltage source and what is the gain of that voltage control voltage source? What should it be? What should it be? Even if you see an infinitesimally small voltage at  $V_x - I_{in}R$  as  $V_x - I_{in}R$ , you must kick the output voltage very hard. So, what does this mean? The gain must be?

Student: Infinite.

Infinite. What should be the sign of the gain? If  $V_x - I_{in}R$  is greater than 0,  $V_x$  must?

Student: Reduce.

Reduce. So, what must be the gain?

Student: Negative.

The sign of the gain must be negative.

(Refer Slide Time: 22:39)

Lecture 11

$\frac{V_o}{V_i} = \frac{1}{f} \frac{Lg}{1+Lg}$   $Lg = Af$

$\frac{V_o}{V_i} = \frac{1}{1+Lg}$

if  $V_x - I_{in}R > 0$ , must  $V_x \downarrow$   
if  $V_x - I_{in}R < 0$ , must  $V_x \uparrow$

$V_o = I_{in}R$

The slide features a grid background with handwritten equations and circuit diagrams. A green circle highlights a specific op-amp circuit diagram. A small video inset shows a person in a pink shirt. The NPTEL logo is in the top right corner.

So, this therefore, is an op-amp and draws a more respectable picture. Does it make sense, alright? So, as you can see the signs on the op-amps come out naturally without having to guess a copy from the neighbour's open textbook all that, alright. So, what is this voltage?

But we know that it is an op-amp whose gain is infinite. So, what comment can you make about that voltage? That voltage is 0. So, therefore, what is the input resistance looking in here? What is the input impedance of this? So, this is our claimed current control voltage source. What is the resistance as seen by the input source?

Student: 0.

0, why? Because that voltage regardless of how much current you pump in the voltage always remains?

Student: 0.

0. So, the input impedance is 0. What comment can you make about the output resistance? What is the output resistance?

Student: 0.

0, why?

Is there a simpler way of telling me that the output resistance is 0? If  $R_L$  changes, the output is not changing, correct? Because all this current  $I_{in}$  where is it going? Where is it going? Can it go into the op-amp?

Student: No.

No. So, it is all going through R. So, what is this voltage therefore?

Student:  $I_{in}R$ .

$I_{in}R$  irrespective of?

Student:  $R_L$ .

$R_L$ . So, therefore, since the output voltage is independent of the load resistance, it must follow that the output resistance is 0. Is that clear? Alright. So, I mean if the input resistance of this current controlled voltage source is 0, what does it mean? I mean in practice why do you, for instance, use a current control voltage source? What does that buy you in terms of or in other words what I am saying is if the input resistance was not 0. Or rather let us now assume that we have a bad current source. What is the bad current source?

Ideal current source should have an output resistance of infinity. So, let us call this output resistance of this current source equal to  $R_x$ . So, now, what comment can you make about the output voltage?

Student: It will be the same.

It will be the same, why? Well one end of  $R_x$  is grounded, the other end of  $R_x$  is also virtual grounded. So, the voltage difference across the resistance is?

Student: 0.

So, what comment can you make about the current situation? No current flows through  $R_x$ . So,  $I_{in}$  basically continues to flow in R, alright. So, output voltage will be and this is exactly why you need a current control voltage source, so that you can suck out all the current from the current source even though the current source has got some output resistance.

If the current control voltage source was not ideal in the sense that it had some of its own input resistance was not 0, what comment can you make? Only a fraction of that input current

$I_{in}$  will flow into the amplifier. Some of it will get lost through the output resistance  $R_x$  that is exactly what the ideal current control voltage source ensures. Is this clear folks? Alright.

Now, what comment can you make if you have a current like this output voltage is of course  $I_{in} R$ . Can I replace this current source in parallel with a with an equivalent? Current source in parallel with the resistor is equivalent to a voltage source in series with the resistor. So, what is the value of the voltage source?

(Refer Slide Time: 27:59)

Lecture 11

NPTEL

$$\frac{V_o}{V_i} = \frac{1}{F} \cdot \frac{LG}{1+LG} \quad LG = Af$$

$$\frac{V_o}{V_i} = \frac{1}{1+LG}$$

if  $V_x - I_{in} R > 0$ , must  $V_x \downarrow$   
 $V_x - I_{in} R < 0$ , must  $V_x \uparrow$

$V_o = I_{in} R$

This is  $R_x$ . This is  $-I_{in}R_x$ , alright. So, now, I mean if you look at this picture now, it does not make any sense to call this  $I_{in}$  because there is no current at all. So, you might as well call this. If I call this  $V_{in}$  what can I call this? But what is  $V_{out}$  in terms of  $V_{in}$ .

(Refer Slide Time: 28:46)

Lecture 11

$$\frac{V_o}{V_i} = \frac{1}{f} \frac{LG}{1+LG} \quad LG = Af$$

$$\frac{V_o}{V_i} = \frac{1}{1+LG}$$

if  $V_x - I_{in}R > 0$ , must  $V_o \downarrow$   
 if  $V_x - I_{in}R < 0$ , must  $V_o \uparrow$

$V_o = I_{in}R$

$V_{in} \frac{R}{R_x}$

$I_{in}R$

$-V_{in} \frac{R}{R_x}$

It is basically  $V_{in}R_x$ . Is this correct?

Alright and this is this circuit familiar. So, this is the very well-known inverting amplifier, but now where it comes from. So, you try to make a current control voltage source. As a current source is bad then its equivalent is basically equivalent to an inverting amplifier.

I mean there is, of course, another way of deriving this. What do you call again from first principles. If you want  $V_{out}$  to be the negative of  $V_{in}$  what does it mean?  $V_{out}$  plus  $V_{in}$  must be equal to 0. So, you compare you add  $V_{out}$  and  $V_{in}$  and compare the result to 0, correct. And how will you add two voltages KVL of course, but how will you implement addition. Let say you want  $V_1$  and  $V_2$ , you want  $V_1 + V_2$ , can you get  $V_1 + V_2$  using only resistors? Can you get  $(V_1 + V_2)/2$  using only resistors?

Yeah. So, basically if you take  $V_1$ ,  $V_2$  connect both of them together in order through two resistors, the midpoint will basically give you the sum of the two multiplied by some fraction, since we are only comparing it to 0. That fraction does not matter, correct.

(Refer Slide Time: 31:04)

Want  $V_o = -V_i$

$\frac{V_o + V_i}{2} > 0 \Rightarrow$  means  $V_o$  is too high  $\Rightarrow V_o \downarrow$

The circuit diagram shows an operational amplifier with its non-inverting input (+) connected to ground. The inverting input (-) is connected to an input terminal  $V_i$  through a resistor  $R$ . The output terminal  $V_o$  is connected back to the inverting input through another resistor  $R$ . An arrow points to the midpoint between the two resistors, indicating a feedback signal.

So, what I was saying was let us say we want  $V_o$  to be  $-V_i$ . So, what will we do? We will find  $V_o + V_i$  if  $V_o + V_i$  is greater than 0. What does it mean? It means  $V_o$  is too high and therefore,  $V_o$  must reduce and vice versa, is this clear? So, now, the question is  $V_o + V_i$  greater than 0 is equivalent to saying  $(V_o + V_i)/2$  is also greater than 0. So, how will you get  $(V_o + V_i)/2$ ?

Let's say you have  $V_o$ . You have  $V_i$ , how will I get  $(V_o + V_i)/2$ ?

Yeah. So, basically. So, this is  $R$ , this is  $R$ , alright. So, what is that voltage?

$(V_o + V_i)/2$ , and if that is greater than 0,  $V_o$  must go?

Student: Down.

If this goes up this must be pulled down. So what must be a voltage control voltage source between that midpoint of those resistors in the output and what must be the gain of that voltage control voltage source? Even if that voltage is infinitesimally greater than 0 or less than 0 you must kick this note so hard. So you must put an amplifier like this, an op-amp like this, to go and kick.

The output in the direction is correct and since the op-amp is ideal that the midpoint of those resistors is to be is condemned to be in ground and therefore, the output voltage is the negative of the input voltage. Does it make sense?