

Electrical Distribution System Analysis
Dr. Ganesh Kumbhar
Department of Electrical Engineering
Indian Institute of Technology, Roorkee

Lecture – 28
Backward/Forward Sweep Load Flow Analysis
Part II


In the last lecture, we have started analysis of distribution system and we have started with load flow studies. Last lecture we have seen, one algorithm which is called as backward forward sweep algorithm which is classical algorithm of load flow studies in distribution system. Initially what I did actually I have introduced to algorithm with simple example, and after that we have seen step by step algorithm of basically backward forward load flow.

Let us see what we have seen so, we have seen that if there is distribution system.

(Refer Slide Time: 01:05)

Backward/Forward Sweep Load Flow

- Radial balanced distribution system

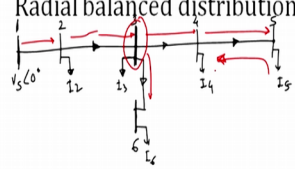

forward sweep

$$V_2 = V_1 - Z_{12} I_1$$

$$V_3 = V_2 - Z_{23} I_2$$

$$V_4 = V_3 - Z_{34} I_3$$

$$V_5 = V_4 - Z_{45} I_4$$

$$V_6 = V_5 - Z_{56} I_5$$

Backward sweep

$$I_4 = I_5$$

$$I_3 = I_4 + I_3$$

$$I_2 = I_3 + I_2$$

$$I_j^{(k)} = \left(\frac{P_j + jQ_j}{V_j} \right)^* \quad \text{for } j: 2, 3, \dots, 6 \quad \checkmark$$

Let us say distribution system is like this, you are having this distribution system here, there are various buses say these are actually there is one branch here, bus number 1 2 3 4 5 and say this is bus number 6. Bus 1 voltage is fixed as a $V \angle 0^\circ$ degree. And, in this case we can write your current equation I_j at any k th iteration will be equal to $P_j + jQ_j$ divided by V_j , which is basically power factor. And, then you have to take the complex conjugated bit and then it will be run for j is equal to 2 in this particular case, it

will run up to 6. So, using this we can get the currents load currents of each bus starting from bus number 2 ending with 6.

And, then we have seen that in case of backward sweep, we are calculating the branch currents. So, in this case you have already calculated this load currents, which are basically say I_5 I_4 I_6 the load current is here it is say I_3 and here say I_2 ; So, this all the load currents are calculated in this step. Then, in backward sweep we have can calculate the branch currents. So, we know that we have to start from end nodes and we have to go towards your source node. So, we will start with this end node as well as this end node here so, end node bus number 6.

So, say I_{45} will be equal to I_5 . So, current into this branch will be just I_5 current. So, I_{45} will be just I_5 . Now, current I_{34} will be equal to this current which is between I_{45} plus I_4 . So, it will be I_{45} plus I_4 I_4 is already calculated you can use it here. Then, I_{63} will be equal to I_6 because in this branch only I_6 current will be flowing. And, then we have calculating I_{23} , which is basically current into this branch will be equal to current which is flowing in I_{34} plus current, which is flowing from I_{63} plus current at bus 3 which is I_3 .

So, here I_{34} and I_{63} we already calculated before that and then I_{12} will be equal to I_{23} , basically this current which is flowing in this branch plus current load current at bus 2. So, this equations we can have an backward sweep, which will give basically line currents in all the lines. And, then we have seen in forward sweep we need to calculate bus voltages. So, in forward sweep we calculate bus voltages.

So, explicitly if you write this is first voltage V_2 will be equal to bus voltage V_1 which is V_S angle 0 degree, which will fixed minus your Z_{12} into I_{12} , which you have calculated at here. So, V_1 is fixed I_{12} is also calculated here Z_{12} impedance is known. So, we can get voltage V_2 , voltage V_3 , will be equal to voltage V_2 minus Z_{23} into I_{23} , I_{23} is calculated V_2 is calculated before V_3 .

So, V_2 I also known then V_4 will be equal to V_3 minus Z_{34} into I_{34} I_{34} is calculated here, and V_3 we have calculated earlier step. Similarly, you get V_5 will may equal to V_4 minus Z_{45} into I_{45} . And, V_4 is taking from here and I_{45} already calculated it here and then V_6 will be equal to V_3 , because this 6 branch is connected 2 branch bus 3 here 6 bus is connected to bus 3 here.

So, it will be V_3 minus Z_{36} into I_{36} . So, I_{36} already known and V_3 can get it from here, which is calculated before calculating V_6 . Because, we are starting with source node, we are starting with source node and then we are going on calculating the voltages till end node. So, voltage when we are calculating voltage of V_6 V_3 will be already calculated. And, then in backward sweep we have seen, we start with end nodes and go towards forward nodes.

So, in that case I_4 will be already calculated before calculating I_{34} because this branch is actually end branch. So, currents in branch which are connected to end nodes will be calculated first, and then we are going towards source node. So, this was basic philosophy of backward forward sweep algorithm. Detailed algorithm of backward forward sweep load flow, we already seen in the last lecture.

Now, let us see how we can use this algorithm for three phase systems, because we have seen that in many cases your distribution system is unbalanced one, and if you are analyzing unbalanced system you have to do load flow analysis with full three phase system. So, you have to consider all the three phases during the analysis. So, let us see or let us consider simple three phase distribution system similar to this.

(Refer Slide Time: 07:55)

Backward/Forward Sweep Load Flow

- Radial un-balanced distribution system

Diagram showing a radial unbalanced distribution system with 5 buses. The system is unbalanced, with different phases connected to different buses. The diagram shows the following parameters:

- Bus 1: $V_{S1} = V_S \angle 0^\circ$
- Bus 2: $V_{S2} = V_S \angle -120^\circ$
- Bus 3: $V_{S3} = V_S \angle 120^\circ$
- Bus 4: $Z_{45} = Z_{43}$
- Bus 5: $Z_{56} = Z_{36}$
- Bus 6: $Z_{67} = Z_{12}$
- Bus 7: $Z_{78} = Z_{12}$
- Bus 8: $Z_{89} = Z_{12}$
- Bus 9: $Z_{90} = Z_{12}$
- Bus 10: $Z_{1011} = Z_{12}$
- Bus 11: $Z_{1112} = Z_{12}$
- Bus 12: $Z_{1213} = Z_{12}$
- Bus 13: $Z_{1314} = Z_{12}$
- Bus 14: $Z_{1415} = Z_{12}$
- Bus 15: $Z_{1516} = Z_{12}$
- Bus 16: $Z_{1617} = Z_{12}$
- Bus 17: $Z_{1718} = Z_{12}$
- Bus 18: $Z_{1819} = Z_{12}$
- Bus 19: $Z_{1920} = Z_{12}$
- Bus 20: $Z_{2021} = Z_{12}$
- Bus 21: $Z_{2122} = Z_{12}$
- Bus 22: $Z_{2223} = Z_{12}$
- Bus 23: $Z_{2324} = Z_{12}$
- Bus 24: $Z_{2425} = Z_{12}$
- Bus 25: $Z_{2526} = Z_{12}$
- Bus 26: $Z_{2627} = Z_{12}$
- Bus 27: $Z_{2728} = Z_{12}$
- Bus 28: $Z_{2829} = Z_{12}$
- Bus 29: $Z_{2930} = Z_{12}$
- Bus 30: $Z_{3031} = Z_{12}$
- Bus 31: $Z_{3132} = Z_{12}$
- Bus 32: $Z_{3233} = Z_{12}$
- Bus 33: $Z_{3334} = Z_{12}$
- Bus 34: $Z_{3435} = Z_{12}$
- Bus 35: $Z_{3536} = Z_{12}$
- Bus 36: $Z_{3637} = Z_{12}$
- Bus 37: $Z_{3738} = Z_{12}$
- Bus 38: $Z_{3839} = Z_{12}$
- Bus 39: $Z_{3940} = Z_{12}$
- Bus 40: $Z_{4041} = Z_{12}$
- Bus 41: $Z_{4142} = Z_{12}$
- Bus 42: $Z_{4243} = Z_{12}$
- Bus 43: $Z_{4344} = Z_{12}$
- Bus 44: $Z_{4445} = Z_{12}$
- Bus 45: $Z_{4546} = Z_{12}$
- Bus 46: $Z_{4647} = Z_{12}$
- Bus 47: $Z_{4748} = Z_{12}$
- Bus 48: $Z_{4849} = Z_{12}$
- Bus 49: $Z_{4950} = Z_{12}$
- Bus 50: $Z_{5051} = Z_{12}$
- Bus 51: $Z_{5152} = Z_{12}$
- Bus 52: $Z_{5253} = Z_{12}$
- Bus 53: $Z_{5354} = Z_{12}$
- Bus 54: $Z_{5455} = Z_{12}$
- Bus 55: $Z_{5556} = Z_{12}$
- Bus 56: $Z_{5657} = Z_{12}$
- Bus 57: $Z_{5758} = Z_{12}$
- Bus 58: $Z_{5859} = Z_{12}$
- Bus 59: $Z_{5960} = Z_{12}$
- Bus 60: $Z_{6061} = Z_{12}$
- Bus 61: $Z_{6162} = Z_{12}$
- Bus 62: $Z_{6263} = Z_{12}$
- Bus 63: $Z_{6364} = Z_{12}$
- Bus 64: $Z_{6465} = Z_{12}$
- Bus 65: $Z_{6566} = Z_{12}$
- Bus 66: $Z_{6667} = Z_{12}$
- Bus 67: $Z_{6768} = Z_{12}$
- Bus 68: $Z_{6869} = Z_{12}$
- Bus 69: $Z_{6970} = Z_{12}$
- Bus 70: $Z_{7071} = Z_{12}$
- Bus 71: $Z_{7172} = Z_{12}$
- Bus 72: $Z_{7273} = Z_{12}$
- Bus 73: $Z_{7374} = Z_{12}$
- Bus 74: $Z_{7475} = Z_{12}$
- Bus 75: $Z_{7576} = Z_{12}$
- Bus 76: $Z_{7677} = Z_{12}$
- Bus 77: $Z_{7778} = Z_{12}$
- Bus 78: $Z_{7879} = Z_{12}$
- Bus 79: $Z_{7980} = Z_{12}$
- Bus 80: $Z_{8081} = Z_{12}$
- Bus 81: $Z_{8182} = Z_{12}$
- Bus 82: $Z_{8283} = Z_{12}$
- Bus 83: $Z_{8384} = Z_{12}$
- Bus 84: $Z_{8485} = Z_{12}$
- Bus 85: $Z_{8586} = Z_{12}$
- Bus 86: $Z_{8687} = Z_{12}$
- Bus 87: $Z_{8788} = Z_{12}$
- Bus 88: $Z_{8889} = Z_{12}$
- Bus 89: $Z_{8990} = Z_{12}$
- Bus 90: $Z_{9091} = Z_{12}$
- Bus 91: $Z_{9192} = Z_{12}$
- Bus 92: $Z_{9293} = Z_{12}$
- Bus 93: $Z_{9394} = Z_{12}$
- Bus 94: $Z_{9495} = Z_{12}$
- Bus 95: $Z_{9596} = Z_{12}$
- Bus 96: $Z_{9697} = Z_{12}$
- Bus 97: $Z_{9798} = Z_{12}$
- Bus 98: $Z_{9899} = Z_{12}$
- Bus 99: $Z_{99100} = Z_{12}$
- Bus 100: $Z_{100101} = Z_{12}$
- Bus 101: $Z_{101102} = Z_{12}$
- Bus 102: $Z_{102103} = Z_{12}$
- Bus 103: $Z_{103104} = Z_{12}$
- Bus 104: $Z_{104105} = Z_{12}$
- Bus 105: $Z_{105106} = Z_{12}$
- Bus 106: $Z_{106107} = Z_{12}$
- Bus 107: $Z_{107108} = Z_{12}$
- Bus 108: $Z_{108109} = Z_{12}$
- Bus 109: $Z_{109110} = Z_{12}$
- Bus 110: $Z_{110111} = Z_{12}$
- Bus 111: $Z_{111112} = Z_{12}$
- Bus 112: $Z_{112113} = Z_{12}$
- Bus 113: $Z_{113114} = Z_{12}$
- Bus 114: $Z_{114115} = Z_{12}$
- Bus 115: $Z_{115116} = Z_{12}$
- Bus 116: $Z_{116117} = Z_{12}$
- Bus 117: $Z_{117118} = Z_{12}$
- Bus 118: $Z_{118119} = Z_{12}$
- Bus 119: $Z_{119120} = Z_{12}$
- Bus 120: $Z_{120121} = Z_{12}$
- Bus 121: $Z_{121122} = Z_{12}$
- Bus 122: $Z_{122123} = Z_{12}$
- Bus 123: $Z_{123124} = Z_{12}$
- Bus 124: $Z_{124125} = Z_{12}$
- Bus 125: $Z_{125126} = Z_{12}$
- Bus 126: $Z_{126127} = Z_{12}$
- Bus 127: $Z_{127128} = Z_{12}$
- Bus 128: $Z_{128129} = Z_{12}$
- Bus 129: $Z_{129130} = Z_{12}$
- Bus 130: $Z_{130131} = Z_{12}$
- Bus 131: $Z_{131132} = Z_{12}$
- Bus 132: $Z_{132133} = Z_{12}$
- Bus 133: $Z_{133134} = Z_{12}$
- Bus 134: $Z_{134135} = Z_{12}$
- Bus 135: $Z_{135136} = Z_{12}$
- Bus 136: $Z_{136137} = Z_{12}$
- Bus 137: $Z_{137138} = Z_{12}$
- Bus 138: $Z_{138139} = Z_{12}$
- Bus 139: $Z_{139140} = Z_{12}$
- Bus 140: $Z_{140141} = Z_{12}$
- Bus 141: $Z_{141142} = Z_{12}$
- Bus 142: $Z_{142143} = Z_{12}$
- Bus 143: $Z_{143144} = Z_{12}$
- Bus 144: $Z_{144145} = Z_{12}$
- Bus 145: $Z_{145146} = Z_{12}$
- Bus 146: $Z_{146147} = Z_{12}$
- Bus 147: $Z_{147148} = Z_{12}$
- Bus 148: $Z_{148149} = Z_{12}$
- Bus 149: $Z_{149150} = Z_{12}$
- Bus 150: $Z_{150151} = Z_{12}$
- Bus 151: $Z_{151152} = Z_{12}$
- Bus 152: $Z_{152153} = Z_{12}$
- Bus 153: $Z_{153154} = Z_{12}$
- Bus 154: $Z_{154155} = Z_{12}$
- Bus 155: $Z_{155156} = Z_{12}$
- Bus 156: $Z_{156157} = Z_{12}$
- Bus 157: $Z_{157158} = Z_{12}$
- Bus 158: $Z_{158159} = Z_{12}$
- Bus 159: $Z_{159160} = Z_{12}$
- Bus 160: $Z_{160161} = Z_{12}$
- Bus 161: $Z_{161162} = Z_{12}$
- Bus 162: $Z_{162163} = Z_{12}$
- Bus 163: $Z_{163164} = Z_{12}$
- Bus 164: $Z_{164165} = Z_{12}$
- Bus 165: $Z_{165166} = Z_{12}$
- Bus 166: $Z_{166167} = Z_{12}$
- Bus 167: $Z_{167168} = Z_{12}$
- Bus 168: $Z_{168169} = Z_{12}$
- Bus 169: $Z_{169170} = Z_{12}$
- Bus 170: $Z_{170171} = Z_{12}$
- Bus 171: $Z_{171172} = Z_{12}$
- Bus 172: $Z_{172173} = Z_{12}$
- Bus 173: $Z_{173174} = Z_{12}$
- Bus 174: $Z_{174175} = Z_{12}$
- Bus 175: $Z_{175176} = Z_{12}$
- Bus 176: $Z_{176177} = Z_{12}$
- Bus 177: $Z_{177178} = Z_{12}$
- Bus 178: $Z_{178179} = Z_{12}$
- Bus 179: $Z_{179180} = Z_{12}$
- Bus 180: $Z_{180181} = Z_{12}$
- Bus 181: $Z_{181182} = Z_{12}$
- Bus 182: $Z_{182183} = Z_{12}$
- Bus 183: $Z_{183184} = Z_{12}$
- Bus 184: $Z_{184185} = Z_{12}$
- Bus 185: $Z_{185186} = Z_{12}$
- Bus 186: $Z_{186187} = Z_{12}$
- Bus 187: $Z_{187188} = Z_{12}$
- Bus 188: $Z_{188189} = Z_{12}$
- Bus 189: $Z_{189190} = Z_{12}$
- Bus 190: $Z_{190191} = Z_{12}$
- Bus 191: $Z_{191192} = Z_{12}$
- Bus 192: $Z_{192193} = Z_{12}$
- Bus 193: $Z_{193194} = Z_{12}$
- Bus 194: $Z_{194195} = Z_{12}$
- Bus 195: $Z_{195196} = Z_{12}$
- Bus 196: $Z_{196197} = Z_{12}$
- Bus 197: $Z_{197198} = Z_{12}$
- Bus 198: $Z_{198199} = Z_{12}$
- Bus 199: $Z_{199200} = Z_{12}$
- Bus 200: $Z_{200201} = Z_{12}$
- Bus 201: $Z_{201202} = Z_{12}$
- Bus 202: $Z_{202203} = Z_{12}$
- Bus 203: $Z_{203204} = Z_{12}$
- Bus 204: $Z_{204205} = Z_{12}$
- Bus 205: $Z_{205206} = Z_{12}$
- Bus 206: $Z_{206207} = Z_{12}$
- Bus 207: $Z_{207208} = Z_{12}$
- Bus 208: $Z_{208209} = Z_{12}$
- Bus 209: $Z_{209210} = Z_{12}$
- Bus 210: $Z_{210211} = Z_{12}$
- Bus 211: $Z_{211212} = Z_{12}$
- Bus 212: $Z_{212213} = Z_{12}$
- Bus 213: $Z_{213214} = Z_{12}$
- Bus 214: $Z_{214215} = Z_{12}$
- Bus 215: $Z_{215216} = Z_{12}$
- Bus 216: $Z_{216217} = Z_{12}$
- Bus 217: $Z_{217218} = Z_{12}$
- Bus 218: $Z_{218219} = Z_{12}$
- Bus 219: $Z_{219220} = Z_{12}$
- Bus 220: $Z_{220221} = Z_{12}$
- Bus 221: $Z_{221222} = Z_{12}$
- Bus 222: $Z_{222223} = Z_{12}$
- Bus 223: $Z_{223224} = Z_{12}$
- Bus 224: $Z_{224225} = Z_{12}$
- Bus 225: $Z_{225226} = Z_{12}$
- Bus 226: $Z_{226227} = Z_{12}$
- Bus 227: $Z_{227228} = Z_{12}$
- Bus 228: $Z_{228229} = Z_{12}$
- Bus 229: $Z_{229230} = Z_{12}$
- Bus 230: $Z_{230231} = Z_{12}$
- Bus 231: $Z_{231232} = Z_{12}$
- Bus 232: $Z_{232233} = Z_{12}$
- Bus 233: $Z_{233234} = Z_{12}$
- Bus 234: $Z_{234235} = Z_{12}$
- Bus 235: $Z_{235236} = Z_{12}$
- Bus 236: $Z_{236237} = Z_{12}$
- Bus 237: $Z_{237238} = Z_{12}$
- Bus 238: $Z_{238239} = Z_{12}$
- Bus 239: $Z_{239240} = Z_{12}$
- Bus 240: $Z_{240241} = Z_{12}$
- Bus 241: $Z_{241242} = Z_{12}$
- Bus 242: $Z_{242243} = Z_{12}$
- Bus 243: $Z_{243244} = Z_{12}$
- Bus 244: $Z_{244245} = Z_{12}$
- Bus 245: $Z_{245246} = Z_{12}$
- Bus 246: $Z_{246247} = Z_{12}$
- Bus 247: $Z_{247248} = Z_{12}$
- Bus 248: $Z_{248249} = Z_{12}$
- Bus 249: $Z_{249250} = Z_{12}$
- Bus 250: $Z_{250251} = Z_{12}$
- Bus 251: $Z_{251252} = Z_{12}$
- Bus 252: $Z_{252253} = Z_{12}$
- Bus 253: $Z_{253254} = Z_{12}$
- Bus 254: $Z_{254255} = Z_{12}$
- Bus 255: $Z_{255256} = Z_{12}$
- Bus 256: $Z_{256257} = Z_{12}$
- Bus 257: $Z_{257258} = Z_{12}$
- Bus 258: $Z_{258259} = Z_{12}$
- Bus 259: $Z_{259260} = Z_{12}$
- Bus 260: $Z_{260261} = Z_{12}$
- Bus 261: $Z_{261262} = Z_{12}$
- Bus 262: $Z_{262263} = Z_{12}$
- Bus 263: $Z_{263264} = Z_{12}$
- Bus 264: $Z_{264265} = Z_{12}$
- Bus 265: $Z_{265266} = Z_{12}$
- Bus 266: $Z_{266267} = Z_{12}$
- Bus 267: $Z_{267268} = Z_{12}$
- Bus 268: $Z_{268269} = Z_{12}$
- Bus 269: $Z_{269270} = Z_{12}$
- Bus 270: $Z_{270271} = Z_{12}$
- Bus 271: $Z_{271272} = Z_{12}$
- Bus 272: $Z_{272273} = Z_{12}$
- Bus 273: $Z_{273274} = Z_{12}$
- Bus 274: $Z_{274275} = Z_{12}$
- Bus 275: $Z_{275276} = Z_{12}$
- Bus 276: $Z_{276277} = Z_{12}$
- Bus 277: $Z_{277278} = Z_{12}$
- Bus 278: $Z_{278279} = Z_{12}$
- Bus 279: $Z_{279280} = Z_{12}$
- Bus 280: $Z_{280281} = Z_{12}$
- Bus 281: $Z_{281282} = Z_{12}$
- Bus 282: $Z_{282283} = Z_{12}$
- Bus 283: $Z_{283284} = Z_{12}$
- Bus 284: $Z_{284285} = Z_{12}$
- Bus 285: $Z_{285286} = Z_{12}$
- Bus 286: $Z_{286287} = Z_{12}$
- Bus 287: $Z_{287288} = Z_{12}$
- Bus 288: $Z_{288289} = Z_{12}$
- Bus 289: $Z_{289290} = Z_{12}$
- Bus 290: $Z_{290291} = Z_{12}$
- Bus 291: $Z_{291292} = Z_{12}$
- Bus 292: $Z_{292293} = Z_{12}$
- Bus 293: $Z_{293294} = Z_{12}$
- Bus 294: $Z_{294295} = Z_{12}$
- Bus 295: $Z_{295296} = Z_{12}$
- Bus 296: $Z_{296297} = Z_{12}$
- Bus 297: $Z_{297298} = Z_{12}$
- Bus 298: $Z_{298299} = Z_{12}$
- Bus 299: $Z_{299300} = Z_{12}$
- Bus 300: $Z_{300301} = Z_{12}$
- Bus 301: $Z_{301302} = Z_{12}$
- Bus 302: $Z_{302303} = Z_{12}$
- Bus 303: $Z_{303304} = Z_{12}$
- Bus 304: $Z_{304305} = Z_{12}$
- Bus 305: $Z_{305306} = Z_{12}$
- Bus 306: $Z_{306307} = Z_{12}$
- Bus 307: $Z_{307308} = Z_{12}$
- Bus 308: $Z_{308309} = Z_{12}$
- Bus 309: $Z_{309310} = Z_{12}$
- Bus 310: $Z_{310311} = Z_{12}$
- Bus 311: $Z_{311312} = Z_{12}$
- Bus 312: $Z_{312313} = Z_{12}$
- Bus 313: $Z_{313314} = Z_{12}$
- Bus 314: $Z_{314315} = Z_{12}$
- Bus 315: $Z_{315316} = Z_{12}$
- Bus 316: $Z_{316317} = Z_{12}$
- Bus 317: $Z_{317318} = Z_{12}$
- Bus 318: $Z_{318319} = Z_{12}$
- Bus 319: $Z_{319320} = Z_{12}$
- Bus 320: $Z_{320321} = Z_{12}$
- Bus 321: $Z_{321322} = Z_{12}$
- Bus 322: $Z_{322323} = Z_{12}$
- Bus 323: $Z_{323324} = Z_{12}$
- Bus 324: $Z_{324325} = Z_{12}$
- Bus 325: $Z_{325326} = Z_{12}$
- Bus 326: $Z_{326327} = Z_{12}$
- Bus 327: $Z_{327328} = Z_{12}$
- Bus 328: $Z_{328329} = Z_{12}$
- Bus 329: $Z_{329330} = Z_{12}$
- Bus 330: $Z_{330331} = Z_{12}$
- Bus 331: $Z_{331332} = Z_{12}$
- Bus 332: $Z_{332333} = Z_{12}$
- Bus 333: $Z_{333334} = Z_{12}$
- Bus 334: $Z_{334335} = Z_{12}$
- Bus 335: $Z_{335336} = Z_{12}$
- Bus 336: $Z_{336337} = Z_{12}$
- Bus 337: $Z_{337338} = Z_{12}$
- Bus 338: $Z_{338339} = Z_{12}$
- Bus 339: $Z_{339340} = Z_{12}$
- Bus 340: $Z_{340341} = Z_{12}$
- Bus 341: $Z_{341342} = Z_{12}$
- Bus 342: $Z_{342343} = Z_{12}$
- Bus 343: $Z_{343344} = Z_{12}$
- Bus 344: $Z_{344345} = Z_{12}$
- Bus 345: $Z_{345346} = Z_{12}$
- Bus 346: $Z_{346347} = Z_{12}$
- Bus 347: $Z_{347348} = Z_{12}$
- Bus 348: $Z_{348349} = Z_{12}$
- Bus 349: $Z_{349350} = Z_{12}$
- Bus 350: $Z_{350351} = Z_{12}$
- Bus 351: $Z_{351352} = Z_{12}$
- Bus 352: $Z_{352353} = Z_{12}$
- Bus 353: $Z_{353354} = Z_{12}$
- Bus 354: $Z_{354355} = Z_{12}$
- Bus 355: $Z_{355356} = Z_{12}$
- Bus 356: $Z_{356357} = Z_{12}$
- Bus 357: $Z_{357358} = Z_{12}$
- Bus 358: $Z_{358359} = Z_{12}$
- Bus 359: $Z_{359360} = Z_{12}$
- Bus 360: $Z_{360361} = Z_{12}$
- Bus 361: $Z_{361362} = Z_{12}$
- Bus 362: $Z_{362363} = Z_{12}$
- Bus 363: $Z_{363364} = Z_{12}$
- Bus 364: $Z_{364365} = Z_{12}$
- Bus 365: $Z_{365366} = Z_{12}$
- Bus 366: $Z_{366367} = Z_{12}$
- Bus 367: $Z_{367368} = Z_{12}$
- Bus 368: $Z_{368369} = Z_{12}$
- Bus 369: $Z_{369370} = Z_{12}$
- Bus 370: $Z_{370371} = Z_{12}$
- Bus 371: $Z_{371372} = Z_{12}$
- Bus 372: $Z_{372373} = Z_{12}$
- Bus 373: $Z_{373374} = Z_{12}$
- Bus 374: $Z_{374375} = Z_{12}$
- Bus 375: $Z_{375376} = Z_{12}$
- Bus 376: $Z_{376377} = Z_{12}$
- Bus 377: $Z_{377378} = Z_{12}$
- Bus 378: $Z_{378379} = Z_{12}$
- Bus 379: $Z_{379380} = Z_{12}$
- Bus 380: $Z_{380381} = Z_{12}$
- Bus 381: $Z_{381382} = Z_{12}$
- Bus 382: $Z_{382383} = Z_{12}$
- Bus 383: $Z_{383384} = Z_{12}$
- Bus 384: $Z_{384385} = Z_{12}$
- Bus 385: $Z_{385386} = Z_{12}$
- Bus 386: $Z_{386387} = Z_{12}$
- Bus 387: $Z_{387388} = Z_{12}$
- Bus 388: $Z_{388389} = Z_{12}$
- Bus 389: $Z_{389390} = Z_{12}$
- Bus 390: $Z_{390391} = Z_{12}$
- Bus 391: $Z_{391392} = Z_{12}$
- Bus 392: $Z_{392393} = Z_{12}$
- Bus 393: $Z_{393394} = Z_{12}$
- Bus 394: $Z_{394395} = Z_{12}$
- Bus 395: $Z_{395396} = Z_{12}$
- Bus 396: $Z_{396397} = Z_{12}$
- Bus 397: $Z_{397398} = Z_{12}$
- Bus 398: $Z_{398399} = Z_{12}$
- Bus 399: $Z_{399400} = Z_{12}$
- Bus 400: Z_{400401}

ending here and they are connected to number node number 4. And stay after this only 1 phase is extended and here your bus number 5 and this phase c will be extended and connected to bus number 6. So, here so, if you see this will be bus which is basically I can call it 2 a, this I can call it 2 b, and this I can call it 2 c. Similarly, this is 3 a, 3 b, and 3 c and this 6 node will be having only 1 phase similarly node 5 will be having 1 phase, and node 4 is having 2 phases.

Now, if you see impedance matrix. So, Z_{12} impedance matrix will be actually 3 by 3, because all the three phases are there and all the 3 phases are basically mutually coupled with each other. So, it will be having Z_{aa} Z_{ab} Z_{ac} Z_{ba} Z_{bb} Z_{bc} Z_{ca} Z_{cb} and Z_{cc} are the impedances of or impedance matrix of all the 3 phases. Now, since these impedances are between node 1 and 2 I can just write this 1 and 2. So, all the impedances of 1 2 will be like this. So, this is nothing, but Z_{12} impedance matrix between node 1 and node 2.

Exactly similar way I can write Z_{23} it will be also similar 3 by 3 size. However, I need to change only this index here index will become 2 3 otherwise it will be same. And, if it is having same structure the same matrix can be used for this section also. However, if you see this section between 3 and 4 so, in this case your Z_{34} will be of 2 by 2 size. So, it will be Z_{aa} Z_{ab} Z_{ba} Z_{bb} . And since it is between 3 and 4 I can just give index 3 4, everywhere.

So, this will be impedance matrix between 3 and 4 this is how we have to write, then impedance matrix Z_{45} . So, Z_{45} will be just since I it is having only 1 phase it will be Z_{aa} and I it is a phase. So, Z_{aa} between 4 and 5 and then when I am setting Z matrix of 3 6, it will be again Z ; however, this phase is c phase. So, it will be Z_{cc} 3 6. So, we can see that depending upon number of phases present in particular section of the line the impedance matrix will change. So, you need to use the particular impedance matrix for particular section of this one.


Similarly of you see the voltages. So, source voltages will be perfectly balance I can assume and having equal magnitude. So, these will be V_S angle 0 degree, which is voltage of a phase V_S angle minus 120 degree. So, I can say this is $V_S a$ $V_S b$ or I can say $V_S a$ will be equal to V_S angle 0 degree, $V_S b$ will be equal to V_S angle minus 120 degree, and $V_S c$ will be equal to V_S angle 120 degree. So, this is this voltages will

be perfectly balance and they will not change during the iteration. So, voltages of other buses will change in during the iterations. So, what I will do actually we will try to write explicit step by step algorithm for this particular system.

(Refer Slide Time: 13:05)

Backward/Forward Sweep Load Flow

- Radial balanced distribution system

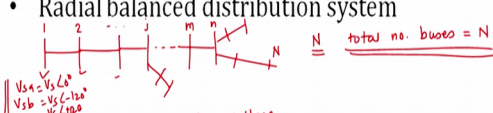

$V_{sA} = V_S \angle 0^\circ$
 $V_{sB} = V_S \angle -120^\circ$
 $V_{sC} = V_S \angle 120^\circ$



Step 1 Initializing bus voltage

$$\begin{bmatrix} V_{a_j}^{(0)} \\ V_{b_j}^{(0)} \\ V_{c_j}^{(0)} \end{bmatrix} = \begin{bmatrix} V_S \angle 0^\circ \\ V_S \angle -120^\circ \\ V_S \angle 120^\circ \end{bmatrix} \quad \text{for } j = 2, 3, \dots, N$$

Step 2 Initialization of iteration count $k=1$

Step 3 Computation of load current

$$\begin{bmatrix} I_{a_j}^{(k)} \\ I_{b_j}^{(k)} \\ I_{c_j}^{(k)} \end{bmatrix} = \begin{bmatrix} ((P_{L_j} + jQ_{L_j}) / V_{a_j}^{(k-1)})^* \\ ((P_{L_j} + jQ_{L_j}) / V_{b_j}^{(k-1)})^* \\ ((P_{L_j} + jQ_{L_j}) / V_{c_j}^{(k-1)})^* \end{bmatrix}$$

 ITR ROORKEE
  NPTEL ONLINE CERTIFICATION COURSE

5

So, that, we will understand, how we can use it for three phase system? So, in this case again I am assuming any three phase generalized system we already seen that how to get the impedance matrix. So, any generalized three phase system similar to earlier system, I can assume that it is having some branches here. And, then some branches are connected here, any generalized system say 1 2 these are the node numbers any zth node, say this is m bus number n and if say there are N number of nodes.

So, total number of nodes are N into the system. So, total numbers of buses are say N. In this case also step 1 is initialization voltage. So, explicitly write the algorithm. So, step 1 will be initializing bus voltages. So, we will initialize the bus voltage.

However, in this case there will be complete matrix of voltages. So, V_{a_j} V_{b_j} and V_{c_j} which are voltages of any zth bus at 0th iteration, because we are initializing it. So, I will just writing 0th iteration will be equal to initially as I told you we are assuming the voltages at this bus which are basically V_S angle 0 degree, V_S angle minus 120 degree, and V_S angle plus 120 degree, which we are initialize initializing for j going from 2 3 up to all the buses that is capital N.


So, all the buses will be initialize to all the 3 all the voltages with initial voltages, which are V_S^a , V_S^b and V_S^c , which is equal to $V_S \angle 0^\circ$, $V_S \angle -120^\circ$ and equal to $V_S \angle +120^\circ$. So, all the buses like 2 3 up to n will be initialize with these voltages at initial bus.

Then, we have seen step 2 step 2 will be initialization of iteration count and we are using k as a nomenclature for this. So, k is equal to 1 is initialization of iteration count and then step 3, we have seen that we need to calculate load currents. So, basically computation of load current will be done in step three. However, in this case there are all the three phase currents. So, depending upon how many number of phases present, how many phases present in a particular section you need to get phase currents.

So, $I_{a,j}$ at kth iteration, $I_{b,j}$ at kth iteration, and $I_{c,j}$ at kth iteration, which are basically three phase load currents, which will be equal to it depends upon loading of this one. So, load $P_{L,j}$ plus $j Q_{L,j}$ load of a phase and zth node, divided by voltage of k minus oneth iteration, and then we are taking complex conjugate of it.

So, this gives me the load current of a phase, similarly load current of b phase will be equal to $P_{L,b}$ real part of the load have b phase plus $j Q_{L,b}$ divided by voltage $V_{a,j}$ $V_{b,j}$ at k minus 1th iteration, and you have to take the complex conjugate of it. Similarly, we can get $P_{L,c,j}$ plus $j Q_{L,c,j}$, which is load at bus number c at jth bus phase number c at jth bus will be equal to $v_{c,j}$ at k minus 1th iteration, and you have to take complex conjugate of it is actually k minus 1th iteration. So, after getting currents we go for step 4.

(Refer Slide Time: 18:45)

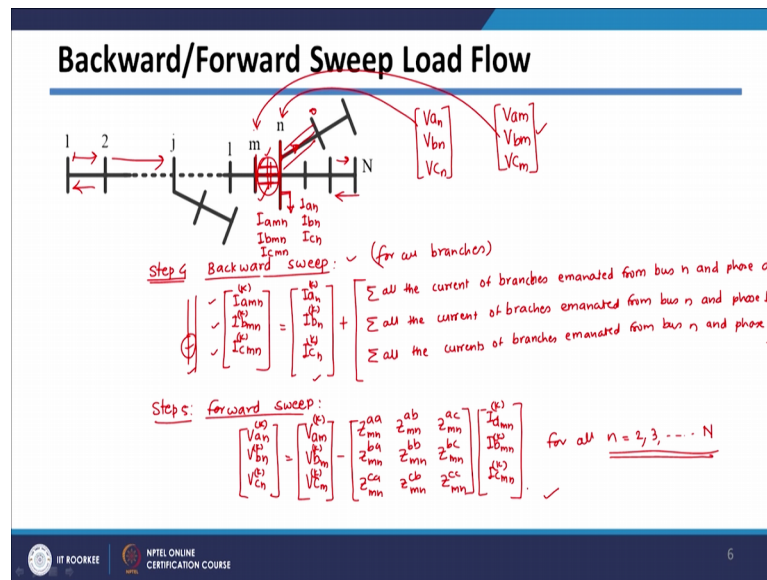

And, step 4 we have seen that it is basically backward sweep and in backward sweep we are calculating line currents. So, line currents now there will be 3 phases. So, there will be 3 line currents here. So, I_{mn} line current in a phase, I_{mn} in b phase, and I_{mn} in c phase. So, we need to calculate all the 3 phases any branch I_{mn} th branch, I can get I_{mna} or I can write instead of this I can just write I_{amn} , I_{bmn} , I_{cmn} . So, in this case also I_{amn} , I_{bmn} and I_{cmn} , which is basically currents flowing in three phases of mn section of the line and it is again at k th iteration. So, I have to write iteration count k here will be equal to.

So, we need to add the phase currents into this one again the phase there are three phase currents. So, I_{an} is phase current, in a phase I_{bn} in phase current, in b phase I_{cn} phase current, in c phase at n th bus. So, it will be I_{an} , I_{bn} and I_{cn} all the 3 currents which already calculated in this k th iteration. So, this currents are already known plus, we have seen that summation, now in this case there will be 3 summation of all the branches, all the currents of branches emanated from bus n and phase a .

Similarly, all the currents of branches emanated from bus n and phase b . So, all the branches which are connected to phase b which are going out of this, because we have seen that in n phase itself there may not be all the branches which are connected to next bus which is connected here say mn or no . So, there is possibly that all the 3 branches may not

be connected to o bus and then in this case all the currents of branches, emanated from bus n and phase c.

So, this will give you all the three phase currents of all the branches of this particular distribution system. So, once you get the current we should go for step 5, which is forward sweep and we have seen that in forward sweep we are basically calculating the nodal voltages. So, in this case nodal voltages V_a , V_b and V_c at kth iteration. So, say this is the this node n. So, at this node the voltages a phase voltage will be V_{an} b phase voltage will be V_{bn} and c phase voltage will be V_{cn} .

They, will be calculated based on voltages of earlier node that is voltage of node m which is basically V_{am} , V_{bm} , and V_{cm} . So, these voltages minus voltages minus voltage drop which is happening in this will give me voltages at n. So, this will be equal to voltages at nth bus will be equal to voltages of mth bus which is V_{am} , V_{bm} , and V_{cm} . At kth iteration, because we have seen that this is forward sweep, we calculate voltages of this bus first and then we will go for this bus. So, this voltages are already known minus.

Now, in this case it will be impedance matrix and if it is all the 3 phases are present into this section, it will be 3 by 3 impedance matrix. So, it will be Z_{aa} Z_{ab} Z_{ac} Z_{ba} Z_{bb} Z_{bc} Z_{ca} Z_{cb} and Z_{cc} and since this section is mn section. So, I can say just write mn everywhere. So, this is nothing, but impedance matrix of this line section here, and then this should be multiplied with your line currents, which are flowing through this line and we have seen that we already calculated this line currents in step number 4. So, this line currents will be I_{amn} , I_{bmn} , and I_{cmn} at kth iteration we already calculated.

So, this will give me voltages of nth bus after completion of forward sweep. And, this will be for all n which is starting from 2 3 and up to N and this sweep will be done for all branches. This will done for all the branches and this will be done for all the nodes. So, this is how we get all the nodal voltages.

(Refer Slide Time: 26:22)

Backward/Forward Sweep Load Flow

Step 6
$$e_j^{(k)} = \max \left(|V_{aj}^{(k)} - V_{aj}^{(k-1)}|, |V_{bj}^{(k)} - V_{bj}^{(k-1)}|, |V_{cj}^{(k)} - V_{cj}^{(k-1)}| \right) \quad j = 2, 3, \dots, N$$

Step 7
$$e_{\max}^{(k)} = \max (e_2^{(k)}, e_3^{(k)}, e_4^{(k)}, \dots, e_N^{(k)})$$

Step 8 If $e_{\max}^{(k)} \leq \epsilon$ (tolerance) print results
 else update iteration count $k = k+1$ and go to step (3)

0.00001

7

And, then we have seen that step number 6 is to get the errors of the voltages, now here there will be 3 errors. So, error of the voltages of jth bus in kth iteration will be equal to max of. So, first you have to calculate the at jth bus there will be 3 voltages. So, if you are considering say this is your jth bus. So, you will be having V_{aj} V_{bj} and V_{cj} 3 voltages, which are calculated kth iteration as well as k minus oneth iteration this voltages will be available.

So, by taking the difference of particular voltage so, it will be V_{aj} at kth iteration minus V_{aj} at k minus 1th iteration, this will be 1 error in error in a phase. Then error in b phase. So, you have to subtract the 2 iteration voltages that is kth iteration voltage of b phase and kth iteration voltage of b k minus 1th iteration voltage of b phase, and then third V_{cj} at kth iteration minus V_{cj} at k minus 1th iteration at mode of it you have to take it.

And, maximum of it maximum is becoming in a phase or b phase or c phase will be nothing, but or error in voltages of say jth bus. So, this will learn for j j equal to 2 3 and it will go up to N. So, it will get errors in bus voltages maximum error in bus voltages, at each of the bus. And, then step 7 will be similar to our algorithm. So, e max of kth iteration will be equal to your max of e 1 kth iteration, e 2 kth iteration, up to e N at kth iteration.

So, here all these values e 1 sorry e 2 start from 2 so, e 2 e 3 e 4 at kth iteration. So, this e 2 e there e 4 they have already calculated in step 6 and we are getting the maximum

errors, by calculating the max of it. So, these are nothing, but errors of the voltages at particular bus, and getting maximum error will get maximum error bit might be happening at any bus in to the system. And, once you get the maximum error in step 8 you have to compare this maximum error with respect to your tolerance value.


So, e_{max} at your k th iteration will be if it is lesser than your epsilon, which is tolerance, which is given if this condition is getting (Refer Time: 29:43). So, there we have to use if statement here. So, if this is true you have converge then print the results, and as well as store the results. And, else if this condition is not a not satisfied means e_{max} is still more than your tolerance value you have to update, iteration count k is equal to k plus 1 iteration is updated and go to step number 3.

So, if this error is more than your tolerance value you have to go to the step number 3, where by using the voltages of earlier step, you have to get the currents and from the currents load currents, you have to get the branch currents using the backward sweep starting from end node and moving towards the source node, you will get all the branch currents.

And, once you get the all the branch currents, you can use the which is called as forward sweep; So, starting from your source node keep on getting the voltages till your end node by using step number 5. And, once you go get the voltages compare the voltages of this iteration with respect to earlier iteration for all the three phases here and get the maximum deviation at 1 particular phase for that particular bus.

And, then calculate maximum error at all the buses. So, this will give you what is called as a maximum error for all the buses and then compare this maximum error with respect to your tolerance value, which may be 0.0001 for if you are using per unit system. This will be sufficient and then if you are comparing this if the error is lesser than this tolerance value, you can say your converged with algorithm print the result, otherwise again a iteration count and go to the step 3. So, you will keep you will be this loop till your algorithm converges.

(Refer Slide Time: 32:14)

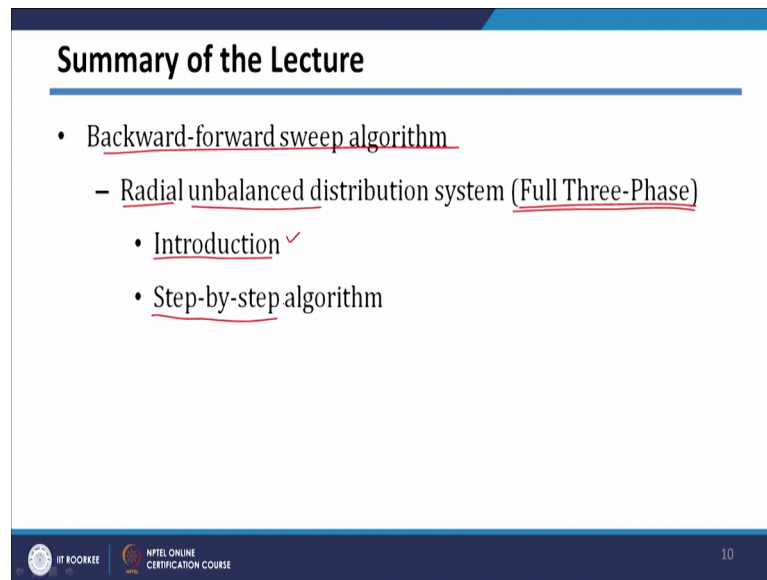A presentation slide titled "Summary of the Lecture" with a blue header and footer. The content is a bulleted list. The first bullet is "Backward-forward sweep algorithm". The second bullet is "Radial unbalanced distribution system (Full Three-Phase)", which is further indented and has two sub-bullets: "Introduction ✓" and "Step-by-step algorithm". The footer contains the IIT Roorkee logo, the text "IIT ROORKEE", "NPTEL ONLINE CERTIFICATION COURSE", and the page number "10".

Summary of the Lecture

- Backward-forward sweep algorithm
- Radial unbalanced distribution system (Full Three-Phase)
 - Introduction ✓
 - Step-by-step algorithm

IIT ROORKEE NPTEL ONLINE CERTIFICATION COURSE 10

So, in this particular lecture we have seen backward forward sweep algorithm applied for radial system, but unbalanced system. So, we have seen that whenever unbalanced system is there we have to consider all the three phases. So, we have seen how to use this backward sweep forward sweep algorithm for full three phase system, where all the three phases are considered. Here, I have introduced you concept where we have seen what are the impedance matrices for different sections of the line; and, how they are defined and after defining your impedance matrices we have seen step by step algorithm for 3 phase, backward forward sweep algorithm.

Next time we will see another algorithm, which is based on direct approach in that case we will see how this process of backwards forward sweep is simplified and effectively used.

Thank you very much.